

EEE205 – Digital Electronics (II)

Lecture 7

Xiaoyang Chen, Jiangmin Gu, Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

In This Session

Sequential Circuits in AHDL


- The Latches and Flip-Flops
- Counters
- Shift Registers

Register Primitives

- Several types of register primitives are available in AHDL.
- Registers that use these primitives are declared in the VARIABLE section.

Primitive	Description
LATCH	Data (D) Latch
DFF/DFFE	Data (D) Flip-Flop
JKFF/JKFFE	JK Flip-Flop
SRFF/SRFFE	Set/Reset (SR) Flip-Flop
TFF/TFFE	Toggle (T) Flip-Flop

The D Latch

 

Inputs		Output
EN	D	Q
0	X	Q_0 (no change)
1	0	0
1	1	1

- Primitive: **LATCH**
- Inputs
 - Data Input (**d**)
 - Enable (**ena**)
- Outputs
 - Data Output (**q**)

The D Latch

- `dlatch` is an instance of `LATCH`.
- `enable`, `din` and `q` are the ports of the circuit block `dlatch_ahdl`.

```
SUBDESIGN dlatch_ahdl
(
    enable, din           :INPUT;
    q                     :OUTPUT;
)
VARIABLE
    dlatch                :LATCH;
BEGIN
    dlatch.ena = enable;
    dlatch.d = din;
    q = dlatch.q;
END;
```

The D Latch

- If the instance name `q` is the same as the name of the circuit block output, it means the output of the latch is connected to the output port.


```
SUBDESIGN dlatch_ahdl
(
    enable, din           :INPUT;
    q                     :OUTPUT;
)
VARIABLE
    q                    :LATCH;
BEGIN
    q.ena = enable;
    q.d = din;
END;
```

The D Flip Flop

- Primitive: **DFF** or **DFFE**
- Inputs
 - Data Input (**d**)
 - Clock (**clk**)
 - Asynchronous Clear (**clrn**) and Preset (**prn**), both active-LOW.
 - Enable (**ena**), **DFFE** only
- Outputs
 - Data Output (**q**)

The J-K Flip Flop

 - Primitive: **JKFF** or **JKFFE**
- Inputs
 - Set (**j**) and Reset (**k**)
 - Clock (**clk**)
 - Asynchronous Clear (**clrn**) and Preset (**prn**), both active-LOW.
 - Enable (**ena**), **JKFFE** only
- Outputs
 - Data Output (**q**)



The S-R Flip Flop

- Primitive: **SRFF** or **SRFFE**
- Inputs
 - Set (**s**) and Reset (**r**)
 - Clock (**clk**)
 - Asynchronous Clear (**clrn**) and Preset (**prn**), both active-LOW.
 - Enable (**ena**), **SRFFE** only
- Outputs
 - Data Output (**q**)

The T Flip Flop


- Primitive: **TFF** or **TFFE**
- Inputs
 - Toggle (**t**)
 - Clock (**clk**)
 - Asynchronous Clear (**clrn**) and Preset (**prn**), both active-LOW.
 - Enable (**ena**), **TFFE** only
- Outputs
 - Data Output (**q**)

An Example

```
1  %      JK flip-flop circuit      %
2  SUBDESIGN fig5_65
3  (
4      jin, kin, clkin, preset, clear    :INPUT;
5      qout                               :OUTPUT;
6  )
7  VARIABLE
8  ff1      :JKFF;      -- define this flip-flop as a JKFF type
9  BEGIN
10      ff1.prn = preset; -- these are optional and default to vcc
11      ff1.clrn = clear;
12      ff1.j = jin;      -- connect primitive to the input signal
13      ff1.k = kin;
14      ff1.clk = clkin;
15      qout = ff1.q;      -- connect the output pin to the primitive
16  END;
```

Asynchronous Counters

MOD-8 Counter

 


- The name of this register is q, like the name of the output port.
- So the output of each flip-flop is connected to the output port.

Asynchronous Counters

```
1  % MOD 8 ripple up counter. %
2  SUBDESIGN fig5_71
3  (
4      clock                :INPUT;
5      q[2..0]              :OUTPUT;
6  )
7  VARIABLE
8      q[2..0] :JKFF;        -- defines three JK FFs
9  BEGIN
10                                     -- note: prn, clrn default to vcc!
11      q[2..0].j = VCC;        -- toggle mode J=K=1 for all FFs
12      q[2..0].k = VCC;
13      q[0].clk = !clock;
14      q[1].clk = !q[0].q;
15      q[2].clk = !q[1].q;    -- connect clocks in ripple form
16  END;
```

Synchronous Counters

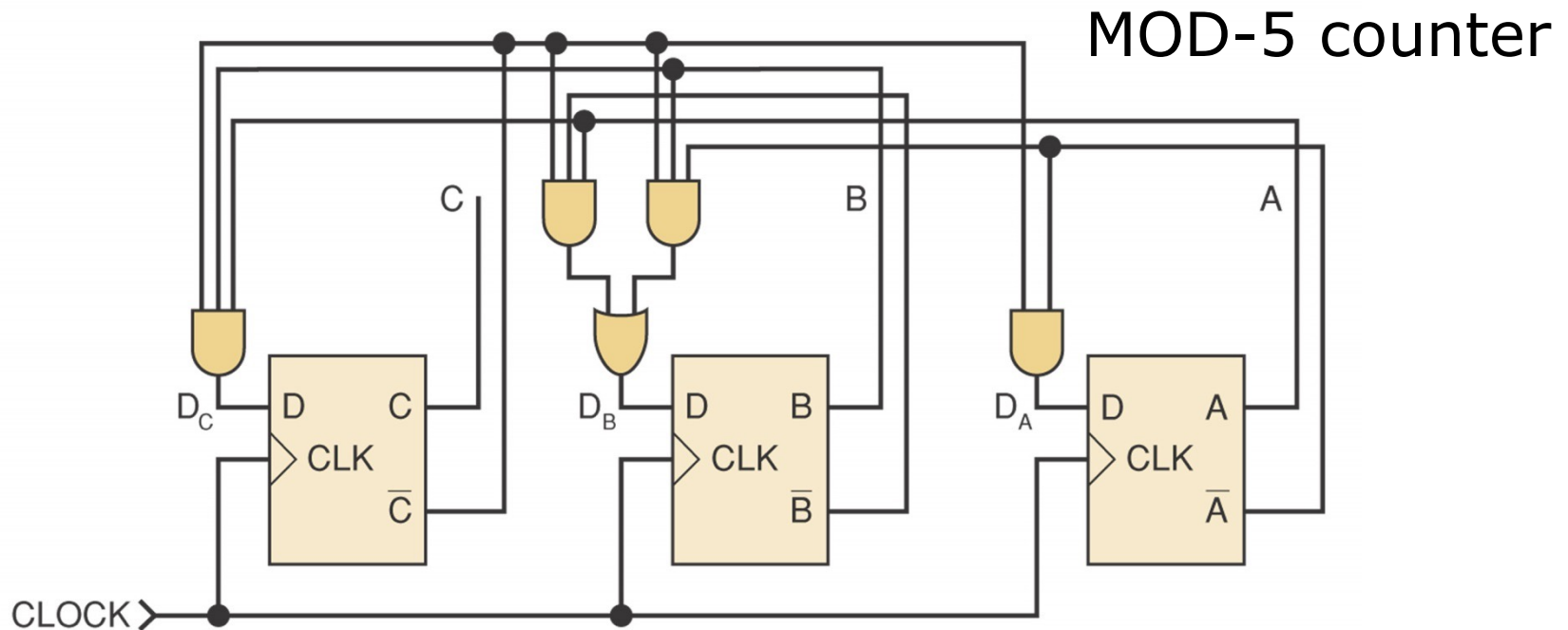- When using AHDL to implement a synchronous counter, we are no longer focusing on *wiring issues* but rather on describing the *circuit operation* concisely.



Synchronous Counters

State Description – An MOD-5 Counter

```
1  SUBDESIGN fig7_35
2  (
3      clock      :INPUT;
4      q[2..0]    :OUTPUT;
5  )
6  VARIABLE
7      count[2..0] :DFF;      --create a 3-bit register
8  BEGIN
9      count[].clk = clock;    --connect all clocks in parallel
10
11      CASE count[] IS
12  --          Present          Next
13  -----
14          WHEN 0    =>    count[].d = 1;
15          WHEN 1    =>    count[].d = 2;
16          WHEN 2    =>    count[].d = 3;
17          WHEN 3    =>    count[].d = 4;
18          WHEN 4    =>    count[].d = 0;
19          WHEN OTHERS =>    count[].d = 0;
20      END CASE;
21      q[] = count[];          -- assign register to output pins
22  END;
```

Synchronous Counters

Behavioral Description – An MOD-5 Counter

```
1  SUBDESIGN fig7_39
2  (
3      clock      :INPUT;
4      q[2..0]    :OUTPUT; -- declare 3-bit array of output bits
5  )
6  VARIABLE
7      count[2..0] :DFF; -- declare a register of D flip flops.
8
9  BEGIN
10     count[].clk = clock; -- connect all clocks to synchronous source
11     IF count[].q < 4 THEN -- note; count[] is the same as count[].q
12         count[].d = count[].q + 1; -- increment current value by one
13     ELSE count[].d = 0;           -- recycle to zero: force unused states to 0
14     END IF;
15     q[] = count[];               -- transfer register contents to outputs
16 END;
```

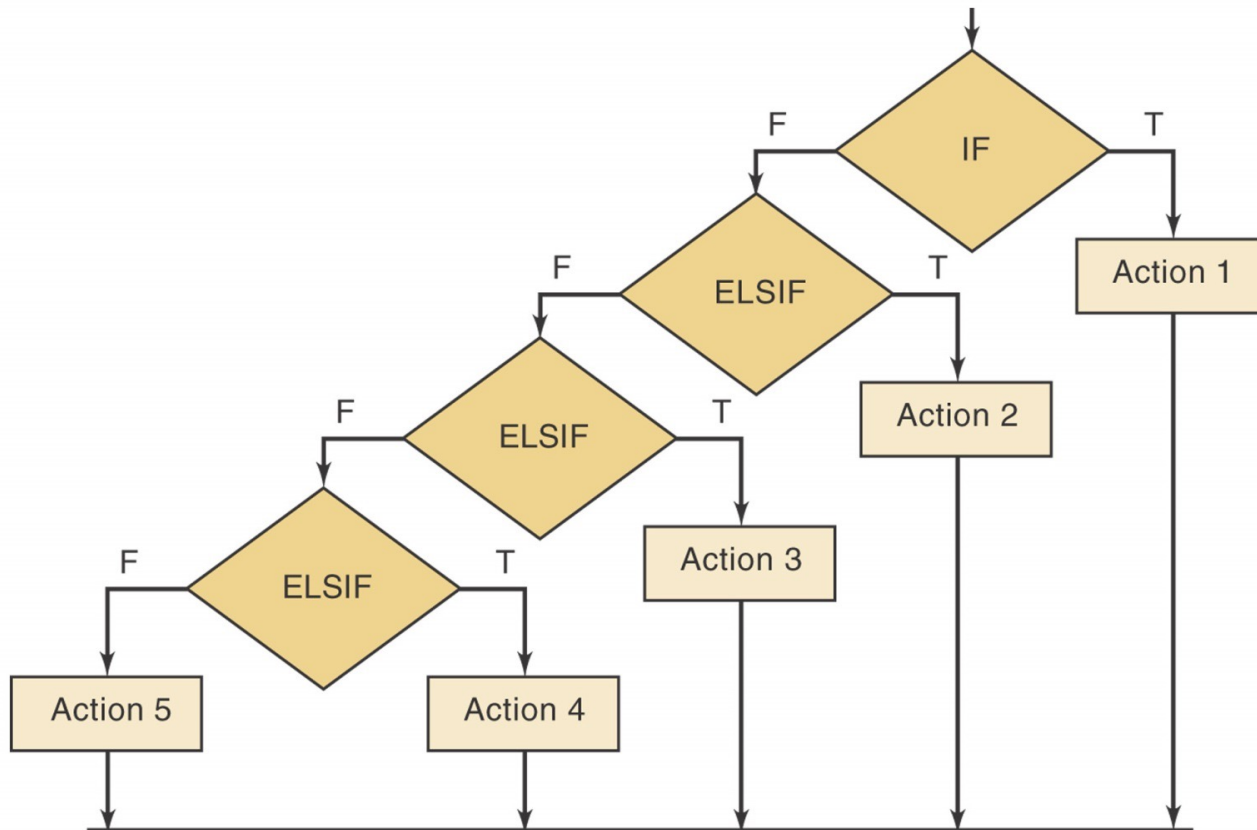

Synchronous Counters

Behavioral Description – A Full Feature Counter


```
1  SUBDESIGN fig7_42
2  (
3      clock, clear, load, cntenabl, down, din[3..0]      :INPUT;
4      q[3..0], term_ct :OUTPUT;  -- declare 4-bit array of output bits
5  )
6  VARIABLE
7      count[3..0]      :DFF;          -- declare a register of D flip flops
8
9  BEGIN
10     count[].clk = clock;              -- connect all clocks to synch source
11     count[].clrn= !clear;             -- connect for asynch active HIGH clear
12     IF load THEN count[].d = din[]; -- synchronous load
13         ELSIF !cntenabl THEN count[].d = count[].q; -- hold count
14         ELSIF !down THEN count[].d = count[].q + 1; -- increment
15         ELSE count[].d = count[].q - 1;              -- decrement
16     END IF;
17     IF ((count[].q == 0) & down # (count[].q == 15) & !down)& cntenabl
18     THEN      term_ct = VCC;          -- synchronous cascade output signal
19     ELSE term_ct = GND;
20     END IF;
21     q[] = count[];                    -- transfer register contents to outputs
22 END;
```

Synchronous Counters

- The **IF/ELSIF** indicates the priority of functions.
- In this example, `load > cntenabl > down`



Shift Registers

 


(a) Parallel load


PRESENT



NEXT

 

(b) Shift right

 


(c) Shift left

PRESENT



NEXT

 

(d) Hold data

Shift Registers

Serial In/ Serial Out

```
1  SUBDESIGN  fig7_77
2  (
3      clk, shift, serial_in      :INPUT;
4      serial_out                 :OUTPUT;
5  )
6  VARIABLE
7      q[3..0]                   :DFF;
8  BEGIN
9      q[].clk = clk;
10     serial_out = q[0].q;        -- output last register bit
11     IF (shift == VCC) THEN
12         q[3..0].d = (serial_in, q[3..1].q); -- concatenates for shift
13     ELSE
14         q[3..0].d = (q[3..0].q); -- hold data
15     END IF;
16 END;
```

Shift Registers

Universal Shift Register

```
1  SUBDESIGN fig7_83
2  (
3      clock      :INPUT;
4      din[3..0]  :INPUT;  -- parallel data in
5      ser_in     :INPUT;  -- serial data in from Left or Right
6      mode [1..0] :INPUT;  -- MODE Select: 0=hold, 1=right, 2=left, 3=load
7      q[3..0]    :OUTPUT;
8  )
9  VARIABLE
10     ff[3..0] :DFF;      -- define register set
11 BEGIN
12     ff[].clk = clock;    -- synchronous clock
13     CASE mode[] IS
14         WHEN 0 => ff[].d    = ff[].q;          -- hold shift
15         WHEN 1 => ff[2..0].d = ff[3..1].q);    -- shift right
16                 ff[3].d    = ser_in;          -- new data from left
17         WHEN 2 => ff[3..1].d = ff[2..0].q;    -- shift left
18                 ff[0].d    = ser_in;          -- new data bit from right
19         WHEN 3 => ff[].d    = din[];          -- parallel load
20     END CASE;
21     q[] = ff[];          -- update outputs
22 END;
```

EEE205 – Digital Electronics (II)

Lecture 8

Xiaoyang Chen, Jiangmin Gu, Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU



In This Session

- A Revision of Karnaugh Maps
- The Terminology
- Five-Variable Karnaugh Maps

A Revision of Karnaugh Maps

Grouping the 1s

  
- The goal is to **maximize the size** of the groups (shorter product terms) and to **minimize the number** of groups (less product terms).
- A group may contain 1, 2, 4, 8, or 16 adjacent cells.
- Each 1 must be included in one or **more** groups.



A Revision of Karnaugh Maps

Determine the Minimum SOP

 1. When a variable appears in both complemented and uncomplemented form in a group, that variable is eliminated.
2. Variables that are the same for all cells of the group must appear — 1 for uncomplemented form and 0 for complemented form.



The Terminology

- A **minterm** is a product term that includes all the variables in a Boolean function.
- It corresponds a 1 cell in a K-map.
- Here 7 minterms in total.

		AB			
		00	01	11	10
CD	00	1		1	
	01			1	
	11	1	1	1	1
	10				

The Terminology

- A minterm is often referred to by the decimal number converted from its binary value.

ABC	Minterm	Number
000	$A'B'C'$	0
001	$A'B'C$	1
010	$A'BC'$	2
011	$A'BC$	3
100	$AB'C'$	4
101	$AB'C$	5
110	ABC'	6
111	ABC	7

$$m_1 = A'B'C$$

$$m_6 = ABC'$$

The Terminology

- Minterms are often used to express a specific Boolean function or a truth table in a compact way.

ABC	f
000	0
001	1
010	1
011	1
100	1
101	1
110	0
111	0

$$f(A, B, C) = A' B' C + A' B C' + A' B C + A B' C' + A B' C$$

$$f(A, B, C) = m_1 + m_2 + m_3 + m_4 + m_5 = \Sigma m(1, 2, 3, 4, 5)$$

The Terminology

- If the function includes **don't cares**, those terms are included in a separate sum.

abc	g
000	X
001	1
010	1
011	X
100	0
101	1
110	0
111	0

$$g(a,b,c) = \Sigma m(1,2,5) + \Sigma d(0,3)$$

The Terminology

- An **implicant** is a product form that can be used in the sum-of-products expression for a function.
- An implicant corresponds to a rectangle of 1, 2, 4, 8, ... (any power of 2) 1's in a K-map.
- Here 14 implicants: seven 1's, six groups of 2 and one group of 4.

		A B			
		00	01	11	10
C D	00	1		1	
	01			1	
	11	1	1	1	1
	10				

The Terminology

- A **prime implicant** is an implicant which can not be merged with another implicant to remove a variable.
- It corresponds to a 1's group which is not fully contained in another group.
- Here 4 prime implicants:
 $A'B'C'D'$, ABC' , ABD and CD .

$\begin{array}{c} C D \\ \hline A B \end{array}$		$A B$			
		00	01	11	10
00	1			1	
01				1	
11	1	1	1	1	
10					

The Terminology

- An **essential prime implicant** is a prime implicant that includes at least one 1 that is not included in any other prime implicant.
- Essential prime implicants must appear in a fully minimized SOP expression.
- Here 3 essential prime implicants: $A'B'C'D'$, ABC' and CD .

		A B			
		00	01	11	10
C D	00	1		1	
	01			1	
	11	1	1	1	1
	10				

Karnaugh Maps

Find prime implicants

$$f(a, b, c, d) =$$



$$\Sigma m(0, 1, 2, 5, 6, 7, 8, 9, 10, 14)$$

ab \ cd	00	01	11	10
00	1	1		1
01		1	1	1
11				1
10	1	1		1

ab \ cd	00	01	11	10
00	1	1		1
01		1	1	1
11				1*
10	1	1*		1


Karnaugh Maps

Find essential prime implicants

  

Five-Variable Karnaugh Maps

 - Boolean functions with five variables can be simplified using **two** 4-variable maps.
- Squares directly above or below each other are adjacent.



Five-Variable Karnaugh Maps

Example 2:

Alternative
Solution !

		0			
		BC	00	01	11
DE	00	1	1	1	1
	01		1	1	
	11			1	
	10	1			1

A		1			
		BC			
D	E	00	01	11	10
	00				
	01		1	1	
	11			1	
	10	1		1	

		0			
		BC	00	01	11
DE	00	1	1	1	1
	01		1	1	
	11			1	
	10	1			1

		1			
		BC	00	01	11
DE	00				
	01		1	1	
	11			1	
	10	1		1	

$$\begin{aligned}
 F &= \bar{A}\bar{C}\bar{E} + ABCD + C\bar{D}\bar{E} \\
 &\quad + BCE + \bar{B}\bar{C}\bar{D}\bar{E} + \bar{A}C\bar{D} \\
 F &= \bar{A}\bar{C}\bar{E} + ABCD + C\bar{D}\bar{E} \\
 &\quad + BCE + \bar{B}\bar{C}\bar{D}\bar{E} + \bar{A}\bar{D}\bar{E}
 \end{aligned}$$