

Lecture 10a
of
EEE201

CMOS Digital Integrated Circuits

Department of Electrical & Electronic Engineering
Xi'an Jiaotong-Liverpool University (XJTLU)

Monday, 11th November 2024

□ Logic Inverter VTC

- ideal logic inverter
- voltage transfer characteristics
- with a resistive load
- graphical method





Xi'an Jiaotong-Liverpool University
西交利物浦大學

Input-Output Voltage Relation

(ideal logic inverter)

  - ❑ In *ideal* digital circuits, the logic states “0” and “1” are represented by only two fixed voltages (e.g. 0 V and V_{DD}).
- In such *ideal* situation, the **input-output voltage relationship** is simple (e.g. in a logic inverter):



V_{in}	V_{out}
0 V	V_{DD}
V_{DD}	0 V

If $V_{DD} = 5V$, $V_{in} = 2V$, then

V_{in} is: “0”

V_{out} is: “1”

nMOSFET: V_{Tn}

pMOSFET: V_{Tp}

inverter: V_{th}




Xi'an Jiaotong-Liverpool University

西交利物浦大学

Input-Output Voltage Relation

(real logic inverter)

 - ❑ In ***real*** digital circuits, there is a **continuous** range of voltages for the logic states “0” and “1”. And MOS transistors are not ideal switches.



- The **input-output voltage relationship** will fall short of the ideal.
- representative case of the logic inverter: **voltage transfer characteristics**




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Voltage Transfer Characteristics

(key voltage quantities)

❑ To specify clearly the **voltage transfer characteristics (VTC)**, several key voltage quantities need to be defined:

 - V_{OH} : max **output voltage** when output is logic “1”
- V_{OL} : min **output voltage** when output is logic “0”
- V_{IL} : max **input voltage** which can be interpreted as “0”
- V_{IH} : min **input voltage** which can be interpreted as “1”




- The definitions apply to not only the logic inverter but also other logic gates.
- Note the **threshold voltage V_{th}** of the logic inverter in the transition region of the VTC.

Noise Margins in Logic Voltages

(for logic “0” & “1”)



**noise margin for
“low” signals (i.e. “0”)**

$$NM_L = V_{IL} - V_{OL}$$

 

**noise margin for
“high” signals (i.e. “1”)**

$$NM_H = V_{OH} - V_{IH}$$

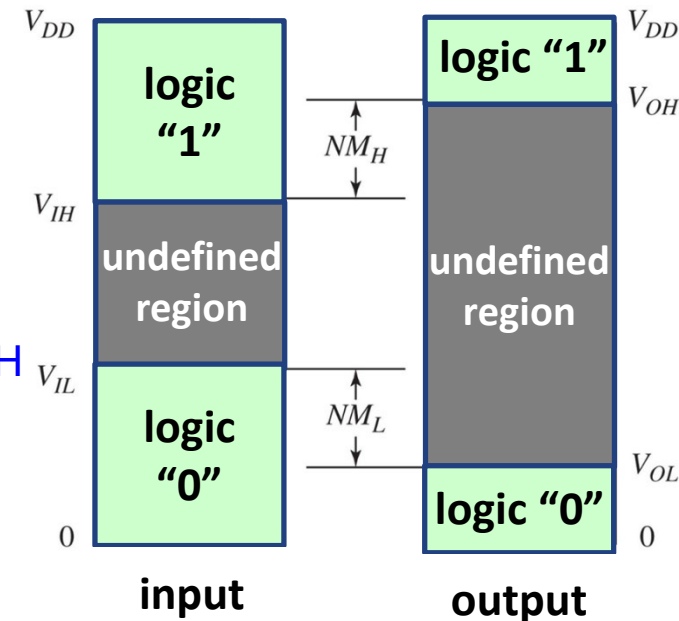 

The noise margins (and the key voltages) are part of the **design consideration**.




Xi'an Jiaotong-Liverpool University
西交利物浦大學

VTC of Logic Inverter

(nMOSFET with a resistor load)

 - ❑ To determine the VTC of the logic inverter, we will use the simple implementation of an nMOSFET with a resistor load to illustrate the techniques:
 - graphical method & solving simultaneous equations
 - In the CMOS logic inverter, the circuit analysis is more complicated.



- One key step is to understand the three major operation modes of the MOSFET: cut-off, triode (linear), and saturation.

- The resistor load has only one “mode”: one equation to define the voltage and current.

(What is that “mode”?)



Xi'an Jiaotong-Liverpool University
西交利物浦大学

VTC of Logic Inverter

(graphical method)

- Resistor's I-V curves & nMOSFET's
 - intersection points of the VTC

