



EEE109: The Field-Effect Transistor

Chapter 3

Dr. Guanying Chu
guanying.chu02@xjtlu.edu.cn
Office:SC427
PPT:Guanying Chu

Table of Content



- Study and understand the structure of MOS.
- Study and understand the structure and operation of the various types of **MOSFETs**.
 - N-channel MOSFET
 - P-channel MOSFET
- Understand the **DC** analysis and design techniques of MOSFET circuits.
 - Put the MOSFET into a specific DC circuit and calculate the electrical parameter

MOS FIELD-EFFECT TRANSISTOR

Understand the operation and characteristics of the various types of **metal-oxide** semiconductor field-effect transistors (MOSFETs).

MOSFET





- **M**etal-**O**xide-**S**emiconductor **F**ield-**E**ffect-**T**ransistor (MOSFET, 金属氧化物半导体场效应晶体管)
- Compare to another transistor (BJT in Chapter 4), MOSFET can be made very small. MOSFET is widely used in integrated circuit (IC).
- In the MOSFET, the current is controlled by an **electric field** applied perpendicular to both the semiconductor surface and to the direction of current. This phenomenon is called 「**Field-Effect**」.

MOSFET



Voltage controlled device (电压控制型器件)


4232BGM

  



Two-Terminals MOS Structure


 
- The heart of the **MOS**FET is the metal-oxide-semiconductor capacitor. It is a classic sandwich or hamburger structure.
- **Metal** could be aluminum or some other type of metal
- **Oxide** (氧化物) is a very good type of insulator
- **Semiconductor**, including P-type and N-type



Two-Terminals MOS (**P**-Type)



  
- E-field direction: point from bottom to the top
- Hole is moving toward the top interface, and electron is moving toward the bottom
- E-field direction: point from top to the bottom
- Hole is moving toward the bottom, and electron is moving toward the top interface
- An 「**Electron Inversion Layer**」 is created at the interface




Two-Terminals MOS (**N-Type**)



 - E-field direction: point from bottom to the top
- Hole is moving toward the top interface, and electron is moving toward the bottom
- An 「**Hole Inversion Layer**」 is created at the interface



 - E-field direction: point from top to the bottom
- Hole is moving toward the bottom, and electron is moving toward the top interface




Inversion Layer (反形层)




- What is inversion layer? Why do we have electron inversion layer at the interface in P-type MOS structure, not the hole inversion layer?
- **inversion layer**: is a layer in semiconductor material where the type of the majority carriers changes to its [opposite] under certain conditions.
- **For example**: In P-type semiconductor, the majority carriers are holes. However, an external voltage creates a region on surface where there are no holes but only electrons. In that region, minority electrons jump to the majority. The layer is called inversion layer.

P-MOS

 

Electron inversion layer

N-MOS

 

Hole inversion layer

N-channel MOSFET




- Now, we apply the concept of an inversion layer charge in a MOS capacitor to a transistor

- The **gate**, **oxide** and **p-type** substrate are the same as those of a MOS capacitor.

- However, we add two n-regions



 
- **Source** terminal
- **Drain** terminal



N-channel MOSFET



  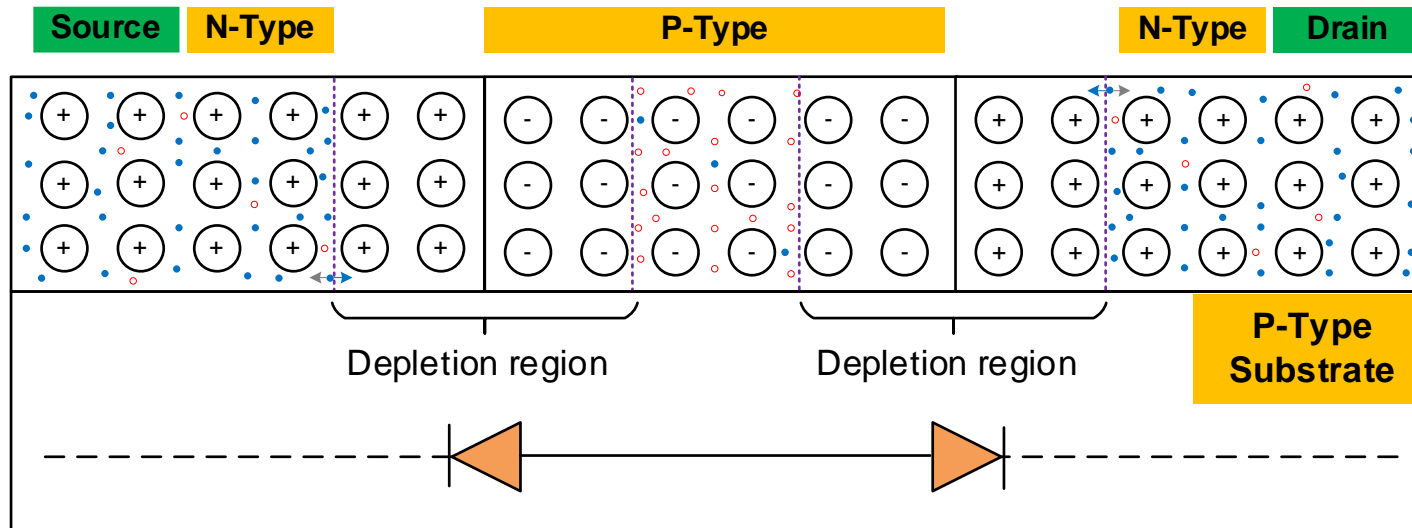
- Let simplify the structure of the NMOS to a 2D structure
- If there is no external voltage on this MOSFET, the source and drain terminal are separated by the p-region (substrate). The current in this case is **zero**



N-channel MOSFET





- If we add an external voltage on **Gate-to-Source**
- The **electron inversion layer** is created at the interface to connects the source and drain.
- **Definition:**
 - Since a external voltage must be applied to the gate to create the inversion layer, this transistor is called **enhancement-mode** MOSFET.
 - Since carrier in the inversion layer are electrons, it calls **n-channel MOSFET** (NMOS).

 

Characteristic curve of ideal NMOS



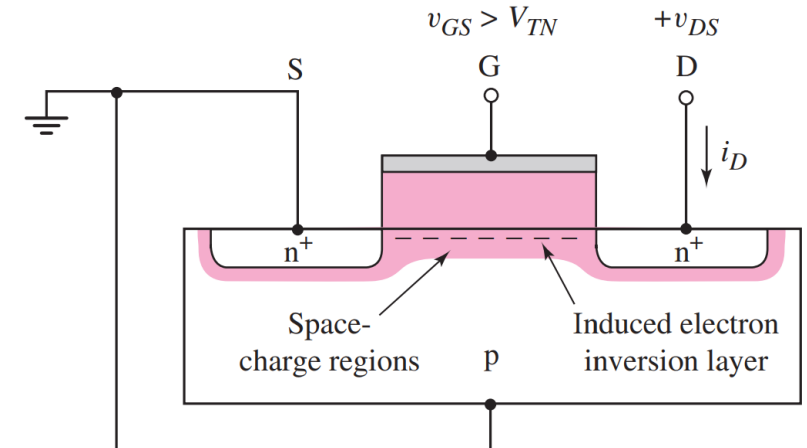 
- 「Threshold Voltage」 (阈值电压) V_{TN} is the voltage to “turn on” the transistor.
- For n-channel MOSFET, the threshold voltage is positive voltage is required to create the inversion layer.
 - When $V_{GS} < V_{TN}$, MOSFET turns OFF, drain current is zero
 - When $V_{GS} \geq V_{TN}$, MOSFET turns ON, current flows through the channel region



Characteristic curve of ideal NMOS



 - The magnitude of current is a function of [amount of charge in the inversion layer] + [Gate voltage]
- When $V_{GS} < V_{TN}$, MOSFET turns OFF, drain current is zero
- When $V_{GS1} > V_{TN}$
 - Channel inversion charge is formed
 - Drain current increases with V_{DS}



- With a larger gate voltage V_{GS2}
 - Larger inversion charge density
 - Drain current is greater for a given value of V_{DS}


I-V Characteristic curve-**N**onsaturation



1. At the beginning, applied V_{DS} is small, a relative constant thickness inversion layer

 2. If V_{DS} is **increasing**, with a bigger value

- The voltage drop across the oxide near the drain terminal decreases
- The induced inversion charge density decreases
- The incremental conductance is decreasing



I-V Characteristic curve-Saturation




3. If $V_{DS} = V_{GS} - V_{TN}$

- The inversion charge density at the drain terminal is zero (Similar to the case when $V_{GS} = V_{TN}$)
- The incremental conductance equal to zero

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN}$$

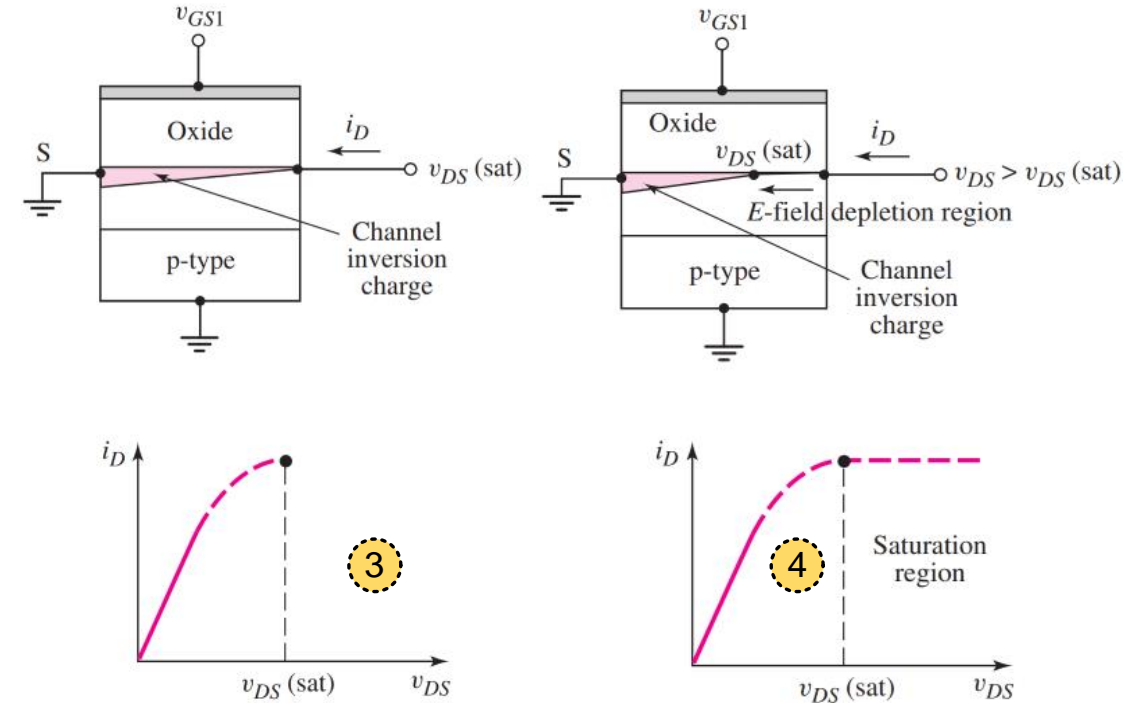4. If $V_{DS} > V_{DS}(\text{sat})$

- Drain current i_D is constant
- This MOSFET is in **[saturation region]**



I-V Characteristic curve-NMOS



- Nonsaturation region:

$$V_{DS} < V_{DS}(\text{sat})$$

$$i_D = K_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

- Saturation point:

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN}$$


- Saturation region: $V_{DS} \geq V_{DS}(\text{sat})$



$$i_D = K_n (V_{GS} - V_{TN})^2$$

K_n is the conduction parameter, constant



I_D is independent of V_{DS}

 

P-channel MOSFET (PMOS)



  - The substrate is **n-type** semiconductor. The source and drain areas are p-type semiconductor. Current is out of the drain terminal.
- The channel length, width, and oxide thickness parameter definitions of PMOS are the **same** as those for the NMOS.




P-channel MOSFET (PMOS)



- In PMOS, **holes** are the carrier
- A negative gate bias voltage is required to induce inversion layers. Therefore, the threshold voltage is negative $V_{TP} < 0$
- For generating of current flow, we should ensure $V_{GS} \leq V_{TP}$

$$|V_{SG}| \geq |V_{TP}|$$

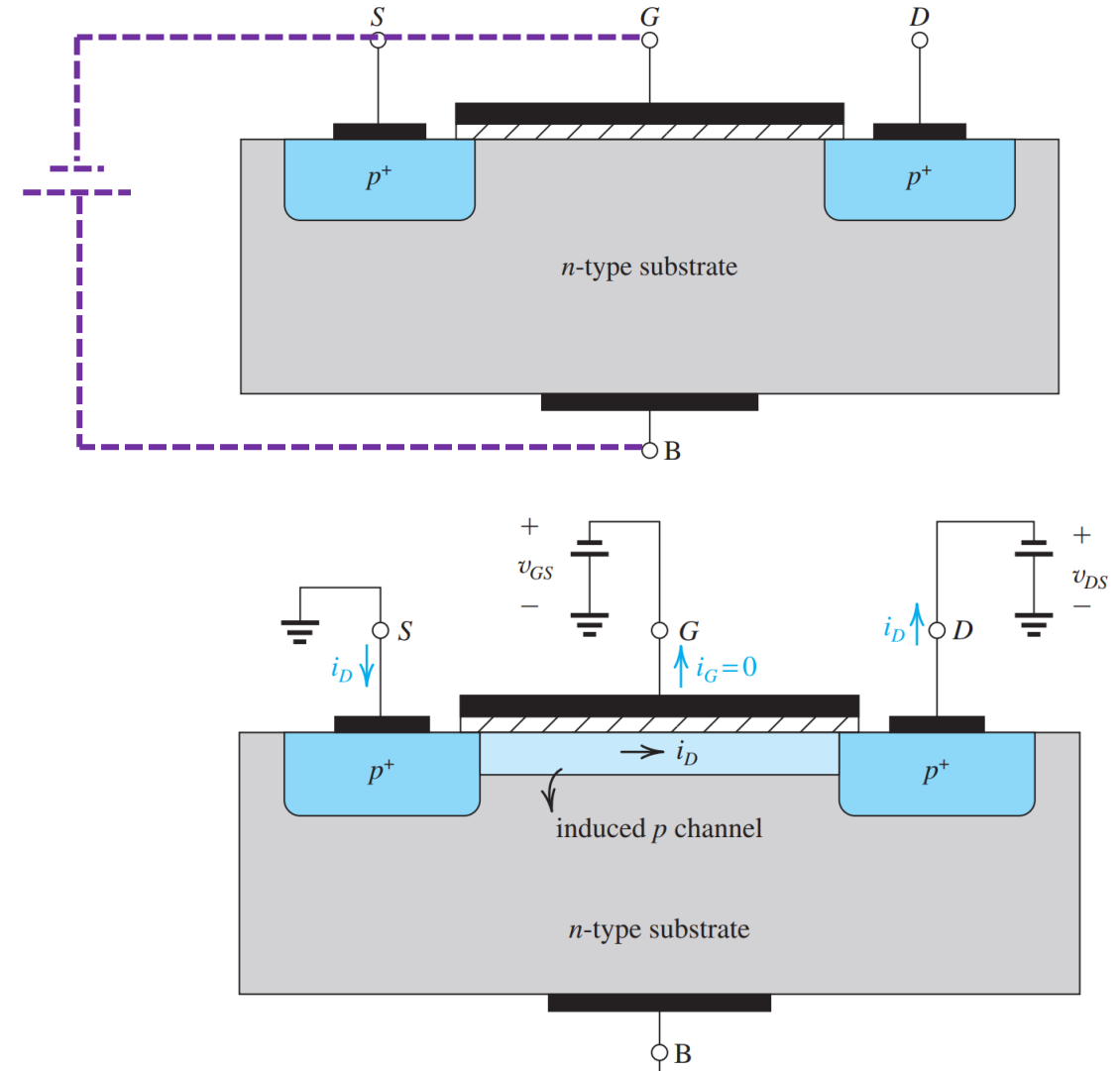

P-channel MOSFET (PMOS)



- V_{DS} is replaced by V_{SD} in PMOS

- Nonsaturation region:

$$i_D = K_n [2(V_{SG} + V_{TP})V_{SD} - V_{SD}^2]$$


- Saturation point:

$$V_{SD}(\text{sat}) = V_{SG} + V_{TP}$$

- Saturation region:





$$i_D = K_p(V_{SG} + V_{TP})^2$$

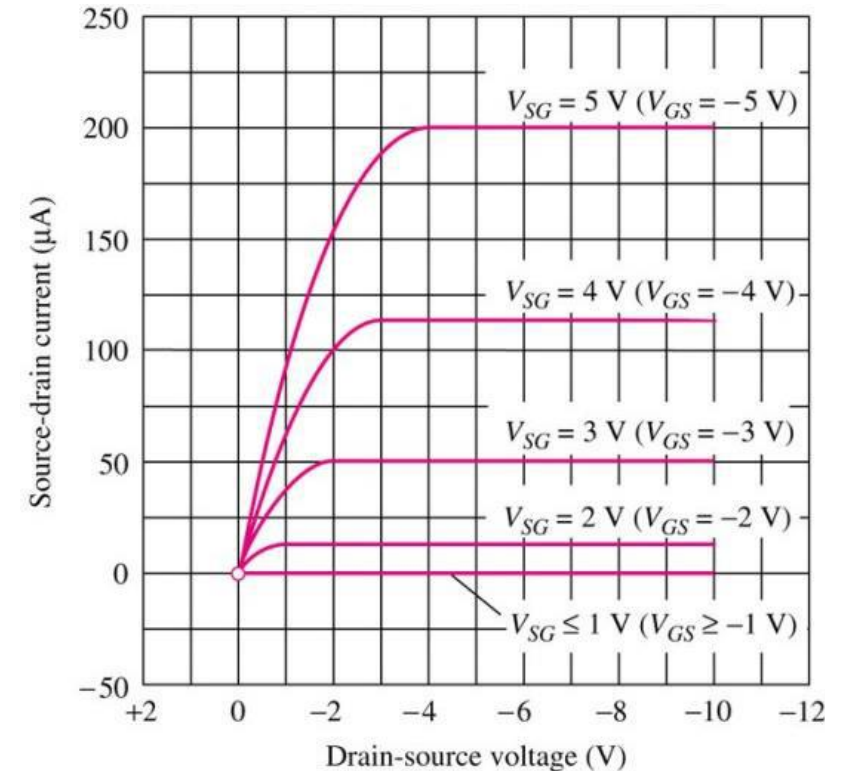



Circuit Symbol



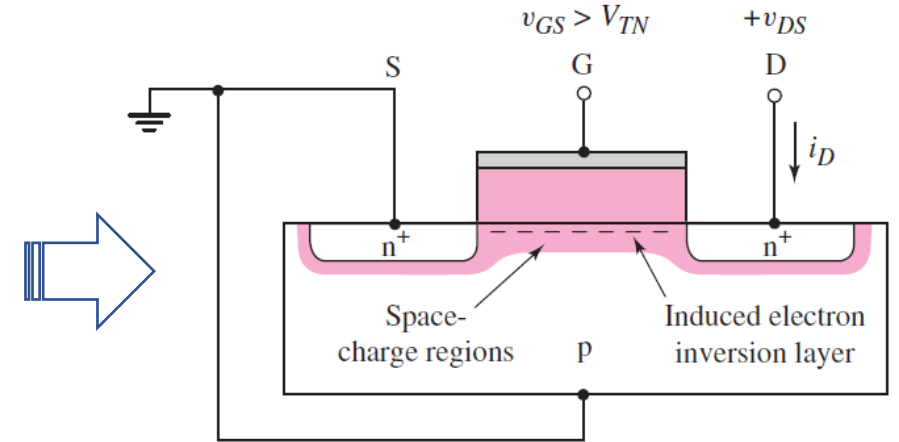 - For **N**MOS
- The “TOP” terminal is the Drain
- The “Bottom” terminal is the Source



  - For **P**MOS
- The “Top” terminal is the Source
- The “Bottom” terminal is the Drain




Summary of Transistor Operation



	NMOS	PMOS
Saturation	$v_{DS} \geq v_{DS}(sat)$ $i_D = k_n(v_{GS} - v_{TN})^2$	$v_{SD} \geq v_{SD}(sat)$ $i_D = k_n(v_{SG} + v_{TP})^2$
Nonsaturation	$v_{DS} < v_{DS}(sat)$ $i_D = k_n [2(v_{GS} - v_{TN})v_{DS} - v_{DS}^2]$	$v_{SD} < v_{SD}(sat)$ $i_D = k_n [2(v_{SG} + v_{TP})v_{SD} - v_{SD}^2]$
Transition point	$v_{DS}(sat) = v_{GS} - v_{TN}$	$v_{SD}(sat) = v_{SG} + v_{TP}$
Enhancement mode	$v_{TN} > 0$	$v_{TP} < 0$


Reinforce Your Learning (Exercise)

 

1. Consider an NMOS transistor having $V_{TN} = 2V$. What is the bias region if we have:

- (a) $V_{GS} = 10V$, $V_{DS} = 1$;
- (b) $V_{GS} = 5V$, $V_{DS} = 5V$;
- (c) $V_{GS} = 1V$, $V_{DS} = 10V$

 2. Consider an NMOS transistor having $V_{TN} = 2V$. In such a circuit (right figure). What is the bias region of the NMOS?




MOSFET DC CIRCUIT ANALYSIS

Understand and become familiar with the **DC** analysis and design techniques of MOSFET circuits.


MOSFET Common Source Circuit



 - Put a MOSFET into a **DC circuit** to analyze the Drain to Source voltage, drain current and power consumption.



NMOS DC CIRCUIT

 

PMOS DC CIRCUIT

- 「Cut-off region」
- 「Non-saturation region」
- 「Saturation region」

Problem-Solving **Tips**: DC Analysis



- To analyze MOSFET circuit with DC sources, we must follow these **Four steps (AACM)**:

1. **ASSUME** an operation model (saturation firstly)
2. **ANALYZE** the circuit with the assumed condition

$$i_D = K_n(V_{GS} - V_{TN})^2 \quad V_{DS} = V_{DD} - I_D R_D \quad V_{DS}(\text{sat}) = V_{GS} - V_{TN}$$

3. **CHECK** the results of the mode for matching with original assumption. If consistent, the analysis is complete; If inconsistent, go to step 4
4. **MODIFY** your original assumption and repeat all steps.



NMOS Common Source Circuit



- The gate current into the transistor is zero, don't forget the oxide (insulator) between metal and substrate

$$V_{GS} = V_G - V_S \quad V_S = 0 \rightarrow V_{GS} = V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

- Then we can calculate the saturation voltage


$$V_{DS}(\text{sat}) = V_{GS} - V_{TN}$$

- Assume $V_{DS} \geq V_{DS(\text{sat})}$ and the transistor bias in **saturation**

$$i_D = K_n (V_{GS} - V_{TN})^2 \quad \Rightarrow \quad V_{DS} = V_{DD} - I_D R_D$$

- Finally, we should verify our assumption
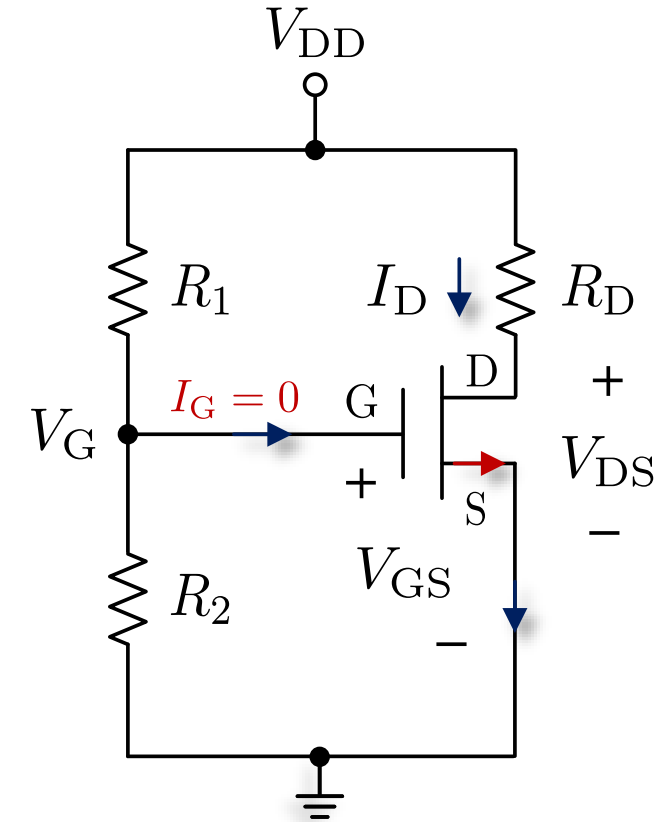
$$\Rightarrow V_{DS} \geq V_{DS}(\text{sat}) \text{ Yes?}$$



NMOS DC CIRCUIT

PMOS Common Source Circuit



- The gate current into the transistor is zero

$$V_{SG} = \frac{R_1}{R_1 + R_2} V_{DD}$$

- Then we can calculate the saturation voltage


$$V_{SD}(\text{sat}) = V_{SG} + V_{TP}$$

- Assume $V_{SD} \geq V_{SD(\text{sat})}$ and the transistor bias in **saturation**

$$i_D = K_n (V_{SG} + V_{TP})^2 \quad \Rightarrow \quad V_{SD} = V_{DD} - I_D R_D$$

- Finally, we should verify our assumption
 
$$\Rightarrow V_{SD} \geq V_{SD}(\text{sat}) \text{ Yes?}$$




PMOS DC CIRCUIT

Reinforce Your Learning (Exercise)



 - Calculate the **drain current** and **drain-to-source voltage** of a common-source circuit with an n-channel enhancement-mode MOSFET. Find the power dissipated in the transistor. Assume $R_1 = 30\text{k}\Omega$, $R_2 = 20\text{k}\Omega$, $R_D = 20\text{k}\Omega$, $V_{DD} = 5\text{V}$, $V_{TN} = 1\text{V}$ and $K_n = 0.1\text{mA/V}^2$
- **Solution**



NMOS DC CIRCUIT


BASIC MOSFET APPLICATION

Examine three applications of MOSFET circuits: a MOS Inverter, digital logic circuit, and an amplifier circuit.

Switch circuit-NMOS Inverter



- The transistor switch considered in this section is also called an MOS **inverter**. The working mode is that value of input signal control the output signal. But, the potentials are reversed.
- If the input signal is **Low-level**, and $V_I < V_{TN}$
 - Transistor is cutoff, and $I_D = 0$. No power is dissipated in the transistor
 - Output voltage $V_O = V_{DD}$, which is high-level
- If the input signal is **High-level**, and $V_I > V_{TN}$
 - Transistor is on, and whole circuit goes on.
 - Output voltage $V_O = V_{DD} - i_D R_D$, which is Low-level

 

V_I Low



V_O High

V_I High




V_O Low

Digital Logic Gate (NOR Gate)



 - Two NMOS Transistors are connected in parallel
- If $V_1 = V_2 = 0$ (M_1 and M_2 are cutoff. $V_o = V_{DD}$, high-level)
- If $V_1 = 5V$ $V_2 = 0V$ or $V_1 = 0V$ $V_2 = 5V$
 - M_1 is turn on, M_2 is cut off. Or, M_1 is cut off, M_2 is turn on
 - $V_o = V_{DD} - I_R R_D$ which is a low-level
- If $V_1 = V_2 = 5V$
 - M_1 and M_2 are turn on
 - V_o is at low-level



NMOS NOR logic circuit response		
$V_1(V)$	$V_2(V)$	$V_o(V)$
0	0	High
5	0	Low
0	5	Low
5	5	Low

MOSFET Amplifier



- An amplifier is an electrical device, used to enhance the **amplitude** of the input signal. It is an essential part of audio sources like a record player or CD player and also other devices
- At present, MOSFET amplifiers are a design choice in 99% of the microchips around the world.
- We will learn such circuit in **CHAPTER 5**.

