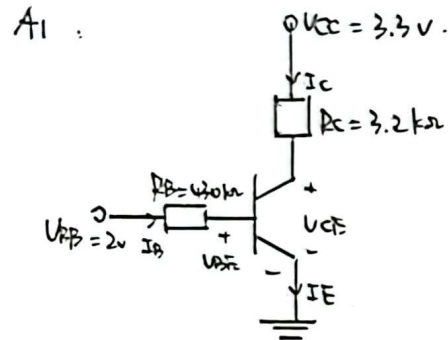


EEE 211 Assignment 1

Q1: $V_{BB} = 2V$, $V_{CC} = 3.3V$, $R_C = 3.2k\Omega$

$R_B = 430k\Omega$, $\beta = 150$, $V_{BE} = 0.7V$

Find base, collector and emitter currents.
and V_{CE}



Step 1: KVL around B-E loop.

$$\Rightarrow V_{BB} = I_B \cdot R_B + V_{BE}$$

Step 2: Assume transistor is biased in forward-active mode and $I_E = (1 + \beta) I_B$.

We can then write base current as

$$\Rightarrow I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{2 - 0.7}{430k} = 3.023 \mu A$$

Step 3: Collector Current, $I_C = \beta I_B = 150 \times 3.023 \mu A = 0.453 mA$


Step 4: Emitter Current, $I_E = (1 + \beta) I_B = 151 \times 3.023 \mu A = 0.457 mA$

Step 5: CE voltage, KVL around C-E loop

$$\Rightarrow V_{CE} = V_{CC} - I_C \cdot R_C = 3.3 - 0.453 mA \times 3.2k = 1.850V$$

Step 6: Verification: $V_{CE} = 1.850V > 0.7V$ verifies the forward-active mode assumption

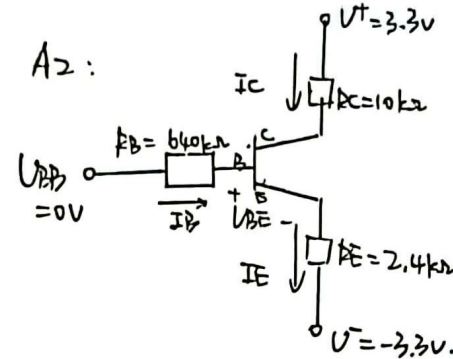Q2: Calculate the characteristics (I_C , V_{CE}) of a circuit including base and emitter currents, which consists of an emitter resistor. The circuit parameters are annotated in the figure and $\beta = 80$ and $V_{BE(on)} = 0.7V$



Step 1: KVL around B-E loop.

$$\Rightarrow V_{BB} = I_B \cdot R_B + V_{BE(on)} + I_E \cdot R_E + V^-$$

Step 2: Assume transistor is biased in forward-active mode and $I_E = (1 + \beta) I_B$.

We can then write base current as

$$\Rightarrow I_B = \frac{V_{BB} - V^- - V_{BE(on)}}{R_B + (1 + \beta) R_E} = \frac{0 - (-3.3) - 0.7}{640k + (1 + 80) \cdot 2.4k} = \frac{3.116}{640k + 192k} = 3.12 \mu A$$

Step 3: Collector Current, $I_C = \beta I_B = 80 \times 3.12 \mu A = 0.249 mA$

Step 4: Emitter Current, $I_E = (1 + \beta) I_B = (1 + 80) \times 3.12 \mu A = 0.252 mA$

Step 5: CE voltage, KVL around C-E loop

$$\Rightarrow V_{CE} = V^+ - I_C \cdot R_C - I_E \cdot R_E - V^- = 3.3 - 0.249 mA \cdot 10k - 0.252 mA \cdot 2.4k + 3$$

$$\Rightarrow V_{CE} = 3.505V$$

Step 6: Verification: $V_{CE} = 3.505V > 0.7V$ verifies the forward-active assumption


Q3: For the circuit shown in Fig. 3, assume $V_{CC} = 5V$, $V_{BE(on)} = 1.025V$,

$$R_B = 100k\Omega, R_C = 6k\Omega, \beta = 150, V_{BE(on)} = 0.7V, V_A = 150V$$

(a) Calculate the Q-point values (I_{CQ} , V_{CEQ}) using DC Analysis

(b) Determine the small signal hybrid- π parameters (r_{π} , g_m , r_o)

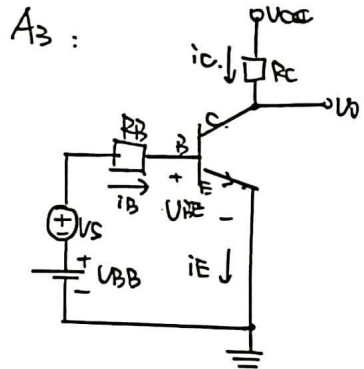(c) Find the small signal voltage gain $A_v = V_o/V_s$



A3:

$$(b) r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{150 \times 26m}{0.488m} = 8.0k\Omega$$


$$g_m = \frac{\beta I_{CQ}}{V_T} = \frac{150}{8.0k} = 18.77mA/V$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{150}{0.488m} = 307k\Omega$$

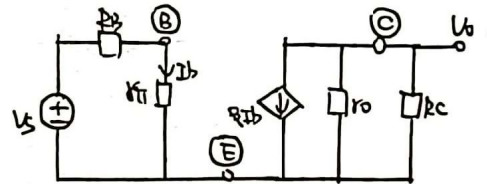(c) Step 1: For the AC Analysis.

We set DC sources to 0

Step 2: Draw the small-signal hybrid- π Equivalent Circuit.



$$\text{Step 3: } V_s = I_b(R_B + r_{\pi})$$

$$\text{Step 4: } V_o = -\beta I_b(r_o || R_C)$$

$$\begin{aligned} \text{Step 5: } A_v &= \frac{V_o}{V_s} = \frac{-\beta I_b(r_o || R_C)}{I_b(R_B + r_{\pi})} \\ &= (-\beta) \frac{r_o || R_C}{R_B + r_{\pi}} \\ &= (-150) \cdot \frac{307k || 6k}{100k + 8k} \\ &= -8.17 \end{aligned}$$

(a) Step 1: For the DC Analysis, we set $V_s = 0$.

Step 2: KVL around B-E loop.

$$V_{BE} = I_{BQ} \cdot R_B + V_{BE(on)} + 0$$

Step 3: Assume transistor is biased in forward-active mode and $I_{EQ} = (1+\beta)I_{BQ}$.

We can write base current (Q-point)

$$\text{as } I_{BQ} = \frac{V_{BE} - V_{BE(on)}}{R_B} = \frac{1.025 - 0.7}{100k} = 3.25\mu A$$

Step 4: Collector Current, $I_{CQ} = \beta I_{BQ}$

$$I_{CQ} = 150 \times 3.25\mu A = 0.488mA$$

Step 5: Emitter Current, $I_{EQ} = (1+\beta)I_{BQ}$

$$I_{EQ} = (150+1) \times 3.25\mu A = 0.491mA$$

Step 6: $V_{CEQ} = V_{CC} - I_{CQ} \cdot R_C - I_{EQ} \cdot R_E = 5 - 0.488mA \cdot 6k - 0.491mA \cdot 100k = 2.431V$

Q4: For the circuit shown in Fig. 4, $R_E = 0.6k\Omega$, $R_C = 5.6k\Omega$, $\beta = 120$, $V_{BE(on)} = 0.7V$.

$$R_1 = 250k\Omega, R_2 = 75k\Omega$$


(a) Calculate Q-point values (I_{CQ} , V_{CEQ}) using DC Analysis.

(b) Determine the small signal hybrid- π parameters (r_{π} , g_m , r_o)

(c) Find the small signal voltage gain $A_v = V_o/V_s$, assuming $V_A = \infty$

(d) Determine the Input resistance looking into the base of transistor

A4:

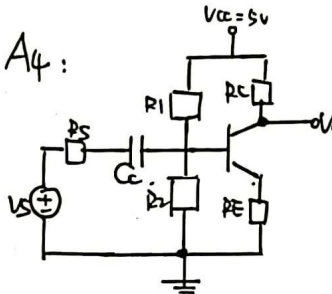

Step 1: KVL around BE loop

$$\Rightarrow V_{TH} = R_{TH} \cdot I_{BQ} + V_{BE(on)} + I_{EQ} \cdot R_E$$

Step 2: Assume transistor is biased in forward-active mode and

$$I_{EQ} = (1+\beta)I_{BQ}$$

We can write base current (Q-point)


$$\begin{aligned} \Rightarrow I_{BQ} &= \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1+\beta)R_E} \\ &= \frac{1.15 - 0.7}{58k + (1+120) \times 0.6} \\ &= 3.446\mu A \end{aligned}$$

(a) Step 1: For DC Analysis.

We set $V_s = 0$

Capacitor open circuit

Step 2: Draw the DC circuit.

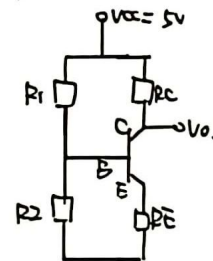


Step 6: Collector Current, $I_{CQ} = \beta I_{BQ}$

$$\Rightarrow I_{CQ} = 120 \times 3.446\mu A = 0.414mA$$

Step 7: Emitter Current, $I_{EQ} = (1+\beta)I_{BQ}$

$$\Rightarrow I_{EQ} = (120+1) \times 3.446\mu A = 0.417mA$$

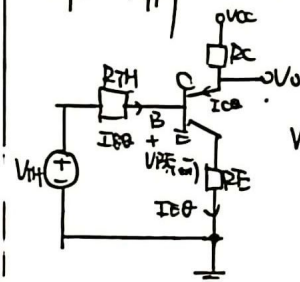Step 3: Apply Thevenin Equivalent Circuit.



Step 8: V_{CEQ} , KVL around CE loop

$$\Rightarrow V_{CEQ} = V_{CC} - I_{CQ} \cdot R_C - I_{EQ} \cdot R_E$$

$$\begin{aligned} V_{TH} &= \frac{R_2}{R_1 + R_2} V_{CC} \\ &= \frac{75k}{250k + 75k} \times 5 \\ &= 1.15V \end{aligned}$$

$$\begin{aligned} R_{TH} &= \frac{R_1 \times R_2}{R_1 + R_2} \\ &= \frac{250k \times 75k}{250k + 75k} = 58k\Omega \end{aligned}$$

$$\begin{aligned} &= 5 - 0.414mA \cdot 5.6k - 0.417mA \cdot 0.6k \\ &= 2.431V \end{aligned}$$

(b) Step 1: parameters for AC

$$r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{120 \times 26m}{0.414m} = 7.5k\Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{120}{7.5k} = 15.92mA/V$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{\infty}{0.414m} = \infty$$


which means we can neglect Early Effect

(c) Step 1: For the AC Analysis

We set DC sources to 0

Step 2: Draw the small-signal hybrid- π Equivalent Circuit

(Capacitor is seen as short circuit)

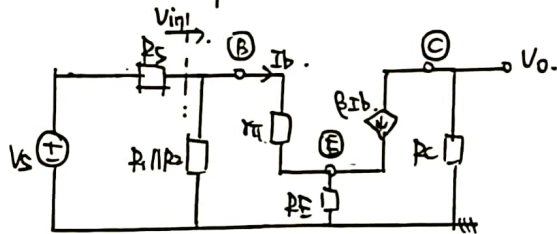

Step 3: $V_s = V_{in} \cdot \frac{(R_{\pi} \parallel R_E) + R_s}{R_{\pi} \parallel R_E}$

$V_{in} = I_B \cdot [r_{\pi} + (1+\beta)R_E]$

Step 4: $V_o = -\beta I_B \cdot R_C$

Step 5: $A_v = \frac{V_o}{V_s} = \frac{-\beta I_B \cdot R_C}{I_B [r_{\pi} + (1+\beta)R_E]} \cdot \frac{(R_{\pi} \parallel R_E) + R_s}{(R_{\pi} \parallel R_E) + R_s}$

$$= \frac{-120 \times 5.6k}{7.5k + (1+120) \times 0.6k} \cdot \frac{\frac{250k \times 7.5k}{250k + 7.5k} + 0.5k}{\frac{250k \times 7.5k}{250k + 7.5k} + 0.5k}$$

$$= -8.318$$


(d) Step 1: $R_{in} = \frac{V_{in}}{I_{in}}$

$$= \frac{I_B [r_{\pi} + (1+\beta)R_E]}{I_B}$$

$$= r_{\pi} + (1+\beta)R_E$$

$$= 7.5k + (1+120) \times 0.6k$$

$$= 80.1k\Omega$$

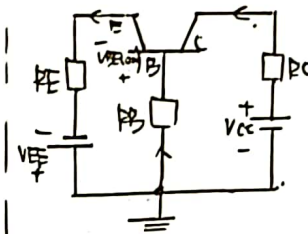

Step 3: KVL around B-E loop.

$$\Rightarrow V_{EE} = I_{BQ} R_B + V_{BE(on)} + I_{EQ} R_E$$

Step 4: Assume transistor is biased in forward-active mode and

$$I_{EQ} = (1+\beta) \cdot I_{BQ}$$

We can write Base current (Q-point)

$$\Rightarrow I_{BQ} = \frac{V_{EE} - V_{BE(on)}}{R_B + (1+\beta)R_E}$$

$$= \frac{3.3 - 0.7}{100k + (1+120) \times 12k}$$

$$= 1.675 \mu A$$

Q5: For the circuit shown as Fig. 5, $V_{CC} = V_{EE} = 3.3V$

$$R_S = 500k\Omega, R_C = 6k\Omega, R_B = 100k\Omega, R_E = 12k\Omega$$

$$R_C = 12k\Omega, \beta = 120, V_{BE(on)} = 0.7V, V_A = \infty$$

(a) Calculate Q-point values: I_{CQ}, V_{CEQ}

(b) Determine small signal hybrid- π parameters (r_{π}, g_m, r_o)

(c) Find $A_v = V_o/V_s$

(d) Find the small signal current gain $A_i = i_o/i_i$

(e) Determine the input resistance R_i and output resistance R_o

Step 5: Collector Current, $I_{CQ} = \beta I_{BQ}$

$$\Rightarrow I_{CQ} = 120 \times 1.675 \mu A = 0.201 mA$$

Step 6: Emitter Current, $I_{EQ} = (1+\beta) I_{BQ}$

$$\Rightarrow I_{EQ} = (1+120) \times 1.675 \mu A = 0.203 mA$$

Step 7: V_{CEQ} , KVL around C-E loop


$$\Rightarrow V_{CC} = V_{CEQ} + I_{EQ} R_E - V_{EE}$$

$$\Rightarrow V_{CEQ} = V_{CC} + V_{EE} - I_{EQ} R_E$$

$$= 3.3 + 3.3 - 0.203m \times 12k$$

$$= 4.164 V$$

As:

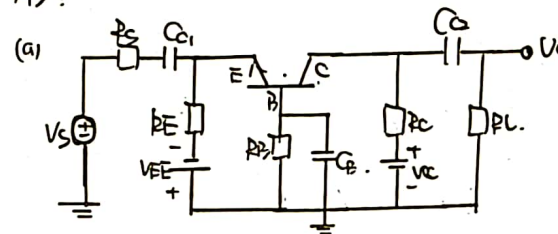

Step 1: For DC Analysis

We set $V_s = 0$

Capacitors, open circuit.

Step 2: Draw the DC Circuit.

$$(b) r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{120 \times 26m}{0.201m} = 15.52k$$


$$g_m = \frac{\beta}{r_{\pi}} = \frac{120}{15.52k} = 7.731 mA/V$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{\infty}{0.201m} = \infty$$

which means that we can neglect Early Effect

(c) Step 1: For the AC Analysis,
we set DC sources to 0

Step 2: Draw the Small-Signal

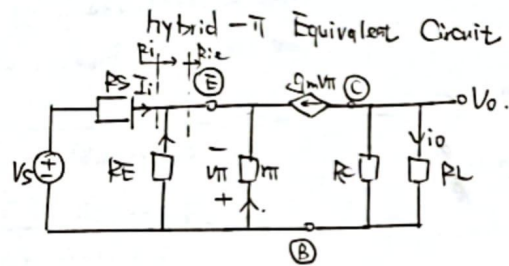

Step 3: KCL at Emitter Node,

$$\Rightarrow g_m v_{\pi} + \frac{v_{\pi}}{r_{\pi}} + \frac{v_{\pi}}{R_E} + \frac{v_s - (-v_{\pi})}{R_S} = 0$$

$$\Rightarrow v_{\pi} = \frac{-v_s}{R_S} \cdot \frac{1}{g_m + \frac{1}{r_{\pi}} + \frac{1}{R_E} + \frac{1}{R_S}}$$

$$g_m = \frac{\beta}{r_{\pi}}$$

$$\Rightarrow v_{\pi} = \frac{-v_s}{R_S} \left(\frac{r_{\pi}}{1+\beta} \parallel R_E \parallel R_S \right)$$

Step 4: $v_o = -g_m v_{\pi} \cdot (R_C \parallel R_L)$

Step 5: $A_v = \frac{v_o}{v_s} = (g_m) (R_C \parallel R_L) \cdot \frac{-v_s \cdot \left(\frac{r_{\pi}}{1+\beta} \parallel R_E \parallel R_S \right)}{v_s}$

$$\Rightarrow A_v = g_m \cdot \frac{R_C \parallel R_L}{R_S} \cdot \left[\frac{r_{\pi}}{1+\beta} \parallel R_E \parallel R_S \right]$$

$$\Rightarrow A_v = 7.731m \cdot \frac{12k \parallel 6k}{500k} \times \frac{1}{\frac{15.52}{1+120} + \frac{1}{12k} + \frac{1}{500k}}$$

$$\Rightarrow A_v = 7.847$$

(d) Step 1: KCL at Emitter Node.

$$\Rightarrow g_m v_{\pi} + \frac{v_{\pi}}{r_{\pi}} + \frac{v_{\pi}}{R_E} + i_i = 0$$

$$\Rightarrow i_i = -v_{\pi} \left(\frac{1+\beta}{r_{\pi}} + \frac{1}{R_E} \right)$$

$$\Rightarrow i_i = -v_{\pi} \cdot \left(\frac{r_{\pi}}{1+\beta} \parallel R_E \right)^{-1}$$

Step 2: Ohm's Law at Collector Node

$$\Rightarrow i_o = -g_m v_{\pi} \cdot \frac{R_C}{R_C + R_L}$$

Step 3: $A_i = \frac{i_o}{i_i}$

$$\Rightarrow A_i = \frac{i_o}{i_i}$$

$$= \frac{(-g_m) v_{\pi} \cdot \frac{R_C}{R_C + R_L}}{(-1) \cdot v_{\pi} \cdot \left(\frac{r_{\pi}}{1+\beta} \parallel R_E \right)^{-1}}$$

$$= g_m \cdot \frac{R_C}{R_C + R_L} \cdot \left[\frac{r_{\pi}}{1+\beta} \parallel R_E \right]$$

$$= 7.731m \cdot \frac{12k}{12k + 6k} \cdot \frac{\frac{15.52k}{1+120} \times 12k}{\frac{15.52k}{1+120} + 12k}$$

$$= 0.654$$

(e) Step 1: R_{ie} : Input Resistance

$$R_{ie} = R_E \parallel R_{ie}$$

$$R_{ie} = \frac{-v_{\pi}}{-(g_m v_{\pi} + \frac{v_{\pi}}{r_{\pi}})}$$

$$= \frac{1}{g_m + \frac{1}{r_{\pi}}}$$

$$= \frac{1}{7.731m + \frac{1}{15.52k}}$$


$$= 0.128k\Omega$$

$$R_i = \frac{R_E \parallel R_{ie}}{R_E + R_{ie}} = \frac{12k \cdot 0.128k}{12k + 0.128k} = \frac{12k \cdot 0.128k}{12k + 0.128k}$$

$$= 0.127k\Omega = 0.127k\Omega$$

Step 2: R_o

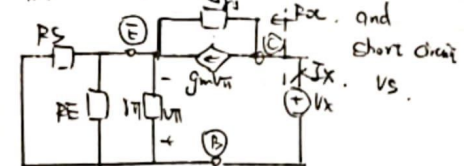Apply a test voltage source near Collector



$$R_{oc} = \frac{v_x}{i_x}$$

Apply KCL at output node, $i_x = g_m v_{\pi} + \frac{v_{\pi}}{r_{\pi}}$

Apply KCL at emitter node, $\frac{v_{\pi}}{R_S \parallel R_E \parallel R_{ie}} + g_m v_{\pi} + \frac{v_{\pi}}{r_{\pi}} = 0$

$$\Rightarrow \text{Thus, } R_{oc} = \frac{v_x}{i_x} = r_o \left[1 + g_m (R_C \parallel R_E \parallel R_{ie}) \right]$$

For $r_o = \infty$, so $R_{oc} = \infty$

Since $R_o = R_{oc} \parallel R_C$

\Rightarrow Therefore $R_o = R_C = 12k\Omega$