

EEE104 – Digital Electronics (I)

Lecture 14

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU


In This Session

Flip-Flops and Related Devices

- Latches
- Edge-Triggered Flip-Flops
- Flip-Flop Applications


Edge-Triggered Flip-Flops

 - An **edge-triggered** flip-flop changes state at the edges of a clock pulse.
- It is identified by a small triangle at the clock (C) input.
- It can be either rising-edge triggered or falling-edge triggered (bubble at C input).




Edge-Triggered Flip-Flops

A Method of Edge-Triggering

 


Edge-Triggered S-R Flip-Flops

 



INPUTS			OUTPUTS		COMMENTS
S	R	CLK	Q	\bar{Q}	
0	0	X	Q_0	\bar{Q}_0	No change
0	1	\uparrow	0	1	RESET
1	0	\uparrow	1	0	SET
1	1	\uparrow	?	?	Invalid

Edge-Triggered S-R Flip-Flops

An Example

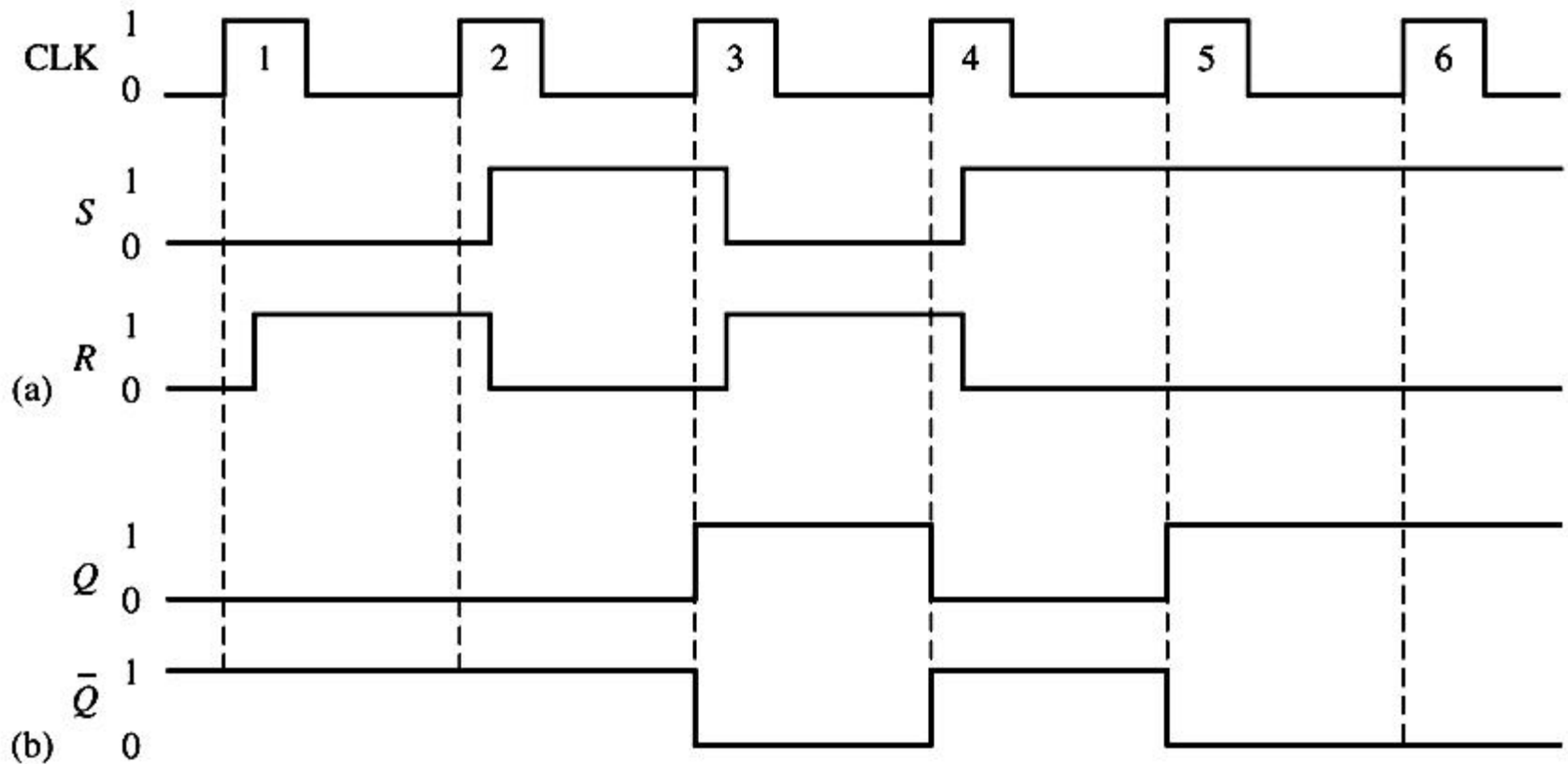


Edge-Triggered D Flip-Flops

  

INPUTS		OUTPUTS		COMMENTS
D	CLK	Q	\bar{Q}	
1	\uparrow	1	0	SET (stores a 1)
0	\uparrow	0	1	RESET (stores a 0)

\uparrow = clock transition LOW to HIGH


Edge-Triggered J-K Flip-Flops

 

- The J-K flip-flop is similar to the S-R flip-flop but has no invalid state.
- When $J = 1$ and $K = 1$, the output will be toggled at the rising edge of the clock.

INPUTS			OUTPUTS		COMMENTS
J	K	CLK	Q	\bar{Q}	
0	0	\uparrow	Q_0	\bar{Q}_0	No change
0	1	\uparrow	0	1	RESET
1	0	\uparrow	1	0	SET
1	1	\uparrow	\bar{Q}_0	Q_0	Toggle


Edge-Triggered J-K Flip-Flops

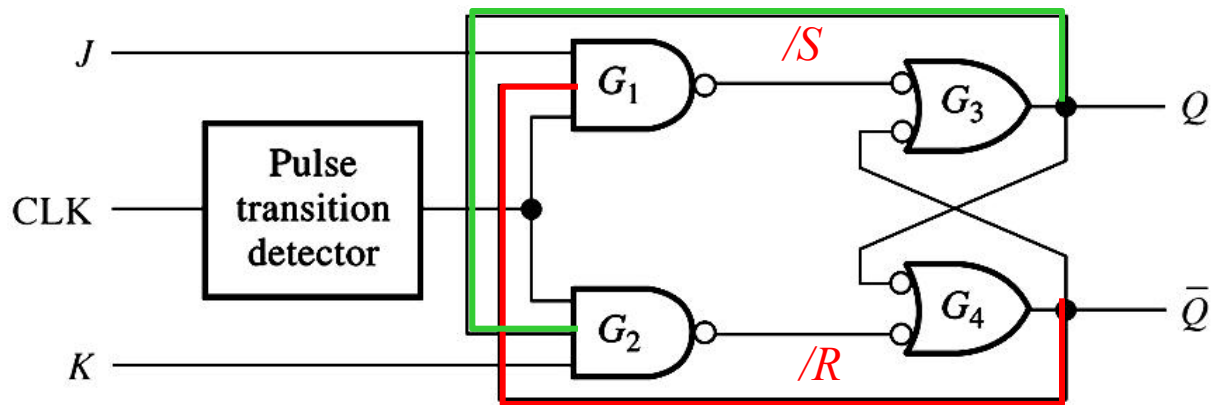

The difference with its S-R counterpart:

- The Q output is fed back to the input of gate G_2 .
- The $/Q$ output is fed back to the input of gate G_1 .

Edge-Triggered J-K Flip-Flops

 


How does it work?

- When both J and K are LOW, /S and /R are HIGH. Q^* will not change.
- When $J = 1$ and $K = 0$, /R is HIGH and /S = Q at triggering edges of CLK. If $Q = 0$, it will be SET. If $Q = 1$, no change. So $Q^* = 1$.

$$/S = \overline{1 \cdot \overline{Q} \cdot 1} = Q$$

Edge-Triggered J-K Flip-Flops

 


How does it work?

- When $J = 0$ and $K = 1$, $/S$ is HIGH and $/R = /Q$ at triggering edges of CLK . If $Q = 1$, it will be RESET. If $Q = 0$, $/R$ is HIGH and no change at Q . So $Q^* = 0$.

$$/R = 1 \cdot \overline{Q} \cdot 1 = \bar{Q}$$

Edge-Triggered J-K Flip-Flops

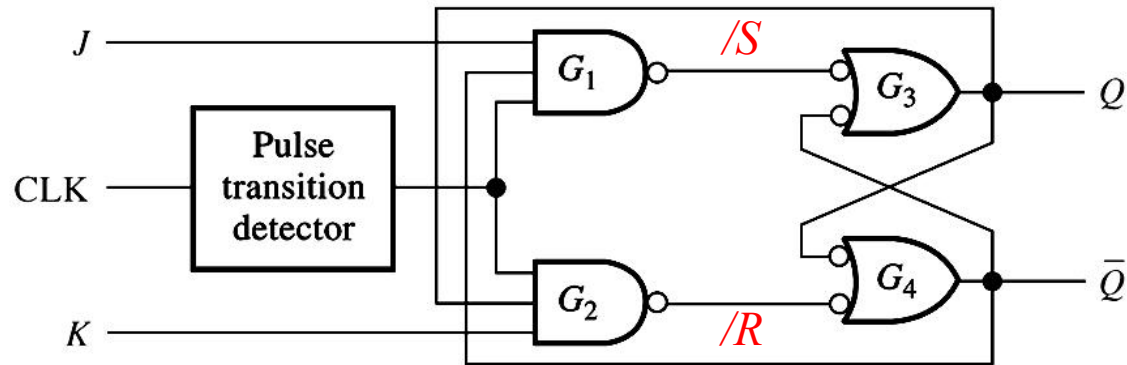

How does it work?


- When both J and K are HIGH, $/Q$ functions as the SET signal and Q functions as the RESET signal. $/S = 1 \cdot \overline{Q} \cdot 1 = \overline{Q}$

$$/R = 1 \cdot Q \cdot 1 = Q$$

- If $Q = 1$, $/S = 1$, $/R = 0$, $Q^* = 0$.
- If $/Q = 1$, $/S = 0$, $/R = 1$, $Q^* = 1$.

Edge-Triggered J-K Flip-Flops


An Example

 

Edge-Triggered J-K Flip-Flops


Asynchronous Preset and Clear Inputs

 - **Synchronous** inputs affects the state of the flip-flop only on the triggering edge of the clock.
- **Asynchronous** inputs affect the state of the flip-flop independent of the clock.



- The Clear input is used to RESET the output.
- The Preset input is used to SET the output.


Edge-Triggered J-K Flip-Flops

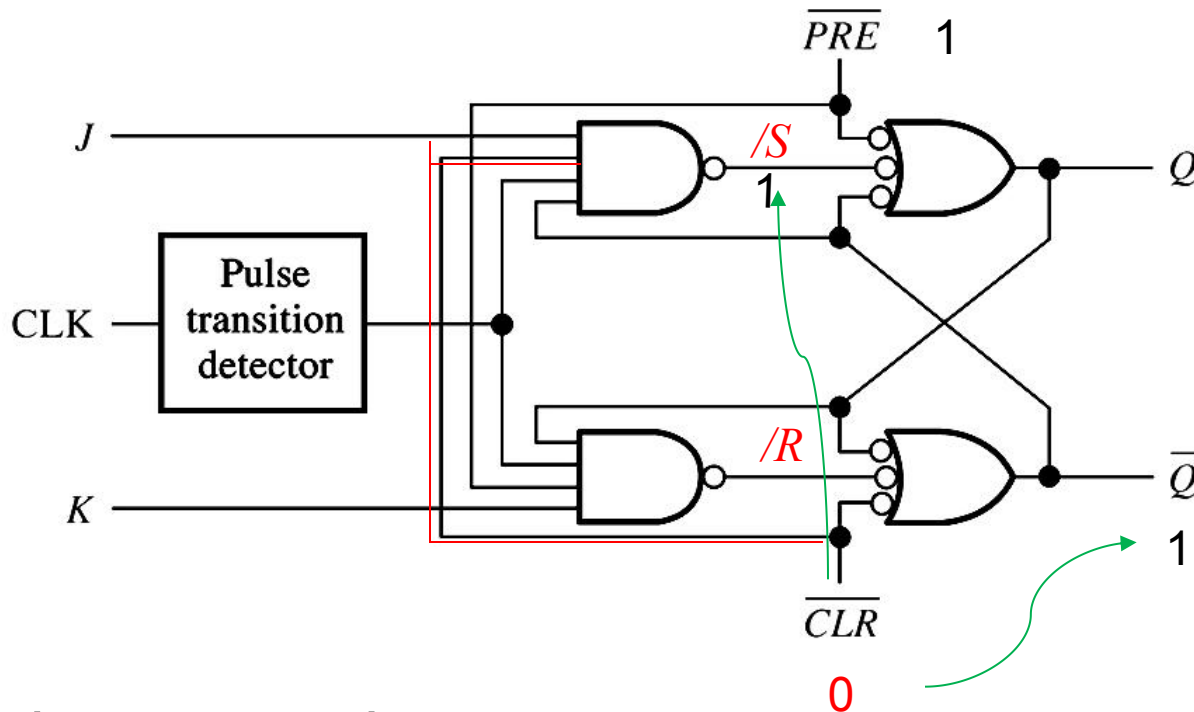

How does it work?

- When $\overline{CLR} = 0$ and $\overline{PRE} = 1$, $/R = 0$ and $/S = 1$. Q will be RESET.

Edge-Triggered J-K Flip-Flops


 


How does it work?

- When $\overline{CLR} = 1$ and $\overline{PRE} = 0$, $\overline{R} = 1$ and $\overline{S} = 0$. Q will be SET.

Flip-Flop Applications



Parallel Data Storage

  

Flip-Flop Applications

Frequency Division

  By connecting n flip-flops in this way, a frequency division of 2^n is achieved.



Flip-Flop Applications

Counting

Negative edge-triggered J-K flip-flops are used.

