

# EEE104 – Digital Electronics (I)

## Lecture 15

Dr. Ming Xu


Dept of Electrical & Electronic Engineering

XJTLU

# In This Session

- Counter Overview
- Asynchronous Counters

# A Revision: J-K Flip-Flops

 

- When  $J = 1$  and  $K = 1$ , the output will be toggled at the rising edge of the clock.

INPUTS			OUTPUTS		COMMENTS
$J$	$K$	CLK	$Q$	$\bar{Q}$	
0	0	$\uparrow$	$Q_0$	$\bar{Q}_0$	No change
0	1	$\uparrow$	0	1	RESET
1	0	$\uparrow$	1	0	SET
1	1	$\uparrow$	$\bar{Q}_0$	$Q_0$	Toggle


# Counter Overview

A **counter** is a group of flip-flops connected together to perform counting operation.


Categories:

- **Asynchronous counters:** each flip-flop is clocked by the output of the preceding flip-flop.
- **Synchronous counters:** all the flip-flops are clocked by the same clock input.

# 2-Bit Asynchronous Binary Counters

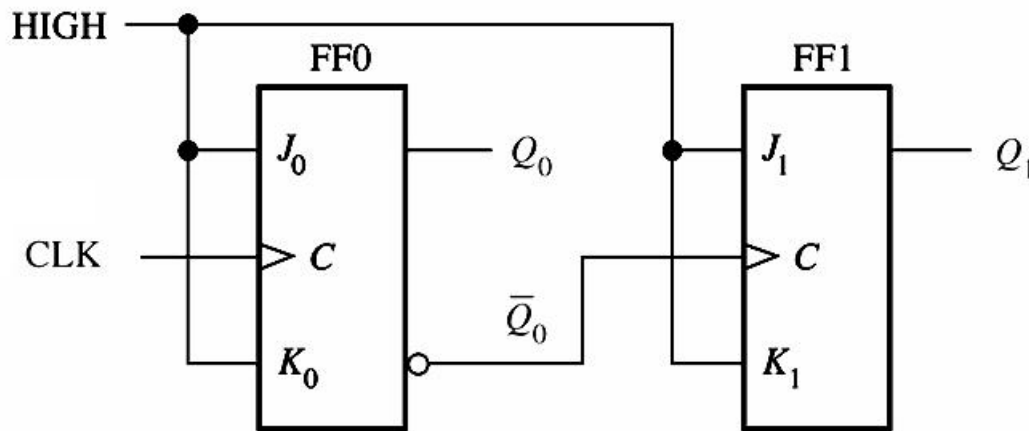


 - J and K are HIGH for all flip-flops.
- FF1 is clocked by the  $\bar{Q}_0$  output of FF0.





CLOCK PULSE	$Q_1$	$Q_0$
Initially	0	0
1	0	1
2	1	0
3	1	1
4 (recycles)	0	0

# 3-Bit Asynchronous Binary Counters

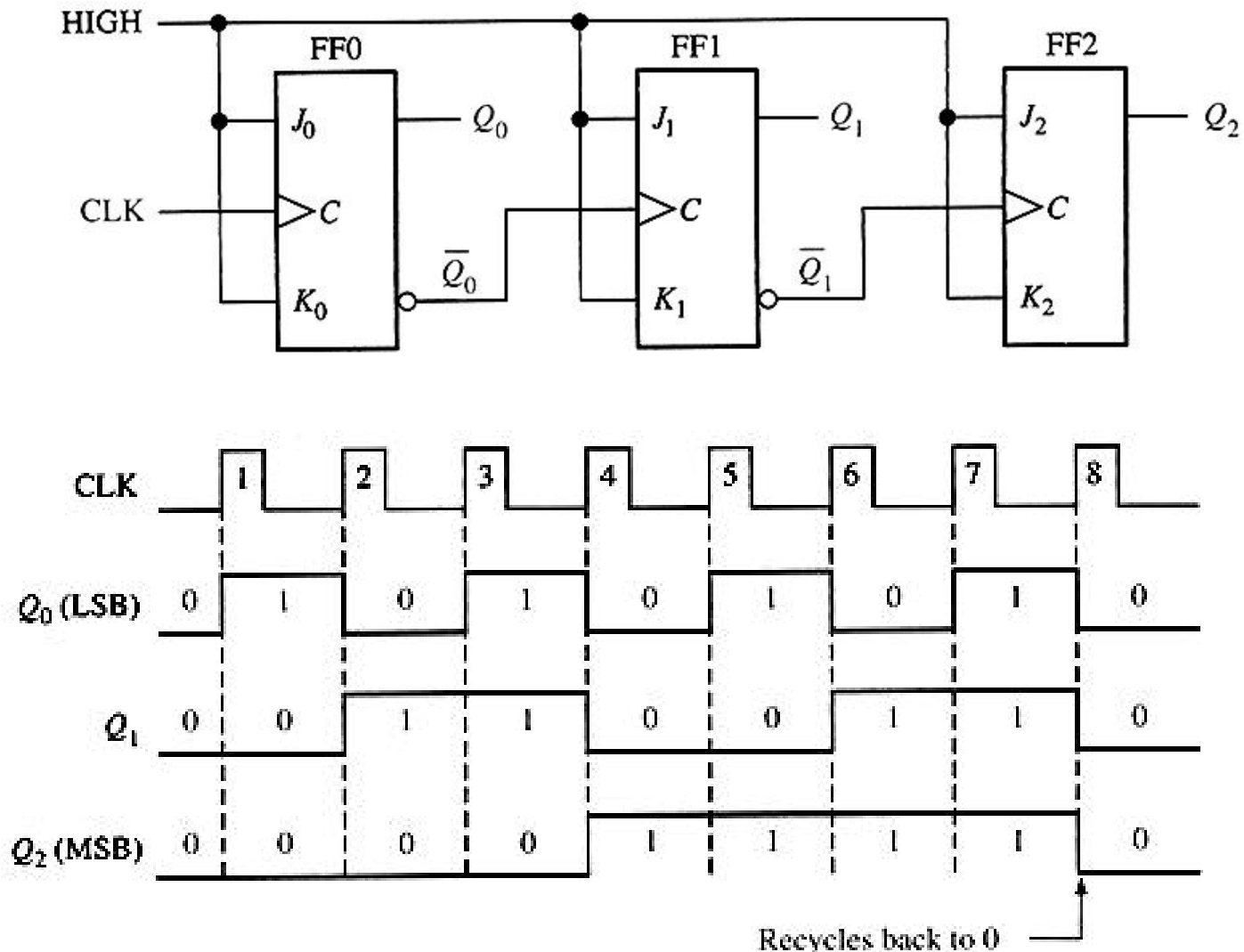

# 4-Bit Asynchronous Binary Counters

  


# Asynchronous Decade Counters


- With  $n$  flip-flops, the maximum number of states of a counter is  $2^n$ .
- A counter may be designed to go through less states or a **truncated** sequence, e.g. **decade counter** which counts from 0000 to 1001.
- The number of unique states that a counter will sequence through is called **modulus**.



# Asynchronous Decade Counter

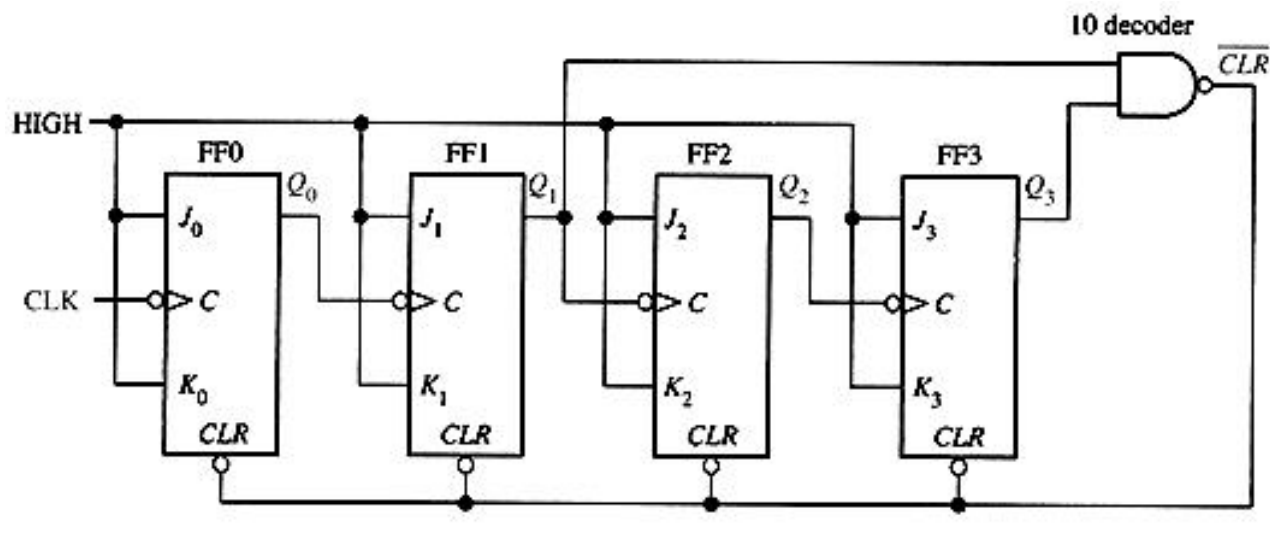


 0000  
0001  
0010  
0011  
0100  
0101  
0110  
0111  
1000  
1001  
1010




- Once state 1010 appears, the decoder will reset the counter.
- Only  $Q_1$  and  $Q_3$  used – Partial Decoding

# Asynchronous Modulus-12 Counters

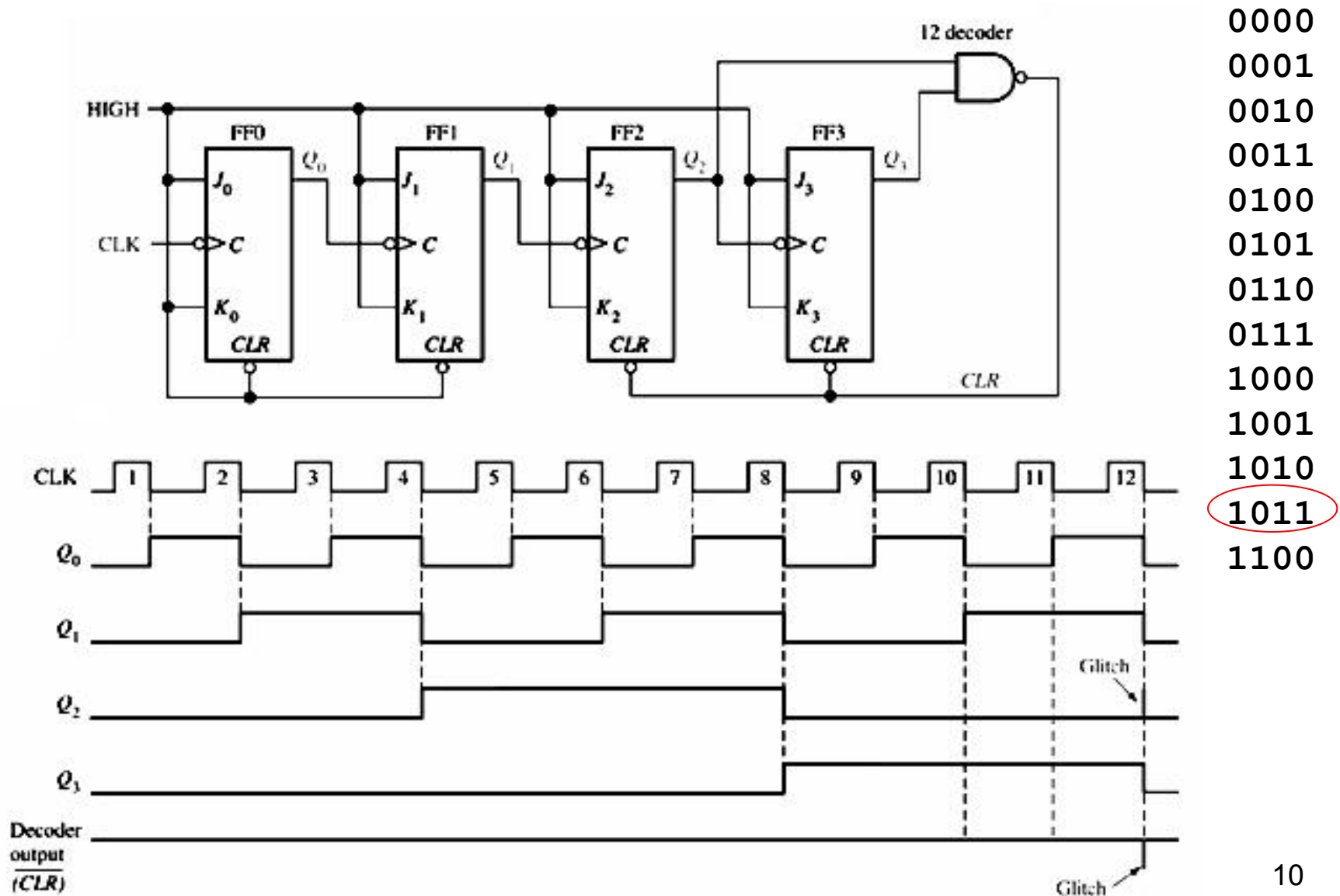
 
# Cumulative Delay in Asynchronous Counters

The **propagation delay time** is the time interval for the output to change after an input has been applied.




74HC74A

$t_{PHL}$

17 ns

$t_{PLH}$

17 ns


 


74LS74A

40 ns

25 ns
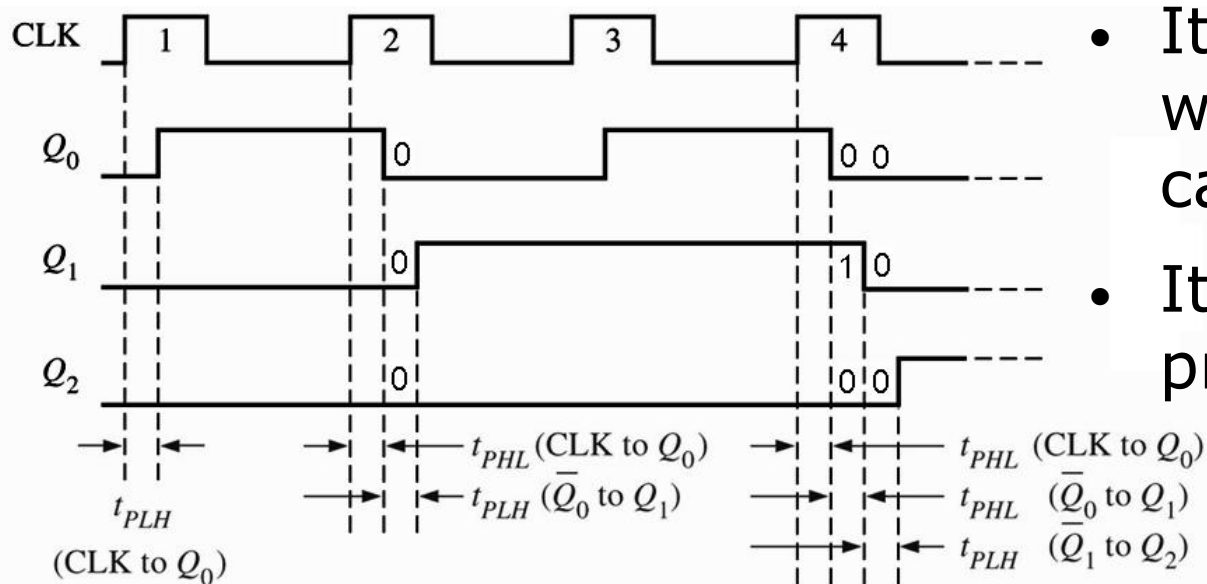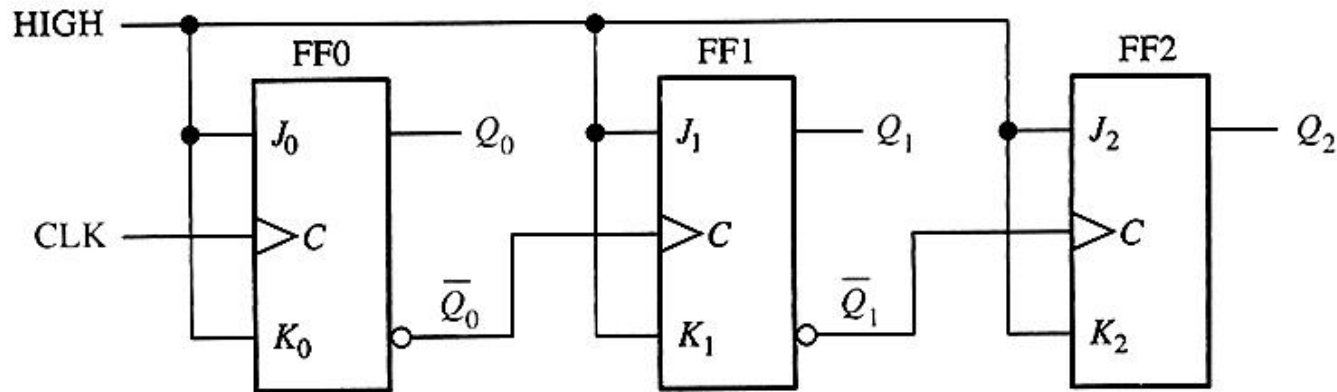
# Cumulative Delay in Asynchronous Counters




- It limits the rate at which the counter can be clocked.
- It creates decoding problems.


# IC Asynchronous Counters
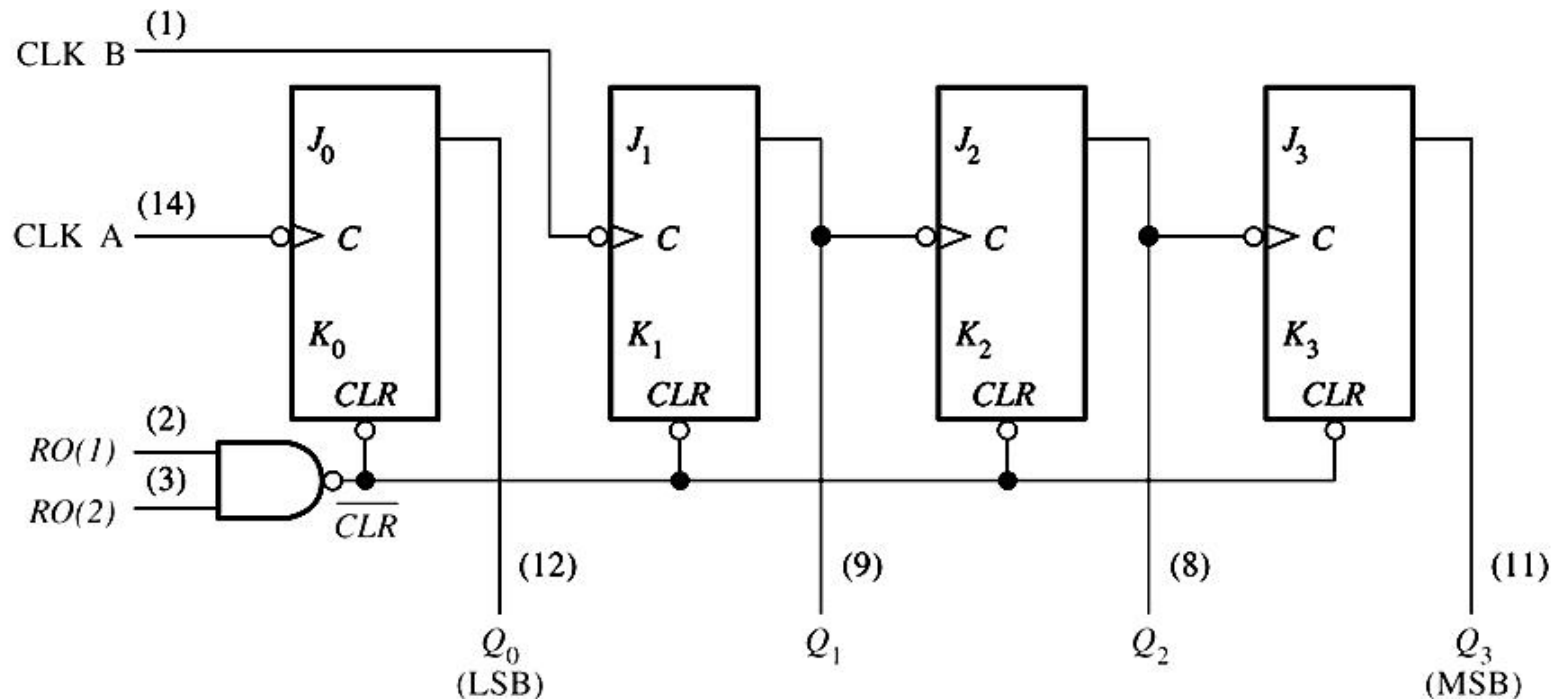
## 74LS93A


- $Q_0$  should be connected with CLK B when used as a counter.
- The NAND gate can be used as the decoder.




# IC Asynchronous Counters

 


Modulus-16 counter

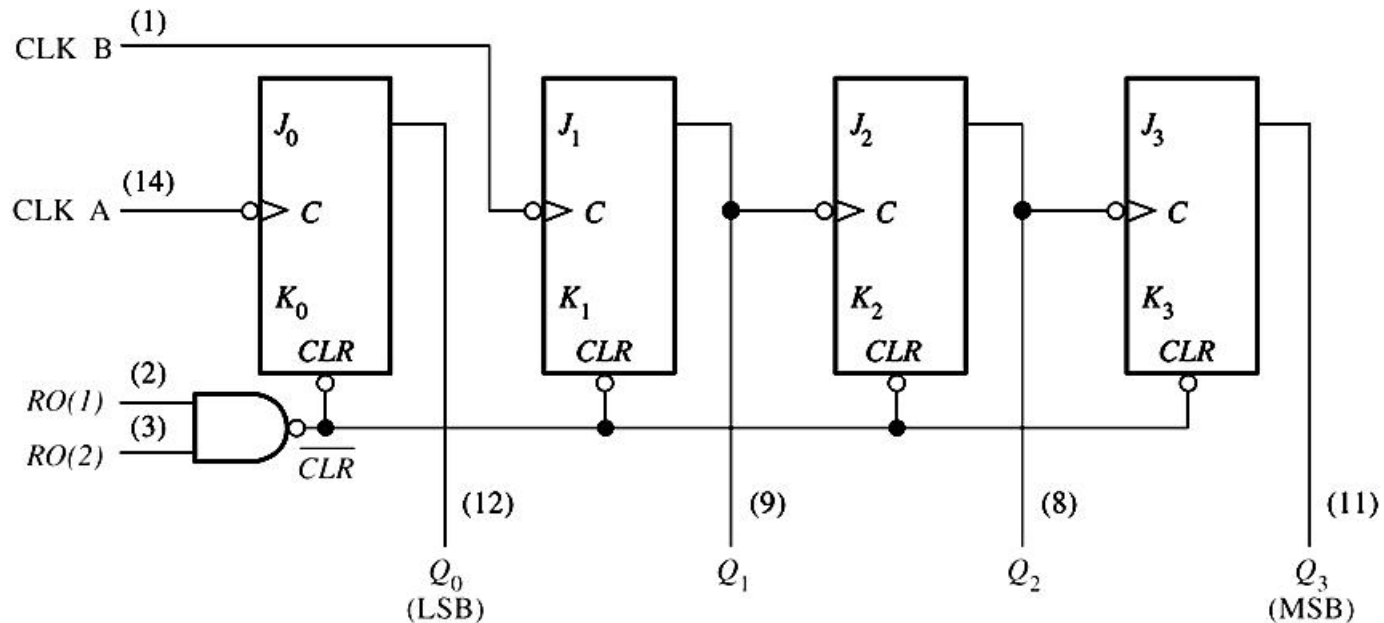


# IC Asynchronous Counters

 

Decade counter

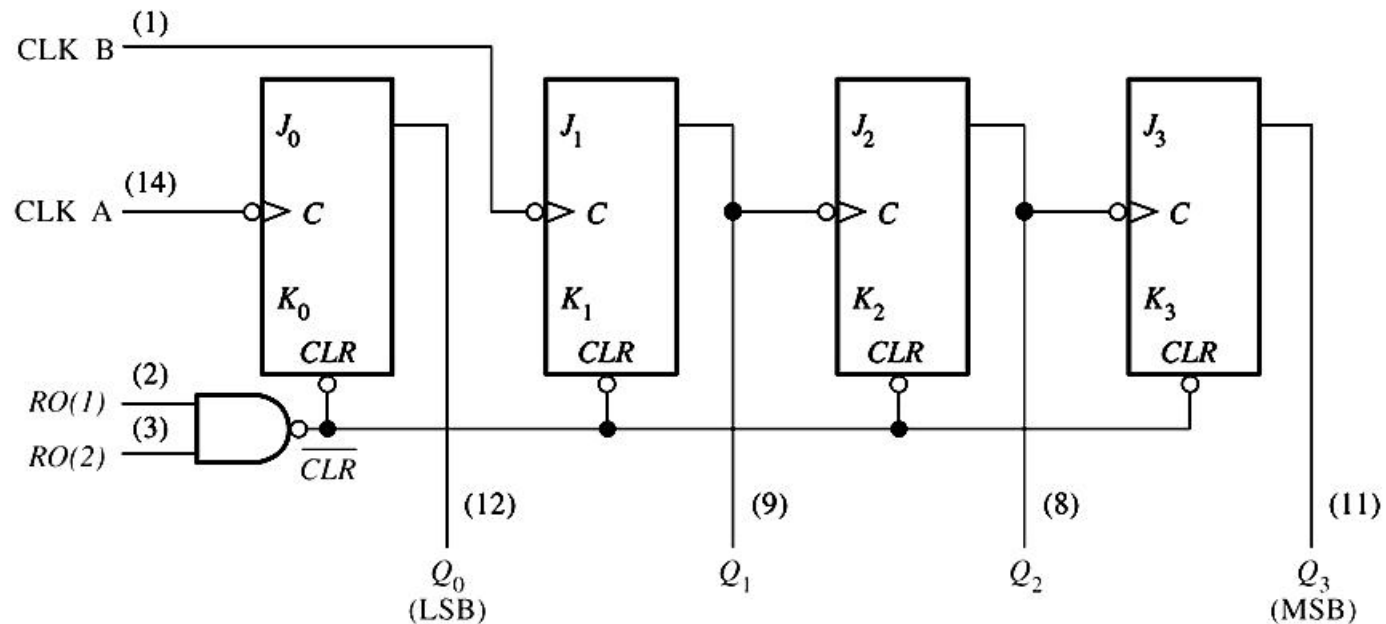

# IC Asynchronous Counters

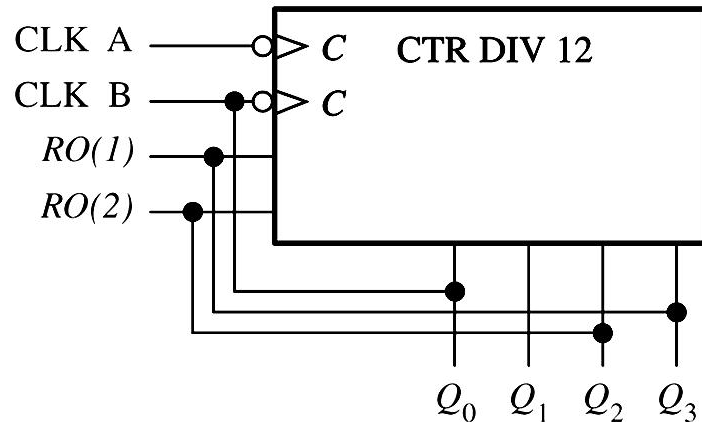

Modulus-12 counter

