

Revision


Dr. Suneel Kommuri

Email: Suneel.Kommuri@xjtlu.edu.cn

Dept. Electrical & Electronic Engineering

Lecture 1 Introduction


- **What is power electronics?**
 - Definition: electronics applied to convert and control of electric power
 - Conversion between AC and DC electric power

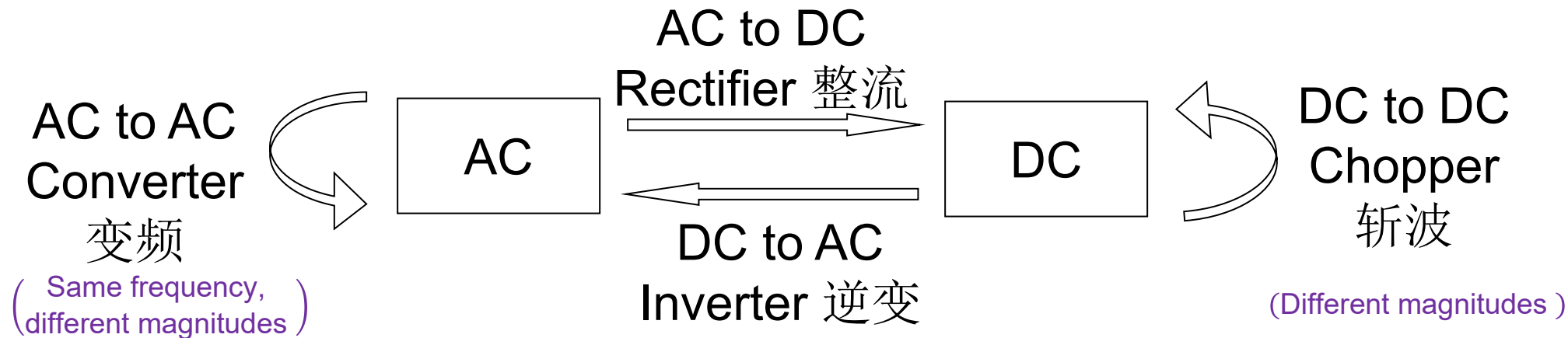


Lecture 2: Uncontrolled Rectifier (1-phase)

- Controllability
 - Uncontrolled ➔ Uncontrolled turn-ON & OFF (e.g., diode)
 - Semiconrolled \Rightarrow Controlled turn-ON and uncontrolled turn-OFF (e.g., SCR)
 - Controlled \Rightarrow Controlled turn-ON & OFF (GTO, BJT, MOSFET, IGBT)
- Input power (source)
 - Single phase
 - Three phase
- Waveform
 - Half-wave
 - Full-wave

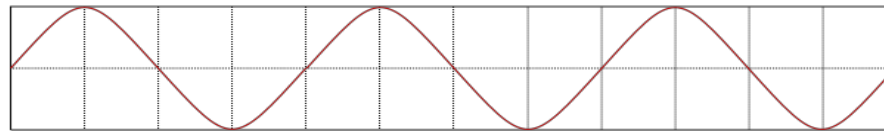
Provides larger efficiency, small fluctuations, filtering of unwanted frequency is easier



Input

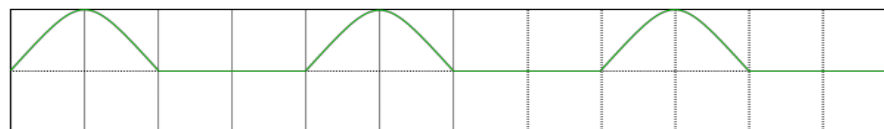

Half-wave

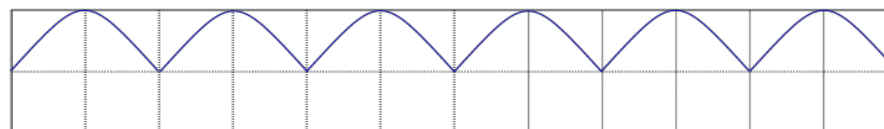

Full-wave



Lecture 3: Uncontrolled Rectifier (3-phase)


- Single phase rectifiers are extensively used in *low-power applications* particularly for power supplies to electronic circuits.
- Single phase rectifiers have several *disadvantages*:
 - Large output voltage and current form factor;
 - Large low frequency harmonic ripple current causing harmonic power loss and reduced efficiency;
 - Very large filter capacitor for obtaining smooth output dc voltage;
 - Low frequency harmonic current is injected in the input ac line which is difficult to filter. The situation becomes worse with capacitive loads.
- Many of these disadvantages are *mitigated/attenuated* to a large extent using *three-phase rectifiers*.



Lecture 3: Uncontrolled Rectifier (3-phase)


Source is star-connected with V_a , V_b , V_c (whose magnitudes & frequencies are same with 120 degree phase difference).

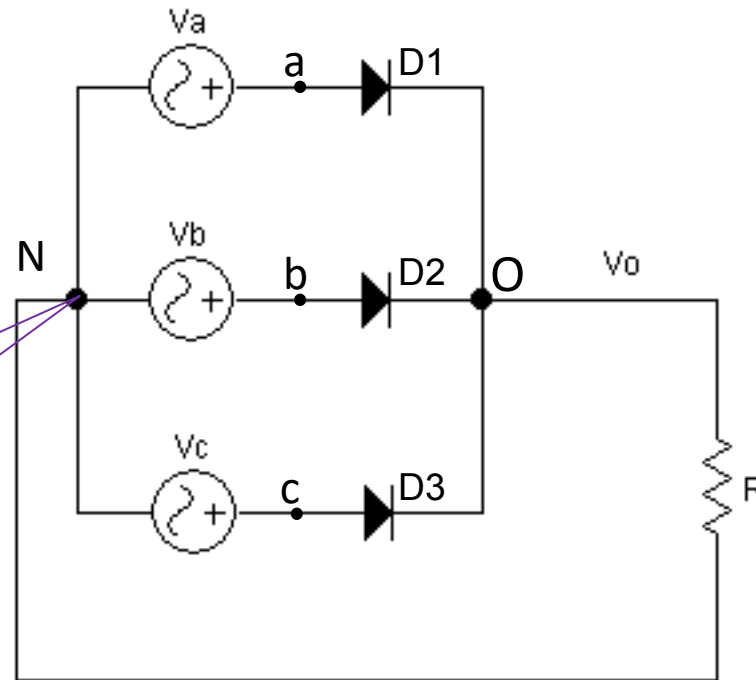Negative ends of the sources are connected together to ground (GND)



Half-bridge rectifier (Common-Cathode)

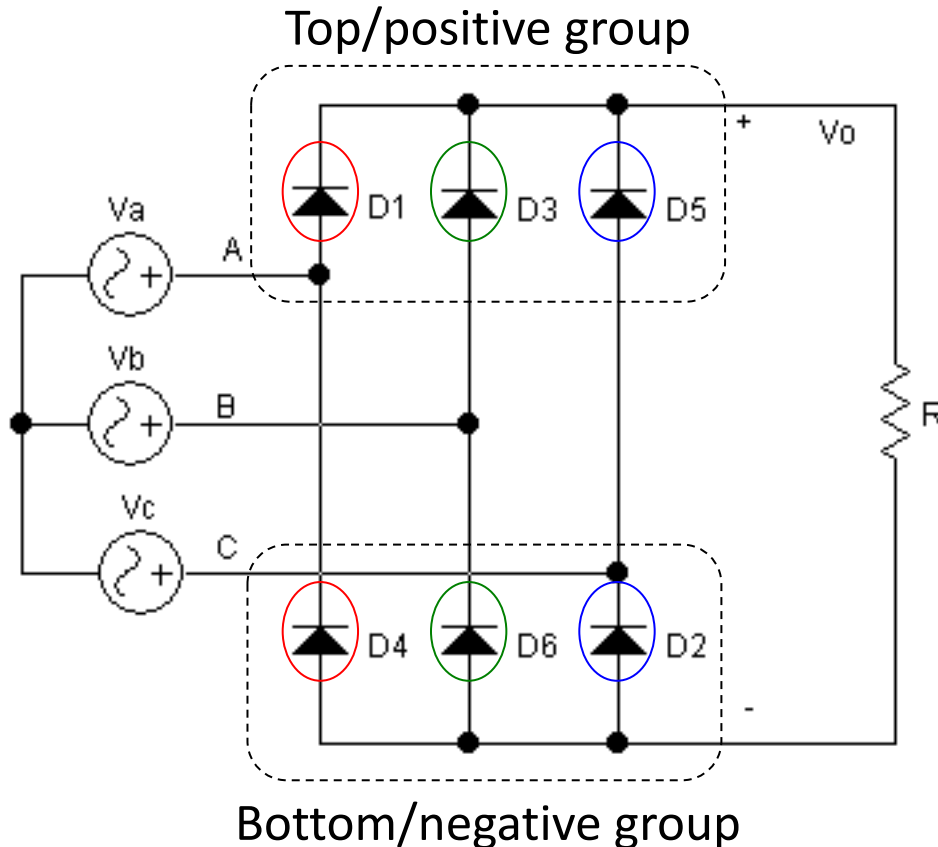Lecture 3: Uncontrolled Rectifier (3-phase)







Full-bridge rectifier

- For full-wave circuit, *6 diodes* are used and arranged in three legs – each leg has two series-connected diodes.
- Top group: Diodes D1, D3, and D4.
- Bottom group: Diodes D4, D6, and D2.
- Note that *diodes are not in the sequence*.
- To form a conduction loop, there always are two diodes conducting, *one from top group and one from bottom group*:
 - Top group: the one has the highest anode voltage will conduct;
 - Bottom group: the one has the lowest cathode voltage will conduct;


Lecture 4: Controlled Rectifier (1-phase)

- SCR acts as bi-stable switches, conducting when their gate receives a current pulse, and continue to conduct for as long as they are forward biased (that is, as long as the voltage across the device has not reversed).
 - Three-terminals: anode, cathode, gate

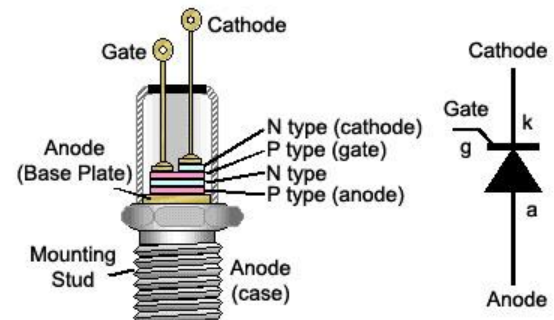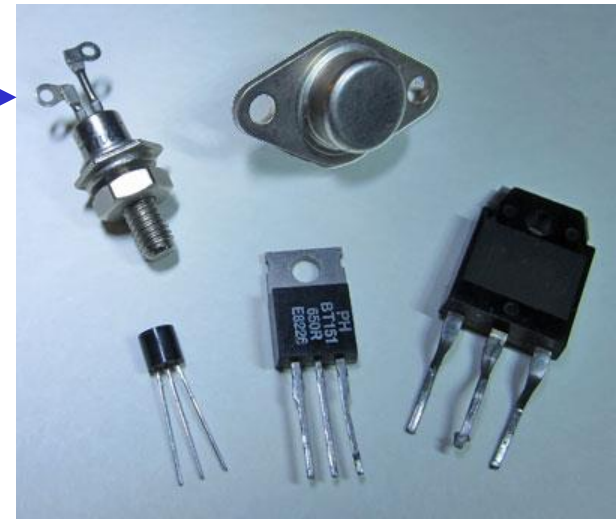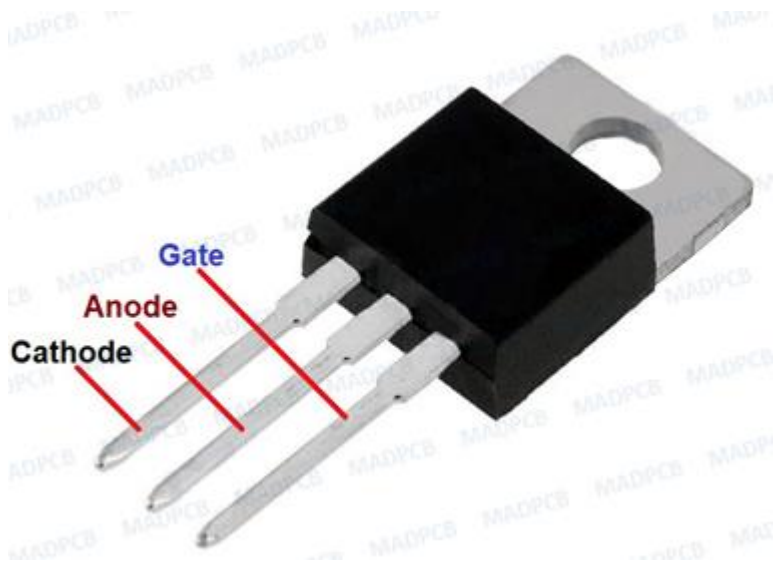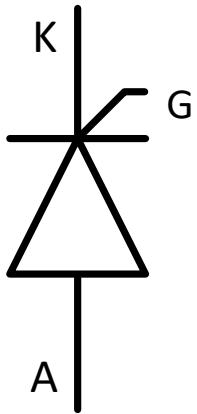

Lecture 4: Controlled Rectifier (1-phase)

- Two conditions must be met before the SCR can conduct:
 1. The SCR must be forward biased ($v_{AK} > 0$).
 2. A current must be applied to the gate of SCR.
- A *SCR is turned ON* by increasing the anode current. This can be accomplished in one of the following ways:
 1. Forward voltage triggering
 2. Gate triggering
 3. The dv/dt triggering
 4. Temperature triggering
 5. Light triggering

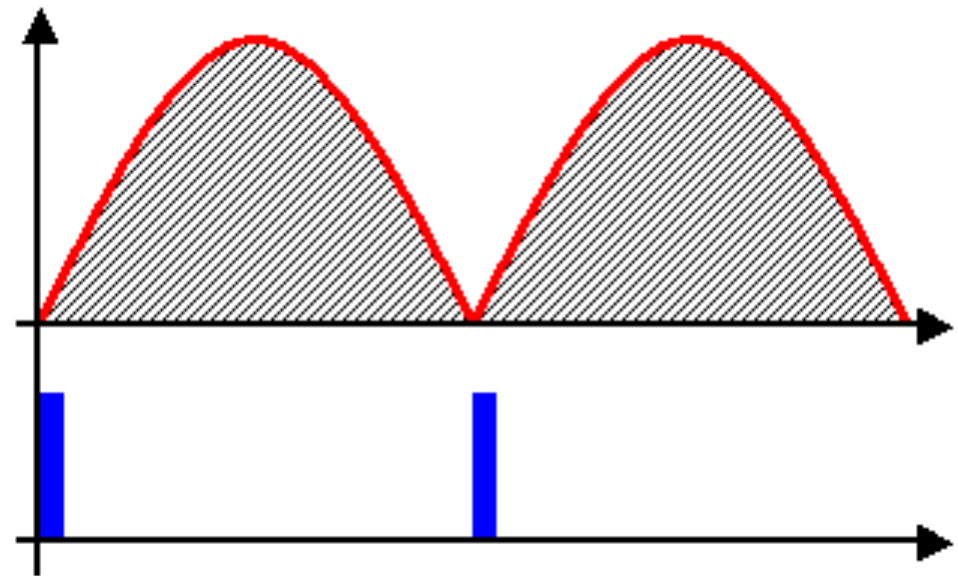

Lecture 4: Controlled Rectifier (1-phase)

• 1. Half-wave *controlled* rectifier

– In the positive half


- $[0, \alpha]$: i_R is zero, v_o is zero;
- $[\alpha, \pi]$: $v_o = v_s = V_m \sin \omega t$;

$$i_A = i_R = \frac{V_m}{R} \sin \omega t.$$

– In the negative half


- $[\pi, 2\pi]$: i_R drops to zero, v_o is zero.

- Firing angle: α
- Conduction angle: $\gamma = \pi - \alpha$

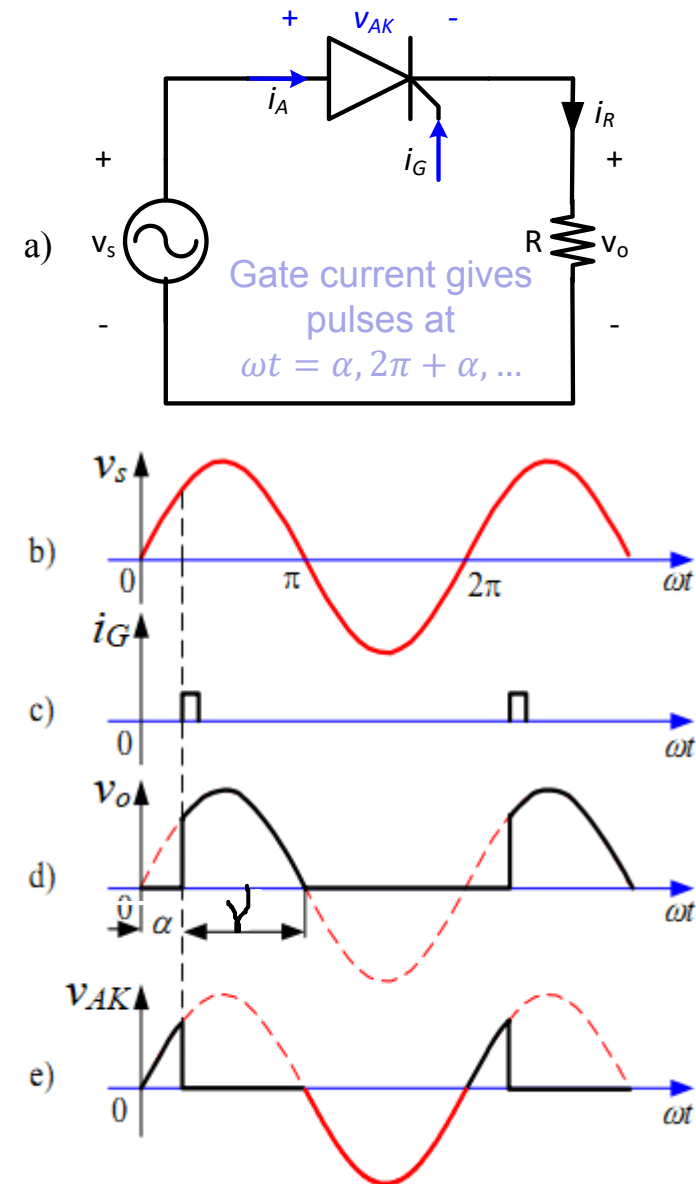


Lecture 4: Controlled Rectifier (1-phase)

- Full-bridge rectifier (R)
 - T_1 and T_2 is a pair of bridge arm: In the positive half of v_s , they start to conduct when triggered by a pulse, and will be closed when v_s passes 0 to negative.
 - → Blue current path
 - T_3 and T_4 is another pair of bridge arm: In the negative half of v_s , they start to conduct when triggered by a pulse, and will be closed when v_s passes 0 to positive.
 - → Red current path

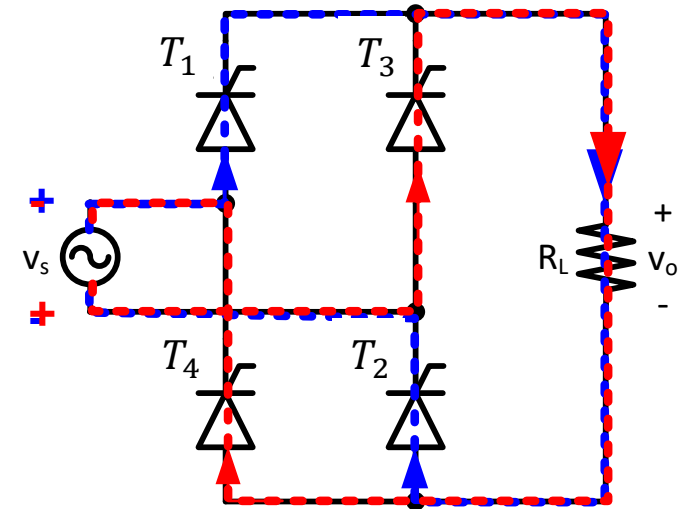

Lecture 5: Controlled Rectifier (3-phase)


- In controlled rectifier, controllability of the circuit is realized by triggering the thyristors at different phases, which is called the **firing/triggering angle**. It is usually represented by “ α ”;
 - This trigger signal is a current pulse at the “gate” terminal of thyristors;
 - For **single phase circuit**, $\alpha = 0$ means trigger signal is sent at $\omega t = 0$;
 - For **three-phase circuit**, $\alpha = 0$ means trigger signal is sent at $\omega t = \pi/6$, which is the first **natural commutation (phase changing) point**.

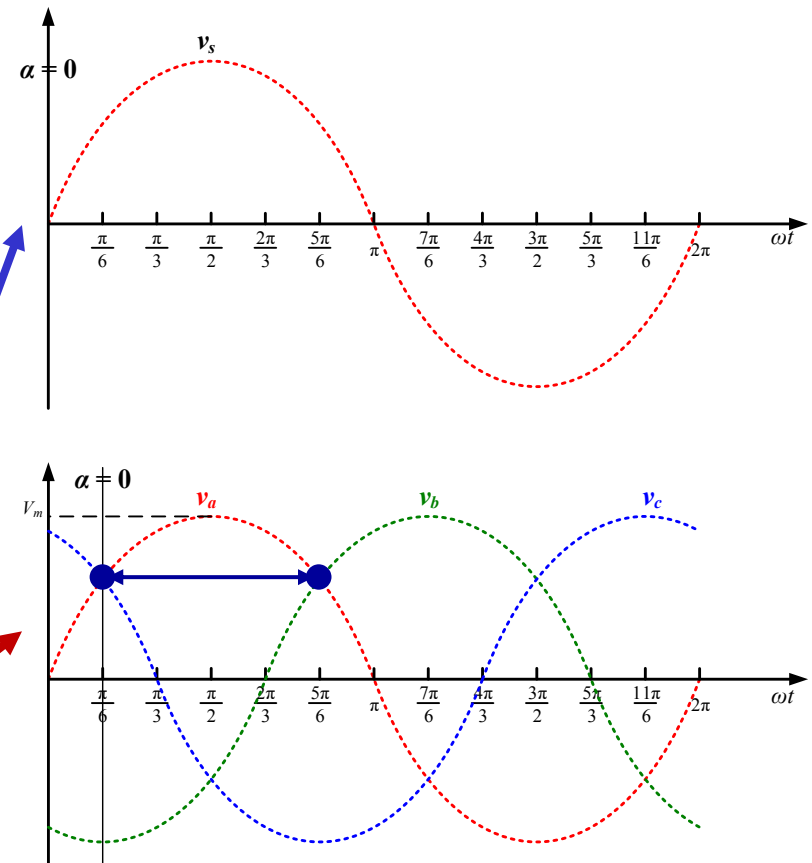

Lecture 5: Controlled Rectifier (3-phase)


- Resistive load

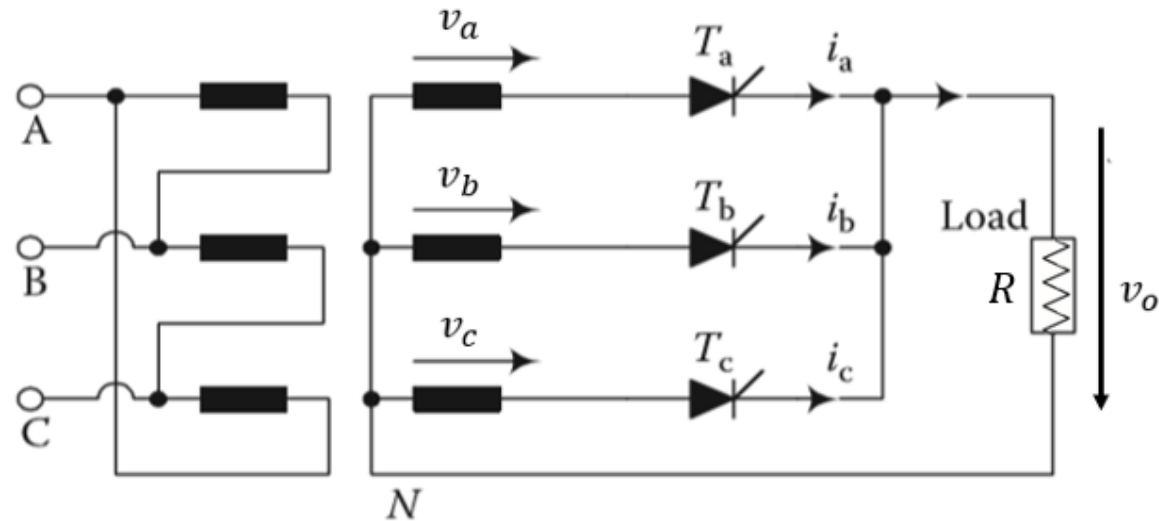- ❖ Three phase supply – primary in delta and secondary in star connection.
- ❖ Common-cathode connection.




- Natural commutation (phase-changing) point

- It is considered as the starting point for thyristor triggering angle α , i.e. $\alpha = 0^\circ$.
- Phase-shift range: $\alpha \leq 120^\circ$.

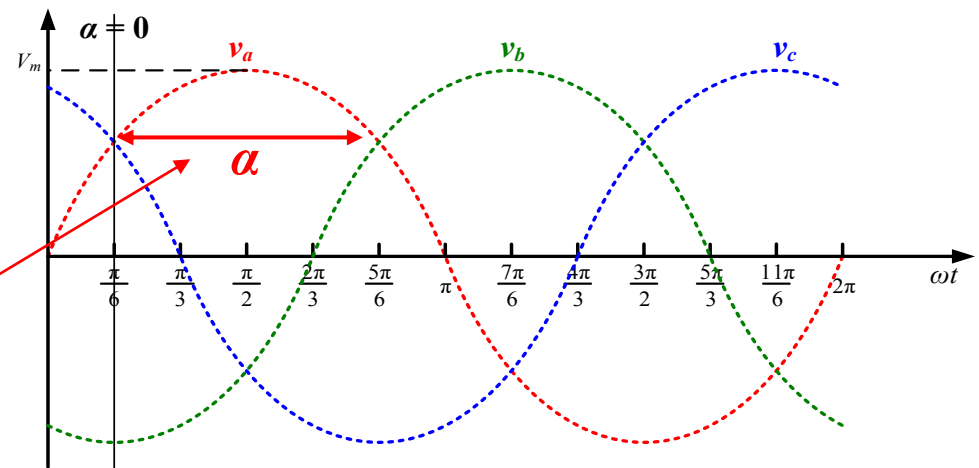

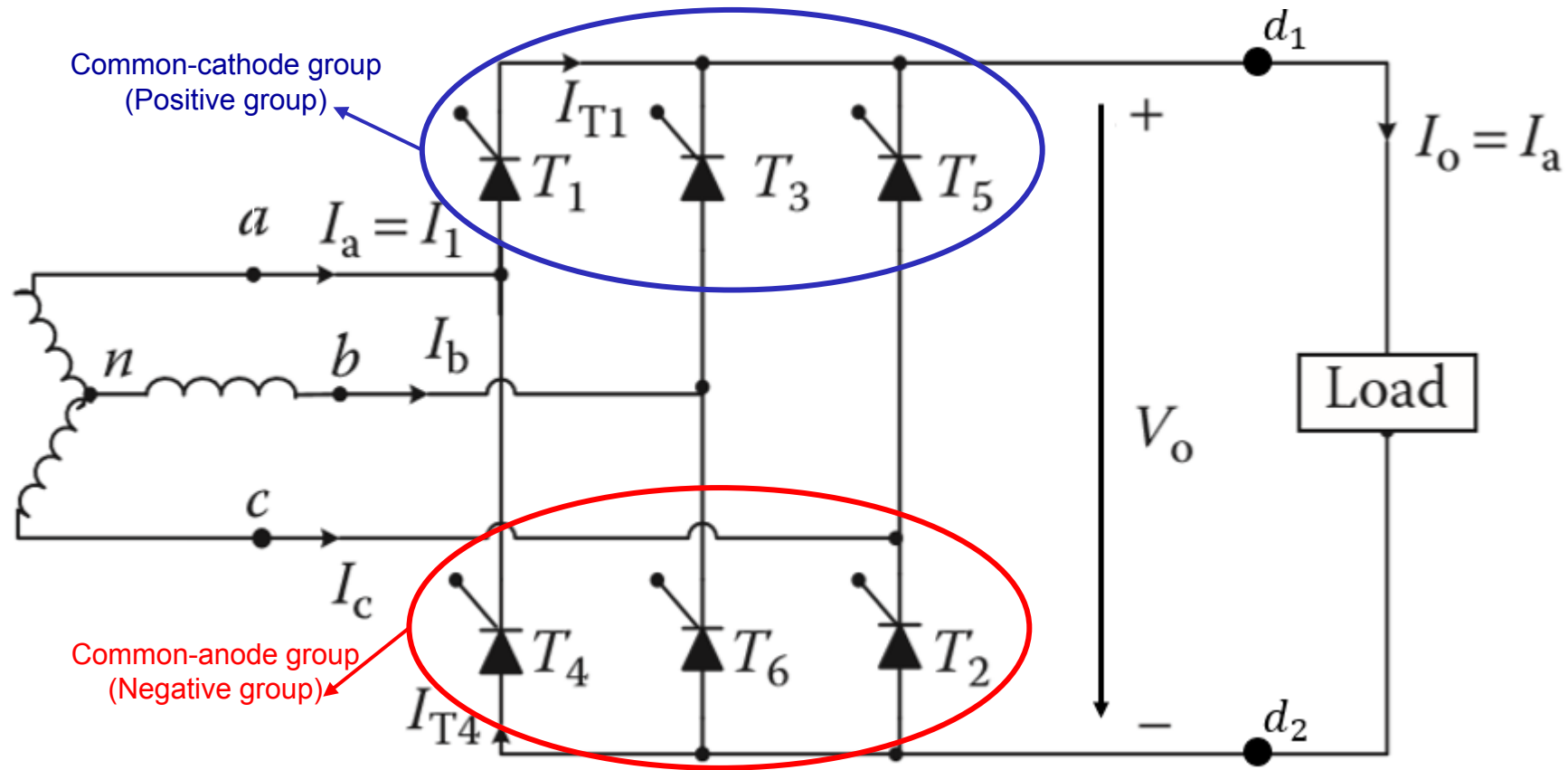
Lecture 5: Controlled Rectifier (3-phase)



- Numbering of the 6 thyristors indicates the trigger sequence:

$$T_1 \rightarrow T_2 \rightarrow T_3 \rightarrow T_4 \rightarrow T_5 \rightarrow T_6$$

Lecture 6: AC-AC Converters

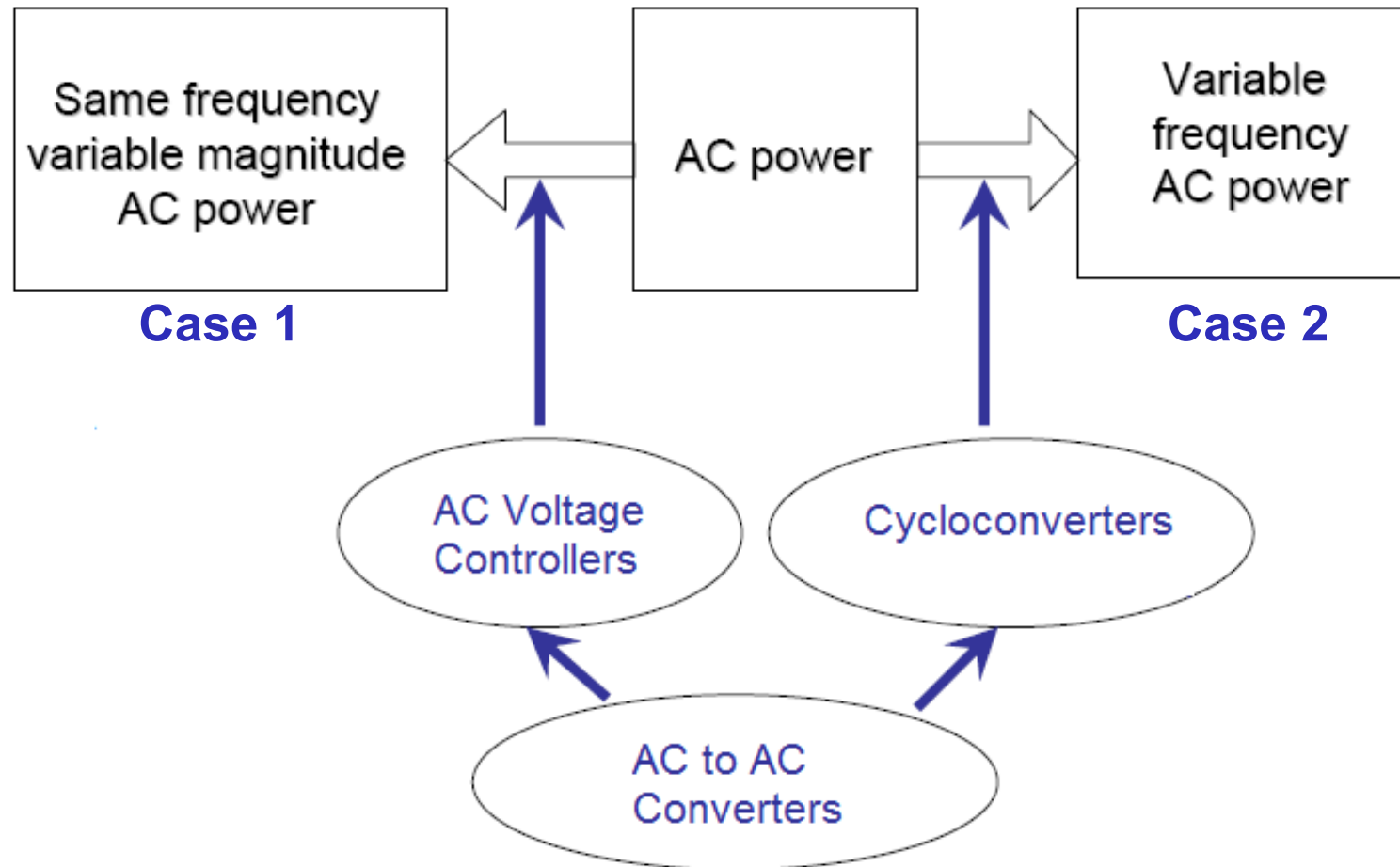

✓ Used to obtain a variable ac output voltage from a fixed ac source.



Lecture 6: AC-AC Converters

In order to get variable AC voltage from an AC source, two techniques are often used:

Allows a current flow
in both directions

- **Phase control**

- The strategy is to use anti-parallel connected thyristors or **TRIACS** (Triode AC Switch).
- Like AC-DC converters, the firing angle of the devices are controlled.
- The devices conduct for a portion of each cycle.

- **On-off/integral-cycle control**

- The devices conduct some cycles in a period of time and then disconnect some cycles.
- The firing angle of devices is 0. But for some cycles, the firing pulses are turned off.
- Lower switching losses.




Lecture 6: AC-AC Converters

Cycloconverters

- Converts input power at one frequency to output power at a different frequency with one-stage conversion.
- It can be used to eliminate the requirement of one or more intermediate converters.
 - ✓ Another name—*direct frequency converter* (as compared to AC-DC-AC frequency converter)
 - If the output frequency is greater than input frequency → *step-up (forced)*
 - If the output frequency is less than input frequency → *step-down (natural)*
- Applications of cycloconverters are:
 - ✓ Speed control of very high power ac drives
 - ✓ Industrial heating etc.,



Lecture 7: DC to DC Converters

- DC-DC converters (also called *choppers*) can be used to obtain a *variable dc voltage from a fixed dc supply*.
- Step-down (*Buck converters*) – output voltage is less than input voltage.
- Step-up (*Boost converters*) – output voltage is higher than input voltage.
- Step-up/down: *Buck-boost converters*
 - the output voltage can be higher or less than the input voltage.

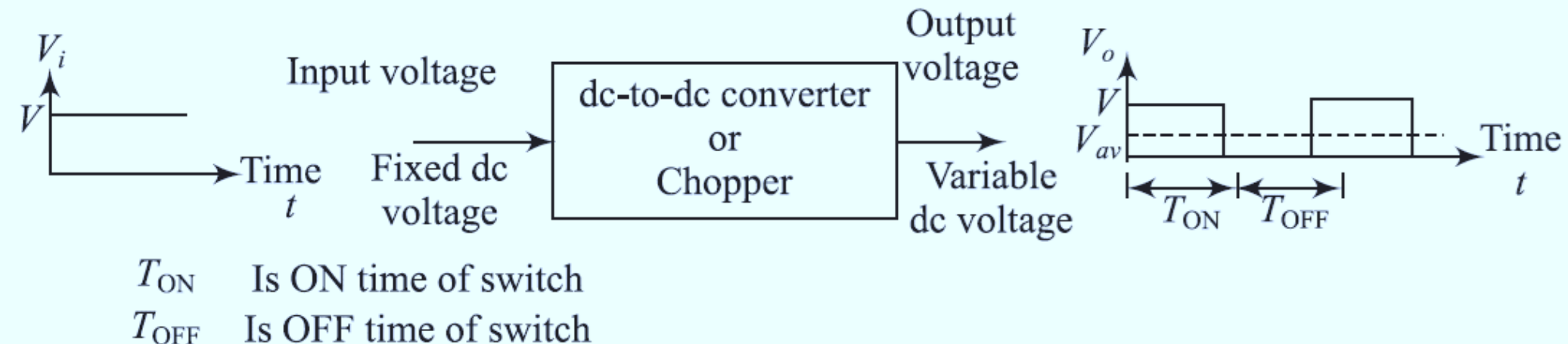



Lecture 7: DC to DC Converters (Buck)

- Average output voltage is *less than* input voltage – hence, called *buck* converter.
- One switch and one diode (to overcome the problem of stored inductive energy).
- Switch S can be a power BJT and acts as a controlled switch; diode D is uncontrolled switch – operate as *two* SPST bidirectional switches, shown below.
- LC filter to remove switching harmonics and to pass only the DC component so that the output voltage v_o is nearly a constant.

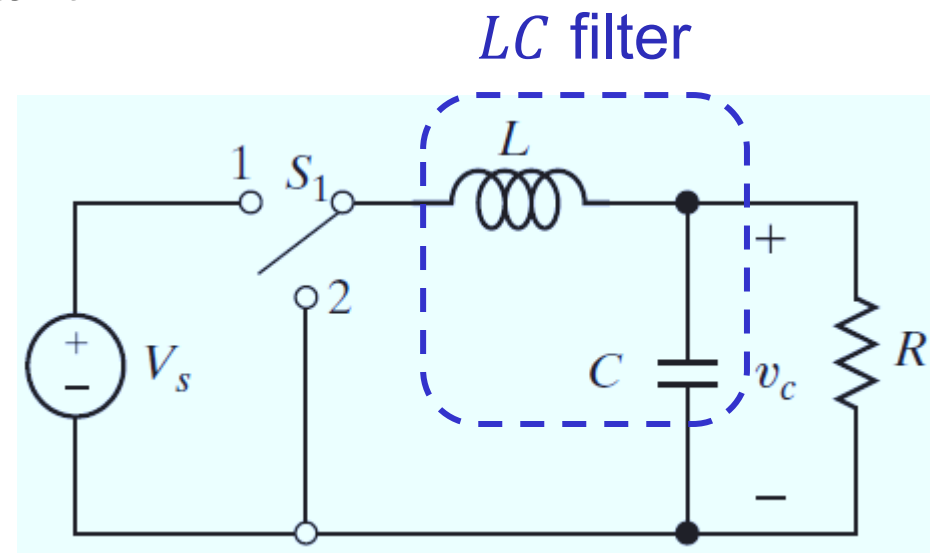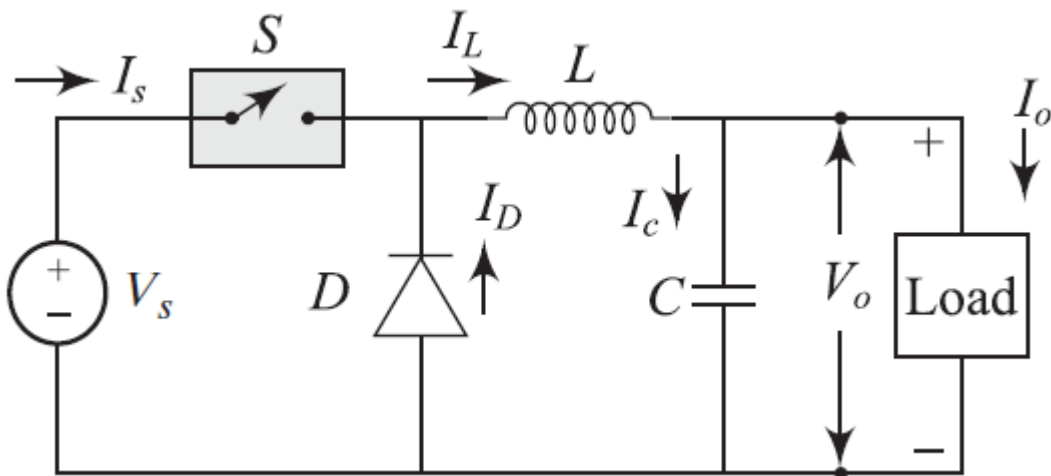



Lecture 7: DC to DC Converters (Boost)

- Average output voltage is *greater than* input voltage – hence, called *boost* converter.
- One switch and one diode (to overcome the problem of stored inductive energy).
- Switch S can be a power MOSFET and acts as a controlled switch; diode D is uncontrolled switch – operate as *two* SPST bidirectional switches, shown below.

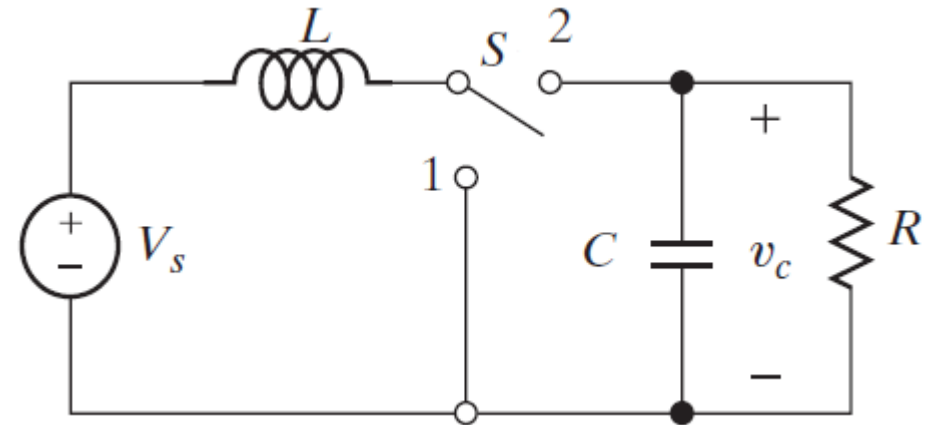
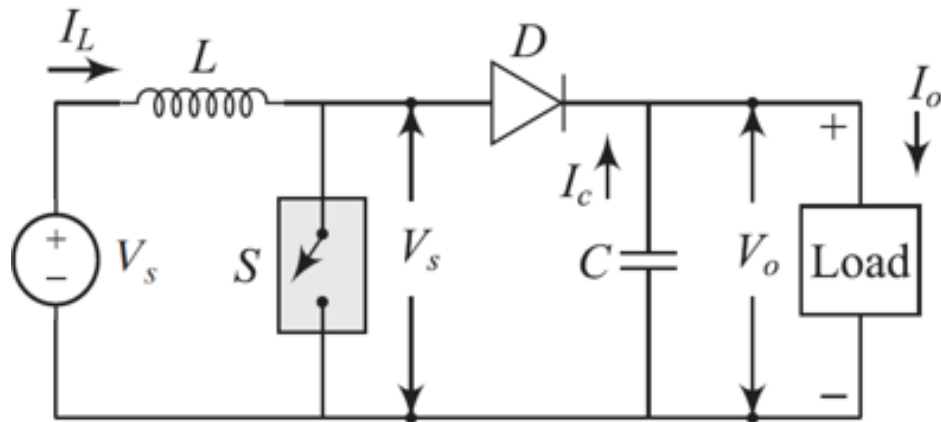


Lecture 7: DC to DC Converters (Comparison)



Buck

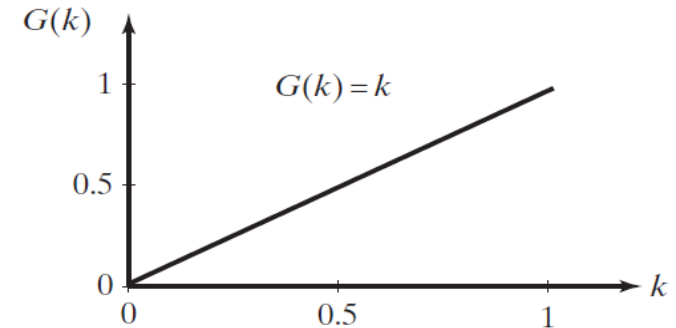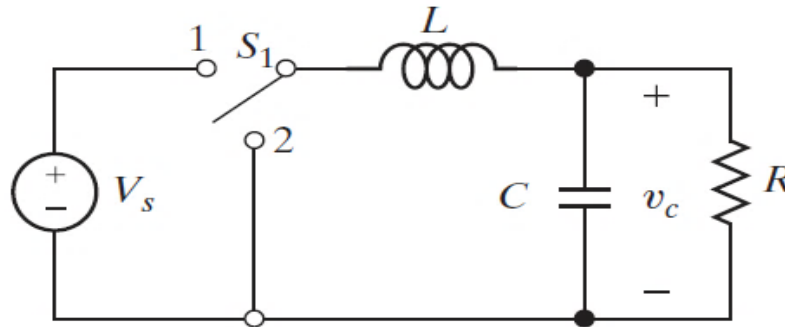

Boost

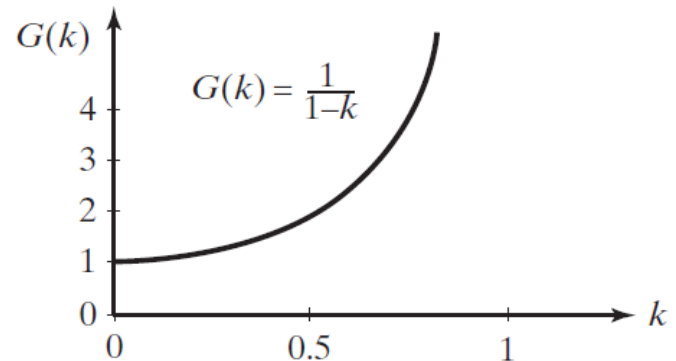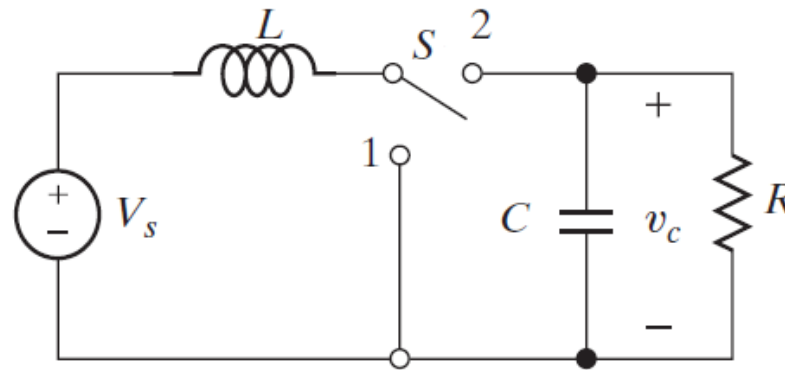

Buck-Boost

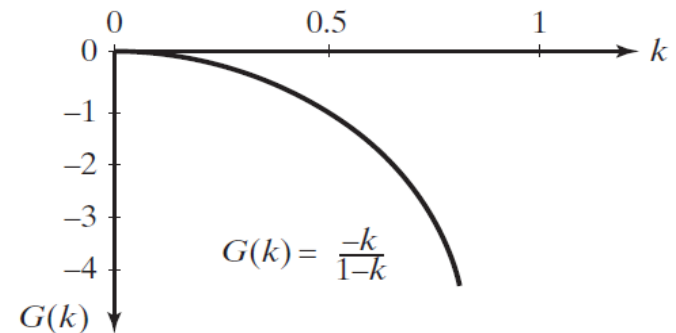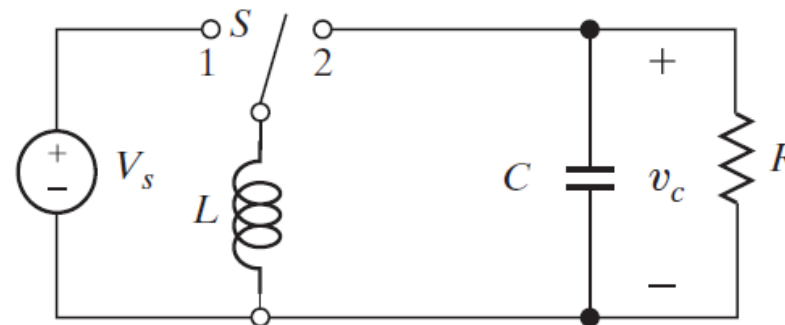

Switch representation




Comparison of voltage gains

Lecture 8: DC to AC Inverters

- Changes DC input voltage to a symmetric AC output voltage of desired magnitude and frequency – *Inverter*
- Variable output voltage can be obtained by *varying the input dc voltage* and maintaining the gain of the inverter constant
- If the *DC input voltage is fixed*, the output voltage can be controlled using – *pulse-width-modulation (PWM)*
- The output voltage should be sinusoidal, *however*, practical inverters are non-sinusoidal and contain *certain harmonics*
- Inverters are widely used in industrial applications – inputs may be battery, fuel cell, solar cell, or other dc source
- The inverters use *fully controlled devices* – BJTs, MOSFETs





Lecture 8: Single-phase half-bridge VSI

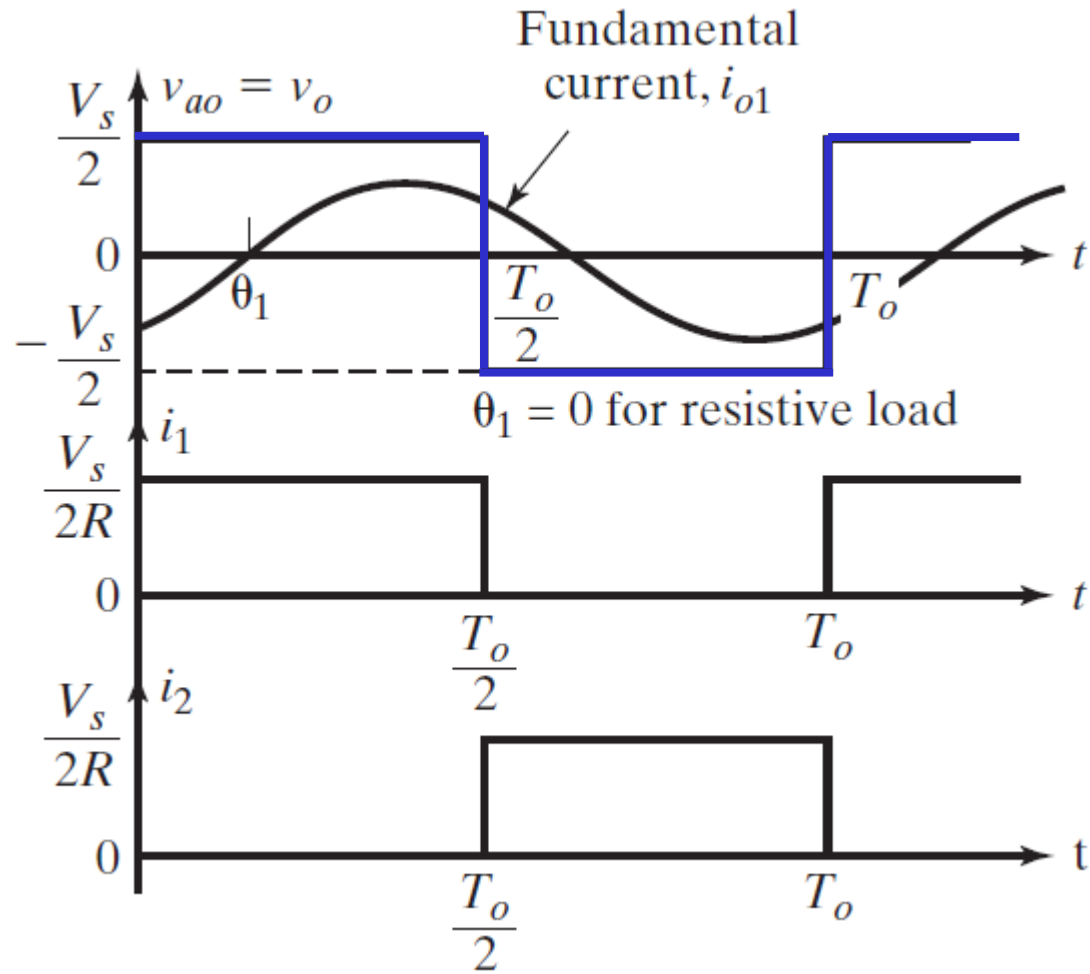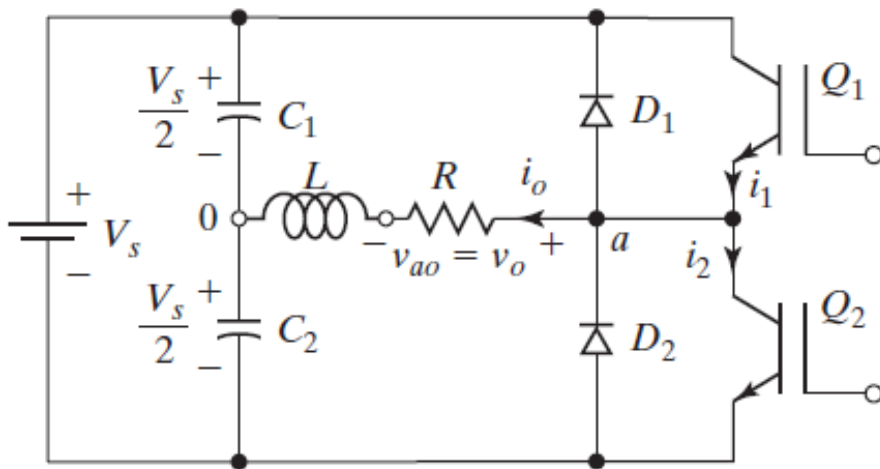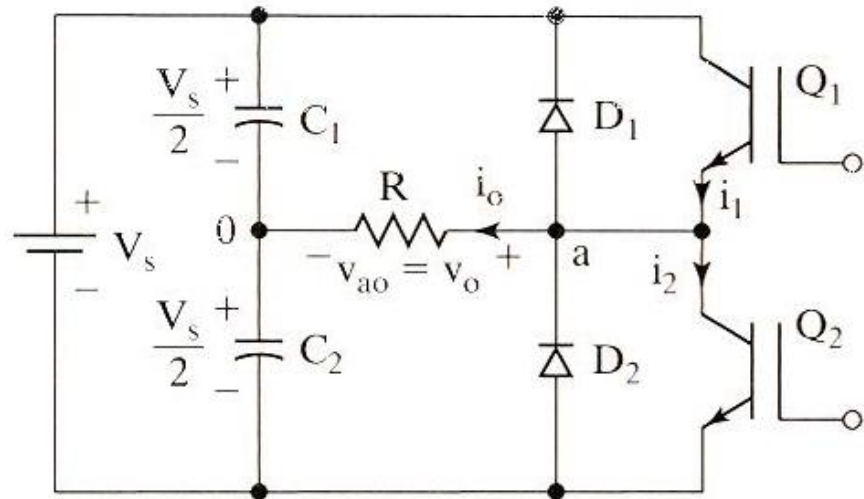


Waveforms of output voltage & transistor currents with resistive load

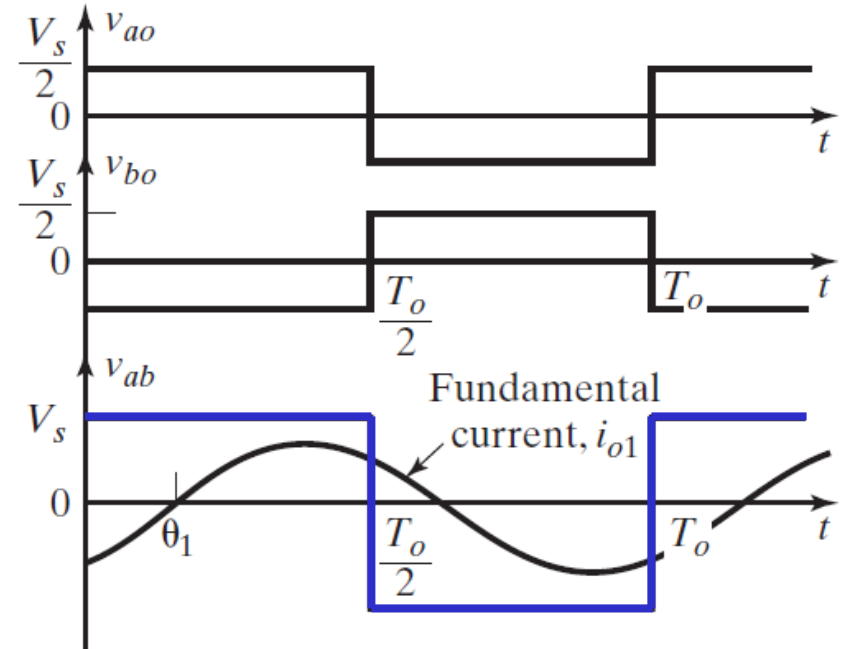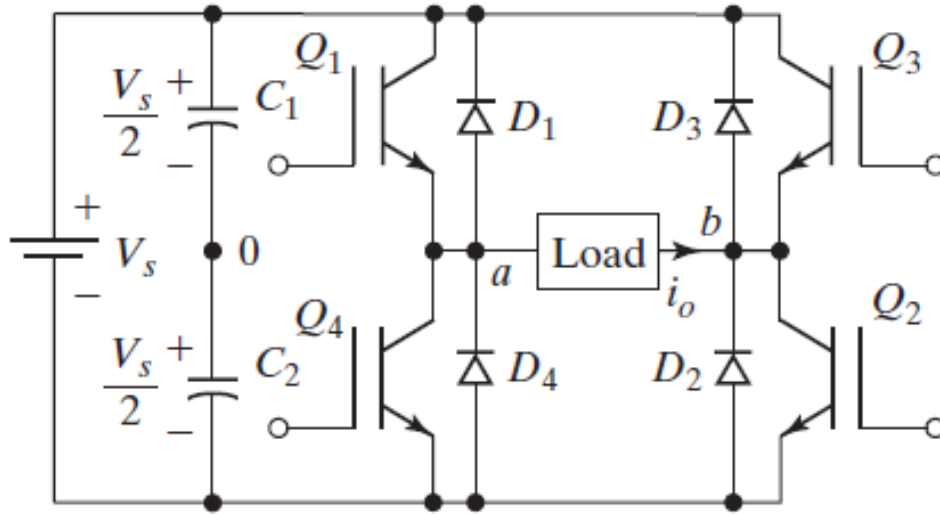Lecture 8: Single-phase full(H)-bridge VSI



- Consists of 4 choppers – 1) When Q_1 & Q_2 are turned ON simultaneously, V_s appears across the load, 2) If Q_3 & Q_4 are turned ON simultaneously, $-V_s$ appears across the load.
- When the load is highly inductive, the current waveform is triangular.
- The RMS output voltage is,

$$V_o = \left(\frac{2}{T_o} \int_0^{T_o/2} V_s^2 dt \right)^{1/2} = V_s$$

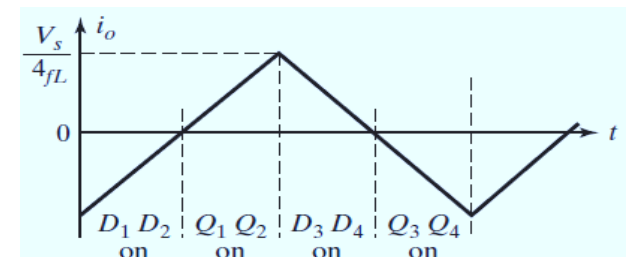

Lecture 8: Types of DC Motors


- Two types depending on type of field winding connections:
 - **Shunt:** field excitation is independent of armature circuit
 - controlled independently (*separately excited motor*)
 - armature and field currents are different
 - **Series:** the field excitation is in series with the armature
 - armature and field currents are same

Lecture 8: Separately Excited DC Motor

- When *excited* by a field current (i_f) and an armature current of i_a flows in the circuit, the *motor develops* a back *EMF* & a *torque* to balance the load torque at particular speed of motor.
- The i_f is *independent* of i_a and any change in one of them would not affect other current. Normally, $i_f \ll i_a$.
- Instantaneous field current i_f is described as

$$v_f = R_f i_f + L_f \frac{di_f}{dt}$$

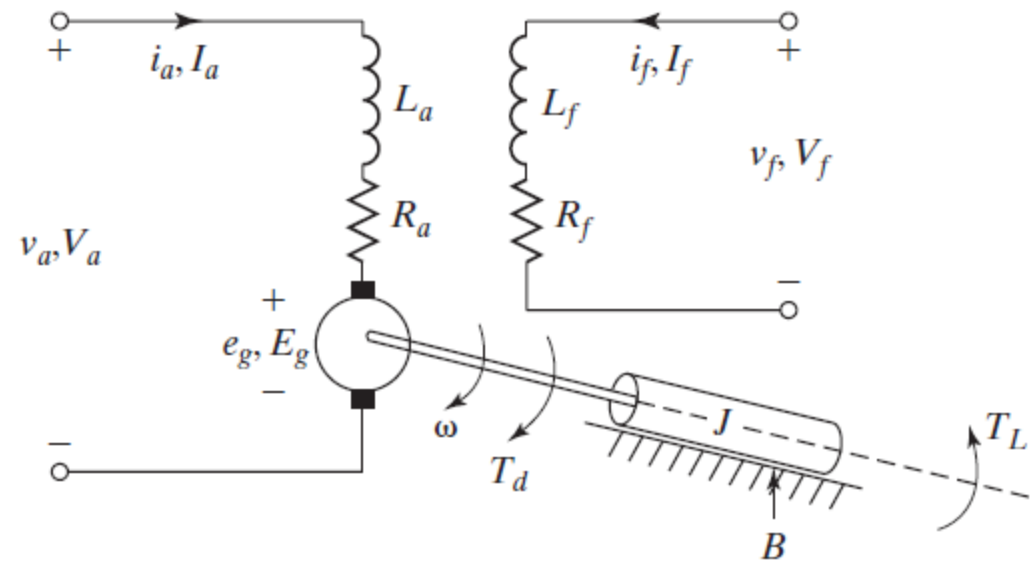- Instantaneous armature current can be found from, $v_a = R_a i_a + L_a \frac{di_a}{dt} + e_g$
- The motor back emf (or *speed voltage*) is, $e_g = K_v \omega i_f$



Equivalent circuit

Lecture 8: Series Excited DC Motor

- The field circuit is designed to carry the armature current. The steady-state quantities:
- The motor back emf is, $E_g = K_v \omega I_a$
- Instantaneous armature current can be found:


$$V_a = (R_a + R_f)I_a + E_g = (R_a + R_f)I_a + K_v \omega I_f$$
- The torque developed by the motor,

$$T_d = K_t I_f I_a = B\omega + T_L$$

- The speed of a series motor can be found as


$$\omega = \frac{V_a - (R_a + R_f)I_a}{K_v I_f}$$

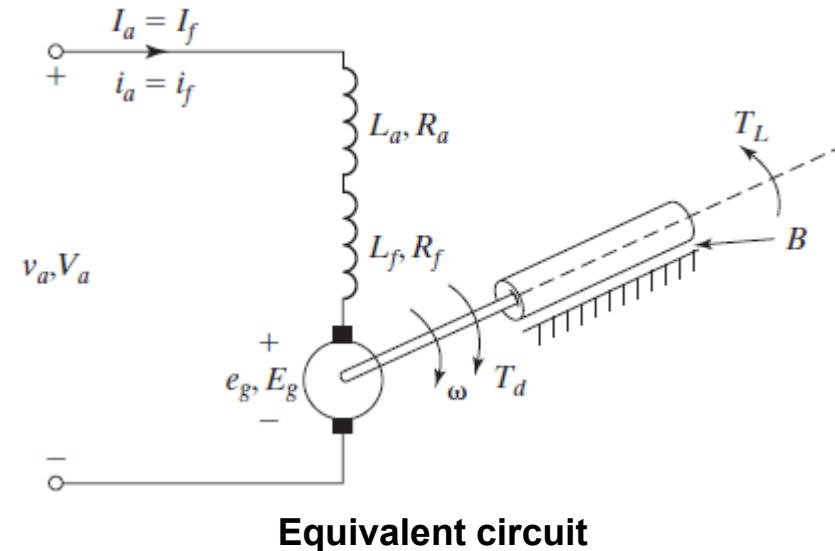- The speed can be varied by controlling the 1) armature voltage; or 2) armature current, which is a measure of the torque demand.
- Series motor can provide a high torque, especially at starting – commonly used in traction applications.



Guidelines – Final Exam

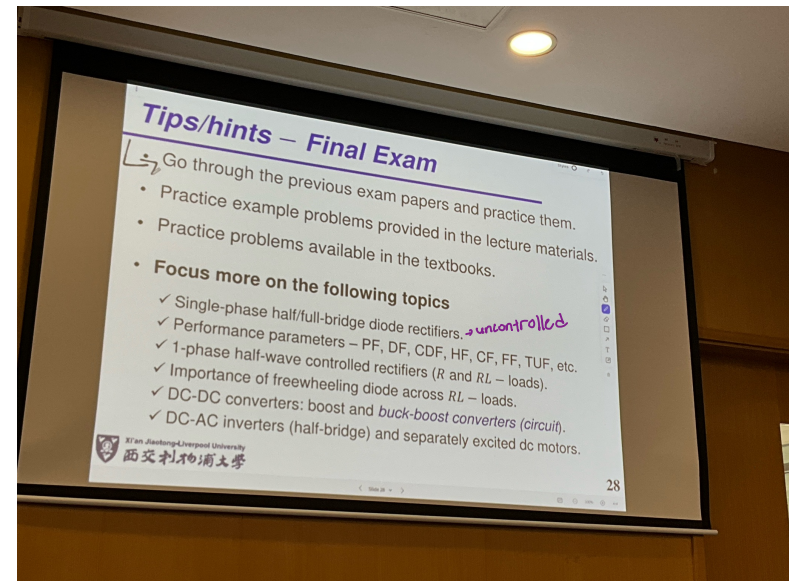- *Exam date:* **27th May 2025 (Tuesday) @10:00 AM**
- *Exam duration:* **2 hrs**
- *Exam venue:* **ESG09**
- *Format:* **Onsite**



You may need to write about the buck-boost circuit or output expression. There won't be any exercise problems on buck-boost converter tested in the exam



See you in the final exam

- Hope you got *some knowledge* from this module.
- All the best for final exam.
- NO formulae sheet is provided in the final exam.

The End