

Lecture 13
of
EEE201

CMOS Digital Integrated Circuits

Department of Electrical & Electronic Engineering
Xi'an Jiaotong-Liverpool University (XJTLU)

Monday, 9th December 2024

❑ Ratioed Logic

- pull-up network replaced by a load
- pseudo-NMOS

❑ Dynamic Logic & Domino Logic


- precharge & evaluation phases



Combinational Logic Circuits

(pull-up & pull-down networks)

 - ❑ In CMOS technology, a **combinational logic circuit** consists of basically a **pull-up network (PUN)** and a **pull-down network (PDN)**.
 - The **PUN** consists of only **PMOS** transistors while **PDN** only **NMOS** transistors.




- In the steady state, either the PUN provides a low-resistance path to connect the output (F) to V_{DD} or the PDN make a low-resistance connection between the output and ground (or V_{SS}), hence *pulling up* or *down* the output voltage.

NMOS Combinational Logic Circuits

(pull-up network replaced with a load device)

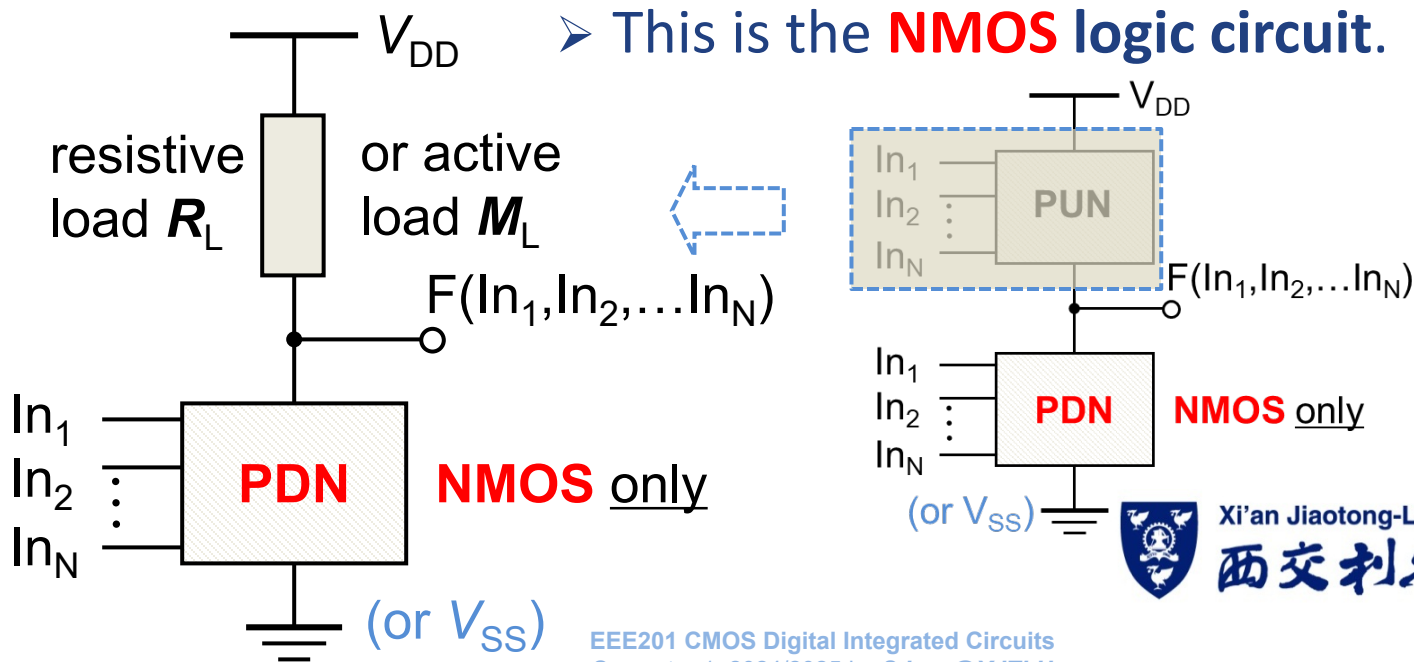- Before CMOS technology became mature, only one type of MOS transistors was available for implementation of digital integrated circuits. The **pull-down network (PDN)** consists of only **NMOS transistors** but the **PUN** is *replaced* by either a **resistive load** or an NMOS transistor as an active load.




Xi'an Jiaotong-Liverpool University
西交利物浦大學

NMOS Combinational Logic Circuits

(pull-down network fights with load device)

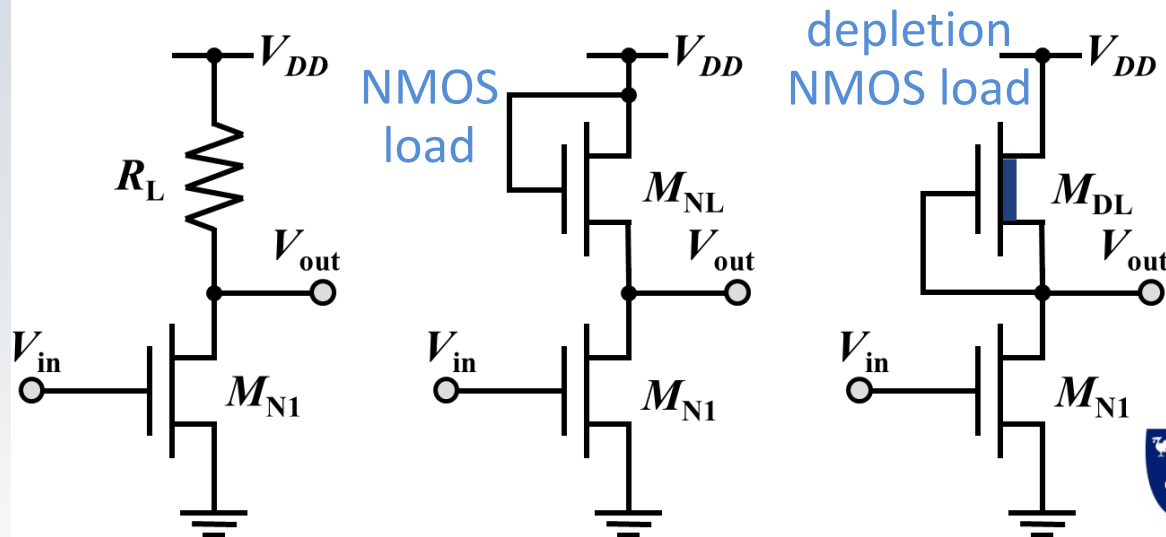- ❑ In the **NMOS** logic circuits, when the **pull-down network** turns on, it “fights” with the resistive or active load to pull down the output voltage.
 - The **equivalent load resistance** should be high enough so that the NMOS **pull-down network** can pull down the output to an acceptably low logic “0” voltage V_{OL} .



- This can be understood with the VTC of the simple NMOS inverter.





Xi'an Jiaotong-Liverpool University
西交利物浦大学

VTC of NMOS Inverters

(pull-down NMOS transistors fights with load device)

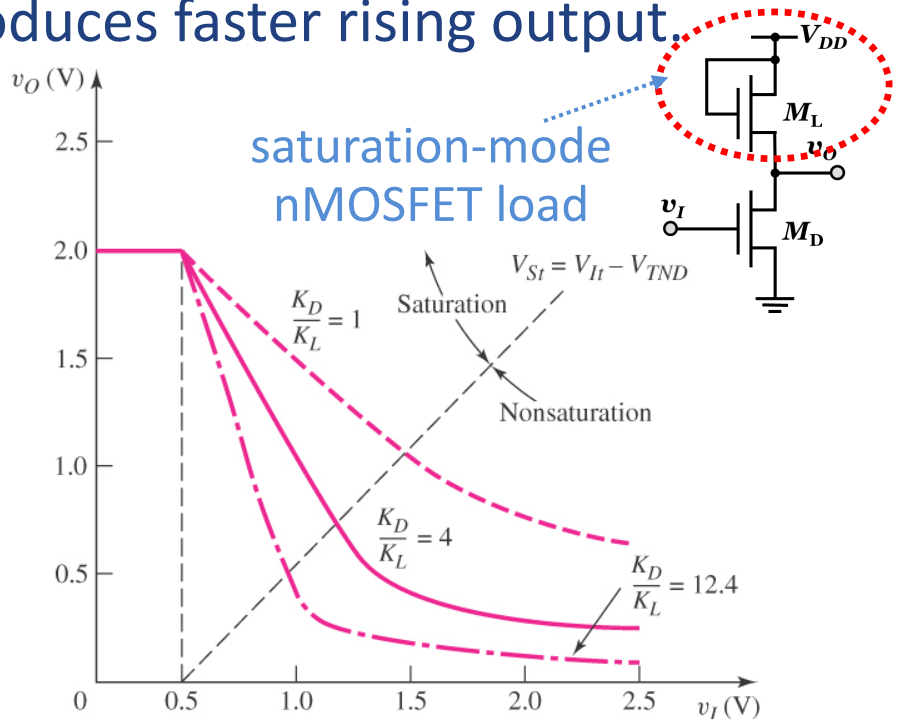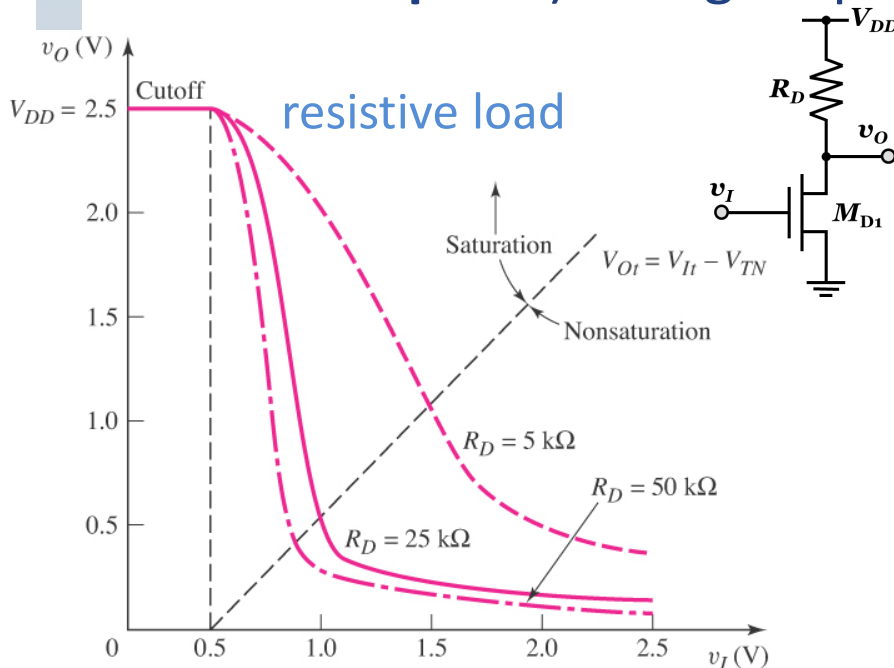- ❑ A lower **equivalent** load resistance gives higher V_{OL} and hence degrading the **noise margin** NM_L (also static **power consumption**) though it produces faster rising output



From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition, © 2010 McGraw-Hill, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大學


VTC of NMOS Inverters

(depletion load with negative V_{TN})

 - In the case of using a depletion-mode nMOSFET as the load device, VTC are better for certain gain factor (K_D , K_L) ratios.



 
depletion load with negative threshold voltage V_{TNL}



Ratioed Logic Circuits

(ratioed load resistance or transistor size)

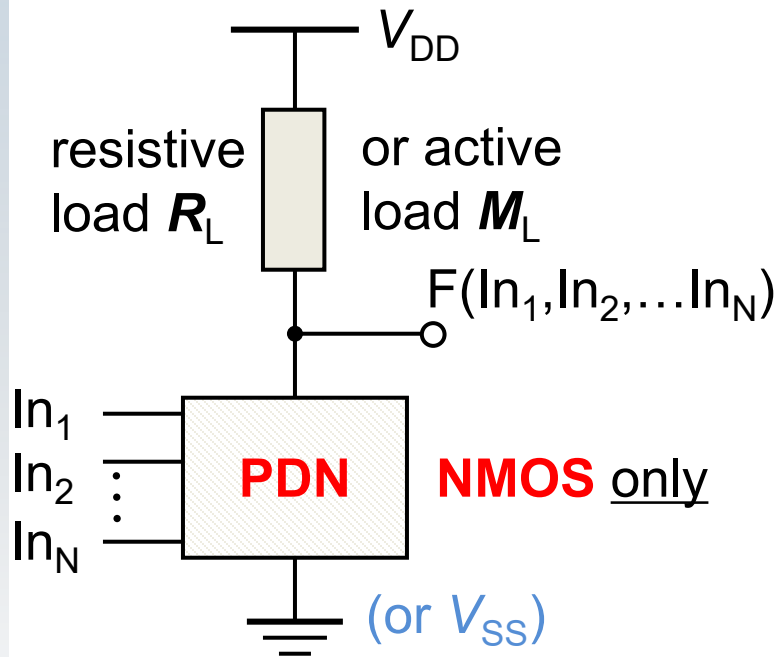- ❑ With the static load, the proper operation of the **NMOS** logic circuits depends on the appropriate load resistance R_L or transistor size (i.e. W/L).






- ❑ Typically, the static load is a MOSFET. Its size and that of those NMOS transistors in the pull-down network (PDN) have a **ratio** constraint.
- ❑ Such logic circuits are called ratioed logic, with the logic function performed solely by the PDN.

Ratioed Logic Circuits

(examples other than inverter)

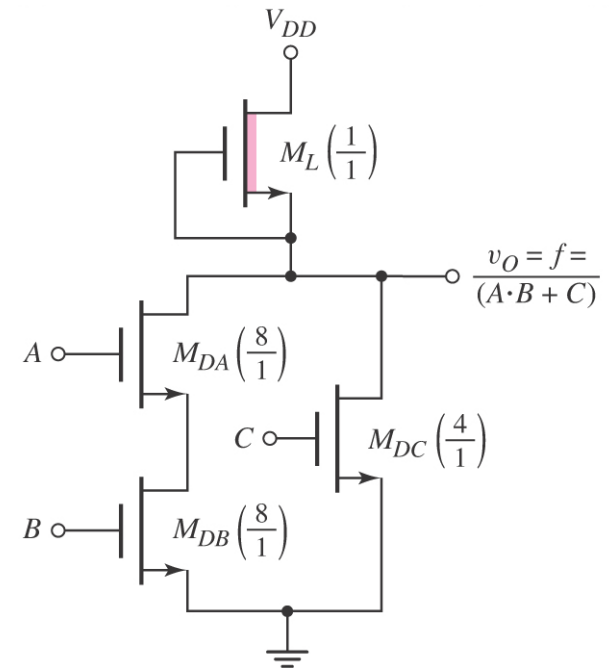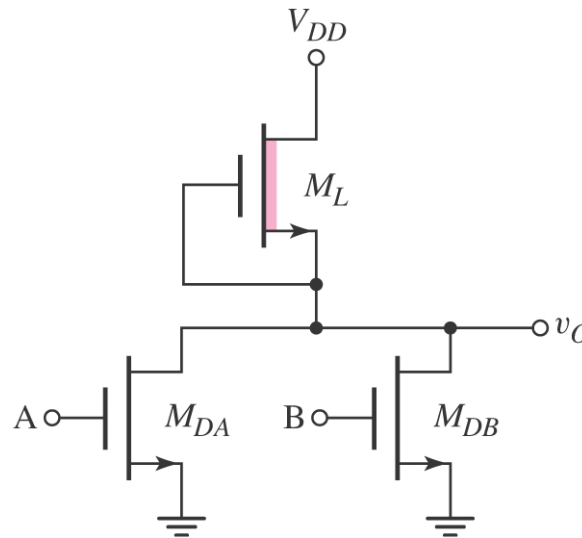 - Examples of ratioed logic have more than one NMOS transistors in the pull-down network (instead of one nMOSFET in the inverter).



From: Donald A. Neamen, *Microelectronics: Circuit Analysis & Design*, 4th edition, © 2010 McGraw-Hill, USA.

Ratioed Logic Circuits

(disadvantages compared with CMOS)

- ❑ **Ratioed logic** is generally not as good as CMOS logic circuits:
 - It is less **robust** (in terms of fabrication variation from the components' nominal values and circuit operation), with a simple load device replacing the PUN which provides a conditional path between V_{DD} and the output when the PDN is turned off.
 - **Static power dissipation** in **ratioed logic** may not be acceptable when the number of logic gates increases; (think about 10 mA static current in each logic gate and there are 10k logic gates).
 - $V_{OL} > 0$ (hence $NM_L = V_{IL} - V_{OL}$ decreases) in **ratioed logic** circuit while CMOS has $V_{OL} = 0$.

Ratioed Logic Circuits


(less transistors & input capacitance)

- ❑ Despite the disadvantages compared with CMOS logic, **ratioed logic** is used in some special applications.
- ❑ **Ratioed logic** can be used to achieve certain purposes:
 - It reduces the number of transistors required to implement a given logic function.
 - If there are N inputs in a logic circuit, ratioed logic requires only $N+1$ MOSFETs but CMOS requires $2N$.
 - It reduces the input capacitances of the logic gates as pMOSFETs typically have much larger transistor size than nMOSFETs in CMOS logic and hence contributing much to the input capacitance. As a result, ratioed logic circuits can have a faster switching speed.


Ratioed Logic Circuits

(4-input NAND gate example)

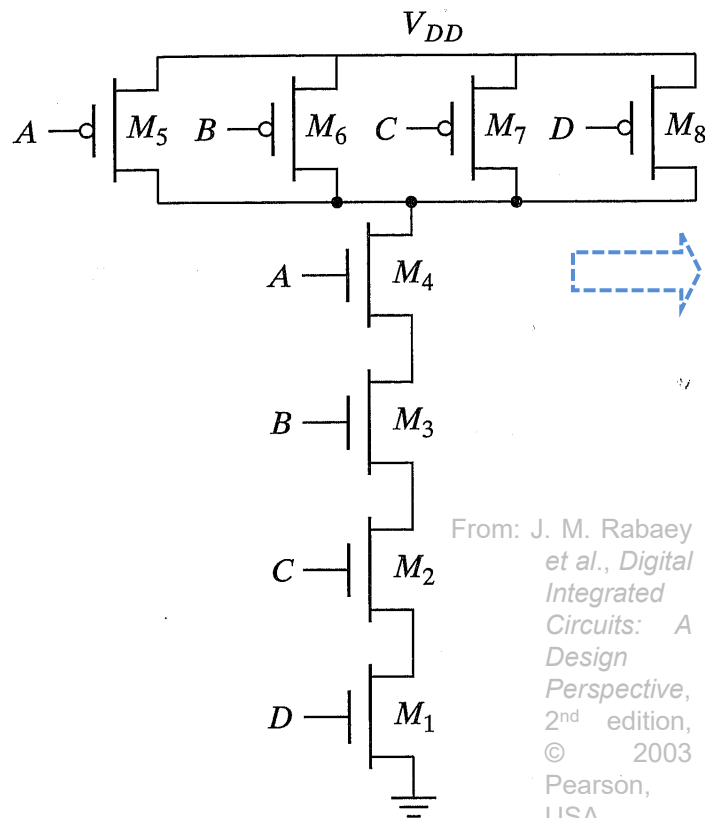- ❑ The reduced number of MOSFETs can be seen in an example of a four-input NAND gate.



 From: J. M. Rabaey
et al., *Digital
Integrated
Circuits: A
Design
Perspective*,
2nd edition,
© 2003
Pearson,
USA.




- 4 inputs require only 5 MOSFETs in ratioed logic but 8 in CMOS.
- Imagine the layout of the 4-input NAND gate and the chip area saved in replacing the 4-transistor PUN with one pMOSFET.

Ratioed Logic: pseudo-NMOS

(implemented in CMOS technology)

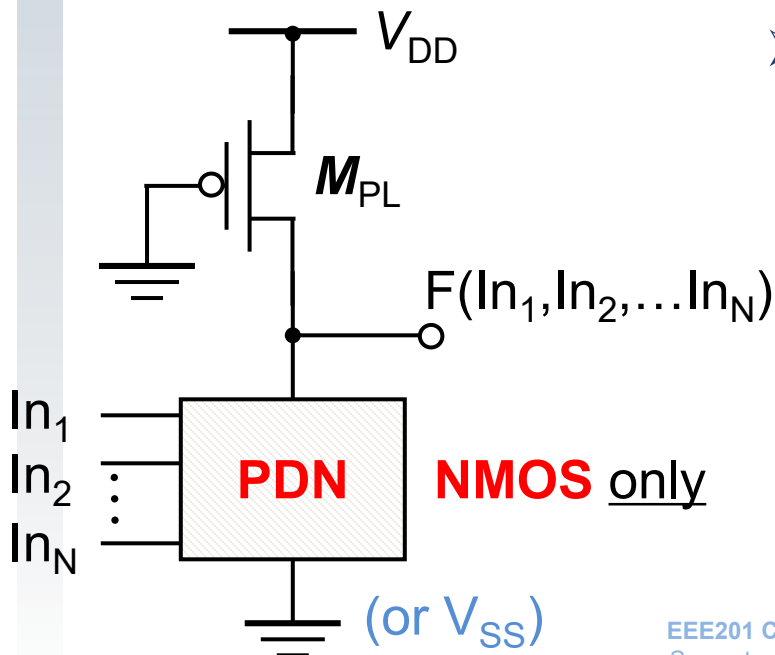- ❑ **Ratioed logic** can be implemented in CMOS technology with a pMOSFET as the load device replacing the PUN.
 - The gate of pMOSFET as the load device is grounded (or connected to the negative power supply V_{SS}).
- ❑ Such **ratioed logic** is referred to as **pseudo-NMOS** logic.




- As expected in **ratioed logic**, the size of the pMOSFET relative to that of the nMOSFETs in the PDN can be used to trade off parameters such as **noise margin**, **propagation delay**, and **power dissipation**.

Ratioed Logic: pseudo-NMOS

(pseudo NMOS inverter)

- ❑ The performance trade-off in the **pseudo-NMOS** logic can be seen in the simple case of a pseudo-NMOS inverter.

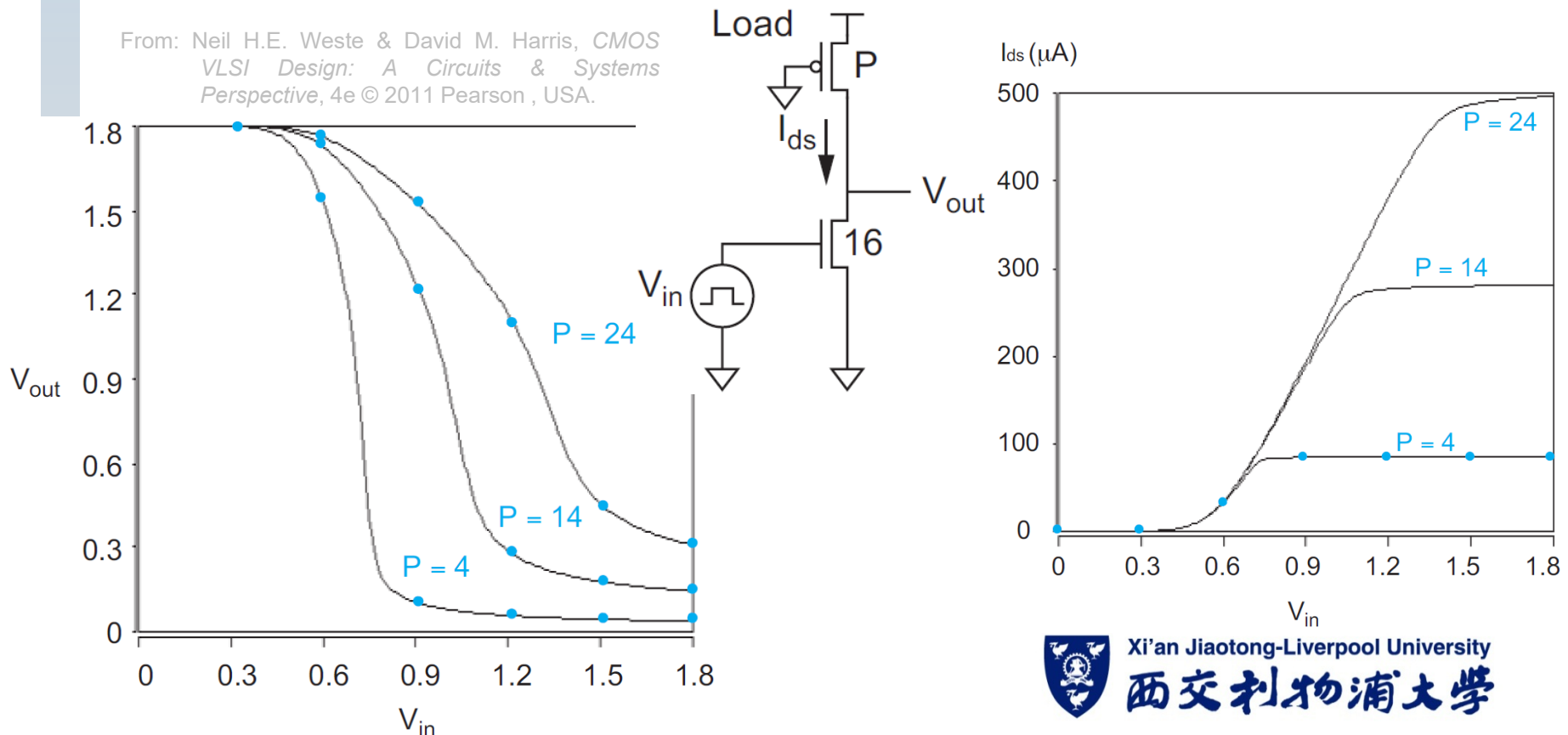From: Neil H.E. Weste & David M. Harris, *CMOS VLSI Design: A Circuits & Systems Perspective*, 4e © 2011 Pearson, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Ratioed Logic: pseudo-NMOS

(pseudo NMOS inverter)

 - In a pseudo-NMOS inverter, the size of nMOSFET is $0.5\mu\text{m}/0.25\mu\text{m}$.






$(W/L)_p$	V_{OL} (V)	Static Power Dissipation (μW)	t_{pLH} (ps)
4	0.693	564	14
2	0.273	298	56
1	0.133	160	123
0.5	0.064	80	268
0.25	0.031	41	569

➤ **trade-off** between power dissipation & propagation delay (hence speed)

Pseudo-NMOS to Dynamic Logic

(overcoming static power dissipation)

   
- ❑ The drawbacks (especially the static power dissipation) of **pseudo-NMOS** can be overcome by using a clocked pull-up transistor rather than a pMOSFET that is always on.
 - Logic circuits with a clocked pull-up device are referred to as **dynamic logic**.
 - The idea can be illustrated using the inverter case.




Dynamic Logic – precharge mode

(precharge & evaluation modes)

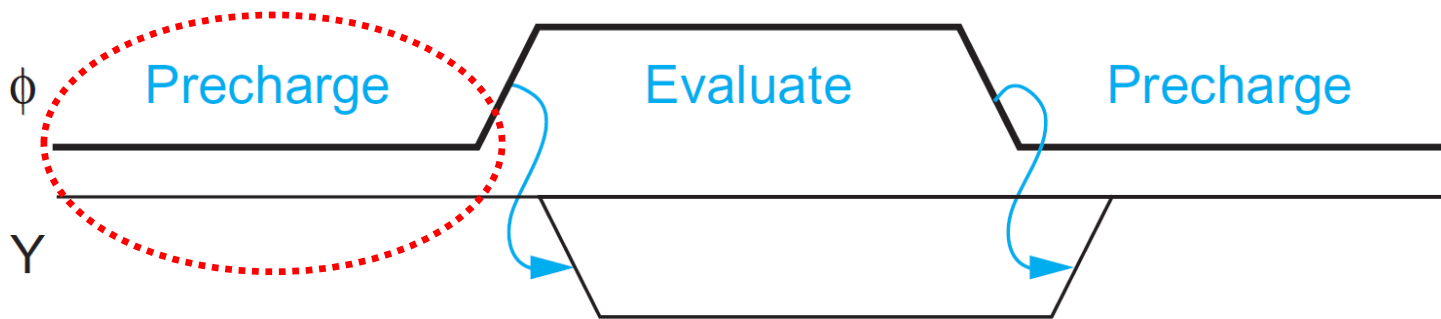- ❑ The operation of the **dynamic inverter** is divided into two modes (or phases): **precharge** and **evaluation**, in sequence.
 - The operation mode is determined by the clock input ϕ .



 - During the **precharge** mode (i.e. when the clock ϕ is “0”), the clocked pMOSFET turns on and the output Y is **precharged** to V_{DD} .




From: Neil H.E. Weste & David M. Harris, *CMOS VLSI Design: A Circuits & Systems Perspective*, 4e © 2011 Pearson, USA.



Xi'an Jiaotong-Liverpool University
西交利物浦大學


Dynamic Logic – evaluation mode

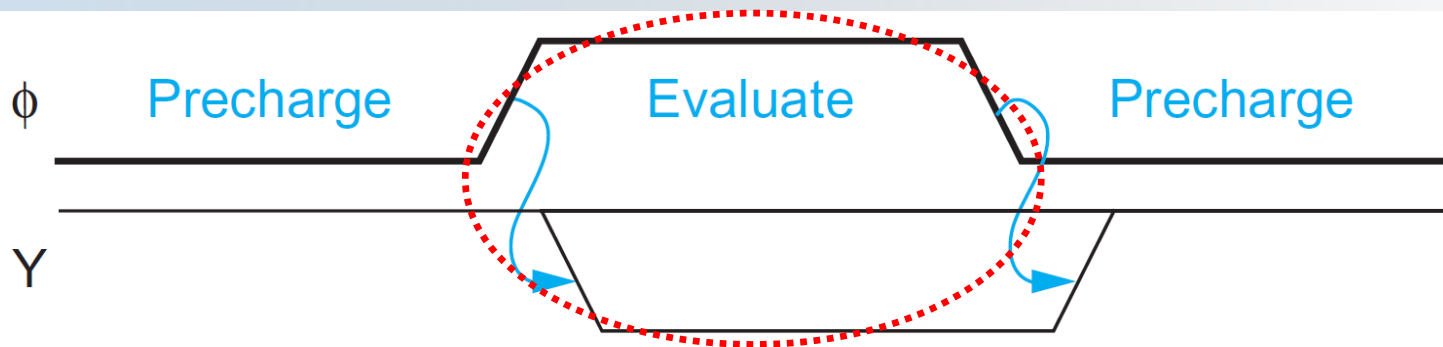(no static power dissipation in evaluation mode)



- During the **evaluation** mode (i.e. when the clock ϕ is “1”), the clocked pMOSFET turns off and the output Y may remain at V_{DD} or may be discharged to “0” through the pull-down network (an nMOSFET in the inverter case).

 - As the clocked pMOSFET turns off during the **evaluation** mode, there is no static power dissipation in this mode whatever the input A is.



From: Neil H.E. Weste & David M. Harris, *CMOS VLSI Design: A Circuits & Systems Perspective*, 4e © 2011 Pearson, USA.





Xi'an Jiaotong-Liverpool University
西交利物浦大學

Dynamic Logic – precharge mode

(contention in pulling up & down)

  - ❑ With only the pull-up pMOSFET clocked, there can be problems during the **precharge** mode:
 - if the input A is “1” hence the pull-down nMOSFET turns on, both the pMOSFET and nMOSFET are on and contention will take place between them (i.e. the two MOSFETs fight to pull up or down the output voltage).




From: Neil H.E. Weste & David M. Harris, *CMOS VLSI Design: A Circuits & Systems Perspective*, 4e © 2011 Pearson, USA.

Dynamic Logic – precharge mode

(extra clocked evaluation transistor)

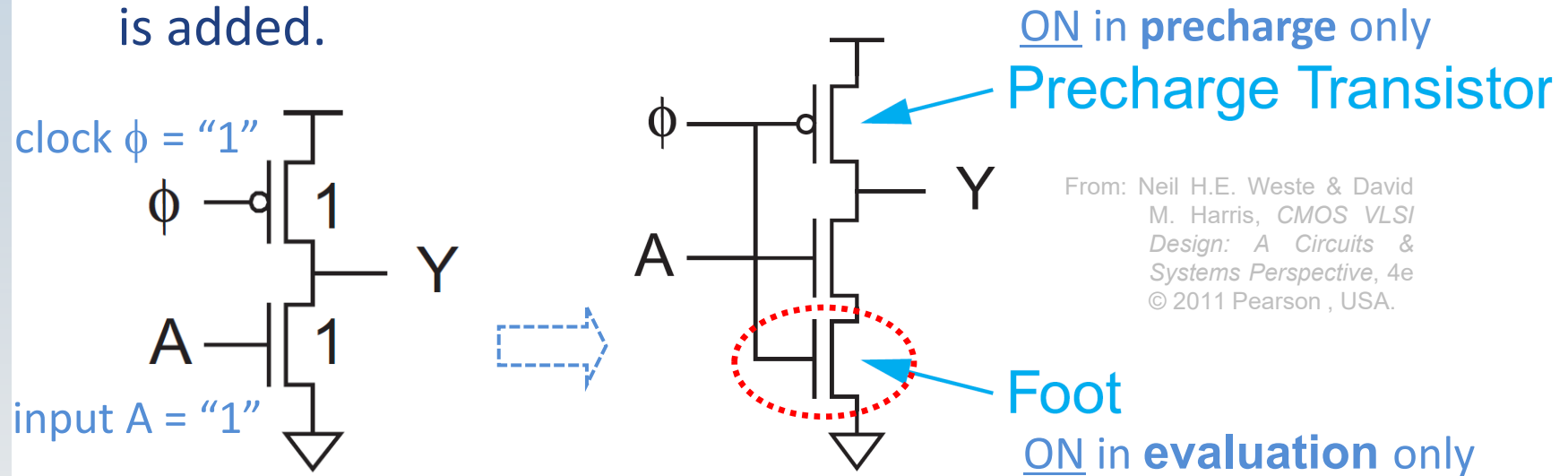- ❑ To avoid such a contention situation that both pull-up and pull-down MOSFETs turn on, an extra **evaluation** transistor is added.



- The extra **clocked** transistor is an nMOSFET stacked under the pull-down network (one nMOSFET in the inverter case). It is sometimes called a **foot**.


Dynamic Logic

(footed & unfooted logic gates)


- Examples of dynamic logic gates with the extra clocked MOSFET is shown below:

unfooted
logic gates


inverter

 

2-input NAND gate



 


2-input NOR gate

 

From: Neil H.E. Weste & David M. Harris, *CMOS VLSI Design: A Circuits & Systems Perspective*, 4e © 2011 Pearson, USA.

footed
logic gates

   


Xi'an Jiaotong-Liverpool University
西交利物浦大學

Dynamic Logic

(footed & unfooted logic gates)

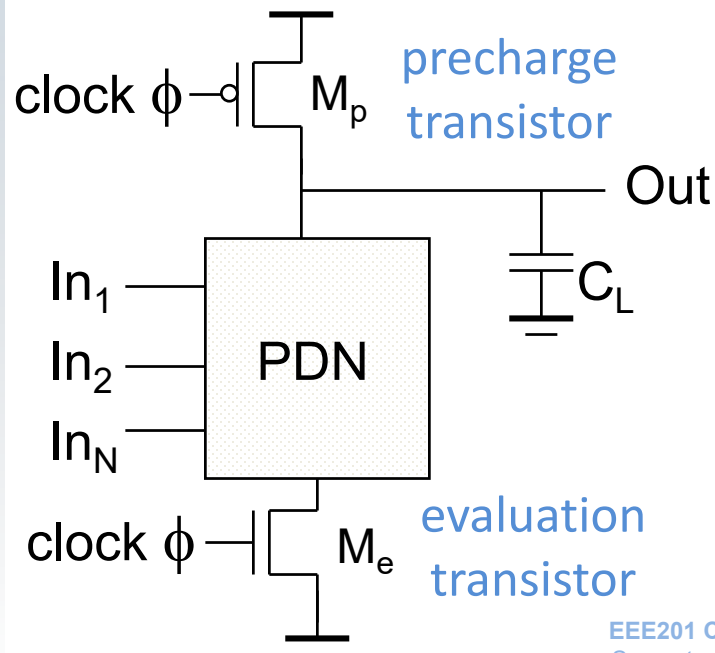- ❑ In general, a **dynamic logic** circuit consists of three parts stacked on one another:
 - a **clocked pMOSFET** (called a precharge transistor);
 - a **pull-down network** (PDN) of nMOSFETs for performing logic function; it is exactly the same as that in CMOS logic;



- a **clocked nMOSFET** (called a foot or evaluation transistor).
- The number of MOSFETs required for implementing a logic circuit of N inputs is $N+2$ which is generally smaller than $2N$ in CMOS logic.

Dynamic Logic

(important properties)

- ❑ Several important properties can be derived for the **dynamic logic**:
 - It is non-ratioed: the size of the precharge pMOSFET is not important for the correct operation of the logic gates; the size of the pMOSFET can be made large to improve the low-to-high transition time (but at a cost to the high-to-low transition time).
 - It consumes only **dynamic power**. Ideally, there is no static current path exists between V_{DD} and the ground.
 - The logic gates have faster **switching speed**, due to the reduced input capacitance of the logic gates (with less MOSFETs per gate).
 - V_{OL} is ground (or V_{SS}) & $V_{OH} = V_{DD}$.



Xi'an Jiaotong-Liverpool University


西交利物浦大學

Dynamic Logic


(monotonicity problem)

- ❑ Despite the apparent advantages (especially the faster switching speed and zero static power dissipation) of the **dynamic logic**, it suffers from monotonicity problem:
 - During evaluation, the inputs must be monotonically rising; they cannot start “1” and fall to “0”.

 From Neil H.E. Weste & David M. Harris, *CMOS VLSI Design: A Circuits & Systems Perspective*, 4e © 2011 Pearson, USA.



$A = 1$

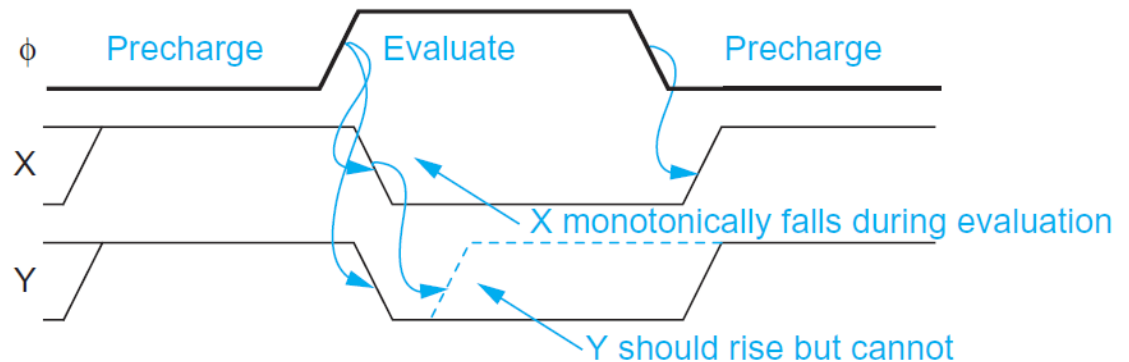


- The problem can be seen in cascaded dynamic logic gates.

Domino CMOS Logic

(monotonicity problem)

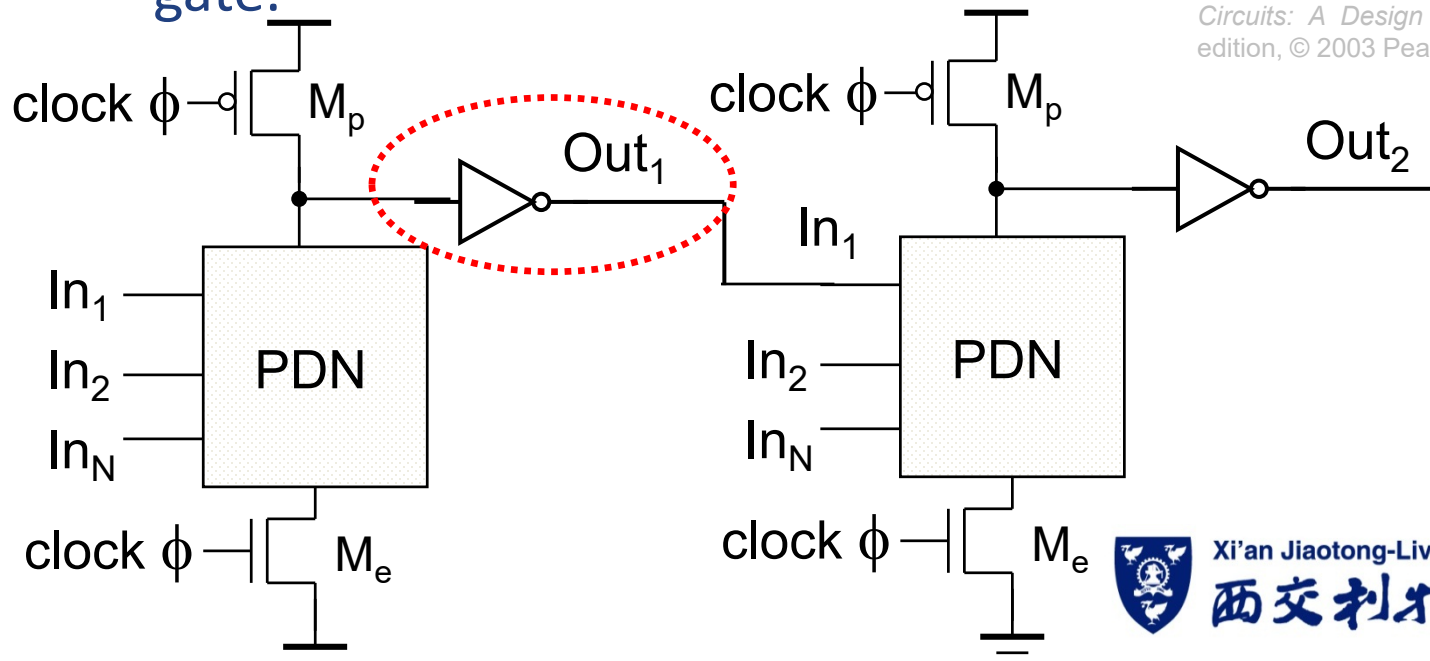- ❑ The monotonicity problem in the **dynamic logic** can be resolved by placing a static CMOS inverter between the dynamic logic gates.
 - The **dynamic-static pair** together is called a **domino logic gate**.



From: J. M. Rabaey et al., *Digital Integrated Circuits: A Design Perspective*, 2nd edition, © 2003 Pearson, USA.





Xi'an Jiaotong-Liverpool University
西交利物浦大学

Domino CMOS Logic

(like dominoes tipping over)

- ❑ The name domino logic derives from the fact that precharge resembles setting up a chain of dominoes and evaluation causes the logic gates to fire like dominoes tipping over, each triggering the next.

 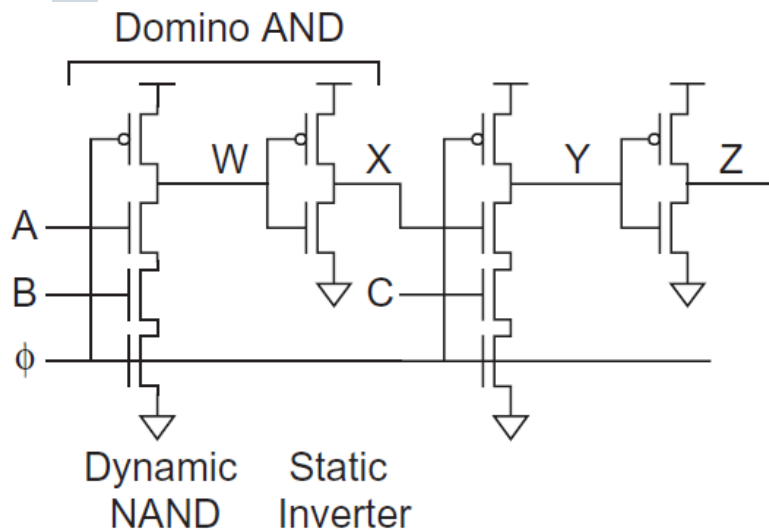From: Neil H.E. Weste & David M. Harris, *CMOS VLSI Design: A Circuits & Systems Perspective*, 4e © 2011 Pearson, USA.




- This can be illustrated using a two cascading domino AND gates.

Pseudo-NMOS to Dynamic Logic

(comparisons with CMOS logic)

 - ❑ The **domino logic** is developed from **dynamic logic** which is in turn from pseudo-NMOS (which is ratioed logic and has static power dissipation problems).
 - Their comparisons can be seen using a 2-input NAND gate.



From: D.A. Hodges et al., *Analysis and Design of Digital Integrated Circuits: In Deep Submicron Technology*, 3rd edition, © 2003 McGraw Hill, USA.



Xi'an Jiaotong-Liverpool University
西交利物浦大學