

Capacitors and Inductors

EEE103 ELECTRICAL CIRCUITS (Part 2)
Week 6
S1, 2022/23

Lecturer: Xuchen Wang
Xuchen.Wang@xjtlu.edu.cn



Content

- Voltage-current relationship of an ideal capacitor
- Current-voltage relationship of an ideal inductor
- Calculating energy stored in capacitors and inductors
- Series and parallel combinations
- Op amp circuits with capacitors



Active and passive elements


- An **active element** is an element that is capable of supplying an average power greater than zero to some external device over an infinite time interval (e.g. Ideal sources, the operational amplifier, the transistor)
- A **passive element** is defined as an element that cannot supply an average power greater than zero over infinite time interval. (e.g. the resistor, **more?**)

Capacitor and Inductors



The Capacitor

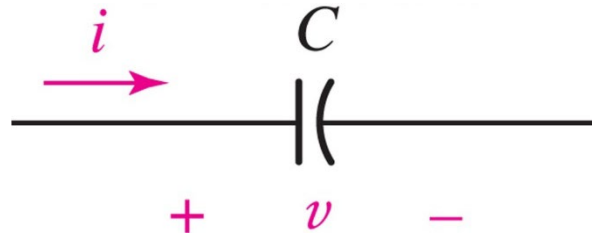- The ideal capacitor is a passive element with circuit symbol



- The current-voltage relation is

$$i = C \frac{dv}{dt}$$

- Capacitance C is measured in ampere-second per volt or coulomb per volt or **farad (F)**.





Example capacitors

- Capacitors vary in size depending on capacitance and voltage tolerance
- Typical values range from pF to μF



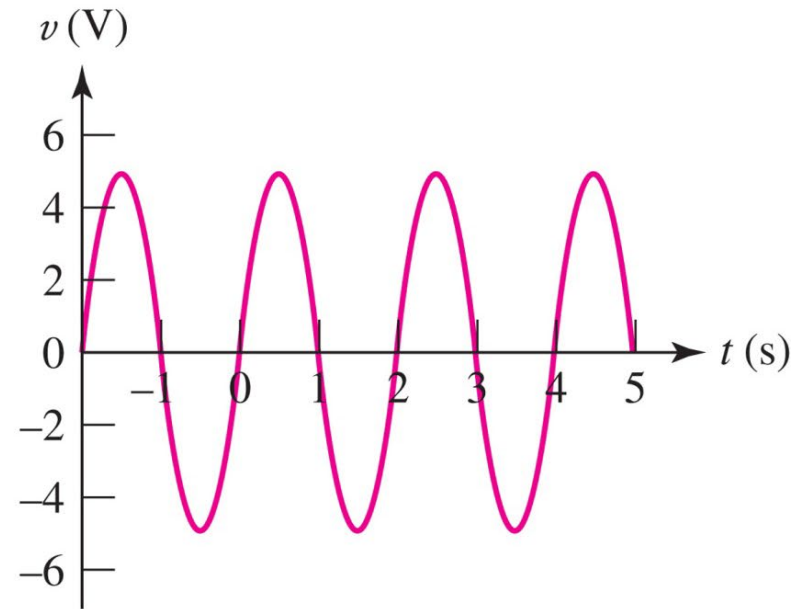
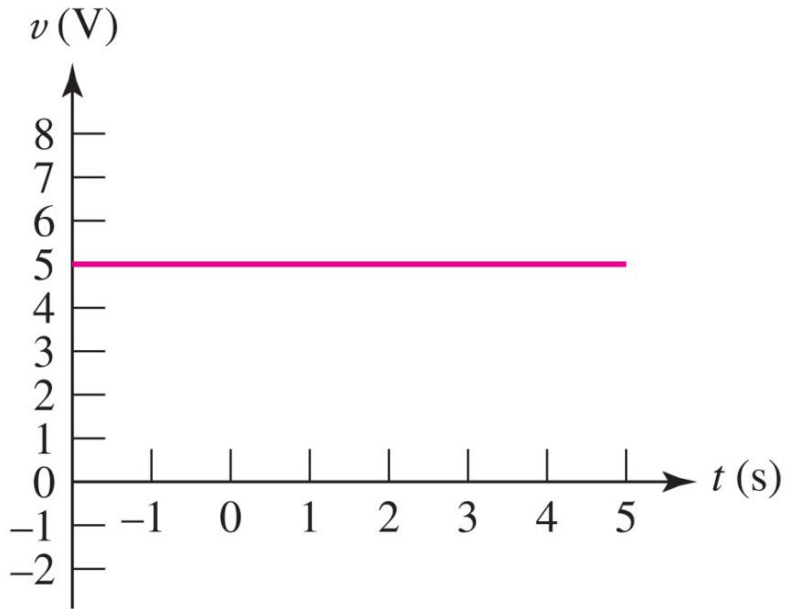
Example 1

Find $i(t)$ for the voltages shown, if $C = 2F$.



Solution to Example 1

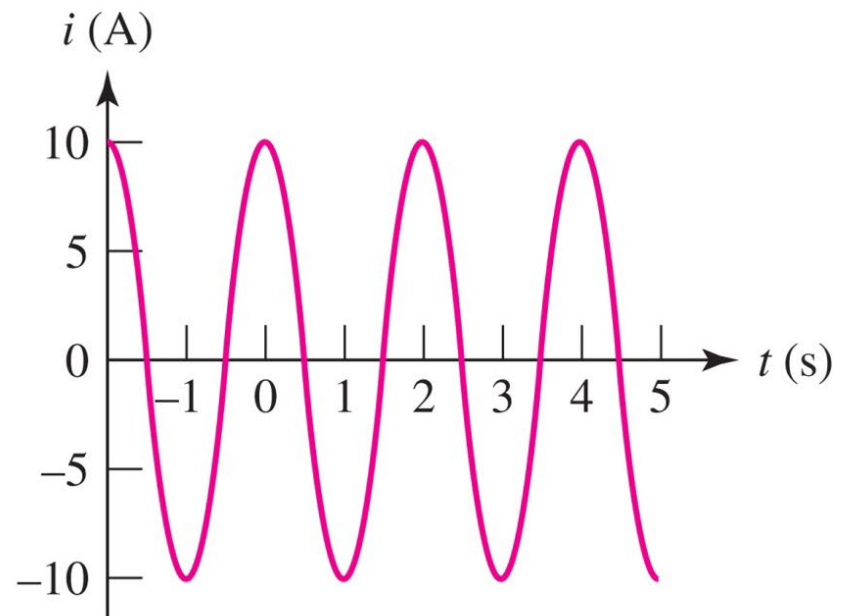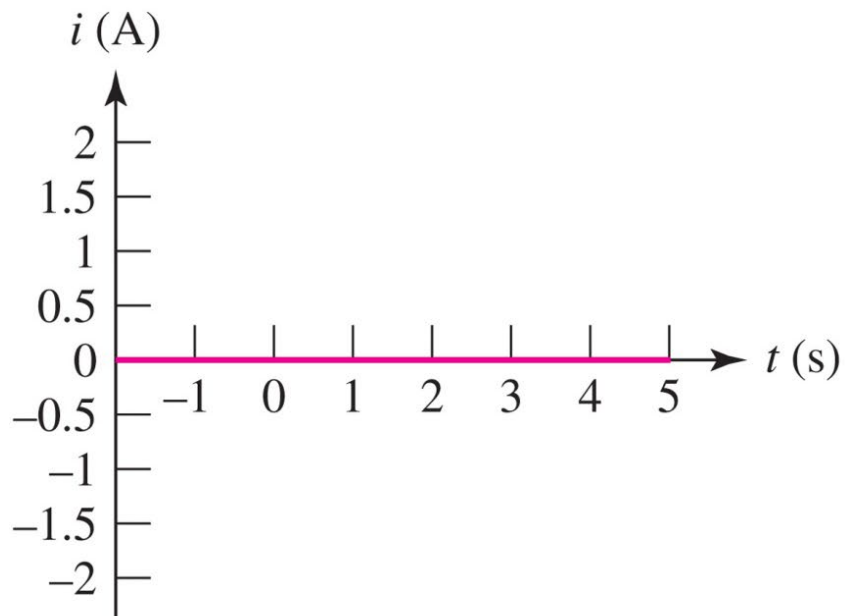Apply $i(t) = 2 \frac{dv}{dt}$ and graph:



Key capacitor behaviors

- A constant voltage across a capacitor results in zero current passing it; thus capacitors are “open circuits” to constant dc voltages.
- A sudden jump in the voltage requires an infinite current, which is physically impossible. Therefore the voltage on a capacitor cannot jump.

$$i = C \frac{dv}{dt}$$



Integral Voltage-Current relationships

- The capacitor voltage-current relationship

$$i = C \frac{dv}{dt} \quad [1]$$

- Integrating Eq.[1], we first obtain

$$dv = \frac{1}{C} i(t) dt \quad [2]$$

- Then integrate between times t_0 and t and between corresponding voltages $v(t_0)$ and $v(t)$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t') dt' + v(t_0) \quad [3]$$

- Eq.[3] may also be written as an indefinite integral plus a constant of integration:

$$v(t) = \frac{1}{C} \int i dt + k \quad [4]$$



Integral Voltage-Current relationships

- Finally, in many situations the voltage initially across the capacitor cannot be discerned. Thus set $t_0 = -\infty$ and $v(-\infty) = 0$, so that

$$v(t) = \frac{1}{C} \int_{-\infty}^t i dt' \quad [5]$$


- According to Eq.[5], the charge accumulated on the capacitor plate can be represented as:

$$q(t) = Cv(t) \quad [6]$$



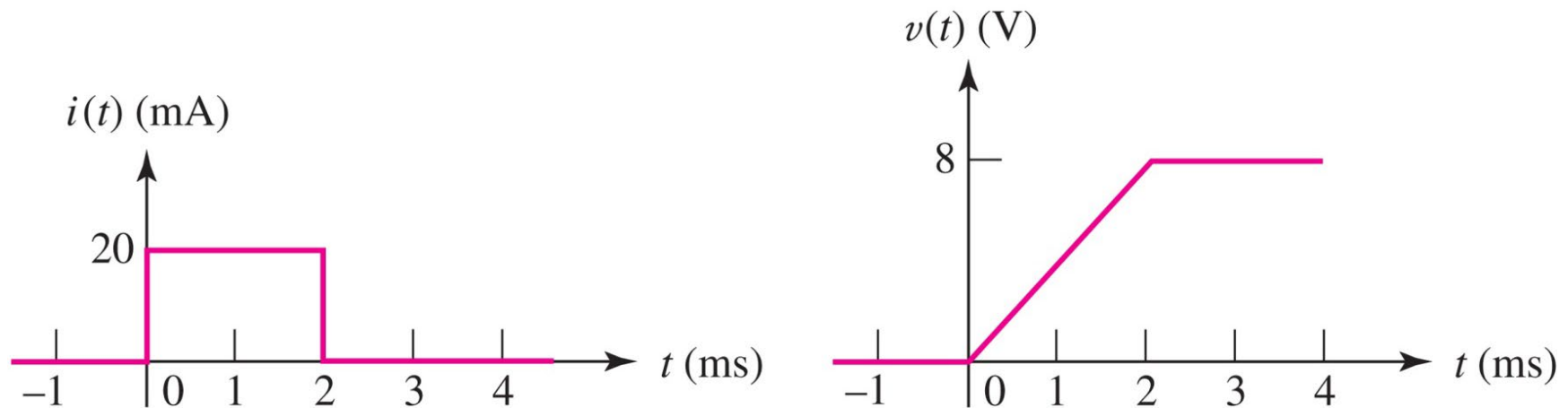Example 2

Show that the following graphs are matching voltage and current graphs for a capacitor of $C = 5\mu F$.




Solution:

$$v(t) = \begin{cases} 0, & t \leq 0 \text{ ms} \\ 4000t, & 0 \leq t \leq 2 \text{ ms} \\ 8 & t > 2 \text{ ms} \end{cases}$$



The inductor

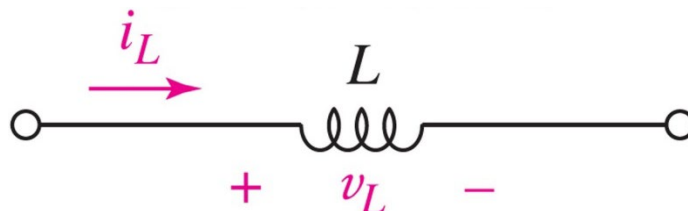- The ideal inductor a passive element with circuit symbol



- The current-voltage relation is


$$v = L \frac{di}{dt}$$

- The unit of inductance L is volt-second per ampere or **henry (H)**




Example Inductors

- Inductors can be bulky, with typical values ranging from μH to H

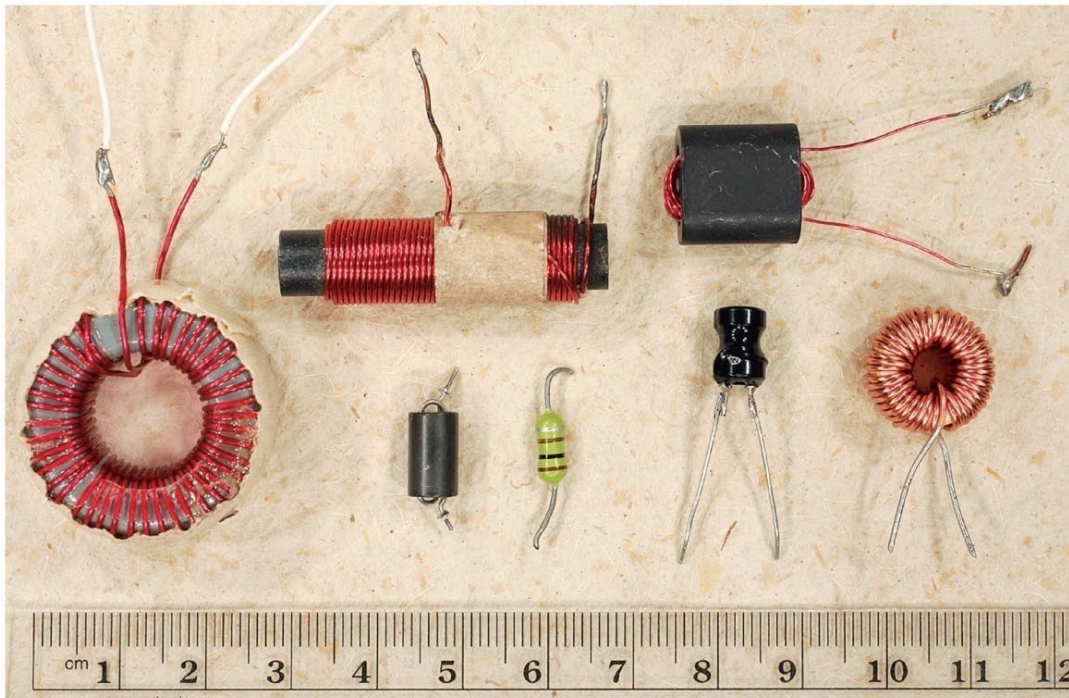

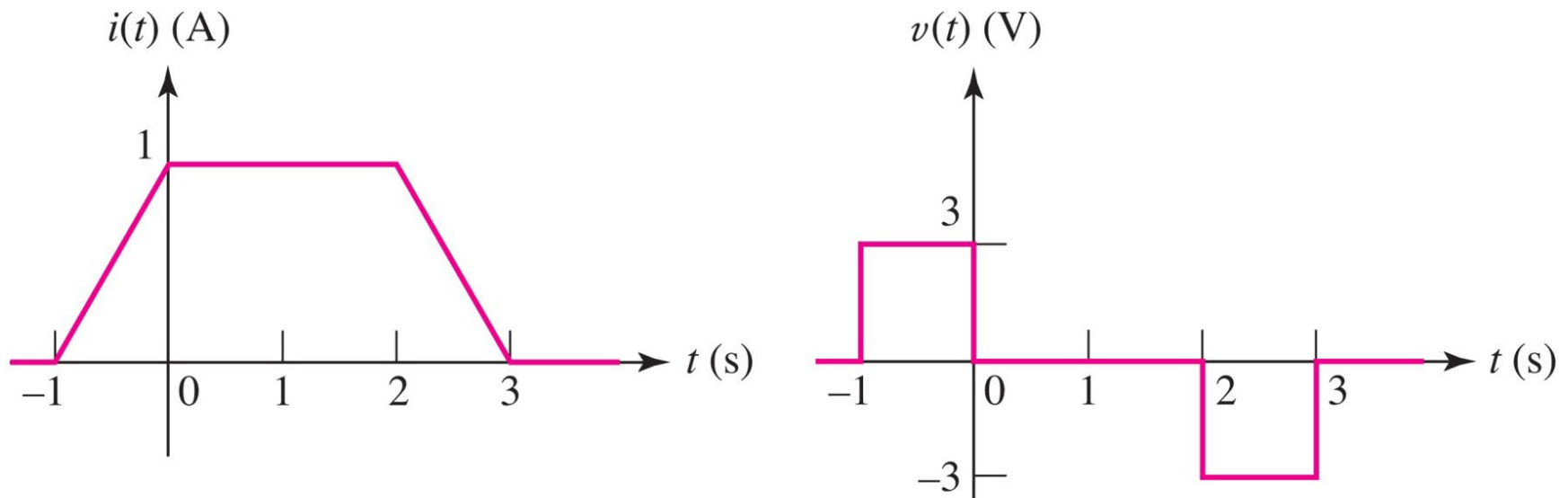Example 3

Show that the following graphs are matching voltage and current graphs for an inductor of $L = 3 \text{ H}$.



Solution:


$$v(t) = 3 \frac{di}{dt}$$

$$v(t) = \begin{cases} 0, & t \leq -1 \\ 3, & -1 \leq t \leq 0 \\ 0, & 0 \leq t \leq 2 \\ -3, & 2 \leq t \leq 3 \\ 0, & t > 3 \end{cases}$$




The inductor behavior

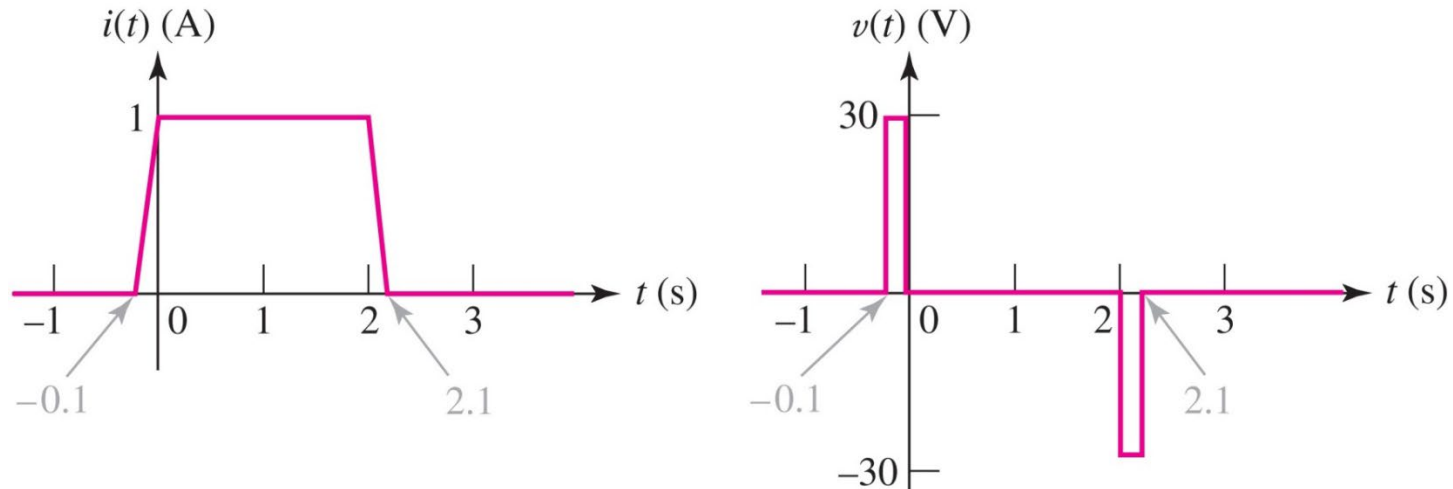- For the same 3-H inductor, the voltages are 10 times larger when the current is ramped 10 times faster.



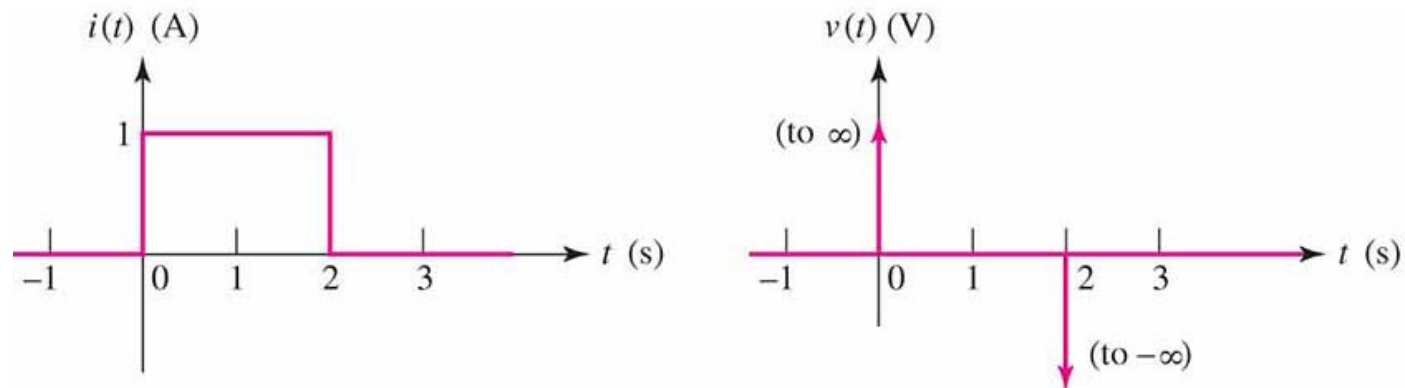- A sudden change in the current will cause the infinite voltage “spikes”,



Key inductor behaviors

- A constant current across an inductor results in zero voltage across it; thus inductors are “short circuits” to constant dc currents.
- A sudden or discontinuous change in the current must be associated with an infinite voltage across the inductor, which is physically impossible. Therefore, **the current through an inductor cannot jump.**

$$v = L \frac{di}{dt}$$



Integral Current-Voltage relationships

- The inductor current-voltage relationship

$$v = L \frac{di}{dt} \quad [1]$$

- Integrating Eq.[1], we first obtain

$$di = \frac{1}{L} v(t) dt \quad [2]$$

- Then integrate between times t_0 and t and between corresponding currents $i(t_0)$ and $i(t)$

$$i(t) = \frac{1}{L} \int_{t_0}^t v(t') dt' + i(t_0) \quad [3]$$

- Eq.[2] may also be written as an indefinite integral plus a constant of integration:

$$i(t) = \frac{1}{L} \int v dt + k \quad [4]$$



Integral Voltage-Current relationships

- We also may assume that we are solving a realistic problem that no current or energy in the inductor at initial stage. Thus set $t_0 = -\infty$ and $i(-\infty) = 0$, so that

$$i(t) = \frac{1}{L} \int_{-\infty}^t v dt' \quad [5]$$



Capacitor energy storage

- Capacitors store energy ($iv > 0$) or deliver energy ($iv < 0$).

- Since

$$p(t) = vi = Cv \frac{dv}{dt} \quad [1]$$

- Integrate over times between t_0 and t .

$$\int_{t_0}^t p(t') dt' = C \int_{t_0}^t v \frac{dv}{dt'} dt' = C \int_{v(t_0)}^{v(t)} v' dv' \quad [2]$$

- Thus,

$$w_c(t) - w_c(t_0) = \frac{1}{2} C \{[v(t)]^2 - [v(t_0)]^2\} \quad [3]$$

- Assuming zero energy at t_0 , then the energy stored in a capacitor is:

$$w_c(t) = \frac{1}{2} C v^2 \quad [4]$$



Inductor energy storage

- Inductors store energy ($iv > 0$) or deliver energy ($iv < 0$).

- Since

$$p(t) = vi = Li \frac{di}{dt} \quad [1]$$

- Integrate over times between t_0 and t .

$$\int_{t_0}^t p(t') dt' = L \int_{t_0}^t i \frac{di}{dt'} dt' = L \int_{i(t_0)}^{i(t)} i' di' \quad [2]$$

- Thus,

$$w_L(t) - w_L(t_0) = \frac{1}{2} L \{ [i(t)]^2 - [i(t_0)]^2 \} \quad [3]$$

- Assuming zero current at t_0 , then the energy stored in a inductor is:

$$w_L(t) = \frac{1}{2} Li^2 \quad [4]$$




Important characteristics of the ideal capacitor and inductor

- A finite amount of energy can be stored in a capacitor even if the current through the capacitor is zero, such as when the voltage across it is constant.
- A finite amount of energy can be stored in a inductor even if the voltage across the inductor is zero, such as when the current through it is constant.
- An ideal capacitor and inductor **never dissipates energy**, but only stores it.



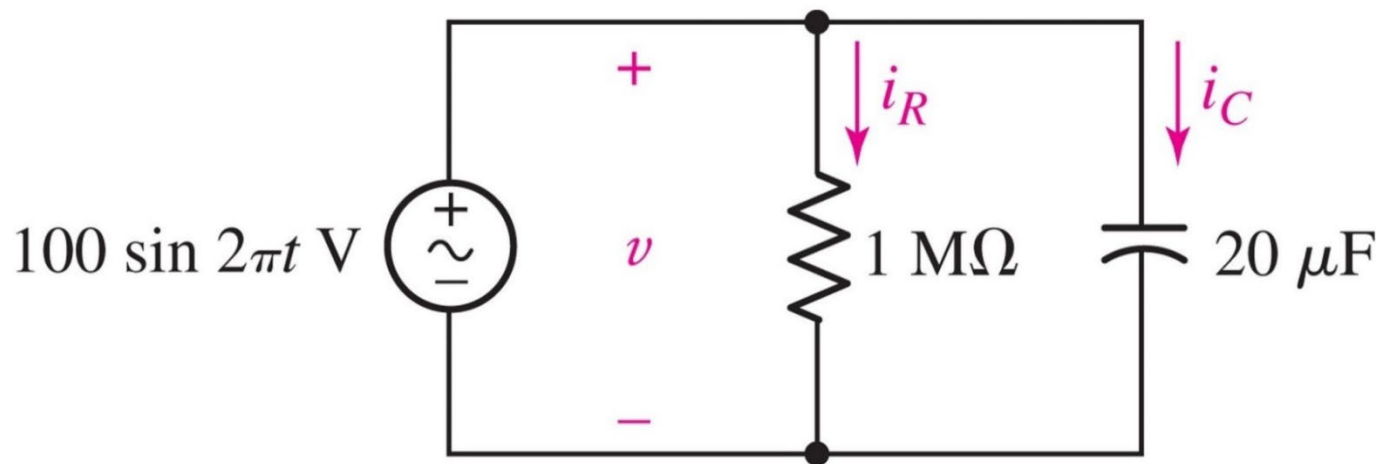Example 4

Determine the maximum energy stored in the capacitor, and plot i_R and i_C .



Note: The $1 \text{ M}\Omega$ resistor might represent the finite resistance of the “real” capacitor’s dielectric layer.



Solution to Example 4

- The energy stored in the capacitor is:

$$w_c(t) = \frac{1}{2} C v^2 = 0.1 \sin^2 2\pi t \text{ J}$$

- The resistor current:


$$i_R = \frac{v}{R} = 10^{-4} \sin 2\pi t \text{ A}$$

- The capacitor current:

$$i_C = C \frac{dv}{dt} = 20 \times 10^{-6} \frac{dv}{dt} = 0.04\pi \cos 2\pi t \text{ A}$$



Solution to Example 4

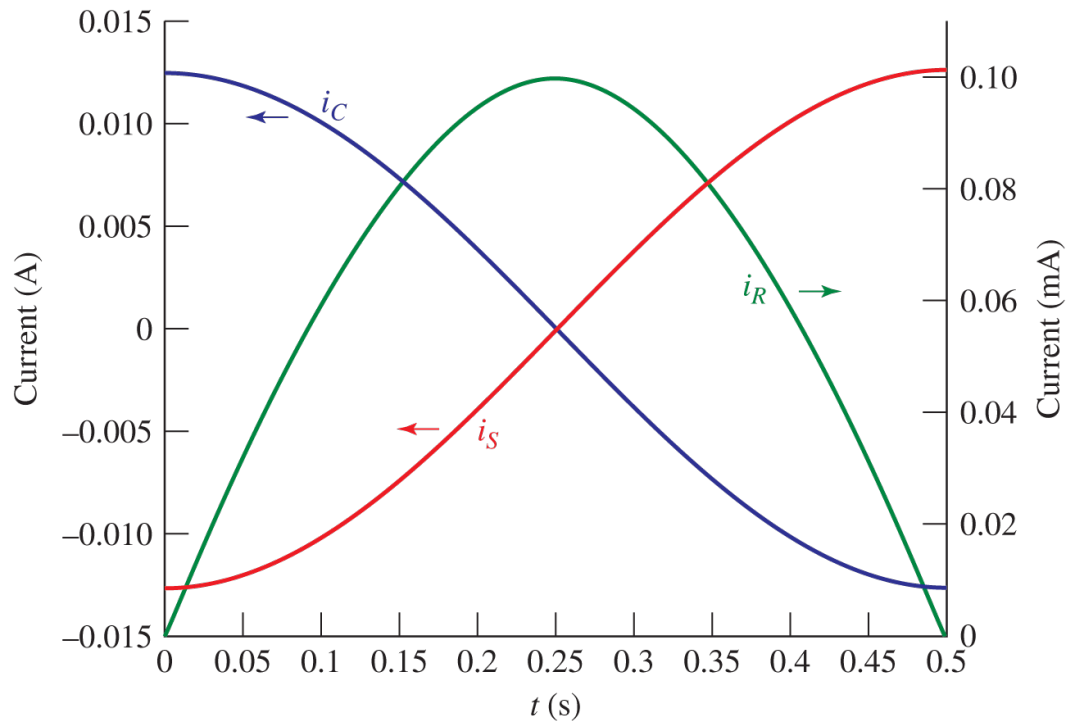


The current i_s is defined as the current flowing into the positive terminal of the source:

$$i_s = -i_c - i_R$$



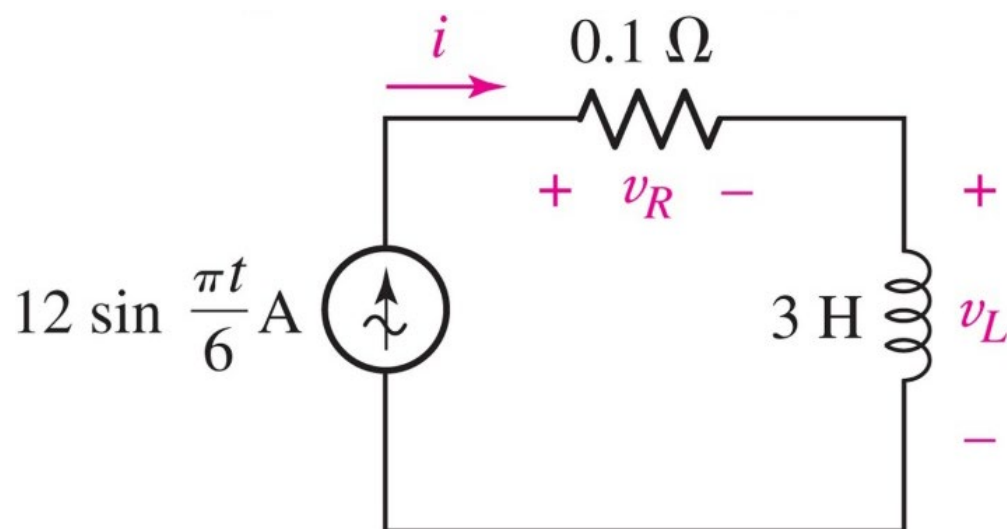Example 5

Determine the maximum energy stored in the inductor, and find the energy lost to resistor from $t = 0$ to $t = 6$ s.



Note: The 0.1Ω resistor represents the inherent resistance of the wire from which the inductor is fabricated.



Solution to Example 5

- The energy stored in the inductor is:

$$w_L(t) = \frac{1}{2} L i^2 = 216 \sin^2 \frac{\pi t}{6} \text{ J}$$

Thus the maximum energy stored in the inductor is 216 J at $t=3\text{s}$.

- The power dissipated in the resistor is:

$$p_R = i^2 R = 14.4 \sin^2 \frac{\pi t}{6} \text{ W}$$


- The energy lost to resistor from $t = 0$ to $t = 6 \text{ s}$:

$$w_R = \int_0^6 p_R dt = \int_0^6 14.4 \left(\frac{1}{2}\right) (1 - \cos \frac{\pi}{3} t) dt = 43.2 \text{ J}$$

Note: $\cos^2 \alpha = \frac{1 + \cos 2\alpha}{2}$, $\sin^2 \alpha = \frac{1 - \cos 2\alpha}{2}$



Inductors in series

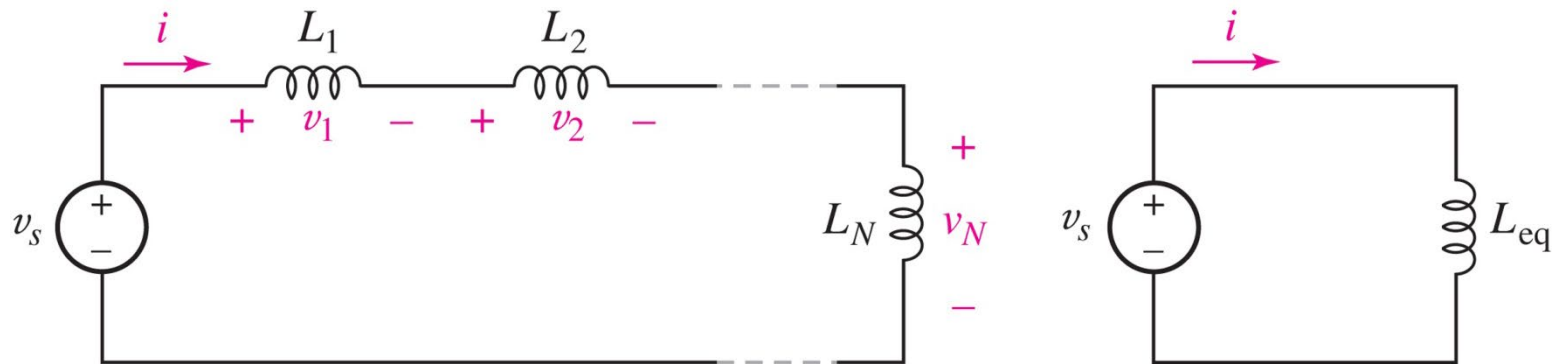

- Applying KVL to the original circuit:

$$\begin{aligned}
 v_s &= v_1 + v_2 + \cdots + v_N \\
 &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \cdots + L_N \frac{di}{dt} \\
 &= (L_1 + L_2 + \cdots + L_N) \frac{di}{dt}
 \end{aligned} \tag{1}$$

- For the equivalent circuit we have:

$$v_s = L_{eq} \frac{di}{dt} \tag{2}$$



Inductors in series


- Thus the equivalent inductance is:

$$L_{\text{eq}} = L_1 + L_2 + \cdots + L_N \quad [3]$$

- The equivalent inductance is the sum of all the inductances connected in series. **This is exactly the same result we obtained for the resistor in series.**



Inductors in Parallel

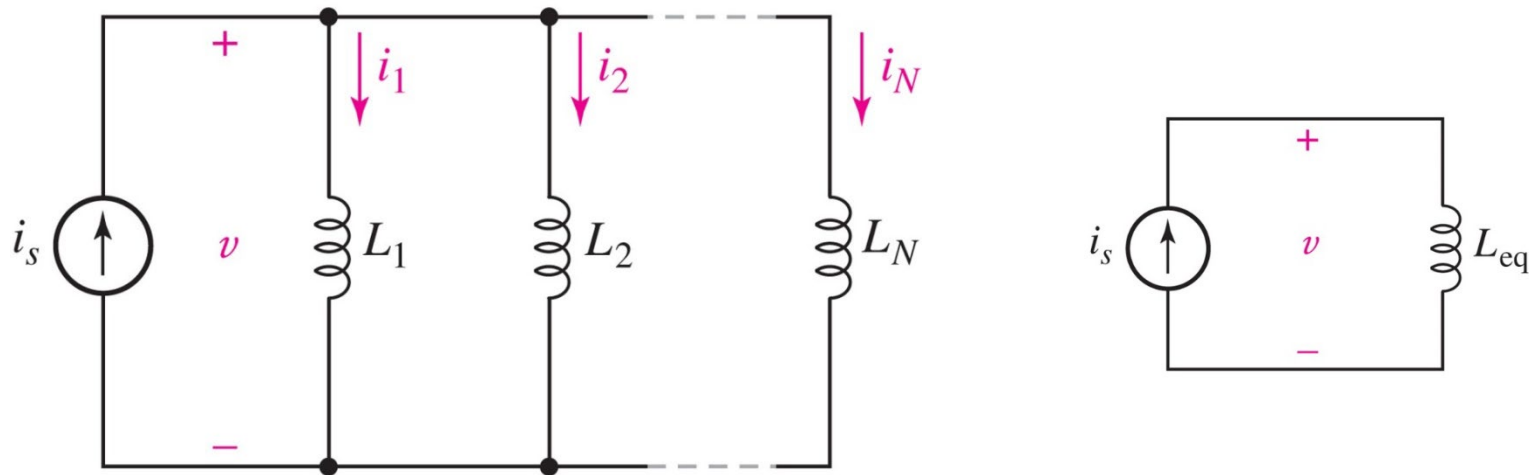

- Applying KCL to the original circuit:

$$\begin{aligned}
 i_s &= \sum_{n=1}^N i_n = \sum_{n=1}^N \left[\frac{1}{L_n} \int_{t_0}^t v dt' + i_n(t_0) \right] \\
 &= \left(\sum_{n=1}^N \frac{1}{L_n} \right) \int_{t_0}^t v dt' + \sum_{n=1}^N i_n(t_0)
 \end{aligned} \tag{1}$$

- For the equivalent circuit we have:

$$i_s = \frac{1}{L_{eq}} \int_{t_0}^t v dt' + i_s(t_0) \tag{2}$$



Inductors in Parallel



- According to KCL, $i_s(t_0)$ is equal to the sum of branch currents at t_0 , thus,

$$L_{\text{eq}} = \frac{1}{1/L_1 + 1/L_2 + \cdots + 1/L_N} \quad [3]$$

- This is also exactly the same result we obtained for the resistor in parallel.



Capacitors in series

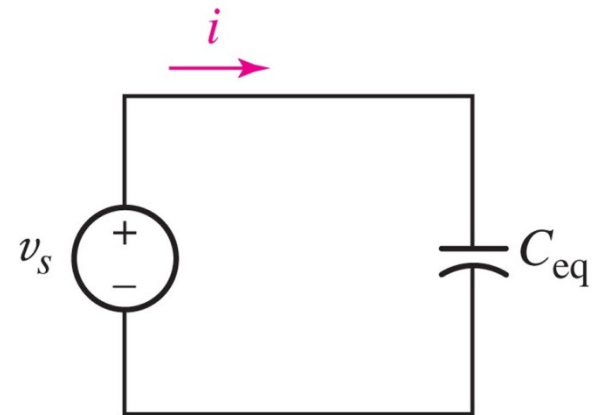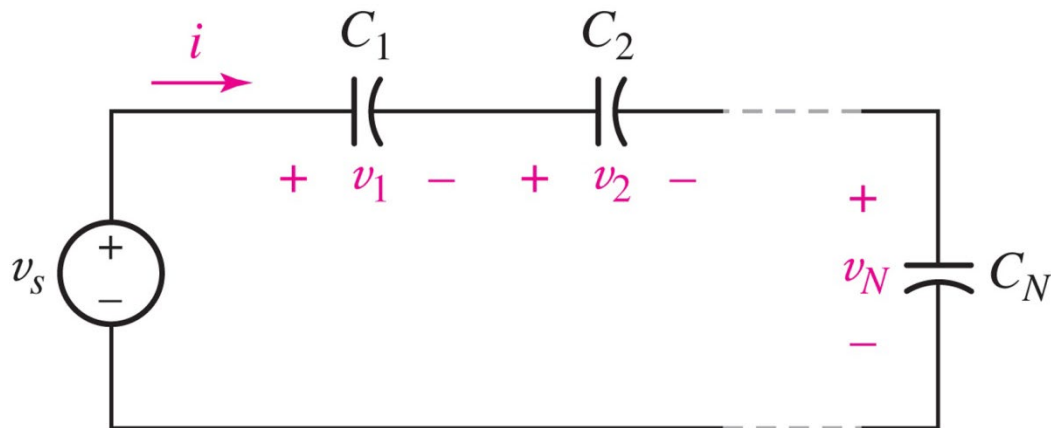

- Applying KVL to the original circuit:

$$\begin{aligned} v_s &= \sum_{n=1}^N v_n = \sum_{n=1}^N \left[\frac{1}{C_n} \int_{t_0}^t i dt' + v_n(t_0) \right] \\ &= \left(\sum_{n=1}^N \frac{1}{C_n} \right) \int_{t_0}^t i dt' + \sum_{n=1}^N v_n(t_0) \end{aligned} \quad [1]$$

- For the equivalent circuit we have:

$$v_s = \frac{1}{C_{eq}} \int_{t_0}^t i dt' + v_s(t_0) \quad [2]$$




Capacitors in series

- According to KVL, $v_s(t_0)$ is equal to the sum of capacitor voltages at t_0 , thus,

$$C_{\text{eq}} = \frac{1}{1/C_1 + 1/C_2 + \cdots + 1/C_N} \quad [3]$$



Capacitors in parallel

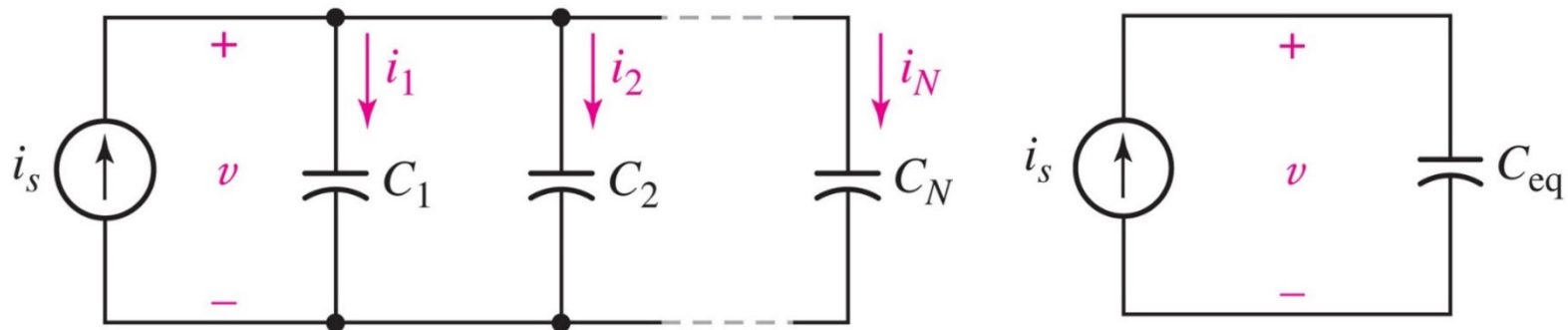

$$C_{eq} = C_1 + C_2 + \dots + C_N \quad [1]$$

- C_{eq} can be found by applying KCL and equation $i = C \frac{dv}{dt}$.



Two-element Shortcuts

- Two capacitors in series:

$$C_{eq} = \frac{c_1 c_2}{c_1 + c_2}$$

- Two inductors in parallel:

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$


- Two resistors in parallel:

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$




Example 6

Simplify the network shown below.

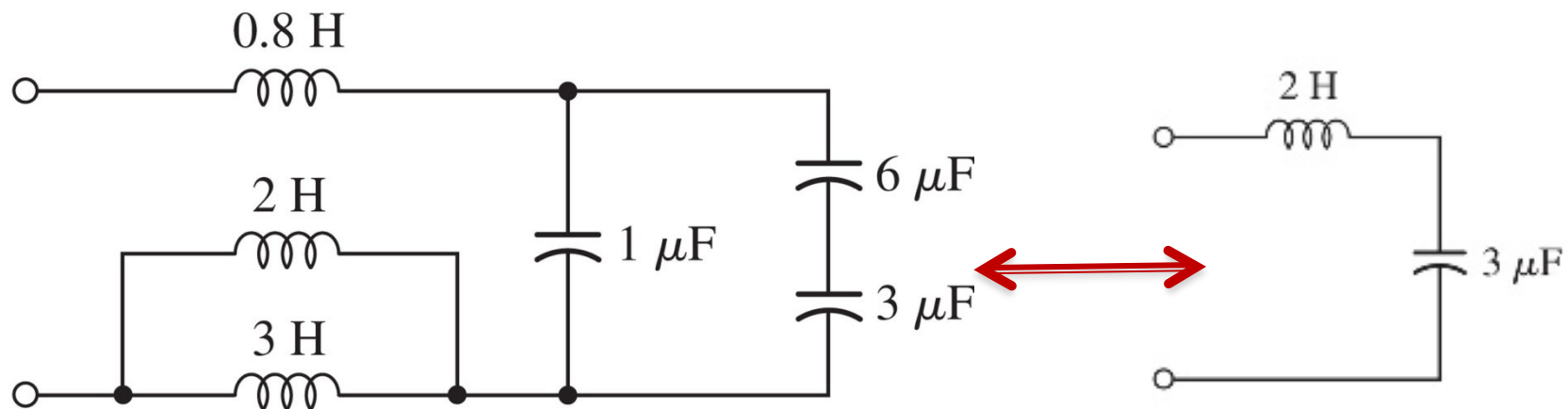

Example 7

Simplify the network shown below.

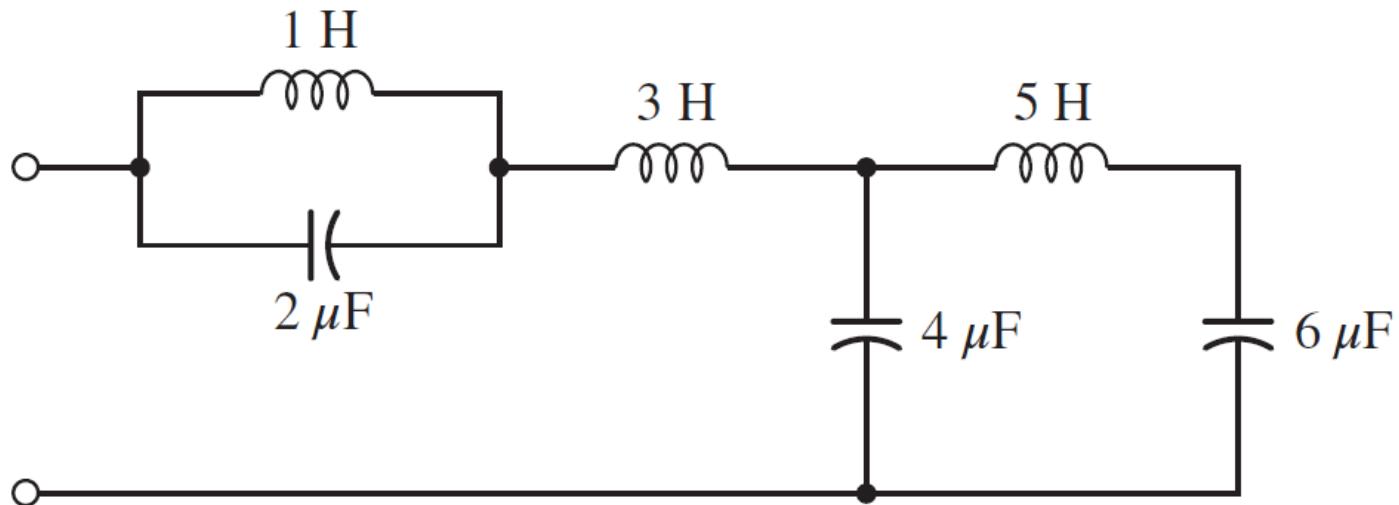


Solution: **cannot** be simplified 😊.



Op Amp Integrator

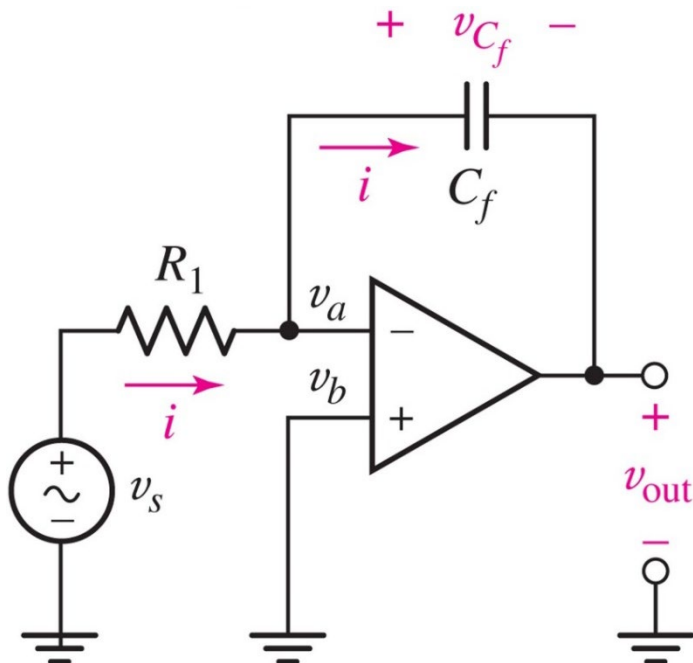- Incorporating energy storage elements (L or C) with op amp circuits can provide important time-varying functions.
- Solve V_{out} , use KVL, KCL, and op amp rules.



- According to op amp rule 1:

$$i_{c_f}(t) = i = \frac{v_s - v_a}{R_1} \quad [1]$$


- According to op amp rule 2, we know that $v_a = v_b = 0$, so

$$\begin{aligned} v_{c_f}(t) &= -v_{out}(t) \\ &= \frac{1}{C_f} \int_{t_0}^t i_{c_f}(t') dt' + v_{c_f}(t_0) \end{aligned} \quad [2]$$

$$i_{c_f}(t) = \frac{v_s - v_a}{R_1} = \frac{v_s}{R_1} \quad [3]$$



Op Amp Integrator

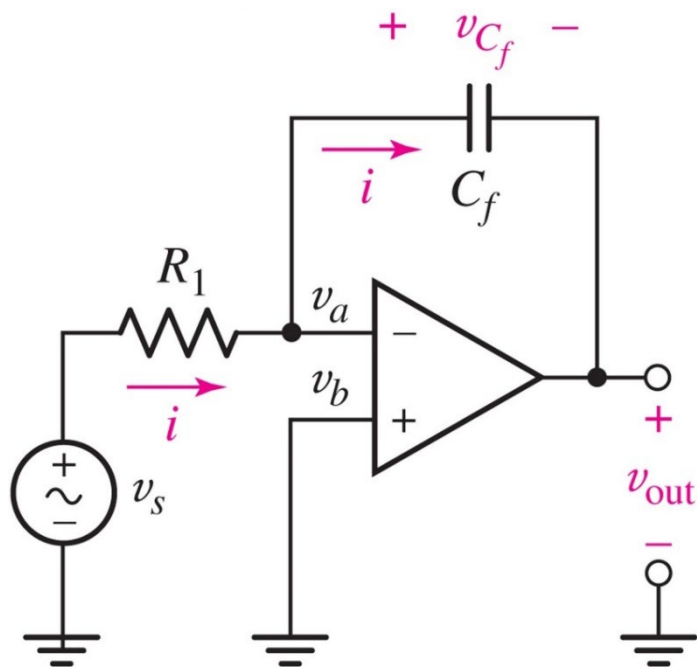

- Substituting Eq.[3] into Eq.[2], and assuming $t_0 = 0$,


$$v_{out}(t) = -\frac{1}{R_1 C_f} \int_0^t v_s(t') dt' - v_{C_f}(0)$$

- We therefore have combined a resistor, a capacitor and an op amp to form an **integrator**.



Op Amp Differentiator

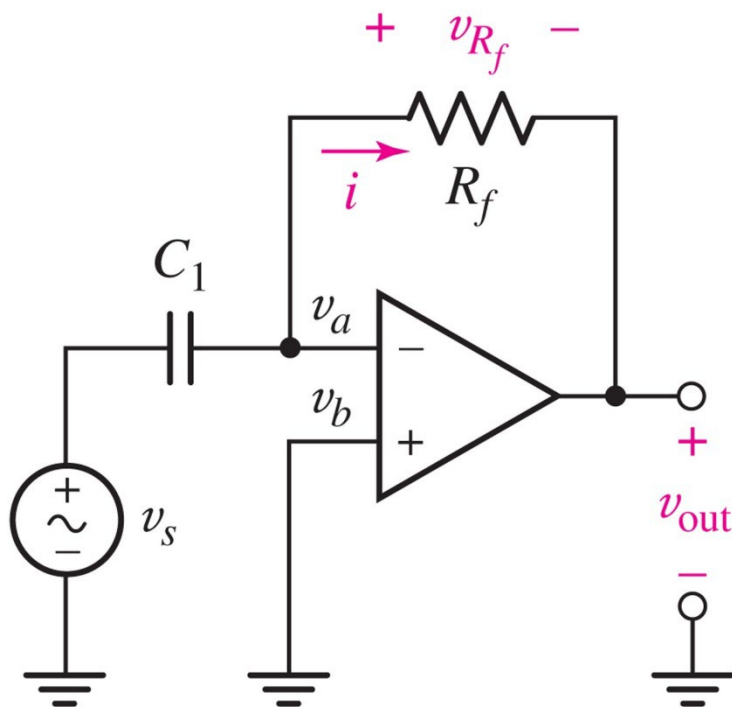- Solve V_{out} , use KVL, KCL, and op amp rules.



- According to op amp rule 1:

$$C_1 \frac{dv_{c1}}{dt} = \frac{v_a - v_{out}}{R_f} \quad [1]$$

- According to op amp rule 2,
 $v_a = v_b = 0$, so


$$C_1 \frac{dv_{c1}}{dt} = \frac{-v_{out}}{R_f} \quad [2]$$

- Since $v_c = v_s - v_a = v_s$, solving v_{out} ,

$$v_{out} = -R_f C_1 \frac{dv_s}{dt} \quad [3]$$

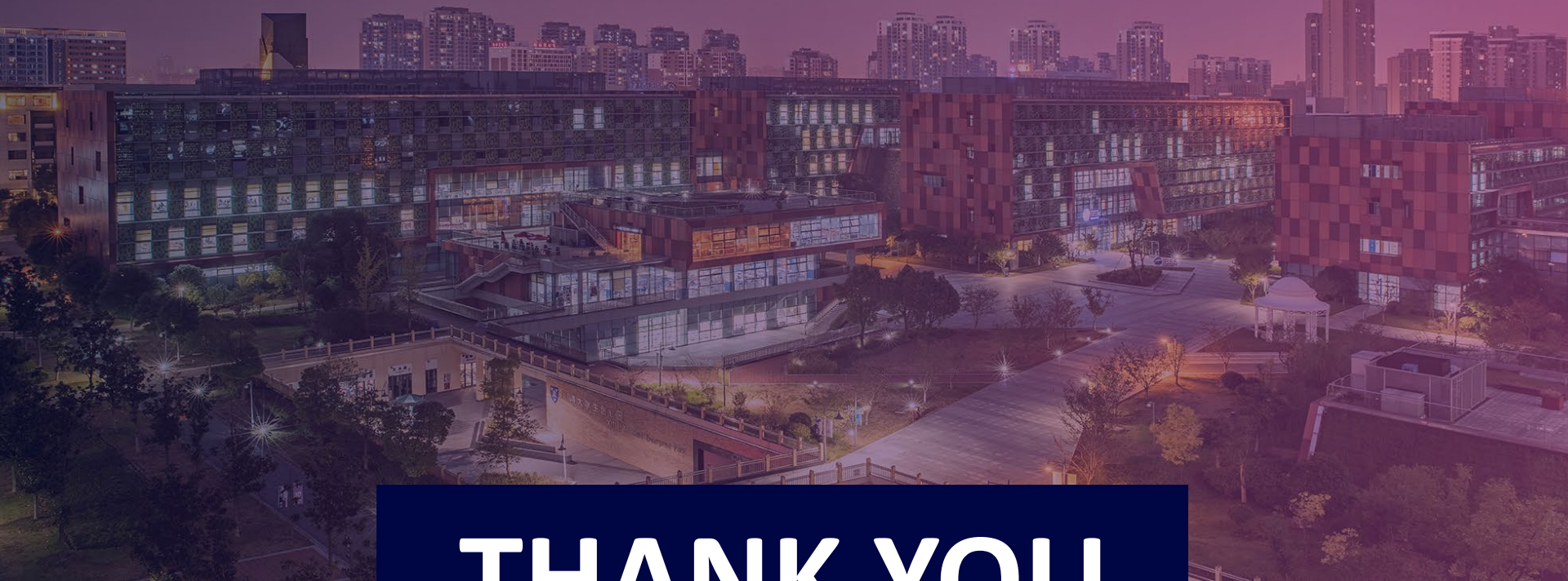- We therefore have combined a resistor, a capacitor and an op amp to form an **differentiator**.





THANK YOU



Xi'an Jiaotong-Liverpool University

西交利物浦大學

