

Lecture 11a
of
EEE201

CMOS Digital Integrated Circuits

Department of Electrical & Electronic Engineering
Xi'an Jiaotong-Liverpool University (XJTLU)

Monday, 18th November 2024

□ CMOS Logic Inverter VTC

- VTC – static case
- MOSFET terminal voltages related to V_{in} & V_{out}
- I - V curves with same coordinates
- intersection points of V_{in} & V_{out}



Xi'an Jiaotong-Liverpool University
西交利物浦大學

Voltage Transfer Characteristics

(static characteristics of CMOS inverter)

- ❑ The **voltage transfer characteristics** (VTC) of the logic inverter (and in general other logic gates such as NAND and NOR) *relate* the output voltage to the input voltage.
 - Note that the VTC refer to the *static* case of relationship between the output voltage and the input voltage. It does not take into account of transient behaviour.
 - The logic inverter's VTC are also called **DC transfer characteristics** or simply **static characteristics**.
 - In the *static* case, there is no need to consider the charging & discharging processes.

CMOS Inverter VTC


(definitions of quantities)

- ❑ To obtain the CMOS inverter VTC, we need to find how the output voltage V_{out} varies as a function of the input voltage V_{in} (from 0 V to V_{DD}).
 - When V_{in} varies (from 0 V to V_{DD}), the nMOSFET and pMOSFET of the CMOS logic inverter will go through different operation modes.
 - The operation modes of the two MOSFETs depend on the their terminal voltages (mainly V_{GS} & V_{DS}).
 - We need to relate the MOSFETs' terminal voltages to V_{in} and V_{out} .
 - two sets of MOSFET voltages:
 V_{GSn}, V_{DSn}, V_{Tn} & V_{GSp}, V_{DSp}, V_{Tp}

CMOS Inverter VTC

(relate MOSFETs' terminal voltages to V_{in} & V_{out})

- Since there is no need to consider the charging and discharging in the static case, the drain current flowing out of the pMOSFET must flow into the drain of the nMOSFET $\Rightarrow |I_{Dsp}| = |I_{DSn}|$ in the CMOS logic inverter.

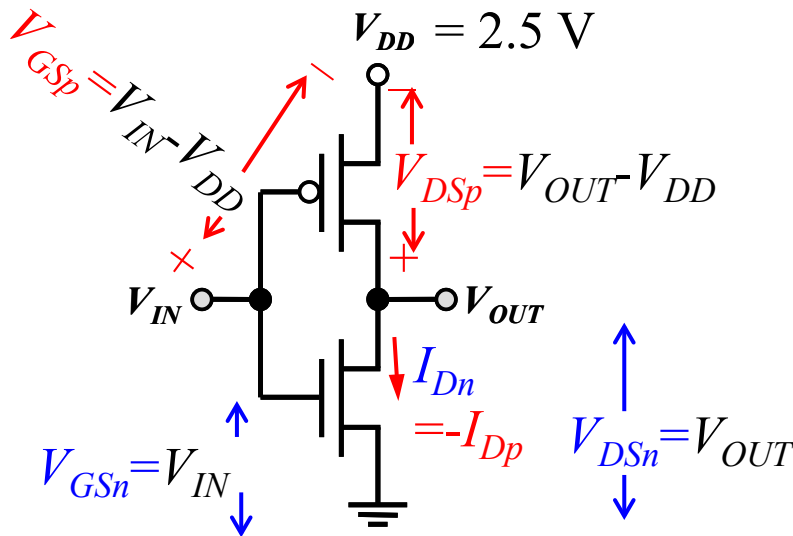



$$\begin{aligned} I_{Dp} &= -I_{Dn} \\ V_{GSn} &= V_{IN} \\ V_{GSp} &= V_{IN} - V_{DD} \\ V_{DSn} &= V_{OUT} \\ V_{DSp} &= V_{OUT} - V_{DD} \end{aligned}$$

CMOS Inverter VTC

(relate **n**MOSFET terminal voltages to V_{in} & V_{out})

- It is straightforward to relate the **n**MOSFET's terminal voltages to V_{in} & V_{out} :

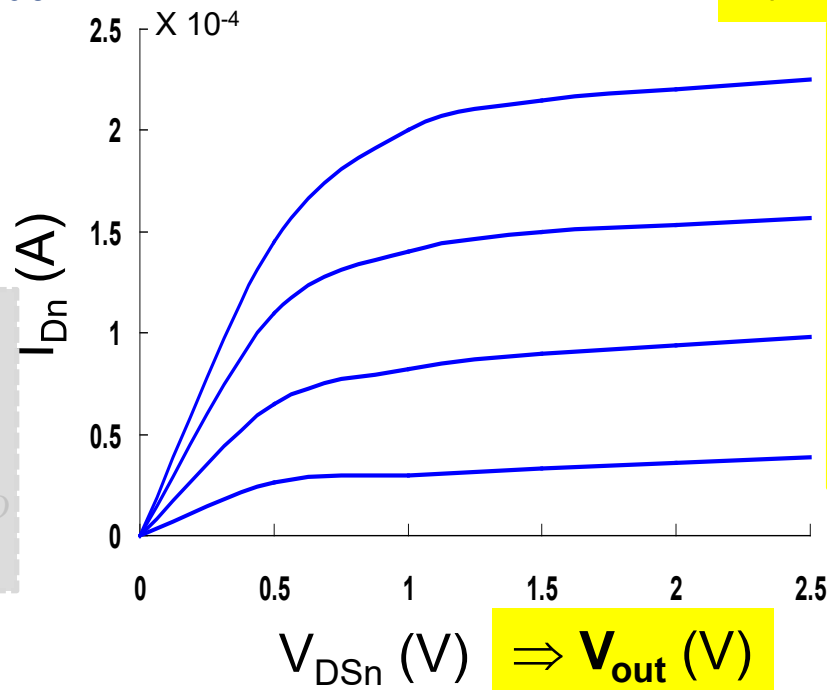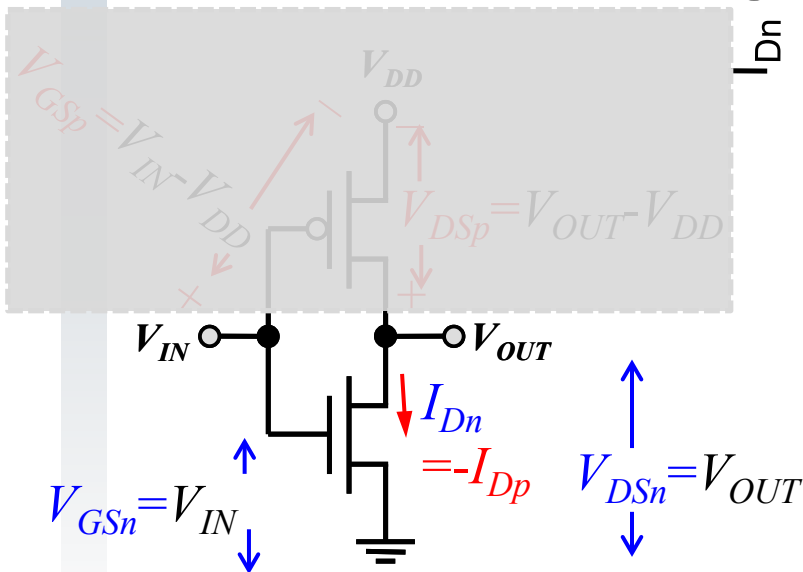$V_{Tn0} = 0.4 \text{ V}$ &
 $V_{DD} = 2.5 \text{ V}$ as
 an example



$\Rightarrow V_{in} = 0 - 2.5 \text{ V}$

$V_{GSn} = 2.5\text{V}$

$V_{GSn} = 2.0\text{V}$

$V_{GSn} = 1.5\text{V}$



$V_{GSn} = 1.0\text{V}$

CMOS Inverter VTC

(I - V curves of p MOSFET in the original form)

- To relate the p MOSFET's terminal voltages to V_{in} & V_{out} , it needs transformation of the curves. V_{DSp} (V) $\Rightarrow V_{out} = ?$ (V)

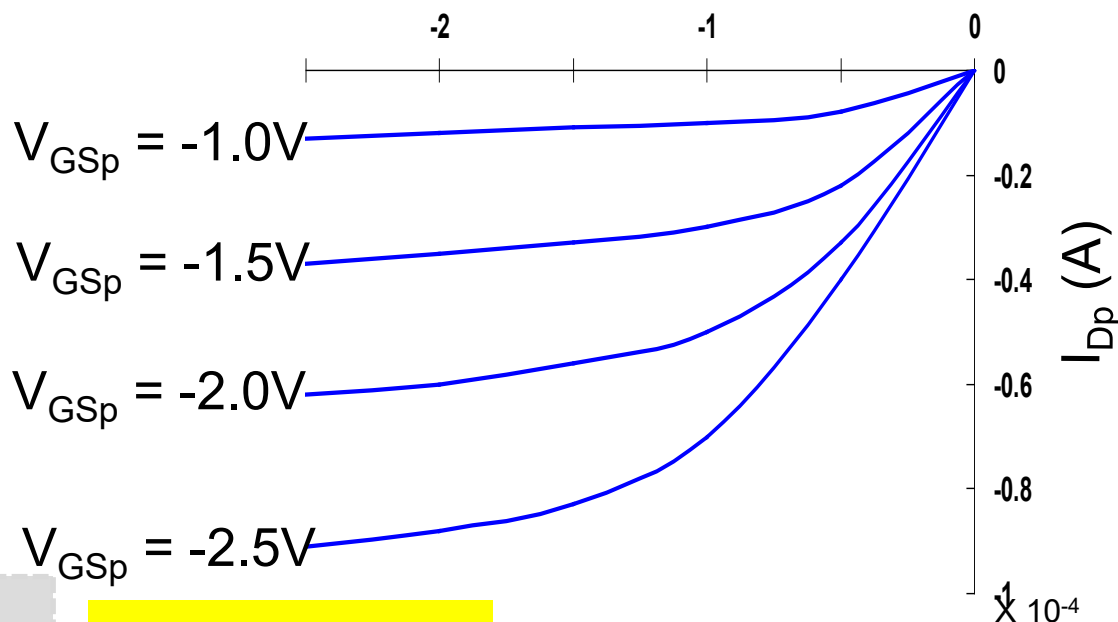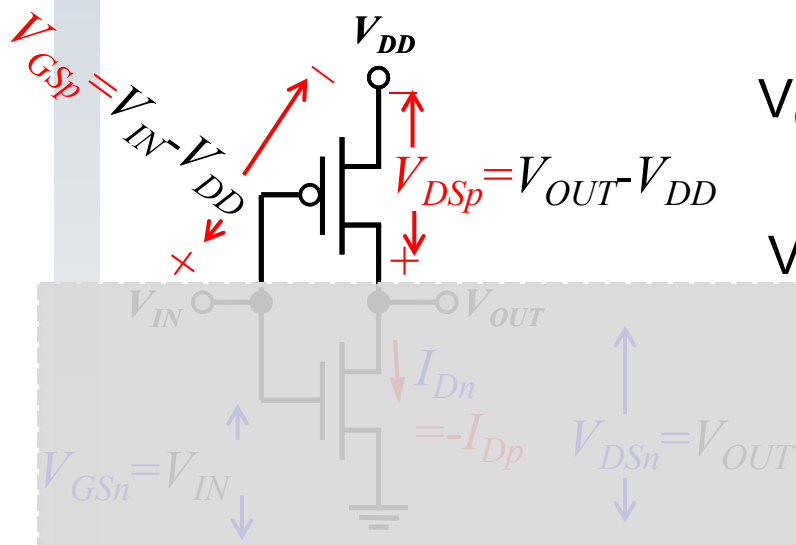$V_{Tp0} = -0.4$ V &
 $V_{DD} = 2.5$ V as
 an example



$$\Rightarrow V_{in} = ? - ? \text{ V}$$

$$V_{in} = V_{DD} + V_{GSp}$$

$$= 1.5 - 0 \text{ V}$$






Xi'an Jiaotong-Liverpool University
 西交利物浦大学

CMOS Inverter VTC

(relate pMOSFET terminal voltages to V_{in} & V_{out})

- Transforming the pMOSFET's I - V curves in terms of V_{in} &


V_{out} :

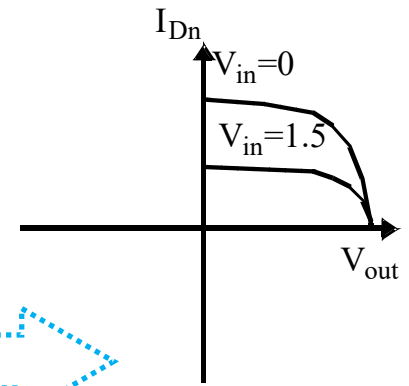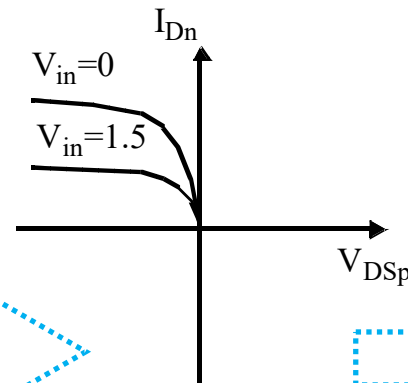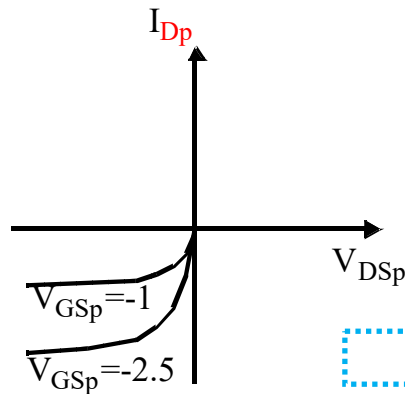

$$I_{Dn} = -I_{Dp}$$

$$V_{in} = V_{DD} + V_{GSp} \\ = 1.5 - 0 \text{ V}$$

$$V_{out} = V_{DSp} + V_{DD}$$

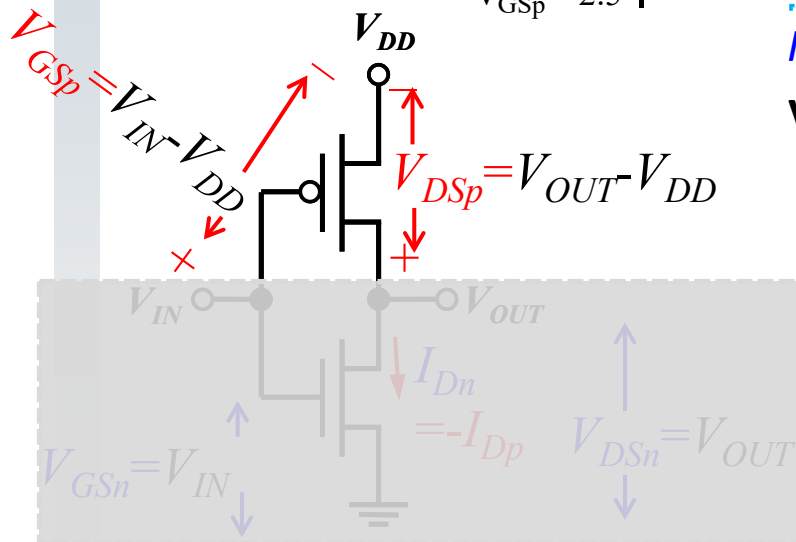

$V_{Tp0} = -0.4 \text{ V}$ & $V_{DD} = 2.5 \text{ V}$ as an example




Xi'an Jiaotong-Liverpool University
西交利物浦大學

CMOS Inverter VTC

(I - V curves with the same coordinates)

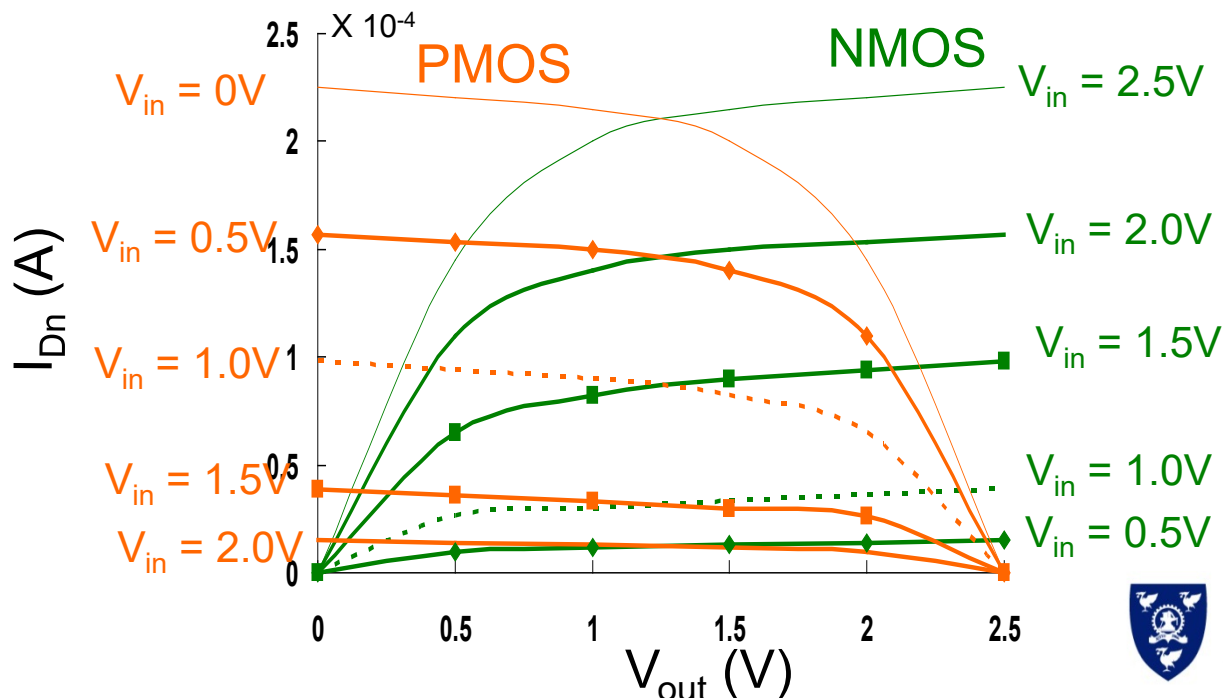- When the I - V curves of both the nMOSFET and pMOSFET have the same coordinates (i.e. in terms of the same V_{in} & V_{out} and I_{Dn}), it is now ready for finding out the CMOS inverter's VTC using the graphical approach:




Xi'an Jiaotong-Liverpool University
西交利物浦大學

CMOS Inverter VTC

(intersection points of the I - V curves)


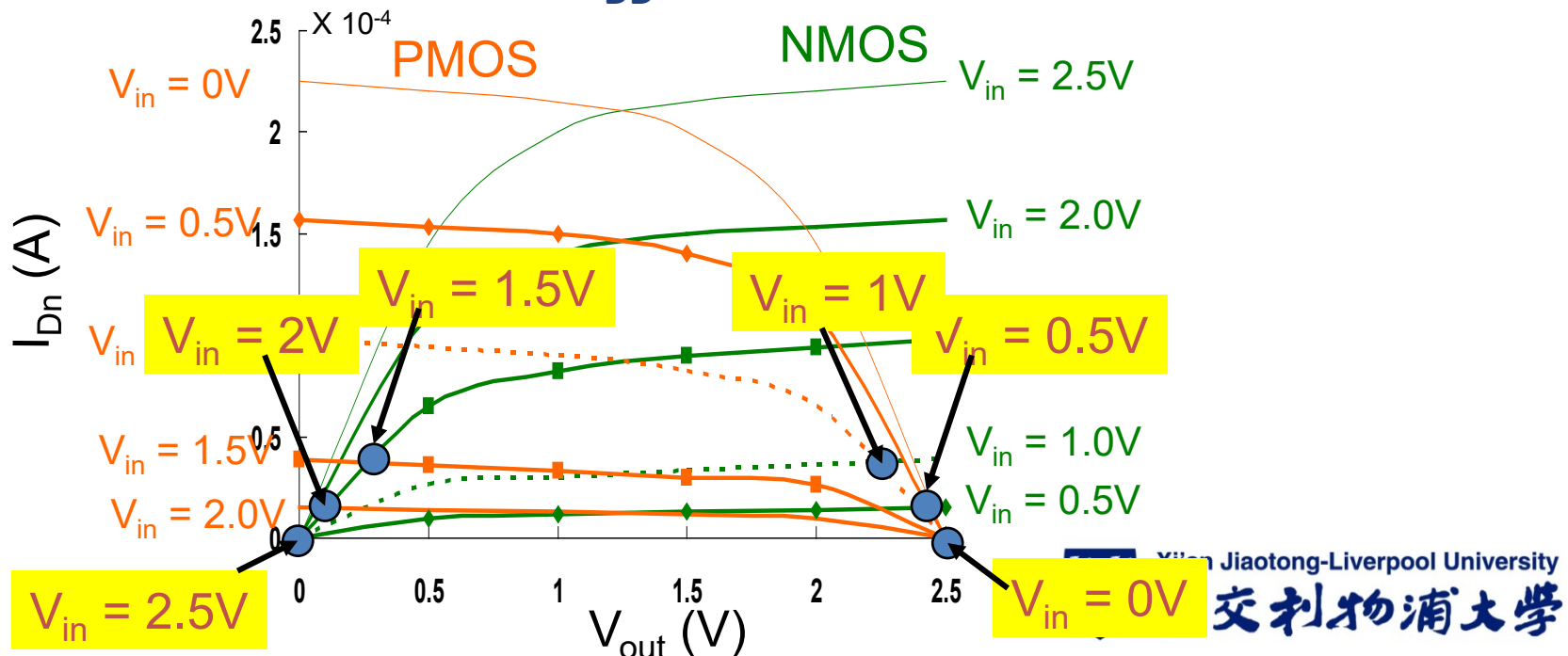
- ❑ As V_{in} increases from 0 V to $V_{DD} = 2.5$ V, there are intersection points of the I - V curves (nMOS & pMOS).
- The intersection points correspond also to V_{out} , decreasing from $V_{DD} = 2.5$ V to 0 V.



CMOS Inverter VTC

(V_{in} & V_{out} from the intersection points)

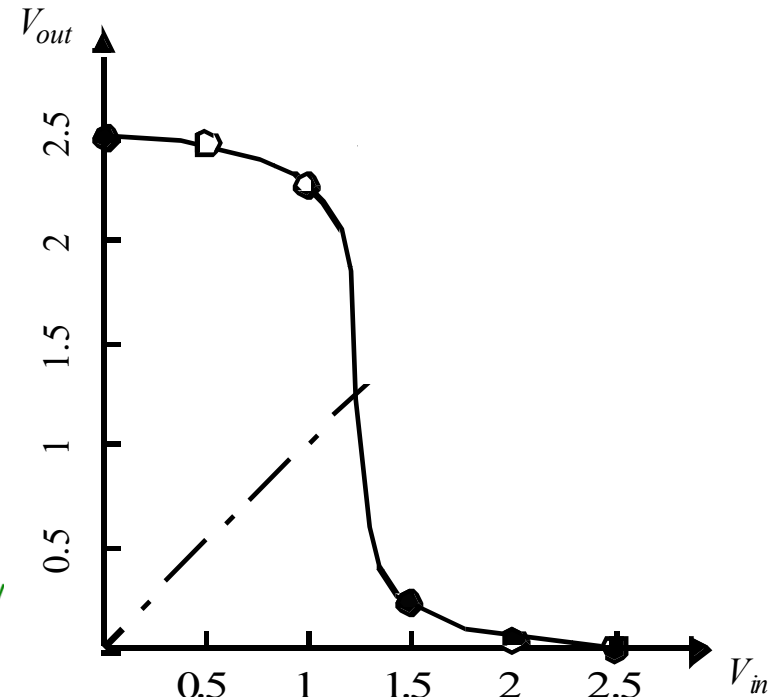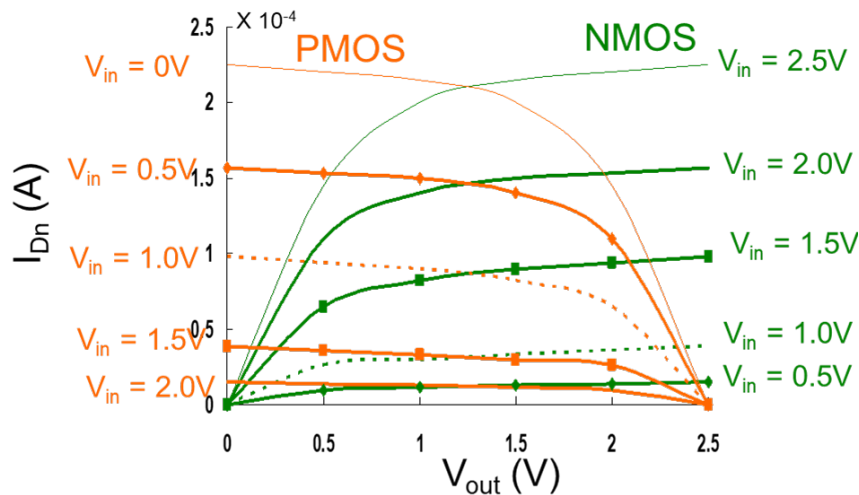- The corresponding intersection points of the I - V curves of both the nMOSFET and pMOSFET are data points the CMOS inverter's VTC:





Xi'an Jiaotong-Liverpool University
西交利物浦大學

CMOS Inverter VTC

(dynamic current during switching)

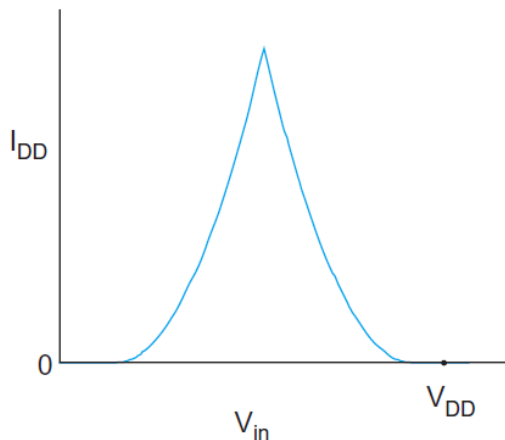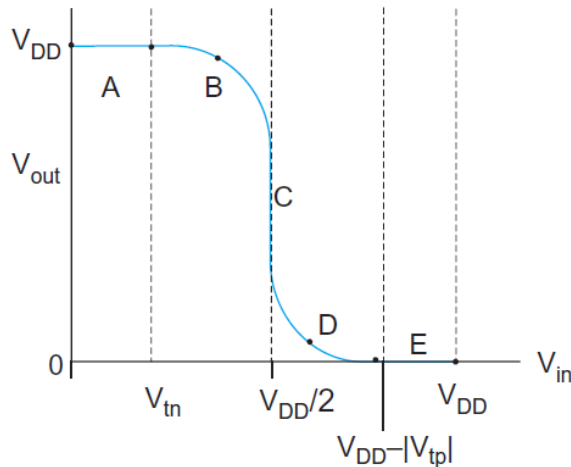- ❑ Note that there is current flow directly from V_{DD} to ground in the transition region of the CMOS inverter's VTC.



- In the steady state, there is almost zero power consumption in the CMOS inverter (and generally other logic gates).
- However, in the dynamic situation (i.e. when the input changes from logic “0” to “1” or vice versa, there is current consumption.