

EEE103 ELECTRICAL CIRCUITS

WEEK4-HANDY CIRCUIT ANALYSIS TECHNIQUES

Ye Wu

ye.wu@xjtlu.edu.cn



Xi'an Jiaotong-Liverpool University

西交利物浦大學



CONTENT

- Linearity and Superposition
- Source Transformations
- Thévenin and Norton Equivalent Circuits
- Maximum Power Transfer
- Delta-Wye Conversion




Linear Elements and Circuits

Linear element: Passive element has a linear voltage-current relationship:


- if $i(t)$ produces $v(t)$, then $Ki(t)$ produces $Kv(t)$
- if $i_1(t)$ produces $v_1(t)$ and $i_2(t)$ produces $v_2(t)$, then $i_1(t) + i_2(t)$ produces $v_1(t) + v_2(t)$,
- Resistors are linear elements

$$v(t) = Ri(t)$$

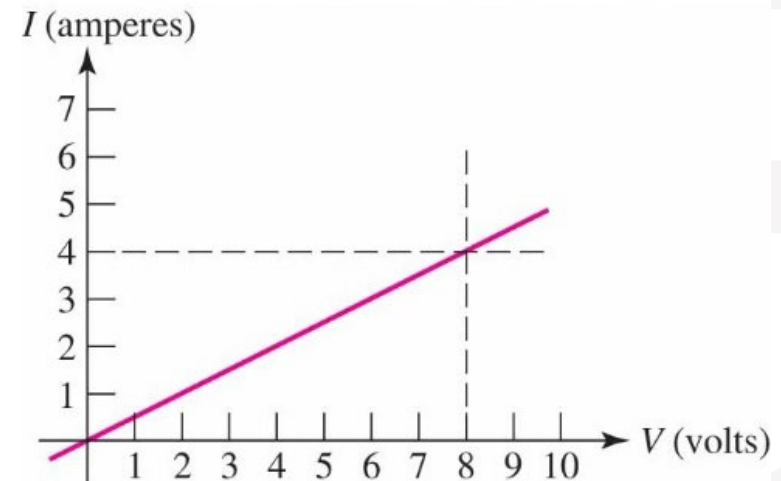

Linear Elements and Circuits

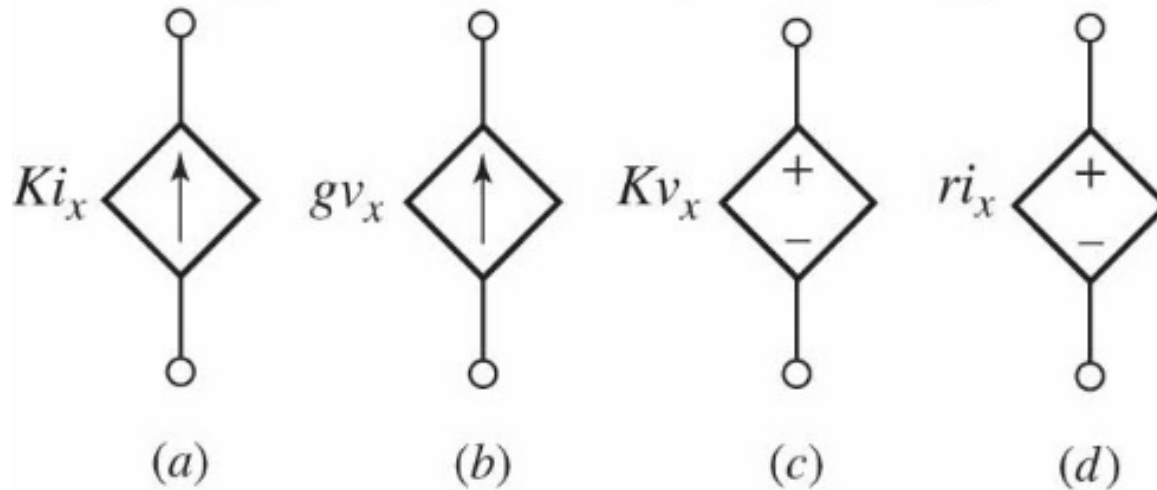Linear dependent source: dependent current or voltage source whose output current or voltage is proportional only to the first power of a specified current or voltage variable in the circuit (or to the sum of such quantities).




Linear circuit: A circuit has only **independent sources**, **linear dependent sources**, and **linear elements**



The Superposition Concept₁

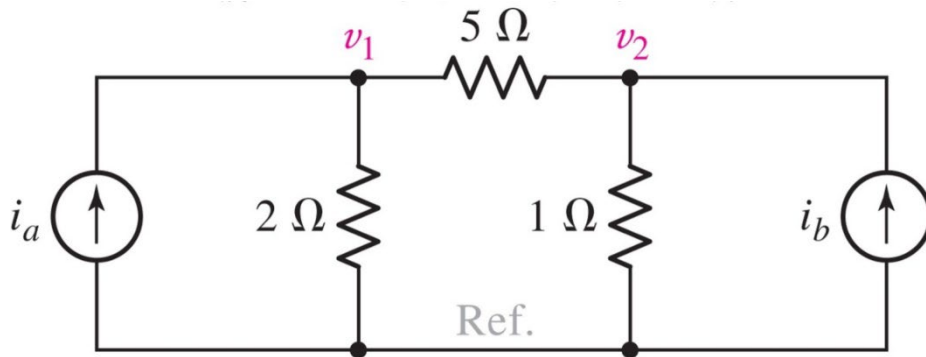For the circuit shown, we have 2 independent source i_a, i_b



Question: How much of v_1 is due to source a , and how much is because of source b ?

If the two sources are i_a, i_b , we get v_1, v_2

Apply KCL to node 1: $\frac{v_1 - v_2}{5} + \frac{v_1}{2} - i_a = 0$

Apply KCL to node 2: $\frac{v_2 - v_1}{5} + \frac{v_2}{1} - i_b = 0$


$$\rightarrow \begin{cases} 0.7v_1 - 0.2v_2 = i_a \\ -0.2v_1 + 1.2v_2 = i_b \end{cases}$$

Sources i_a, i_b : forcing functions;

Nodal voltages v_1, v_2 : response functions(or simply responses).



The Superposition Concept₁

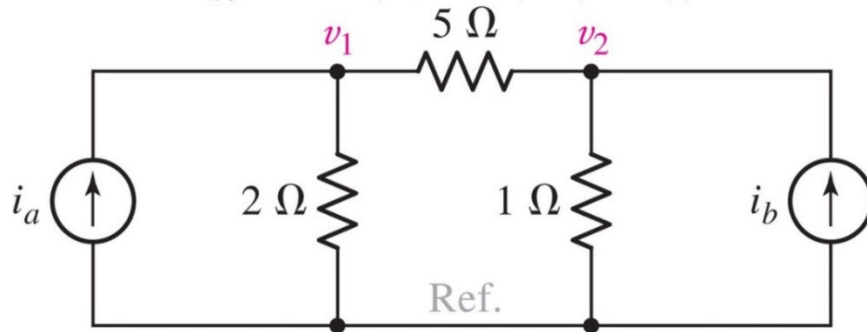

$$\rightarrow \begin{cases} 0.7v_1 - 0.2v_2 = i_a \\ -0.2v_1 + 1.2v_2 = i_b \end{cases}$$

Experiment X: i_{ax}, i_{bx} , new v_{1x}, v_{2x} $\rightarrow \begin{cases} 0.7v_{1x} - 0.2v_{2x} = i_{ax} \\ -0.2v_{1x} + 1.2v_{2x} = i_{bx} \end{cases}$

Experiment Y: i_{ay}, i_{by} , new v_{1y}, v_{2y} $\rightarrow \begin{cases} 0.7v_{1y} - 0.2v_{2y} = i_{ay} \\ -0.2v_{1y} + 1.2v_{2y} = i_{by} \end{cases}$


Add X and Y: $\rightarrow \begin{cases} 0.7(v_{1x} + v_{1y}) - 0.2(v_{2x} + v_{2y}) = i_{ax} + i_{ay} \\ -0.2(v_{1x} + v_{1y}) + 1.2(v_{2x} + v_{2y}) = i_{bx} + i_{by} \end{cases}$

If we have: $i_{ax} + i_{ay} = i_a$ & $i_{bx} + i_{by} = i_b$

$$\rightarrow v_1 = v_{1x} + v_{1y}, v_2 = v_{2x} + v_{2y}$$



The Superposition Concept₁

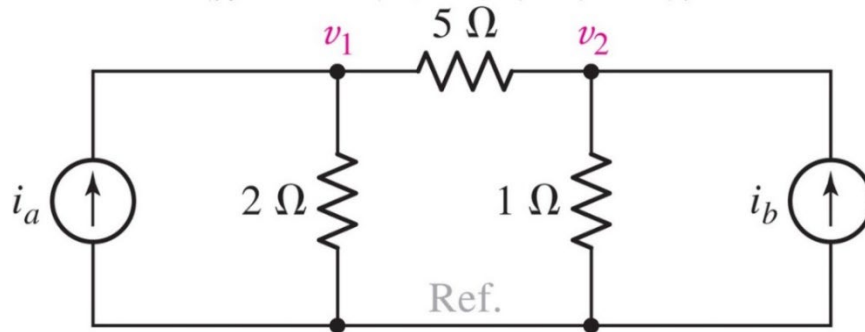

Experiment X: $i_{ax} = i_a, i_{bx} = 0$

$$\Rightarrow \begin{cases} 0.7v_1 - 0.2v_2 = i_a \\ -0.2v_1 + 1.2v_2 = i_b \end{cases}$$

$$\Rightarrow \begin{cases} 0.7v_{1x} - 0.2v_{2x} = i_a \\ -0.2v_{1x} + 1.2v_{2x} = 0 \end{cases}$$

Experiment Y: $i_{ay} = 0, i_{by} = i_b$

$$\Rightarrow \begin{cases} 0.7v_{1y} - 0.2v_{2y} = 0 \\ -0.2v_{1y} + 1.2v_{2y} = i_b \end{cases}$$


Add X and Y:

$$\Rightarrow \begin{cases} 0.7(v_{1x} + v_{1y}) - 0.2(v_{2x} + v_{2y}) = i_a \\ -0.2(v_{1x} + v_{1y}) + 1.2(v_{2x} + v_{2y}) = i_b \end{cases}$$

$$\Rightarrow v_1 = v_{1x} + v_{1y}, v_2 = v_{2x} + v_{2y}$$




The Superposition Concept₁

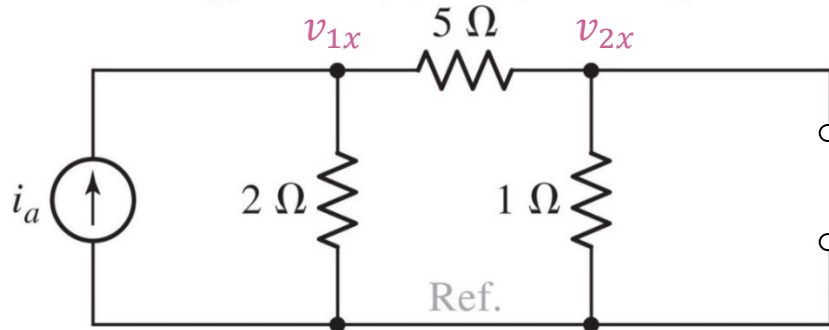

If : $i_{ax} = i_a, i_{bx} = 0$

$$\rightarrow \begin{cases} 0.7v_{1x} - 0.2v_{2x} = i_a \\ -0.2v_{1x} + 1.2v_{2x} = 0 \end{cases}$$

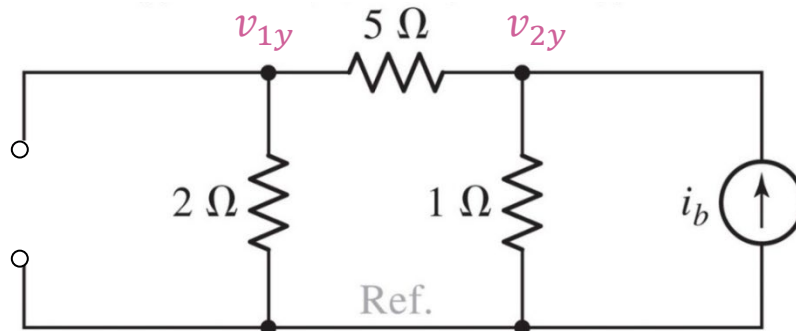Apply KCL to node 1: $\frac{v_{1x}}{6} + \frac{v_{1x}}{2} - i_a = 0$



If : $i_{ay} = 0, i_{by} = i_b \Rightarrow v_{1y}, v_{2y}$

Apply KCL to node 2: $\frac{v_{2y}}{1} + \frac{v_{2y}}{7} - i_b = 0$

Question: How much of v_1 is due to source a , and how much is because of source b ?

$$v_1 = v_{1x} + v_{1y}$$



The Superposition Theorem

In a linear network, the **voltage across** or the **current through** any element may be calculated by *adding algebraically* all the individual voltages or currents caused by the separate **independent sources** acting “alone”, that is, with

- all other independent voltage sources replaced by short circuits
- all other independent current sources replaced by open circuits





Applying Superposition

Leave one source ON and turn all other sources OFF:


- current sources: set $i=0$.
- These become *open circuits*.
- voltage sources: set $v=0$.
- These become *short circuits*.
- *Find the response from this source.*

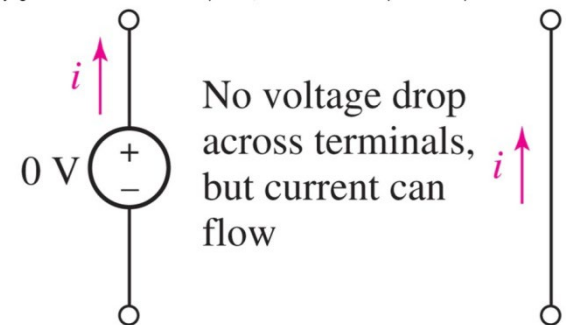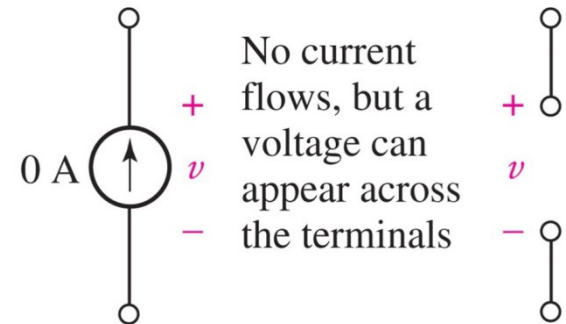Add the resulting responses to find the total response.




Superposition Example

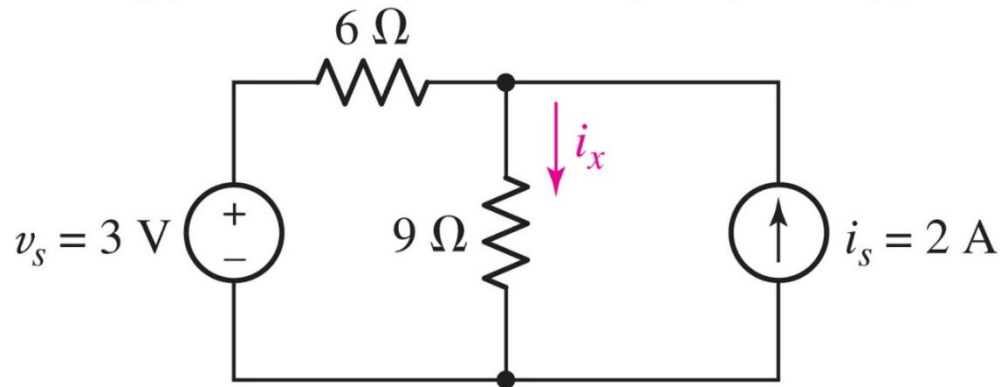Use superposition to solve for the current i_x



Superposition Example

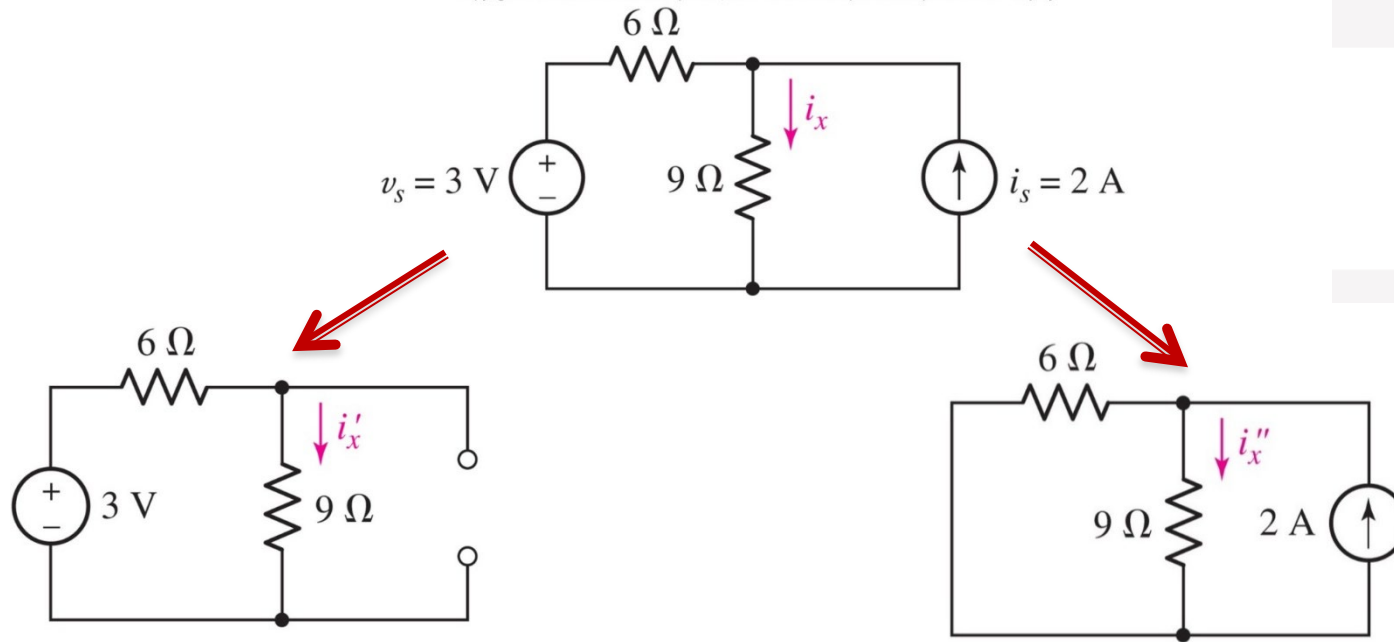

First, turn the current source off:

$$i'_x = \frac{3}{6+9} = 0.2 \text{ A}$$

Then, turn the voltage source off:

$$i''_x = \frac{6}{6+9}(2) = 0.8 \text{ A}$$


Finally, combine the results:

$$i_x = i'_x + i''_x = 0.2 + 0.8 = 1.0 \text{ A}$$



Superposition with a Dependent Source₁

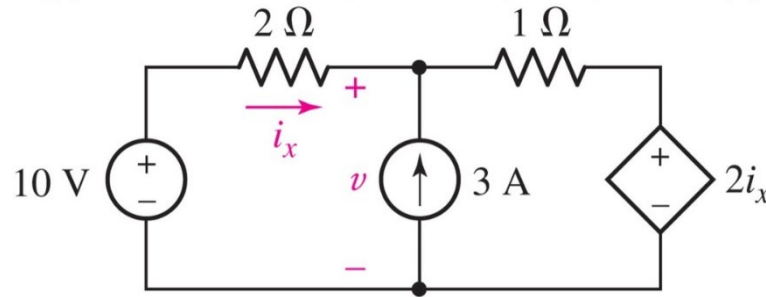Use superposition to solve for the current i_x



Nodal analysis:

Apply KCL at node 1: $\frac{v_1 - 10}{2} + \frac{v_1 - 2i_x}{1} = 3$


Relate i_x with v_1 : $i_x = \frac{10 - v_1}{2}$

Solve: $v = v_1 = 7.2 \text{ V}$, $i_x = 1.4 \text{ A}$




Superposition with a Dependent Source₂

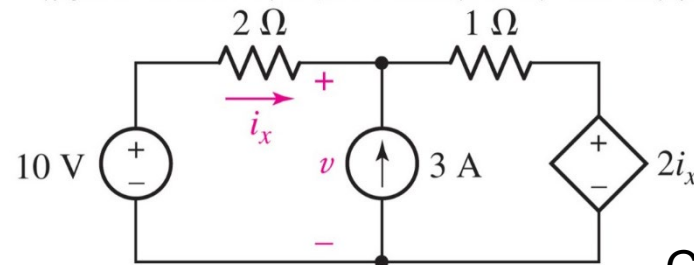Use superposition to solve for the current i_x



Voltage source off

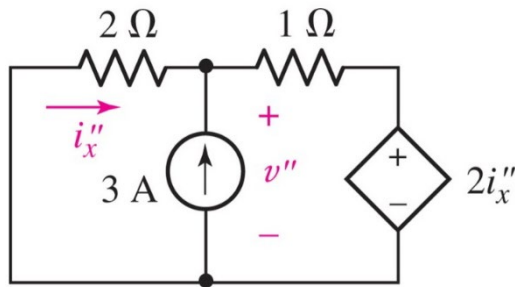


Apply KCL at node 1: $\frac{v''}{2} + \frac{v'' - 2i''_x}{1} = 3$

Relate i''_x with v'' : $i''_x = \frac{-v''}{2}$

Solve: $i''_x = -0.6 \text{ A}$

Current source off

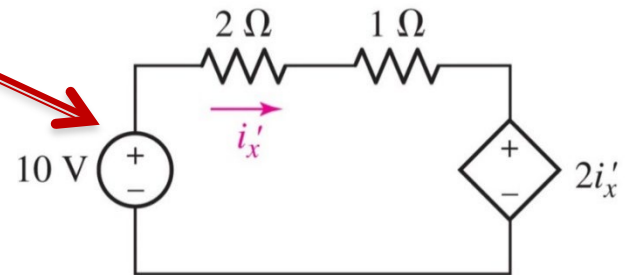

$$-10 + 2i'_x + i'_x + 2i'_x = 0$$

$$i'_x = 2 \text{ A}$$


$$i_x = i'_x + i''_x = 2 + (-0.6) = 1.4 \text{ A}$$

When applying superposition to circuits with *dependent* sources, these *dependent* sources **are never "turned off."**



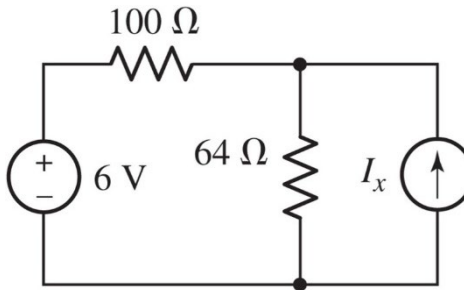Example: Power Ratings

Each resistor is rated to a maximum of 250 mW. Determine the maximum *positive* current to which the source I_x can be set before any resistor exceeds its power rating.




The maximum current of each resistor

$$i_{max} = \sqrt{\frac{P_{max}}{R}}, \quad i_{100\Omega} < 50\text{mA}, \quad i_{64\Omega} < 62.5\text{mA}$$


$$V_{max} = \sqrt{P_{max}R}, \quad V_{100\Omega} < 5\text{V}, \quad V_{64\Omega} < 4\text{V}$$



Example: Power Ratings

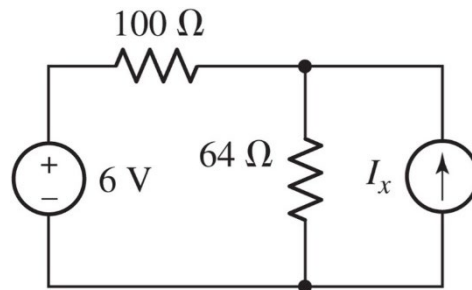


Current source off

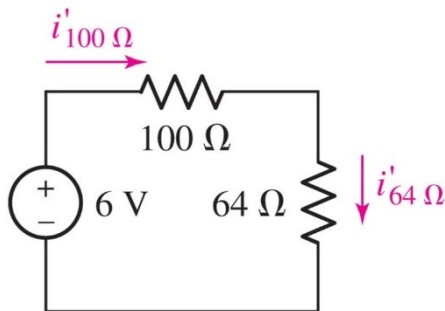

$$i'_{100\Omega} = i'_{64\Omega} = 36.59\text{mA}$$

Voltage source off

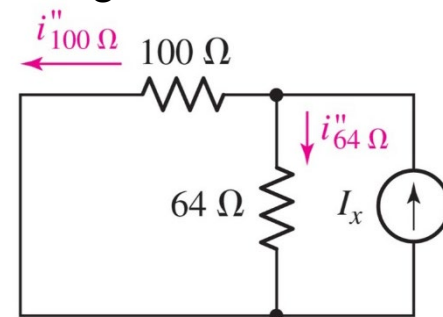

$$i''_{100\Omega} = \frac{64}{100 + 64} I_x = 0.39 I_x$$

$$i''_{64\Omega} = \frac{100}{100 + 64} I_x = 0.61 I_x$$

$$i''_{100\Omega} - i'_{100\Omega} < 50\text{mA}$$


$$i'_{64\Omega} + i''_{64\Omega} < 62.5\text{mA}$$

$$\text{Answer : } I_x < 42.49 \text{ mA}$$



Practical Voltage Sources

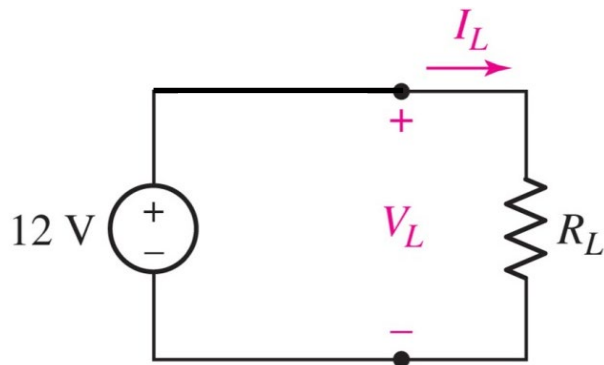Ideal voltage sources: a first approximation model for a battery.




If $R_L = 1\Omega$, $I_L = ?$

If $R_L = 1\mu\Omega$, $I_L = ?$

If $R_L = 0$, $I_L = ?$

Why do real batteries have a current limit and experience voltage drop as current increases?



Two battery models:

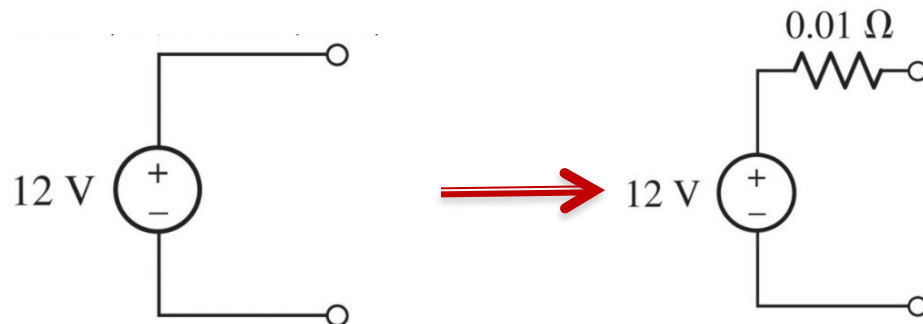

Practical Source: Effect of Connecting a Load

The practical voltage source model:

$$V_L = 12 - 0.01 I_L$$

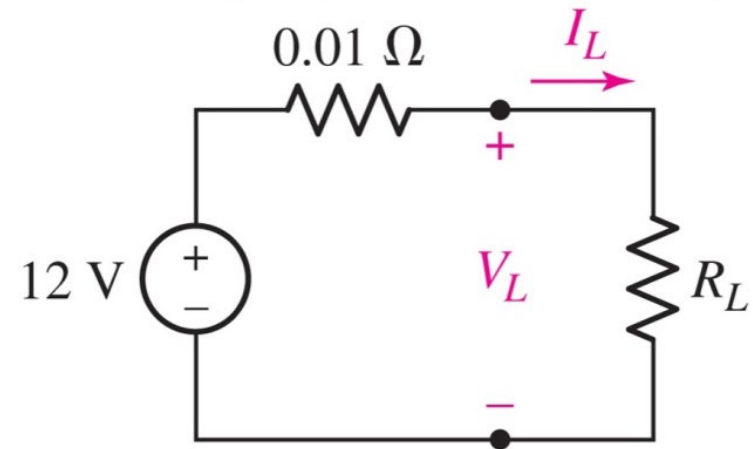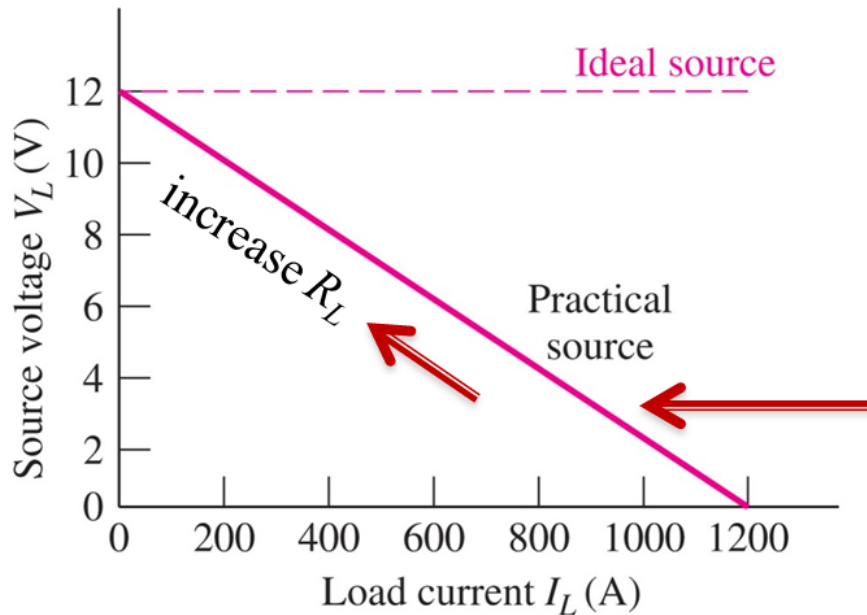


This line represents all possible R_L



Practical Voltage Source

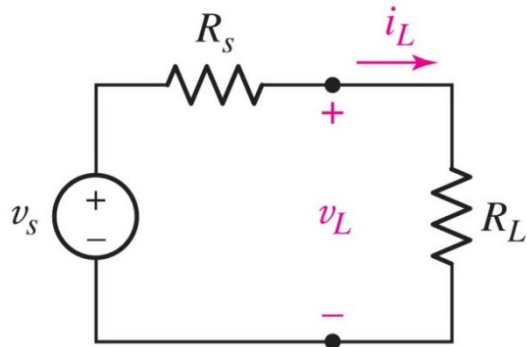The source has an internal resistance or output resistance, which is modeled as R_s




The linear relationship between v_L and i_L :

$$v_L = v_s - R_s i_L$$


short circuit current (when $R_L=0$)

open circuit voltage (when $R_L=\infty$)

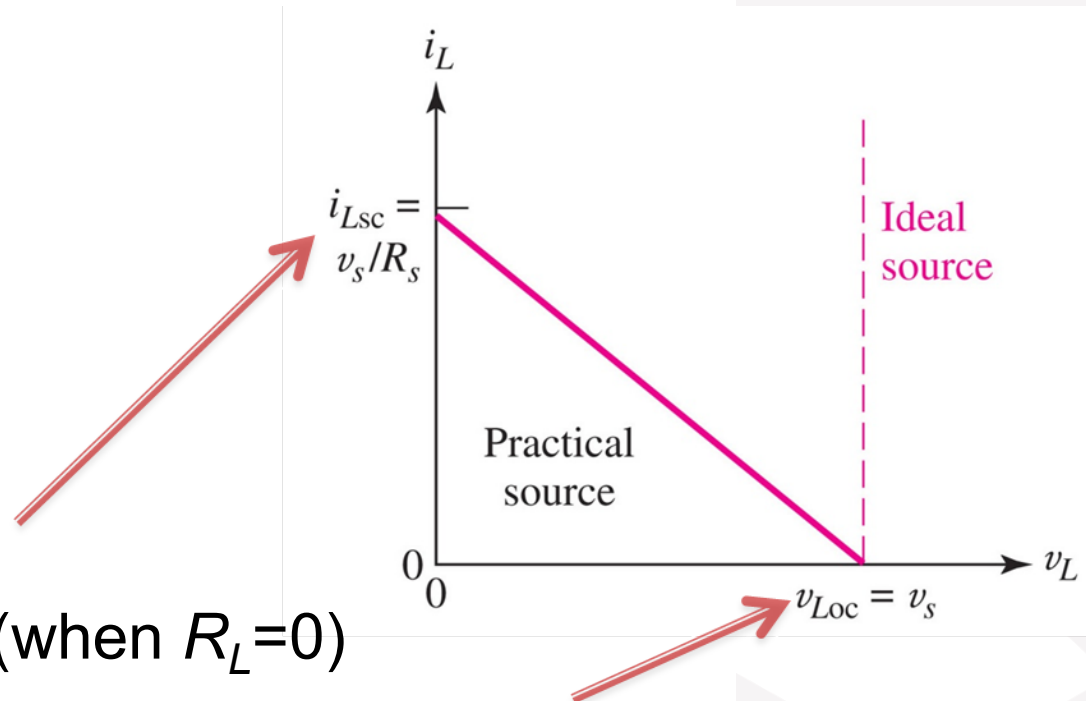

Practical Current Source

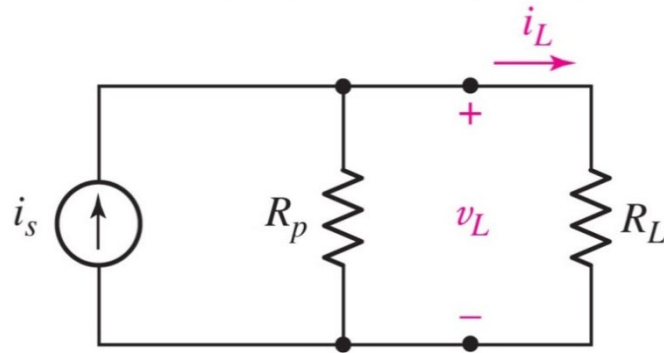The source has an internal *parallel* resistance which is modeled as R_p




The linear relationship between v_L and i_L :


$$i_L = i_s - \frac{v_L}{R_p}$$

short circuit current (when $R_L=0$)


open circuit voltage (when $R_L=\infty$)

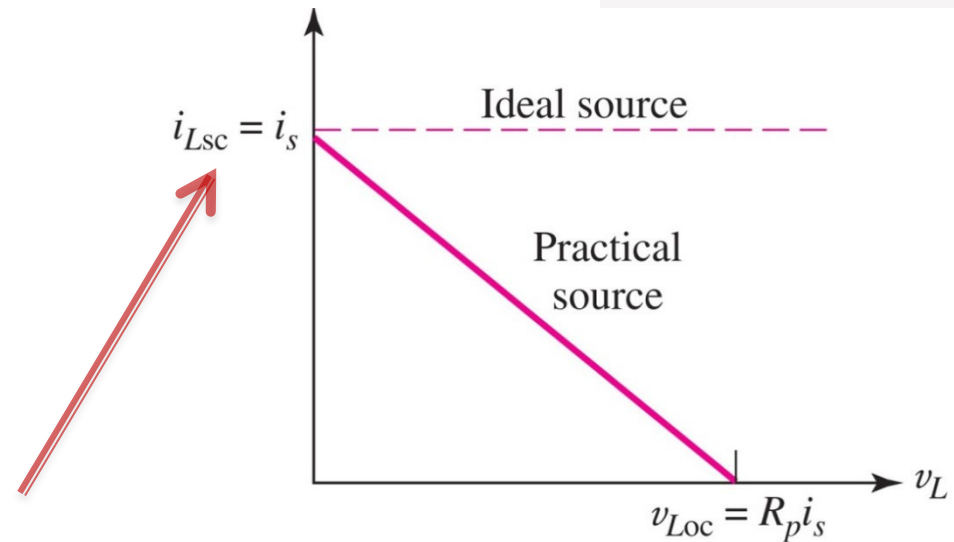

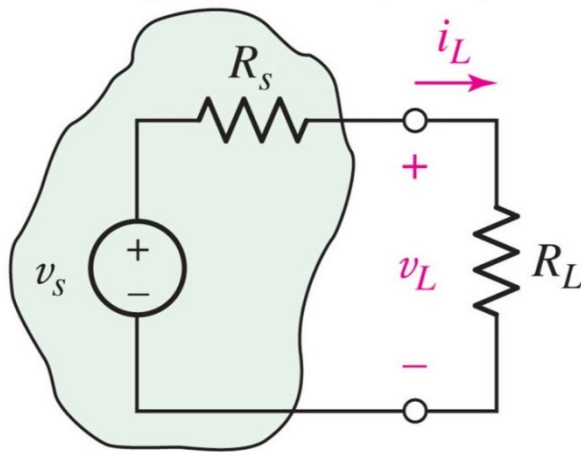Source Transformation and Equivalent Sources



$$v_L = v_s \frac{R_L}{R_s + R_L}$$

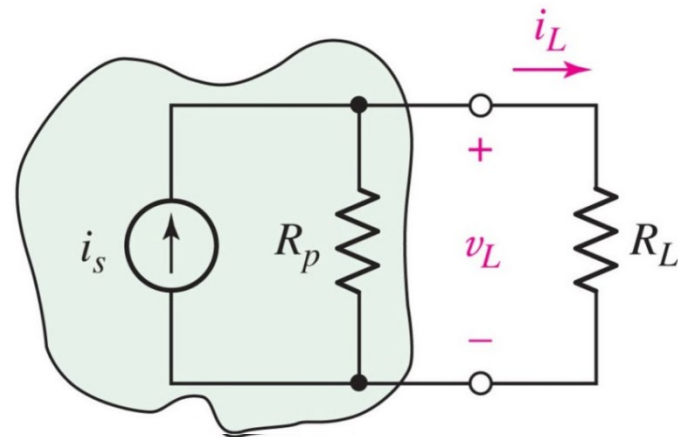

$$v_L = i_s \frac{R_p}{R_p + R_L} \cdot R_L$$

The sources are equivalent if

$$R_s = R_p \text{ and } v_s = i_s R_s$$



Source Transformation

The circuits (a) and (b) are equivalent at the terminals.

$$R_s = R_p = 2\Omega$$


$$v_s = i_s R_s = 3A * 2\Omega = 6V$$

If given circuit (a), but circuit (b) is more convenient, switch them!


This process is called

source transformation.

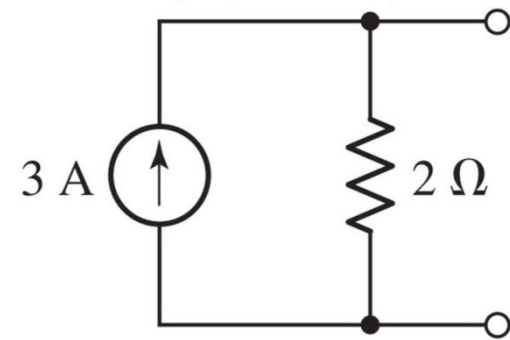The **head** of the current source arrow corresponds to the “+” terminal of the voltage source.



(a)

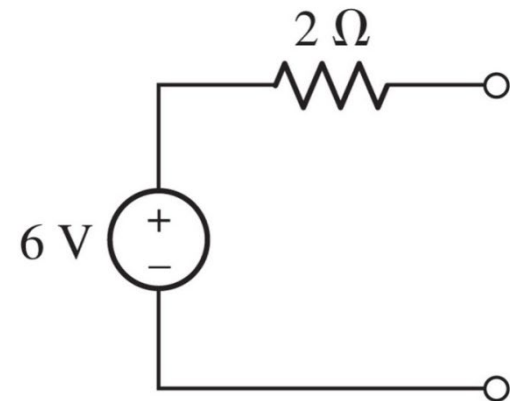

(b)



Source Transformation

If $R_L = 4\Omega$:


(a) Load terminal:

$$i_L = \frac{R_s}{R_s + R_L} i_s = 1A, V_L = i_L R_L = 4V,$$

$$P_{R_L} = i_L v_L = 4W$$

Inside the practice source:
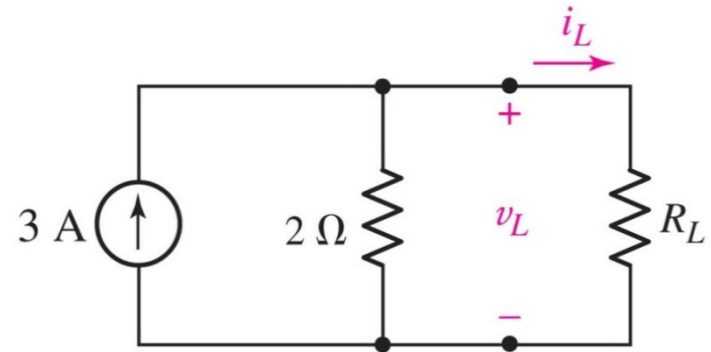
$$P_{3A} = -3A * v_L = -12W, P_{R_s} = v_L^2 / R_s = 8W$$



(a)


(b) Load terminal:

$$i_L = \frac{v_s}{R_s + R_L} = 1A, V_L = i_L R_L = 4V,$$

$$P_{R_L} = i_L v_L = 4W$$

Inside the practice source:
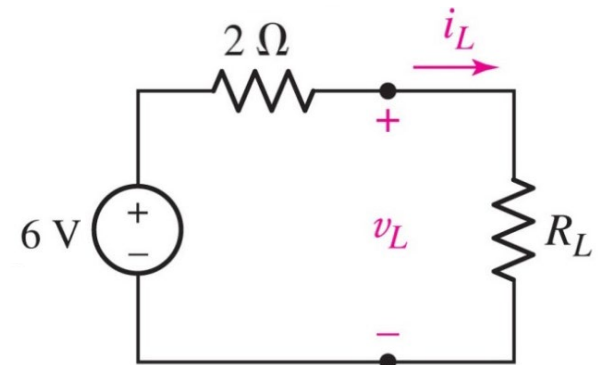
$$P_{6V} = -6V * i_L = -6W, P_{R_s} = i_L^2 * R_s = 2W$$




(b)

The two practical sources are equivalent only with respect what transpires at the **load terminals**; they are **not equivalent internally**!



Example: Source Transformation

Calculate the current I in the circuit below:

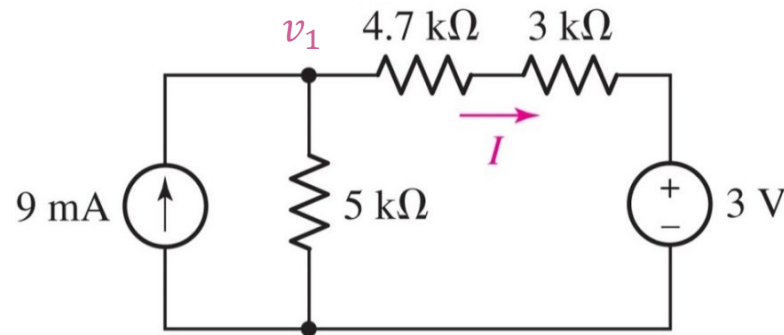

Method 1:

$$\text{Apply KCL: } 9\text{mA} - \frac{v_1}{5\text{k}\Omega} - \frac{v_1 - 3\text{V}}{4.7\text{k}\Omega + 3\text{k}\Omega} = 0$$


$$v_1 = 28.465\text{ V}$$

$$I = \frac{v_1 - 3\text{V}}{7.7\text{k}\Omega} = 3.307\text{mA}$$



Example: Source Transformation

Calculate the current I in the circuit below using **source transformation**

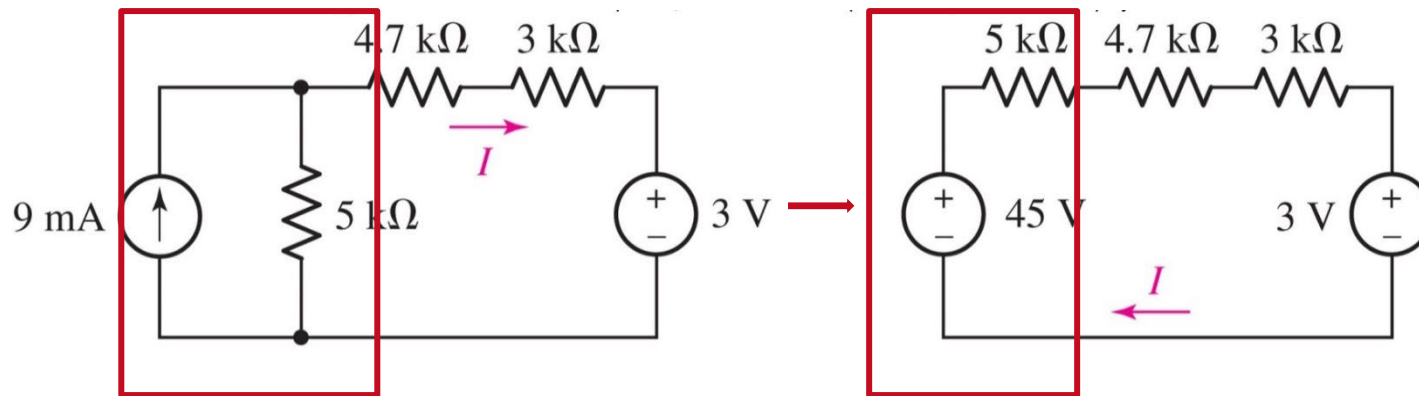

Method 2: **source transformation**

Equivalent voltage source:


$$R_s = R_p = 5k\Omega, V_s = i_s R_s = 45V$$

$$I = (45 - 3) / (5 + 4.7 + 3) = 3.307 \text{ mA}$$





Thévenin Equivalent Circuits

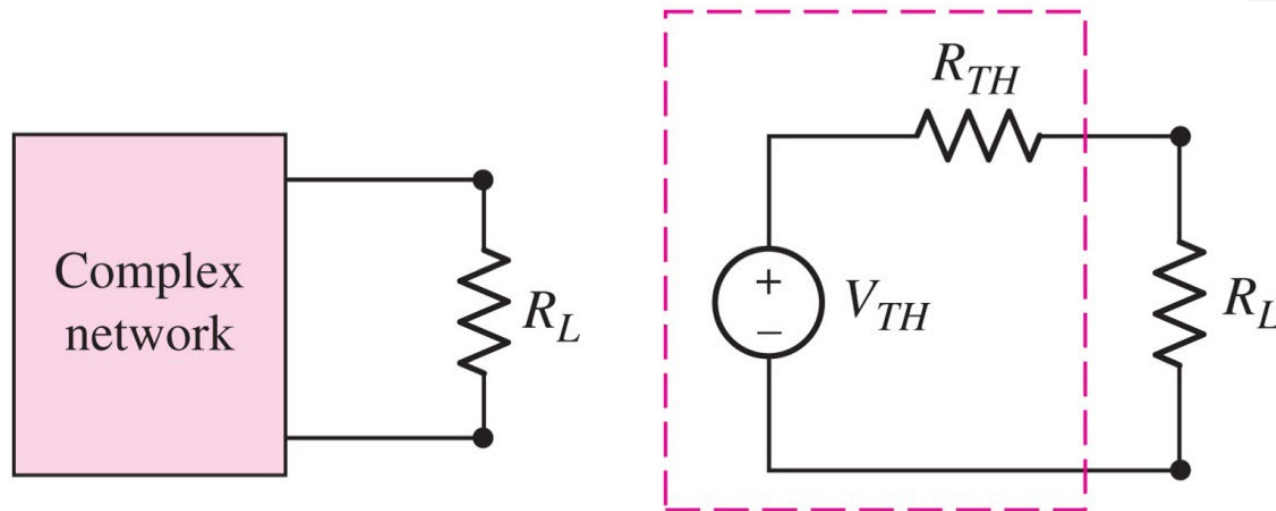Thévenin's theorem: a linear network can be replaced by its Thévenin equivalent circuit, as shown below:





Thévenin Equivalent using Source Transformation ²⁷

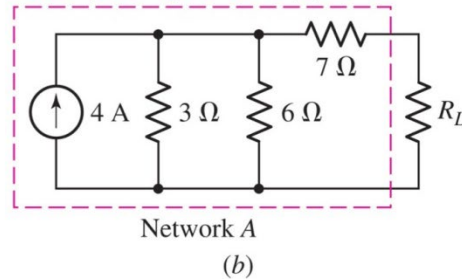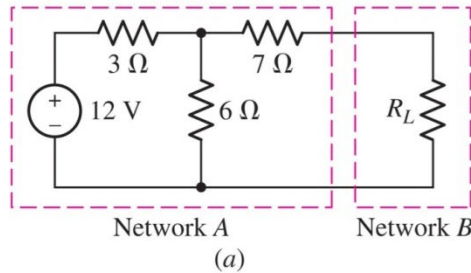
We can repeatedly apply source transformation on network A to find its Thévenin equivalent circuit.



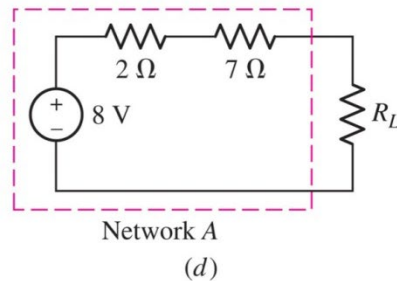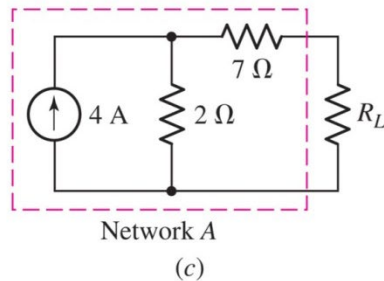(a) to (b) Source transformation:
 $R_p = R_s = 3\Omega, i_s = \frac{v_s}{R_s} = 4A$



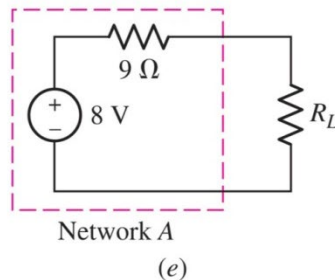(c) to (d) Source transformation:
 $R_s = R_p = 2\Omega, v_s = i_s R_s = 8V$



This method has limitations- not all circuits can be source transformed.



Finding the Thévenin Equivalent



Step1: Disconnect the load ($R_L = \infty$). Find the open circuit voltage v_{oc}

Step2: Find the equivalent resistance R_{eq} of the network with all independent sources turned off.


Then:

$$V_{TH} = v_{oc} \text{ and}$$

$$R_{TH} = R_{eq}$$

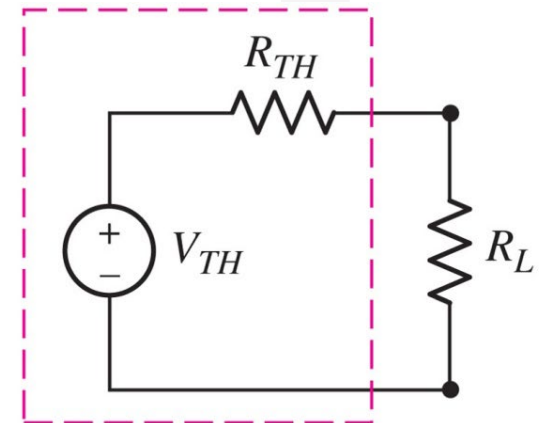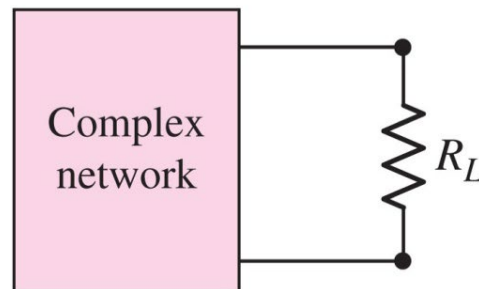


Thévenin Example

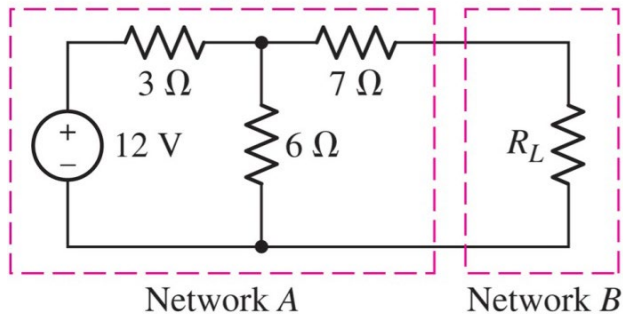


$$V_{TH} = v_{oc} \text{ and}$$


$$R_{TH} = R_{eq}$$

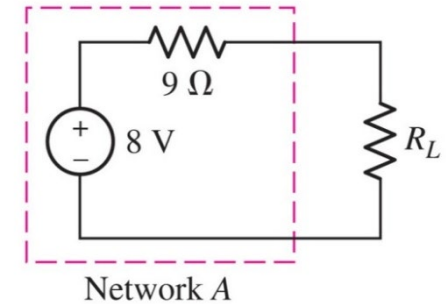

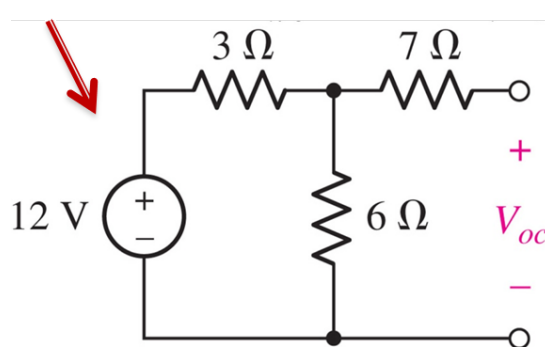Disconnect the load ($R_L = \infty$). Find the open circuit voltage v_{oc}



$$V_{oc} = 12 \frac{6}{3 + 6} = 8V$$

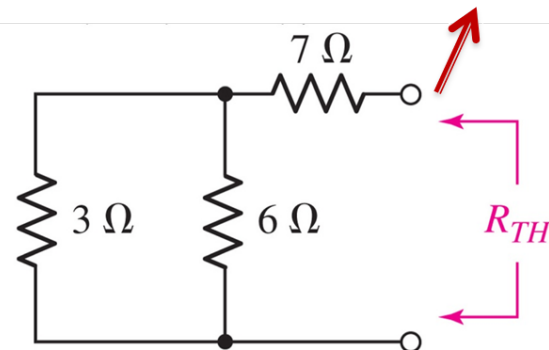



Find R_{eq} of the network with all independent sources turned off.

$$R_{TH} = 3 || 6 + 7 = 9\Omega$$




Norton Equivalent Circuits

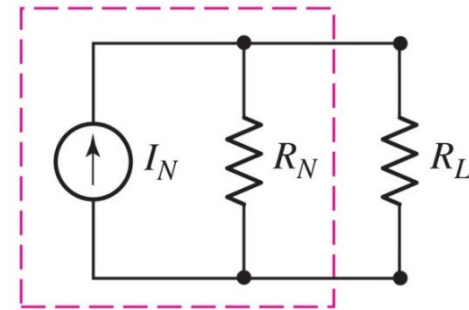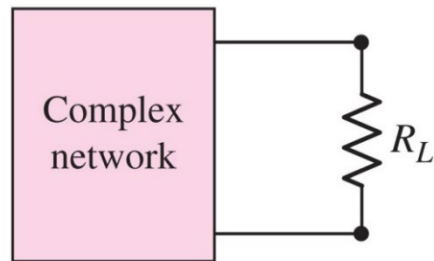Norton's theorem: a linear network can be replaced by its Norton equivalent circuit, as shown below:



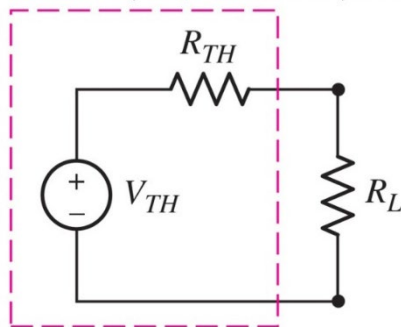The Thévenin and Norton equivalents are source transformations of each other!



$$R_{TH} = R_N = R_{eq} \text{ and } v_{TH} = i_N R_{eq}$$




Finding the Norton Equivalent

Step1: Replace the load with a short circuit. ($R_L = 0$) Find the short circuit current i_{sc}

Step2: Disconnect the load ($R_L = \infty$). Find the equivalent resistance R_{eq} of the network with all independent sources turned off.

Then:

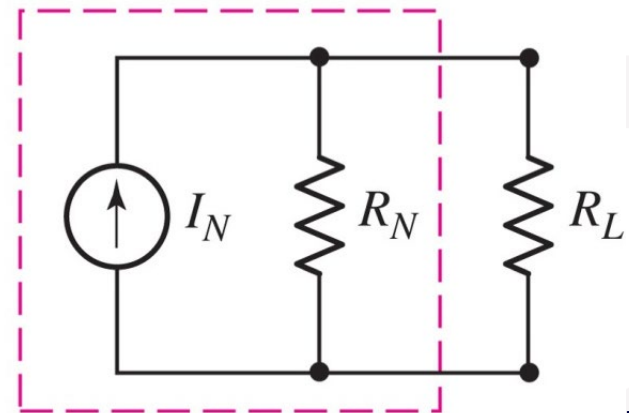
$$I_N = i_{sc} \text{ and } R_N = R_{eq}$$






Example: Norton and Thévenin₁

Find the Thévenin and Norton equivalents for the network faced by the $1\text{ k}\Omega$ resistor.


Answer: next slide

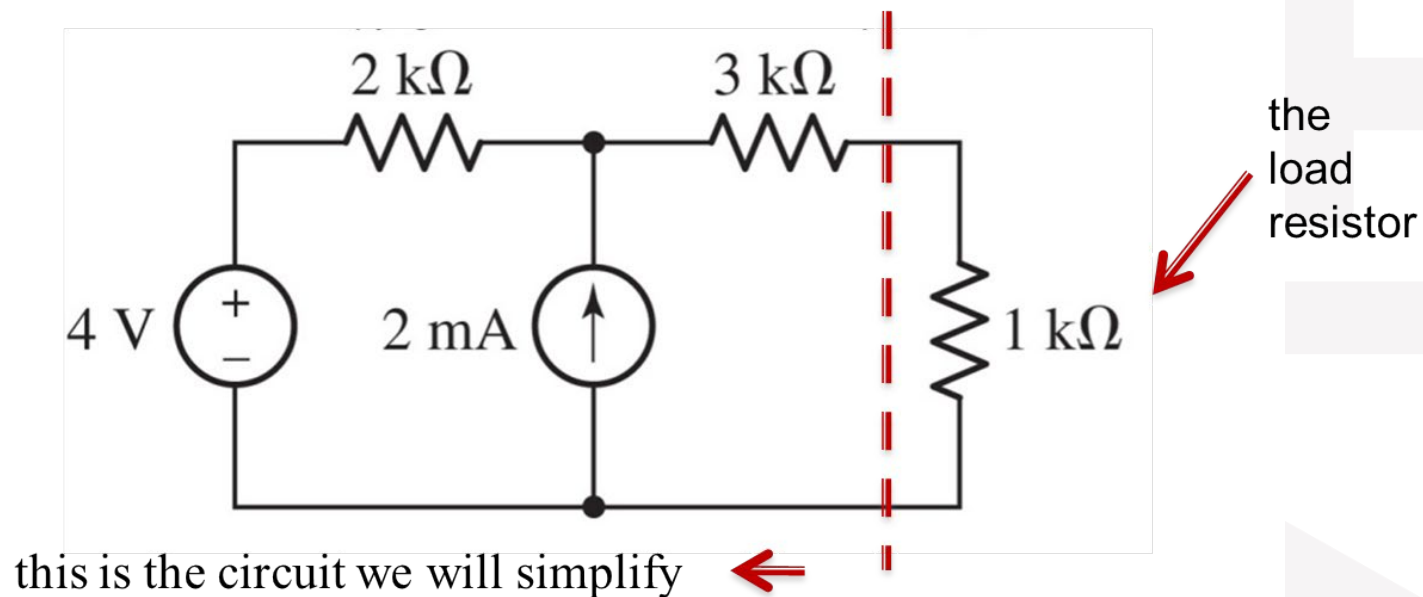

Example: Thévenin and Norton₂

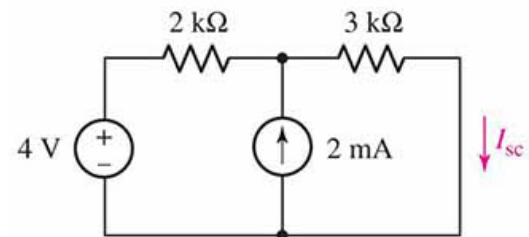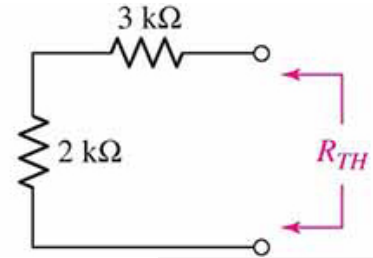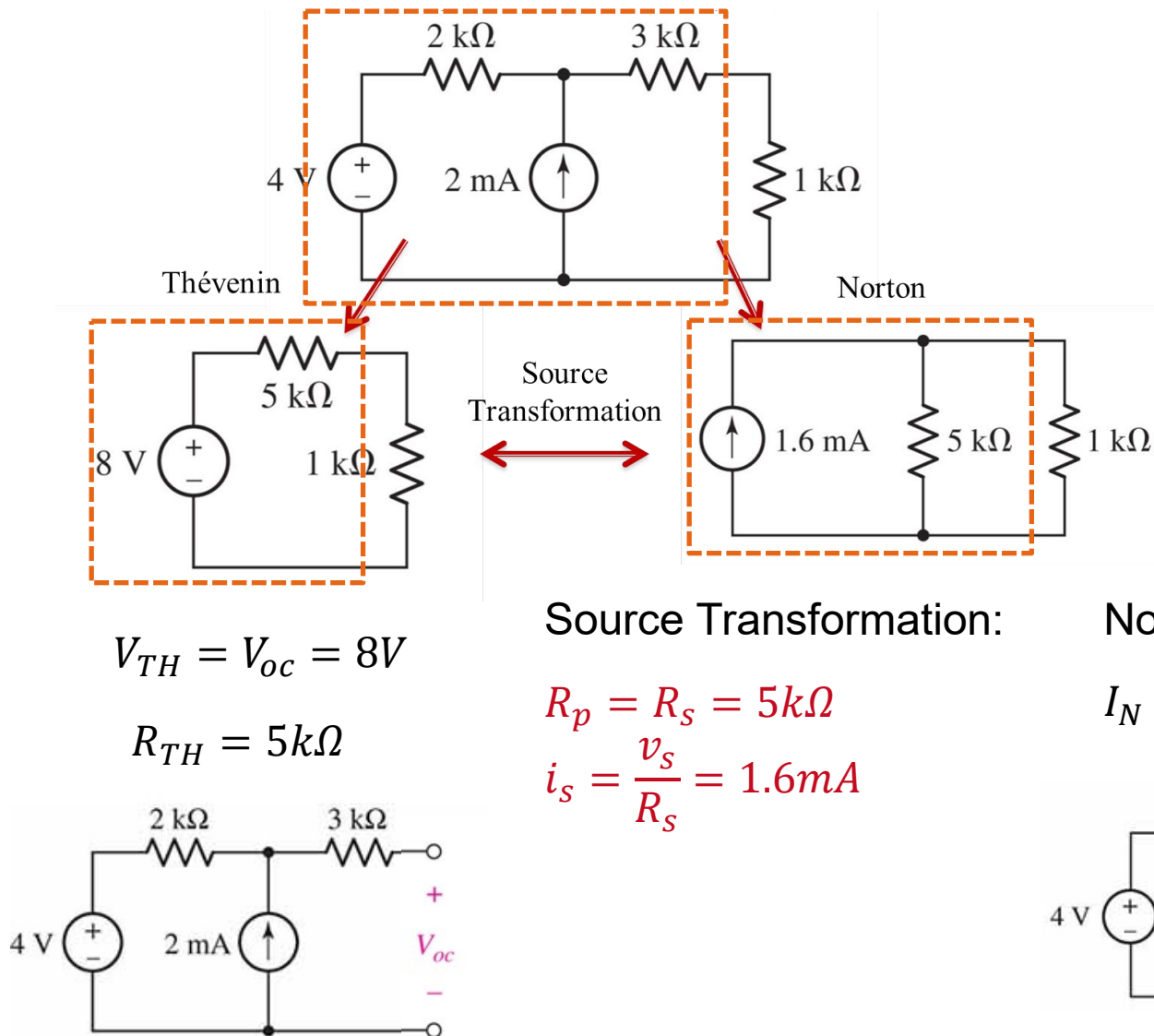

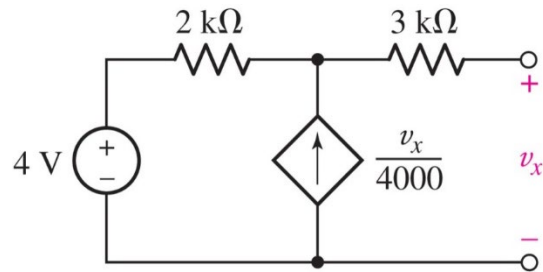Thévenin Example: Handling Dependent Sources₁




Thévenin:

Apply KVL: $-4 + \left(-\frac{v_x}{4000}\right) * 2000 + v_x = 0$

$V_{oc} = v_x = 8V$


$R_{TH} = ?$

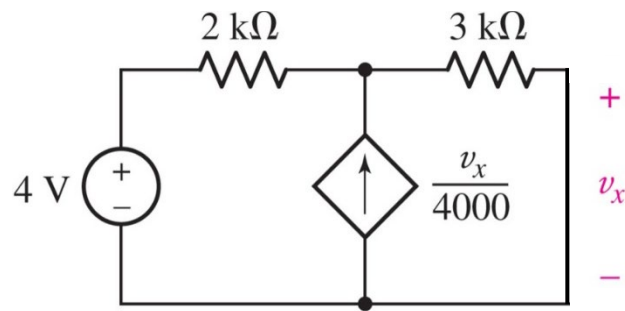

Norton:

$v_x = 0, I_{sc} = \frac{4}{2000 + 3000} = 0.8mA$

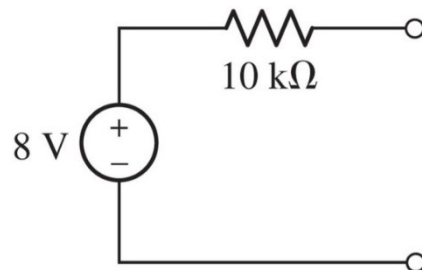$R_{TH} = \frac{V_{oc}}{I_{sc}} = 10k\Omega$





One method to find the Thévenin equivalent of a circuit with a dependent source:

find V_{TH} and I_N and solve for $R_{TH} = V_{TH} / I_N$



Thévenin Example: Handling Dependent Sources₂

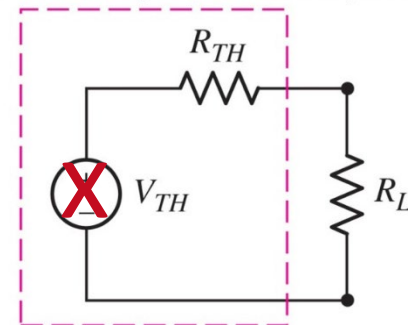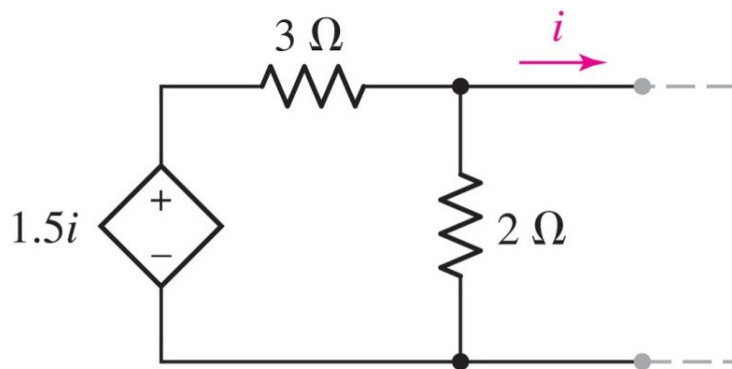Finding the ratio V_{TH} / I_N fails when both quantities are zero




$R_{TH} = ?$

Open circuit:


$$i = 0 \rightarrow V_{oc} = 0$$

Short circuit:

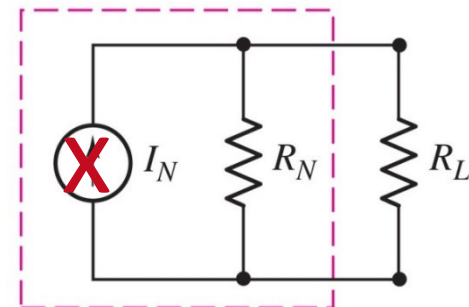
$$-1.5i + 3i = 0 \rightarrow I_{sc} = i = 0$$



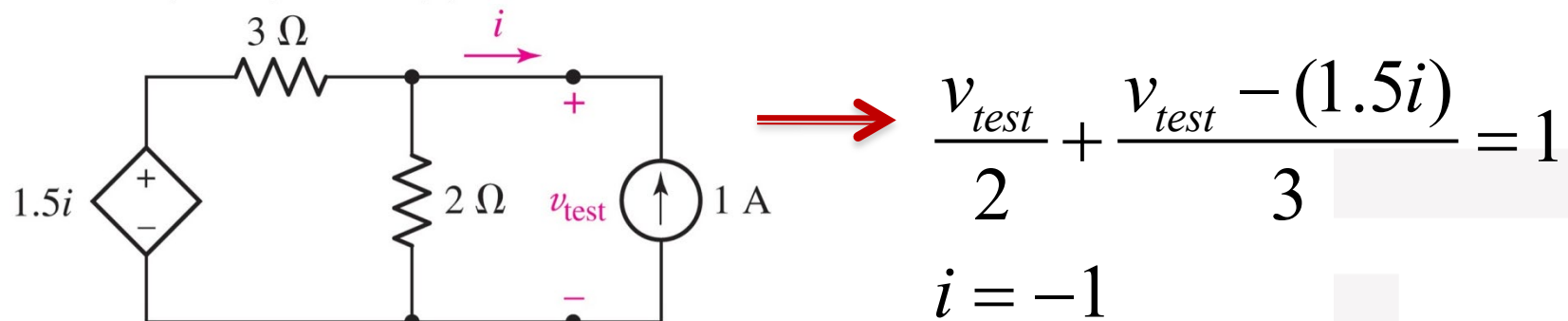Thévenin Example: Handling Dependent Sources₃



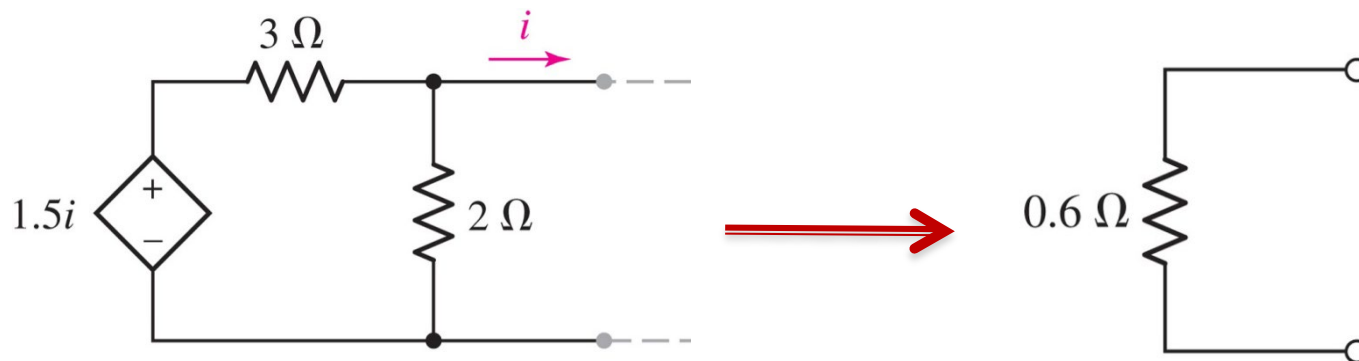Solve: $v_{test} = 0.6 \text{ V}$, and so $R_{TH} = 0.6 \Omega$




One method to find the Thévenin equivalent of a circuit with a dependent source:

apply a test source




Maximum Power Transfer

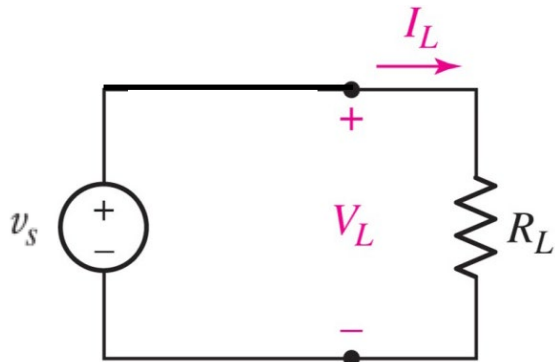What load resistor will allow the **practical source** to deliver the maximum power to the load?



Idear source:

$$p_L = \frac{v_s^2}{R_L}$$

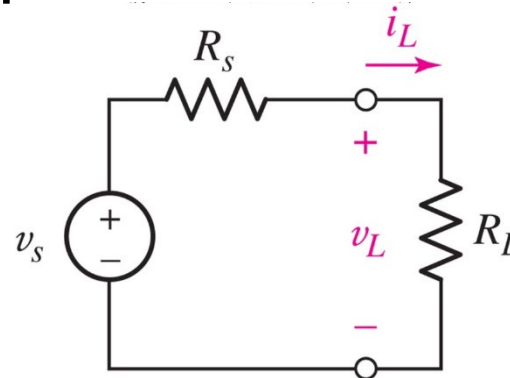

Practical source:

$$p_L = i_L^2 R_L = \frac{v_s^2 R_L}{(R_s + R_L)^2}$$

[solve $dp_L/dR_L = 0$, check $R_L = 0$ & $R_L = \infty$]

Answer: $R_L = R_s$

$$p_{\text{max|delivered to load}} = \frac{v_s^2}{4R_s}$$



Maximum Power Transfer

Maximum power transfer theorem:

An independent voltage source in series with a resistance R_s (or an independent current source in parallel with a resistance R_s) delivers maximum power to a load resistance R_L such that $R_L = R_s$.

An alternative expression:(In terms of the Thévenin equivalent resistance of a network):

A network delivers maximum power to a load resistance R_L when R_L is equal to the Thévenin equivalent resistance of the network (R_{TH}).


$$P_{\max} |_{\text{delivered to load}} = \frac{v_s^2}{4R_s} = \frac{v_{TH}^2}{4R_{TH}}$$



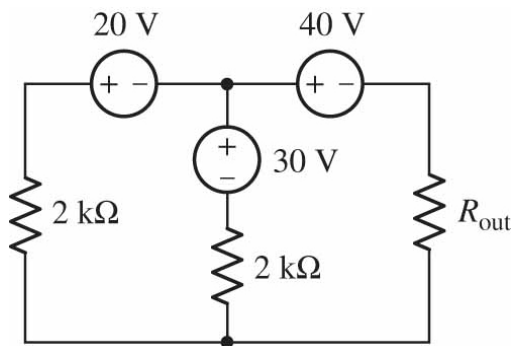Example: Maximum Power Transfer

Consider the circuit below:

- What is the maximum power that can be delivered to R_{out} ?
- If $R_{out} = 3 \text{ k}\Omega$, find the power delivered to it.
- What two different values of R_{out} will have exactly 20 mW delivered to them?




Open circuit:

$$\text{In single loop: } \frac{v+20}{2} + \frac{v-30}{2} = 0$$

$$V_{TH} = V_{oc} = v - 40 = -35V$$

$$R_{TH} = 1k\Omega$$

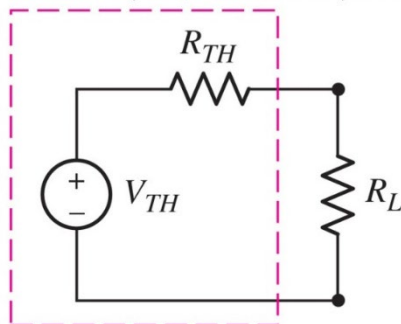

(a) When $R_{out} = R_{TH}$ the load get the maximum power

$$p_{max} = \left(\frac{V_{TH}}{R_{TH} + R_{out}} \right)^2 R_{out} = 306mW$$

$$(b) \quad p = \left(\frac{V_{TH}}{R_{TH} + R_{out}} \right)^2 R_{out} = 230mW$$


$$(c) \left(\frac{V_{TH}}{R_{TH} + R_{out}} \right)^2 R_{out} = 20mW$$

$$R_{out1} = 59.2k\Omega, R_{out2} = 16.88\Omega$$




Δ -Y (delta-wye) Conversion₁


The following resistors form a Δ :

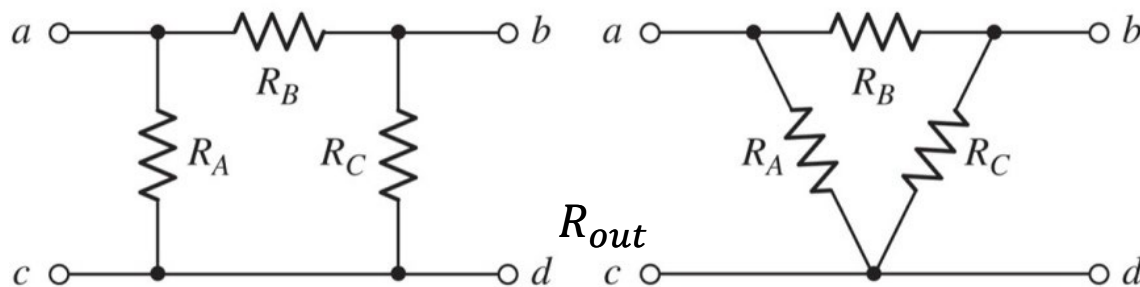

The following resistors form a Y:

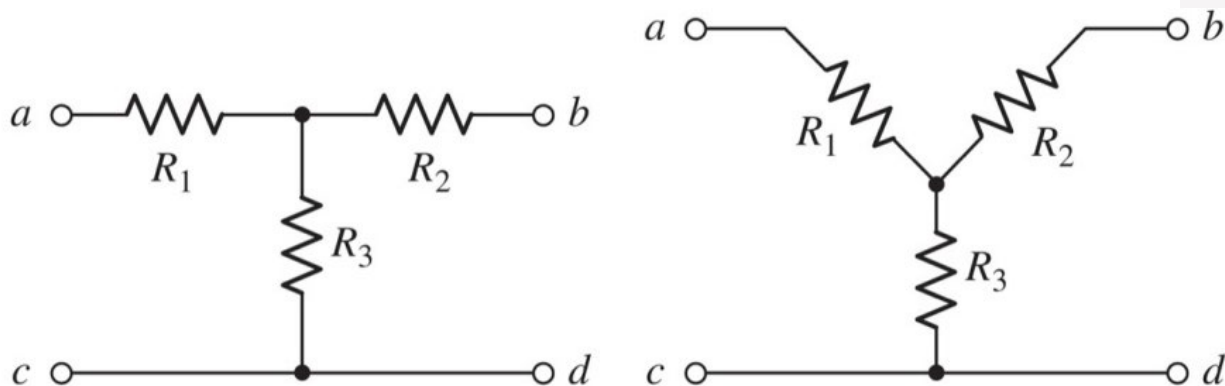

Δ -Y (delta-wye) Conversion₂

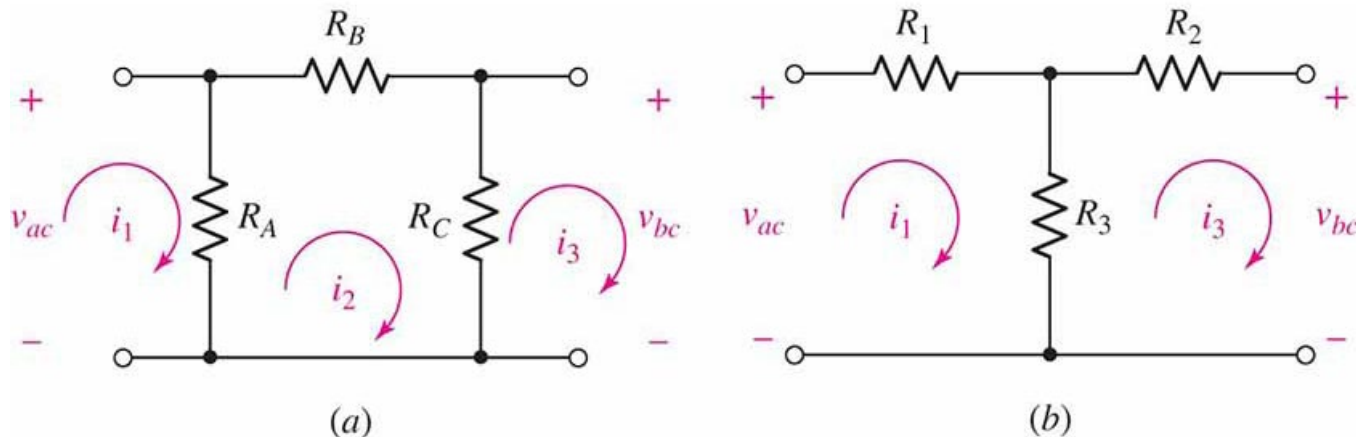

If the two networks are equivalent, then the terminal voltages and currents must be equal.

$$\begin{aligned} R_A i_1 - R_A i_2 &= v_{ac} \\ -R_A i_1 + (R_A + R_B + R_C) i_2 - R_C i_3 &= 0 \\ -R_C i_2 + R_C i_3 &= -v_{bc} \end{aligned}$$

$$\begin{aligned} (R_1 + R_3) i_1 - R_3 i_3 &= v_{ac} \\ -R_3 i_1 + (R_2 + R_3) i_3 &= -v_{bc} \end{aligned}$$




Remove i_2

$$\begin{aligned} \left(R_A - \frac{R_A^2}{R_A + R_B + R_C} \right) i_1 - \frac{R_A R_C}{R_A + R_B + R_C} i_3 &= v_{ac} \\ -\frac{R_A R_C}{R_A + R_B + R_C} i_1 + \left(R_C - \frac{R_C^2}{R_A + R_B + R_C} \right) i_3 &= -v_{bc} \end{aligned}$$




Δ -Y (delta-wye) Conversion₃

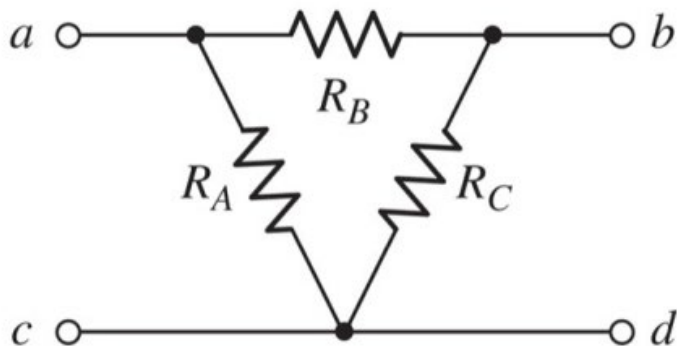

This Δ is equivalent to the Y if
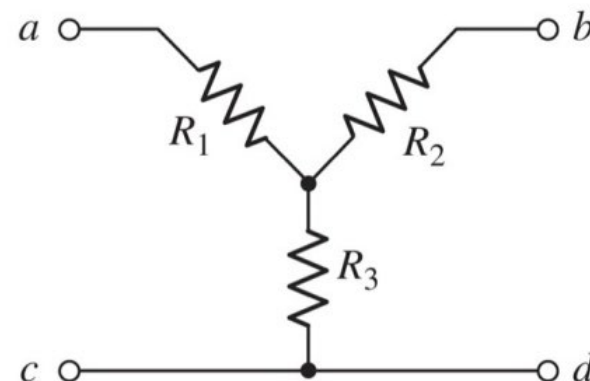
$$\begin{aligned} R_A &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \\ R_B &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \\ R_C &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \end{aligned}$$




This Y is equivalent to the Δ if

$$\begin{aligned} R_1 &= \frac{R_A R_B}{R_A + R_B + R_C} \\ R_2 &= \frac{R_B R_C}{R_A + R_B + R_C} \\ R_3 &= \frac{R_C R_A}{R_A + R_B + R_C} \end{aligned}$$



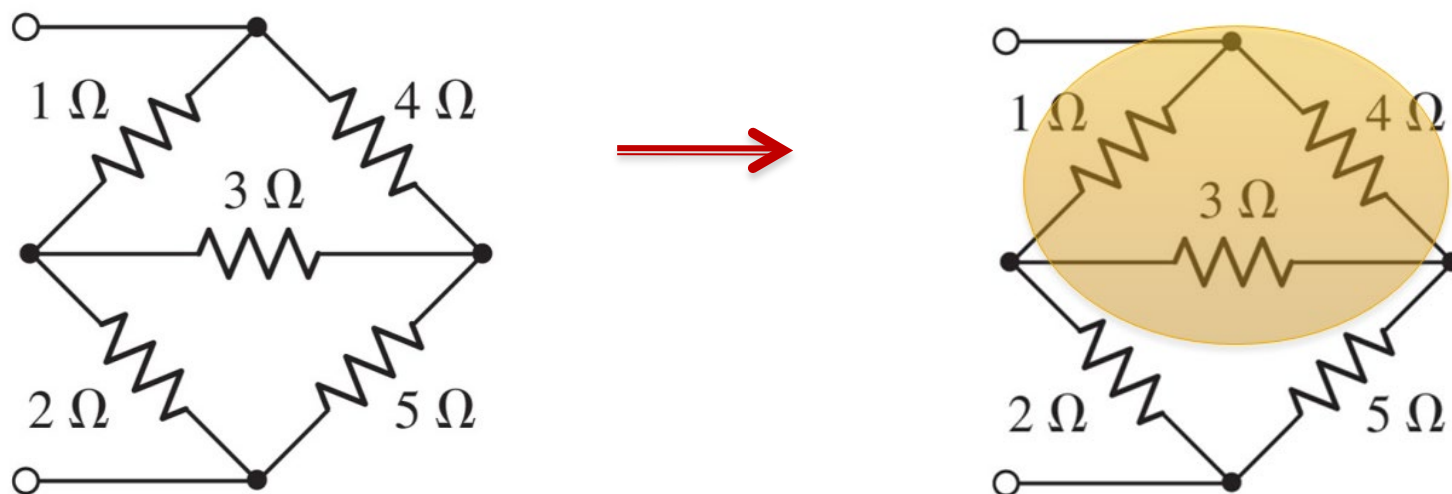
Example: Δ -Y Conversion₁

How do we find the equivalent resistance of the following network? Convert a Δ to a Y




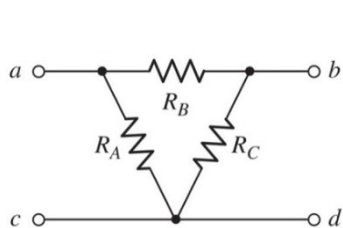Example: Δ -Y Conversion₂



How do we find the equivalent resistance of the following network? Convert a Δ to a Y




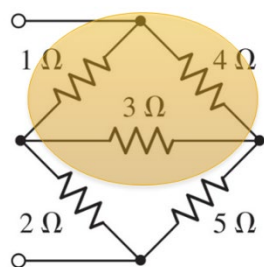
$$\begin{aligned} R_A &= 1\Omega \\ R_B &= 3\Omega \\ R_C &= 4\Omega \end{aligned}$$



Use the Δ to Y equations

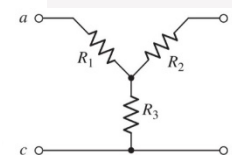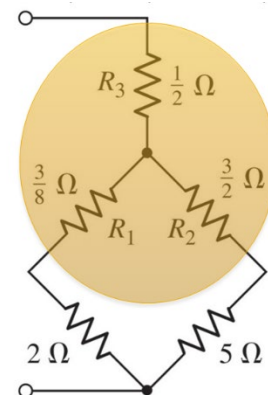
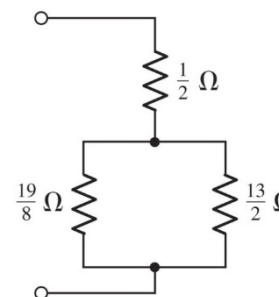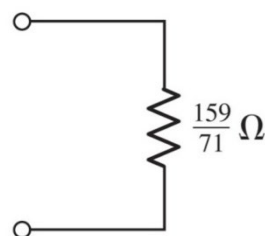
$$\begin{aligned} R_1 &= \frac{R_A R_B}{R_A + R_B + R_C} \\ R_2 &= \frac{R_B R_C}{R_A + R_B + R_C} \\ R_3 &= \frac{R_C R_A}{R_A + R_B + R_C} \end{aligned}$$





Use standard serial and parallel combinations



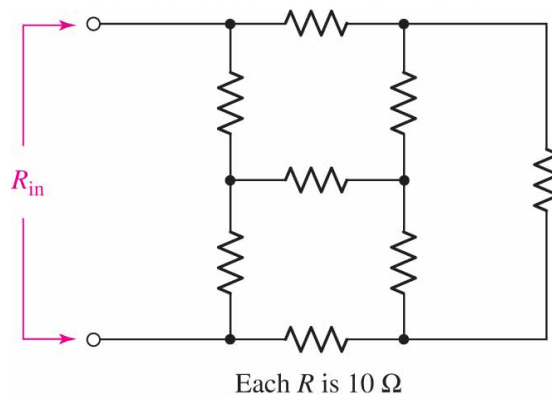Example: Δ -Y Conversion₃

Use the technique of Y- Δ conversion to find the Thévenin equivalent resistance of the circuit



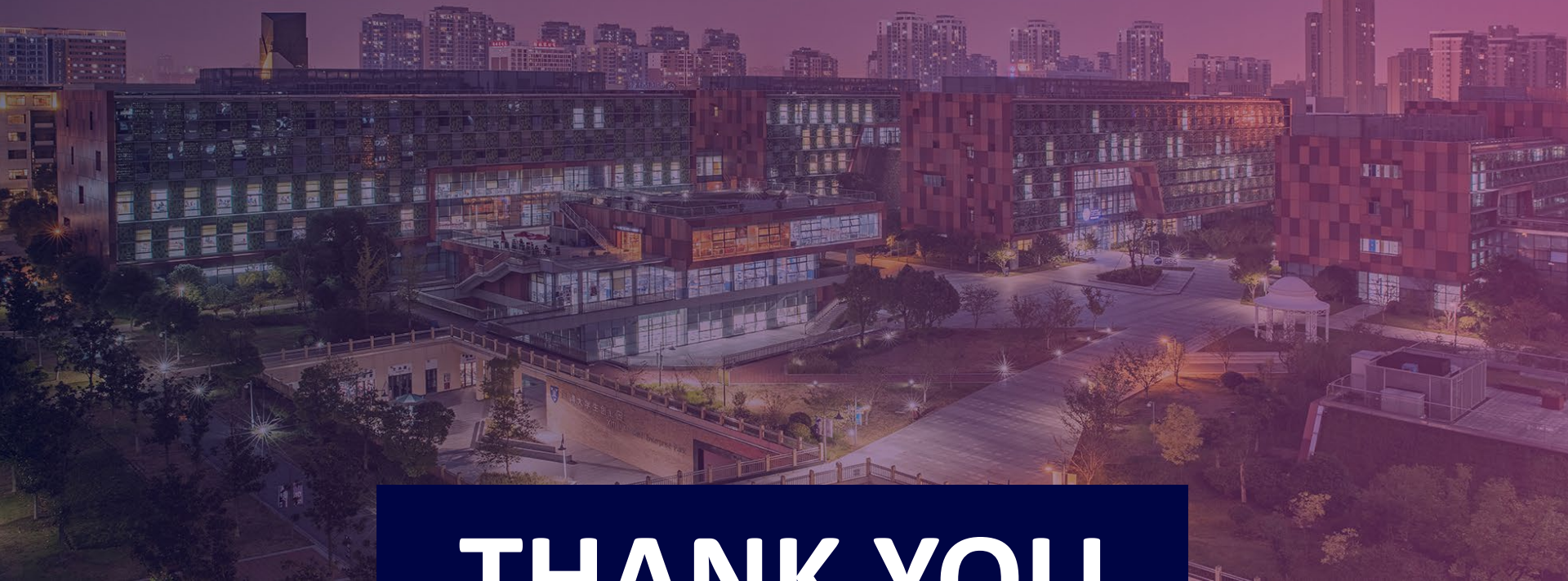

THANK YOU



Xi'an Jiaotong-Liverpool University
西交利物浦大學

