

EEE205 – Digital Electronics (II)

Lecture 11

Xiaoyang Chen, Jiangmin Gu, Ming Xu

Dept of Electrical & Electronic Engineering


XJTLU

In This Session

- Design of Synchronous Counters

General Model of Sequential Circuits

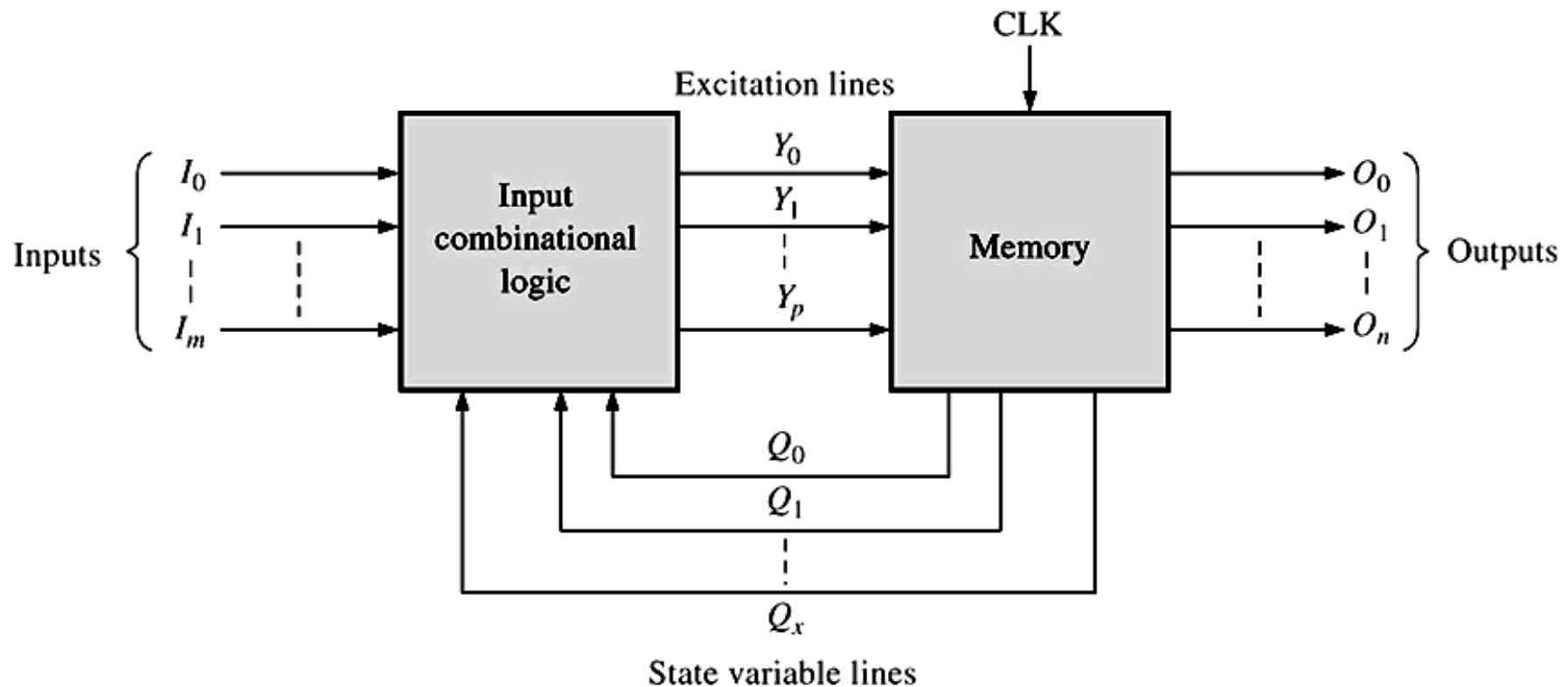- A sequential circuit consists of a combinational logic section and a memory section (flip-flops).
- To design a sequential circuit (**state machine**) is to decide the combinational logic.




Design of Synchronous Counters

Step 1: State Diagram

- A **state diagram** shows the progression of states when the counter is clocked.

 Example: a 3-bit **Gray code counter**, which exhibits only a single bit change from one code number to the next.



Design of Synchronous Counters

Step 2: Next-State Table


- A **next-state table** lists the present state along with the corresponding next state of the counter.

Present State			Next State		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

Design of Synchronous Counters

Step 3: Flip-Flop Transition Table

 - A transition table lists all possible output transitions and the corresponding inputs.




Output Transitions		Flip-Flop Inputs	
Q_N	Q_{N+1}	J	K
0	→ 0	0	X
0	→ 1	1	X
1	→ 0	X	1
1	→ 1	X	0

Design of Synchronous Counters

More flip-flop transition tables (q^* for next states)


JK flip flop state diagram.

 

JK flip flop design table.

q	q^*	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

D flip flop state diagram

 


D flip flop design table.

q	q^*	D
0	0	0
0	1	1
1	0	0
1	1	1

Design of Synchronous Counters

More flip-flop transition tables (q^* for next states)


SR flip flop state diagram

 

SR flip flop design table

q	q^*	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

T flip flop state diagram

 


T flip flop design table

q	q^*	T
0	0	0
0	1	1
1	0	1
1	1	0

Design of Synchronous Counters

Step 4: Karnaugh Maps

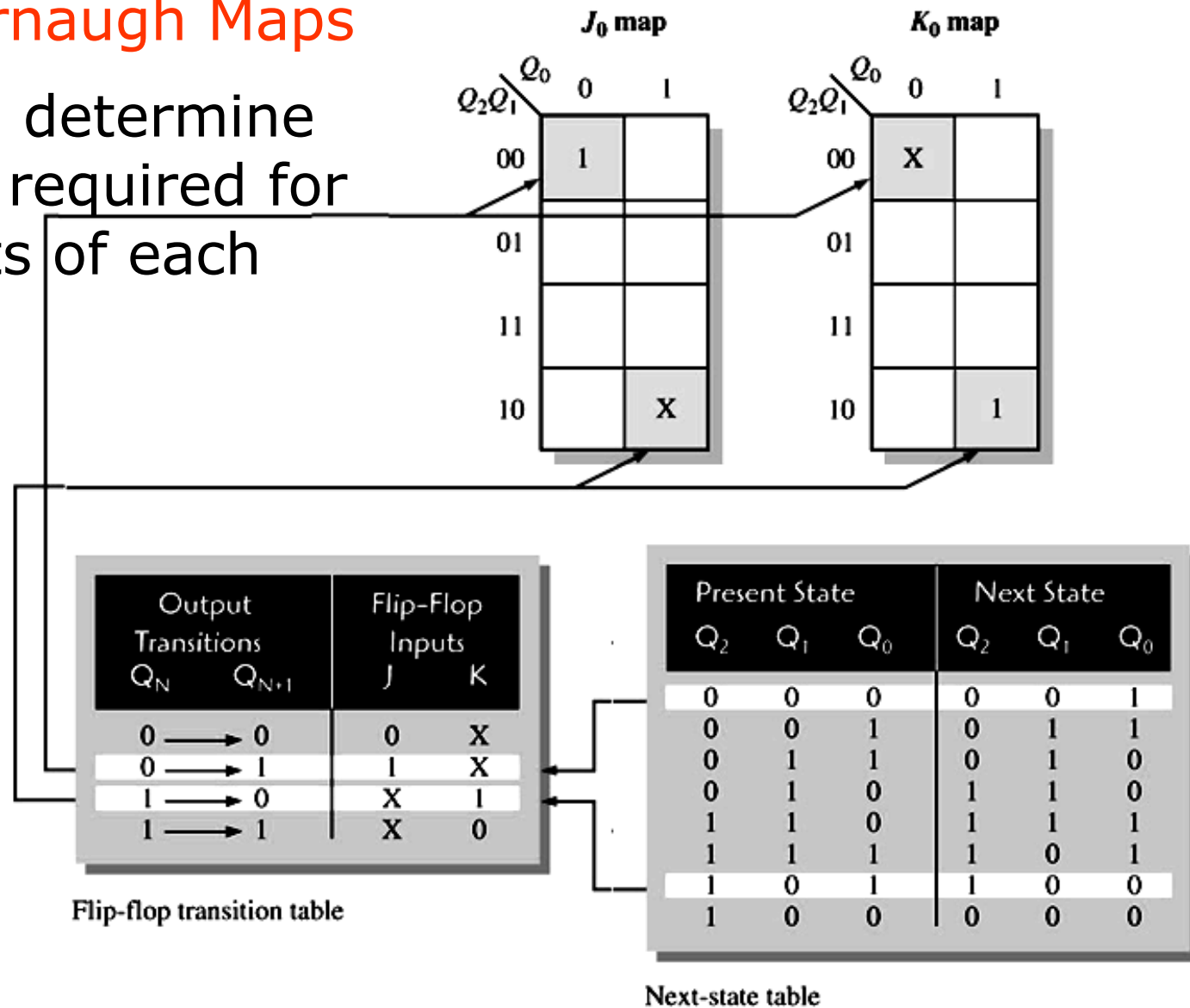- This is to determine the logic required for the inputs of each flip-flop.



Design of Synchronous Counters

Q_2Q_1		Q_0	
		0	1
00		0	0
01		1	0
11	$Q_1\bar{Q}_0$	X	X
10		X	X

J_2 map

Q_2Q_1		Q_0	
		0	1
00		0	1
01		X	X
11		X	X
10		0	0

J_1 map

Q_2Q_1		Q_0	
		0	1
00		1	X
01		0	X
11		1	X
10		0	X

J_0 map

Q_2Q_1		Q_0	
		0	1
00		X	X
01		X	X
11		0	0
10		1	0

K_2 map

Q_2Q_1		Q_0	
		0	1
00		X	X
01		0	0
11		0	1
10		X	X

K_1 map

Q_2Q_1		Q_0	
		0	1
00		X	0
01		X	1
11		X	0
10		X	1

K_0 map

Design of Synchronous Counters

Step 5: Logic Expressions for Flip-Flop Inputs

$$J_0 = Q_2Q_1 + \overline{Q_2}\overline{Q_1} = \overline{Q_2 \oplus Q_1}$$

$$K_0 = Q_2\overline{Q_1} + \overline{Q_2}Q_1 = Q_2 \oplus Q_1$$

$$J_1 = \overline{Q_2}Q_0$$

$$K_1 = Q_2Q_0$$

$$J_2 = Q_1\overline{Q_0}$$

$$K_2 = \overline{Q_1}\overline{Q_0}$$

Design of Synchronous Counters

Step 6: Counter Implementation

$$J_0 = Q_2Q_1 + \overline{Q_2}\overline{Q_1} = \overline{Q_2} \oplus Q_1$$


$$K_0 = Q_2\overline{Q_1} + \overline{Q_2}Q_1 = Q_2 \oplus Q_1$$

$$J_1 = \overline{Q_2}Q_0$$

$$K_1 = Q_2Q_0$$

$$J_2 = Q_1\overline{Q_0}$$


$$K_2 = \overline{Q_1}\overline{Q_0}$$

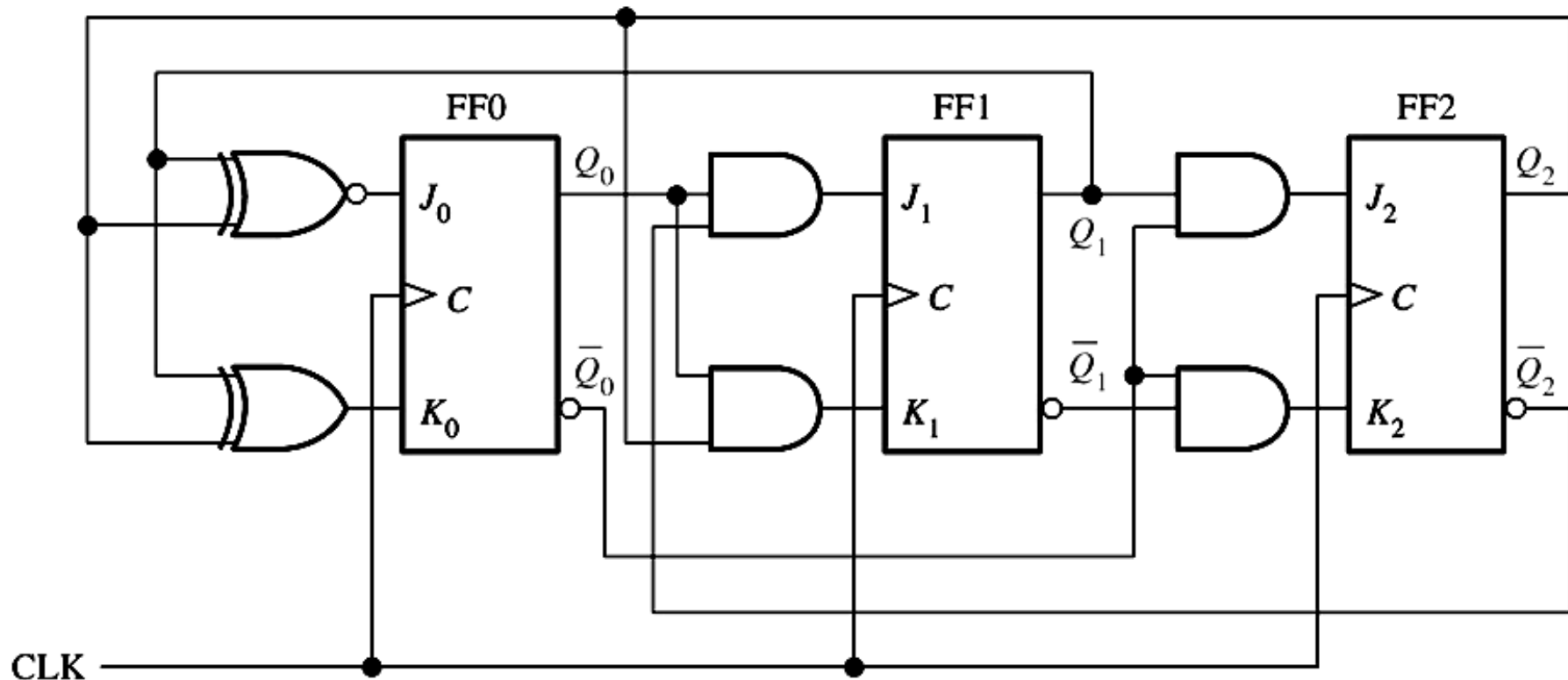

Design of Synchronous Counters

Example: Design a counter with **missing states**, as shown in the state diagram. Use J-K flip-flops.

State Diagram

 


Next-State Table

Present State			Next State		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	1	0	1	0
0	1	0	1	0	1
1	0	1	1	1	1
1	1	1	0	0	1

The next state for an invalid state (0, 3, 4 or 6) is "don't care". The J and K inputs are also "don't cares"

Design of Synchronous Counters

 


Design of Synchronous Counters

$$J_0 = 1, K_0 = \overline{Q_2}$$

$$J_1 = K_1 = 1$$

$$J_2 = K_2 = Q_1$$

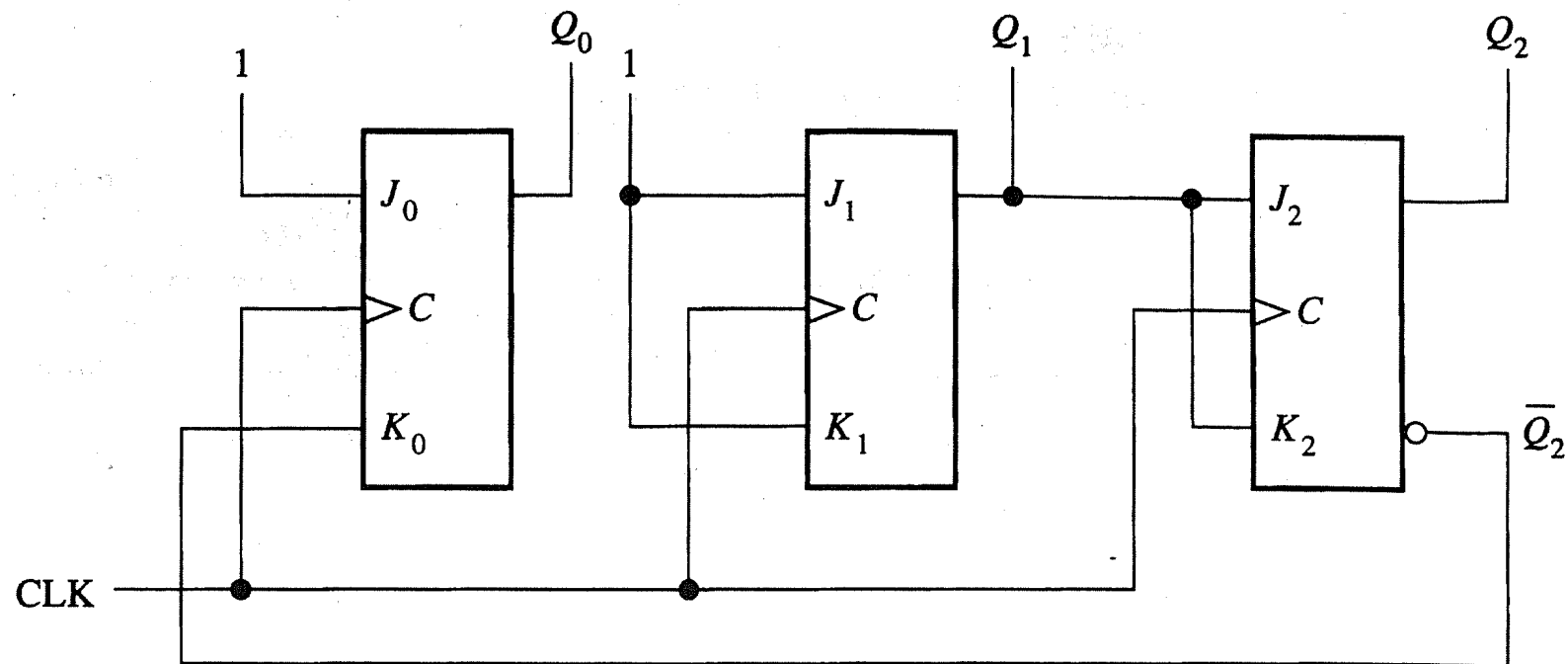

Design of Synchronous Counters

The next state for an invalid state (0, 3, 4 or 6) is originally "don't care" but has a specific value now. From the input equations:

present state									next state		
Q2	Q1	Q0	J2	K2	J1	K1	J0	K0	Q2	Q1	Q0
0	0	0	0	0	1	1	1	1	0	1	1
0	1	1	1	1	1	1	1	1	1	0	0
1	0	0	0	0	1	1	1	0	1	1	1
1	1	0	1	1	1	1	1	0	0	0	1


$$J_0 = 1, K_0 = \overline{Q_2}$$

$$J_1 = K_1 = 1$$

$$J_2 = K_2 = Q_1$$

Design of Synchronous Counters

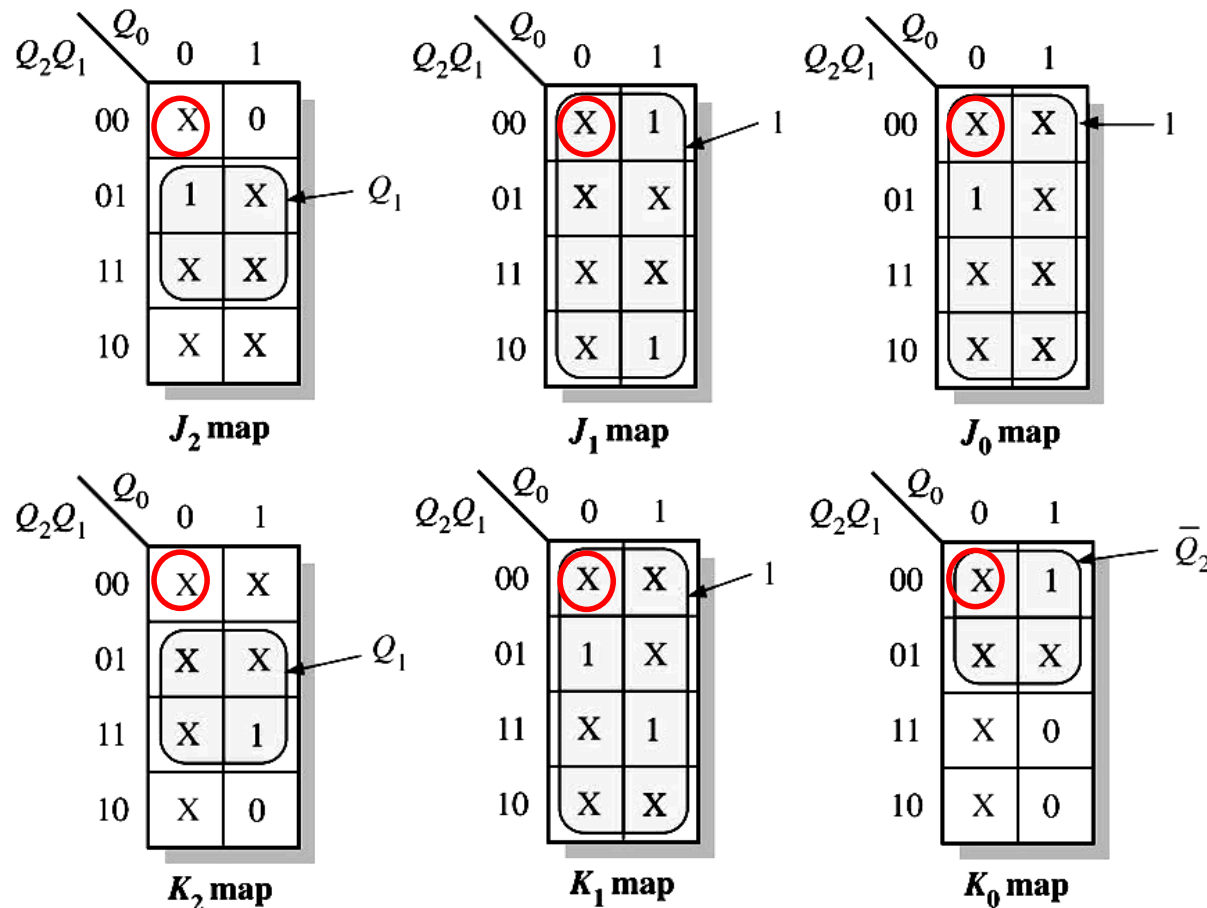The next state of missing states can also be derived from the K-map:




A grouped X is 1;
Otherwise it is 0.

present state

Q2	Q1	Q0
0	0	0
J2 0	K2 0	Q2 0
J1 1	K1 1	Q1 1
J0 1	K0 1	Q0 1

Design of Synchronous Counters

New State Diagram

 

Design of Synchronous Counters

Example: Design a 3-bit up/down counter. Use J-K flip-flops.

x	C	B	A	C^*	B^*	A^*
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	1
0	0	1	1	1	0	0
0	1	0	0	1	0	1
0	1	0	1	1	1	0
0	1	1	0	1	1	1
0	1	1	1	0	0	0
1	0	0	0	1	1	1
1	0	0	1	0	0	0
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

x is up/down control, 0 for up and 1 for down.

Design of Synchronous Counters

xC \ BA	00	01	11	10
00			1	
01	X	X	X	X
11	X	X	X	X
10	1			

J_C

$$J_C = K_C = x'BA + xB'A'$$

xC \ BA	00	01	11	10
00	X	X	X	X
01			1	
11	1			
10	X	X	X	X

Design of Synchronous Counters

xC \ BA	00	01	11	10
00		1	X	X
01		1	X	X
11	1		X	X
10	1		X	X

J_B

$$J_B = K_B = x'A + xA'$$

xC \ BA	00	01	11	10
00	X	X	1	
01	X	X	1	
11	X	X		1
10	X	X		1

Design of Synchronous Counters

xC	BA			
	00	01	11	10
00	1	X	X	1
01	1	X	X	1
11	1	X	X	1
10	1	X	X	1


J_A

$$J_A = K_A = 1$$

		K_A			
		BA	00	01	11
xC	00	X	1	1	X
	01	X	1	1	X
	11	X	1	1	X
	10	X	1	1	X

Design of Synchronous Counters

3-bit up/down counter

 

$$J_C = K_C = x'BA + xB'A'$$

$$J_B = K_B = x'A + xA'$$

$$J_A = K_A = 1$$