

# EEE104 – Digital Electronics

## Lecture 17

Dr. Ming Xu

Dept of Electrical & Electronic Engineering


XJTLU

# In This Session


- Cascaded Counters
- Counter Decoding
- Counter Applications
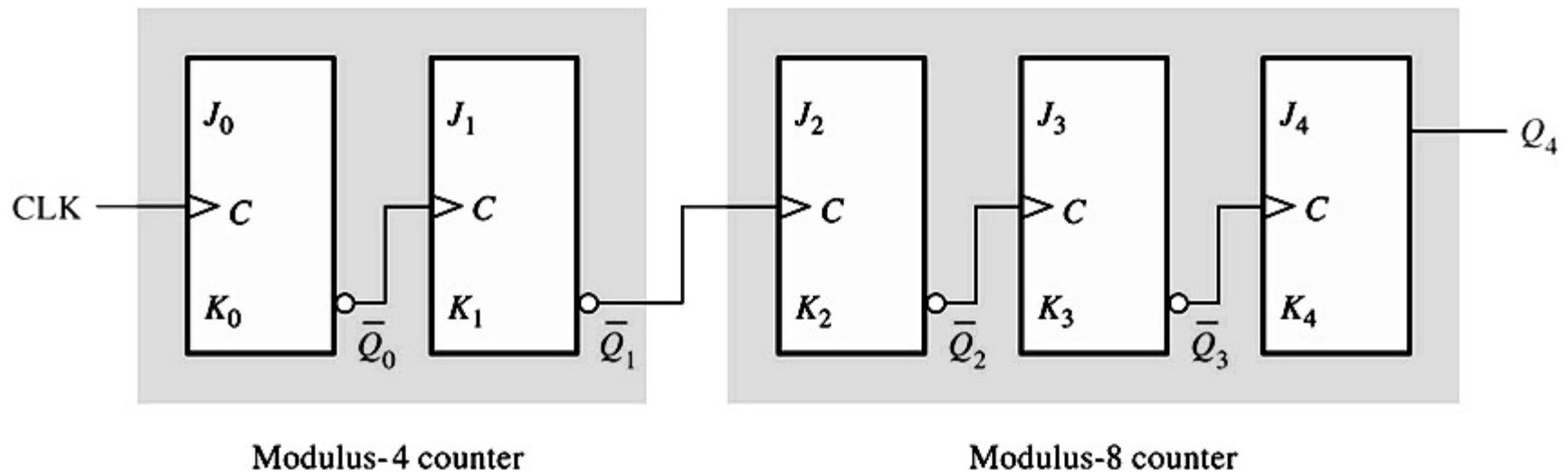
# Cascaded Counters

- **Cascading** means that the output of one counter drives the input of the next counter.
- Counters can be cascaded to achieve higher-modulus operation.



# Cascaded Counters

 


- The overall modulus of cascaded counters equals to the product of the individual moduli.
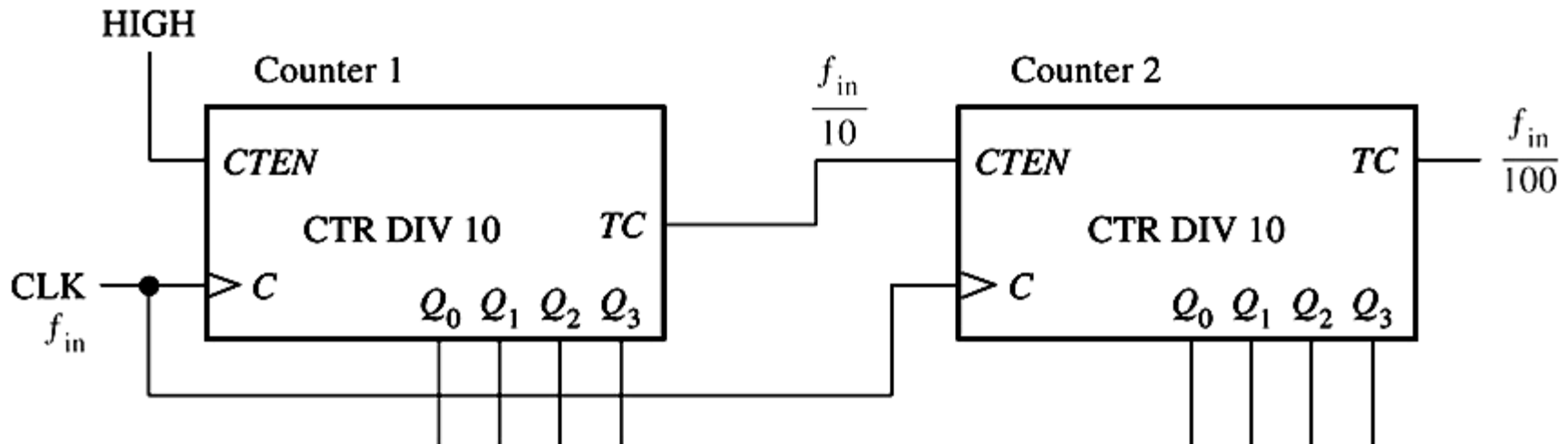
# Cascaded Counters


For IC synchronous counters

- The count enable (CTEN) of counter 1 is HIGH.
- The terminal count (TC) output of counter 1 is connected to CTEN of counter 2.


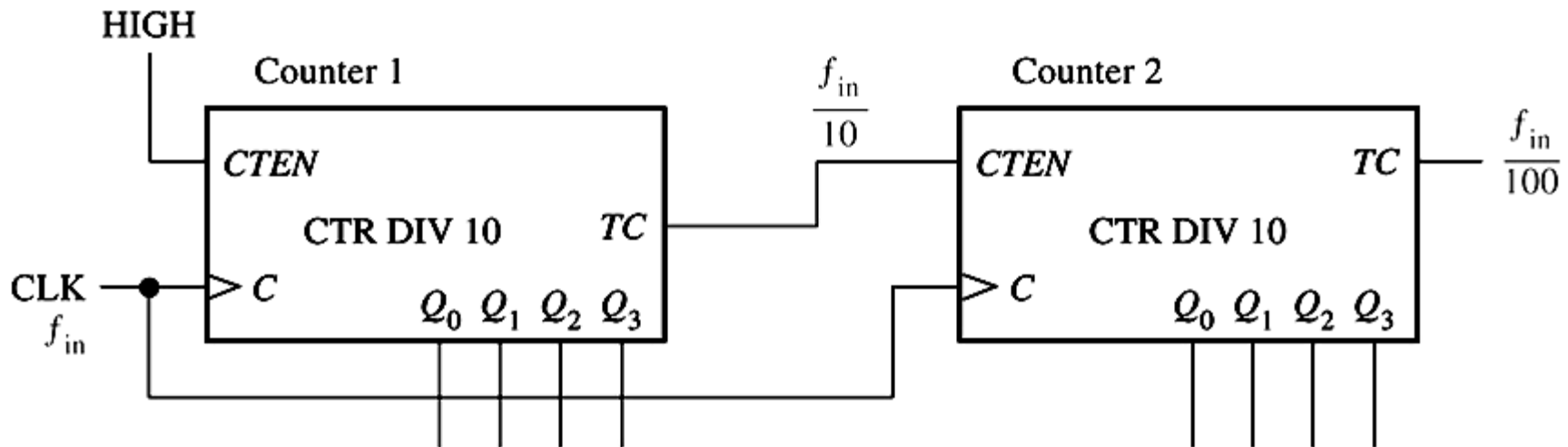
# Cascaded Counters

- At first, TC = LOW, only counter 1 counts.
- When counter 1 reaches its terminal count 9, TC = HIGH, which enables counter 2 to increment at the rising edge of the next CLK.
- Then counter 1 is cleared and TC becomes LOW.



# Cascaded Counters


00      TC1=0

01

.....

09      TC1=1


10      TC1=0

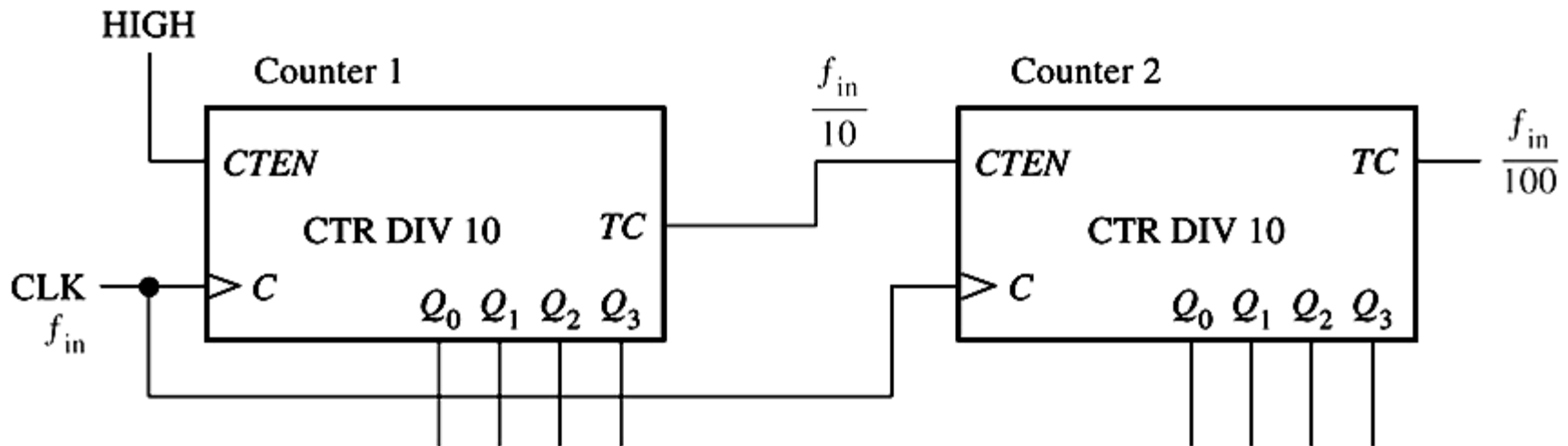
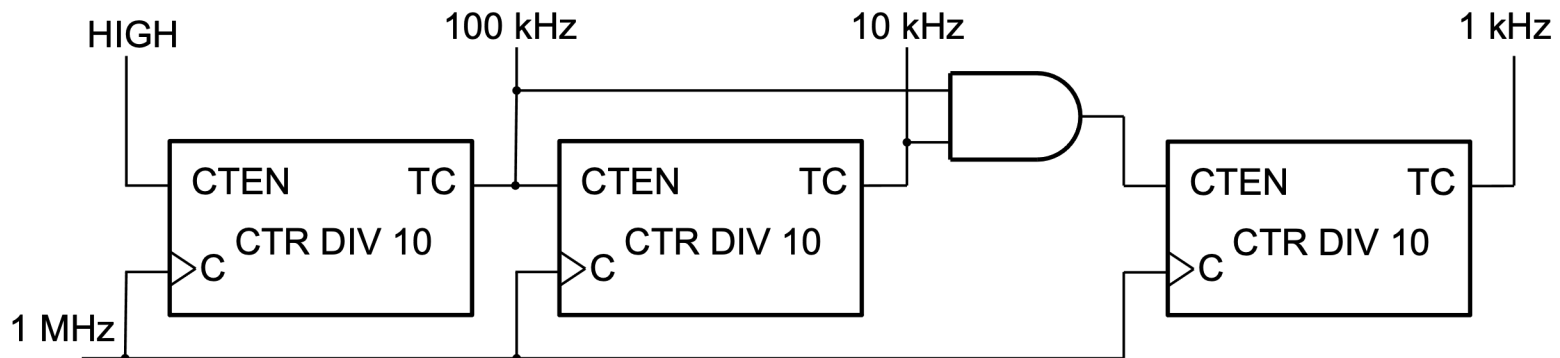
# Cascaded Counters

Cascaded counters can be used as


- A higher-modulus counter
- A frequency divider – to generate a lower-frequency and synchronized clock.




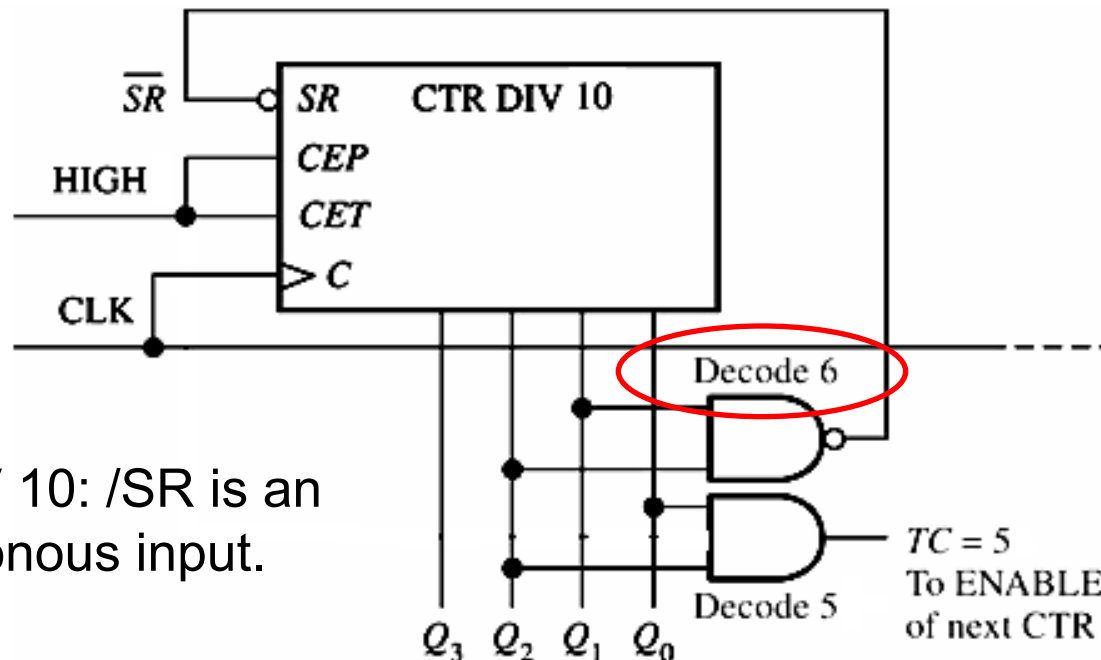
# Cascaded Counters


Truncated sequences can be realized by *decoding the terminal count and then clearing the counters*, e.g. a divide-by-6 counter



CTR DIV 10:  $\overline{SR}$  is an asynchronous input.
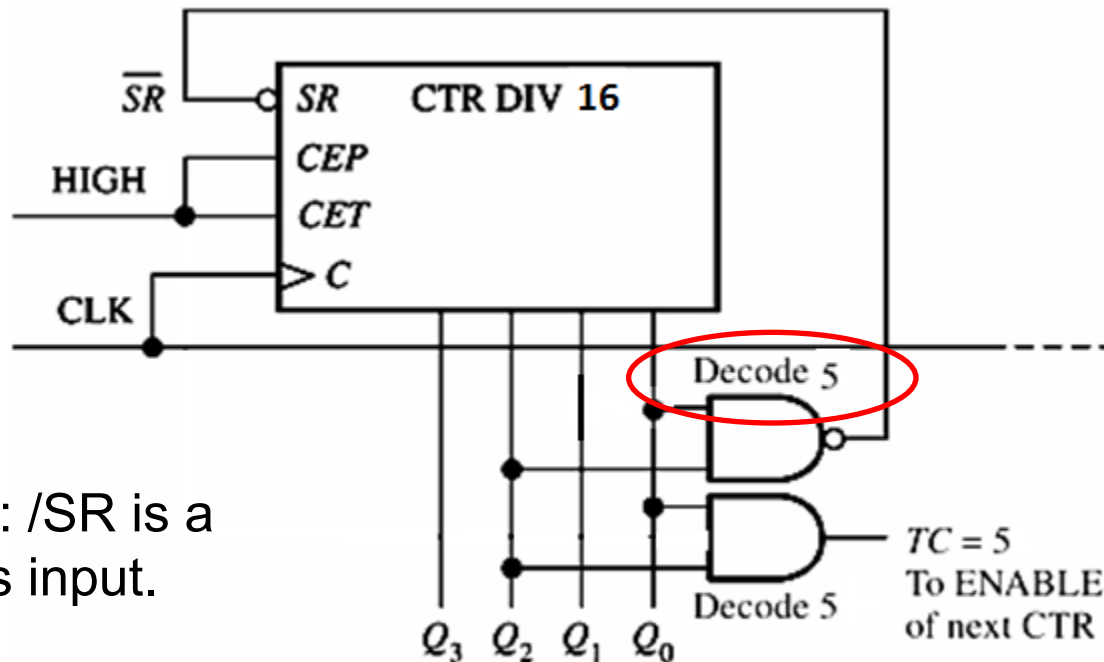
# Cascaded Counters

Truncated sequences can be realized by *decoding the terminal count and then clearing the counters*, e.g. a divide-by-6 counter




CTR DIV 16:  $\overline{SR}$  is a synchronous input.
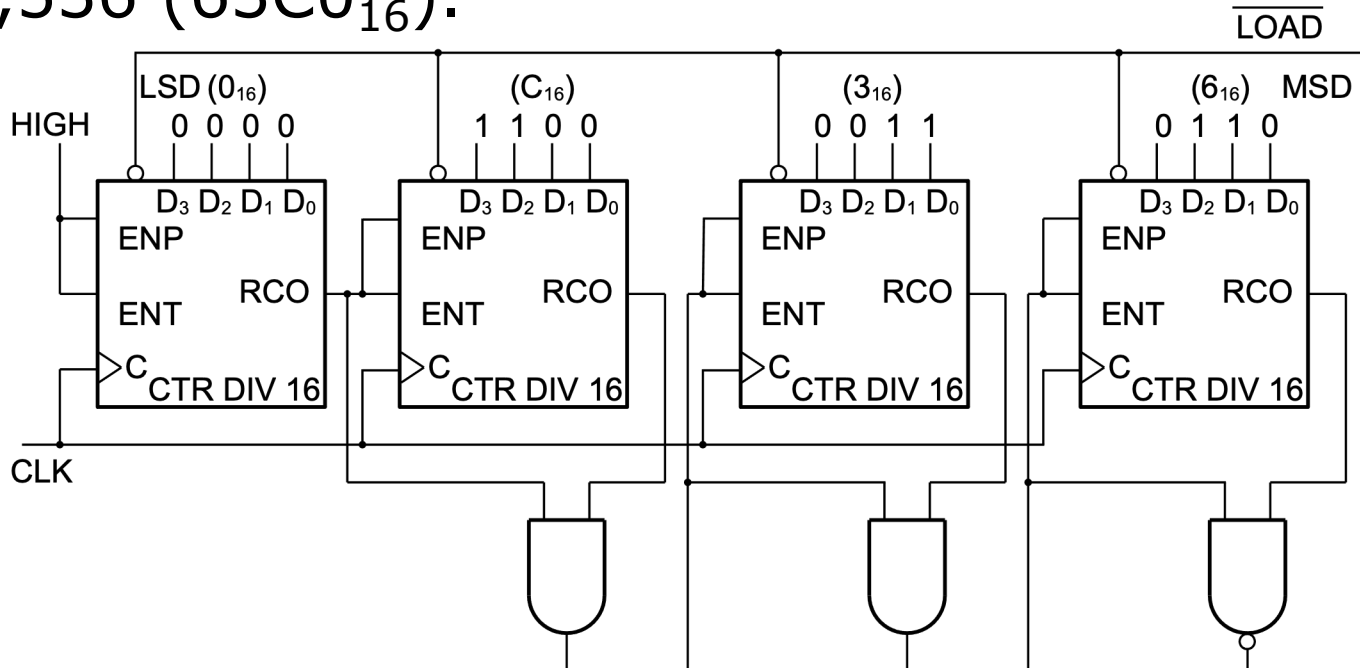
# Cascaded Counters


Truncated sequences can also be realized by *loading an initial count at the terminal count*.

E.g. in a divide-by-40,000 counter, at the last count 65,535, output is HIGH, which loads a count 25,536 ( $63C0_{16}$ ).



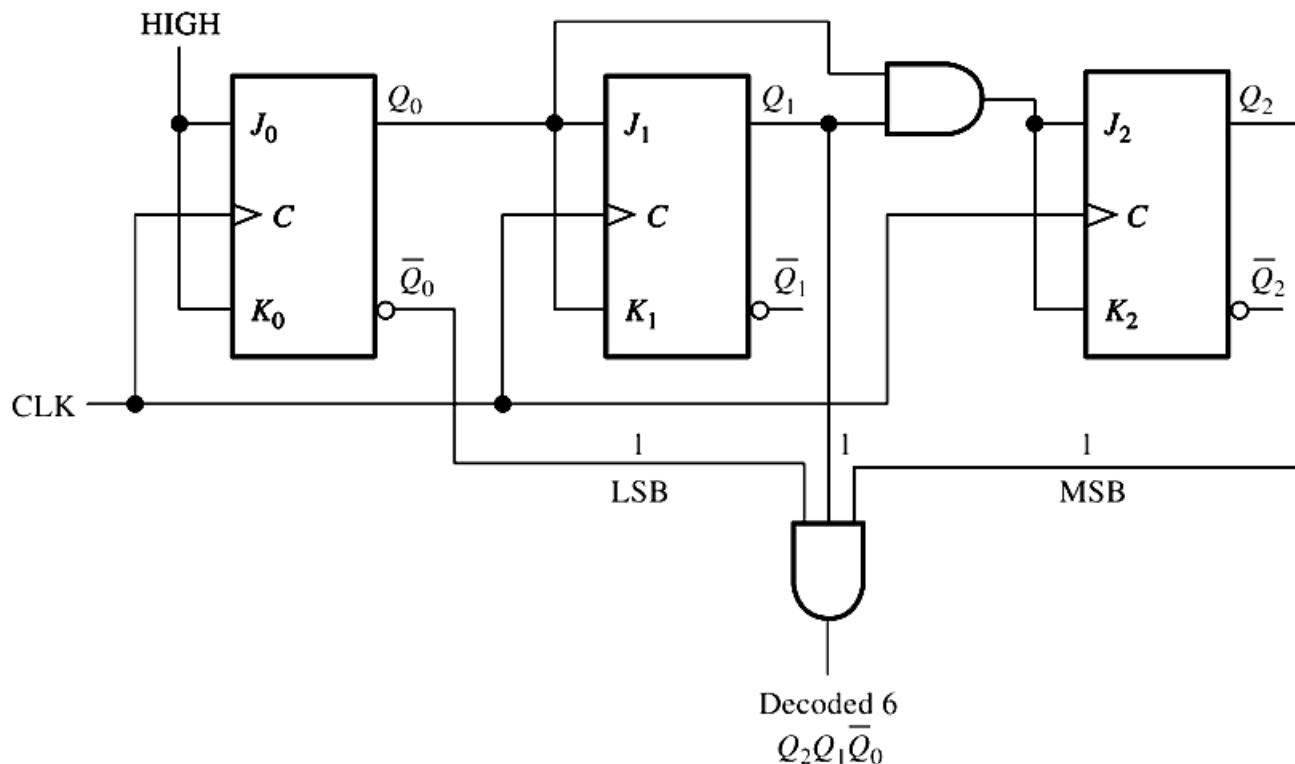
# Counter Decoding

The *decoding of a counter* is to determine when a certain state appears in the sequence, e.g to decode state 6 (110).



 
# Counter Decoding

- In an asynchronous counter, the propagation delays create transitional states.
- They produce glitches on the output of the decoder.




# Counter Decoding

 

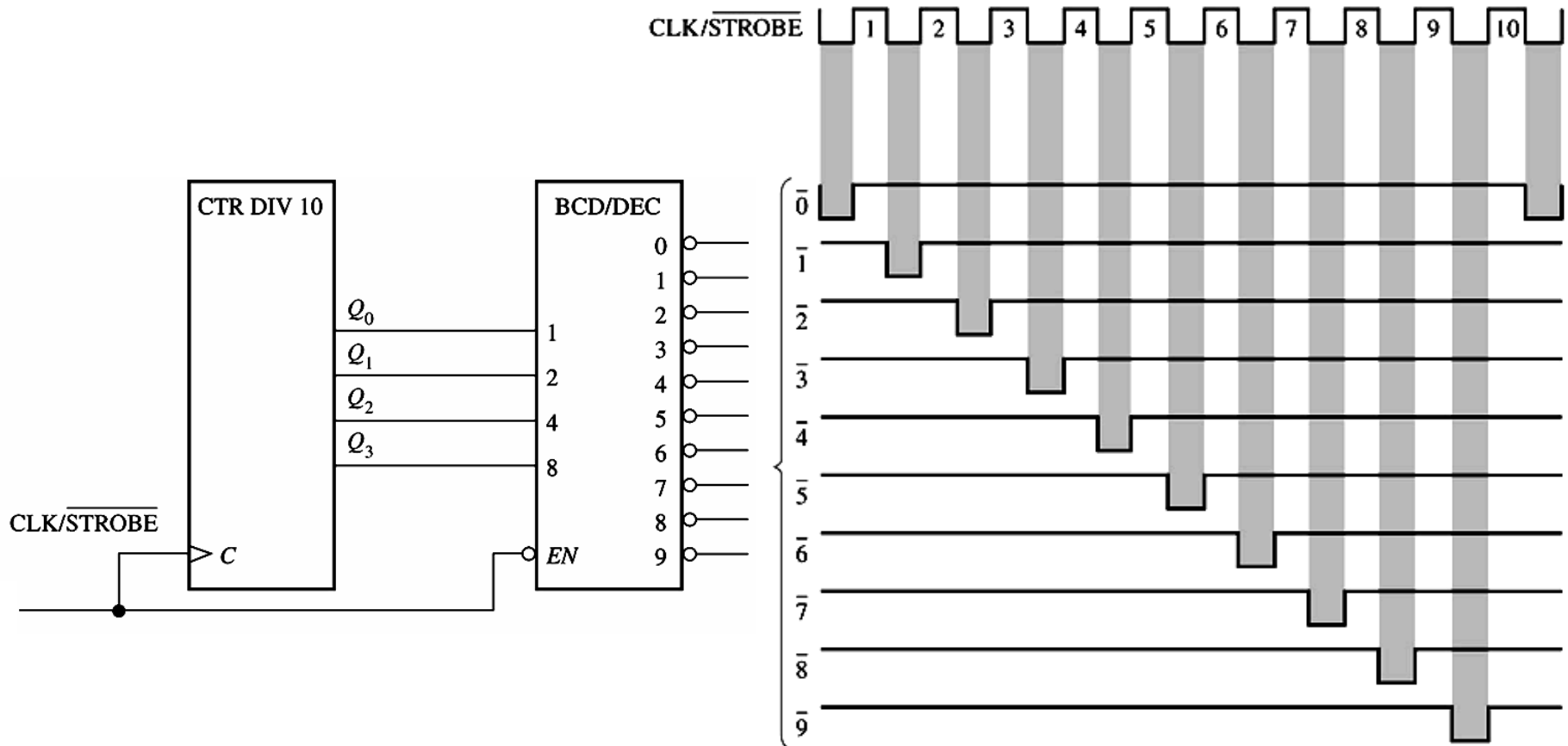
# Counter Decoding

- A remedy is to enable the decoded outputs after the transitional states.




# Counter Applications – Digital Clock

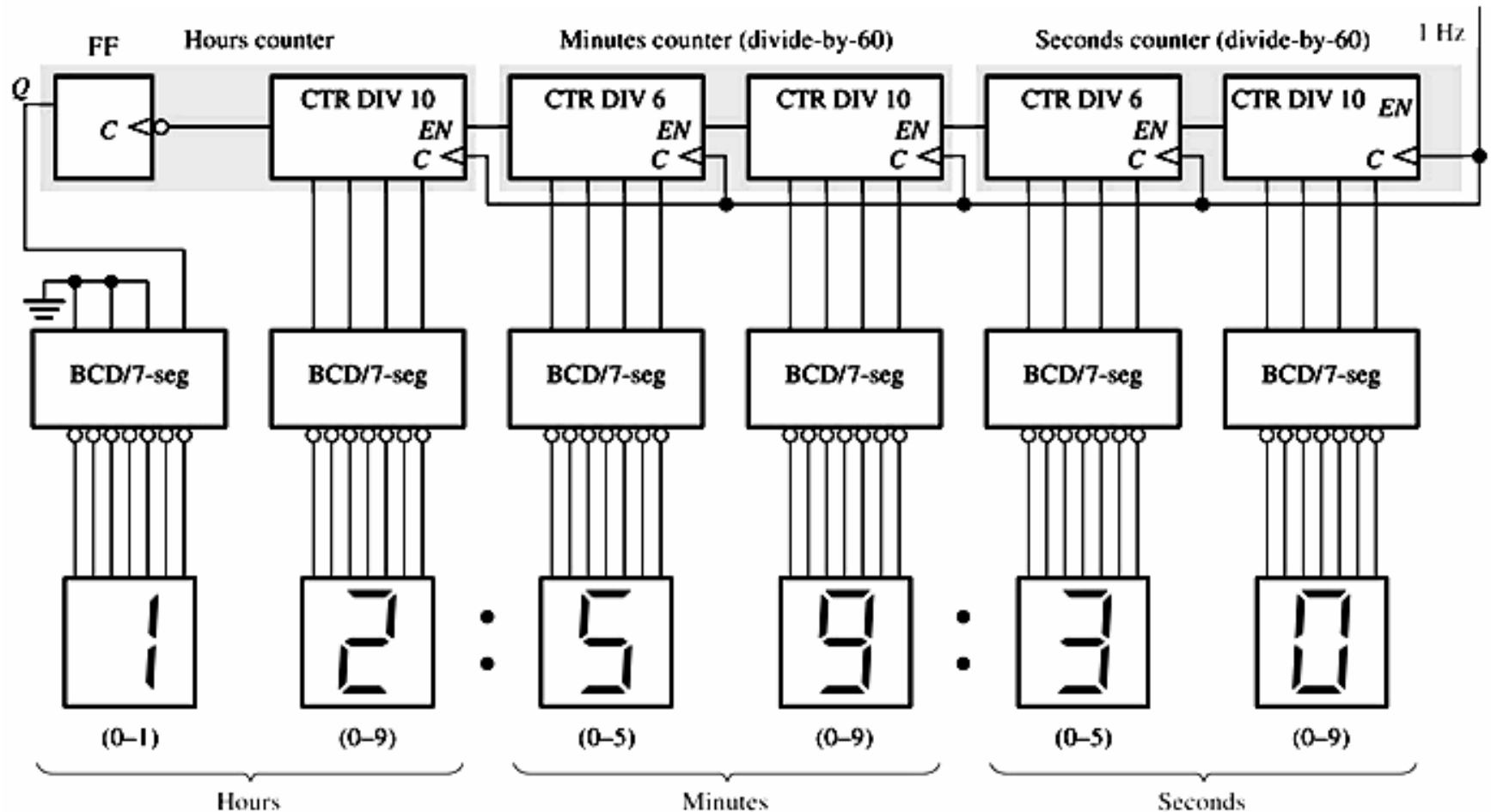



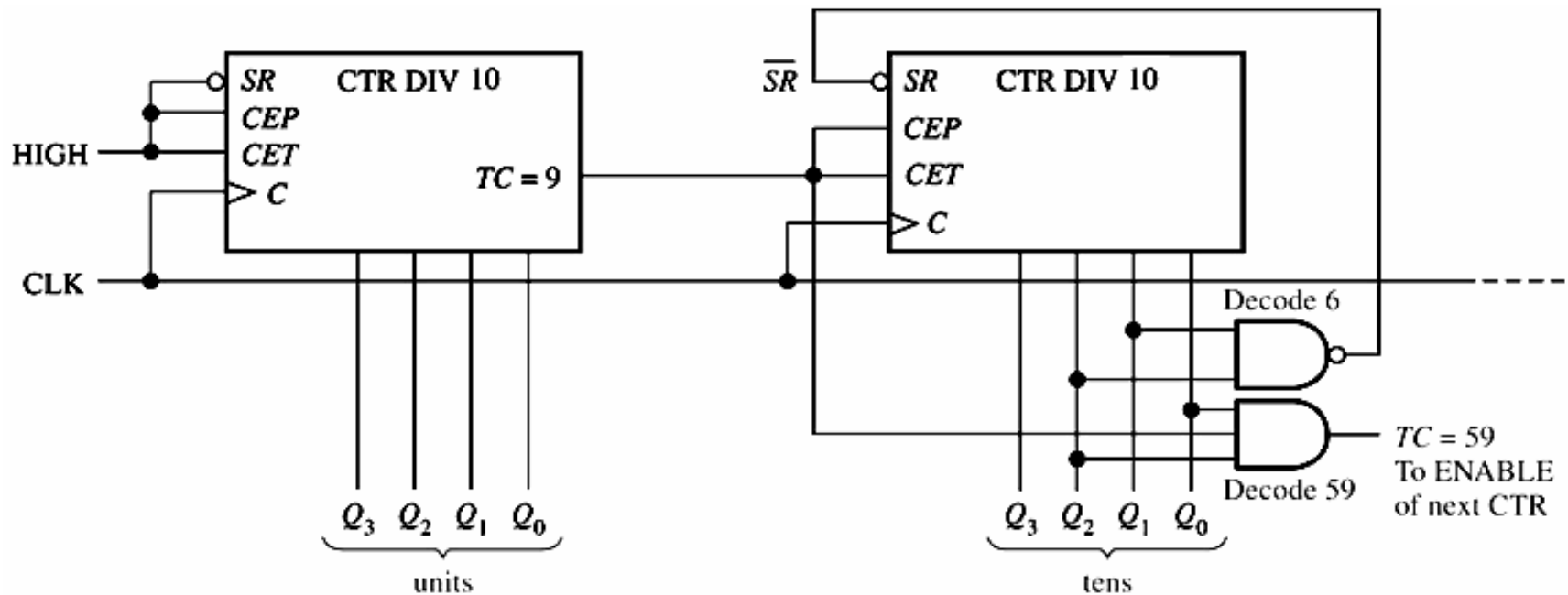
# Counter Applications – Digital Clock

The *seconds* and *minutes* counters: divide-by-60 counters



# Counter Applications – Digital Clock

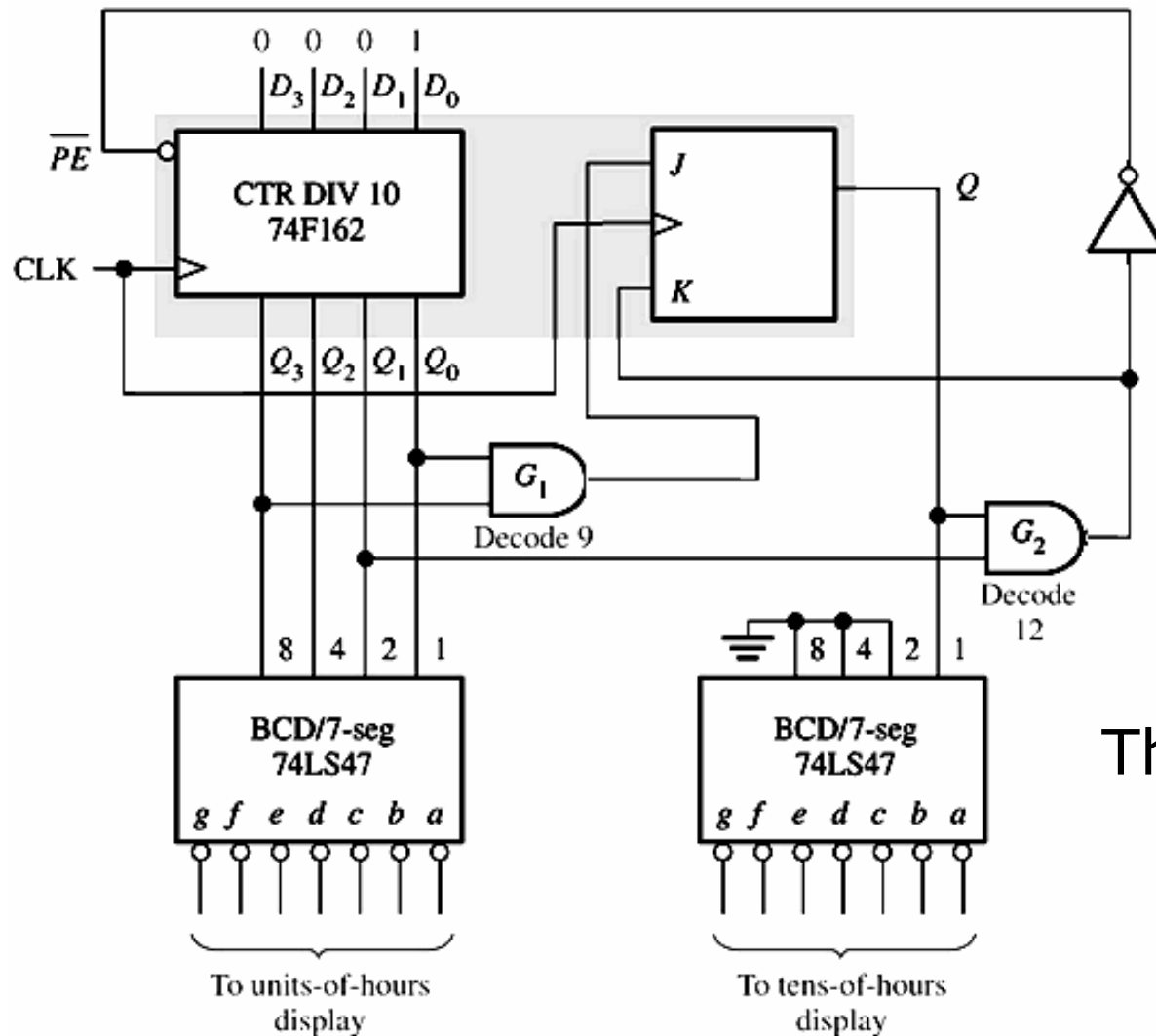

|       |                 |
|-------|-----------------|
| 00    | J=0, K=0        |
| 01    |                 |
| ..... |                 |
| 09    | J=1, K=0        |
| 10    | J=0, K=0        |
| 11    |                 |
| 12    | J=0, K=1, /PE=0 |
| 01    | J=0, K=0        |
| ..... |                 |

# The hours counters