

Plan for the following weeks

W9: Multi-stage Amplifiers for Integrated Circuits

W10: Ideal Operational Amplifier Circuits ← HW3 release

W11: Nonideal Effects in Operational Amplifiers + Feedback on HW2 ← HW3 deadline

W12: Revision1 ← HW3 cut-off

W13: Revision2+Feedback on HW3 (Lab 2)

Office: SC429

Office Hours: Thursday, 2-4 pm

Email: Xiaoyang.Chen02@xjtlu.edu.cn


Multi-Stage Amplifiers for Integrated Circuits

Dr. Xiaoyang Chen

Part 1: Basic Building Blocks in Multi-Stage Circuits

1. Basic Amplifiers (with Load Resistor)

- Common Emitter

 


$$R_i = r_\pi$$

$$R_o = R_C || r_o \approx R_C$$

$$A_v = \frac{v_o}{v_i} = -g_m R_C || R_L || r_o \approx -g_m R_C || R_L$$

Usage: Gain stage

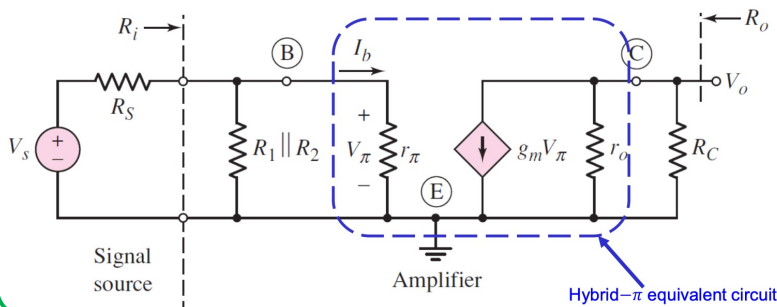


The output voltage can be written as, $V_o = -g_m V_\pi (r_o || R_C)$

The control voltage V_π is found to be, $V_\pi = \frac{R_1 || R_2 || r_\pi}{R_1 || R_2 || r_\pi + R_S} \times V_S$

Thus, the small-signal voltage gain is, $A_v = \frac{V_o}{V_S} = -g_m (r_o || R_C) \frac{R_1 || R_2 || r_\pi}{R_1 || R_2 || r_\pi + R_S}$

W3 P7

 - Common Emitter with Emitter Resistor (Degradation)




$$R_i = r_\pi + (1 + \beta)R_E$$

$$R_o = R_C || r_o \approx R_C$$

$$A_v = -\frac{g_m R_C || R_L}{1 + g_m R_E}$$

Usage: R_E gives increased stability;
Gain stage

W3 P9

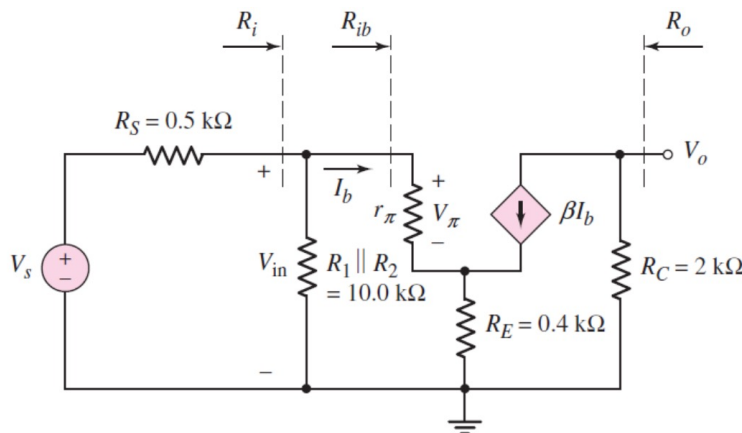

Voltage gain A_v :

The output voltage is, $V_o = -(\beta I_b) R_C$

The input resistance to the amplifier, $R_i = R_1 || R_2 || R_{ib}$


Moreover, $V_{in} = \left(\frac{R_i}{R_i + R_S} \right) V_S$

Therefore, $A_v = \frac{V_o}{V_S} = \frac{-(\beta I_b) R_C}{V_S} = -\beta R_C \left(\frac{V_{in}}{R_{ib}} \right) \left(\frac{1}{V_S} \right) = \frac{-\beta R_C}{r_\pi + (1 + \beta) R_E} \left(\frac{R_i}{R_i + R_S} \right)$

Input resistance R_{ib} : It is the input resistance looking into the base

Use KVL for the loop, $V_{in} = I_b r_\pi + (I_b + \beta I_b) R_E \rightarrow R_{ib} = \frac{V_{in}}{I_b} = r_\pi + (1 + \beta) R_E$

• Common Collector (Emitter Follower)

 


$$R_i = r_\pi + (1 + \beta)R_E \parallel R_L \quad \text{High}$$

$$R_o = \frac{r_\pi + R_S}{1 + \beta} \parallel R_E \quad \text{Low}$$

$$A_v = \frac{g_m R_E \parallel R_L}{1 + g_m R_E \parallel R_L} \quad \text{Low}$$


Usage: Impedance matching; Buffer ★

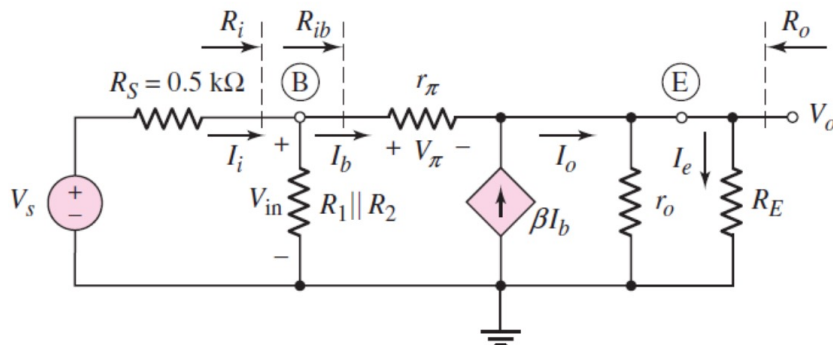

$$R_{ib} = \frac{V_{in}}{I_b} = r_\pi + (1 + \beta)(r_o \parallel R_E)$$


$$A_v = \frac{V_o}{V_s} = \frac{(1 + \beta)(r_o \parallel R_E)}{r_\pi + (1 + \beta)(r_o \parallel R_E)} \left(\frac{R_i}{R_i + R_S} \right)$$

W3 P15-17

 

$$R_o = \frac{V_x}{I_x} = \frac{1}{g_m} \parallel R_E \parallel r_o \parallel r_\pi$$

- Common Base

 


$$R_i = \frac{r_\pi}{1 + \beta} \approx \frac{1}{g_m} = r_e \text{ Low}$$


$$R_o = R_C \text{ High}$$

$$A_v = g_m R_C || R_L \text{ High}$$

Usage: Impedance matching

 

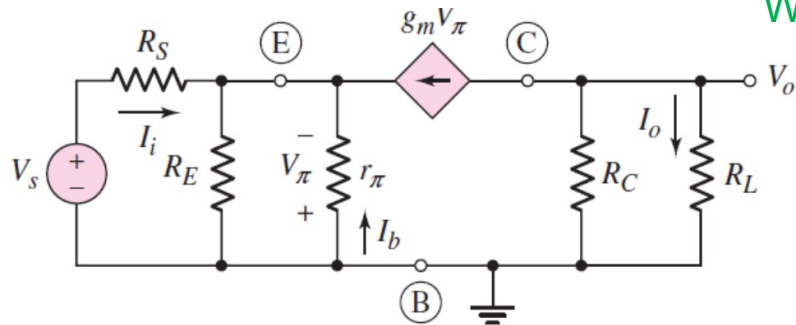
$$R_{ie} = \frac{V_\pi}{I_i} = \frac{r_\pi}{1 + \beta} \equiv r_e$$



$$A_v = \frac{V_o}{V_s} = g_m \left(\frac{R_C || R_L}{R_S} \right) \left[\left(\frac{r_\pi}{1 + \beta} \right) || R_E || R_S \right]$$


W3 P21-23

2. Differential Amplifier

 



- Although the diff-amp contains two transistors, it is considered as **an individual module** in IC design.
- A diff-amp has characteristics very similar to a CE amplifier
- Usage: **Input stage** to virtually all multi-stage amplifiers and integrated circuits

 AC equivalent circuit for differential-mode input signal



- With differential-mode input, we have $v_e = 0$, so the emitters of Q_1 and Q_2 remain at signal ground
- Since v_e is always at ground potential, we can treat each half of the diff-amp as a CE circuit
- The differential-mode characteristics of the diff-amp can be determined by analyzing the half circuit

Properties (Differential Mode)

  

$$R_i = \frac{v_d}{i_b} = 2 \cdot \frac{\frac{v_d}{2}}{i_b} = 2r_{\pi}$$

W4 P23


$$R_o = \frac{v_o}{i_o} = R_C || r_o$$

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_d} = -\frac{1}{2} \cdot \frac{v_o}{-\frac{v_d}{2}} = -\frac{1}{2} \cdot A_v(CE) \approx \frac{g_m R_C}{2}$$

Must Remember!



3. Darlington Pair Configuration

 

- It's a multi-transistor configuration. In ICs, we consider the Darlington Pair as an individual building block
- Usage: Gain stage

Small signal equivalent circuit W3 P32

We see that $V_{\pi1} = I_i r_{\pi1}$, hence

$$g_{m1} V_{\pi1} = g_{m1} r_{\pi1} I_i = \beta_1 I_i$$

Then, $V_{\pi2} = (I_i + \beta_1 I_i) r_{\pi2}$, and we can write:



$$V_i = V_{\pi1} + V_{\pi2} = I_i r_{\pi1} + I_i (1 + \beta_1) r_{\pi2}$$

so that the input resistance is:

$$R_i = \frac{V_i}{I_i} = r_{\pi1} + (1 + \beta_1) r_{\pi2}$$

The output resistance can be easily found by:

$$R_o = \frac{V_o}{I_o} = R_C || r_o \approx R_C$$

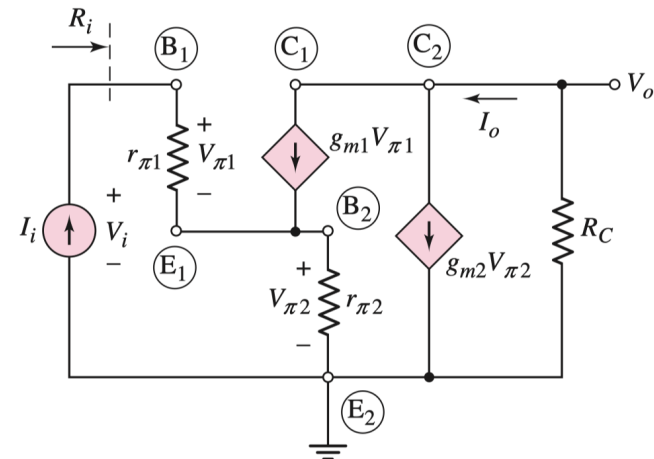 

Small signal equivalent circuit

For a Darlington Pair, the current gain is:

$$A_i = \frac{I_o}{I_i} \approx \beta_1 \beta_2$$



Hence we have $I_o = I_i \cdot \beta_1 \beta_2$

The voltage gain then can be found by:

$$\begin{aligned} A_v &= \frac{V_o}{V_i} = \frac{I_o R_o}{I_i R_i} = \frac{I_i \cdot \beta_1 \beta_2 \cdot R_C}{I_i (r_{\pi 1} + (1 + \beta_1) r_{\pi 2})} \\ &= \frac{\beta_1 \beta_2 \cdot R_C}{r_{\pi 1} + (1 + \beta_1) r_{\pi 2}} \approx \frac{\beta_1 \beta_2 \cdot R_C}{r_{\pi 1} + \beta_1 r_{\pi 2}} \end{aligned}$$

If we have two identical transistors, then
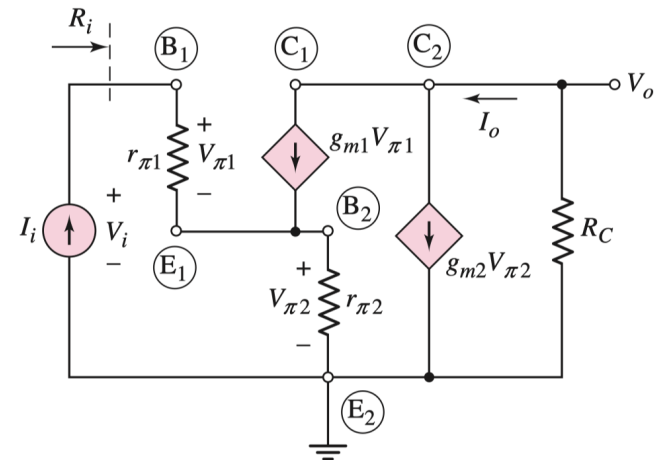 
$$A_v = \frac{\beta_1 \beta_2 \cdot R_C}{r_{\pi 1} + \beta_1 r_{\pi 2}} = \frac{\beta^2 R_C}{r_{\pi 1} + \beta r_{\pi 2}}$$




4. Active Loads

- When a bipolar transistor is used as a linear amplifying device, it must be biased in the forward-active mode.
- In discrete circuits, biasing are basically achieved with resistor biasing.
- In integrated circuits, we would like to **eliminate** as many resistors as possible because they require larger surface area than transistors.
- A bipolar transistor can be biased by using **a constant-current source** I_Q .


Advantages:

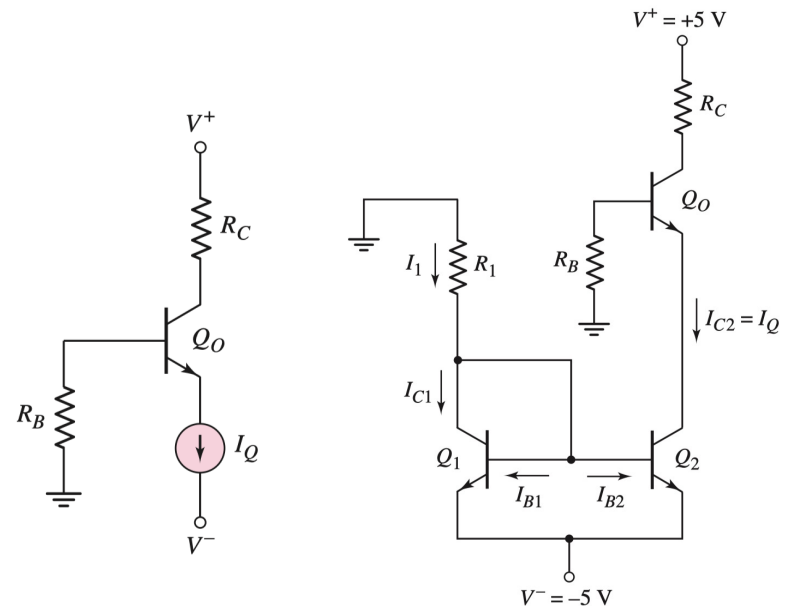- The emitter current is **independent** of β and R_B
- The collector current are essentially **independent** of β
- The value of R_B can be increased, thus increasing the input resistance at the base, **without disturbing the bias stability**



Current mirror circuits

Basic two transistor current source

 

W5 P7, 10


Must Remember!



$$I_{C2} = I_o = \frac{I_{REF}}{1 + \frac{2}{\beta}} \approx I_{REF}$$

$$R_o = r_{o2}$$

Widlar current source

 


W5 P18, 21

$$I_o R_E = V_T \ln\left(\frac{I_{REF}}{I_o}\right)$$

$$R_o \approx r_{o2}(1 + g_{m2} R_E)$$

Differential amplifier with active load

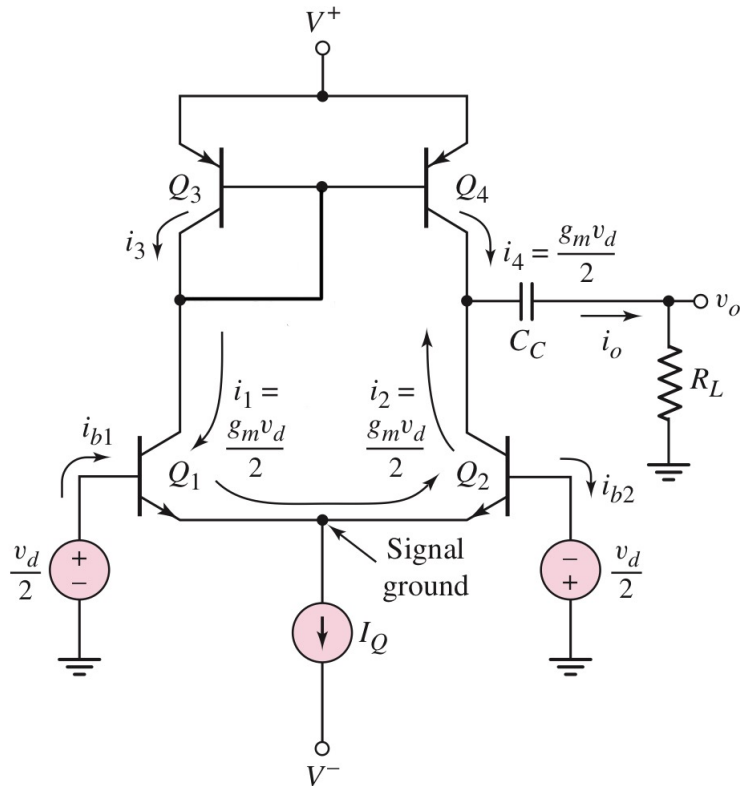


$$A_v = g_m(r_{o2} \parallel r_{o4} \parallel R_L)$$

$$R_o = r_{o2} \parallel r_{o4} \parallel R_L$$


W5 P27

Must Remember!

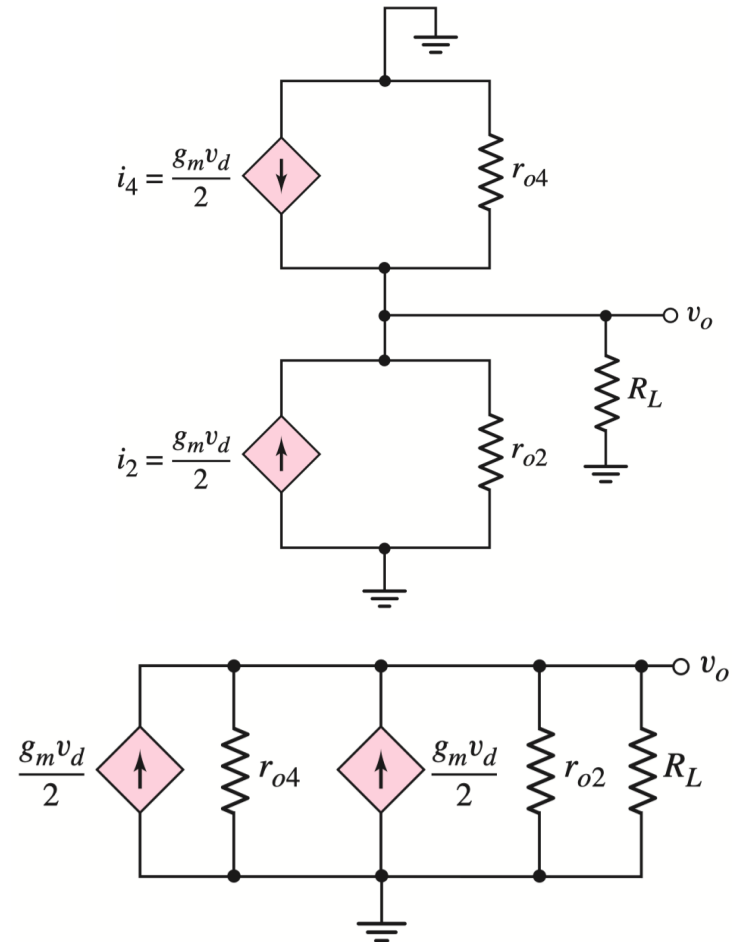

Part 2: Multi-Stage Amplifier Circuits Analysis

Main Principles

 

1. Perform the DC analysis of the circuit to determine the small-signal parameters of the transistors. **In most cases the base currents can be neglected.** This assumption will normally provide sufficient accuracy for a hand analysis.
2. Perform the AC analysis on each stage of the circuit, **taking into account the loading effect of the following stage.**




The properties of the previous stage (e.g., output resistance) can be a function of the input resistance (load) of the next stage, and vice versa.


3. The overall small-signal voltage gain is **the product of the gains of each stage** as long as the loading effect is taken into account.

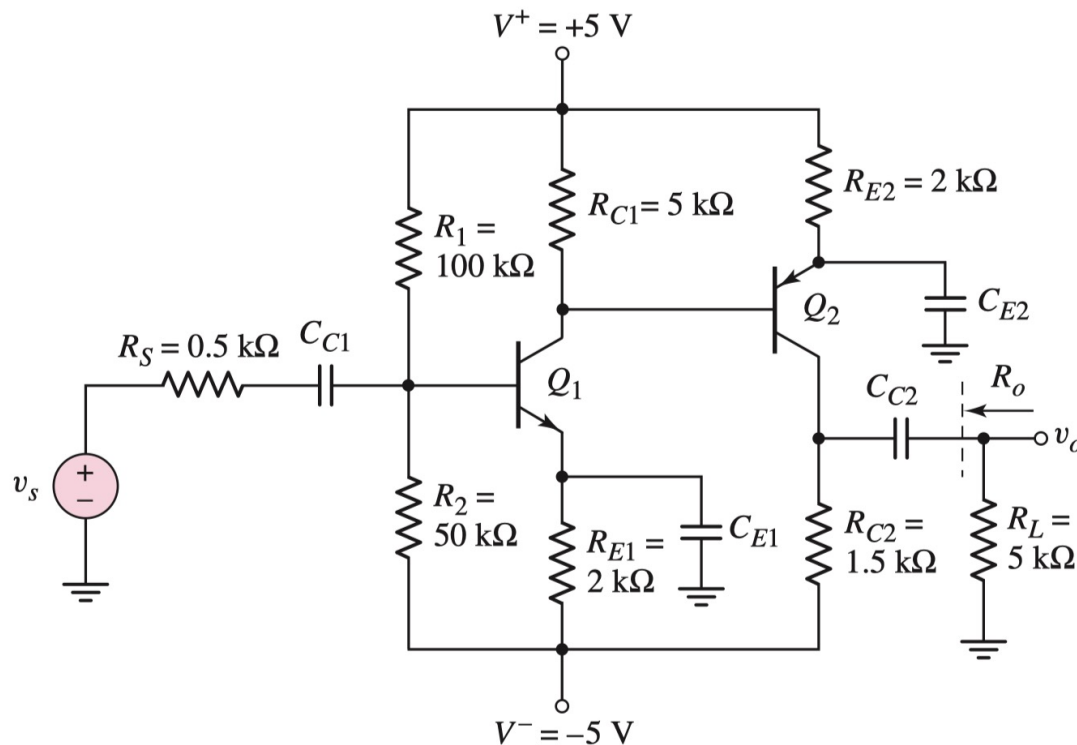Example 1 (Revisit)

Find the mathematical expression of the overall voltage gain for the amplifier shown below ($V_A = \infty$).



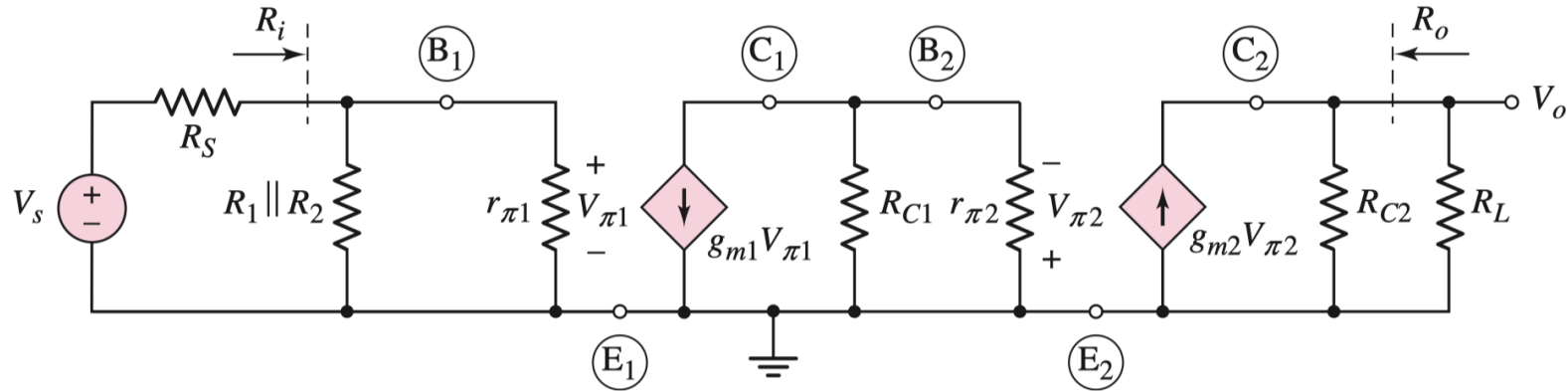Solution (traditional small-signal equivalent circuit approach):



According to the two-stage small-signal equivalent circuit, we have:

$$A_V = \frac{V_o}{V_s} = \frac{V_o}{V_{\pi 2}} \times \frac{V_{\pi 2}}{V_{\pi 1}} \times \frac{V_{\pi 1}}{V_s} \quad (\text{Chain rule})$$

$$\frac{V_{\pi 1}}{V_s} = \frac{R_i}{R_s + R_i}$$

and

$$g_{m2} V_{\pi 2} R_{C2} || R_L = V_o \Rightarrow \frac{V_o}{V_{\pi 2}} = g_{m2} R_{C2} || R_L$$

$$g_{m1} V_{\pi 1} R_{C1} || r_{\pi 2} = V_{\pi 2} \Rightarrow \frac{V_{\pi 2}}{V_{\pi 1}} = g_{m1} R_{C1} || r_{\pi 2}$$

Therefore:

$$A_V = g_{m1} g_{m2} (R_{C1} || r_{\pi 2}) (R_{C2} || R_L) \left(\frac{R_i}{R_i + R_s} \right)$$

where $R_i = R_1 || R_2 || r_{\pi 1}$

Solution (applying loading effect):

This amplifier is composed of two stages

- A CE amplifier at the input with Q1 (stage 1)
- A CE amplifier at the output with Q2 (stage 2)

Stage 1:

According to the formula sheet, we have:

$$A_{v1} = -g_{m1}R_{C1}||R_{L1}$$


In this case, R_{L1} is just the input resistance of stage 2, then we have:

$$R_{L1} = R_{i2} = r_{\pi 2}$$

Hence: $A_{v1} = -g_{m1}R_{C1}||r_{\pi 2}$

Stage 2:

$$A_{v2} = -g_{m2}R_{C2}||R_L$$

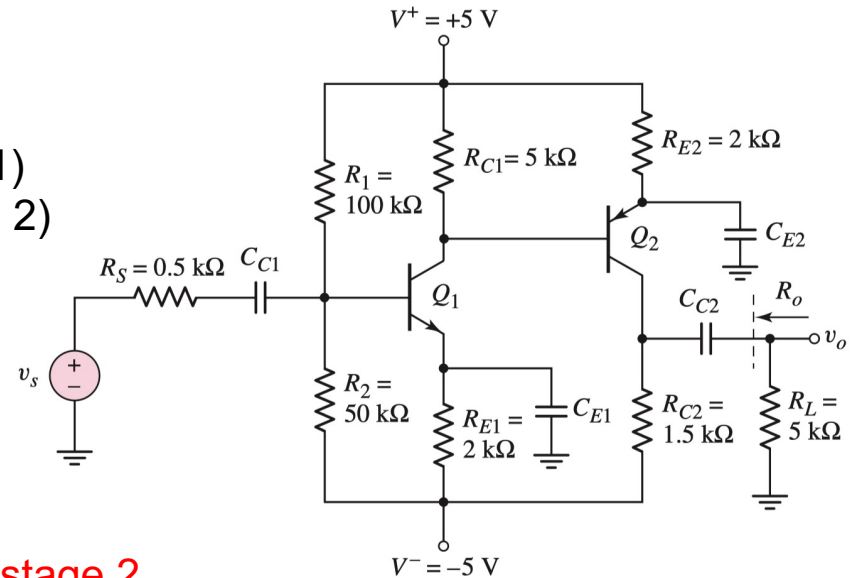

Therefore, the overall voltage gain can be found as:


$$A_V = \frac{v_o}{v_s} = g_{m1}g_{m2}(R_{C1}||r_{\pi 2})(R_{C2}||R_L)\left(\frac{R_i}{R_i + R_S}\right)$$

where $R_i = R_1||R_2||r_{\pi 1}$

Example 2

Consider the circuit shown below. Assume $V_{BE}(on) = 0.7\text{ V}$ for all transistors.

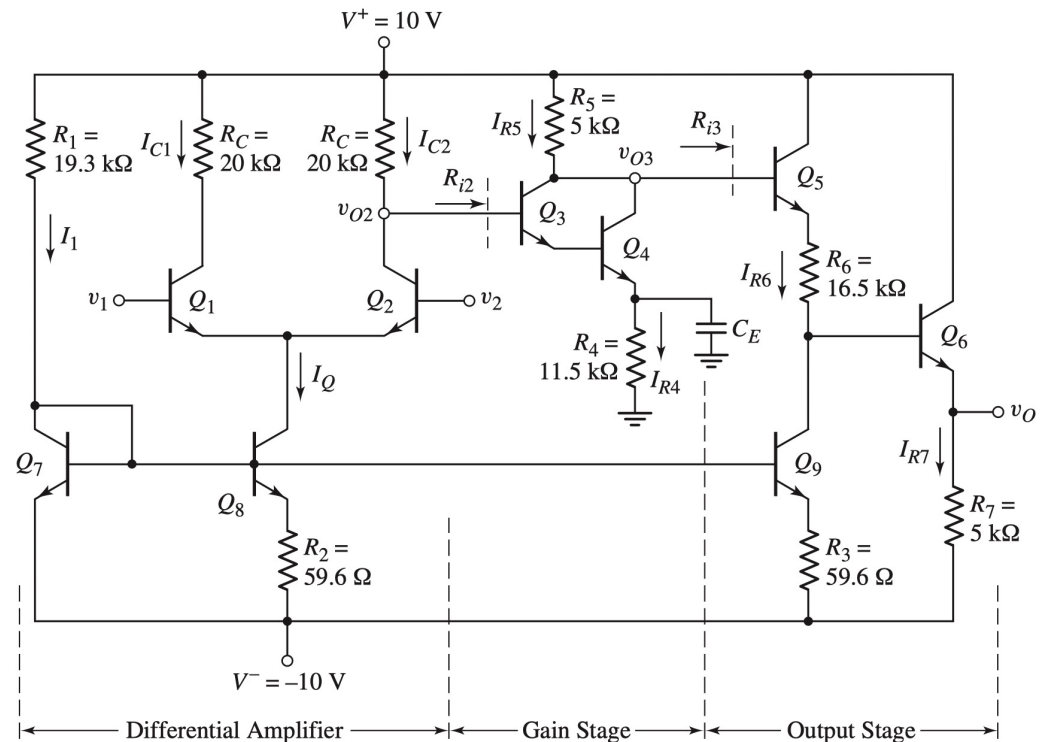- a) Perform DC analysis and find the currents:
 $I_1, I_Q, I_{C1}, I_{C2}, I_{R4}, I_{R5}, I_{R6}$, and I_{R7}
 (Neglect base currents)
- b) Determine the small signal voltage gain of the circuit, assuming $\beta = 100$ and $V_A = \infty$



Solution a):

The circuit is composed of three stages

- A differential amplifier biased by a Widlar current source (stage 1)
- A gain stage with a Darlington pair (stage 2)
- An output circuit with CC (stage 3)

The reference current I_1 is:


$$I_1 = \frac{V^+ - 0.7 - V^-}{R_1} = 1 \text{ mA}$$

The bias current I_Q is found by:

$$I_Q R_2 = V_T \ln \left(\frac{I_1}{I_Q} \right) \rightarrow I_Q = 0.4 \text{ mA}$$

The collector currents are then:
 
$$I_{C1} = I_{C2} = \frac{1}{2} I_Q = 0.2 \text{ mA}$$



The DC voltage at the collector of Q2 is:

$$V_{O2} = V^+ - I_{C2} R_C = 6 \text{ V}$$

The current I_{R4} is then determined to be:

$$I_{R4} = \frac{V_{O2} - 2V_{BE(on)}}{R_4} = 0.4 \text{ mA}$$

Solution a):

Since base currents are negligible, we have: $I_{R5} \approx I_{R4} = 0.4 \text{ mA}$

The DC voltage at the collectors of Q3 and Q4 is then:

$$V_{O3} = V^+ - I_{R5}R_5 = 8 \text{ V}$$

Since $R_2 = R_3$, we have:


$$I_{R6} = I_Q = 0.4 \text{ mA}$$

The DC voltage at the base of Q6 is found to be:

$$V_{B6} = V_{O3} - V_{BE(on)} - I_{R6}R_6 = 0.7 \text{ V}$$

Finally, current I_{R7} is:
 
$$I_{R7} = \frac{V_O - V^-}{R_7} = \frac{0 - (-10)}{5} = 2 \text{ mA}$$



This produces $V_O = 0 \text{ V}$. This is desired as a zero differential-mode voltage is now applied (DC analysis)

Solution b):

Taking the loading resistance into account, the overall small-signal gain is the product of the individual stage gains: $A_V = A_{V1} \cdot A_{V2} \cdot A_{V3}$

Stage 1:

The differential-mode voltage gain is:

$$A_{V1} = \frac{g_m(R_C || R_{L1})}{2}$$

In this case,


$$R_{L1} = R_{i2} = r_{\pi3} + (1 + \beta)r_{\pi4}$$

$$\text{where } r_{\pi4} = \frac{\beta V_T}{I_{R4}} = 6.5 \text{ k}\Omega$$

$$\text{and } r_{\pi3} \approx \frac{\beta^2 V_T}{I_{R4}} = 650 \text{ k}\Omega$$

Therefore, $R_{i2} = 1307 \text{ k}\Omega$
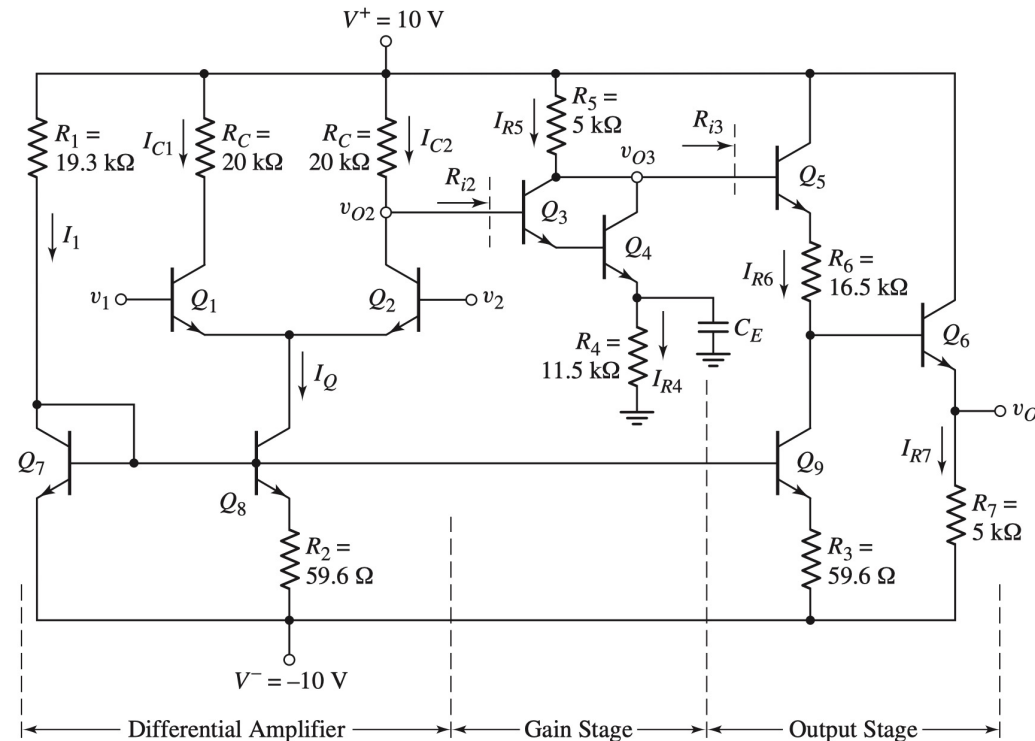
$$\text{The transconductance is } g_m = \frac{I_Q}{2V_T} = 7.7 \text{ mA/V}$$



The gain of stage 1 is therefore:

$$A_{V1} = \left(\frac{7.7}{2}\right) (20 || 1307) = 75.8$$

Solution b):

Stage 2:

For the Darlington pair, the voltage gain is:

$$A_{V2} = \frac{\beta^2 (R_5 || R_{L2})}{r_{\pi3} + \beta r_{\pi4}}$$

In this case,

$$R_{L2} = R_{i3} = r_{\pi5} + (1 + \beta)(R_6 + R_{iQ6})$$

$$\text{and } R_{iQ6} = r_{\pi6} + (1 + \beta)R_7$$


We find that

$$r_{\pi5} = \frac{\beta V_T}{I_{R6}} = 6.5 \text{ k}\Omega \text{ and } r_{\pi6} = \frac{\beta V_T}{I_{R7}} = 1.3 \text{ k}\Omega$$

$$\text{Therefore, } R_{i3} = 52.8 \text{ M}\Omega$$



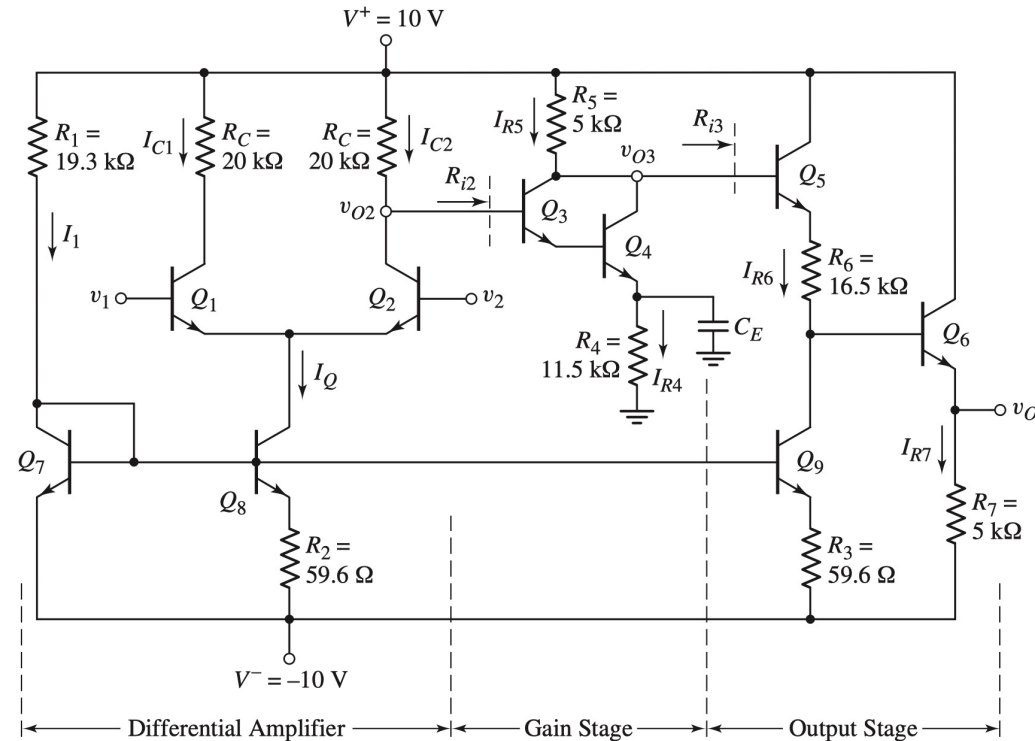The input resistance of CC is very large,
so the loading effect can be ignored



Hence,

$$A_{V2} = 38.5$$

Solution b):

Stage 3:


The output stage is a CC formed by Q5 and Q6, whose gain is:

$$A_{V3} \approx 1$$

CC acts like a good buffer to isolate two stages

The overall small-signal voltage gain is therefore:


$$A_V = A_{V1} \cdot A_{V2} \cdot A_{V3} = 2918$$

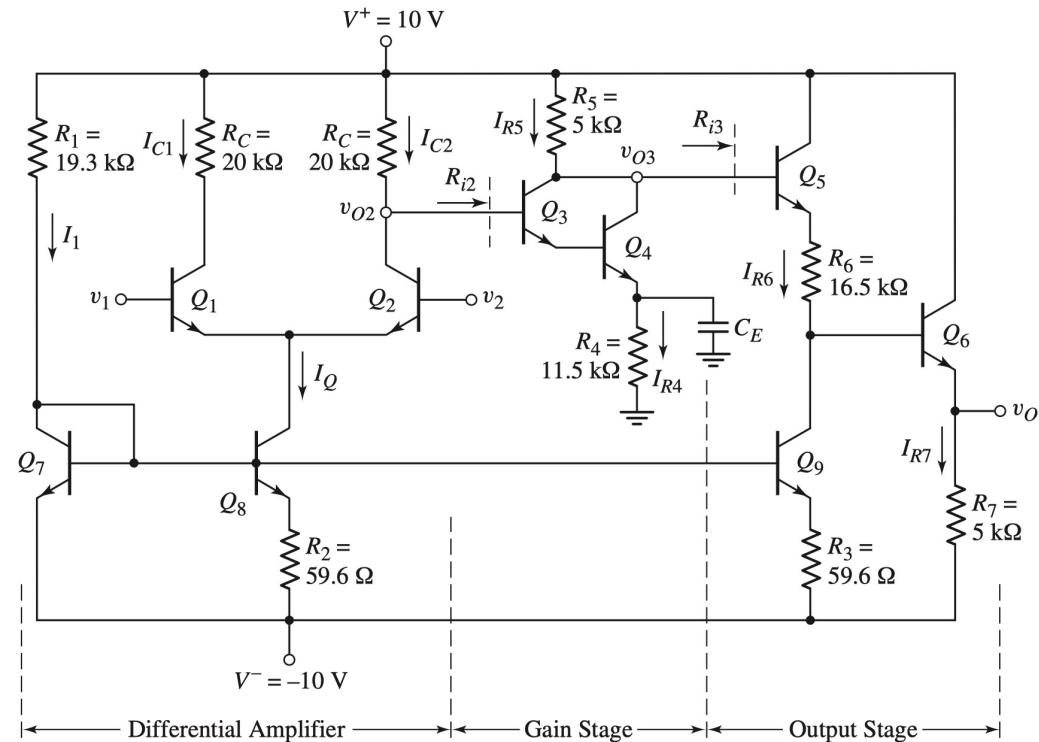

Example 3

Consider the multi-stage voltage amplifier shown below (labelled by 5 stages):

 - a) Briefly describe the function of each of the 5 stages
- b) If $I_2 = 0.1 \text{ mA}$, make reasonable approximations to estimate the total current drawn by the circuit from the $\pm 15 \text{ V}$ DC voltage supply when the amplifier is biased so that the DC value of $V_{out} = 0 \text{ V}$ and the ac input signals are zero ($V_{BE(on)} = 0.6 \text{ V}$).



- c) Assuming $I_2 = 0.1 \text{ mA}$, make reasonable approximations to estimate the overall small signal voltage gain of the circuit. Assume all transistors have a current gain $\beta = 100$ and Early voltage -100 V .

Solution a):


Stage 1 is the bias current section, which forms a Widlar current mirror with Q2 and a basic current mirror with Q9

Stage 2 is a differential amplifier with active load. It forms the input of the circuit and provides the first voltage gain

Stage 3 is an emitter-follower (CC) circuit forming an impedance matching buffer between stages 2 and 4. It also reduces the loading effect.

Stage 4 is a CE amplifier with current mirror as active load that significantly contributes to the overall voltage gain.

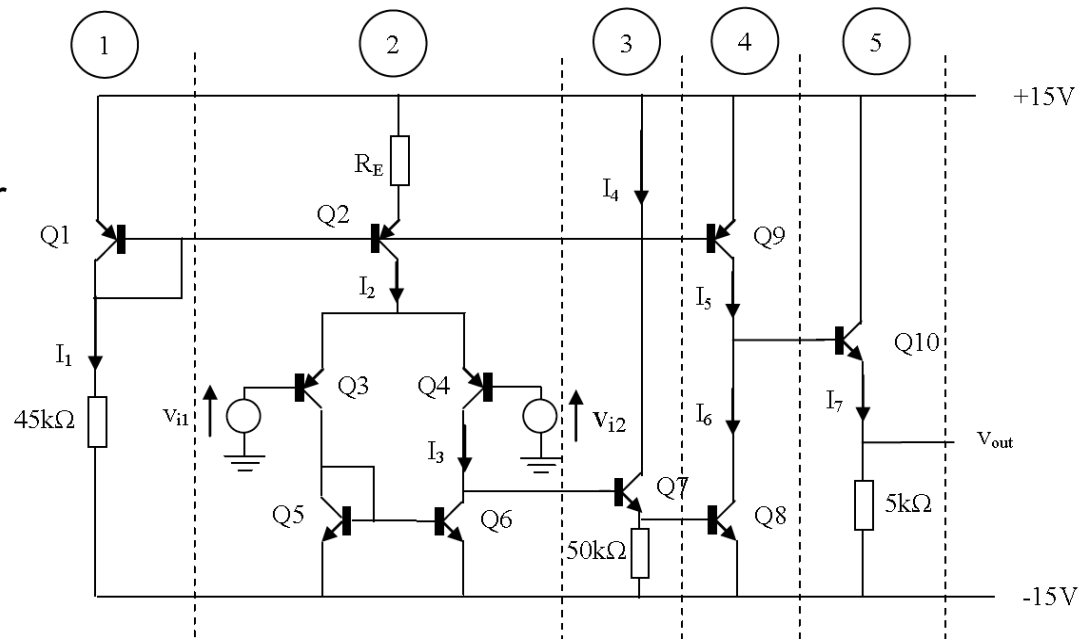Stage 5 is a CC circuit forming the output stage and reducing loading effect.



Solution b):

At stage 1, we have:

$$I_1 = \frac{V^+ - 0.6 - V^-}{45} = 0.653 \text{ mA}$$

From the current mirror, we have:

$$I_5 = I_1 = 0.653 \text{ mA}$$


$$I_4 = \frac{0.6}{50} = 0.012 \text{ mA}$$

Since we have $V_{out} = 0 \text{ V}$, we have:

$$I_7 = \frac{0 - (-15)}{5} = 3 \text{ mA}$$

Therefore, the total current drawn from the source is:
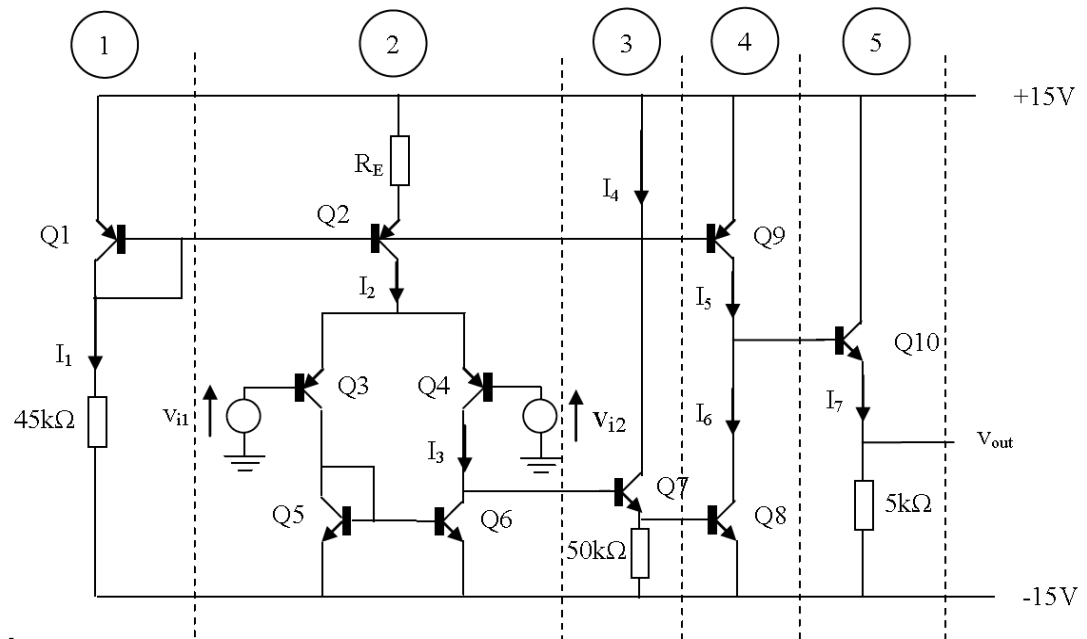
$$I_{total} = I_1 + I_2 + I_4 + I_5 + I_7 = 4.42 \text{ mA}$$



Solution c):

Stage 1:

Stage 1 is a bias reference, and will not contribute to the overall voltage gain

Stage 2:

For a differential amplifier with active loads, we have:

$$A_{v2} = g_{m4}(r_{o4} || r_{o6} || R_{L2})$$


where

$$R_{L2} = R_{i3} = r_{\pi7} + (1 + \beta)50 || R_{L3}$$

$$\text{and } R_{L3} = R_{i4} = r_{\pi8}$$

Then we have:
 
$$g_{m4} = \frac{I_{CQ4}}{V_T} = \frac{I_2}{2V_T} = 2 \text{ mA/V}$$



$$r_{o4} = r_{o6} = \frac{100}{0.5I_2} = 2000 \text{ k}\Omega$$

$$r_{\pi7} = \frac{\beta}{g_{m7}} = \frac{\beta}{40I_4} = 208 \text{ k}\Omega$$

At the base of Q10, we have:

$$I_6 = I_5 - \frac{I_7}{\beta} = 0.623 \text{ mA}$$

Therefore:

$$R_{L3} = r_{\pi8} = \frac{\beta}{40I_6} \approx 4 \text{ k}\Omega$$

$$R_{L2} \approx 582 \text{ k}\Omega$$

and

$$\underline{A_{v2} \approx 736}$$

Solution c):

Stage 3:

Stage 3 is a CC circuit with $A_{V3} = 1$

Stage 4:

For a CE amplifier, we have:

$$A_{V4} = -g_{m8}(R_{L4} || r_{o8} || r_{o9})$$

(Here $R_C = r_{o9}$)

where $R_{L4} = R_{i5}$


and $R_{i5} = r_{\pi10} + (1 + \beta) \cdot 5$ with $r_{\pi10} = \frac{\beta}{40I_7} = 0.83 \text{ k}\Omega$

Hence $R_{i5} \approx 505 \text{ k}\Omega$

We have $r_{o8} \approx r_{o9} = \frac{100}{I_5} = 153 \text{ k}\Omega$

and $g_{m8} = 40I_6 = 25 \text{ mA/V}$

Then $A_{v4} = -25 \times 153 || 153 || 505 \approx -1660$

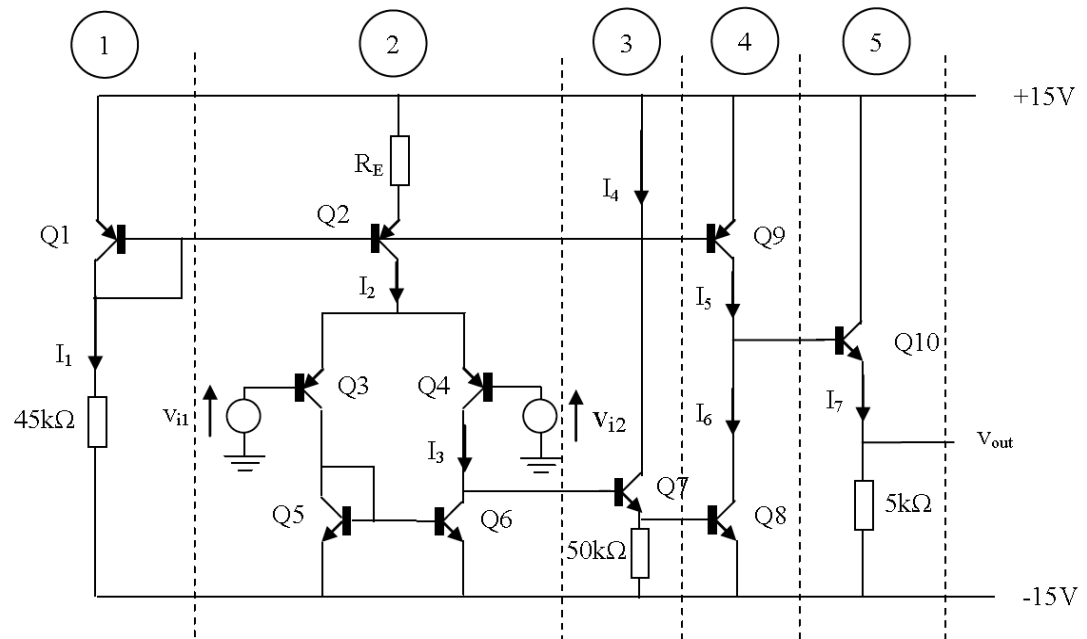

Stage 5:

Stage 5 is a CC circuit with $A_{V5} = 1$

Finally we have:

$$|A_v| = |A_{v2} \times A_{v3} \times A_{v4} \times A_{v5}| = 1.2 \times 10^6$$

See you in the next lecture...

The End