

1. Power Transistors

2. DC–DC Converters

Dr. Suneel Kommuri

Email: Suneel.Kommuri@xjtlu.edu.cn

Dept. Electrical & Electronic Engineering

1.0 Outline – Power Transistors

- Power Electronic Devices
- Power Transistors
 - Power BJT
 - Power MOSFET
 - IGBT
- Comparison

Power semiconductor devices

- Power Diode – uncontrollable
- Thyristor (THYRatron tube & transISTOR)
 - SCR (Silicon Controlled Rectifier) – ON controllable
 - TRIAC (Triode ac switch) – ON controllable
 - GTO (Gate turn-off thyristor) – **ON/OFF controllable**
- Power Transistors – **ON/OFF controllable**
 - Power BJT
 - Power MOSFET
 - IGBT

Important feature

Controllability

Static induction
transistor (SIT)

No*
required



1.0 Power Transistors

- **Feature:**


- Controlled characteristics: The transistor is turned ON when a current signal is given to base, or control terminal. It will remain in the ON-state as long as control signal is present – if the control signal is removed, the transistor is turned OFF.

- **Applications**


- In use from 1980s
- GTR and GTO are seldom in use today
- IGBT and power MOSFET are the two major power semiconductor devices nowadays

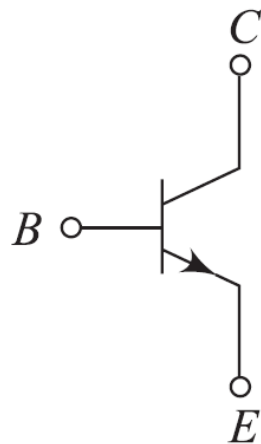1.1 Power BJT (Bipolar Junction Transistor)


- Three terminals – collector (C), emitter (E), and base (B).
- Emitter with an *arrowhead* indicates the *direction* of emitter current.
- Three layer, two junction *NPN* or *PNP* semiconductor device.
- NPN type transistors are easy to manufacture, cheaper and very wide in high-voltage and high-current applications.
- *Bipolar* – the current flow in the device is due to the movement of both holes and electrons.



NPN type


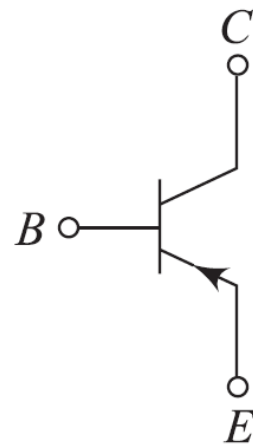


PNP type

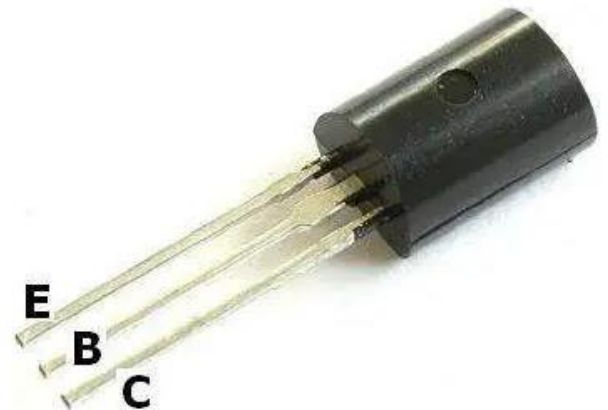


BJT I-V Characteristics

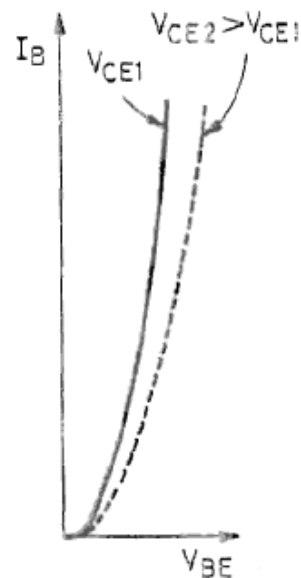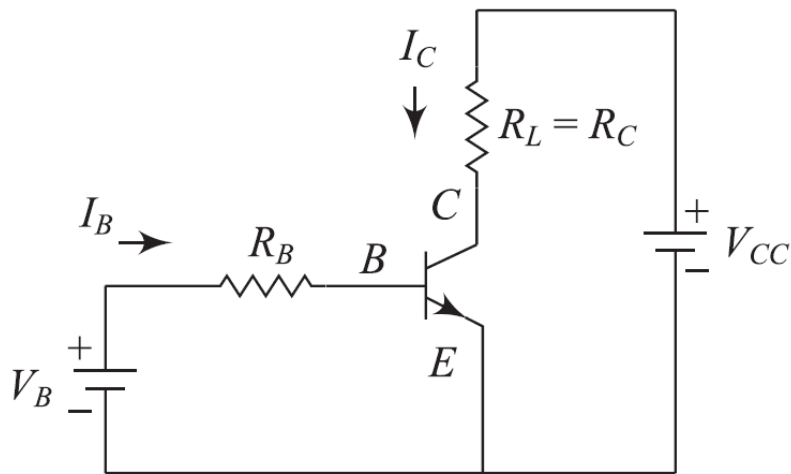- Common-emitter (CE) is more common in switching applications.
- Output characteristics: Collector current (I_C) versus collector-emitter voltage (V_{CE}).
- For $I_B = 0$, as V_{CE} is increased, a small leakage current exists.
- As the base current is increased from $I_B = 0$ to I_{B1}, I_{B2} etc., collector current also rises as shown below:



Input characteristics

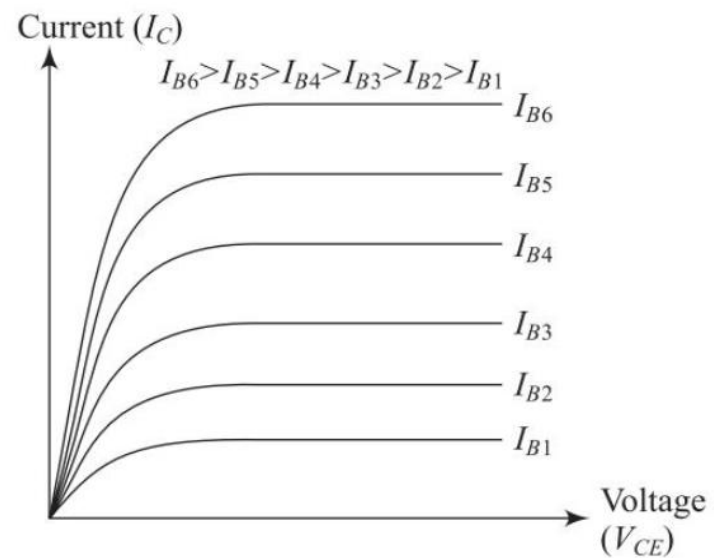


Output characteristics




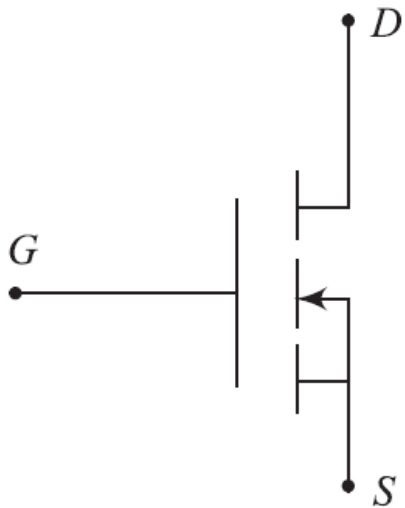1.2 Power MOSFET


- Three-terminals – drain (D), source (S), and gate (G).
- Arrow indicates the direction of electron flow.
- BJT is current-controlled device whereas MOSFET is a voltage-controlled device.
- MOSFETs are used in low-power high-frequency converters.



n –channel MOSFET

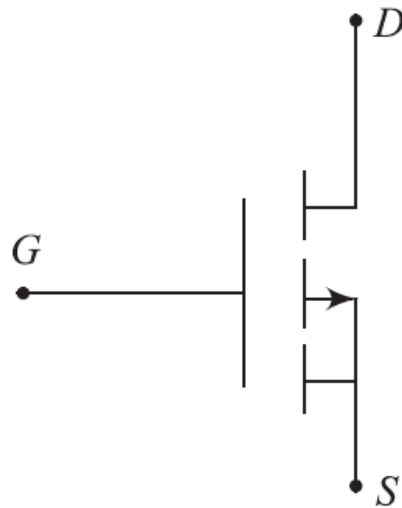


p –channel MOSFET

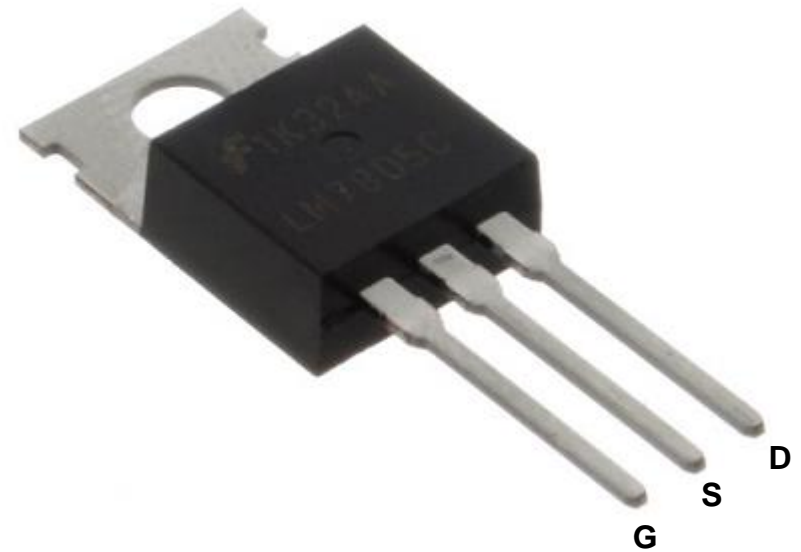


MOSFET I-V Characteristics


- Input signal V_{GS} is applied across gate to source & output signal V_{DS} is obtained from drain. Source terminal (S) is common between input & output of a MOSFET.
- Transfer characteristics:** I_D is a function of V_{GS} . When $V_{GS} < V_{GS(th)}$, the device is in OFF-state. In general, the value of $V_{GS(th)}$ is about 2 to 3 V.
- Output characteristics:** I_D is a function of V_{DS} with V_{GS} as a parameter. For given V_{GS} , if V_{DS} is increased, output characteristic is relatively flat indicating that drain current is nearly constant. It consists of cut-off, active and ohmic regions.

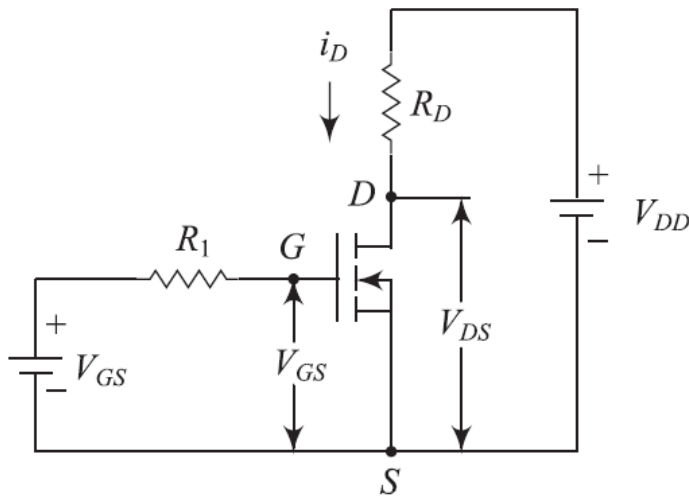

n – channel MOSFET

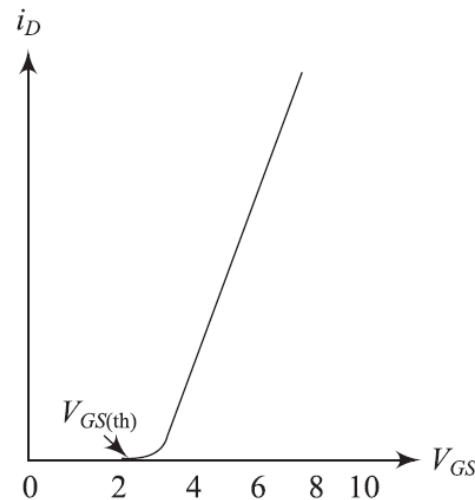



**Transfer
characteristics**

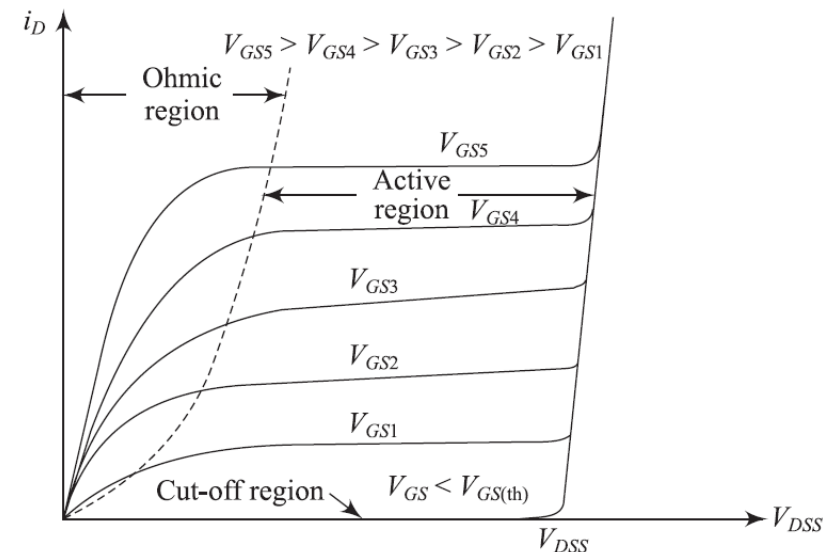

Output characteristics


Switching Characteristics

- When a pulse input voltage is applied to the gate of MOSFET, the device will turn-ON if $V_{GS} > V_{GS(th)}$.
- Switching characteristics' are influenced to large extent by internal capacitance.
- At $t = t_o$, input voltage $V_G = 0$ & $V_{GS} < V_{GS(th)} \rightarrow I_D = 0$, device in OFF state.
- At $t = t_1$, voltage starts to increase from 0 to $V_1 \rightarrow C_{gs}$ starts to charge. During t_d , C_{gs} is charged to $V_{GS(th)}$. During t_r , V_{GS} increases from $V_{GS(th)}$ to full gate voltage V_{GSP} to operate the transistor in linear region, also increases to I_D .

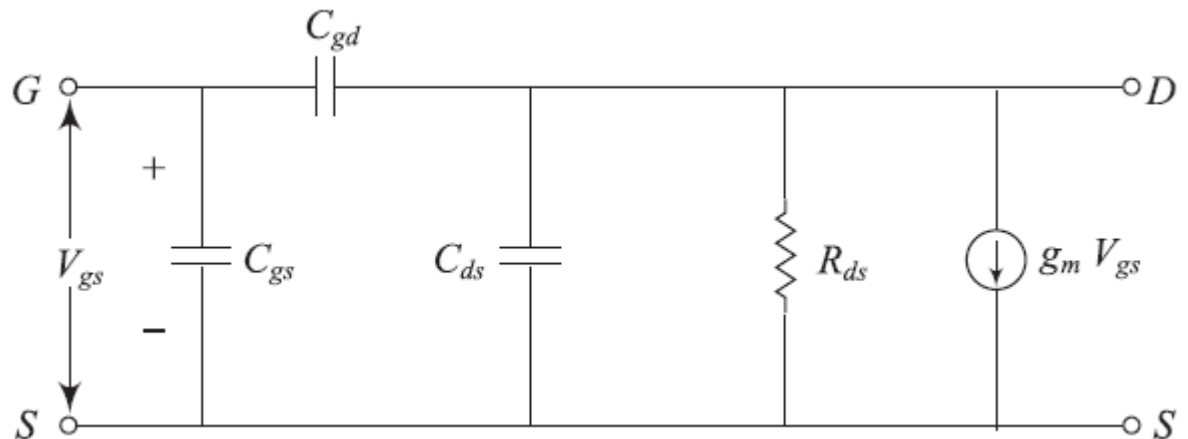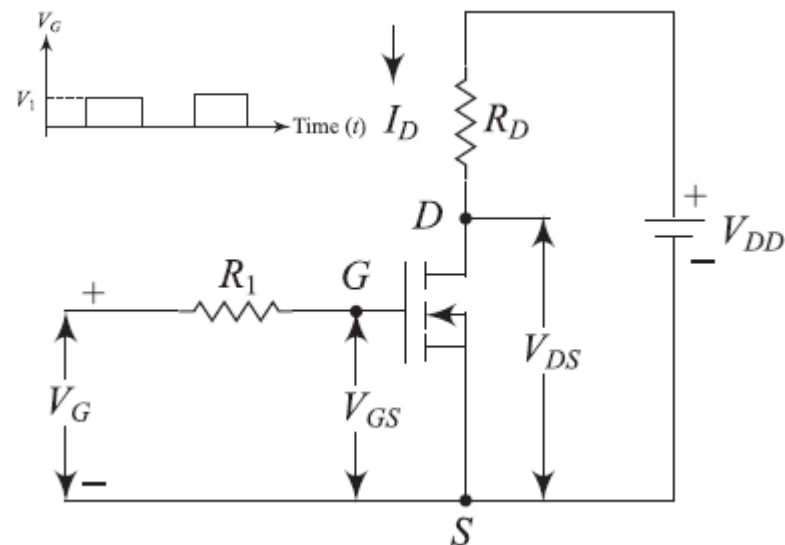

Switching model of MOSFET

Switching Characteristics

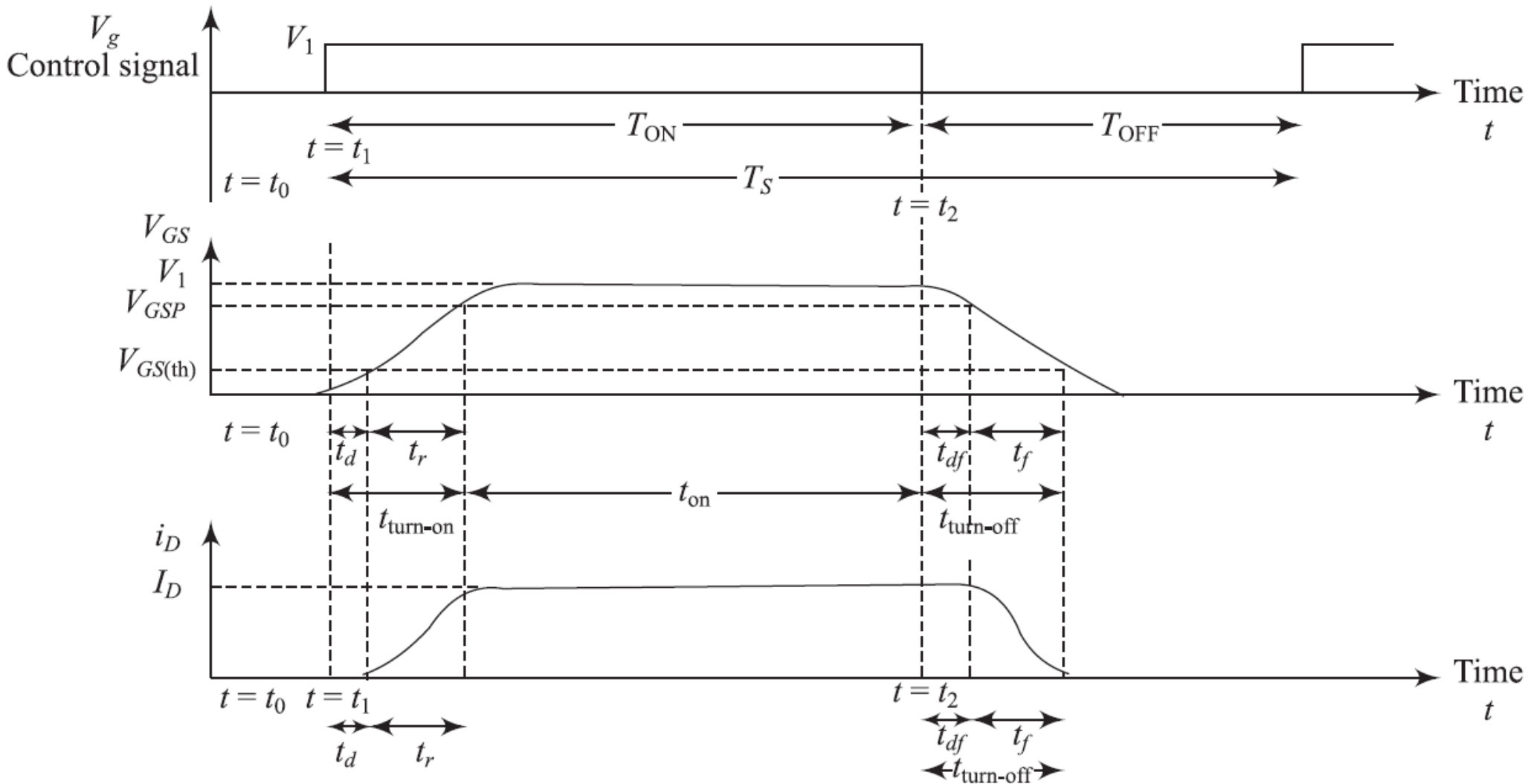


Applications and Features different from BJT

- High-frequency switching applications, varying from few W to kW.
- Very popular in switch mode power supplies and inverters.
- Unipolar device whereas BJT is bipolar device.
- High input impedance whereas BJT has low impedance.
- Voltage controlled device whereas BJT is current controlled device.
- Conduction loss of MOSFET is larger than that of BJT due to a larger voltage drop for high-voltage applications.
- Lower switching losses whereas BJT has higher switching losses.

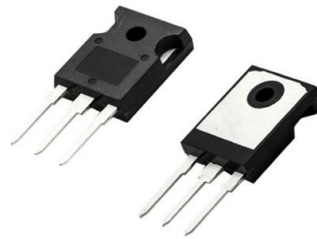
1.3 IGBT (Insulated Gate Bipolar Transistor)

- Combination of power transistors BJT and MOSFET.
- High input impedance like MOSFET and low on-state power loss as in BJT.
- Voltage controlled device.
- IGBT is very popular amongst power electronic engineers.
- MOSIGT ↔ COMFET ↔ GEMFET




Features

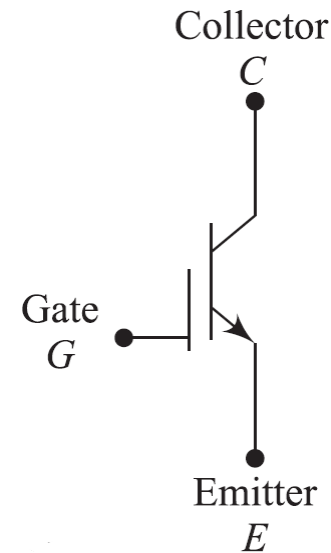- Low conduction loss (BJT)
 - High-speed turn-ON (MOSFET)
 - Low-power, easy drive (MOSFET)





n-channel IGBT

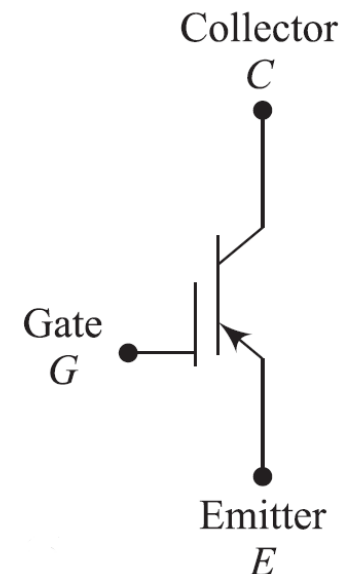


p-channel IGBT

IGBT I-V Characteristics

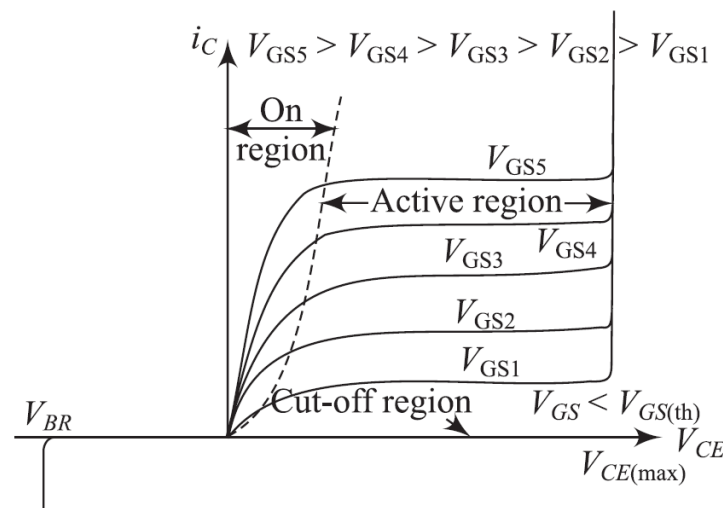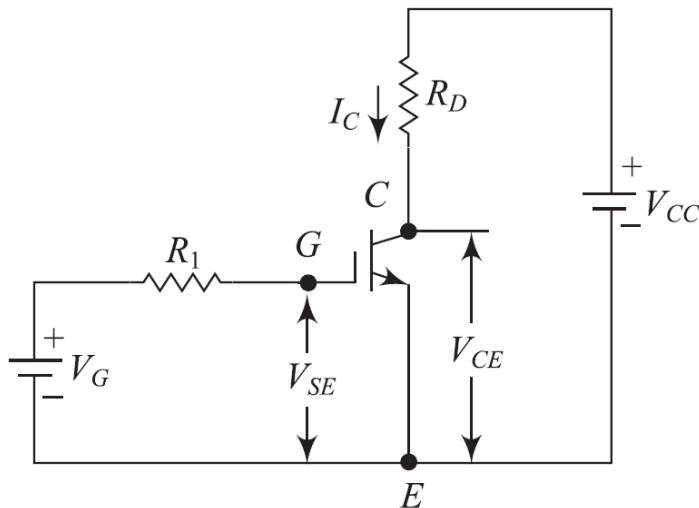- Emitter terminal is common between input and output of IGBT.
- *Transfer characteristics:* I_C versus the V_{GE} – similar to MOSFET.
- *Output characteristics:* I_C versus V_{CE} for various values of V_{GE1}, V_{GE2} etc., In the forward direction, the shape of the output characteristic is like that of BJT. But here the controlling parameter is V_{GE} because IGBT is voltage-controlled device.




Output characteristics

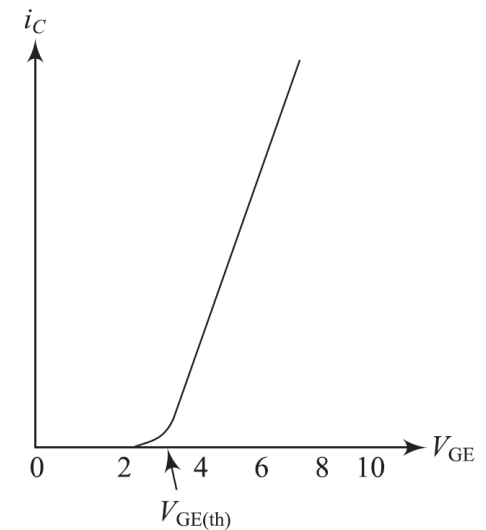


Transfer characteristics 13

Review of the classifications

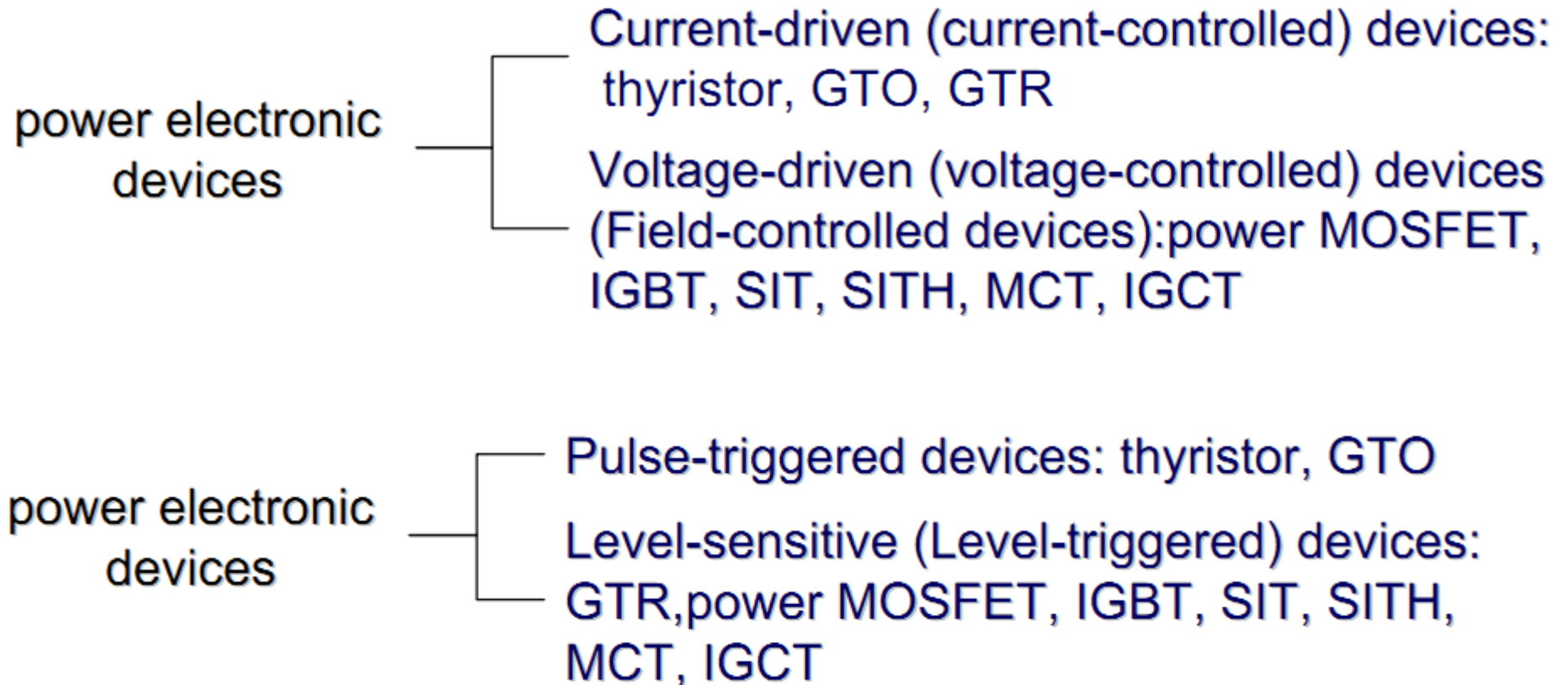

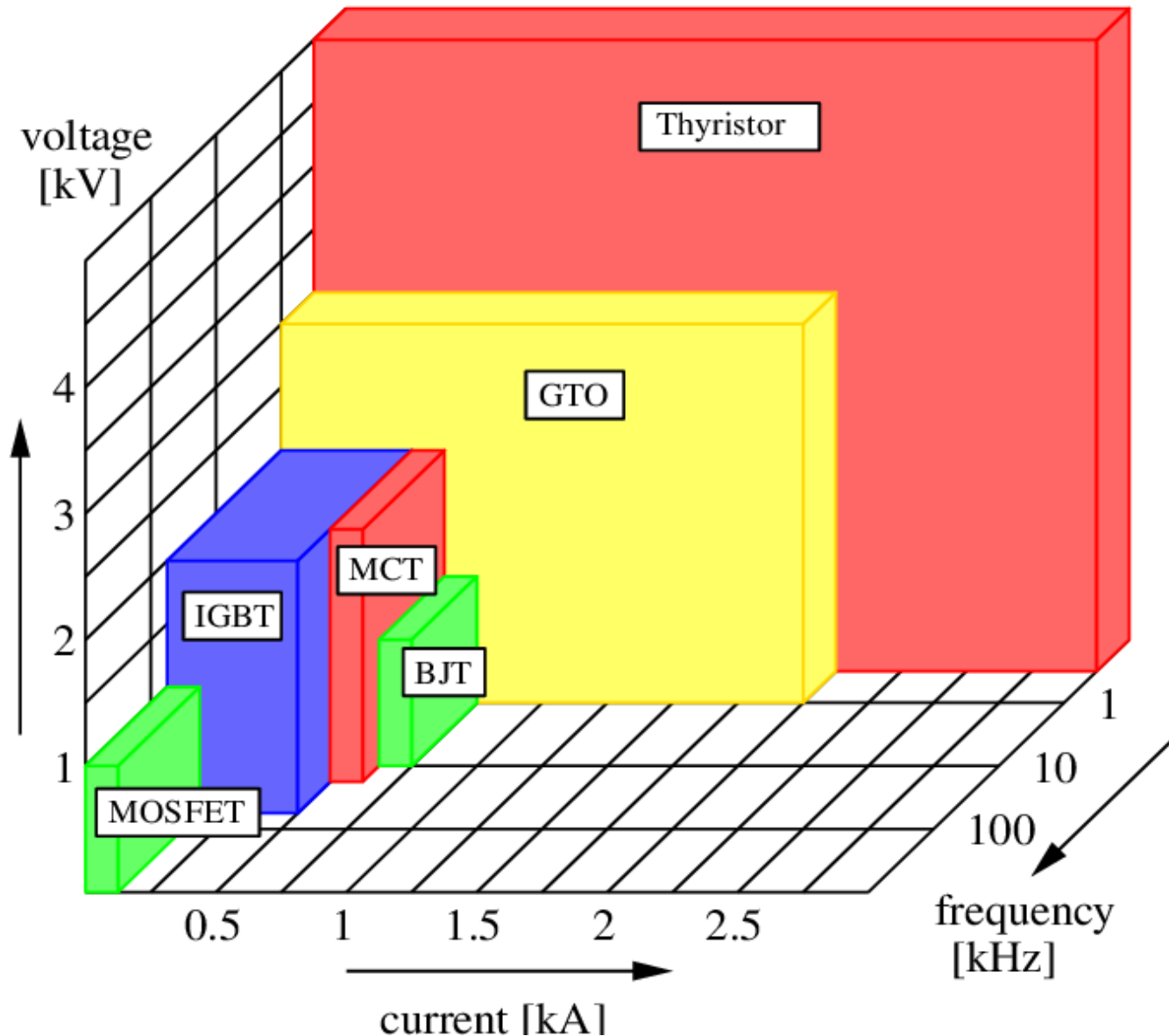Comparison of power semiconductor devices




2.0 Outline – DC to DC Converters

- ✓ Step-down operation
 - Duty cycle generation
- ✓ Types of DC-DC converter
 - Buck converters
 - Boost converters
 - Buck-Boost converter
- ✓ Closed-loop control of DC-DC converters

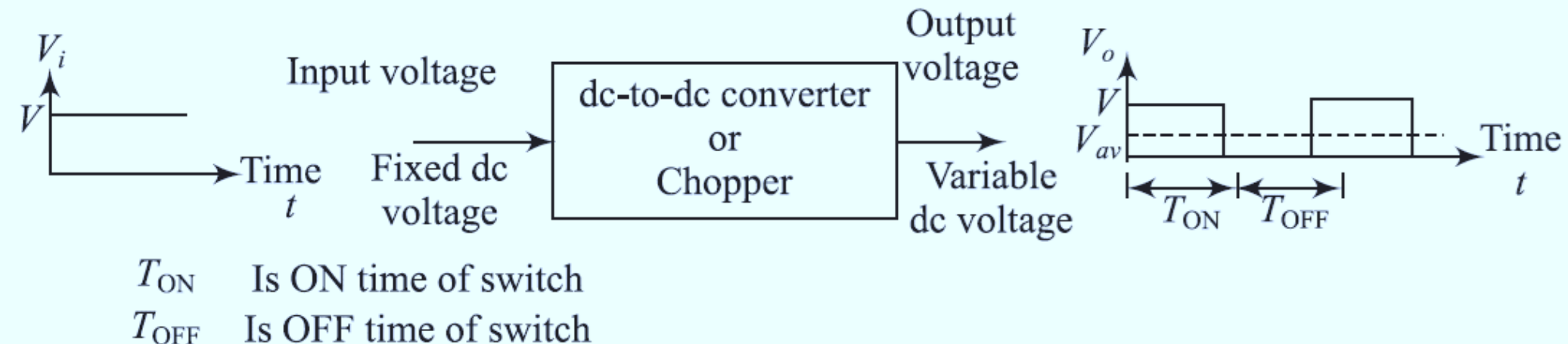2.1 Types of DC-DC Converters

- DC-DC converters (also called *choppers*) can be used to obtain a *variable dc voltage from a fixed dc supply*.
- Step-down (*Buck converters*) – output voltage is less than input voltage.
- Step-up (*Boost converters*) – output voltage is higher than input voltage.
- Step-up/down: *Buck-boost converters*
 - the output voltage can be higher or less than the input voltage.



2.1.1 Step-down operation

- Operates in two modes:
 - Switch S is ON $\rightarrow v_o = V_s$
 - Switch S is OFF $\rightarrow v_o = 0$
- Average output voltage:

$$V_o = \frac{1}{T} \int_0^T v_o(t) dt = \frac{1}{T} \int_0^{t_1} V_s dt = \frac{t_1}{T} V_s = k V_s$$



where k is the duty cycle;

t_1 – ON time period of switch.

t_2 – OFF time period of switch.

- RMS output voltage:



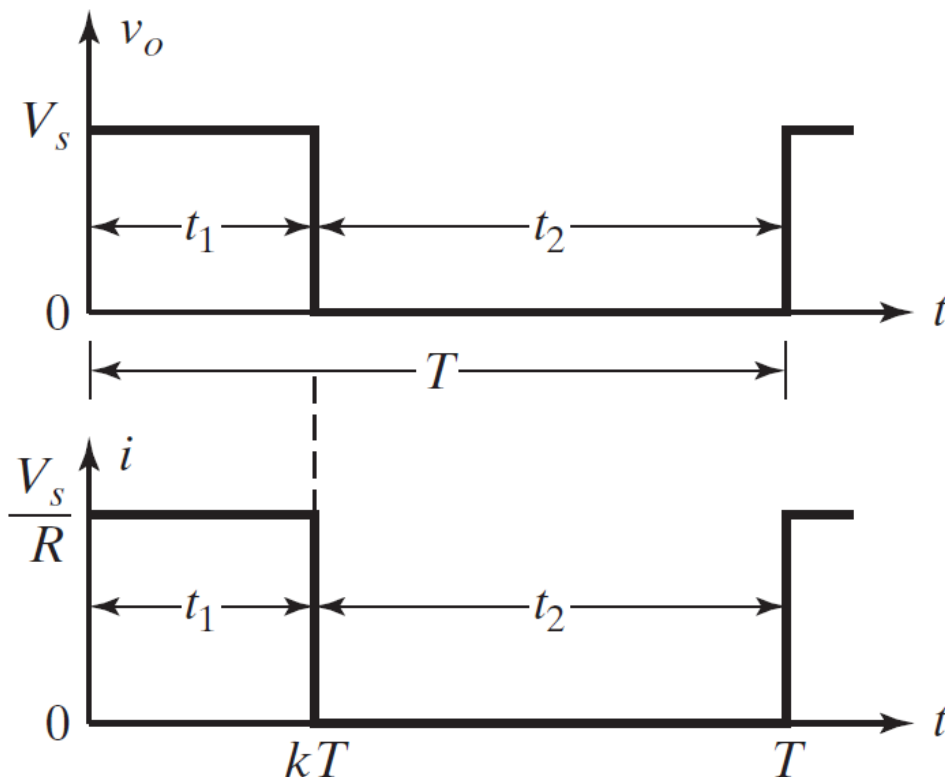
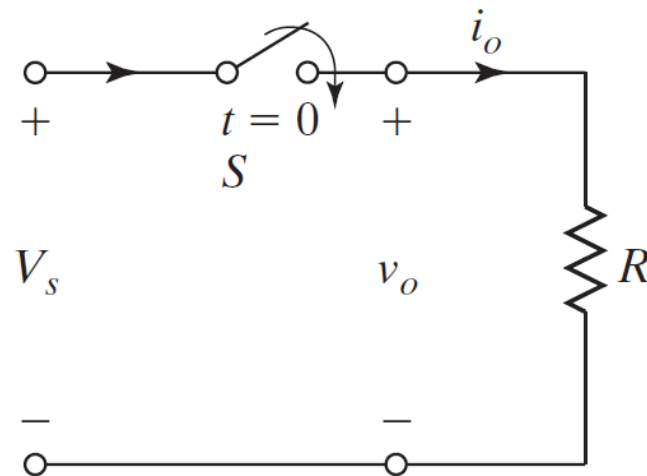
$$V_{RMS} = \left[\frac{1}{T} \int_0^T v_o^2(t) dt \right]^{1/2} = \sqrt{k} V_s$$



Switch \Rightarrow BJT, MOSFET, IGBT

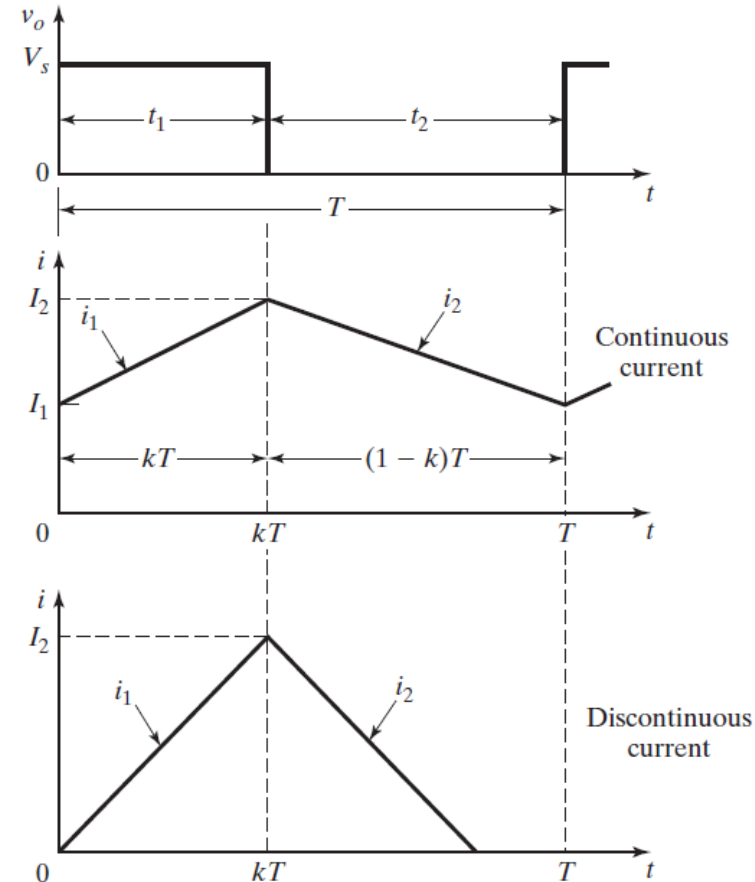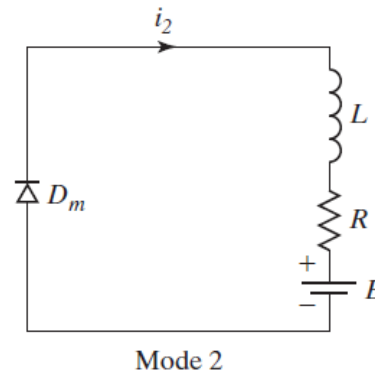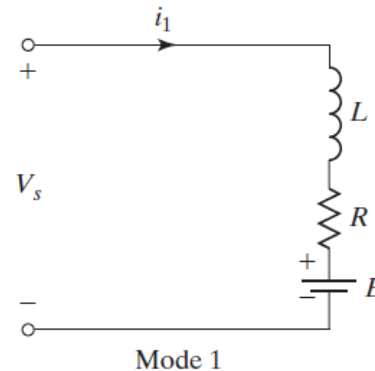
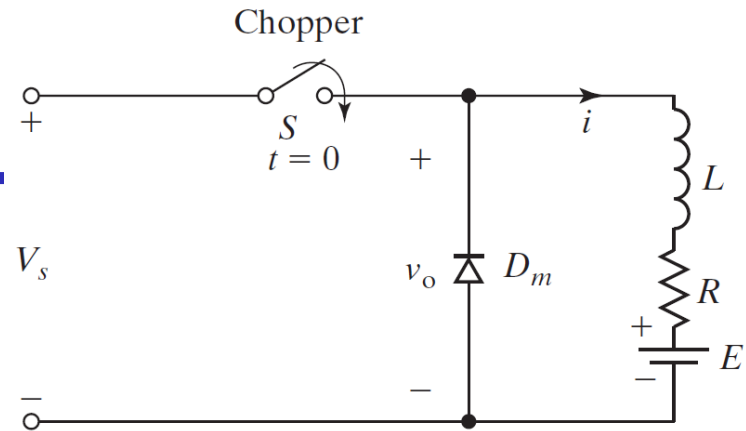
2.1.2 Step-down operation

- Operates in two modes (RL –load):
 - Switch S is ON \rightarrow current flows from supply to load
 - Switch S is OFF \rightarrow load current continues to flow thru freewheeling diode.
- Assume that the load current rises linearly.
- However, the current flowing through an RL load rises or falls exponentially with a time constant ($\tau = L/R$), which is generally much higher than switching period T .



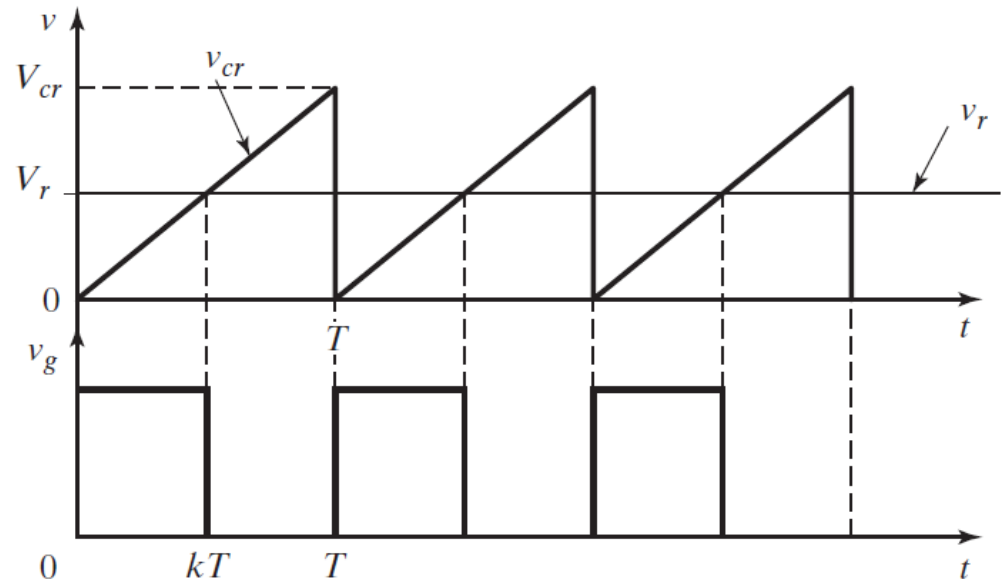
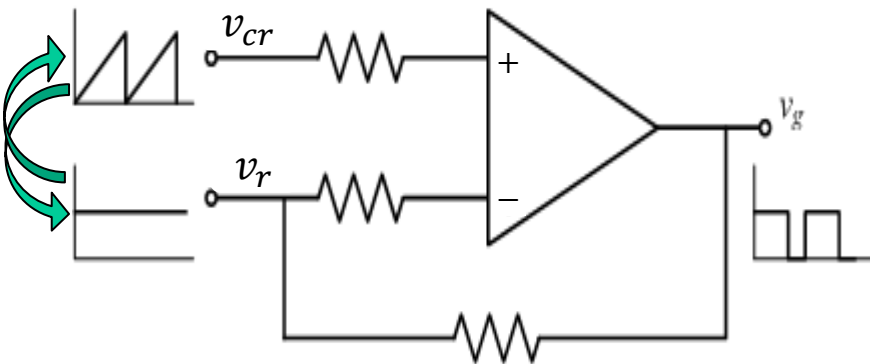
2.1.3 Generation of duty cycle

- If a saw-tooth signal v_{cr} and a DC reference signal v_r are supplied to a comparator, then the output of comparator is shown as v_g .
- The duty cycle of v_g is given as, $k = \frac{V_r}{V_{cr}}$
 - ✓ V_{cr} – is the peak value of v_{cr} ; V_r – is the peak value of v_r .
 - ✓ By varying the carrier signal v_{cr} from 0 to V_{cr} , the k can be varied from 0 to 1.
- This is how we control the voltage of a DC-DC converter.



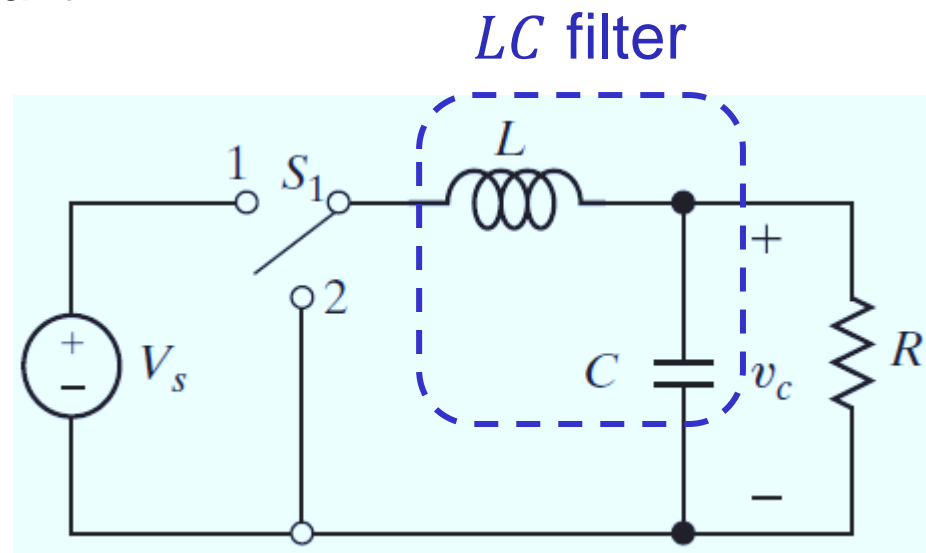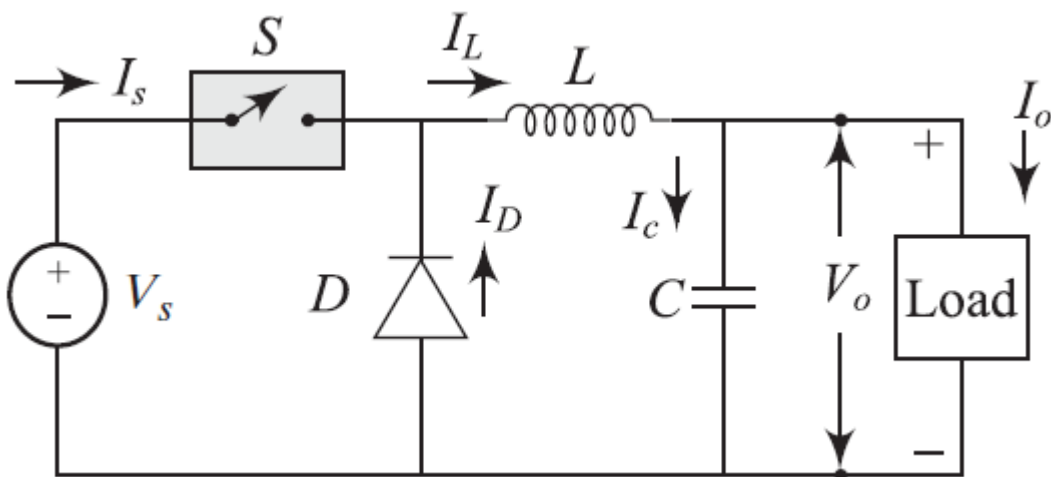2.2 Buck Converter



- Average output voltage is *less than* input voltage – hence, called *buck* converter.
- One switch and one diode (to overcome the problem of stored inductive energy).
- Switch S can be a power BJT and acts as a controlled switch; diode D is uncontrolled switch – operate as *two* SPST bidirectional switches, shown below.
- LC filter to remove switching harmonics and to pass only the DC component so that the output voltage v_o is nearly a constant.



2.2.1 Small ripple approximation


- The L-C form a practical low-pass filter.
 - Actual output voltage waveform:
- $$v_o = V_o + v_{ripple}$$
- In a well-designed converter, the output voltage ripple is small.
 - Hence, the waveforms can be easily determined by ignoring the ripple: $\|v_{ripple}\| \ll V_o$

$$\therefore v_o \approx V_o$$

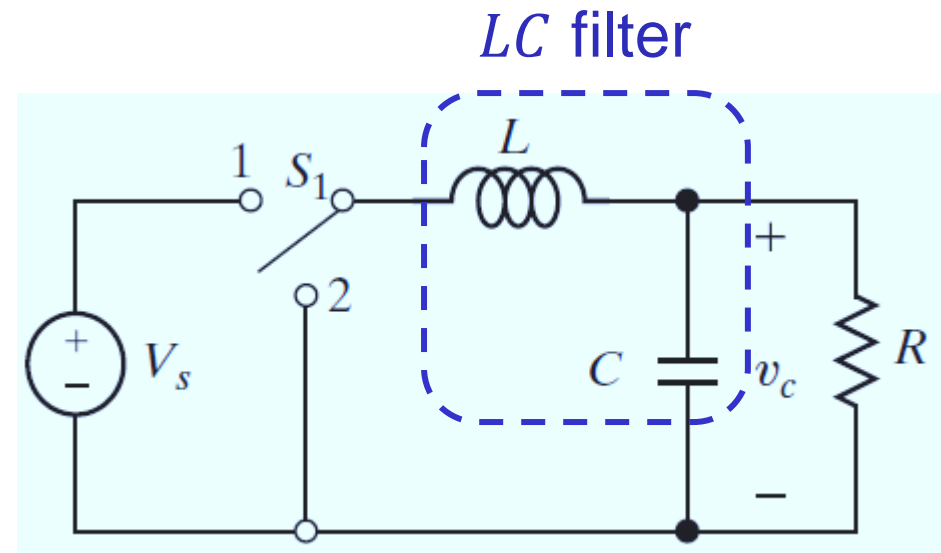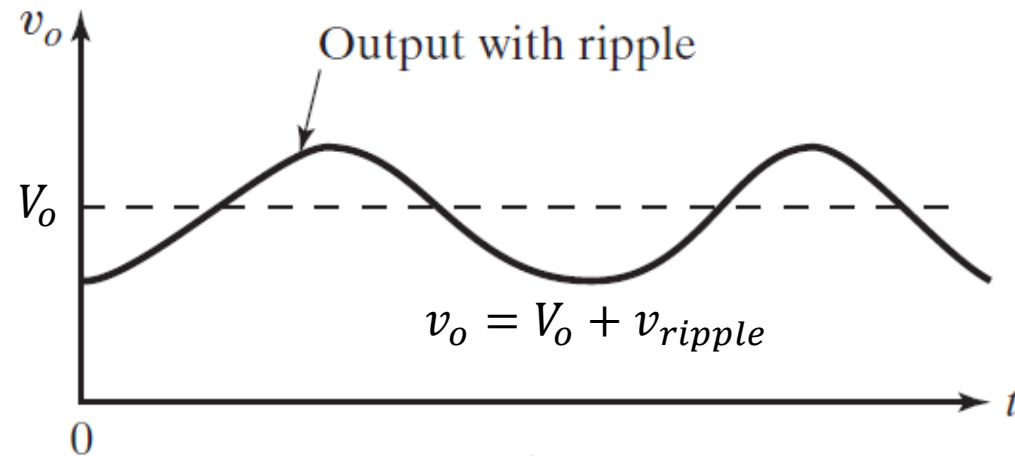


2.2.2 Operation modes

- **Mode 1:** Switch is ON (position 1 at $t = 0$)
 - Input current, rises, flows through L, C and load resistor R .
- **Mode 2:** Switch is OFF (position 2 at $t = t_1$)
 - Diode D conducts due to energy stored in the inductor & inductor current continues to flow through L, C, R , and D .
 - Inductor current falls until switch is ON again in the next cycle.

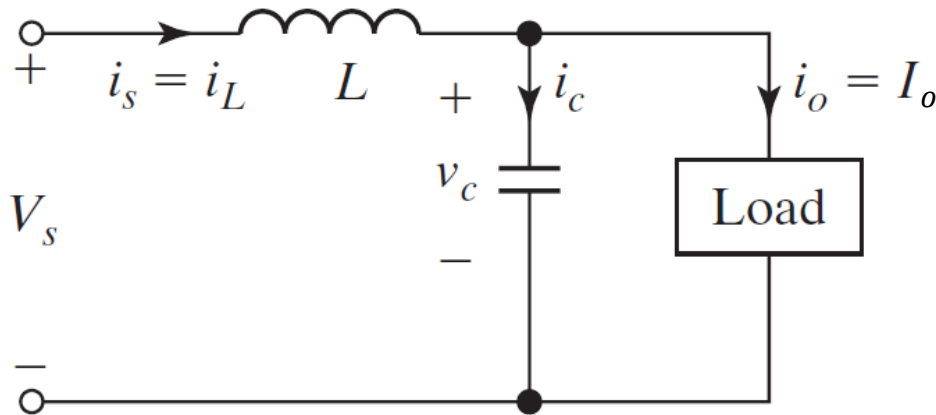

Mode 1

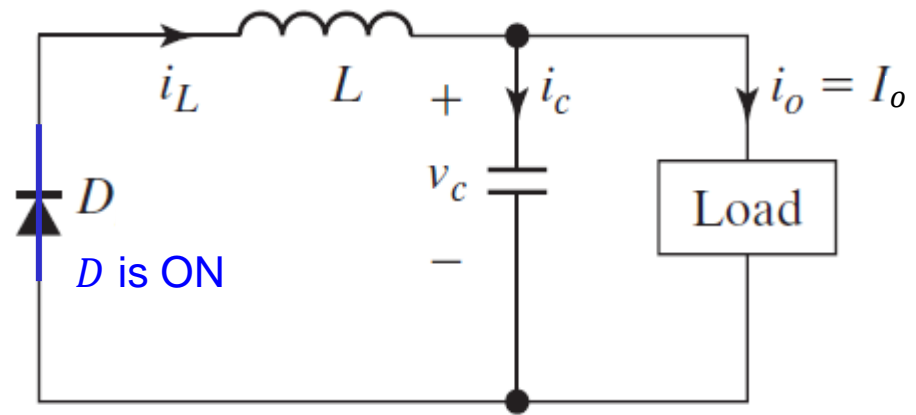

Mode 2

2.2.2 Operation modes


- The waveforms of voltages and currents are shown for a *continuous current flow in the L*.
- Assumed that the *current rises and falls linearly*.
- Depending on the *switching frequency*, filter inductance, capacitance, and inductor current could be *discontinuous*.
- Voltage across L , in general is, $v_L = L \frac{di_L}{dt}$

Mode 1: i_L rises linearly from I_1 to I_2 in time t_1

$$\therefore v_L = V_s - V_o = L \frac{I_2 - I_1}{t_1} = L \frac{\Delta I}{t_1} \rightarrow t_1 = \frac{L \Delta I}{V_s - V_o}$$

Mode 2: i_L falls linearly from I_2 to I_1 in time t_2
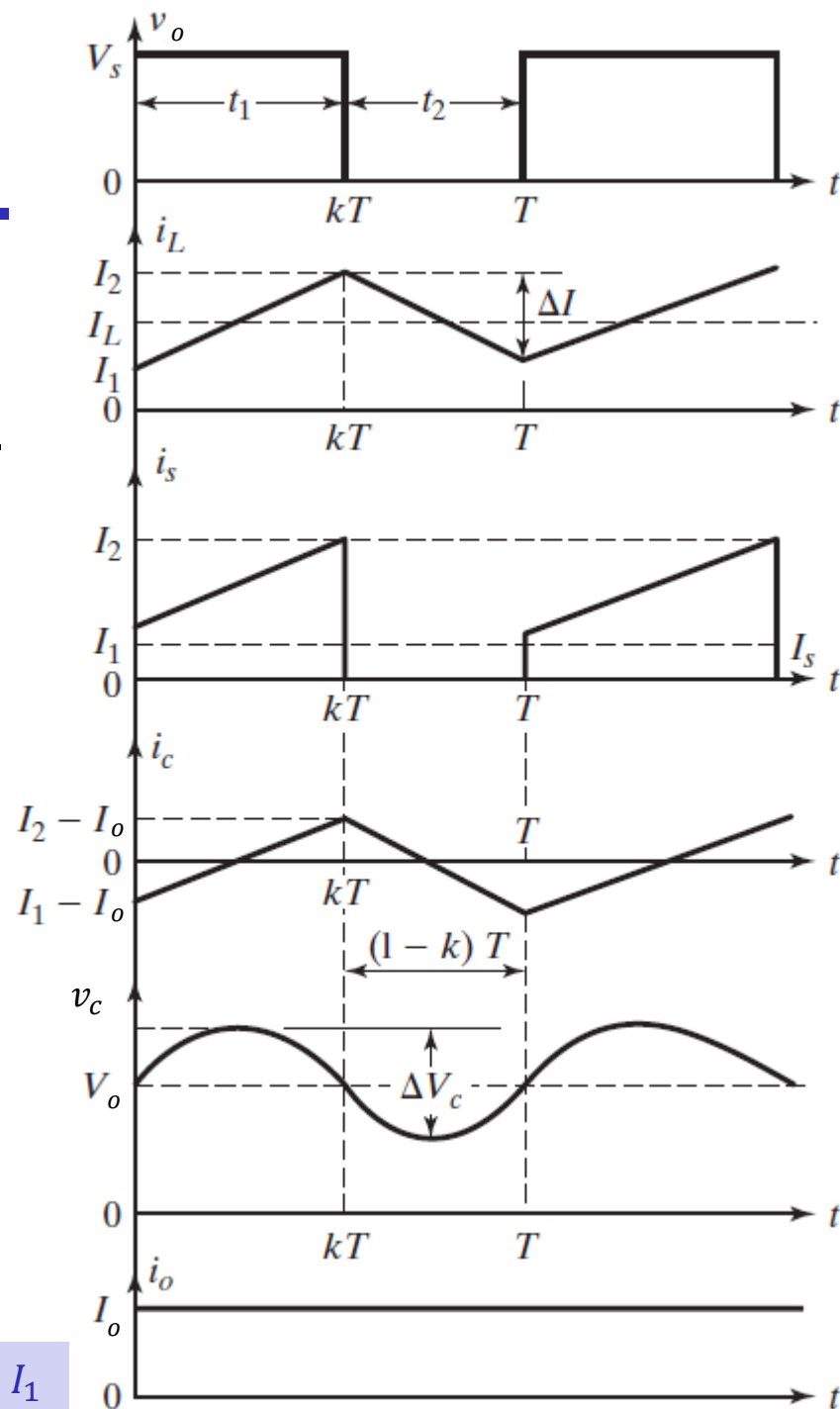
$$\therefore v_L = -V_o = L \frac{I_1 - I_2}{t_2} \rightarrow t_2 = \frac{L \Delta I}{V_o}$$




2.2.2 Operation modes


Volt-second balance

Since in *steady-state operation*, the waveform must repeat from one time period to the next, the integral of the v_L over one time period must be zero, i.e., $\int_0^T v_L dt = \int_0^{t_1} v_L dt + \int_{t_1}^T v_L dt = 0$.
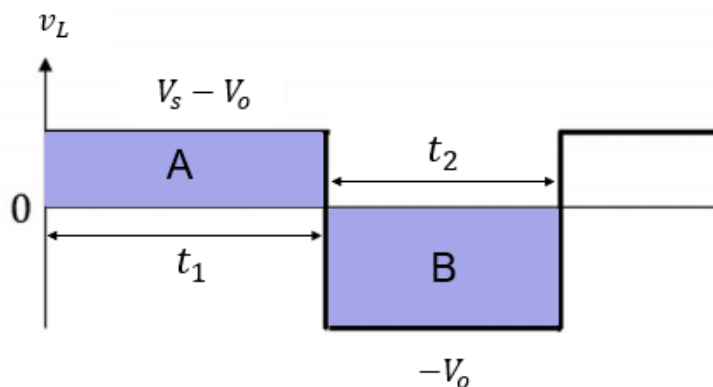
$$\therefore (V_s - V_o)t_1 = V_o(T - t_1) \rightarrow \frac{V_o}{V_s} = \frac{t_1}{T} = k$$



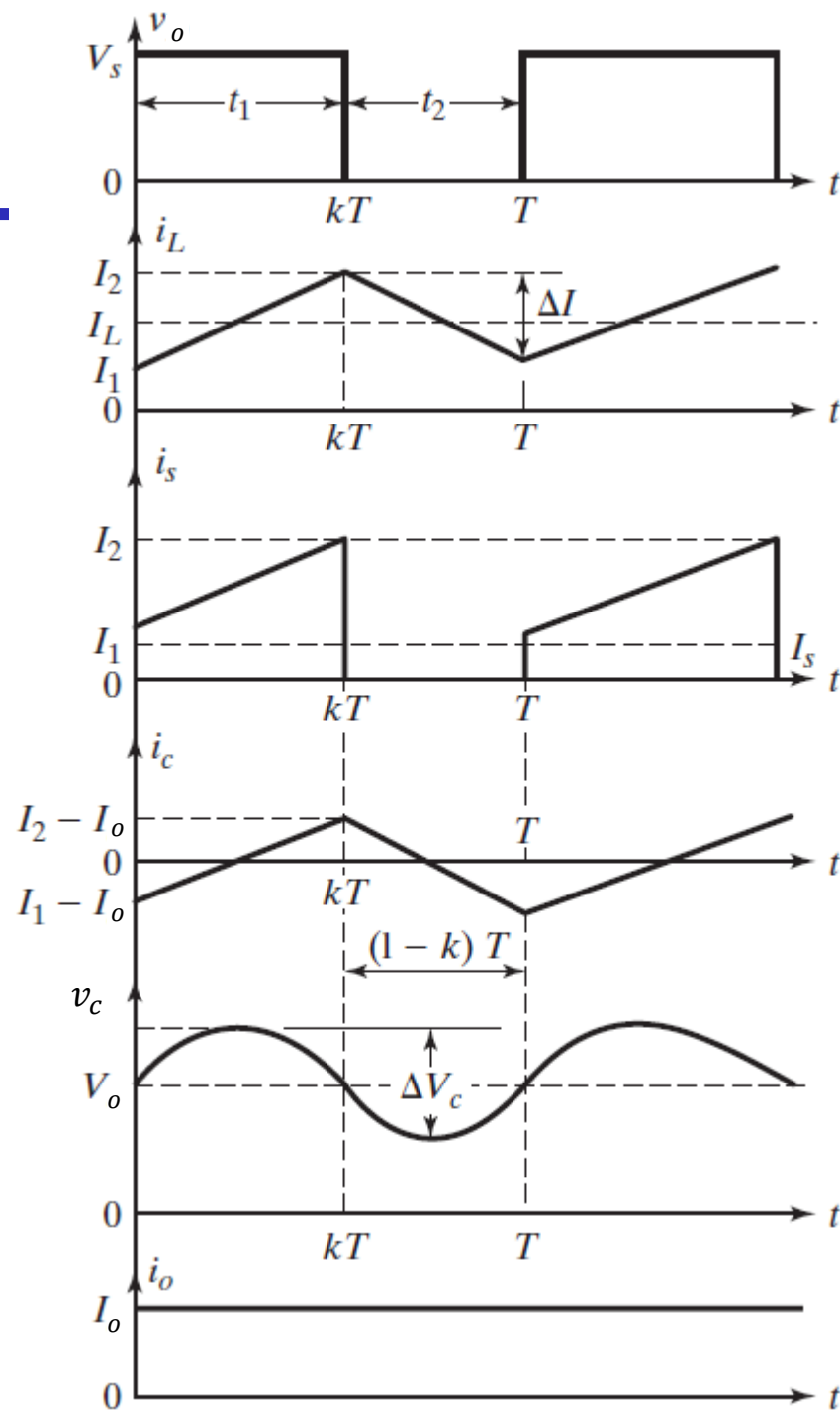- Neglecting power losses associated with all the circuit elements, the input power, $P_s = P_o$.
- Therefore, $V_s I_s = V_o I_o \rightarrow I_s = k I_o$.



Peak-to-peak inductor ripple current

- Switching period can be expressed as

$$T = \frac{1}{f} \rightarrow f = \frac{1}{T} = \frac{1}{t_1 + t_2} = \frac{1}{\frac{L \Delta I}{V_s - V_o} + \frac{L \Delta I}{V_o}} = \frac{V_o(V_s - V_o)}{L V_s \Delta I}$$


which gives the peak-to-peak ripple current as

$$\Delta I = \frac{V_o(V_s - V_o)}{f L V_s} \equiv \frac{k V_s (1 - k)}{f L}$$

- Maximum and minimum values of inductor current are given by

$$I_2 = I_L + \frac{1}{2} \Delta I$$

$$I_1 = I_L - \frac{1}{2} \Delta I$$

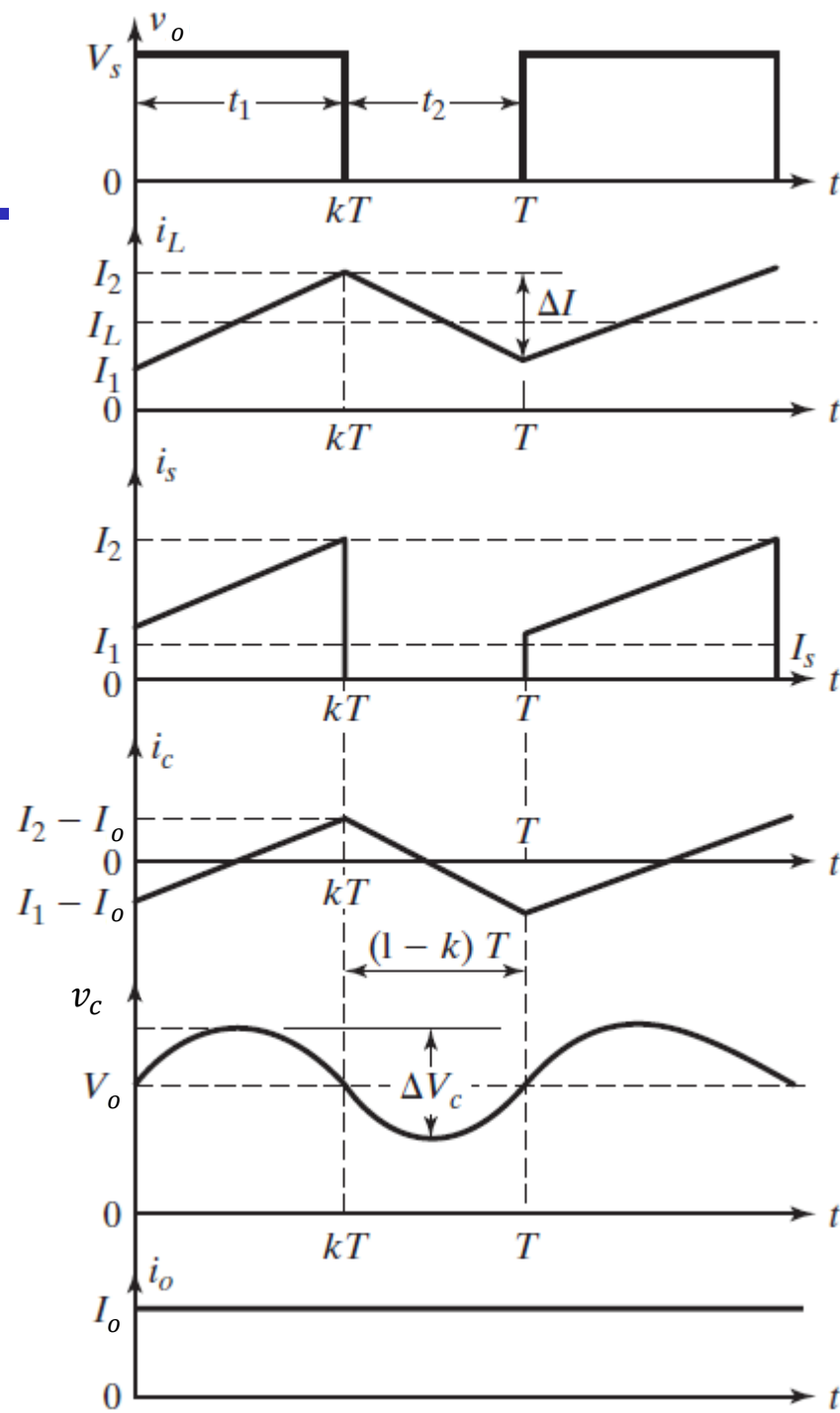

Peak-to-peak capacitor ripple voltage

- Using KCL, $i_L = i_c + i_o$
- Assume load ripple current Δi_o is very small and negligible, i.e., $\Delta i_L = \Delta i_c$.
- The average capacitor current, which flows for $t_1/2 + t_2/2 = T/2$, is $I_c = \Delta I/4$ \Rightarrow Think!
- The voltage across capacitor is expressed as


$$v_c = \frac{1}{C} \int i_c dt + v_c(t=0)$$

- The peak-to-peak ripple capacitor voltage is

$$\Delta V_c = v_c - v_c(t=0) = \frac{1}{C} \int_0^{T/2} \frac{\Delta I}{4} dt = \frac{\Delta I}{8fC}$$

- Substituting the value of ΔI from previous slide
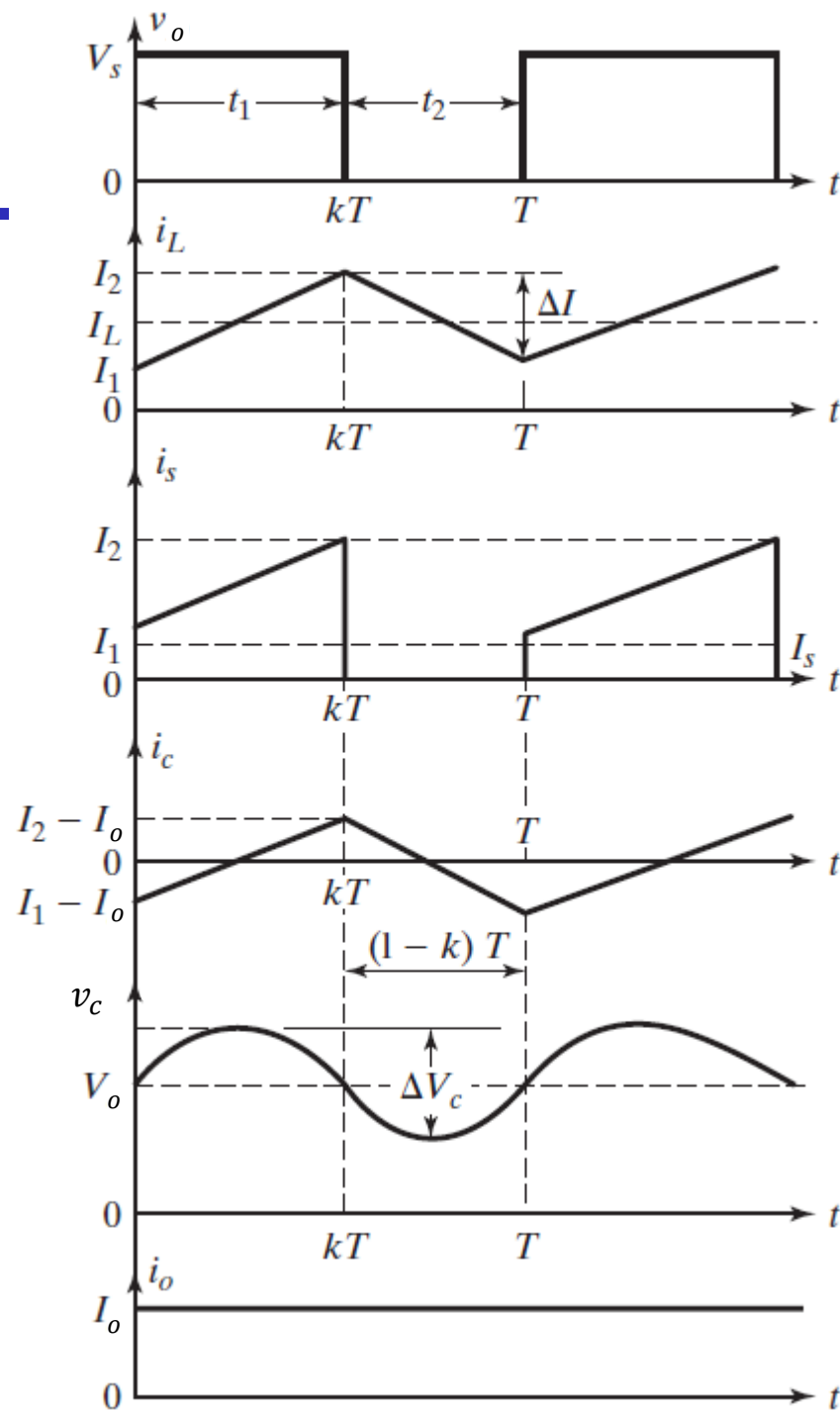
$$\Delta V_c = \frac{V_o(V_s - V_o)}{8f^2LCV_s} = \frac{kV_s(1-k)}{8f^2LC}$$



Condition for continuous inductor current and capacitor voltage

- If I_L is the average inductor current, the inductor ripple current $\Delta I = 2I_L$.

$$\Delta I = \frac{kV_s(1-k)}{fL} = 2I_L = 2I_o = \frac{2kV_s}{R}$$

which gives the critical value of the inductor L_c as

$$L_c = L = \frac{(1-k)R}{2f}$$

- If V_c is the average capacitor voltage, the capacitor ripple voltage $\Delta V_c = 2V_o$.

$$\Delta V_c = \frac{kV_s(1-k)}{8f^2LC} = 2V_o = 2kV_s$$

which gives the critical value of the capacitor C_c as

$$C_c = C = \frac{1-k}{16Lf^2}$$

Example 1

A buck converter has an input voltage $V_s = 12V$. The required output voltage is $V_o = 5V$ at $R = 500\ \Omega$ and the peak-to-peak output ripple voltage is 20 mV. The switching frequency is 25kHz. If the peak-to-peak ripple current of inductor is limited to 0.8A, determine

- (1) the duty cycle, k .
- (2) the filter inductance L .
- (3) the filter capacitance C .
- (4) and the critical values of L and C .

Solution

$$V_s = 12\text{ V}, \Delta V_c = 20\text{mV}, \Delta I = 0.8\text{A}, f = 25\text{ kHz}, V_o = 5\text{ V}$$

$$1) \quad \therefore V_o = kV_s \rightarrow k = 0.4167 = 41.67\%$$

$$2) \quad \Delta I = \frac{(1-k)kV_s}{fL} \rightarrow L = 145.83\text{ }\mu\text{H}$$

$$3) \quad \Delta V_c = \frac{kV_s(1-k)}{8f^2LC} \rightarrow C = 200\text{ }\mu\text{F}$$

Solution

4) If I_L is average inductor current, the inductor ripple current

$$\Delta I = \frac{kV_s(1-k)}{fL} = 2I_L = 2I_o = \frac{2kV_s}{R}$$

gives critical value of inductor $L_C = L = \frac{(1-k)R}{2f} = 5.83 \text{ mH}$



If V_C is average capacitor voltage, the capacitor ripple voltage

$$\Delta V_C = \frac{kV_s(1-k)}{8f^2LC} = 2V_o = 2kV_s$$

gives critical value of capacitor, $C_C = C = \frac{1-k}{16Lf^2} = 0.4 \text{ } \mu\text{F}$

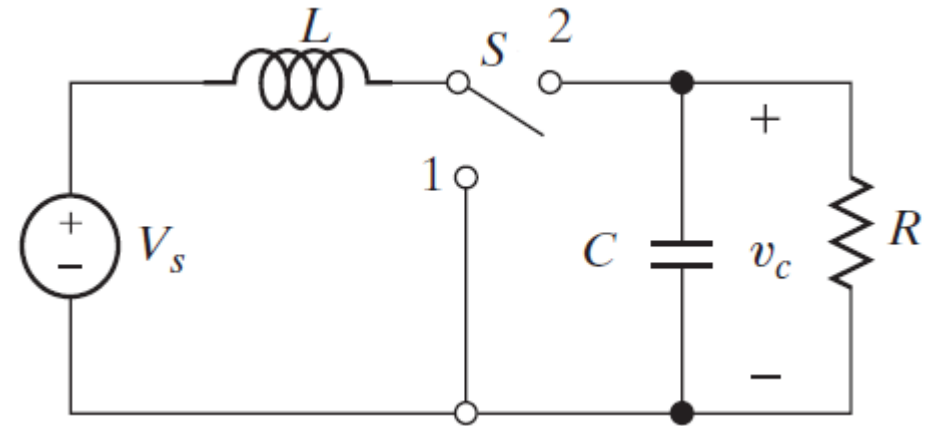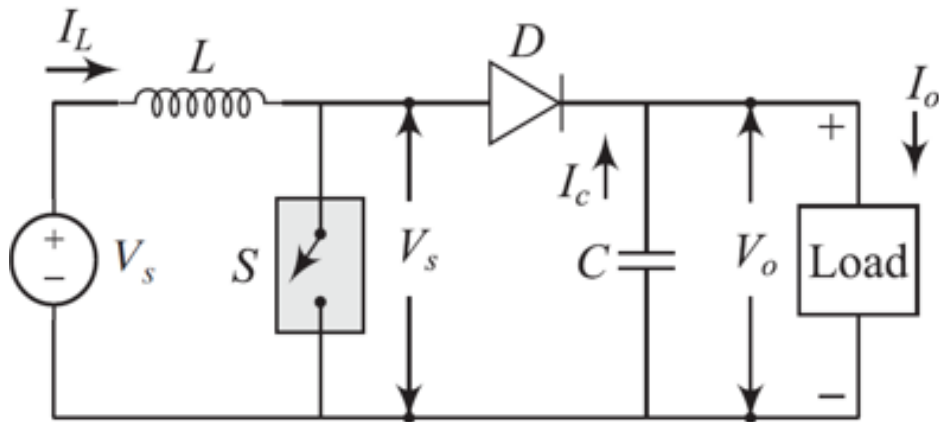
2.3 Boost Converter

- Average output voltage is *greater than* input voltage – hence, called *boost* converter.
- One switch and one diode (to overcome the problem of stored inductive energy).
- Switch S can be a power MOSFET and acts as a controlled switch; diode D is uncontrolled switch – operate as *two* SPST bidirectional switches, shown below.




2.3.1 Operation modes

- **Mode 1:** Switch is ON (position 1 at $t = 0$)
 - Input current, rises, flows through L and transistor (i.e., switch).
- **Mode 2:** Switch is OFF (position 2 at $t = t_1$)
 - Current that was flowing through transistor would now flow through L, C, R & D .
 - Inductor current falls until switch is ON again in the next cycle.
 - Energy stored in inductor L is transferred to the load.

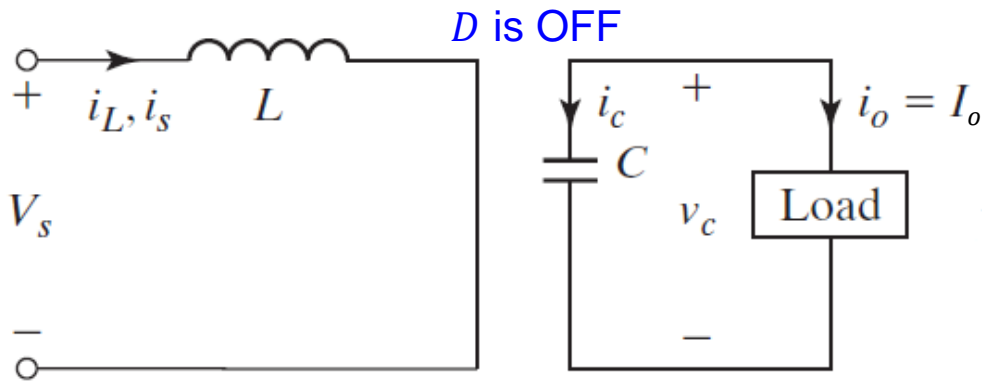

Mode 1

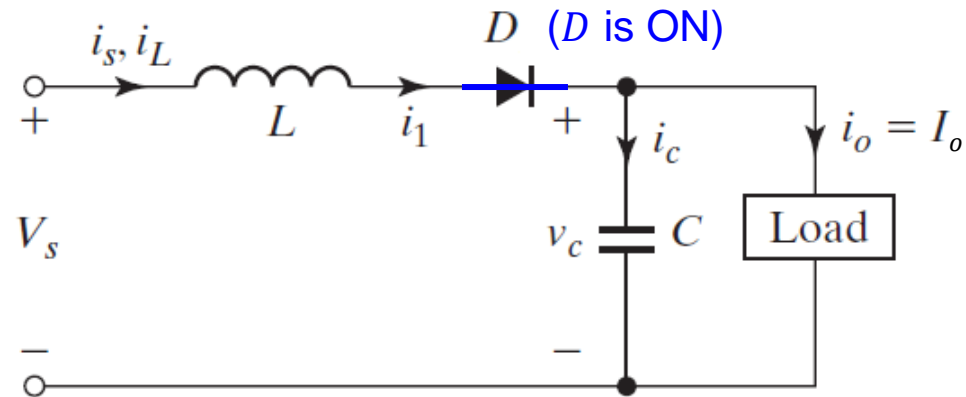

Mode 2

2.3.1 Operation modes

- The waveforms of voltages and currents are shown *for continuous load current*.
- Assumed that the *current rises and falls* linearly.
- Voltage across L , in general is, $v_L = L \frac{di_L}{dt}$


Mode 1: i_L rises linearly from I_1 to I_2 in time t_1

$$V_s = L \frac{I_2 - I_1}{t_1} = L \frac{\Delta I}{t_1} \rightarrow t_1 = \frac{L \Delta I}{V_s}$$

Mode 2: i_L falls linearly from I_2 to I_1 in time t_2

$$V_s - V_o = L \frac{I_1 - I_2}{t_2} \rightarrow t_2 = \frac{L \Delta I}{V_o - V_s}$$

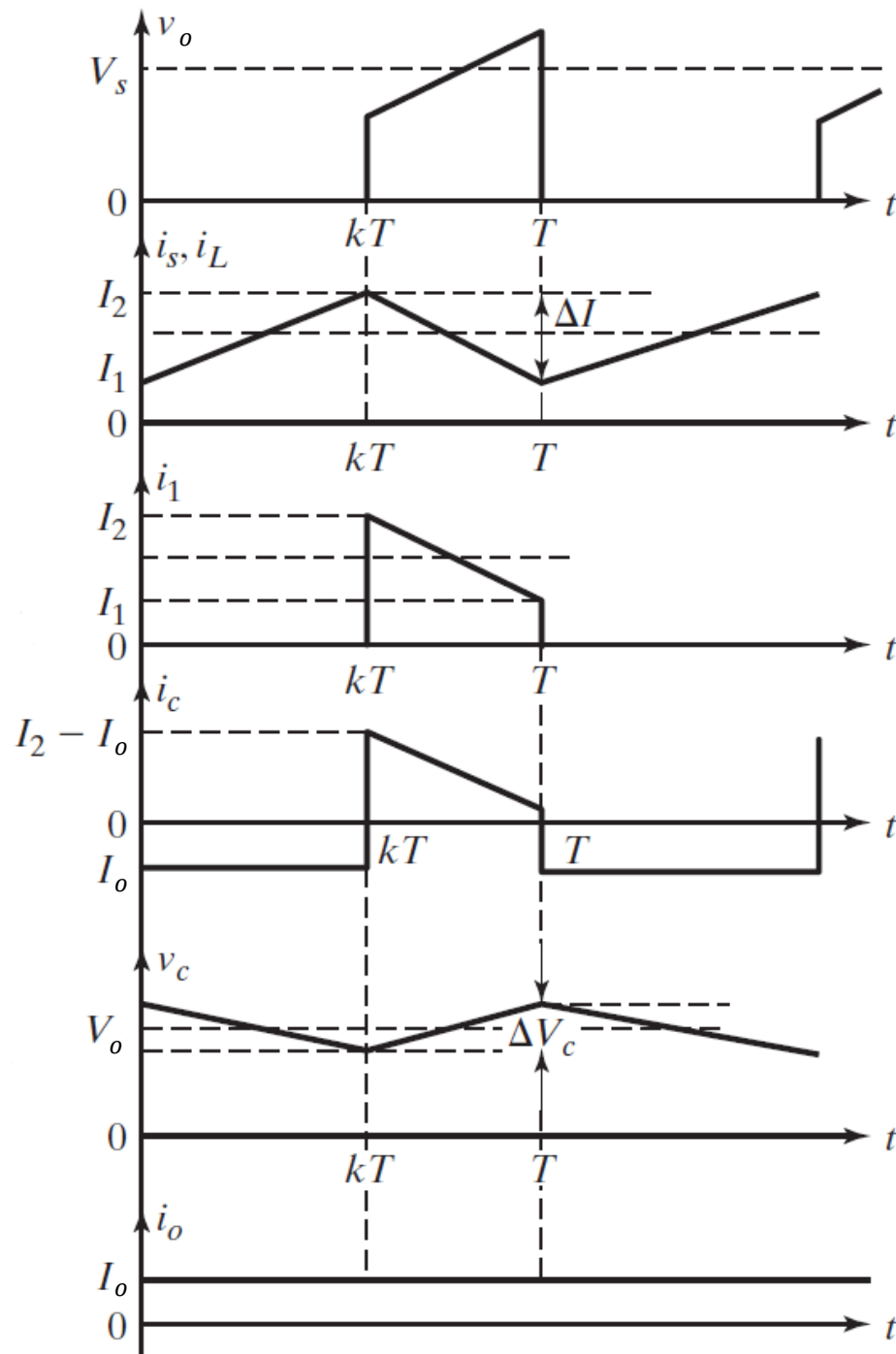Peak-peak ripple current, $\Delta I = I_2 - I_1$




2.3.1 Operation modes


- Since in *steady-state operation*, the waveform must repeat from one time period to the next, the integral of the v_L over one time period must be zero, i.e.,

$$\int_0^T v_L dt = \int_0^{t_1} v_L dt + \int_{t_1}^T v_L dt = 0.$$
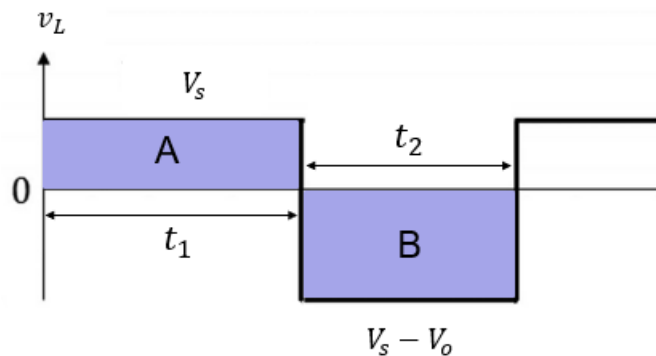
$$V_s t_1 + (V_s - V_o)(T - t_1) \rightarrow \frac{V_o}{V_s} = \frac{T}{T - t_1} = \frac{1}{1 - k}$$



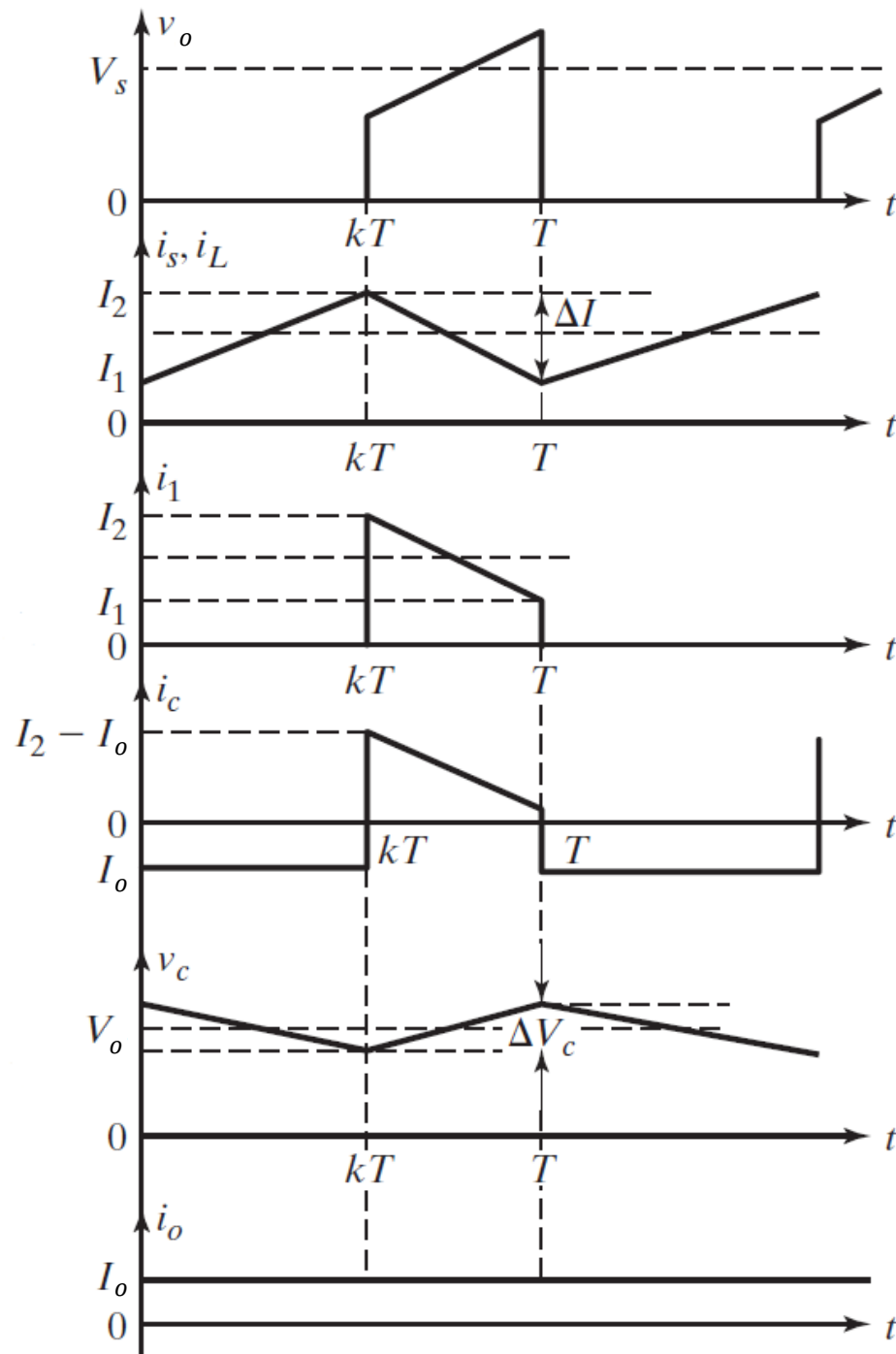- Neglecting power losses associated with all circuit elements, input power, $P_s = P_o$.
- Therefore, $V_s I_s = V_o I_o \rightarrow I_s = \frac{I_o}{1 - k}$



Peak-to-peak inductor ripple current

- Switching period can be expressed as

$$T = \frac{1}{f} \rightarrow f = \frac{1}{T} = \frac{1}{t_1 + t_2} = \frac{1}{\frac{L \Delta I}{V_s} + \frac{L \Delta I}{V_o - V_s}} = \frac{V_s(V_o - V_s)}{L V_o \Delta I}$$


which gives the peak-to-peak ripple current as

$$\Delta I = \frac{V_s(V_o - V_s)}{f L V_o} \equiv \frac{k V_s}{f L}$$

- Maximum and minimum values of inductor current are given by

$$I_2 = I_L + \frac{1}{2} \Delta I$$

$$I_1 = I_L - \frac{1}{2} \Delta I$$

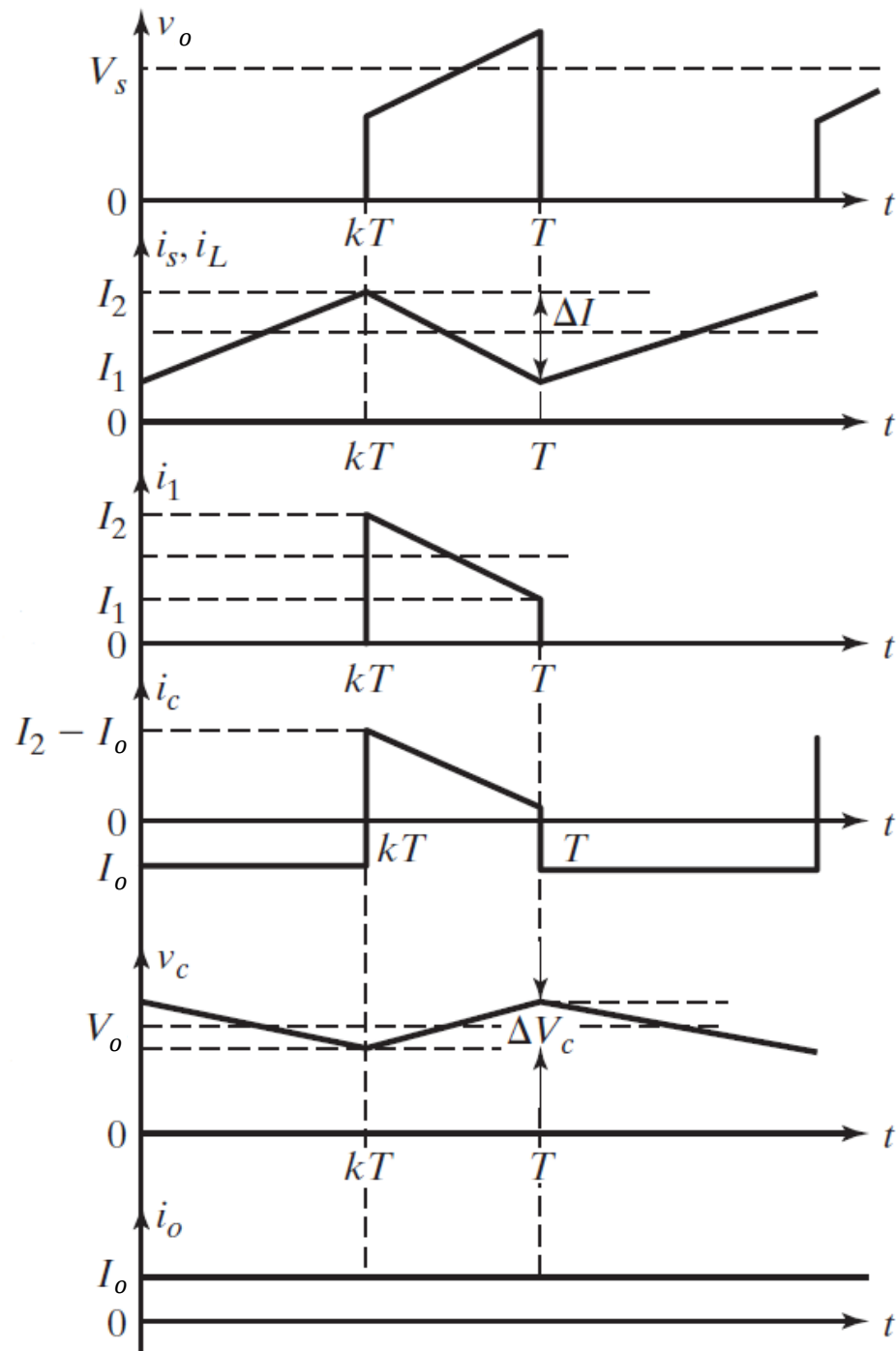

Peak-to-peak capacitor ripple voltage


- When switch is ON, the capacitor supplies load current for $t = t_1$. The average capacitor current during time t_1 is $I_c = I_o$ and the peak-to-peak ripple voltage of capacitor is

$$\Delta V_c = v_c - v_c(t = 0) = \frac{1}{C} \int_0^{t_1} I_c dt = \frac{1}{C} \int_0^{t_1} I_o dt = \frac{I_o t_1}{C}$$

Recall, $\frac{V_o}{V_s} = \frac{T}{T-t_1} = \frac{1}{1-k} \rightarrow t_1 = \frac{V_o - V_s}{V_o f}$

- Substituting the value of $t_1 = \frac{V_o - V_s}{V_o f}$ above,
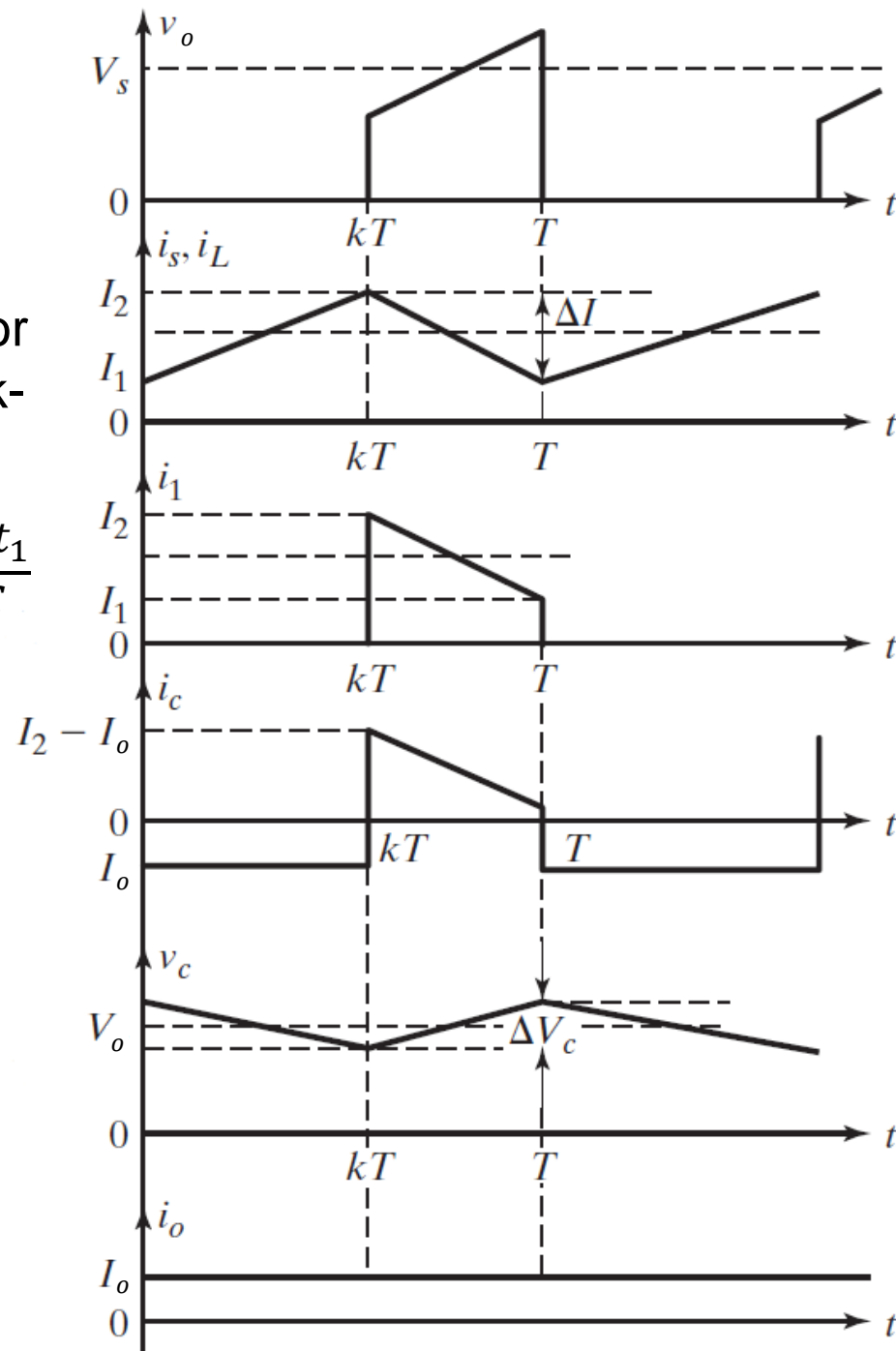
$$\Delta V_c = \frac{I_o (V_o - V_s)}{V_o f C} = \frac{I_o k}{f C}$$



Condition for continuous inductor current and capacitor voltage

- If I_L is the average inductor current, the inductor ripple current $\Delta I = 2I_L$.

$$\Delta I = \frac{kV_s}{fL} = 2I_L = 2I_s = \frac{2I_o}{1-k} = \frac{2V_o}{(1-k)R} = \frac{2V_s}{R(1-k)^2}$$

which gives the critical value of the inductor L_c as

$$L_c = L = \frac{k(1-k)R}{2f}$$

- If V_c is the average capacitor voltage, the capacitor ripple voltage $\Delta V_c = 2V_o$.

$$\Delta V_c = \frac{I_o k}{fC} = 2V_o = 2I_o R$$

which gives the critical value of the capacitor C_c as

$$C_c = C = \frac{k}{2Rf}$$

Example 2

A boost converter has an input voltage of $V_s = 5V$. The average output voltage $V_o = 15V$ and the load current $I_o = 0.5A$. The switching frequency is 25 kHz. If $L = 150 \mu H$ and $C = 220 \mu F$, determine

- (1) the duty cycle.
- (2) the ripple current of inductor ΔI .
- (3) The peak current of inductor I_2 .
- (4) the ripple voltage of filter capacitor ΔV_C .

Solution

$$V_s = 5\text{ V}, V_o = 15\text{ V}, f = 25\text{ kHz}, L = 150\text{ }\mu\text{H}, C = 220\text{ }\mu\text{F}$$




$$1) V_o = \frac{V_s}{1-k} \rightarrow k = 0.6667 = 66.67\%$$

$$2) \Delta I = \frac{kV_s}{fL} = 0.89\text{ A}$$


$$3) I_L = \frac{I_o}{1-k} = \frac{0.5}{1-0.667} = 1.5\text{ A} \rightarrow I_2 = I_L + \frac{\Delta I}{2} = 1.945\text{ A}$$

$$4) \Delta V_c = \frac{I_o k}{fC} = 60.61\text{ mV}$$

2.4 Buck-Boost converter

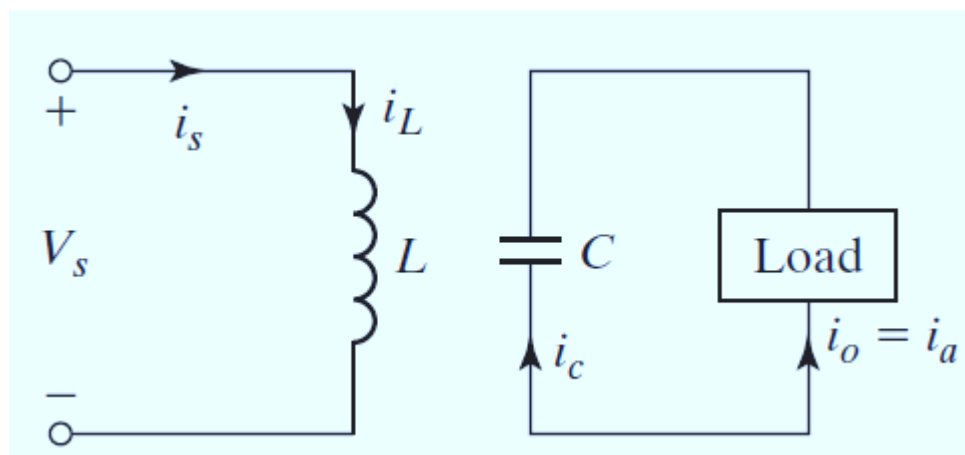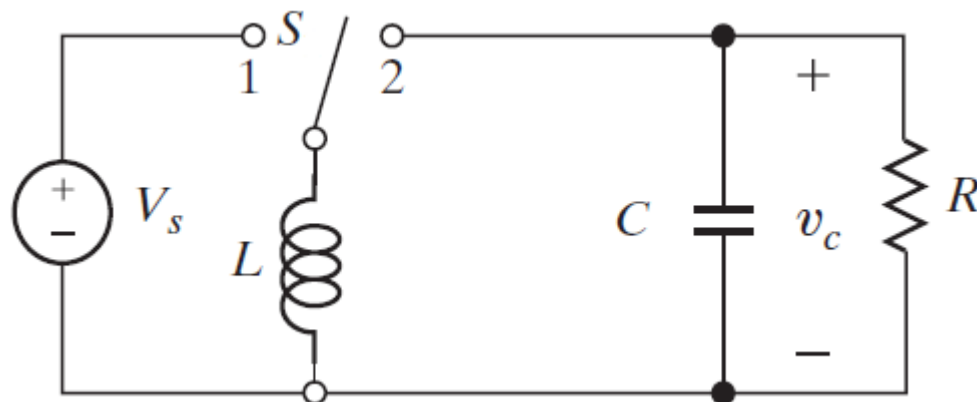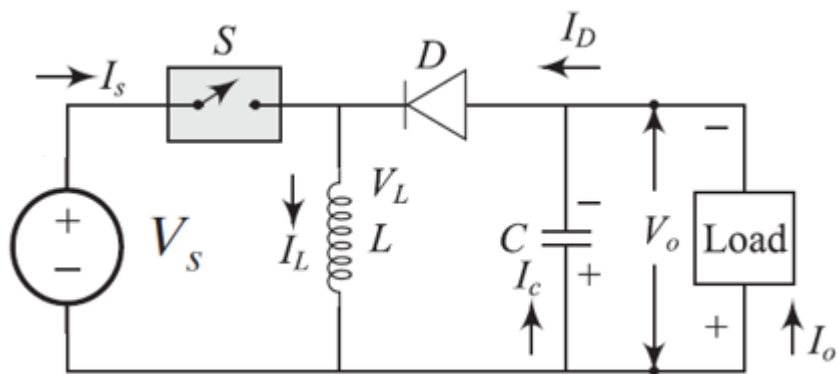

Mode 1

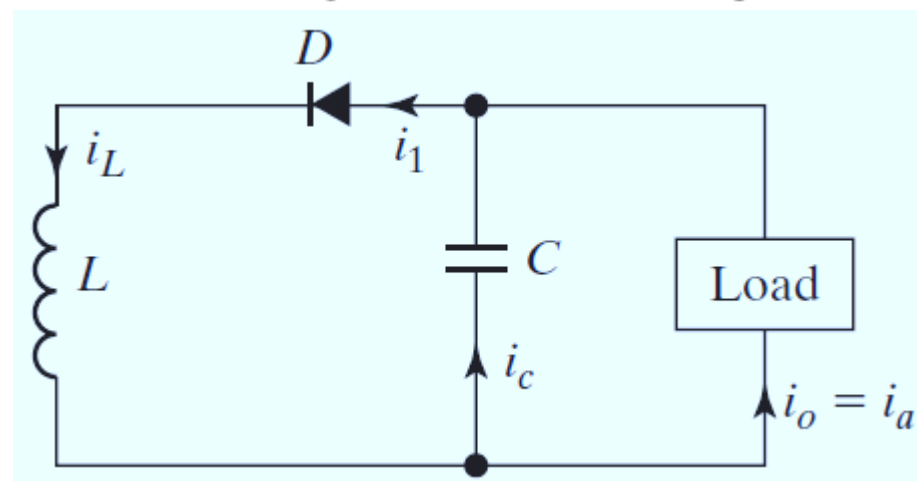



Mode 2

- Output voltage may be *less or greater than* input voltage; the output voltage polarity is *opposite* to that of input voltage.



$$V_o = -\frac{V_s k}{1 - k}$$

2.5 Comparison of basic Converters



Buck

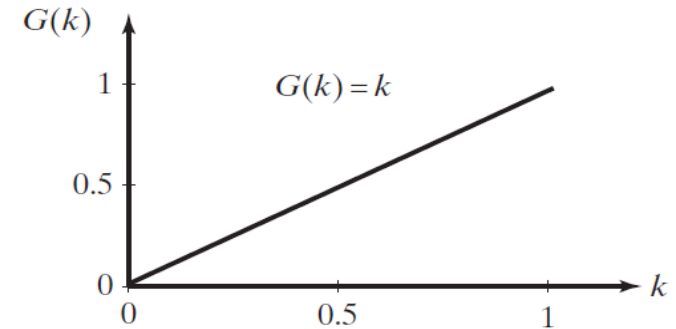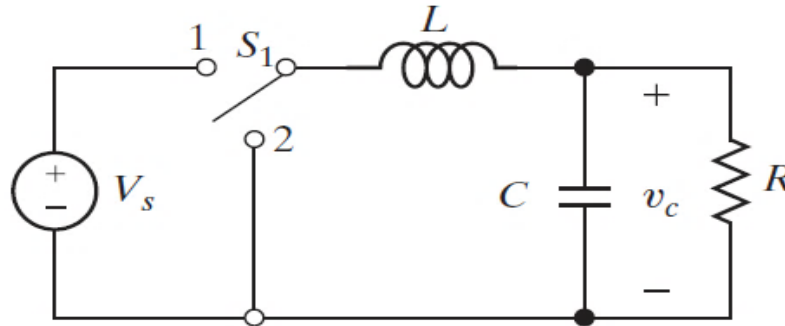

Boost

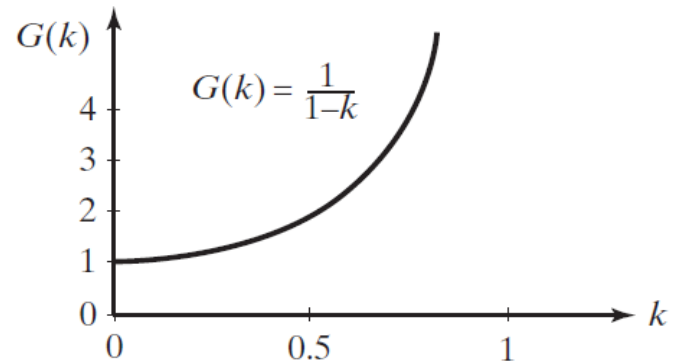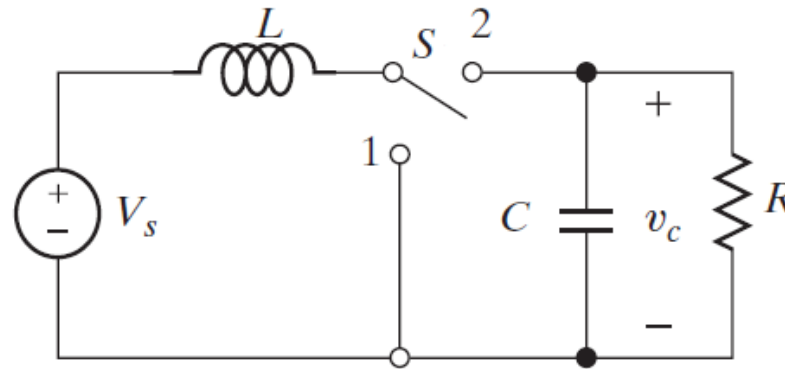

Buck-Boost

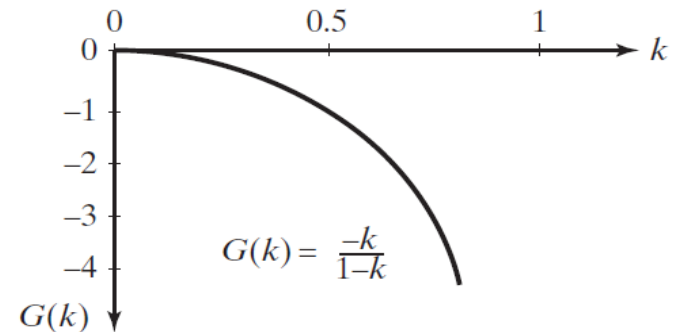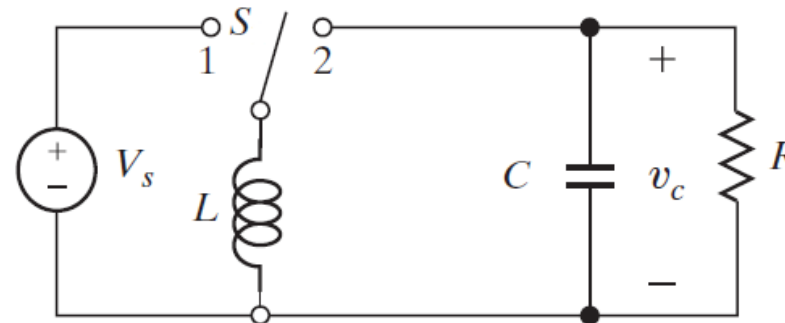


Switch representation

Comparison of voltage gains



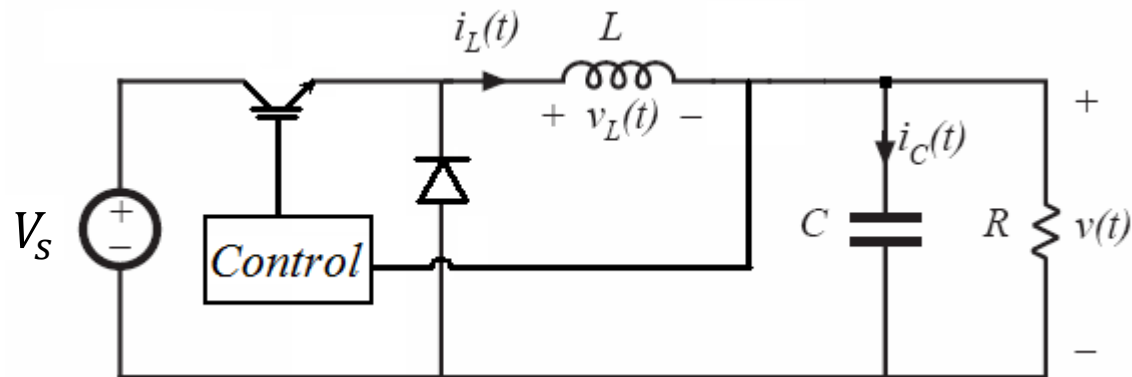2.6 Closed-loop control of DC-DC converters

- As have been seen, the output voltage of a DC-DC converter is related to the duty cycle k . In practice, one will never get an accurate output voltage if the duty cycle is fixed at the calculated value because
 - The components are not ideal: switching losses, diode voltage drop, inductor resistance etc
 - The load might change
 - There are fluctuations in the supply voltage V_s
 - ...
- A closed-loop controller to regulate the output voltage is needed!



Summary – 1. Power Transistors

- ✓ Power transistors are mainly: BJTs, MOSFETs, and IGBTs.
- ✓ BJTs are current-controlled devices.
- ✓ MOSFETs are voltage-controlled devices and require very low-gating power.
- ✓ IGBTs (combine the advantages of BJTs and MOSFETs), are voltage-controlled devices.
- ✓ Transistors can be connected in series or parallel
 - Parallel operation usually requires current-sharing elements
 - Series requires matching of parameters during turn-on & off

Summary – 2. DC to DC Converters

- ✓ Converters (*duty cycle*):

$$\text{Buck } (k), \quad \text{Boost } \left(\frac{1}{1-k}\right), \quad \text{Buck-boost } \left(\frac{-k}{1-k}\right)$$

- ✓ A DC converter can be used as a *dc transformer* to step up or step down a fixed dc voltage.
- ✓ Filters are used to reduce the harmonics generated at the input and load side of the converter.
- ✓ Average output voltage is controlled by controlling the switch on and off durations.

See you in the next class (April 28th)

❖ **Reminder (Lab report deadline – April 25th, 23:55 PM)**

The End