

EEE205 – Digital Electronics (II)

Lecture 13

Xiaoyang Chen, Jiangmin Gu, Ming Xu


Dept of Electrical & Electronic Engineering

XJTLU

In This Session

- We have learned how to derive the state graph from a given circuit and to analyze the circuit.
- Next we will learn how to derive the state table or graph from a problem statement and to design the circuit.
- State Assignment

General Form of A Sequential Circuit.

 

- The sequential circuits whose outputs depend only on the state of the circuit are of **Moore type**.
- Those whose outputs depend on both the state and the inputs are of **Mealy type**.

Moore State Model.

We wish to design such a circuit:

- The circuit has one input w and one output z .
- All changes in the circuit occur on the positive edge of a clock signal.
- The output z is 1 if during the past two clock cycles w was 1. Otherwise z is 0.


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

Sequences of input and output signals.

Moore State Model.

State Diagram

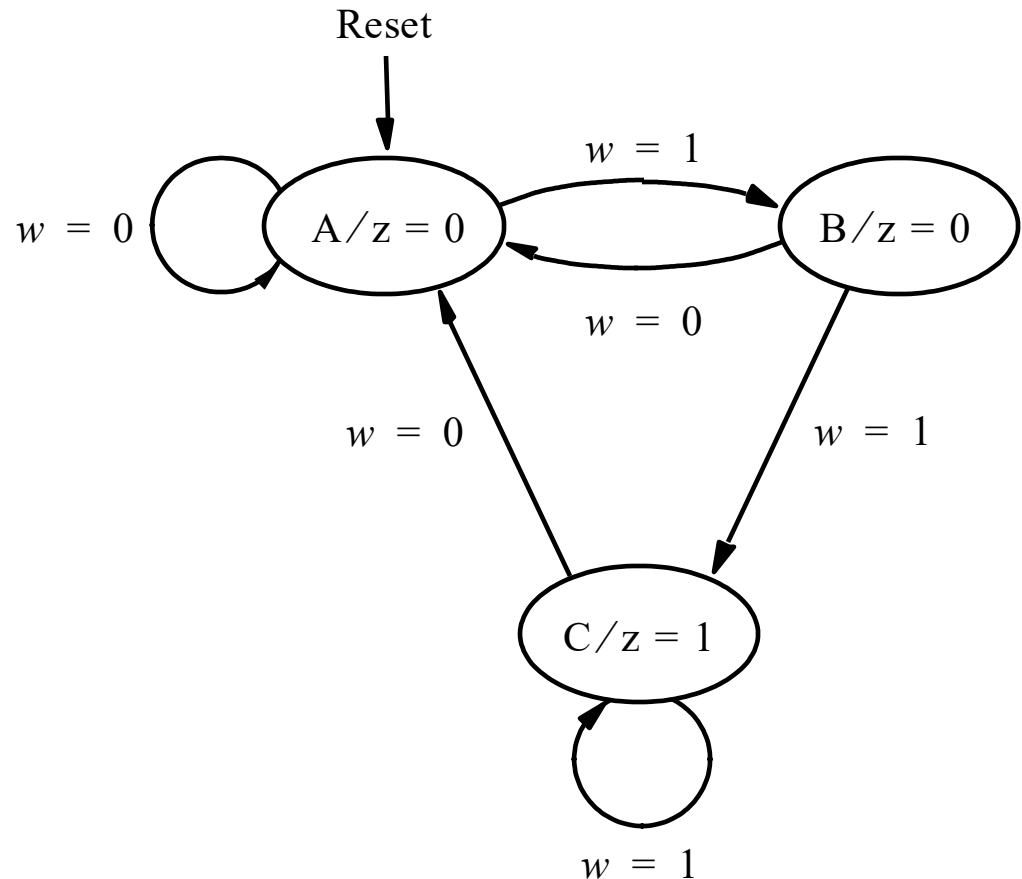- State A: w is 0 during past 1 clock cycle.
- State B: w has been 1 for just 1 clock cycle.
- State C: w has been 1 for 2 clock cycles.



Moore State Model.

State Table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

	Present state	Next state		Output z
		$w = 0$	$w = 1$	
	$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

Moore State Model.

Next-State and Output Expressions

$y_2 y_1$		00	01	11	10
		0	0	d	0
w	0	0	0	d	0
	1	1	0	d	0

$$Y_1 = w\bar{y}_1\bar{y}_2$$

y_1		0	1
		0	0
y_2	0	0	0
	1	1	d

$$z = y_2$$

$y_2 y_1$		00	01	11	10
		0	0	d	0
w	0	0	0	d	0
	1	0	1	d	1

$$\begin{aligned} Y_2 &= wy_1 + wy_2 \\ &= w(y_1 + y_2) \end{aligned}$$

Moore State Model.


Implementation

Output z depends on the state only.


$$Y_1 = w\bar{y}_1\bar{y}_2$$

$$\begin{aligned} Y_2 &= wy_1 + wy_2 \\ &= w(y_1 + y_2) \end{aligned}$$

$$z = y_2$$

 

Moore State Model - Timing Diagram

 

Input w changes slightly after the clock edges, because it is often an output of another circuit synchronized by the same clock.


Moore State Model.

Alternative State Assignment

	Present state y_2y_1	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	dd	dd	d

Moore State Model.

Improved
Implementation

 

Mealy State Model.

We wish to design such a circuit:

- The circuit has one input w and one output z .
- The output z is 1 in the clock cycle when the second occurrence of $w = 1$ is detected. Otherwise z is 0.


Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals.

Mealy State Model.

State Diagram

 - State A: w is 0, producing an output $z = 0$.
- State B: w is 1.
- If $w = 1$ for two or consecutive clock cycles, the machine remains in state B and produce an output $z = 1$.



Mealy State Model.

State Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1


	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

Mealy State Model.

Implementation

$$Y = D = w$$

$$z = wy$$

 


Output *z* depends on both the state and the input.

Mealy State Model - Timing Diagram

$$Y = D = w$$

$$z = wy$$

 

State Assignments

- The state assignment should be made so as to minimize the cost of the logic.
- If the number of states is small, it may be possible to try all possible state assignments.
- For a state table with 3 states, there are $4 \times 3 \times 2 = 24$ possible state assignments.
- But many of these are equivalent in cost of realization.

	1	2	3	4	5	6	7		19	20	21	22	23	24
S_0	00	00	00	00	00	00	01	...	11	11	11	11	11	11
S_1	01	01	10	10	11	11	00		00	00	01	01	10	10
S_2	10	11	01	11	01	10	10		01	10	00	10	00	01

State Assignments

- If we interchange two columns in an assignment, the cost will be unchanged, e.g. 1/3, 2/4, 5/6.
- If symmetrical flip-flops such as J-K, S-R or T are used, complementing one or more columns of an assignment will not change the cost, e.g. 2/7, 6/19.
- So there are only 3 non-equivalent assignments for 3 or 4 states.

	3-State Assignments			4-State Assignments		
States	1	2	3	1	2	3
<i>a</i>	00	00	00	00	00	00
<i>b</i>	01	01	11	01	01	11
<i>c</i>	10	11	01	10	11	01
<i>d</i>	—	—	—	11	10	10

State Assignments

One-Hot State Assignment


- For FPGAs it may not be important to minimize the number of flip-flops used in the design.
- The one-hot assignment uses one flip-flop for each state and only one flip-flop is set to 1 in each state.

e.g. a system with 4 states could use 4 flip-flops (Q_0, Q_1, Q_2, Q_3) with the state assignment:

$$S_0: Q_0 Q_1 Q_2 Q_3 = 1000, \quad S_1: 0100, \quad S_2: 0010, \quad S_3: 0001$$

State Assignments
 
$$Q_3^+ = X_1 (Q_0 Q_1' Q_2' Q_3') + X_2 (Q_0' Q_1 Q_2' Q_3') + X_3 (Q_0' Q_1' Q_2 Q_3') + X_4 (Q_0' Q_1' Q_2' Q_3)$$



$Q_0 = 1$ implies $Q_1 = Q_2 = Q_3 = 0$,
the $Q_1' Q_2' Q_3'$ term is redundant

$$Q_3^+ = X_1 Q_0 + X_2 Q_1 + X_3 Q_2 + X_4 Q_3$$

Each term in the next-state equation contains exactly one state variable.