

EEE104 – Digital Electronics (I)

Lecture 11

Dr. Ming Xu

Dept of Electrical & Electronic Engineering
XJTLU

In This Session

- Functions of Combinational Logic Gates
 - Adders
 - Comparators
 - Decoders

Basic Adders – The Half-Adder



The half-adder does not add an input carry.

A	B	C_{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Σ = sum

C_{out} = output carry


A and B = input variables (operands)

  

- The sum is 1 only when the inputs are different — an XOR operation.
- The output carry is 1 only when both the inputs are 1 — an AND operation.

Basic Adders – The Full-Adder

A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$\Sigma = (A \oplus B) \oplus C_{in}$$


$$\begin{aligned}
 C_{out} &= ABC_{in} + AB\bar{C}_{in} + A\bar{B}C_{in} + \bar{A}BC_{in} \\
 &= (ABC_{in} + AB\bar{C}_{in}) + (A\bar{B}C_{in} + \bar{A}BC_{in}) + (ABC_{in} + \bar{A}BC_{in}) \\
 &= AB + AC_{in} + BC_{in}
 \end{aligned}$$

Comparators — Equality Comparators


1. An XOR gate is a 1-bit comparator.



2. 2-bit comparators

 


Comparators — Inequality Comparators

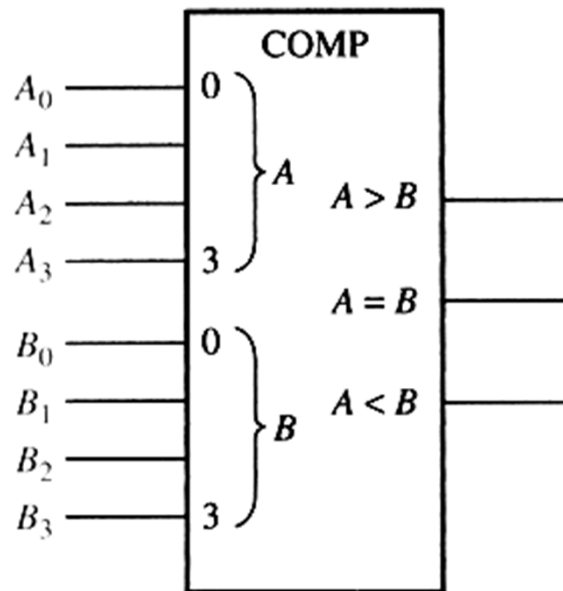

1. Check the highest-order bit first.
2. If $A_3 = 1$ and $B_3 = 0$, $A > B$.
3. If $A_3 = 0$ and $B_3 = 1$, $A < B$.
4. If $A_3 = B_3$, examine the next lower bit position.


MSI magnitude comparator: 74HC85, which has three cascade inputs $A < B$, $A = B$, $A > B$.

Comparators — Inequality Comparators

 

Decoders

 A decoder is used to detect a specified combination of input bits (code), e.g. to determine when the inputs are 1001.




- The output is 1 only when $A_3 A_2 A_1 A_0 = 1001$.
- Implemented with an AND (NAND) gate and inverters for an active-HIGH (LOW) output.

Decoders – The 4-Bit Decoder

The truth table (with **active-LOW** output)


BINARY INPUTS				DECODING FUNCTION	OUTPUTS															
A ₃	A ₂	A ₁	A ₀		0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	0	0	$\overline{A_3}\overline{A_2}\overline{A_1}\overline{A_0}$	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0	0	0	1	$\overline{A_3}\overline{A_2}\overline{A_1}A_0$	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0	0	1	0	$\overline{A_3}\overline{A_2}A_1\overline{A_0}$	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1
0	0	1	1	$\overline{A_3}\overline{A_2}A_1A_0$	1	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1
0	1	0	0	$\overline{A_3}A_2\overline{A_1}\overline{A_0}$	1	1	1	1	0	1	1	1	1	1	1	1	1	1	1	1
0	1	0	1	$\overline{A_3}A_2\overline{A_1}A_0$	1	1	1	1	1	0	1	1	1	1	1	1	1	1	1	1
0	1	1	0	$\overline{A_3}A_2A_1\overline{A_0}$	1	1	1	1	1	1	0	1	1	1	1	1	1	1	1	1
0	1	1	1	$\overline{A_3}A_2A_1A_0$	1	1	1	1	1	1	1	0	1	1	1	1	1	1	1	1
1	0	0	0	$A_3\overline{A_2}\overline{A_1}\overline{A_0}$	1	1	1	1	1	1	1	1	0	1	1	1	1	1	1	1
1	0	0	1	$A_3\overline{A_2}\overline{A_1}A_0$	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1	1
1	0	1	0	$A_3\overline{A_2}A_1\overline{A_0}$	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1
1	0	1	1	$A_3\overline{A_2}A_1A_0$	1	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1
1	1	0	0	$A_3A_2\overline{A_1}\overline{A_0}$	1	1	1	1	1	1	1	1	1	1	1	1	0	1	1	1
1	1	0	1	$A_3A_2\overline{A_1}A_0$	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1	1
1	1	1	0	$A_3A_2A_1\overline{A_0}$	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1
1	1	1	1	$A_3A_2A_1A_0$	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0

Decoders – The 4-Bit decoder

 

- The 4-bit decoder is usually called a *4-line-to-16-line decoder*.
- The 74HC154 is an MSI decoder.
- Both chip select inputs must be LOW to enable the device, otherwise all the outputs are HIGH.

Decoders – The 4-Bit decoder

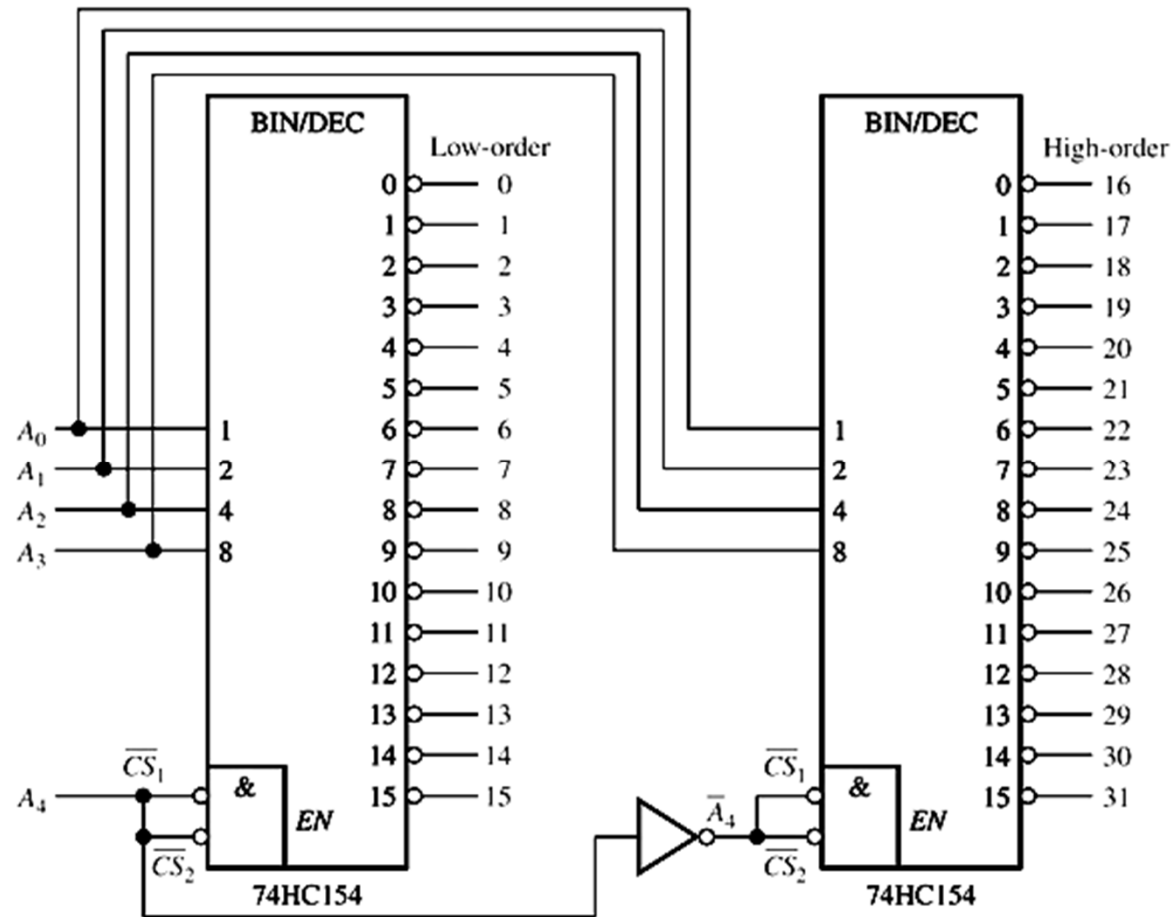



The chip select inputs may be used to expand the decoder to higher orders.

E.g. to decode a 5-bit number.

Decoders — BCD-to-7-Segment Decoders

LED Displays

  - A 7-segment LED display consists of light-emitting diodes (LED).
- For common-cathode displays, the LED is turned on when a HIGH is applied.




(a) Common-anode

(b) Common-cathode

Decoders — BCD-to-7-Segment Decoders

LED Displays

 

DECIMAL DIGIT	INPUTS				SEGMENT OUTPUTS						
	<i>D</i>	<i>C</i>	<i>B</i>	<i>A</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
10	1	0	1	0	X	X	X	X	X	X	X
11	1	0	1	1	X	X	X	X	X	X	X
12	1	1	0	0	X	X	X	X	X	X	X
13	1	1	0	1	X	X	X	X	X	X	X
14	1	1	1	0	X	X	X	X	X	X	X
15	1	1	1	1	X	X	X	X	X	X	X


Decoders — BCD-to-7-Segment Decoders

Karnaugh map to simplify the segment-a logic.

INPUTS				
D	C	B	A	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Standard SOP expression:

 
$$\overline{D}\overline{C}\overline{B}\overline{A} + \overline{D}\overline{C}\overline{B}A + \overline{D}\overline{C}B\overline{A} + \overline{D}\overline{C}BA + \overline{D}C\overline{B}\overline{A} + \overline{D}C\overline{B}A + D\overline{C}\overline{B}\overline{A} + D\overline{C}\overline{B}A$$



Minimum SOP expression: $D + B + CA + \overline{C}\overline{A}$

Decoders — BCD-to-7-Segment Decoders

MSI Decoder/Driver — 74LS47

 

- LT is for lamp test.
- RBI and RBO are for zero suppression.