

# Electronic Circuits and Systems (EEE211)

## Course Work: Assignment–1

**Deadline: 09-October-2024, 17:00 hours @ LMO**

- 1) Calculate the base, collector, and emitter currents and the C-E voltage for a common-emitter circuit shown in Figure. 1. The circuit parameters are:  $V_{BB} = 2\text{ V}$ ,  $V_{CC} = 3.3\text{ V}$ ,  $R_C = 3.2\text{ k}\Omega$ , and  $R_B = 430\text{ k}\Omega$ . The transistor parameters are  $\beta = 150$  and  $V_{BE} = 0.7\text{ V}$ . **[10 Marks]**

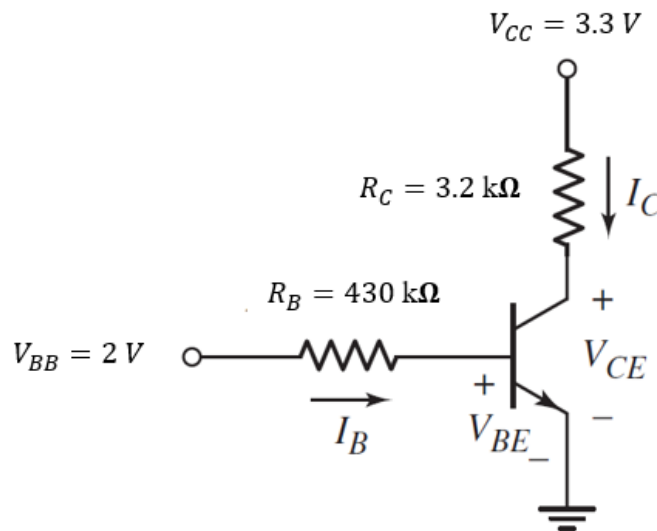


Figure. 1

- 2) Calculate the characteristics ( $I_C$ ,  $V_{CE}$ ) of a circuit including base and emitter currents, which consists of an emitter resistor shown in Figure. 2. The circuit parameters are annotated in the figure and the transistor parameters are:  $\beta = 80$  and  $V_{BE(on)} = 0.7\text{ V}$ . **[13 Marks]**

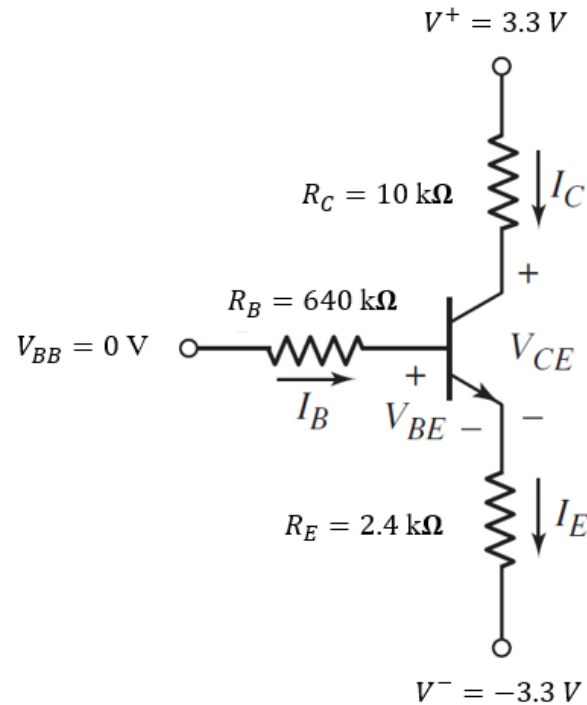


Figure. 2

- 3) For the circuit shown in Figure. 3, assume the circuit parameters are:  $V_{CC} = 5\text{ V}$ ,  $V_{BB} = 1.025\text{ V}$ ,  $R_B = 100\text{ k}\Omega$ , and  $R_C = 6\text{ k}\Omega$ . Consider the transistor parameters as  $\beta = 150$ ,  $V_{BE(on)} = 0.7\text{ V}$ , and  $V_A = 150\text{ V}$ . (a) Calculate the Q-point values ( $I_{CQ}$ ,  $V_{CEQ}$ ) using DC analysis, (b) Determine the small-signal hybrid- $\pi$  parameters ( $r_\pi$ ,  $g_m$ ,  $r_o$ ), (c) Find the small-signal voltage gain  $A_v = V_o/V_s$ . [22 Marks]

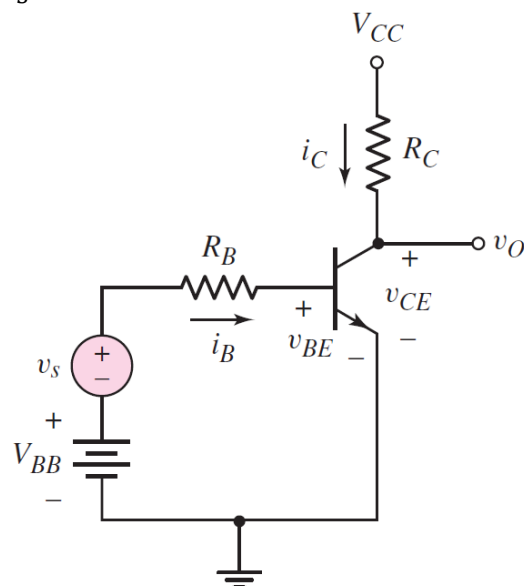


Figure. 3

- 4) For the circuit shown in Figure. 4, consider  $R_E = 0.6 \text{ k}\Omega$ ,  $R_C = 5.6 \text{ k}\Omega$ ,  $\beta = 120$ ,  $V_{BE(on)} = 0.7 \text{ V}$ ,  $R_1 = 250 \text{ k}\Omega$ , and  $R_2 = 75 \text{ k}\Omega$ . (a) Calculate the Q-point values ( $I_{CQ}$ ,  $V_{CEQ}$ ) using DC analysis, (b) Determine the small-signal hybrid- $\pi$  parameters ( $r_\pi$ ,  $g_m$ ,  $r_o$ ), (c) Find the small-signal voltage gain  $A_v = V_o/V_s$ , assuming  $V_A = \infty$ , (d) Determine the input resistance looking into the base of the transistor. **[25 Marks]**

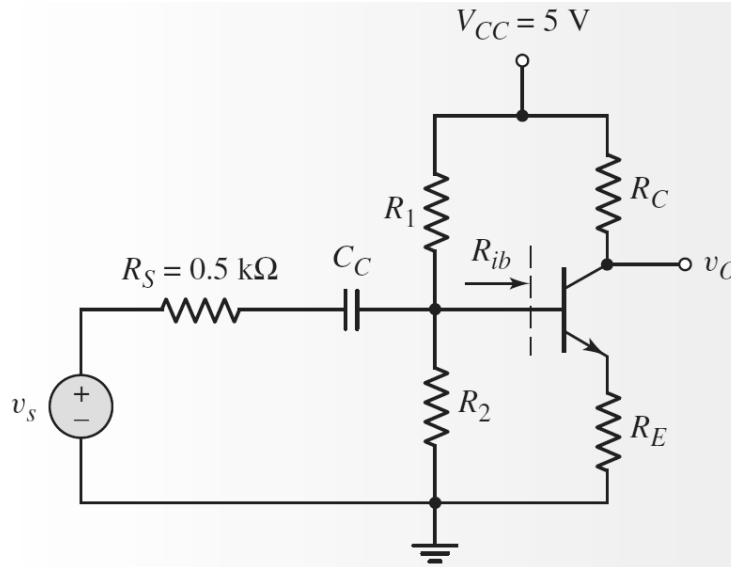


Figure. 4

- 5) For the circuit shown in Figure. 5, consider the circuit parameters as  $V_{CC} = V_{EE} = 3.3 \text{ V}$ ,  $R_S = 500 \text{ k}\Omega$ ,  $R_L = 6 \text{ k}\Omega$ ,  $R_B = 100 \text{ k}\Omega$ ,  $R_E = 12 \text{ k}\Omega$ , and  $R_C = 12 \text{ k}\Omega$ . The transistor parameters are:  $\beta = 120$ ,  $V_{BE(on)} = 0.7 \text{ V}$ , and  $V_A = \infty$ . (a) Calculate the Q-point values ( $I_{CQ}$ ,  $V_{CEQ}$ ) using DC analysis, (b) Determine the small-signal hybrid- $\pi$  parameters ( $r_\pi$ ,  $g_m$ ,  $r_o$ ), (c) Find the small-signal voltage gain  $A_v = v_o/v_s$ , (d) Find the small-signal current gain  $A_i = i_o/i_i$ , (e) Determine the input resistance  $R_i$  and output resistance  $R_o$ . **[30 Marks]**

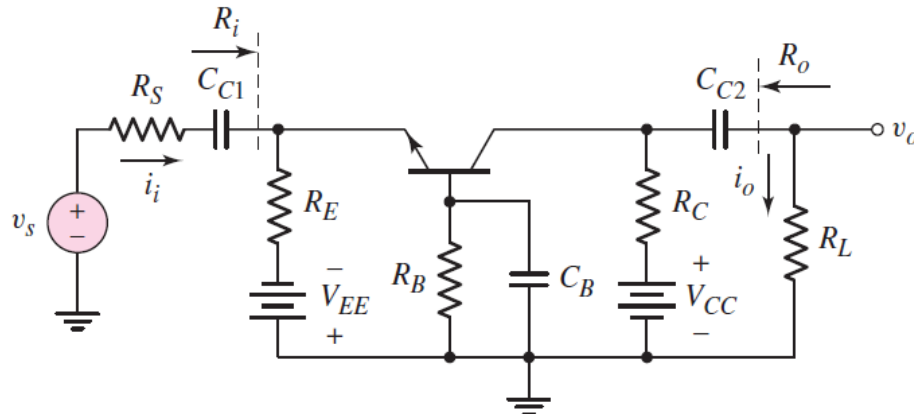


Figure. 5