

# EEE104 – Digital Electronics (I)

## Lecture 16

Dr. Ming Xu


Dept of Electrical & Electronic Engineering

XJTLU



# In This Session

- Synchronous Counters


# 2-Bit Synchronous Binary Counters

 

  
- All the flip-flops are clocked by CLK.
- J and K of FF1 are connected to  $Q_0$  output of FF0.




# 2-Bit Synchronous Binary Counters

 



(c)

 

(d)

 



# 3-Bit Synchronous Binary Counters

 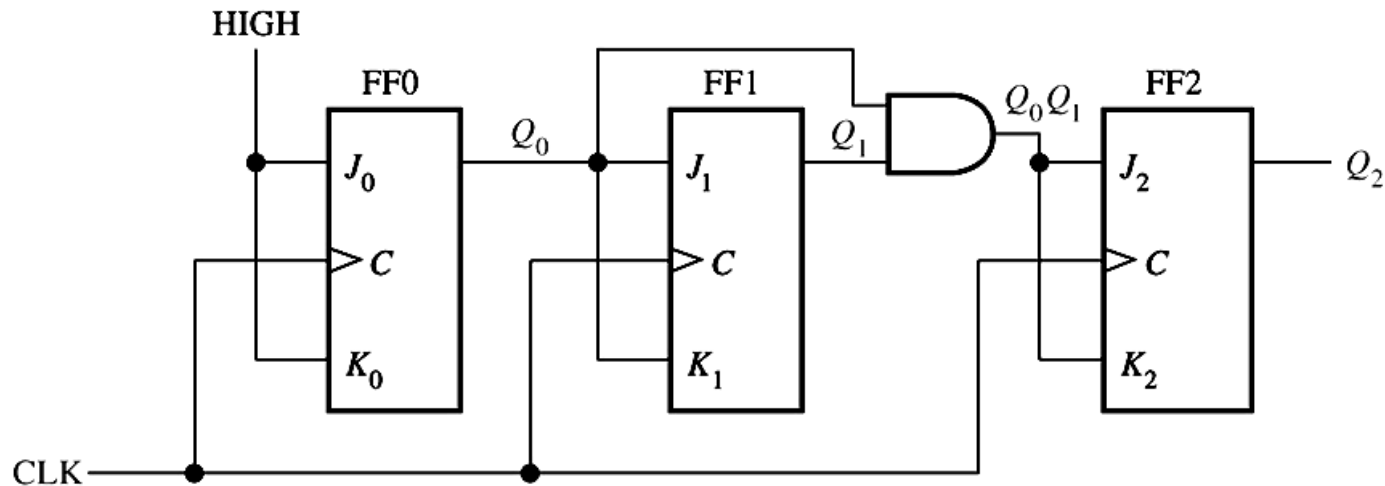

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

$Q_2$  is toggled at states 011 and 111. So  $J_2 = K_2 = Q_0Q_1$

# 4-Bit Synchronous Binary Counters

 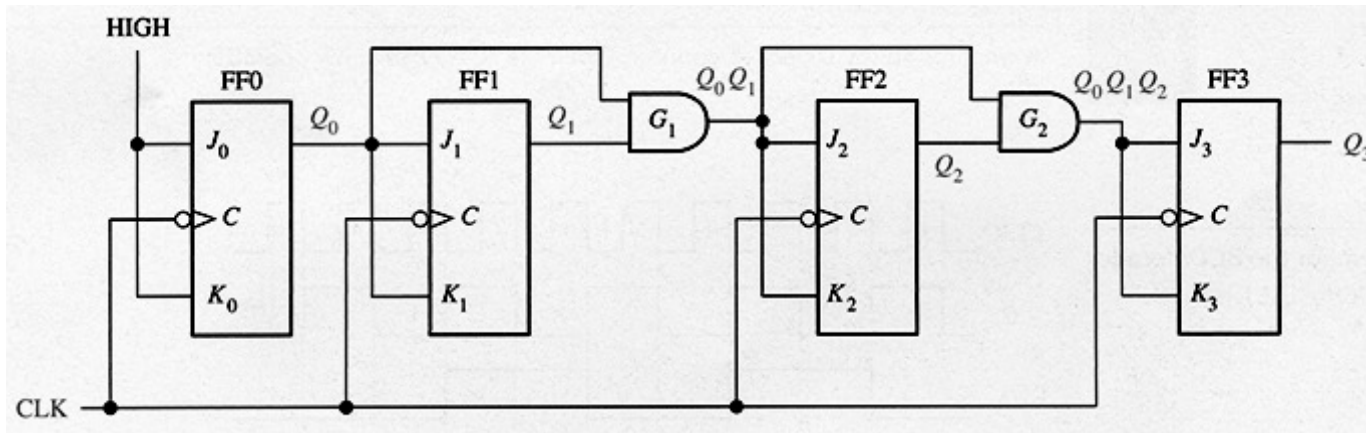

Q3 Q2 Q1 Q0

Q3	Q2	Q1	Q0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Q<sub>3</sub> is toggled at states 0111 and 1111. So

$$J_3 = K_3 = Q_0 Q_1 Q_2$$

# 4-Bit Synchronous Decade Counters

Q3	Q2	Q1	Q0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

- $Q_0$  is always toggled.

- $Q_1$  is toggled at states 0001, 0011, 0101, 0111.

- $Q_2$  is toggled at states 0011, 0111.

- $Q_3$  is toggled at states 0111, 1001.



$$J_0 = K_0 = 1$$

$$J_1 = K_1 = Q_0 \bar{Q}_3$$

$$J_2 = K_2 = Q_0 Q_1$$

$$J_3 = K_3 = Q_0 Q_1 Q_2 + Q_0 Q_3$$


# 4-Bit Synchronous Decade Counters

 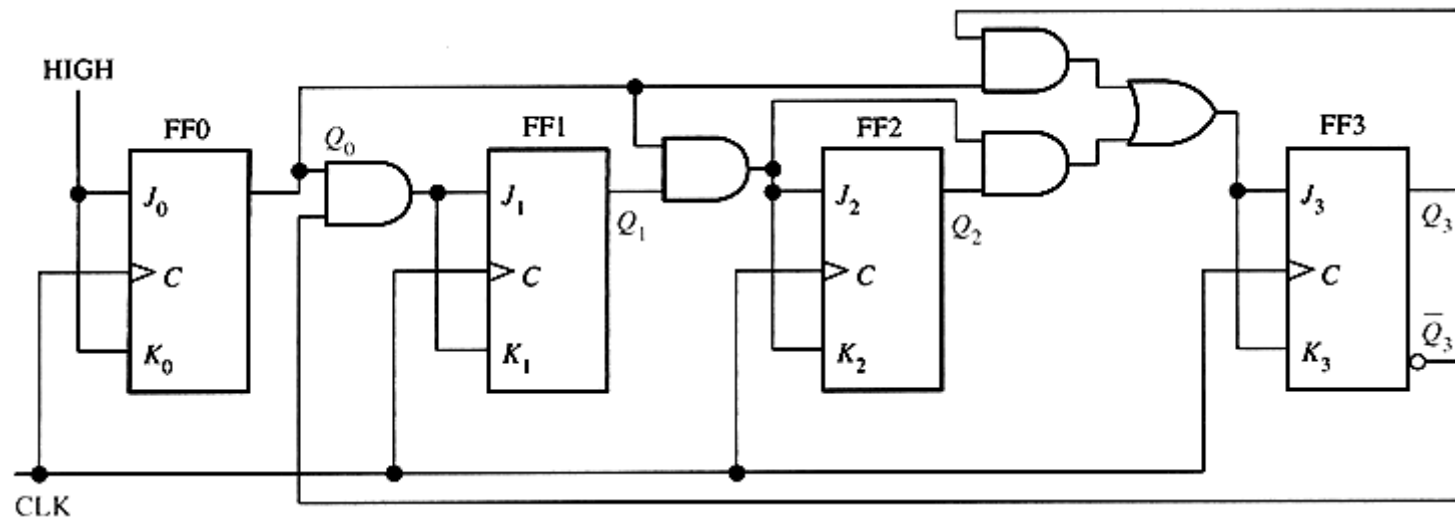



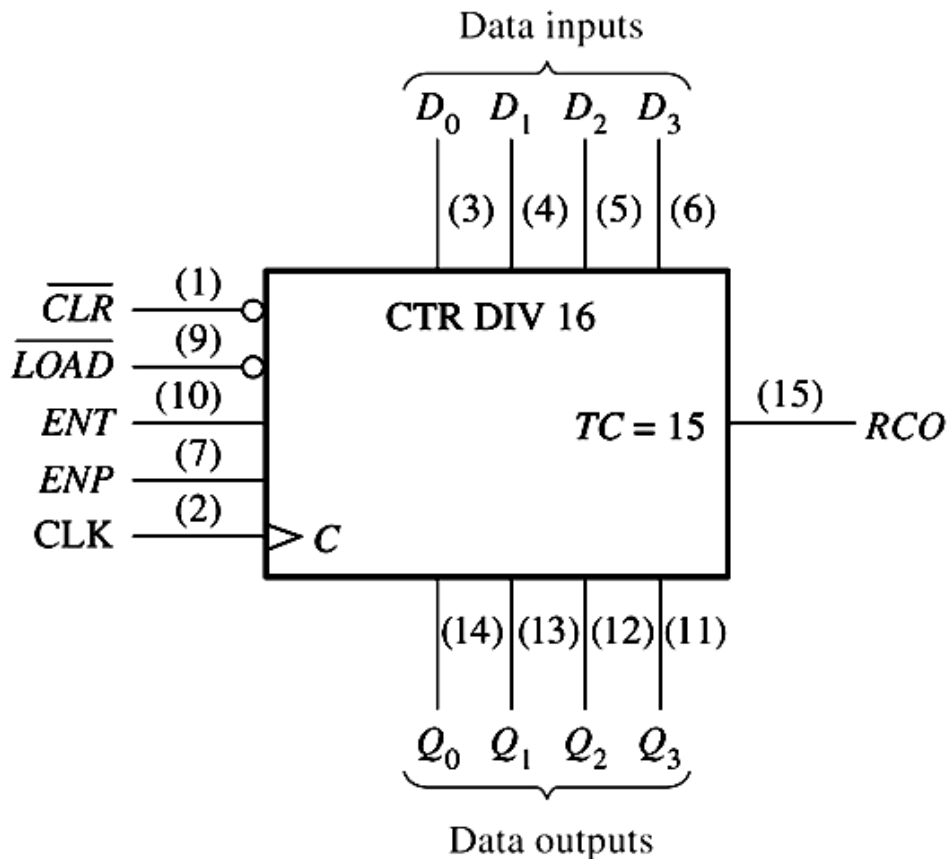
# IC Synchronous Counters

74HC163 — a 4-bit synchronous binary counter




- $\overline{CLR}$ : synchronous clear
- $\overline{LOAD}$ : synchronous preset
- $ENT, ENP$ : enable
- $RCO$ : ripple clock output, which goes to 1 at count 15

# IC Synchronous Counters

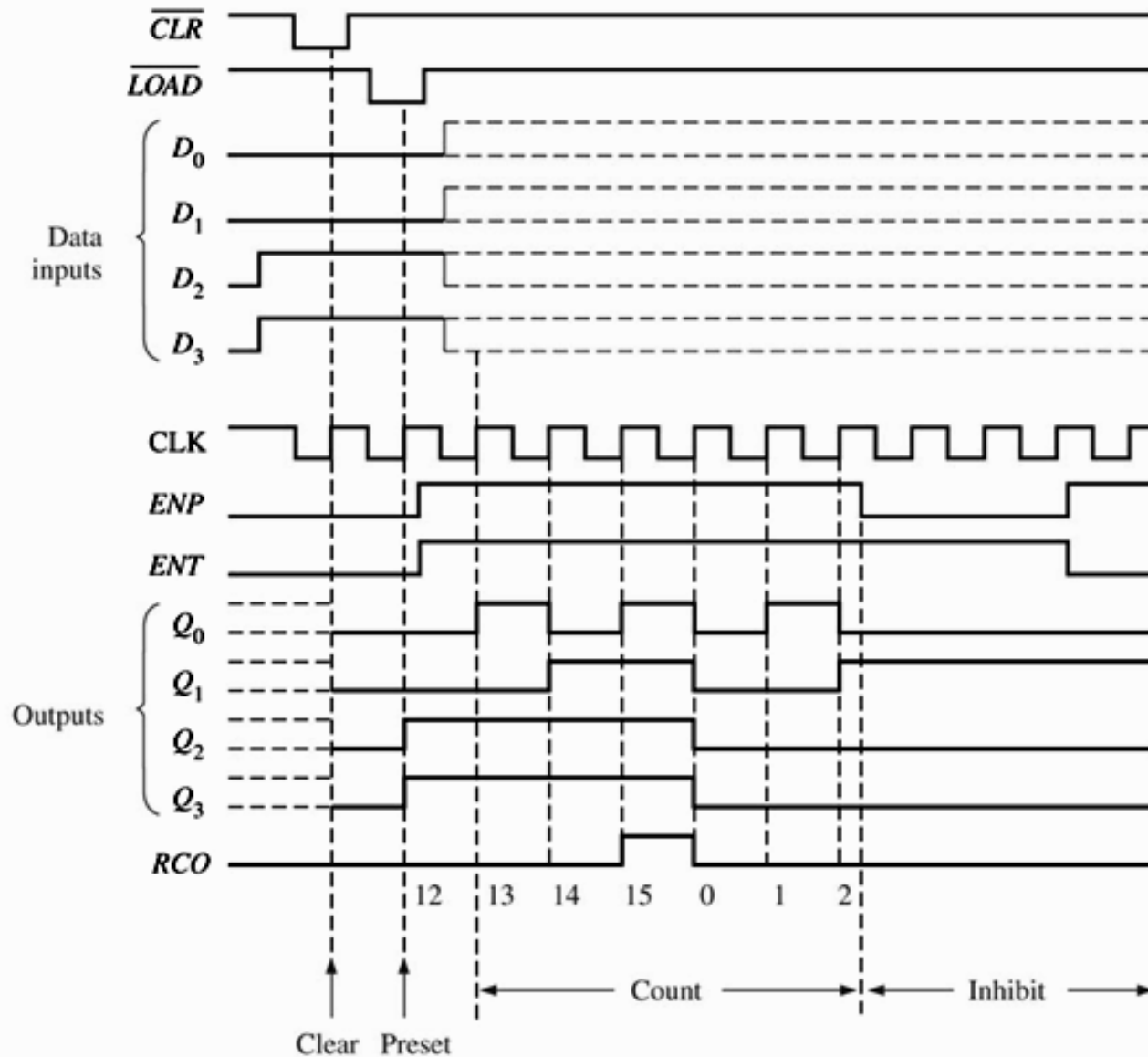

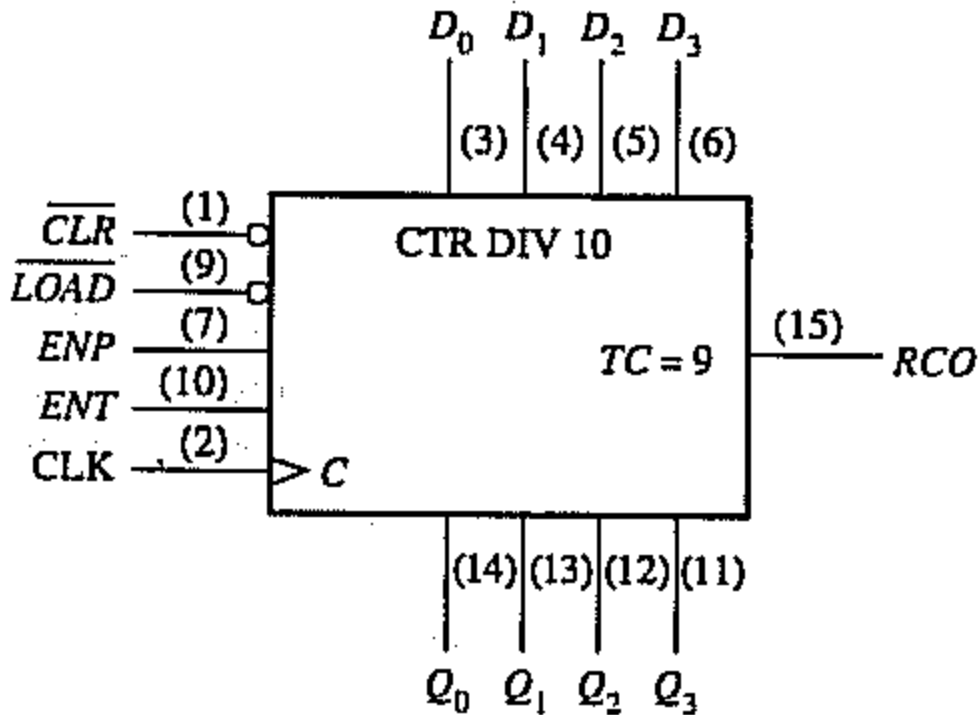
# IC Synchronous Counters

74HC160 — a 4-bit synchronous decade counter





- $\overline{CLR}$ : asynchronous clear
- $\overline{LOAD}$ : synchronous preset
- $ENT$ ,  $ENP$ : enable
- $RCO$ : ripple clock output, which goes to 1 at count 9
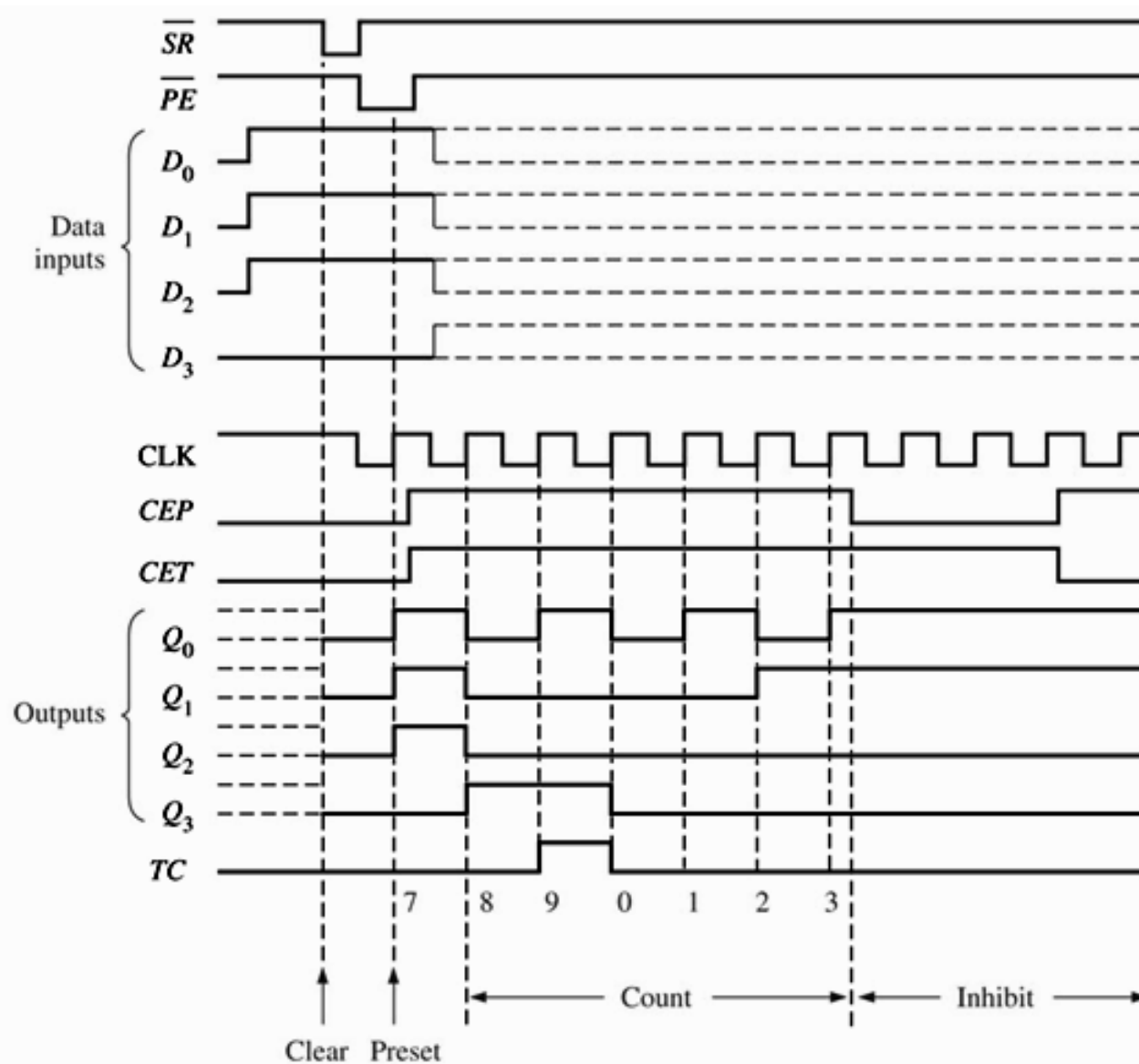
# IC Synchronous Counters



# Up/Down Synchronous Counters


An **up/down counter** is one that is capable of progressing in either direction through a sequence.

CLOCK PULSE	UP	$Q_2$	$Q_1$	$Q_0$	DOWN
0		0	0	0	
1		0	0	1	
2		0	1	0	
3		0	1	1	
4		1	0	0	
5		1	0	1	
6		1	1	0	
7		1	1	1	

In count-down mode:

- $Q_0$  is always toggled.
- $Q_1$  is toggled at states 110, 100, 010, 000. So  $J_1 = K_1 = \neg Q_0$ .
- $Q_2$  is toggled at states 100, 000. So  $J_2 = K_2 = \neg Q_0 \neg Q_1$

# Up/Down Synchronous Counters

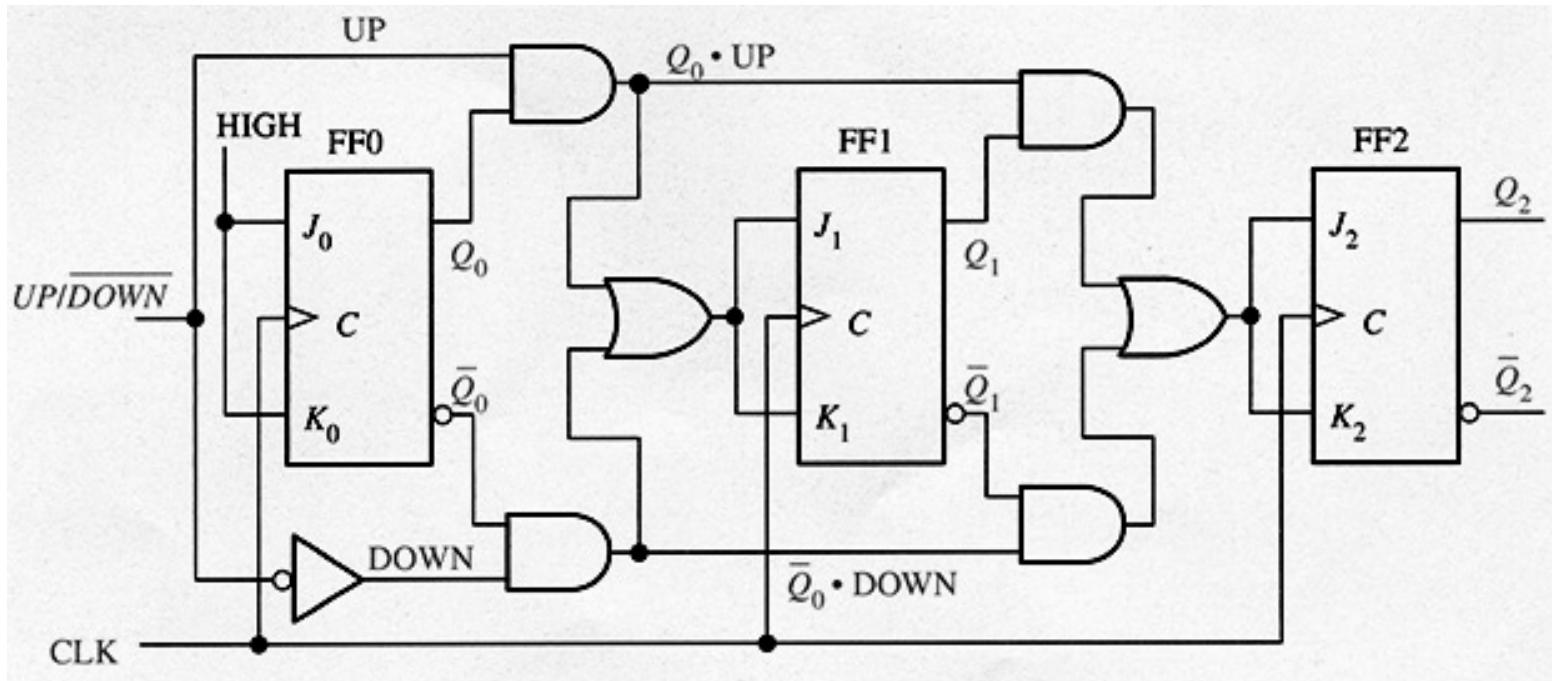


$$J_0 = K_0 = 1$$


$$J_1 = K_1 = (Q_0 \cdot UP) + (\overline{Q_0} \cdot \overline{DOWN})$$

$$J_2 = K_2 = (Q_0 \cdot Q_1 \cdot UP) + (\overline{Q_0} \cdot \overline{Q_1} \cdot \overline{DOWN})$$

# Up/Down Synchronous Counters

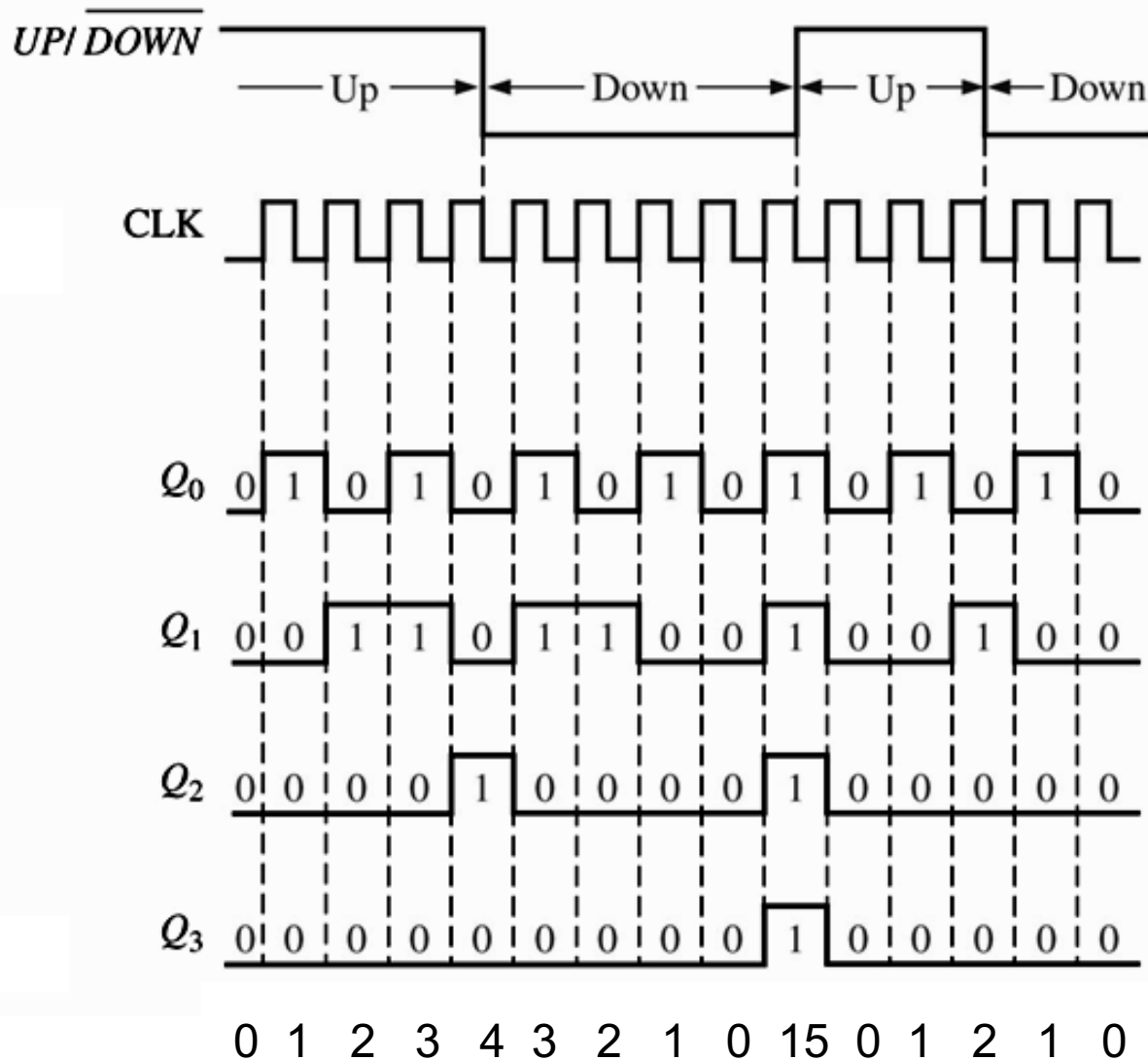

# An IC Up/Down Decade Counter

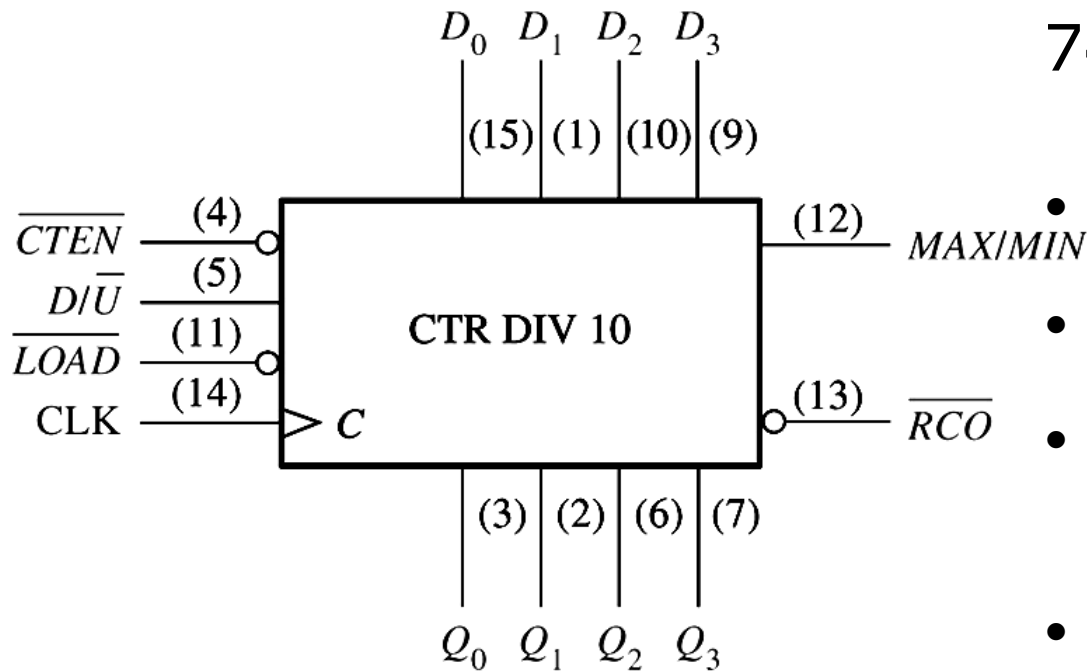

## 74LS190

- $CTEN$ : enable
- $D/U$ : down/up
- $LOAD$ : synchronous preset
- $MAX/MIN$ : HIGH when 1001 or 0000 is reached.
- $RCO$ : ripple clock output, which is 0 at count 9