

Electronic Circuits and Systems (EEE211)

Course Work: Assignment–3

Deadline: 01-December-2024, 23:59 @ LMO

- 1) Consider the circuit shown in Figure 1. (a) Determine the ideal output voltage v_o if $v_I = -0.40$ V. (b) Assume the op-amp is ideal except it has a finite open-loop gain. Determine the actual output voltage if the open-loop gain of the op-amp is $A_{od} = 5 \times 10^3$. [20 Marks]

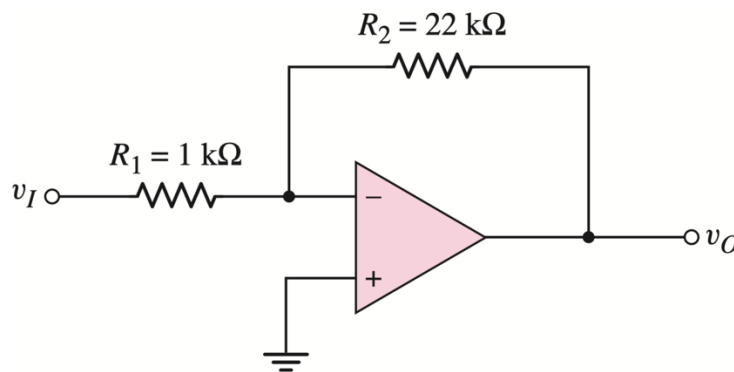


Figure 1

- 2) The op-amp in the circuit shown in Figure 2 is ideal except it has a finite open-loop gain. (a) If $A_{od} = 10^4$ and $v_o = -2$ V, determine v_I . (b) If $v_I = 2$ V and $v_o = 1$ V, determine A_{od} . [20 Marks]

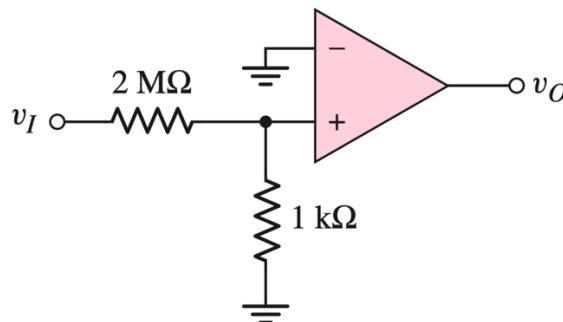


Figure 2

- 3) The parameters of the two inverting op-amp circuits connected in cascade shown in Figure 3 are $R_1 = 10 \text{ k}\Omega$, $R_2 = 80 \text{ k}\Omega$, $R_3 = 20 \text{ k}\Omega$, and $R_4 = 100 \text{ k}\Omega$. For $v_I = -0.15 \text{ V}$, determine v_{O1} , v_O , i_1 , i_2 , i_3 , and i_4 . [20 Marks]

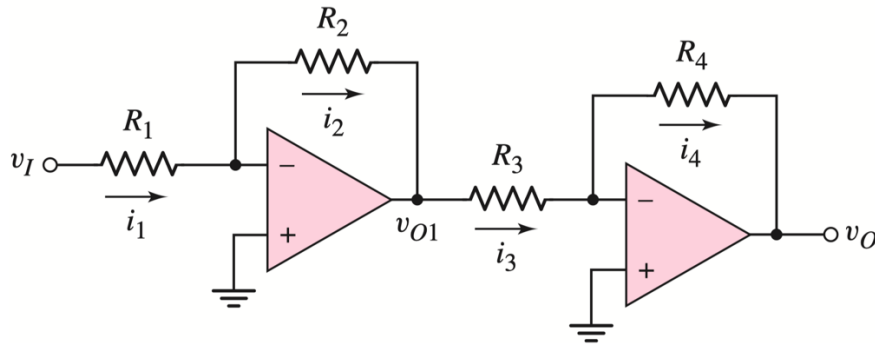


Figure 3

- 4) (a) If an op-amp has a slew-rate of $5 \text{ V}/\mu\text{s}$, find the upper corner frequency for a pulse output voltage of 5 V , 1.5 V , and 0.4 V . (b) An op-amp with a slew rate of $8 \text{ V}/\mu\text{s}$ is driven by a 250 kHz sine wave. What is the maximum output amplitude at which slew-rate limiting is reached? [20 Marks]
- 5) For the circuit shown in Figure 4, the input bias current is $I_B = 0.8 \mu\text{A}$ and the input offset current is $I_{OS} = 0.2 \mu\text{A}$. Determine the output voltage due to the effect of the input offset current. [20 Marks]

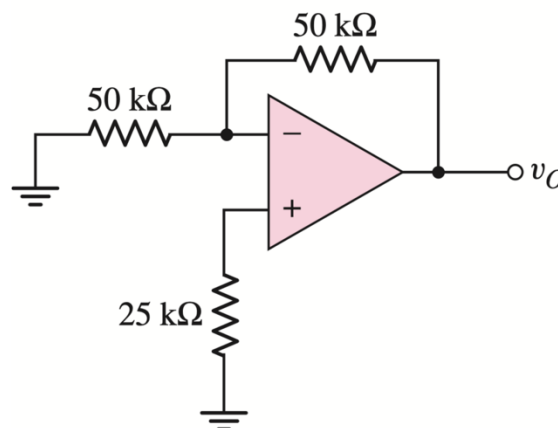


Figure 4