

Power Electronics and Electromechanics (EEE213)


Assignment Solutions with Marking Scheme

Dr. Suneel Kommuri

1)

Solution:

(a) Waveforms

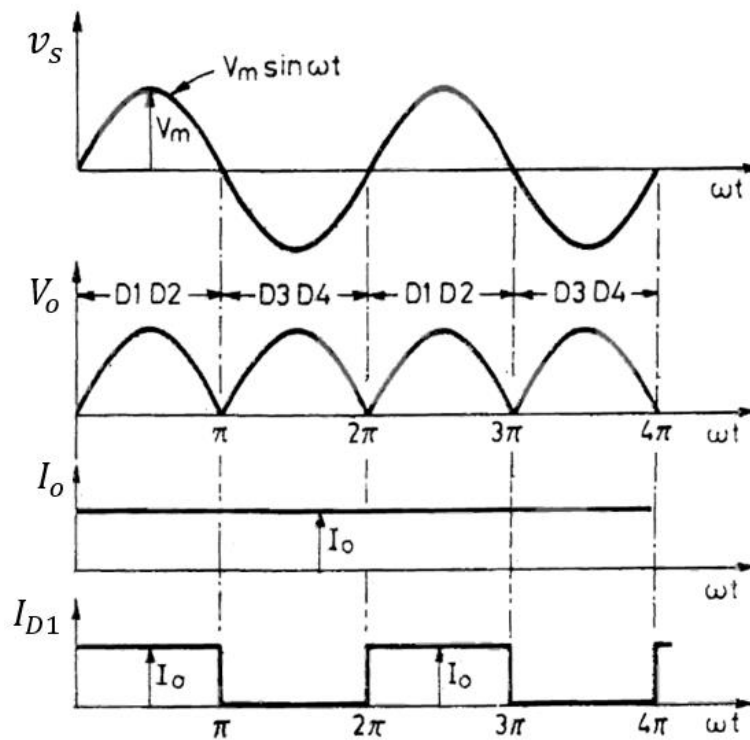

(b) Average output voltage, $V_o = \frac{2V_m}{\pi} = \frac{2 \times \sqrt{2} \times 220}{\pi} = 198.165 \text{ V}$

(c) Average load current, $I_o = \frac{V_o}{R} = \frac{198.165}{20} = 9.9 \text{ A}$

(d) Average diode current, $I_{d,a} = \frac{1}{2\pi} \int_0^\pi I_o d(\omega t) = \frac{I_o \times \pi}{2\pi} = \frac{9.9}{2} = 4.95 \text{ A}$

(e) RMS value of diode current, $I_{DRMS} = \sqrt{\frac{I_o^2 \times \pi}{2\pi}} = \frac{I_o}{\sqrt{2}} = \frac{9.9}{\sqrt{2}} = 7.0 \text{ A}$

(f) DC output power, $P_{dc} = V_o \times I_o = 198.1 \times 9.9 = 1961.83 \text{ W}$

2)

Solution:

Given: $V = 220 \text{ V}$ $R = 10 \text{ } \Omega$ and $\alpha = 45^\circ = 0.785 \text{ rad}$

(a) The average output voltage is equal to

$$V_o = \frac{\sqrt{2}V}{2\pi} (1 + \cos\alpha) = \frac{\sqrt{2} \times 220}{2\pi} (1 + \cos 45) = 84.56 \text{ V}$$

(b) The rms value of output voltage is

$$V_{rms} = \frac{V}{\sqrt{2}} \left[\frac{1}{\pi} (\pi - \alpha + \frac{1}{2} \sin 2\alpha) \right]^{\frac{1}{2}} = 148.35 \text{ V}$$

(c) The form factor, $FF = \frac{V_{rms}}{V_o} = \frac{148.35}{84.56} = 1.754$

(d) The ripple factor, $RF = \sqrt{FF^2 - 1} = \sqrt{1.754^2 - 1} = 1.441$

(e) The dc output current, $I_o = \frac{V_o}{R} = \frac{84.56}{10} = 8.456 \text{ A}$

$$P_{dc} = V_{dc} I_{dc} = V_o \times I_o = 84.56 \times 8.456 \text{ Watt} = 715.039 \text{ W}$$

The rms output current, $I_{rms} = \frac{V_{rms}}{R} = \frac{148.35}{10} = 14.835 \text{ A}$

The ac output power, $P_{ac} = V_{rms} I_{rms} = 148.35 \times 14.835 = 2200.77 \text{ W}$

Rectification efficiency = $\frac{P_{dc}}{P_{ac}} \times 100\% = \frac{715.039}{2200.77} \times 100\% = 32.49\%$

(f) The volt ampere rating of transformer is


$$VA = V I_{rms} = 220 \times 14.835 \text{ VA} = 3263.7 \text{ VA}$$

Transformer utilization factor is

$$TUF = \frac{\text{Power delivered to load}}{\text{Input VA}} = \frac{P_{dc}}{VA} = \frac{715.039}{220 \times 14.835} = 0.219$$

(g) Peak inverse voltage, $PIV = \sqrt{2}V = \sqrt{2} \times 220V = 311.08 \text{ V}$

3)

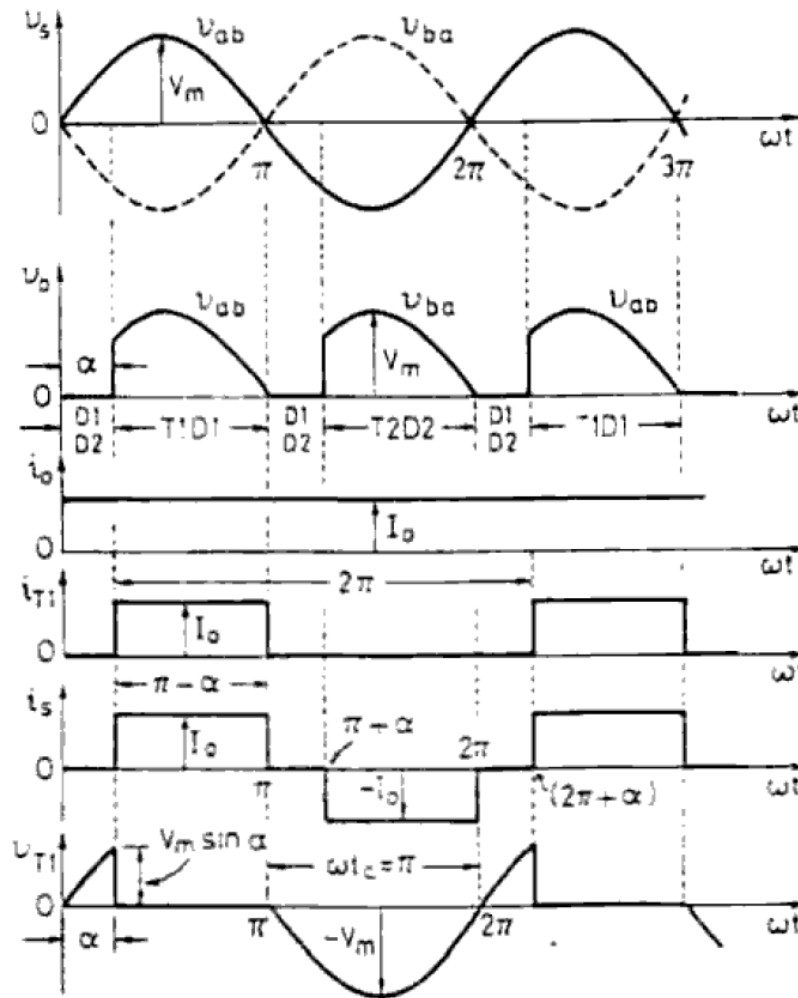Solution:


4)

Solution:

$$a) V_o = \frac{1}{2\pi/3} \int_{-(\frac{\pi}{3}-\alpha)}^{\frac{\pi}{3}+\alpha} V_m \cos \omega t \, d(\omega t) = \frac{3\sqrt{3}}{2\pi} V_m \cos \alpha.$$

$$b) V_{RMS} = \left[\frac{1}{2\pi/3} \int_{-(\frac{\pi}{3}-\alpha)}^{\frac{\pi}{3}+\alpha} V_m^2 \cos^2 \omega t \, d(\omega t) \right]^{1/2} = \sqrt{3} V_m \left[\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2}.$$

5)

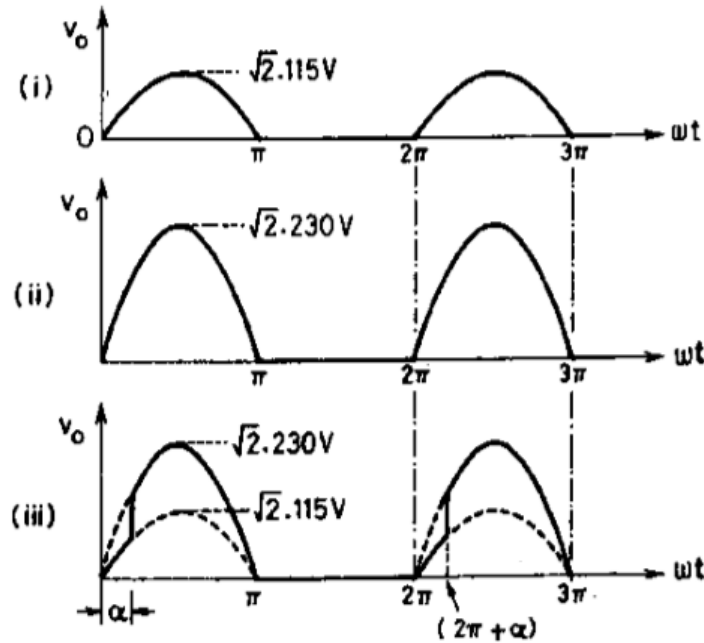Solution:

6)

Solution:

(a) Average output voltage, $V_{o(av)} = \frac{V_{in}}{1-D} \Rightarrow D = 1 - \frac{V_{in}}{V_{o(av)}} = 0.667$

(b) Time period, $T = T_{ON} + T_{OFF} = \frac{1}{f} = \frac{1}{1 \times 10^3} = 1 \text{ ms}$

$$D = \frac{T_{ON}}{T} \Rightarrow T_{ON} = DT = 0.667 \times 1 \times 10^{-3} = 0.667 \text{ ms}$$

$$T_{OFF} = T - T_{ON} = 1 \times 10^{-3} - 0.667 \times 10^{-3} = 0.333 \text{ ms}$$

c) Average output current, $I_{o(av)} = \frac{V_{o(av)}}{R} = \frac{60}{10} = 6 \text{ A}$

d) Average inductor current, $I_{L(av)} = I_{i(av)} = \frac{I_{o(av)}}{1-D} = \frac{6}{1-0.667} = 18 \text{ A}$

e) The maximum I_{max} and minimum I_{min} input currents

$$I_{max} = I_{i(av)} + \frac{1}{2} \Delta I_L = 18.667 \text{ A} \quad I_{min} = I_{i(av)} - \frac{1}{2} \Delta I_L = 17.33 \text{ A}$$

$$\Delta I_L = \frac{V_{i(av)}}{L} T_{ON} = \frac{20}{10 \times 10^{-3}} \times 0.667 \times 10^{-3} = 1.334 \text{ A}$$

7)

Solution:

- a) The rms value of fundamental component of output voltage is

$$V_{1(rms)} = \frac{1}{\sqrt{2}} \frac{4V_s}{\pi} = \frac{1}{\sqrt{2}} \frac{4 \times 200}{\pi} = 179.99 \text{ V}$$

- b) The rms value of output voltage,
- $V_{0(rms)} = V_s = 200 \text{ V}$

$$\text{The output power, } P_0 = \frac{V_o^2}{R} = 8000 \text{ W}$$

- c) The lowest order harmonics,
- $V_{3(rms)} = \frac{1}{\sqrt{2}} \frac{4V_s}{3\pi} = 59.99 \text{ V}$

$$\text{Harmonic factor, } HF_3 = \frac{V_{3(rms)}}{V_{1(rms)}} = 0.333$$

- d) Third harmonic distortion factor,
- $DF_3 = \frac{V_{3(rms)}}{V_1 \times n^2} = 0.037 = 3.7\%$

8)

Solution:

$$V_{o(av)} = E + I_a R_a = K_v \omega + I_a R_a \Rightarrow 220 = K_v \frac{2\pi \times 1000}{60} + 60 \times 0.1$$

$$\Rightarrow K_v = 2.044 \text{ Vs/rad}$$

- a) For rated motor torque, armature current = 60 A

$$V_{o(av)} = K_v \omega + I_a R_a \Rightarrow \frac{2\sqrt{2} \times 230}{\pi} \cos \alpha = 2.044 \frac{2\pi \times 600}{60} + 60 \times 0.1 = 134.4 \text{ V}$$

$$\text{Therefore, } \alpha = \cos^{-1} \left[\frac{134.4 \times \pi}{2\sqrt{2} \times 230} \right] = 49.51$$

- b) At -500 rpm

$$\frac{2\sqrt{2} \times 230}{\pi} \cos \alpha = 2.044 \frac{2\pi \times (-500)}{60} + 60 \times 0.1 = -101.02 \text{ V}$$

$$\text{Therefore, } \alpha = \cos^{-1} \left[\frac{-101.02 \times \pi}{2\sqrt{2} \times 230} \right] = 119.27$$

- c) At half-rated torque, motor armature current =
- $\frac{1}{2}$
- rated current =
- $\frac{1}{2} \times 60 = 30 \text{ A}$

$$\frac{2\sqrt{2} \times 230}{\pi} \cos 150 = 2.044 \times \omega + 30 \times 0.1 \Rightarrow \omega = -89.18 \text{ rad/sec}$$