

Lecture 12
of
EEE201

CMOS Digital Integrated Circuits

Department of Electrical & Electronic Engineering
Xi'an Jiaotong-Liverpool University (XJTLU)

Monday, 2nd December 2024

□ RAM & ROM

- memory architecture
- memory cells of SRAM & DRAM
- memory cell of EEPROM
- address decoder



Circuits for Storing Digital Data

(access time & storage density)

- ❑ To process **digital data**, **combinational logic circuits** are needed to perform logic functions (e.g. addition, multiplication, multiplexing).
- ❑ It is equally important to have electronic circuits to store **digital data** either temporarily or for a long time. Such digital circuits are **memory circuits**.
 - Short **access time** is expected in retrieving the *stored* digital data.
 - High **density** of **storage capacity** is always preferred whenever possible because of the ever increasing amounts of digital data (e.g. videos, images, music, etc.)



Xi'an Jiaotong-Liverpool University
西交利物浦大學

Digital Memory Circuits

(RAM & ROM)

- ❑ The silicon CMOS technology that is good for realisation of **combinational logic circuits** in general can also be used to make **memory circuits**.
 - The semiconductor fabrication however may be modified for optimal manufacturing of memory circuits.
- ❑ There are two basic types of **memory circuits** which can be implemented using CMOS transistors for storing digital data *electronically*.
 - **random access memory (RAM)** – volatile
 - **read-only memory (ROM)** – non-volatile
 - A **volatile memory** loses its stored data when power is removed.




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Semiconductor Memories

(memory types)

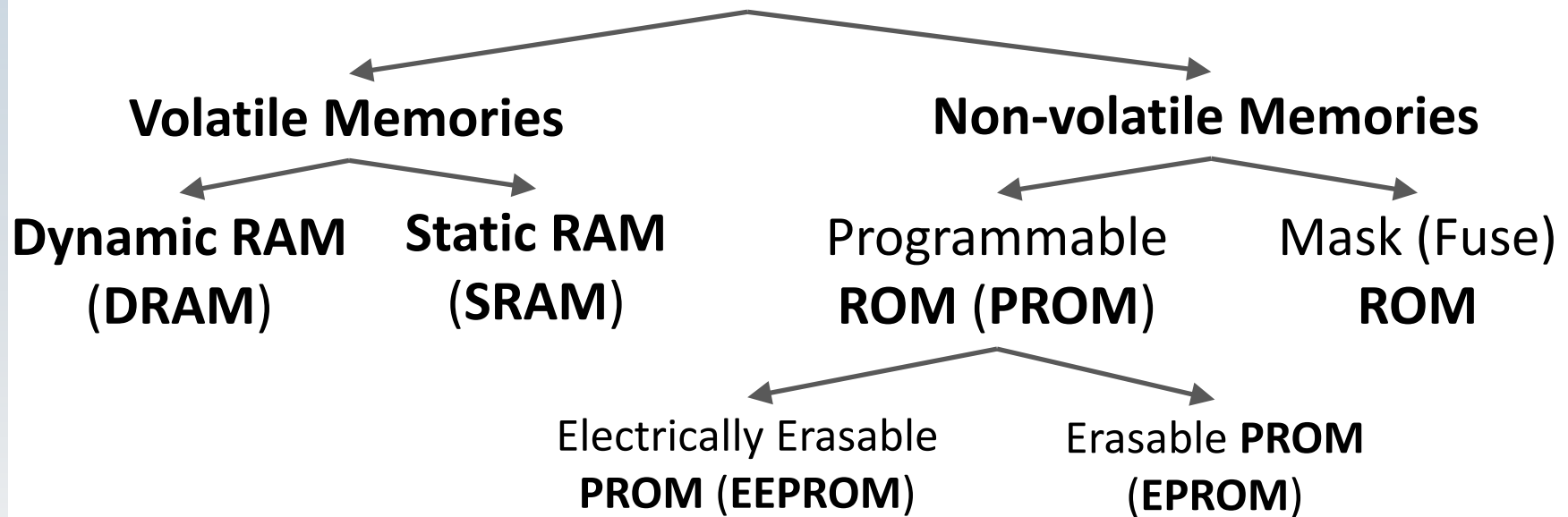- ❑ Semiconductor memories are predominantly used for storing digital data with its fast electronic retrieval and processing.




- Among **EEPROM**, there are **flash memory**, ferroelectric RAM, magnetoresistive RAM, resistive RAM, phase-change RAM



Xi'an Jiaotong-Liverpool University
西交利物浦大学

Memory Architecture

(array of storage cells)

 

- ❑ Both RAM and ROM share the same basic **memory architecture**.
 - It consists of an array of **storage cells** with 2^M columns and 2^N rows.
 - Each **storage cell** (or called **memory cell**) can store one **bit** of digital data “1” or “0”.

Storage Cell or Memory Cell


(varying from RAM to ROM)

- ❑ The **memory cell** varies from RAM to ROM.
- ❑ There are two types of RAM, namely **static RAM** (**SRAM**) and **dynamic RAM** (**DRAM**), and their **memory cells** are different.
 - The **SRAM** and **DRAM** have their trade-off in the **access time** and **memory density** (i.e. amounts of digital data stored per unit chip area). It is again performance and cost trade-off.
- ❑ Regardless the types of RAM or ROM, the **memory cell** uses typically the **voltage** or **charge** to store digital data.
 - **Information** must be *represented* by **physical states** when stored or processed.

Memory Cell of Dynamic RAM

(one transistor & one capacitor)

 - ❑ The **memory cell** of the **DRAM** typically consists of only two devices: a transistor and a capacitor.




- The **charge** on the capacitor is used to store one bit of digital data.
- Since the **charge** on the capacitor *decays* with a finite time constant (about a few millisecond), a ***periodic refresh*** is needed to restore the charge so that the DRAM does not lose the memory.
- Using only two devices in each memory cell, DRAM can be of very high memory density.


Memory Cell of Dynamic RAM

(DRAM cell structure)

 - ❑ In the **DRAM memory cell**, the transistor is typically an nMOSFET.



 From: D.A. Hodges *et al.*, *Analysis and Design of Digital Integrated Circuits: In Deep Submicron Technology*, 3rd edition, © 2003 McGraw Hill, USA.



- The capacitor can be a MOS capacitor, a deep-trench capacitor or a parallel-plate capacitor using the two layers of polysilicon.




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Memory Cell of Static RAM

(two inverters for bistable flip-flop)

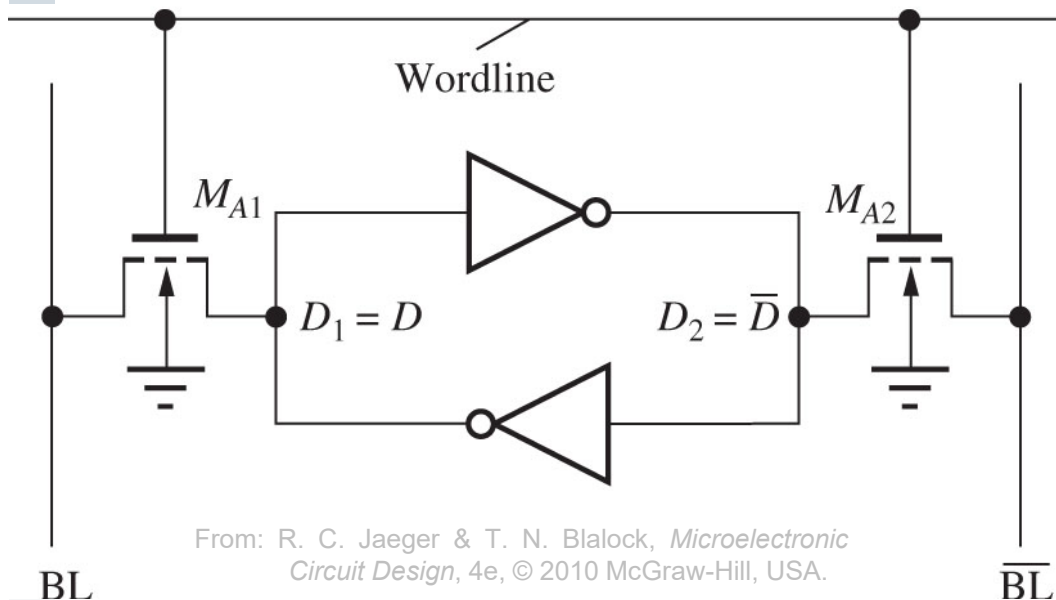- ❑ The **memory cell** of the **SRAM** consists of a basic bistable flip-flop circuit that needs only an applied DC voltage to retain its memory.
 - The bistable flip-flop circuit can be built by two **inverters**.




- Typically six transistors are used.
 - Compared with the DRAM, no refresh cycle is needed to retain the memory.
- ⇒ **static** RAM

Memory Cell of Static RAM


(cross-coupled inverter pair)

 - ❑ The basic electronic storage part in the SRAM cell consists of two **inverters** connected in a loop.



From: R. C. Jaeger & T. N. Blalock,
Microelectronic Circuit Design,
4e, © 2010 McGraw-Hill, USA.

- The output of the second inverter is fed back to the input of the first inverter.
- It forms a logically stable configuration, having two stable states. It is therefore called a **bistable circuit**.
- The alternate representation in the form of a pair of **cross-coupled** inverters is often called a **latch**.
- The inverter **voltage transfer characteristics** can be used to study the circuit behaviour.

 


Xi'an Jiaotong-Liverpool University
西交利物浦大學

Memory Cell of Static RAM

(six transistor implementation)

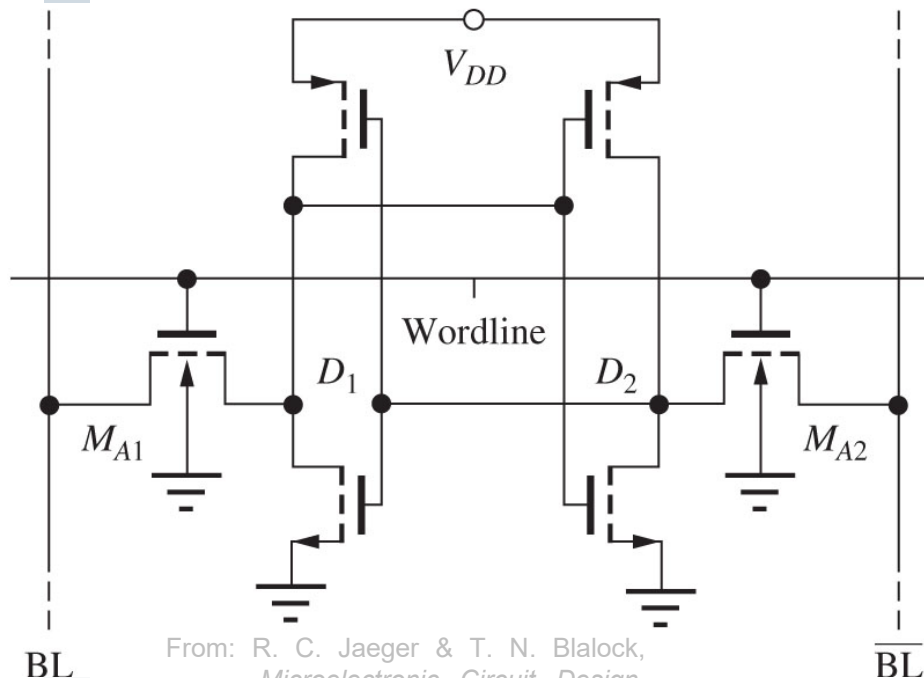- ❑ Two additional transistors are added to the two **bistable circuit** (i.e. two inverters in a loop) to isolate it from other memory cells and to provide an electrical path to read and write data to the cell.




- A CMOS logic inverter is formed by one *p*-channel and one *n*-channel MOSFETs.
- Such an implementation is called a *six-transistor* (6T) SRAM cell.

From: R. C. Jaeger & T. N. Blalock,
Microelectronic Circuit Design,
4e, © 2010 McGraw-Hill, USA.

Memory Cell of Static RAM

(layout of 6T SRAM cell)

 

- The **6T SRAM cell** can be implemented with the IC layout as shown here.
- Note that the MOS transistor sizes are not optimised here.


➤ Can you recognise the six transistors and determine their rough sizes?



Xi'an Jiaotong-Liverpool University
西交利物浦大學

Memory Cell of Static RAM

(array of SRAM cells)

 

- ❑ The 6T SRAM cell layout are duplicated in an array of 2^M columns and 2^N rows for storing 2^{M+N} bits of digital data.
- ❑ The IC layout shown here is a 16-bit SRAM.


From: S.-M. Kang & Y. Leblebici, *CMOS Digital Integrated Circuits: Analysis & Design*, 3rd edition, © 2003 McGraw-Hill, USA.



Memory Cell of Static RAM

(sense amplifier)

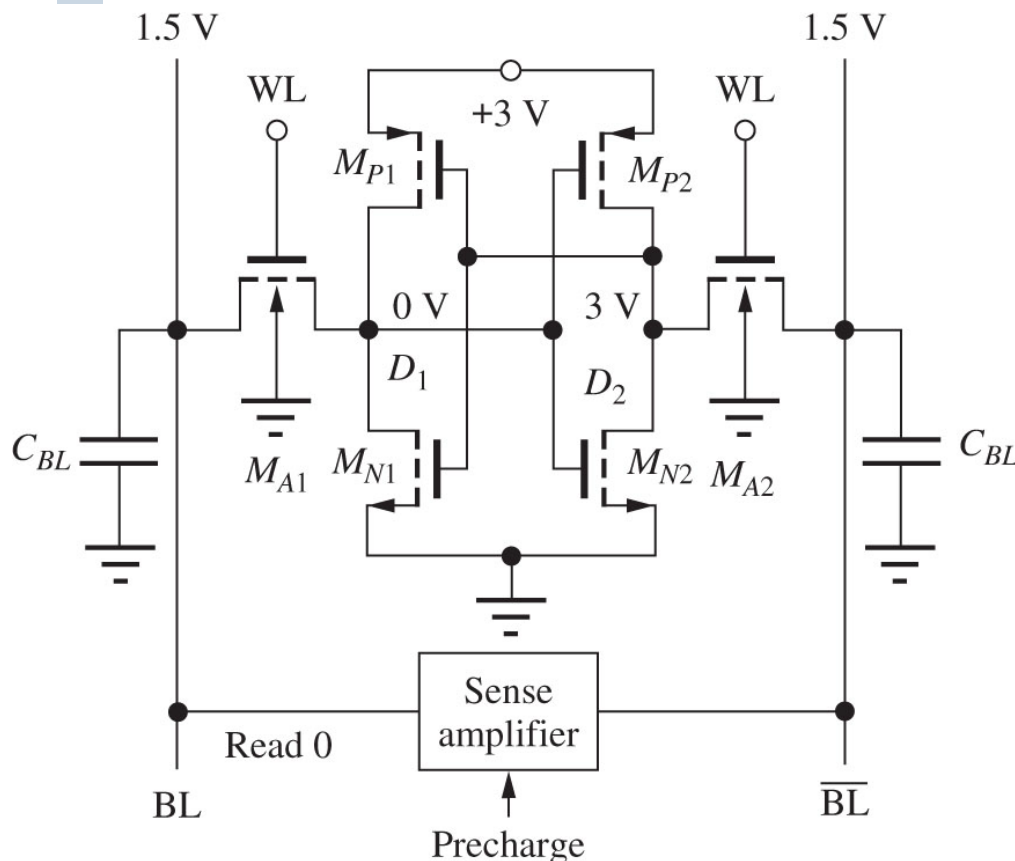- ❑ To read data stored in the SRAM cell, a **sense amplifier** is needed to detect the voltages in the bistable circuit.




- The sense amplifier typically pre-charges the capacitors C_{BL} of the **bit line** (BL) to a voltage of half of the V_{DD} .
- When the **word line** (WL) is activated, voltage signals of the bistable circuit pass to C_{BL} via M_{A1} & M_{A2} .



Xi'an Jiaotong-Liverpool University
西交利物浦大學

Memory Cell of Static RAM

(sense amplifier & read-write circuitry)

 


- The **sense amplifier** (and also the write driver) can be shared among multiple memory cells by using circuits to select the memory cells.

From: D.A. Hodges *et al.*, *Analysis and Design of Digital Integrated Circuits: In Deep Submicron Technology*, 3rd edition, © 2003 McGraw Hill, USA.

Memory Cell of EEPROM

(electrically erasable programmable)

 - ❑ In the case of the ROM, the **memory cell** can consist of only one device (e.g. transistor).



From: R. C. Jaeger & T. N. Blalock, *Microelectronic Circuit Design*, 4e, © 2010 McGraw-Hill, USA.

- ❑ In the electrically erasable programmable ROM (EEPROM), the device in the memory cell is a MOSFET with a **control gate** and a **floating gate**.
 - Charges (namely electrons) are stored in the floating gate.


- Such EEPROM is also known as **flash memory**, used in USB memory sticks.



Xi'an Jiaotong-Liverpool University
西交利物浦大学



Memory Cell of EEPROM

(floating gate for storing charges)

 

(a)

  From: D.A. Hodges *et al.*, *Analysis and Design of Digital Integrated Circuits: In Deep Submicron Technology*, 3rd edition, © 2003 McGraw Hill, USA.



- ❑ The **EEPROM** memory cell is essentially a MOSFET, but with an additional internal node in the gate electrode.
- Note the two gate capacitors in series in the equivalent circuit diagram; charges can be stored in the bottom capacitor C_1 .





Xi'an Jiaotong-Liverpool University
西交利物浦大学

Memory Cell of EEPROM

(threshold voltage of MOS transistor)

  - ❑ The presence of charges in the **floating gate** give a different **threshold voltage** V_{Tn} *sensed* at the control gate of the MOS transistor.
 - Reading data involves *sensing* the V_{Tn} of the transistor.
- ❑ Erasure of data requires a voltage (+ve or -ve) of larger magnitude applied to the **control gate** to introduce or remove charges into or from the **floating gate**.



From: R. C. Jaeger & T. N. Blalock,
Microelectronic Circuit Design,
4e, © 2010 McGraw-Hill, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大学

Memory Cell of EEPROM

(I-V curve of the MOSFET with a floating gate)

- ❑ The presence of electrons in the **floating gate** give a higher **threshold voltage** V_{Tn} *sensed* at the control gate of the nMOS transistor.

 From: D.A. Hodges et al., Analysis and Design of Digital Integrated Circuits: In Deep Submicron Technology, 3rd edition, © 2003 McGraw Hill, USA.





- After removal of electrons in the floating gate, V_{Tn} decreases when *sensed* at the control gate.
- The I_D - V_{GS} curve of the nMOS transistor is shifted horizontally accordingly.

Memory Cell of EEPROM

(write & erasure processes)

  - ❑ In writing data to the EEPROM memory cell, the charges (typically electrons) are injected to the floating gate at the drain end, by hot carrier injection (HCI).
- In erasing data, electrons are removed at the source end from the floating gate.




From: D.A. Hodges et al., *Analysis and Design of Digital Integrated Circuits: In Deep Submicron Technology*, 3rd edition, © 2003 McGraw Hill, USA.

Memory Cell of EEPROM

(electrically erasable programmable)

 - ❑ In some EEPROMs, the erasure of data can also be accomplished more easily with the use of UV light.



- An electron can gain energy by absorbing a photon and hence overcoming the energy barrier to get away from the floating gate.

From: D.A. Hodges *et al.*, *Analysis and Design of Digital Integrated Circuits: In Deep Submicron Technology*, 3rd edition, © 2003 McGraw Hill, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Memory Cell of EEPROM

(additional select transistor)

 - ❑ In some EEPROMs, there is an additional transistor for selecting the memory cell to read/write data.



- Despite certain reliability advantages, the bit density is lower in such EEPROM design.


From: D.A. Hodges et al., *Analysis and Design of Digital Integrated Circuits: In Deep Submicron Technology*, 3rd edition, © 2003 McGraw Hill, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Flash Memory

(NOR array)

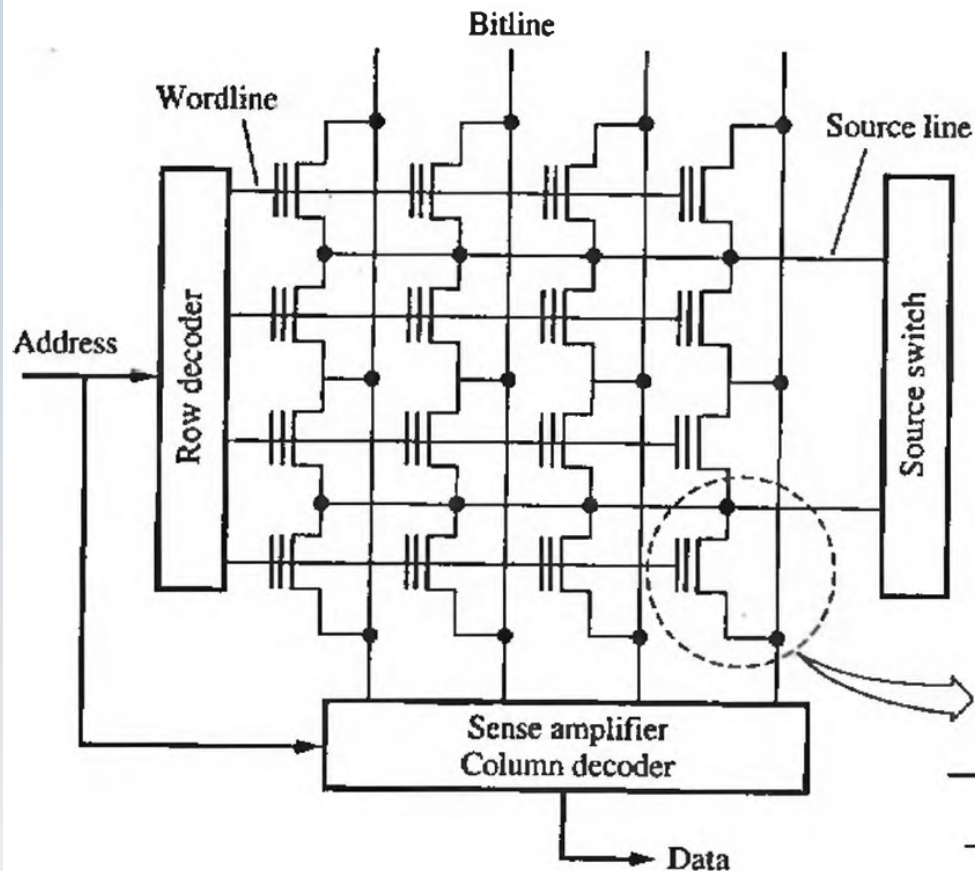

 - The floating gate transistors can be configured in parallel to form an expandable **NOR array** for storing more bits.



From: D.A. Hodges et al., *Analysis and Design of Digital Integrated Circuits: In Deep Submicron Technology*, 3rd edition, © 2003 McGraw Hill, USA.




Xi'an Jiaotong-Liverpool University
西交利物浦大學

Address Decoder

(use combinational logic circuits)

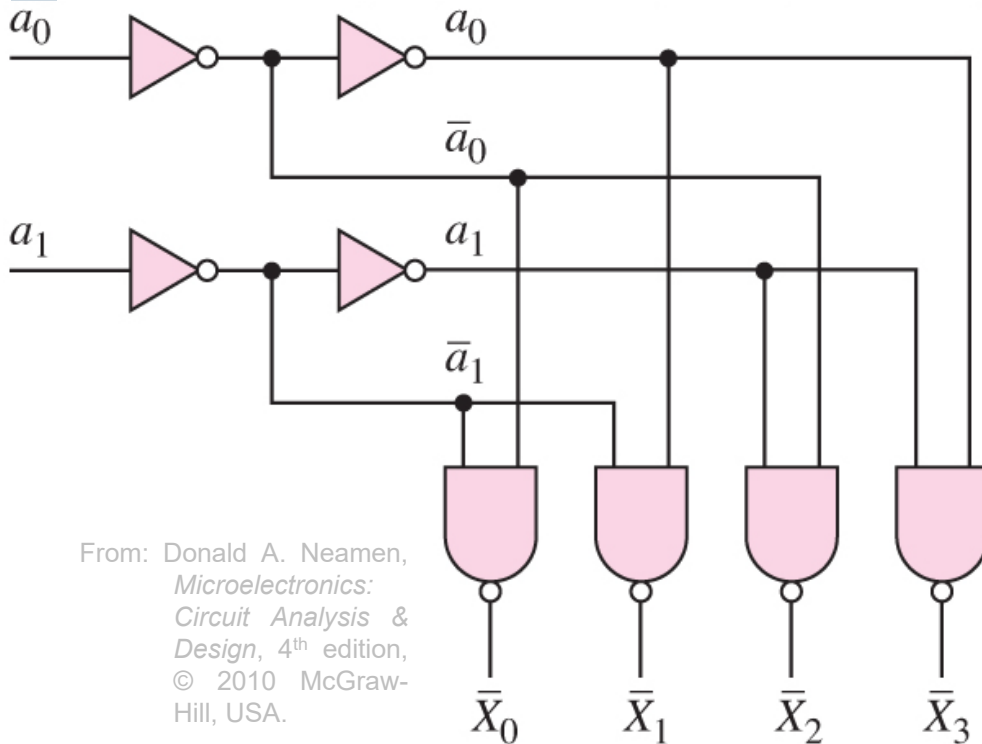- ❑ When the **memory cells** are arranged in an **array**, **address decoders** are needed to read/write data from/to specific cells.



From: Donald A. Neamen,
*Microelectronics:
Circuit Analysis &
Design*, 4th edition,
© 2010 McGraw-
Hill, USA.

- Address decoders are **combinational logic circuits** and can be implemented using basic logic gates.
- A 2-bit address decoder shown here can address four rows or columns.

SRAM vs. DRAM

(memory density)

- ❑ It can be seen that the **SRAM** cell occupies relatively much chip area.
 - As a result, the memory size of the **SRAM** can be quite limited. A modern microprocessor has 25 MB SRAM.
 - $1 \text{ MB} = 1024 \text{ KB}$; $1 \text{ KB} = \underline{1024} \text{ byte} = \underline{2^{10}} \text{ byte}$; $1 \text{ byte} = 8 \text{ bit}$. How many SRAM cells are needed for storing 25MB digital data?
- ❑ With only one transistor and one capacitor, the DRAM cell uses up far less chip area than that of the SRAM.
 - The DRAM can have very high memory density (e.g. 16 GB). $1 \text{ GB} = 1024 \text{ MB}$. But it has lower speed and larger power consumption.

SRAM, DRAM & Flash Memory

(applications)

- ❑ With much faster read/write speed (typically 10 ns or less) of the **SRAM**, it is used as **cache memory** in microprocessors.
 - With its relatively lower cost but reasonable read/write speed, the **DRAM** is used as the main computational memory of the computer.
- ❑ The **flash memory** has only one transistor in the memory cell.
 - As a result, it has somewhat even higher memory density.
 - It is used for memory cards, USB memory sticks and solid-state drives.
 - However, its write speed can be very low ($> 10 \mu\text{s}$).



Xi'an Jiaotong-Liverpool University

西交利物浦大學