

EEE211 - Assn 2.

Q1 : $V^+ = 15V$, $V^- = -5V$, $I_B = 0.8mA$

$R_C = 25k\Omega$, $\beta = \infty$, $V_A = \infty$.


$V_{BE(on)} = 0.7V$, $V_T = 26mV$,

$V_{B1} = 1.001V$, $V_{B2} = 0.999V$

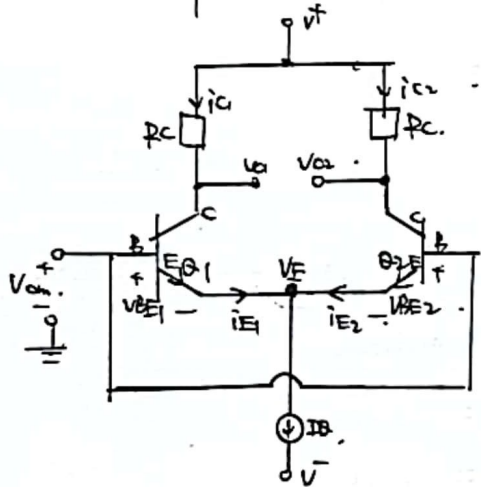i. $V_{cm} = \frac{V_{B1} + V_{B2}}{2} = 1V$.

$\rightarrow V_E = V_{cm} - V_{BE(on)} = 0.3V$

$\rightarrow Q$ - point Circuit shown as below.



\rightarrow Assume negligible base current,

$\rightarrow i_{C1} \approx i_{E1}$ and $i_{C2} \approx i_{E2}$.

\rightarrow Apply KCL at Node (VE)

$\rightarrow i_{E1} + i_{E2} = I_B$

$\rightarrow i_{C1} = i_{C2} = \frac{I_B}{2}$.

\rightarrow Apply KVL

$\rightarrow V_{CE1} = V^+ - i_{C1} R_C - V_E$

$\left\{ \begin{aligned} V_{CE2} &= V^+ - i_{C2} R_C - V_E \end{aligned} \right.$

$\left\{ \begin{aligned} i_{C1} &= i_{C2} = \frac{I_B}{2} \approx, V_E = 0.3V \end{aligned} \right.$

$I_B = 0.8mA$, $R_C = 25k\Omega$, $V^+ = 5V$

$\rightarrow V_{CE1} = V_{CE2} = 15 - \frac{0.8mA \times 25k}{2} - 0.3$

$\rightarrow V_{CE1} = V_{CE2} = 4.7V$

\rightarrow In Summary

$\left\{ \begin{aligned} i_{C1} &= 0.4mA \\ i_{C2} &= 0.4mA \\ V_E &= 0.3V \\ V_{CE1} &= 4.7V \\ V_{CE2} &= 4.7V \end{aligned} \right.$

ii. $\left\{ \begin{aligned} i_{C1} &= I_S \exp\left(\frac{V_{BE1}}{V_T}\right) \\ i_{C2} &= I_S \exp\left(\frac{V_{BE2}}{V_T}\right) \end{aligned} \right.$

$I_B = i_{C1} + i_{C2}$

$\rightarrow \left\{ \begin{aligned} i_{C1} &= \frac{I_B}{1 + \exp\left(\frac{-V_D}{V_T}\right)} \\ i_{C2} &= \frac{I_B}{1 + \exp\left(\frac{+V_D}{V_T}\right)} \end{aligned} \right.$

Where, $V_D = V_{BE1} - V_{BE2}$

Apply KVL

$\rightarrow V_D = V_{B1} - V_{B2} = V_{BE1} - V_{BE2}$

$\rightarrow V_D = 2mV$.

$\left\{ \begin{aligned} V_T &= 26mV \\ I_B &= 0.8mA \end{aligned} \right. \Rightarrow \left\{ \begin{aligned} i_{C1} &= \frac{0.8mA}{1 + \exp\left(\frac{-2mV}{26mV}\right)} = 0.42mA \\ i_{C2} &= \frac{0.8mA}{1 + \exp\left(\frac{2mV}{26mV}\right)} = 0.38mA \end{aligned} \right.$

\rightarrow Apply KVL


$\rightarrow V_{O1} = V^+ - i_{C1} R_C$; $V_{O2} = V^+ - i_{C2} R_C$

$\rightarrow V_{O1} = 15 - 0.42mA \times 25k = 4.62V$

$\rightarrow V_{O2} = 15 - 0.38mA \times 25k = 5.38V$

iii.

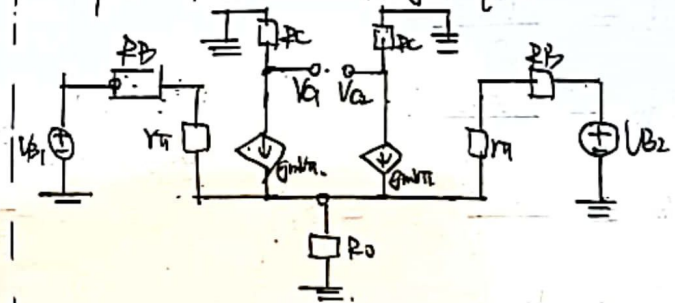Step 1: Draw the small-signal equivalent circuit.



Note: Replace Current Source with R_O
Voltage Source with V_B and a Resistor R_B .

Step 2: Analysis.

Apply KVL

$$\rightarrow V_{C1} = -g_m V_{\pi 1} \cdot R_C$$

$$\left\{ \begin{aligned} V_{C2} &= -g_m V_{\pi 2} \cdot R_C \end{aligned} \right.$$

$$\rightarrow V_o = V_{C2} - V_{C1}$$

$$\rightarrow V_o = g_m R_C (V_{\pi 1} - V_{\pi 2}) = \frac{\beta}{r_{\pi}} R_C (V_{\pi 1} - V_{\pi 2})$$

Apply KCL, KVL and Ohm's Law.

We can find 5 unknowns: $I_{B1}, I_{B2}, V_{\pi 1}, V_{\pi 2}, V_e$

with 5 Equations

$$I_{B1} = \frac{V_{B1} - V_e - V_{\pi 1}}{R_B} = \frac{V_{B1} - V_e}{R_B + r_{\pi}}$$

$$I_{B2} = \frac{V_{B2} - V_e - V_{\pi 2}}{R_B} = \frac{V_{B2} - V_e}{R_B + r_{\pi}}$$

$$I_{B1} + I_{B2} + g_m V_{\pi 1} + g_m V_{\pi 2} = \frac{V_e}{R_E}$$

$$I_{B1} = \frac{V_{\pi 1}}{r_{\pi}}$$

$$I_{B2} = \frac{V_{\pi 2}}{r_{\pi}}$$

$$\rightarrow V_o = \frac{\beta R_C}{r_{\pi} + R_B} (V_{B1} - V_{B2})$$

$$V_d = V_{B1} - V_{B2}$$

$$\rightarrow V_o = \frac{\beta R_C}{r_{\pi} + R_B} V_d$$

Since $R_B = 0 \Omega$, $r_{\pi} = \frac{\beta V_T}{I_{CQ}}$, $I_{CQ} = \frac{I_o}{2}$

\rightarrow Thus, $V_o = \frac{I_o \cdot R_C}{2 V_T} \cdot V_d$

\rightarrow Hence, $A_d = \frac{I_o \cdot R_C}{2 V_T} = \frac{0.8m \cdot 25k}{2 \cdot 26m} = 384.62$

We know that CMRR is defined as

$$CMRR = \left| \frac{A_d}{A_{cm}} \right| \text{ in absolute value}$$


\rightarrow then $CMRR = \left| \frac{384.62}{-0.01} \right| = 38462$

\rightarrow and $CMRR = 20 \log_{10} \left| \frac{A_d}{A_{cm}} \right| = 91.70 \text{ dB}$

\Rightarrow In Summary $\left\{ \begin{aligned} \text{Differential-mode gain } A_d &= 384.62 \\ \text{CMRR in absolute value} &= 38462 \\ \text{CMRR in decibels} &= 91.70 \text{ dB} \end{aligned} \right.$

Q2.

(a) i.

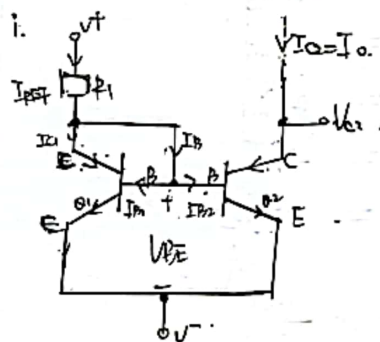

Step 1: KVL around the left Q1.

$$\rightarrow V^+ - V^- = I_{REF} \cdot R_1 + V_{BE(on)}$$

$$\rightarrow I_{REF} = \frac{V^+ - V^- - V_{BE(on)}}{R_1} = \frac{10 - 0 - 0.7}{50k} = 0.186 \text{ mA}$$

Step 2: KCL of BJT Q1 - collector

$$\rightarrow I_{REF} = I_{C1} + I_B = I_{C1} + I_{B1} + I_{B2}$$

Step 3: Current relationship

Since $V_{BE1} = V_{BE2}$

\rightarrow then $I_{B1} = I_{B2}$, $I_{C1} = I_{C2}$

Step 4: Assume both BJT are biased in forward active region

\rightarrow then, $I_{C1} = \beta I_{B1}$

$I_{C2} = \beta I_{B2}$

$I_{C1} = I_{C2} = I_o$

$I_{REF} = I_{C1} + I_{B1} + I_{B2}$

$$\rightarrow I_{REF} = I_{C1} + \frac{I_{C1}}{\beta} + \frac{I_{C1}}{\beta} = \left(1 + \frac{2}{\beta}\right) I_{C1}$$

$$\rightarrow I_o = I_{C1} = \frac{I_{REF}}{\left(1 + \frac{2}{\beta}\right)} = \frac{0.186 \text{ mA}}{1 + \frac{2}{80}} = 0.181 \text{ mA}$$

$$\rightarrow I_{B1} = \frac{I_o}{\beta} = I_{B2} = \frac{I_{C2}}{\beta} = \frac{0.181 \text{ mA}}{80} = 2.268 \text{ mA}$$

Step 5: Conclusion

$I_{REF} = 0.186 \text{ mA}$

$I_o = 0.181 \text{ mA}$


$I_{B1} = 2.268 \text{ mA}$

$I_{B2} = 2.268 \text{ mA}$

ii. Step 1: Find ~~V_{CE2}~~ and V_{CE1}

→ From the configuration, $V_{CE1} = V_{BE(on)} = 0.7V$

Step 2: Apply a Load Circuit to find r_o

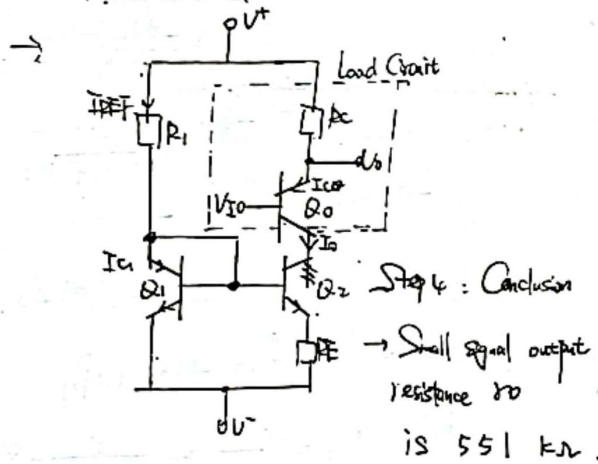

Step 3: Deduction

From the diagram

$$\rightarrow \frac{dI_o}{dV_{CE2}} = \frac{1}{r_o} \quad (1)$$

Apply ohm's law.

$$\rightarrow V_{CE2} = V_{CE1} - V$$


$$\rightarrow dV_{CE2} = dV_{CE1} \quad (2)$$

Given the relation that

$$\rightarrow I_o = \frac{I_{REF}}{(1 + \frac{2}{\beta})} \times \frac{1 + \frac{V_{CE1}}{V_A}}{1 + \frac{1}{\beta}} \quad (3)$$

Combine (1), (2), (3)
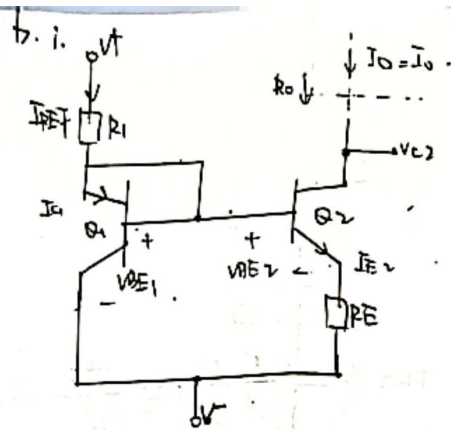
$$\rightarrow \frac{dI_o}{dV_{CE2}} = \frac{I_{REF}}{1 + \frac{2}{\beta}} \times \frac{1}{1 + \frac{1}{\beta}} \times \frac{1}{V_A} = \frac{dI_o}{dV_{CE1}} = \frac{1}{r_o} \rightarrow r_o = 551 k\Omega$$



Step 1: Find β_1

Apply KVL around transistor Q_1

$$\rightarrow V^+ - V - V_{BE(on)} = I_{REF} R_1$$

$$\rightarrow \beta_1 = \frac{V^+ - V - V_{BE(on)}}{I_{REF}} = \frac{3 - (-1) - 0.7}{2m} = 2.65k\Omega$$

Step 2: Find β_E

Apply KVL around the bottom,

$$\rightarrow V_{BE1} = V_{BE2} + I_{E2} R_E \quad (1)$$

Since $I_o = 10 \mu A$, and we ignore Base current

$$\rightarrow \text{Then } I_{C2} = 10 \mu A = I_{E2} \quad (2)$$

Apply KCL to the Collector Node of Q_1

$$\rightarrow I_{REF} = I_{C1} + I_B = I_{C1}$$

$$\rightarrow I_{C1} = 2mA \quad (3)$$

Equation (1) can be simplified as

$$V_T \ln\left(\frac{I_{C1}}{I_S}\right) - V_T \ln\left(\frac{I_{C2}}{I_S}\right) = I_{E2} R_E$$

$$\rightarrow R_E = \frac{V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right)}{I_{E2}} \quad (4)$$

Combine (2), (3), (4)

$$\rightarrow R_E = \frac{26m \cdot \ln\left(\frac{2mA}{10\mu A}\right)}{10\mu A} = 13.78k\Omega$$

ii.

Apply KVL to the ground loop.

$$\rightarrow V_{BE1} = V_{BE2} + I_{E2} R_E \quad (1)$$

Since we know that

$$I_{E2} = I_o = 10 \mu A$$

$$R_E = 13.78 k\Omega$$


$$V_{BE1} = V_{BE(on)} = 0.7V$$

$$\begin{aligned} \rightarrow V_{BE2} &= V_{BE1} - I_{E2} R_E \\ &= 0.7 - 10\mu \cdot 13.78k \\ &= 0.56V \end{aligned}$$

Q3: $S_i = 1\text{mV}$, $S_o = 99.9\text{mV}$, $S_{fb} = 0.999\text{mV}$.

i. Step 1: Deduction.

From the configuration shown as below.

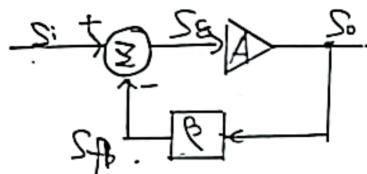

$$\Rightarrow \begin{cases} S_i - \beta S_o = S_e \\ S_e \cdot A = S_o \end{cases}$$

$$\Rightarrow \frac{S_o}{S_i} = \frac{A}{1+A\beta}$$

Step 2: Find A_f , β , A

1° closed-loop gain A_f

$$\Rightarrow A_f = \frac{S_o}{S_i} = \frac{A}{1+A\beta} = \frac{99.9\text{m}}{1\text{m}} = 99.9$$

2° feedback transfer function β .

$$\Rightarrow \beta = \frac{S_{fb}}{S_o} = \frac{0.999\text{m}}{99.9\text{m}} = \frac{1}{100}$$

3° open-loop gain A

$$\Rightarrow A = \frac{S_o}{S_e} = \frac{S_o}{S_i - \beta S_o} = \frac{99.9\text{m}}{1\text{m} - 0.999\text{m}} = 99900$$

$$\Rightarrow A = \frac{99.9\text{m}}{1\text{m} - 0.999\text{m}} = 99900$$

ii. From i, we are able to derive

$$\rightarrow A = 99900$$

Since we know that.

$$A_f = \frac{A}{1+A\beta}$$

$$\rightarrow \text{then } \beta = \left(\frac{A - A_f}{A \cdot A_f} \right)^{-1} = \frac{99900 - 200}{99900 \times 200} = 4.99\text{m}$$

$$\rightarrow \text{Therefore, transfer function } \beta = 4.99 \times 10^{-3}$$

iii. From i and ii, we know that

$$\rightarrow A_f = \frac{A}{1+A\beta}$$

$$\rightarrow \frac{dA_f}{dA} = \frac{1+A\beta - A\beta}{(1+A\beta)^2}$$

$$\rightarrow dA_f = \frac{dA}{(1+A\beta)^2}$$

Then Divide A_f in both sides.

$$\rightarrow \frac{dA_f}{A_f} = \frac{dA}{(1+A\beta)^2} \cdot \frac{1+A\beta}{A} = \frac{1}{(1+A\beta)} \left(\frac{dA}{A} \right)$$

Next, substitute $\beta = 0.005$, $A = 10^5$, $\frac{dA}{A} = \pm 5\%$

$$\rightarrow \frac{dA_f}{A_f} \approx \frac{\pm 5\%}{2.002 \times 10^{-3}} \approx \pm 25\%$$

\rightarrow Case 1: A increases by 50%

$$\text{That means } \frac{dA_f}{A_f} = \frac{1}{1+A\beta} \cdot +50\% = +0.67\%$$

\rightarrow Case 2: A decreases by 50%

$$\text{That means } \frac{dA_f}{A_f} = \frac{1}{1+A\beta} \cdot (-50\%)$$

$$\frac{dA_f}{A_f} = -0.199\%$$

\Rightarrow In Summary, the variation of closed-loop gain A_f in percentage Value is from -0.199% to $+0.67\%$

iv. Step 1: Deduction

$$\rightarrow A_f(s) = \frac{A(s)}{1+A(s)\beta}$$

$$= \frac{A_o}{1+s/\omega_H} \cdot \frac{1}{1+\beta \frac{A_o}{1+s/\omega_H}}$$

$$= \frac{A_o}{1+\beta A_o} \cdot \frac{1}{1+\frac{s}{\omega_H(1+\beta A_o)}}$$

$$\text{where } A_{fo} = \frac{A_o}{1+\beta A_o}$$


$$\omega_{fh} = \omega_H \cdot (1+\beta A_o)$$

Step 2: Find A_{fo} , ω_{fh}

$$\rightarrow A_{fo} = \frac{A_o}{1+\beta A_o} = \frac{10^5}{1+10^2} = 999.10$$

$$\begin{aligned} \rightarrow \omega_{fh} &= \omega_H \cdot (1+\beta A_o) \\ &= 10 \cdot (1+10^2 \times 10^5) \\ &= 1010 \text{ rad/s} \end{aligned}$$

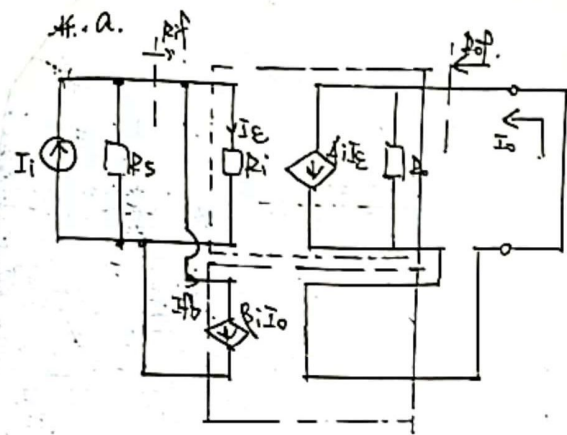\rightarrow In Summary, $A_f(s) = \frac{A_o}{1+\beta A_o} \cdot \frac{1}{1+\frac{s}{\omega_{fh}(1+\beta A_o)}}$
closed-loop low frequency gain $A_{fo} = 999.10$
closed-loop corner frequency $\omega_{fh} = 1010 \text{ rad/s}$



i. Type: Shunt-Series Current Amplifier

Reason:
 Input: feedback affects input signal in terms of current.
 Output: Short-Circuit the output load, it is current-sensing.

ii. Since $R_s = \infty$, and Apply KCL on Input terminal.


$$\rightarrow I_i - I_{fb} = I_E$$

$$\rightarrow I_E = 1\text{mA} - 0.99\text{mA} = 0.01\text{mA}$$

Apply ohm's law at output node

$$\rightarrow I_o = A_i I_E$$
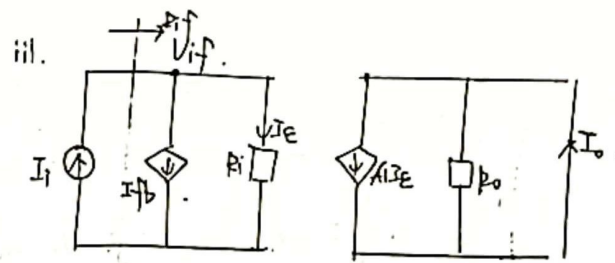
$$\rightarrow \left. \begin{aligned} A_i &= \frac{I_o}{I_E} \\ I_o &= 100\text{mA} \\ I_E &= 0.01\text{mA} \end{aligned} \right\} \Rightarrow \text{Open-loop Gain } A_i = \frac{100\text{mA}}{0.01\text{mA}} = 5 \times 10^4$$



$$\rightarrow R_{if} = \frac{V_{if}}{I_i} \text{ and } I_o = A_i I_E$$

Apply KCL and ohm's law at input terminal

$$\rightarrow I_i = I_{fb} + \frac{V_{if}}{R_i}$$


$$\left. \begin{aligned} I_i &= \beta_i I_o + \frac{V_{if}}{R_i} \\ I_o &= A_i I_E = A_i \frac{V_{if}}{R_i} \end{aligned} \right\} \rightarrow R_{if} = \frac{R_i}{1 + A_i \beta_i}$$

From ii., we know that $A_i = 5 \times 10^4$

$$\left\{ \beta_i = \frac{I_{fb}}{I_o} = 1.98 \times 10^{-1} \right.$$

Since $R_{if} = \frac{R_i}{1 + A_i \beta_i}$
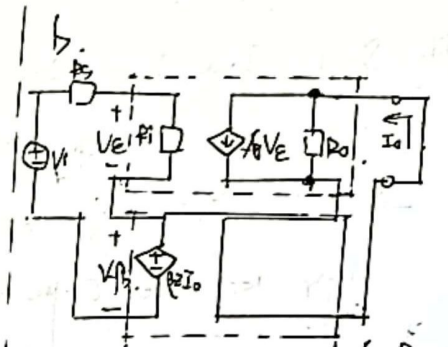
$$\Rightarrow \text{Thus, } R_{if} = \frac{5k}{1 + 99} = 50 \Omega$$



i. Type: Series-Series Transconductance Amplifier

Reason:
 Input: feedback affects input signal in terms of voltage.
 Output: Short-Circuit the output, feedback signal is current sensing.

ii. Apply KVL at Input node

$$\rightarrow V_i = V_E + V_{fb}$$

$$\rightarrow V_i = V_E + R_E I_o \quad (1)$$

Apply KCL at Output node

$$\rightarrow I_o = A_g V_E \quad (2)$$

We know that

$$\rightarrow A_g f = \frac{I_o}{V_i} \quad (3)$$

Then, Combine (1), (2), (3)

$$\rightarrow A_g f = \frac{A_g}{1 + R_E A_g}$$

\Rightarrow Therefore,

$$\text{Closed-loop gain } A_g f = \frac{A_g}{1 + R_E A_g}$$

iii. Step 1: Input Resistance R_{if}

Apply I_i at Input Node

$$\rightarrow V_i = I_i R_i + \beta_z I_o \quad (1)$$

Apply I_{o1} at Output Node

$$\rightarrow I_o = A_\beta V_e \quad (2)$$

Apply Ohm's law at Input Node

$$\rightarrow V_e = I_i \cdot R_i \quad (3)$$


Combine (1), (2), (3)

$$\rightarrow V_i = I_i R_i + \beta_z A_\beta R_i \cdot I_i$$

$$\rightarrow \frac{V_i}{I_i} = R_i (1 + \beta_z A_\beta) = R_{if}$$


Step 2: Output Resistance R_{of}

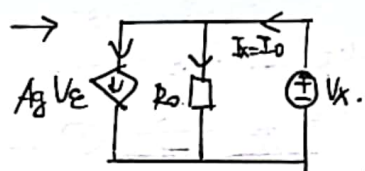Apply a test voltage source at Output Node



→ Apply KVL and
Thevenin Equivalent Circuit
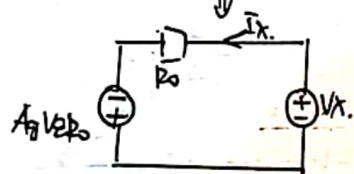
$$\rightarrow V_x = I_x R_o - A_\beta V_e R_o \quad (4)$$




If we would like to apply test source to find R_{of}

→ we have to Disable the voltage supply V_i

→ That means V_i has to be treated as Open-loop

→ And the Circuit will be .

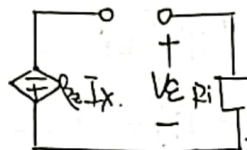

$$\rightarrow V_e = -\beta_z I_x \quad (5)$$

Combine (4) and (5)

$$\rightarrow V_x = I_x (1 + A_\beta \beta_z) R_o$$

$$\rightarrow \frac{V_x}{I_x} = R_o (1 + A_\beta \beta_z) = R_{of}$$

Step 3: Conclusion .

In Summary

$$\left\{ \begin{array}{l} \text{Input resistance } R_{if} = R_i (1 + \beta_z A_\beta) \\ \text{Output resistance } R_{of} = R_o (1 + \beta_z A_\beta) \end{array} \right.$$

$$\left\{ \begin{array}{l} \text{Input resistance } R_{if} = R_i (1 + \beta_z A_\beta) \\ \text{Output resistance } R_{of} = R_o (1 + \beta_z A_\beta) \end{array} \right.$$