

EEE205 – Digital Electronics (II)

Lecture 5

Xiaoyang Chen, Jiangmin Gu, and Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

In This Session

- Representing Data in AHDL
- Operators
- Truth Tables Using AHDL
- Decision Control Structures in AHDL

Identifiers

- Composed of legal characters
 - Letters (a–z, A–Z)
 - Digits (0–9)
 - Slash (/)
 - Underscore (_)
- Can begin with a digit
- Must not be a reserved word
- Identifiers and keywords are **case-insensitive**.

Representing Data in AHDL

- Binary, hexadecimal, and decimal values are represented in AHDL as shown, with a prefix to indicate the number system.

Number System	AHDL	Decimal Equivalent
Binary	B"101"	5
Hexadecimal	H"101"	257
Decimal	101	101

- Constants: **VCC** and **GND**

Representing Data in AHDL

Bit Arrays or **Bit Vectors** are used to describe a port or a node with more than one data bit.

Declaration

- Syntax – a name is followed by the index range.
- Example:

```
p1 [7..0] :INPUT;  -- DEFINE AN 8-BIT INPUT PORT
```
- Individual bits can be accessed by specifying the bits, e.g. p1[5].

Representing Data in AHDL

Bit Array Assignment

- To assign the 8-bit port p1 to a node named temp:

```
VARIABLE    temp [ 7 .. 0 ] : NODE;  
BEGIN  
    temp [ ] = p1 [ ] ;  
END
```

- The empty braces mean that all bits in the array are being connected.
- Individual bits could also be connected, e.g.
temp [0] = p1 [0] ;

Operators

Boolean Operators

Operator	Alternate	Description
!	NOT	Inverter
&	AND	AND
! &	NAND	AND with Inverted Output
#	OR	OR
! #	NOR	OR with Inverted Output
\$	XOR	Exclusive OR
! \$	XNOR	Exclusive OR with Inverted Output

Arithmetic Operators

Operator	Description
- (unary)	Two's Complement Negation
+	Unsigned/Two's Complement Addition
-	Unsigned/Two's Complement Subtraction

Operators

Comparison Operators

Operator	Type	Description
==	Logical	Equal to
!=	Logical	Not equal to
<	Arithmetic	Less than
<=	Arithmetic	Less than or equal to
>	Arithmetic	Greater than
>=	Arithmetic	Greater than or equal to

Operators

The Concatenation Operator

- Combine nodes (and other groups) into a group by placing the node/group names in parentheses

`g[3..0] = (a, b, c, d);`

`(a, b, c, d) = g[3..0];`

- Can also be used to assign multiple ports in a single statement

`(a, b) = B"10";`

Truth Tables Using AHDL

- Circuits can be designed directly from truth tables in AHDL.
- The key point is to use the **TABLE** keyword.

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Truth Tables Using AHDL


```
SUBDESIGN example
(
    a,b,c    :INPUT;      --define inputs to block
    y        :OUTPUT;     --define block output
)
BEGIN
    TABLE
        (a,b,c)    =>  y;  --column headings
        (0,0,0)    =>  0;
        (0,0,1)    =>  0;
        (0,1,0)    =>  0;
        (0,1,1)    =>  1;
        (1,0,0)    =>  0;
        (1,0,1)    =>  1;
        (1,1,0)    =>  1;
        (1,1,1)    =>  1;
    END TABLE;
END;
```

Truth Tables Using AHDL


```
SUBDESIGN another_example
(
    a,b,c  :INPUT;      --define inputs to block
    y      :OUTPUT;     --define block output
)
VARIABLE in_bits[2..0] :NODE;
BEGIN
    in_bits[] = (a,b,c); --concatenating
    TABLE
        in_bits[] => y; --column headings
        b"000"    => 0;
        b"001"    => 0;
        b"010"    => 0;
        b"011"    => 1;
        b"100"    => 0;
        b"101"    => 1;
        b"110"    => 1;
        b"111"    => 1;
    END TABLE;
END;
```

Decision Control Structures in AHDL

 - IF/THEN/ELSE statements provide a framework for making logical decisions in a system.
 - **IF/THEN** is used when there is a choice between doing something and doing nothing.
 - **IF/THEN/ELSE** is used when there is a choice between two possible actions.



(a)

 

(b)

Decision Control Structures in AHDL

- The IF/THEN/ELSE in AHDL:

```
SUBDESIGN FIG4_54
(
    digital_value[3..0]  :INPUT;  -- define inputs to block
    z                    :OUTPUT; -- define block output
)
BEGIN
    IF digital_value[] > 6 THEN
        z = VCC;                -- output a 1
    ELSE z = GND;                -- output a 0
    END IF;
END;
```

Decision Control Structures in AHDL

- The **CASE** construct determines the value of an expression and then goes through a list of values (cases) to determine what action to take, e.g. to implement truth table:

p	q	r	s
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Decision Control Structures in AHDL

- The CASE construct in AHDL:

```
SUBDESIGN fig4_60
(
    p, q, r      :INPUT;      -- define inputs to block
    s            :OUTPUT;     -- define outputs
)
VARIABLE
    status[2..0] :NODE;
BEGIN
    status[] = (p, q, r); -- link input bits in order
    CASE status[] IS
        WHEN b"100"      => s = GND;
        WHEN b"101"      => s = GND;
        WHEN b"110"      => s = GND;
        WHEN OTHERS      => s = VCC;
    END CASE;
END;
```


EEE205 – Digital Electronics (II)

Lecture 6

Xiaoyang Chen, Jiangmin Gu, and Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

In This Session


Combinational Logic in AHDL

- AHDL Decoders and Encoders
- AHDL MUX and DEMUX
- AHDL Comparators

AHDL Decoders

74LS138 — a 3-to-8 decoder or a 1-in-8 decoder:

 - The outputs are active-LOW.
- The decoder responds to the input code only when $\bar{E}_1 = \bar{E}_2 = 0$ and $E_3 = 1$.



\bar{E}_1	\bar{E}_2	E_3	Outputs
0	0	1	Respond to input code $A_2A_1A_0$
1	X	X	Disabled – all HIGH
X	1	X	Disabled – all HIGH
X	X	0	Disabled – all HIGH

```

1  SUBDESIGN fig9_52
2  (
3      a[2..0]                :INPUT;          -- binary inputs
4      e3, e2bar, e1bar       :INPUT;          -- enable inputs
5      y7,y6,y5,y4,y3,y2,y1,y0 :OUTPUT;        -- decoded outputs
6  )
7  VARIABLE
8      enable                 :NODE;
9  BEGIN
10     DEFAULTS
11         y7=VCC;y6=VCC;y5=VCC;y4=VCC;
12         y3=VCC;y2=VCC;y1=VCC;y0=VCC;        -- defaults all HIGH out
13     END DEFAULTS;
14     enable = e3 & !e2bar & !e1bar;          -- all enables activated
15     IF enable THEN
16         CASE a[] IS
17             WHEN 0    =>    y0 = GND;
18             WHEN 1    =>    y1 = GND;
19             WHEN 2    =>    y2 = GND;
20             WHEN 3    =>    y3 = GND;
21             WHEN 4    =>    y4 = GND;
22             WHEN 5    =>    y5 = GND;
23             WHEN 6    =>    y6 = GND;
24             WHEN 7    =>    y7 = GND;
25         END CASE;
26     END IF;
27 END;


```

AHDL Decoders

- The **DEFAULTS** keyword is to establish a value for variable that are not specified elsewhere in the code.
- This allows each case to force one bit LOW without stating that the others must go HIGH.

AHDL Encoders

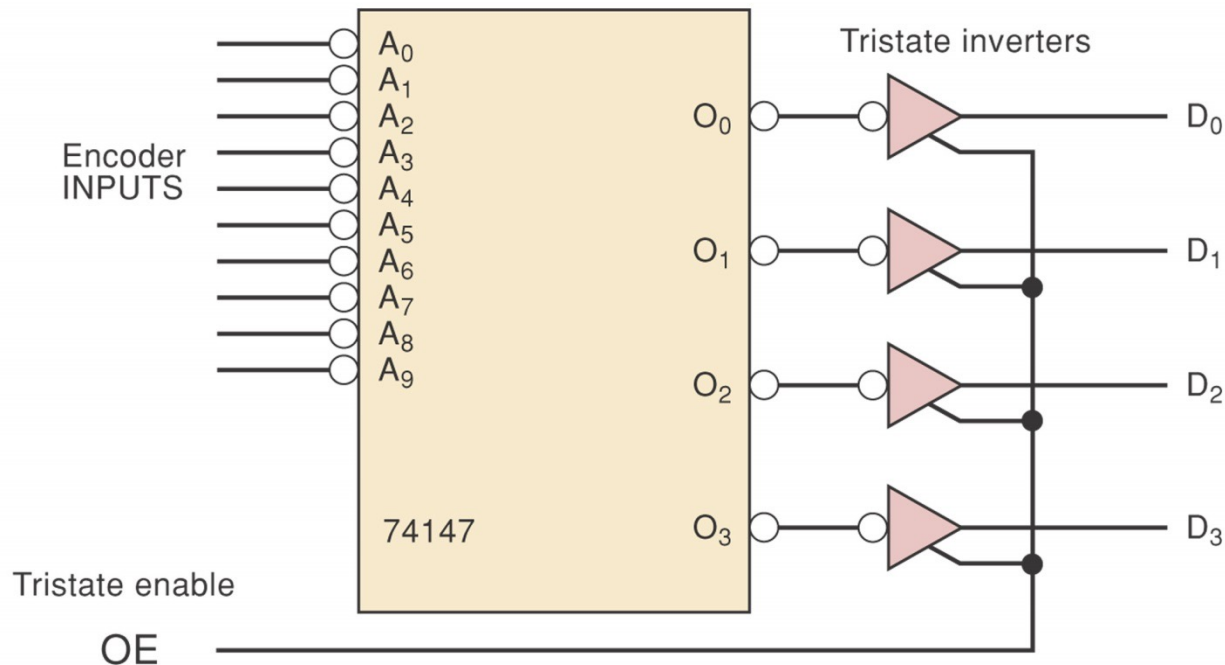- When one of the inputs is activated, it produces a binary number corresponding to that input.
- When more than one of its inputs is activated, it ignores the input of lower significance (Priority Encoder).



```

1  SUBDESIGN fig9_58
2  (
3      a[9..0], oe          :INPUT;
4      d[3..0]              :OUTPUT;
5  )
6  VARIABLE buffer[3..0]    :TRI;
7  BEGIN
8      TABLE
9          a[]              => buffer[].in;
10         B"111111111"     => B"1111";    -- no input active
11         B"1111111110"    => B"0000";    -- 0
12         B"1111111110X"   => B"0001";    -- 1
13         B"1111111110XX"  => B"0010";    -- 2
14         B"1111111110XXX" => B"0011";    -- 3
15         B"1111111110XXXX" => B"0100";   -- 4
16         B"1111111110XXXXX" => B"0101";  -- 5
17         B"1111111110XXXXXX" => B"0110";  -- 6
18         B"1111111110XXXXXXX" => B"0111";  -- 7
19         B"1111111110XXXXXXX" => B"1000";  -- 8
20         B"1111111110XXXXXXX" => B"1001";  -- 9
21     END TABLE;
22     buffer[].oe = oe;    -- hook up enable line
23     d[] = buffer[].out;  -- hook up outputs
24 END;

```

AHDL Encoders

- AHDL has a library **primitive** called **TRI** for tristate buffers.


```
VARIABLE  buffer[3..0]      :TRI;
```

- A primitive can be imagined as a component in a store and is similar to a structure in C.
- This makes the implementation easier — just to connect the primitive's ports to the appropriate signals.

```
buffer[].in = B"0000";  
buffer[].oe = oe;  
d[] = buffer[].out;
```


AHDL Encoders

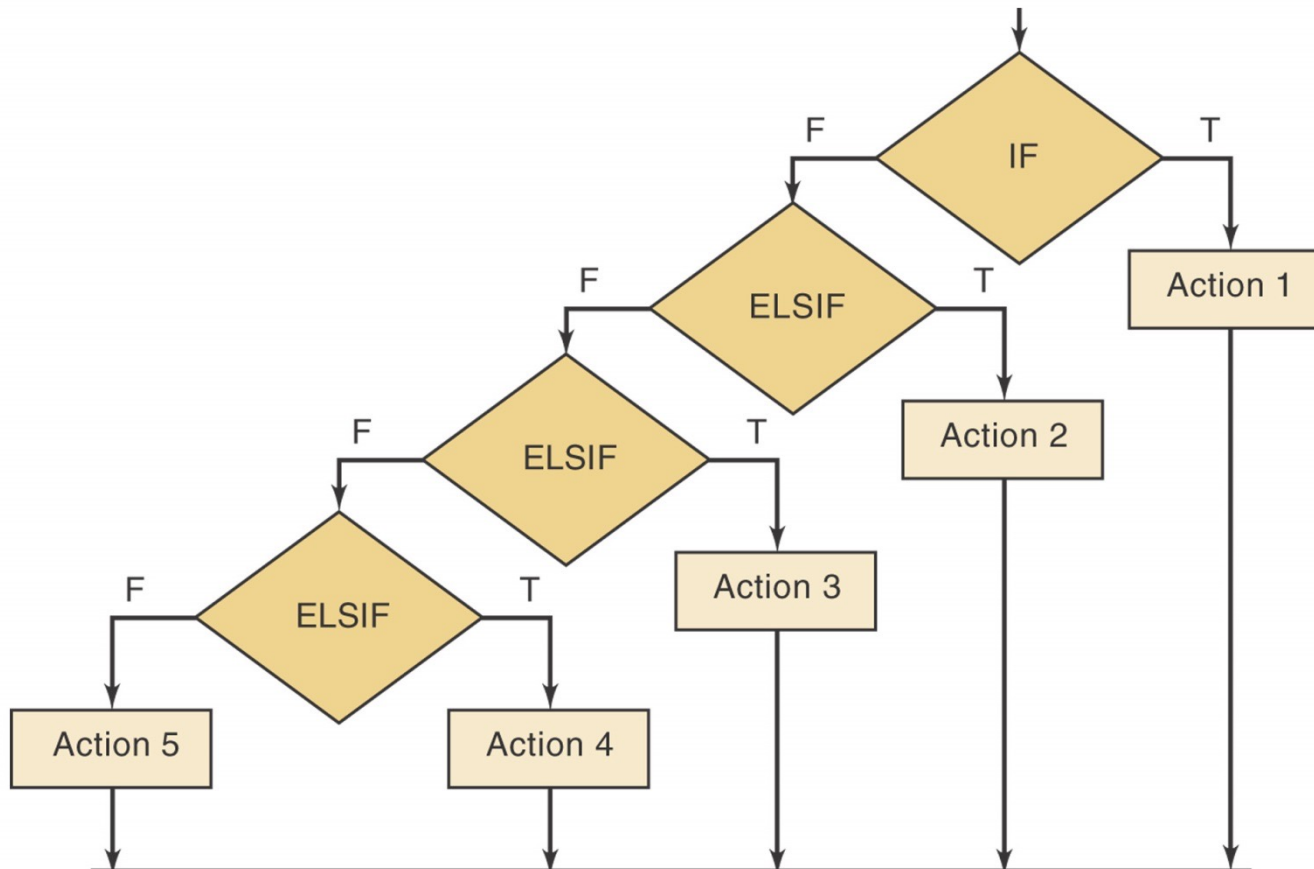- The AHDL encoder can also be implemented using **IF/ELSIF**, which choose one of many possible outcomes.




```

1  SUBDESIGN fig9_59
2  (
3      sw[9..0], oe    :INPUT;
4      d[3..0]        :OUTPUT;
5  )
6  VARIABLE
7      buffers[3..0]  :TRI;
8  BEGIN
9      IF      !sw[9]   THEN  buffers[].in = 9;
10     ELSIF !sw[8]   THEN  buffers[].in = 8;
11     ELSIF !sw[7]   THEN  buffers[].in = 7;
12     ELSIF !sw[6]   THEN  buffers[].in = 6;
13     ELSIF !sw[5]   THEN  buffers[].in = 5;
14     ELSIF !sw[4]   THEN  buffers[].in = 4;
15     ELSIF !sw[3]   THEN  buffers[].in = 3;
16     ELSIF !sw[2]   THEN  buffers[].in = 2;
17     ELSIF !sw[1]   THEN  buffers[].in = 1;
18     ELSE
19         buffers[].in = 0;
20     END IF;
21     buffers[].oe = oe & sw[]!=b"1111111111";  -- enable on any input
22     d[] = buffers[].out;                      -- connect to outputs
23 END;

```

AHDL MUX and DEMUX

 - A multiplexer selects and connects one of the inputs to the output.
- A demultiplexer distributes an input to one of its outputs.




AHDL MUX and DEMUX

```
1  SUBDESIGN fig9_62
2  (
3      ch0[3..0], ch1[3..0], ch2[3..0], ch3[3..0]:INPUT;
4      s[1..0]                                     :INPUT;  -- select inputs
5      dout[3..0]                                   :OUTPUT;
6  )
7  BEGIN
8      CASE S[] IS
9          WHEN 0 =>      dout[] = ch0[];
10         WHEN 1 =>      dout[] = ch1[];
11         WHEN 2 =>      dout[] = ch2[];
12         WHEN 3 =>      dout[] = ch3[];
13     END CASE;
14 END;
```

AHDL MUX and DEMUX

```
1  SUBDESIGN fig9_63
2  (
3      ch0[3..0], ch1[3..0], ch2[3..0], ch3[3..0]  :OUTPUT;
4      s[1..0]                                     :INPUT;
5      din[3..0]                                   :INPUT;
6  )
7  BEGIN
8      DEFAULTS
9          ch0[] = B"1111";
10         ch1[] = B"1111";
11         ch2[] = B"1111";
12         ch3[] = B"1111";
13     END DEFAULTS;
14
15     CASE S[] IS
16         WHEN 0 =>      ch0[] = din[];
17         WHEN 1 =>      ch1[] = din[];
18         WHEN 2 =>      ch2[] = din[];
19         WHEN 3 =>      ch3[] = din[];
20     END CASE;
21 END;
```

AHDL Comparators

 

If we need to compare bigger values, we can simply adjust the size of the input ports.

```
1  SUBDESIGN fig9_66
2  (
3      a[3..0], b[3..0]      :INPUT;
4      agtb, altb, aeqb      :OUTPUT;
5  )
6  BEGIN
7      IF      a[] > b[] THEN
8          agtb = VCC;      altb = GND;  aeqb = GND;
9      ELSIF  a[] < b[] THEN
10         agtb = GND;      altb = VCC;  aeqb = GND;
11      ELSE    agtb = GND ; altb = GND ; aeqb = VCC;
12      END IF;
13  END;
```