

CAN209 Advanced Electrical Circuits and Electromagnetics


Lecture 16 Balanced Three-phase Systems

Dr. Zhenzhen Jiang

Assistant Professor, FHEA

Faculty: School of Advanced Technology

Email: zhenzhen.jiang02@xjtlu.edu.cn

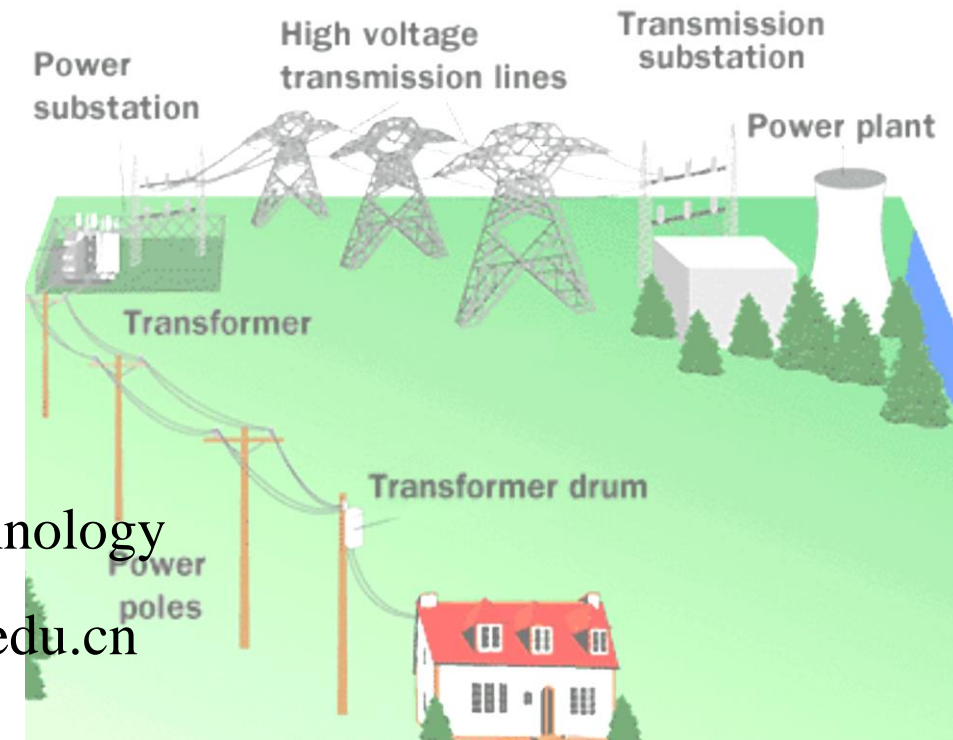


OUTLINE

- Overview
 - ✓ Industrial Applications
 - ✓ Single-phase and Three-phase Supply
- Balanced Three-phase Supply and Load
 - ✓ Y & Δ Connected Supply
 - ✓ Y & Δ Connected Load
- Balanced Three-phase Circuits
 - ✓ Four Connections: Y - Y; Δ - Δ ; Y - Δ ; Δ - Y
- Power Calculations in Balanced Three-phase Circuits

1.1 OVERVIEW

An electric power distribution system:

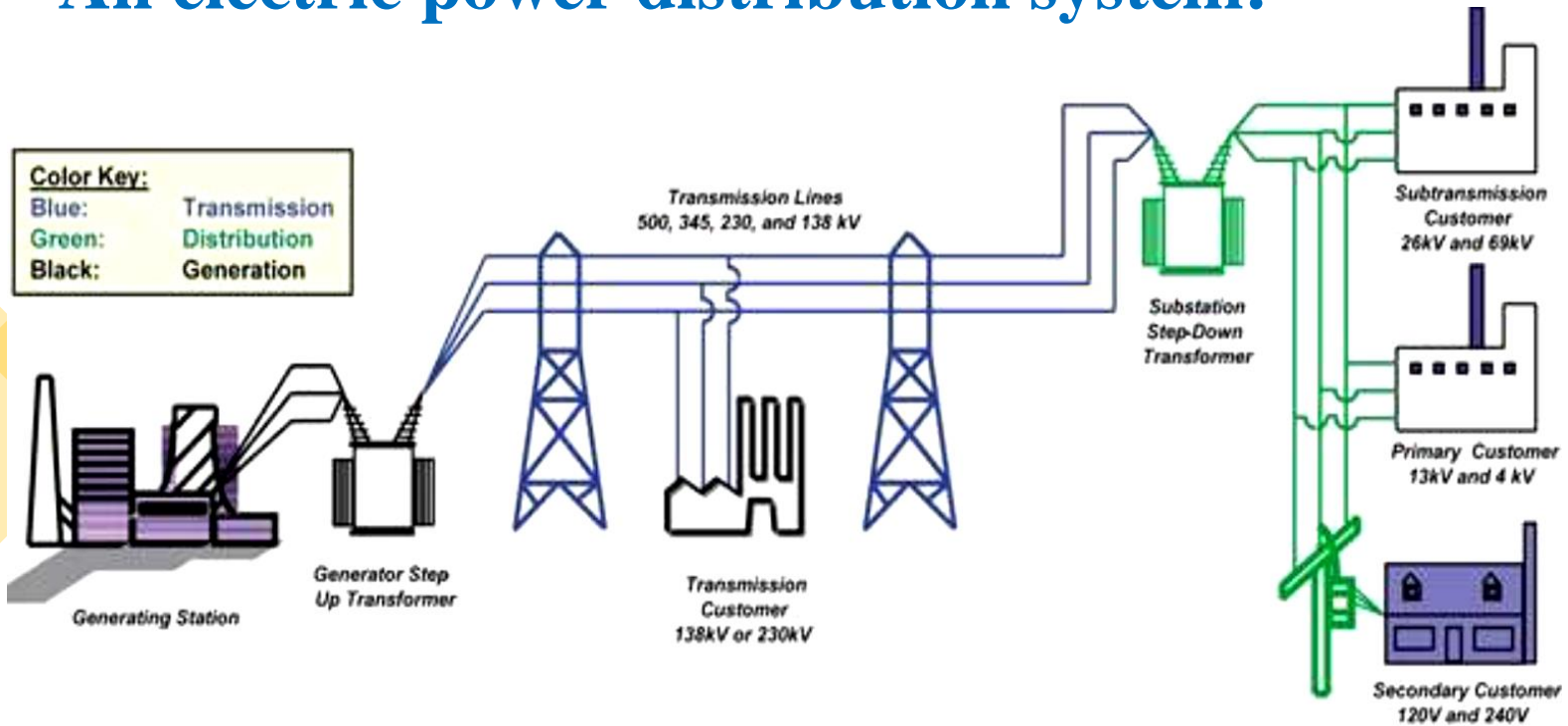

Generation, **Transmission**, and Distribution

Power transmission uses ‘**balanced three-phase**’ configuration



1.2 SINGLE-PHASE SUPPLY

Recall CAN102: One-phase ac generator

Static magnets, **one** rotating coil, **one** output voltage

The voltage induced by a single coil when it rotates in a magnetic field.

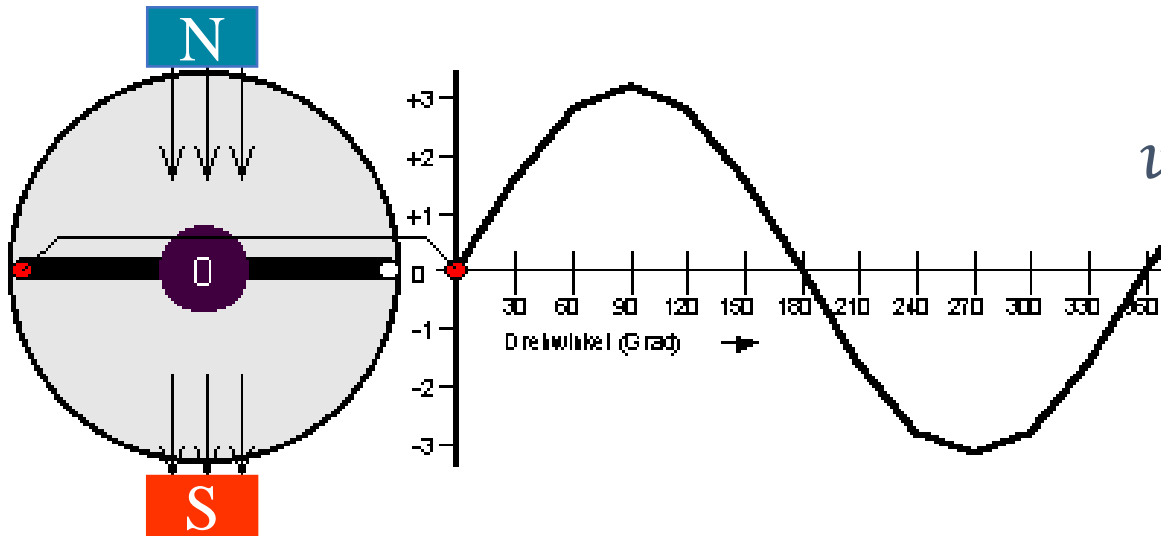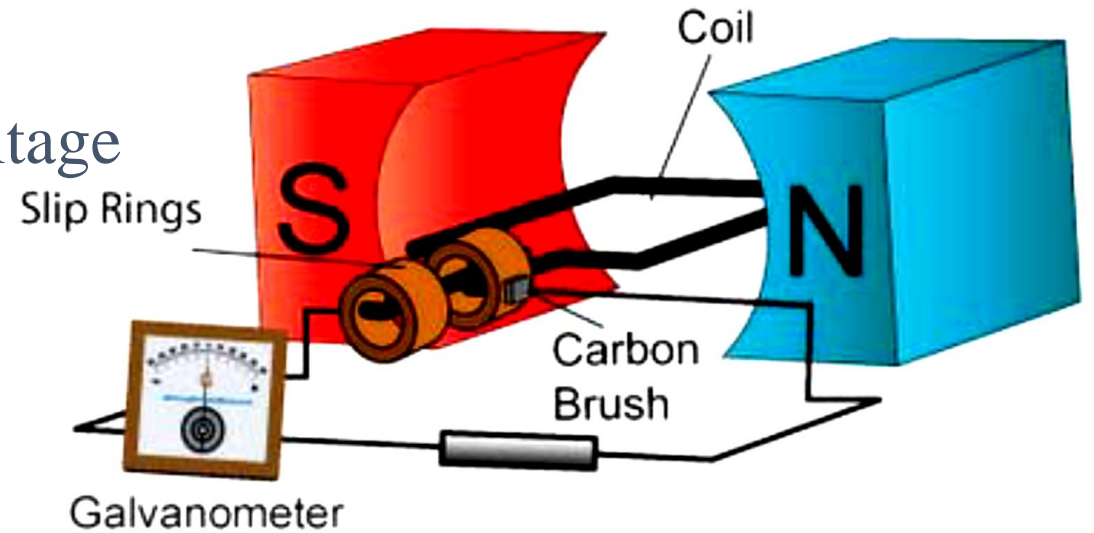All the voltages of the supply vary in unison.



$$v(t) = V_m \cos(\omega t + \theta)$$

$$V = V_m \angle \theta$$





Used mostly for lighting and heating (<10 or 20 kW).

1.3 THREE-PHASE SUPPLY

Polyphase: Circuits or systems where the ac sources operate at the **same frequency**, but with **different phases**.

Three-phase ac generator

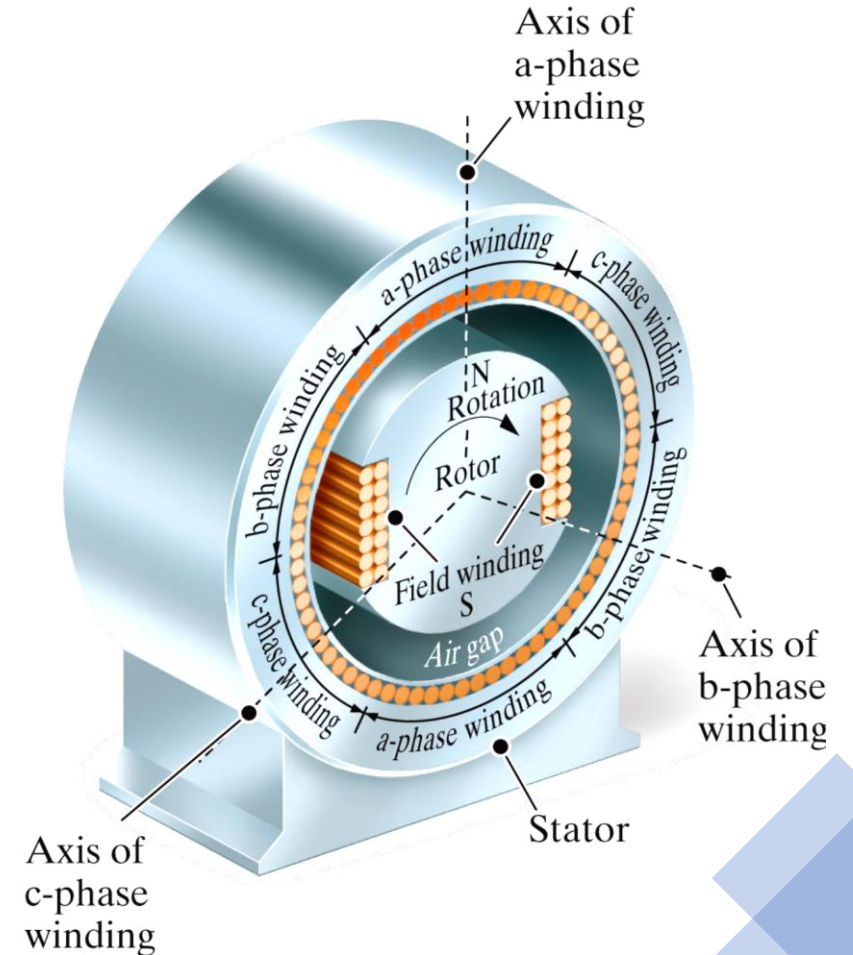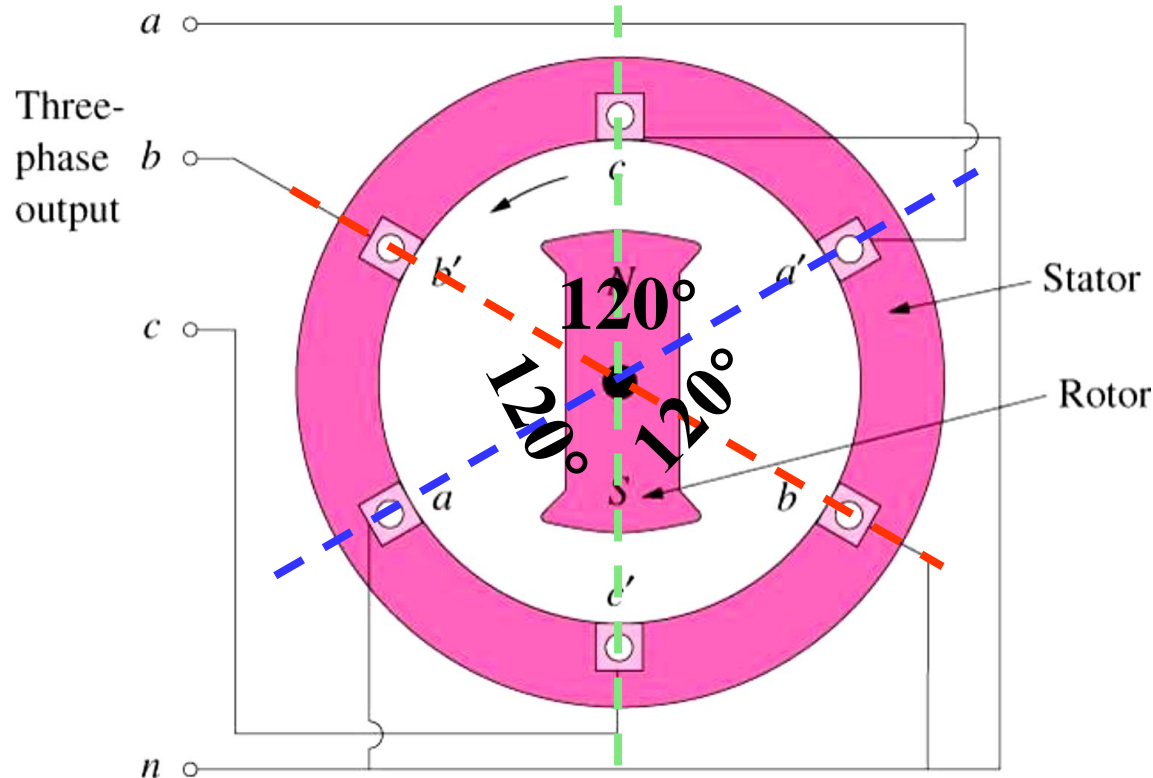Static coils, rotating magnets, **three** output voltages



1.3 THREE-PHASE SUPPLY


Three-phase Expression

Time domain:

$$v_a(t) = V_m \cos(\omega t)$$

$$v_b(t) = V_m \cos(\omega t - 120^\circ)$$
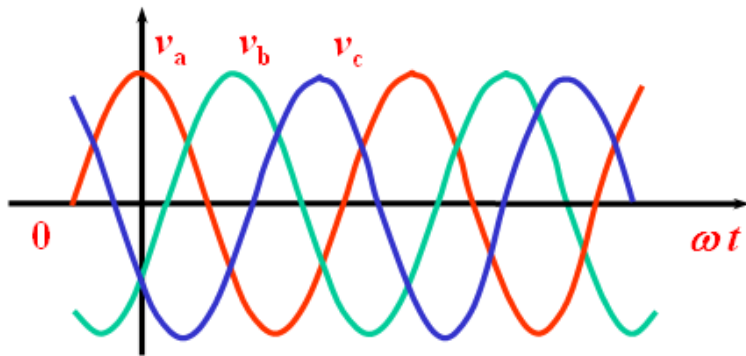
$$v_c(t) = V_m \cos(\omega t - 240^\circ) \\ = V_m \cos(\omega t + 120^\circ)$$




Phasor domain:

$$\mathbf{V}_a = V_m \angle 0^\circ$$

$$\mathbf{V}_b = V_m \angle (-120^\circ)$$
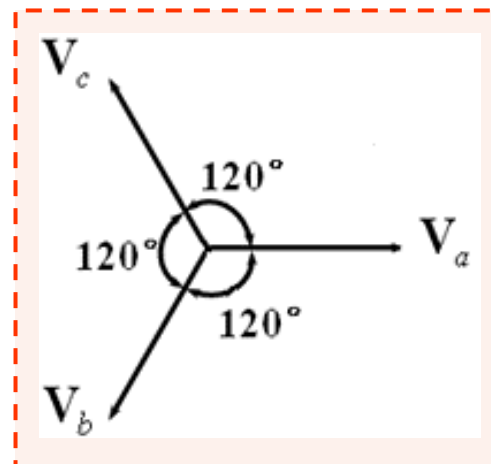
$$\mathbf{V}_c = V_m \angle (-240^\circ) \\ = V_m \angle 120^\circ$$



Phase Sequence

The phase sequence is the time order in which the voltages pass through their respective maximum values.


1. abc sequence (positive sequence) ★

Time-domain: $v_a + v_b + v_c = 0$

Phasor-domain: $\mathbf{V}_a + \mathbf{V}_b + \mathbf{V}_c = 0$

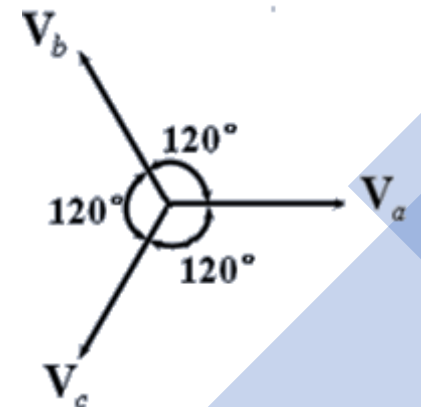2. acb sequence (negative sequence)

$$\left\{ \begin{array}{l} \mathbf{V}_a = V_m \angle 0^\circ \\ \mathbf{V}_c = V_m \angle (-120^\circ) \\ \mathbf{V}_b = V_m \angle (-240^\circ) \\ \quad = V_m \angle 120^\circ \end{array} \right.$$



OUTLINE

- Overview
 - ✓ Industrial Applications
 - ✓ Single-phase and Three-phase Supply
- **Balanced Three-phase Supply and Load**
 - ✓ **Y & Δ Connected Supply**
 - ✓ **Y & Δ Connected Load**
- Balanced Three-phase Circuits
 - ✓ Four Connections: Y - Y; Δ - Δ ; Y - Δ ; Δ - Y
- Power Calculations in Balanced Three-phase Circuits

OVERVIEW

A three-phase system consists of a **three-phase voltage source** that is used to supply a **three-phase load**.

Both the three-phase voltage source and the three-phase load can be connected in two different ways:

Source Connections

Wye (Y) Connected
(or Star Connected)

Delta (Δ) Connected
(or Mesh Connected)

Load Connections

Wye (Y) Connected
(or Star Connected)

Delta (Δ) Connected
(or Mesh Connected)

2.1 Y CONNECTED SOURCE: VOLTAGE

The **negative** ends of the three coils connected to form the **Y (star)** point.

The three remaining ends brought out to form the three terminals.

Phase voltage V_p : voltage across a single phase (line to neutral)



Line voltage V_L : voltage across any pair of lines (line to line)

For a **balanced** Y-connected source, the magnitude of line voltage is $\sqrt{3}$ times the magnitude of phase voltage:

$$V_L = \sqrt{3}V_p$$


where $V_p = |\vec{V}_{an}| = |\vec{V}_{bn}| = |\vec{V}_{cn}|$

$$V_L = |\vec{V}_{ab}| = |\vec{V}_{bc}| = |\vec{V}_{ca}|$$

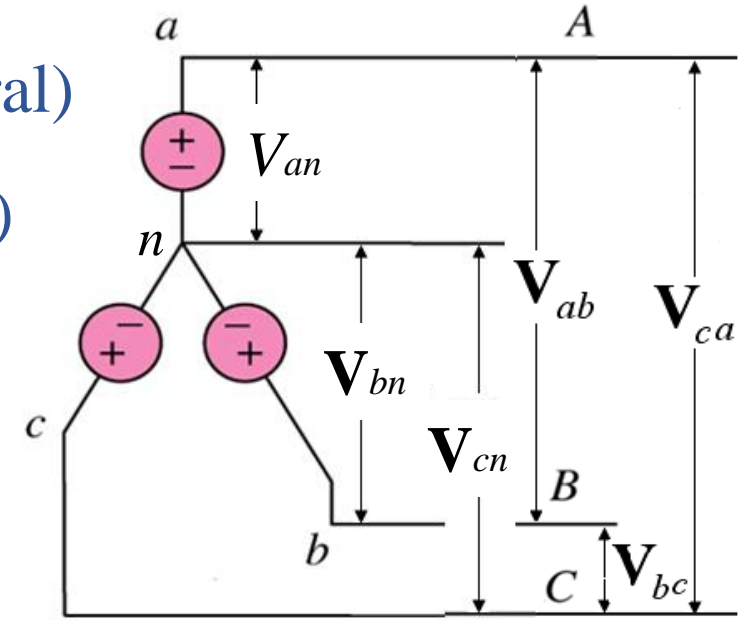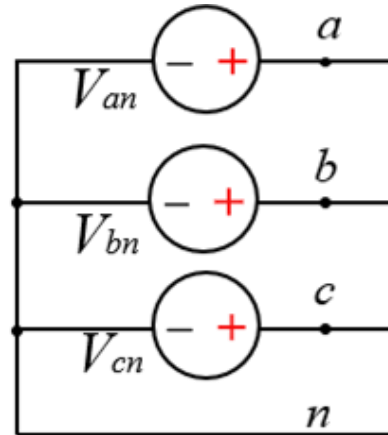

$$\vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn} = 0$$

* VERIFICATION

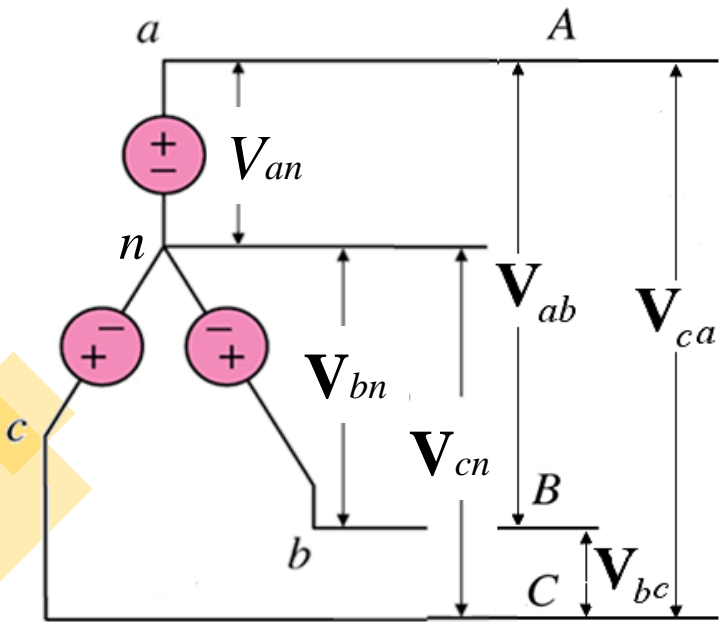

Phase voltages:


$$\vec{V}_{an} = V_m \angle 0^\circ$$

$$\vec{V}_{bn} = V_m \angle (-120^\circ)$$

$$\begin{aligned} \vec{V}_{cn} &= V_m \angle (-240^\circ) \\ &= V_m \angle 120^\circ \end{aligned}$$

$$\begin{aligned} \vec{V}_{ab} &= \vec{V}_{an} - \vec{V}_{bn} \\ &= V_m \angle 0^\circ - V_m \angle (-120^\circ) \\ &= V_m - [V_m \cos(-120^\circ) + jV_m \sin(-120^\circ)] \\ &= V_m \left(\frac{3}{2} + j \frac{\sqrt{3}}{2} \right) \\ &= \sqrt{3} V_m \left(\frac{\sqrt{3}}{2} + j \frac{1}{2} \right) \\ &= \sqrt{3} V_m [\cos(30^\circ) + j \sin(30^\circ)] \\ &= \sqrt{3} V_m \angle 30^\circ \end{aligned}$$

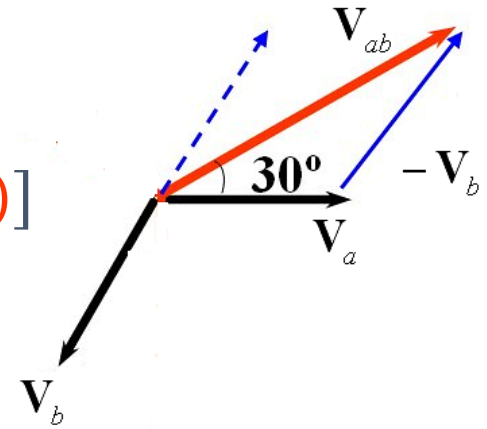the magnitude of line voltage is $\sqrt{3}$ times the magnitude of phase voltage



SUMMARY: VOLTAGE

For any **balanced** Y-connected sources, the magnitude of line voltage is $\sqrt{3}$ times the magnitude of phase voltage:

$$V_L = \sqrt{3}V_p$$


Each line-to-line voltage leads its corresponding phase voltage by 30° .

Phase voltages:


$$\vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn} = 0$$

Line voltages:
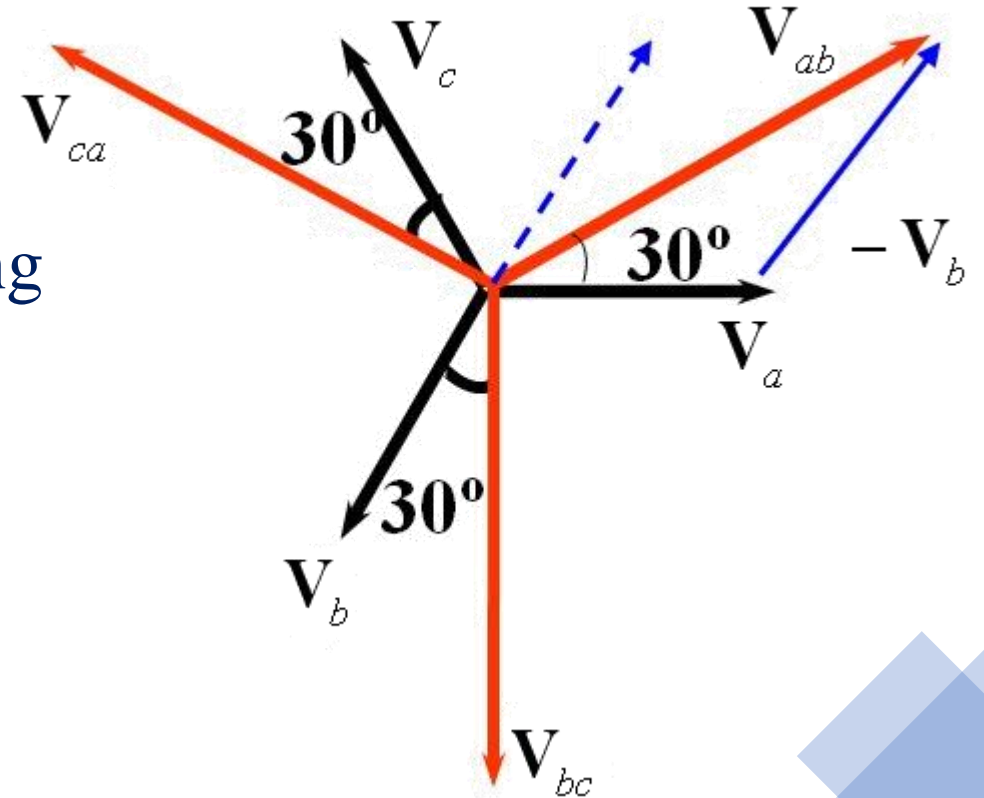
$$\vec{V}_{ab} + \vec{V}_{bc} + \vec{V}_{ca} = 0$$



2.1 Y CONNECTED SOURCE: CURRENT

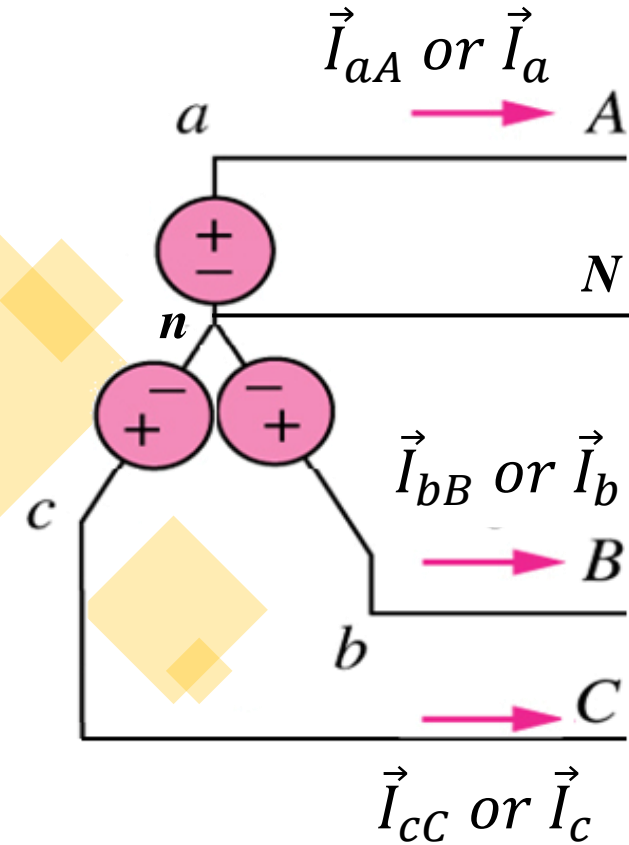

In a system with **balanced** Y-connected sources, **line** currents are the same as their related **phase** currents:

$$I_L = I_p$$


If the load is balanced as well, all line currents form a balanced set:

$$\vec{I}_{aA} = \vec{I}_{an} = \frac{\vec{V}_{an}}{Z} \quad \vec{I}_{bB} = \vec{I}_{bn} = \frac{\vec{V}_{bn}}{Z} \quad \vec{I}_{cC} = \vec{I}_{cn} = \frac{\vec{V}_{cn}}{Z}$$

If one current is known, the other 5 currents can be determined by inspection.

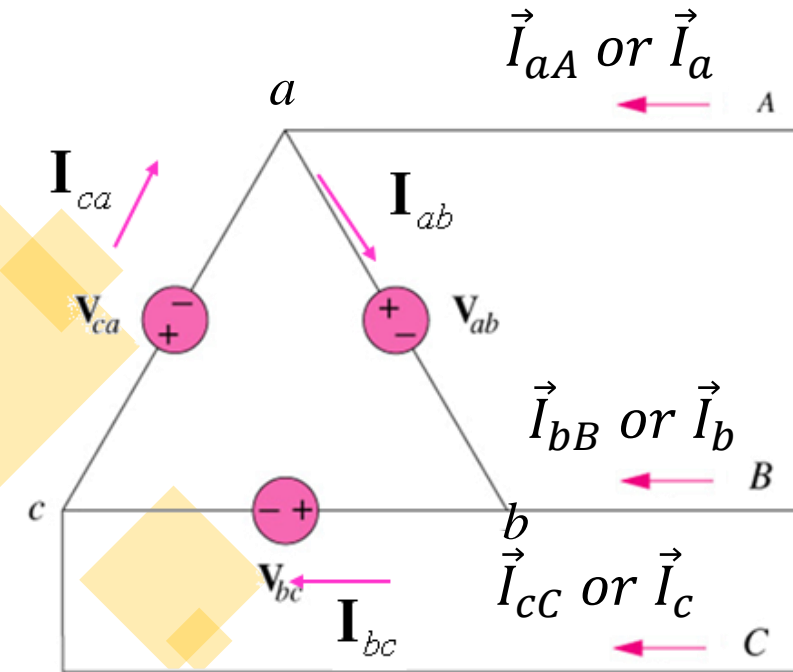2.2 Δ CONNECTED SOURCE: VOLTAGE

The end of one coil is connected to the start of the next coil to form the loop.



$$\begin{aligned}\vec{V}_{AB} &= \vec{V}_{ab} \\ \vec{V}_{BC} &= \vec{V}_{bc} \\ \vec{V}_{CA} &= \vec{V}_{ca}\end{aligned}$$


In a system with **balanced** Δ -connected sources, **line** voltage is the same as its related **phase** voltage:

$$V_L = V_p$$

where


$$V_p = |\vec{V}_{ab}| = |\vec{V}_{bc}| = |\vec{V}_{ca}|$$

$$V_L = |\vec{V}_{AB}| = |\vec{V}_{BC}| = |\vec{V}_{CA}|$$

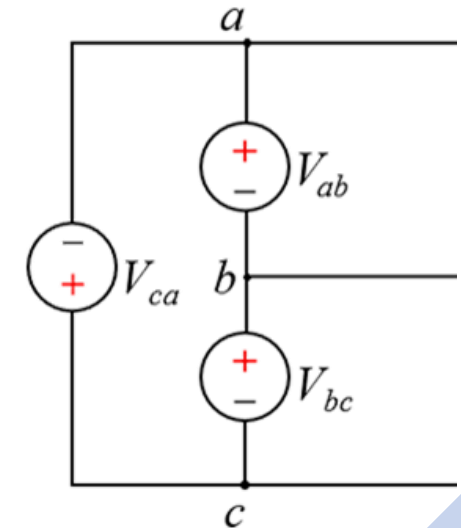

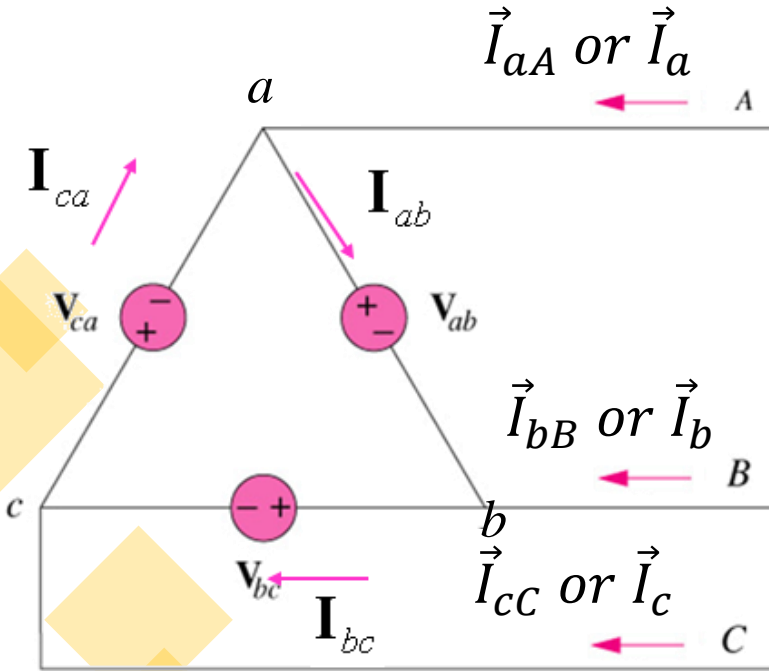2.2 Δ CONNECTED SOURCE: CURRENT

The end of one coil is connected to the start of the next coil to form the loop.




Line currents:

$$\vec{I}_{aA} = \vec{I}_{ab} - \vec{I}_{ca} = \sqrt{3}\vec{I}_{ab} \angle -30^\circ$$

$$\vec{I}_{bB} = \vec{I}_{bc} - \vec{I}_{ab} = \sqrt{3}\vec{I}_{bc} \angle -30^\circ$$
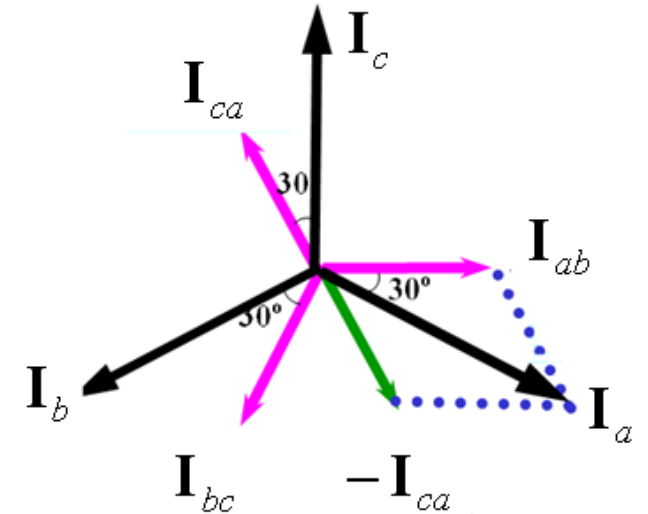
$$\vec{I}_{cC} = \vec{I}_{ca} - \vec{I}_{bc} = \sqrt{3}\vec{I}_{ca} \angle -30^\circ$$



For any **balanced** Δ -connected sources, the magnitude of line current is $\sqrt{3}$ times the magnitude of current voltage:

$$I_L = \sqrt{3}I_p$$


where

$$I_p = |\vec{I}_{ab}| = |\vec{I}_{bc}| = |\vec{I}_{ca}| \quad I_L = |\vec{I}_{aA}| = |\vec{I}_{bB}| = |\vec{I}_{cC}|$$

QUIZ 2.1

1. Which of the following expression is true for an “abc” sequenced three-phase motor with $\vec{V}_{an} = 220 \angle -100^\circ \text{V}$

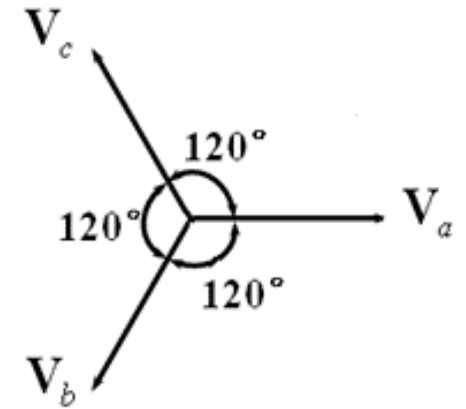- (a) $\vec{V}_{bn} = 220 \angle 140^\circ \text{V}$ (b) $\vec{V}_{cn} = 220 \angle (-20^\circ) \text{V}$





2. For a three-phase supply with the “abc” sequence, if $\vec{V}_{bn} = 220 \angle 140^\circ \text{V}$, which is the correct expression of \vec{V}_{ca} ?

- (a) $380 \angle 50^\circ \text{V}$ (b) $380 \angle (-130^\circ) \text{V}$
(c) $380 \angle 130^\circ \text{V}$ (d) $380 \angle 170^\circ \text{V}$



2.3 LOAD CONNECTIONS

Y Connection

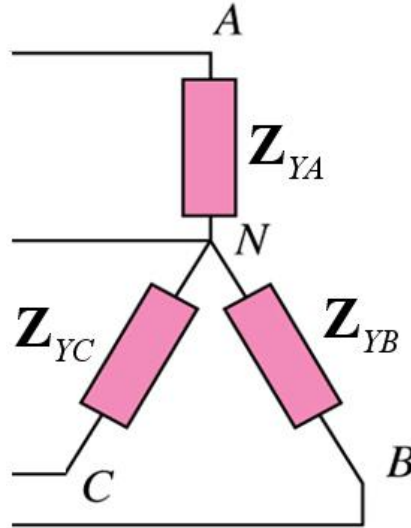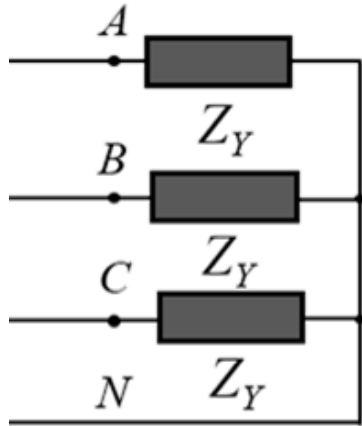

$$Z_Y = Z_{YA} = Z_{YB} = Z_{YC}$$

Δ Connection

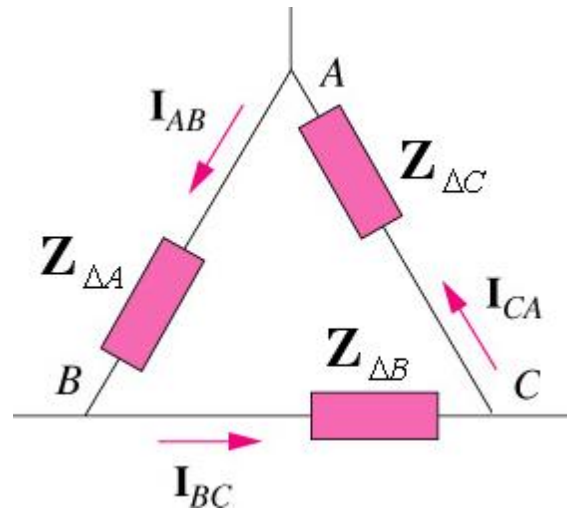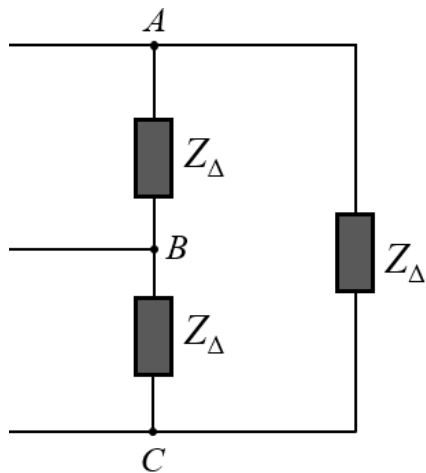

$$Z_{\Delta} = Z_{\Delta A} = Z_{\Delta B} = Z_{\Delta C}$$

$$Z_{\Delta} = 3Z_Y$$

$$Z_Y = \frac{Z_{\Delta}}{3}$$

2.4 COMBINATIONS

A three-phase system consists of a **three-phase voltage source** that is used to supply a **three-phase load**. Both the three-phase voltage source and the three-phase load can be connected in two different ways:

Source Connections


Wye (Y) Connected
(or star Connected)

Delta (Δ) Connected
(or Mesh Connected)

Load Connections

Wye (Y) Connected
(or star Connected)

Delta (Δ) Connected
(or Mesh Connected)

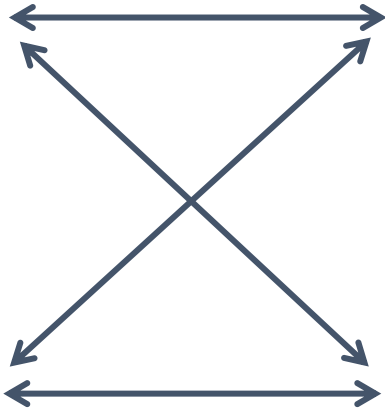


4 possible connections:

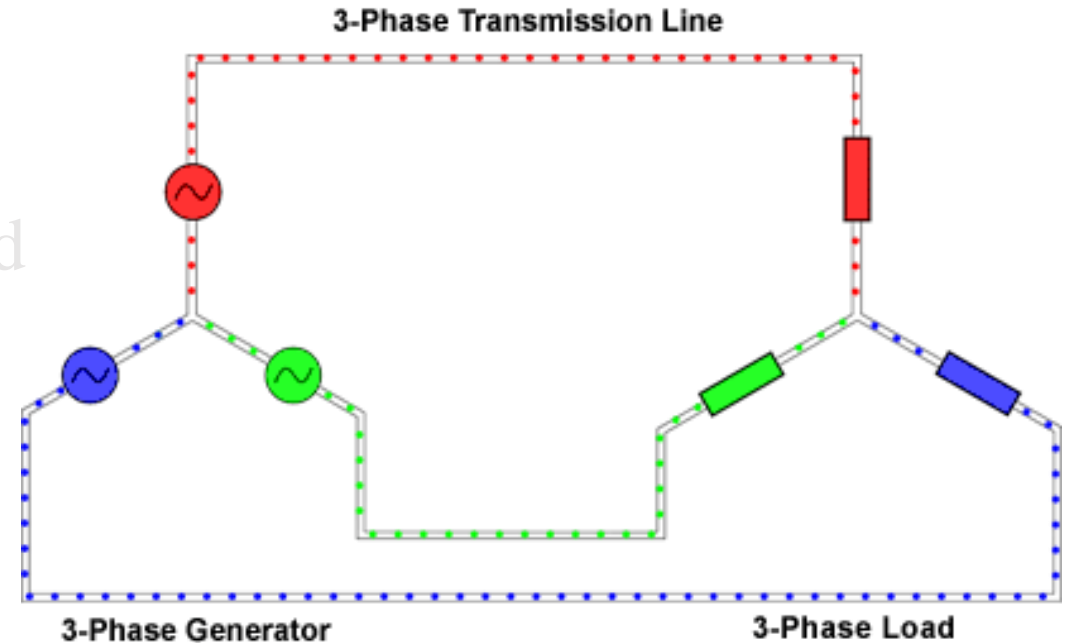1. Y-Y connection
2. Δ - Δ connection
3. Y- Δ connection
4. Δ -Y connection


OUTLINE

- Overview
 - ✓ Industrial Applications
 - ✓ Single-phase and Three-phase Supply
- Balanced Three-phase Supply and Load
 - ✓ Y & Δ Connected Supply
 - ✓ Y & Δ Connected Load
- **Balanced Three-phase Circuits**
 - ✓ **Four Connections: Y - Y; Δ - Δ ; Y- Δ ; Δ - Y**
- Power Calculations in Balanced Three-phase Circuits



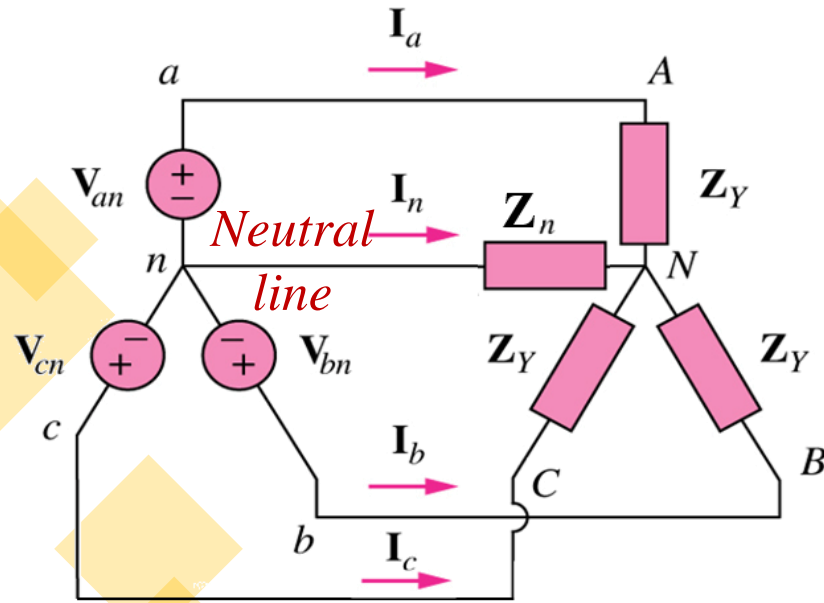3.1 Y - Y CONNECTIONS

A **balanced Y-Y** system is a three-phase system with a **balanced Y**-connected source and a **balanced Y**-connected load.




$$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{bn} &= V_p \angle (-120^\circ) \\ V_{cn} &= V_p \angle (-240^\circ) \end{aligned}$$

Phase
voltages

$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} = \sqrt{3}V_p \angle 30^\circ \\ V_{bc} &= V_{bn} - V_{cn} = \sqrt{3}V_p \angle (-90^\circ) \\ V_{ca} &= V_{cn} - V_{an} = \sqrt{3}V_p \angle (-210^\circ) \end{aligned}$$

Line
voltages

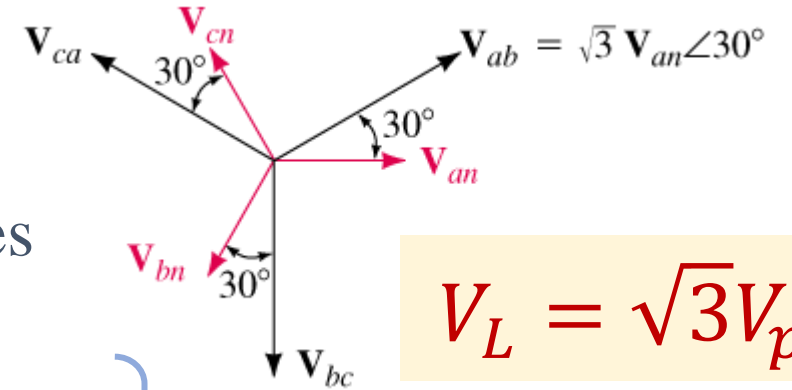

$$V_L = \sqrt{3}V_p$$

$$I_{Nn} = I_a + I_b + I_c = 0$$

$$V_{Nn} = Z_n I_{Nn} = 0$$

$$\begin{aligned} I_a &= \frac{V_{an}}{Z_Y} \\ I_b &= \frac{V_{bn}}{Z_Y} = \frac{V_{an} \angle (-120^\circ)}{Z_Y} = I_a \angle (-120^\circ) \\ I_c &= \frac{V_{cn}}{Z_Y} = \frac{V_{an} \angle (-240^\circ)}{Z_Y} = I_a \angle (-240^\circ) \end{aligned}$$


Line currents
Phase currents
on source & load

$$I_L = I_p$$

QUIZ 3.1

For a balanced Y-Y connection three-phase circuit, line voltage $V_{ab} = 380\angle 30^\circ \text{ V}$ and load $Z_Y = 100\angle 30^\circ \Omega$. The line impedance is zero.

Find expressions of all line currents.

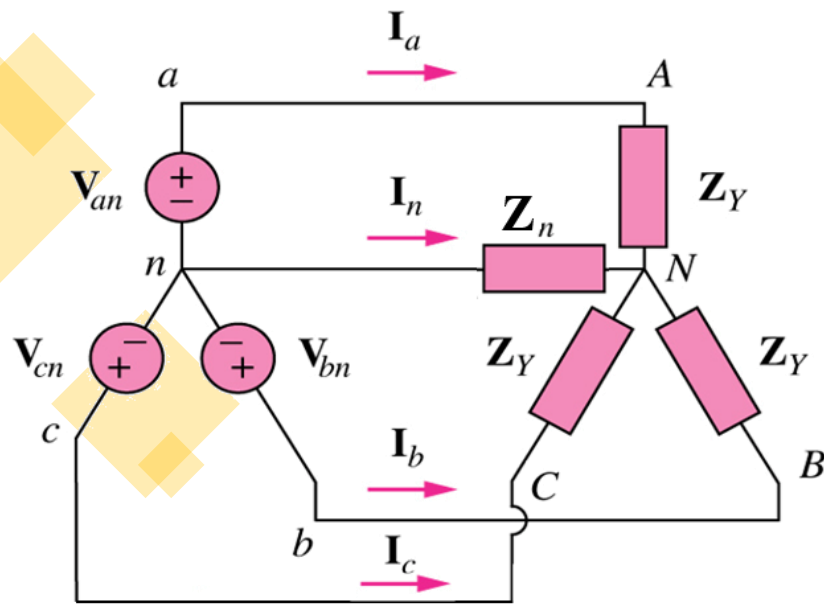


OUTLINE

- Overview
 - ✓ Industrial Applications
 - ✓ Single-phase and Three-phase Supply
- Balanced Three-phase Supply and Load
 - ✓ Y & Δ Connected Supply
 - ✓ Y & Δ Connected Load
- **Balanced Three-phase Circuits**
 - ✓ **Four Connections:** Y - Y; Δ - Δ ; Y - Δ ; Δ - Y
- Power Calculations in Balanced Three-phase Circuits

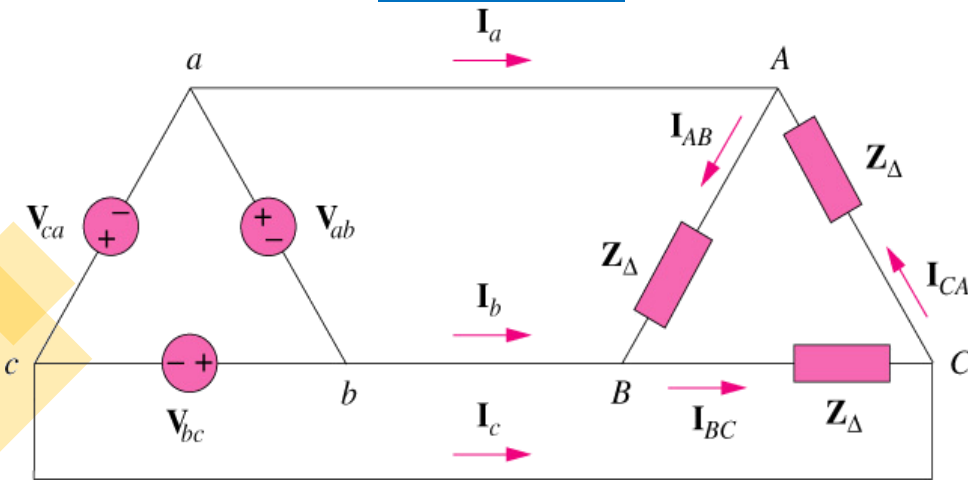3.2 Δ - Δ CONNECTIONS

A **balanced** Δ - Δ system is a three-phase system with a balanced Δ -connected source and a balanced Δ -connected load.



$$V_{ab} = V_p \angle 0^\circ$$

$$V_{bc} = V_p \angle (-120^\circ)$$

$$V_{ca} = V_p \angle (-240^\circ)$$

Phase
voltages

$$V_{ab} = V_{AB}$$

$$V_{bc} = V_{BC}$$

$$V_{ca} = V_{CA}$$

Line
voltages

$$V_L = V_p$$

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{V_{ab}}{Z_{\Delta}}$$

$$I_{BC} = \frac{V_{BC}}{Z_{\Delta}} = \frac{V_{bc}}{Z_{\Delta}}$$

$$I_{CA} = \frac{V_{CA}}{Z_{\Delta}} = \frac{V_{ca}}{Z_{\Delta}}$$

Phase currents
on loads

$$I_L = \sqrt{3} I_p$$

$$I_a = I_{AB} - I_{CA} = \sqrt{3} I_{AB} \angle (-30^\circ)$$

$$I_b = I_{BC} - I_{AB} = \sqrt{3} I_{AB} \angle (-150^\circ)$$

$$I_c = I_{CA} - I_{BC} = \sqrt{3} I_{AB} \angle (-270^\circ)$$

Line currents

where


$$I_L = |I_a| = |I_b| = |I_c|$$

$$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

QUIZ 3.2

A balanced Δ -connected load having an impedance $Z_{\Delta} = 20 - j15 \, \Omega$ is connected to a balanced Δ -connected positive-sequence generator having $V_{ab} = 330 \angle 0^\circ \text{ V}$.

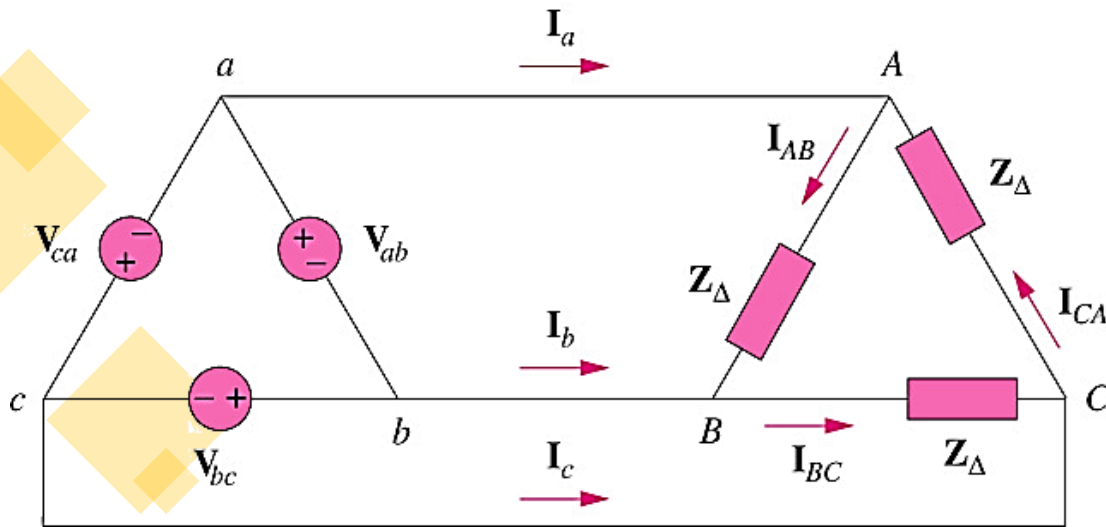Calculate the **phase currents of the load** and the **line currents for the system**.




OUTLINE

- Overview
 - ✓ Industrial Applications
 - ✓ Single-phase and Three-phase Supply
- Balanced Three-phase Supply and Load
 - ✓ Y & Δ Connected Supply
 - ✓ Y & Δ Connected Load
- **Balanced Three-phase Circuits**
 - ✓ **Four Connections:** Y - Y; Δ - Δ ; **Y - Δ** ; Δ - Y
- Power Calculations in Balanced Three-phase Circuits

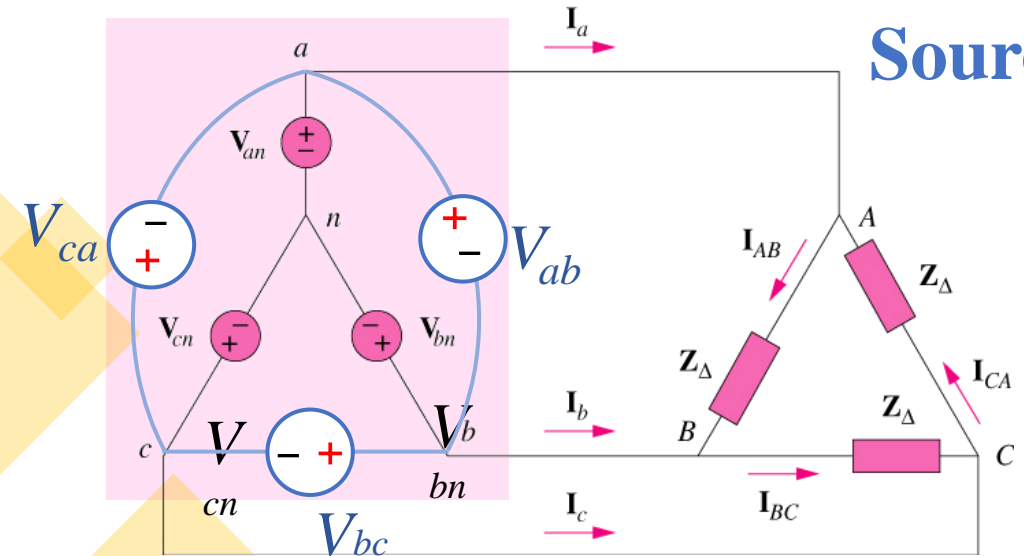3.3 ONE OPTION

A **balanced** Y- Δ system is a three-phase system with a **balanced** Y-connected source and a **balanced** Δ -connected load.



Source Y \rightarrow Δ :

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3}V_p \angle 30^\circ = V_{AB}$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3}V_p \angle (-90^\circ) = V_{BC}$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3}V_p \angle (-210^\circ) = V_{CA}$$

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}}$$

$$I_{BC} = \frac{V_{BC}}{Z_{\Delta}}$$

$$I_{CA} = \frac{V_{CA}}{Z_{\Delta}}$$

Phase currents
on loads

$$I_L = \sqrt{3}I_p$$

$$I_a = I_{AB} - I_{CA} = \sqrt{3}I_{AB} \angle (-30^\circ)$$

$$I_b = I_{BC} - I_{AB} = \sqrt{3}I_{AB} \angle (-150^\circ)$$

$$I_c = I_{CA} - I_{BC} = \sqrt{3}I_{AB} \angle (-270^\circ)$$

Line currents

$$V_{an} = V_p \angle 0^\circ$$


$$V_{bn} = V_p \angle (-120^\circ)$$

$$V_{cn} = V_p \angle (-240^\circ)$$

Phase
voltages

QUIZ 3.3

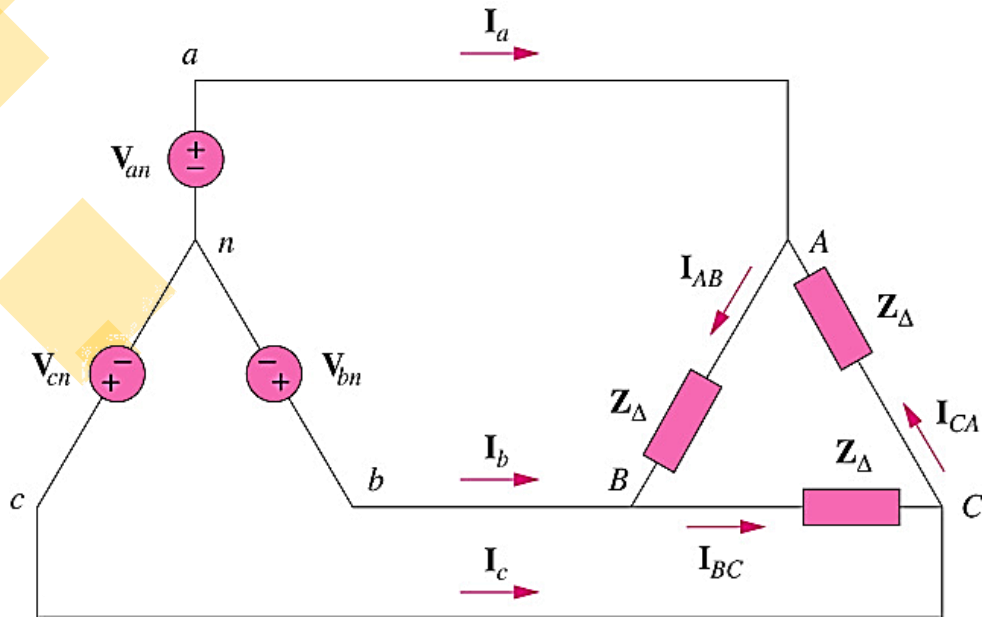A three-phase system with a balanced Y-connected source of line voltage 415 V supplies a balanced *delta*-connected load. The load is purely resistive of $10\ \Omega$ resistance per phase. Calculate the magnitude of currents of this system.



OUTLINE

➤ Overview

- ✓ Industrial Applications
- ✓ Single-phase and Three-phase Supply

➤ Balanced Three-phase Supply and Load

- ✓ Y & Δ Connected Supply
- ✓ Y & Δ Connected Load

➤ Balanced Three-phase Circuits

- ✓ Four Connections: Y - Y; Δ - Δ ; Y - Δ ; Δ - Y

➤ Power Calculations in Balanced Three-phase Circuits


3.4 Δ - Y CONNECTIONS

A **balanced** Δ - Y system is a three-phase system with a balanced Δ -source and a balanced Y -connected connected load.


$$\left. \begin{aligned} \mathbf{V}_{ab} &= V_p \angle 0^\circ \\ \mathbf{V}_{bc} &= V_p \angle (-120^\circ) \\ \mathbf{V}_{ca} &= V_p \angle (-240^\circ) \end{aligned} \right\} \text{Phase voltages}$$

Source $\Delta \rightarrow Y$:
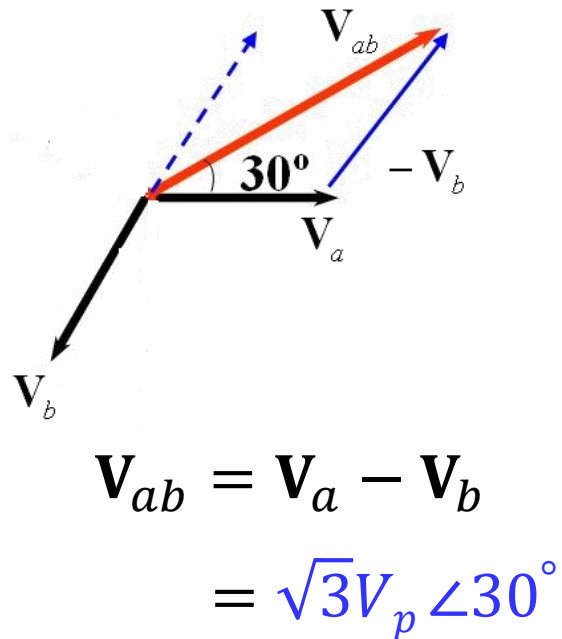
$$\left\{ \begin{aligned} \mathbf{V}_{an} &= \frac{1}{\sqrt{3}} V_p \angle (-30^\circ) \\ \mathbf{V}_{bn} &= \frac{1}{\sqrt{3}} V_p \angle (-150^\circ) \\ \mathbf{V}_{cn} &= \frac{1}{\sqrt{3}} V_p \angle (-270^\circ) \end{aligned} \right.$$



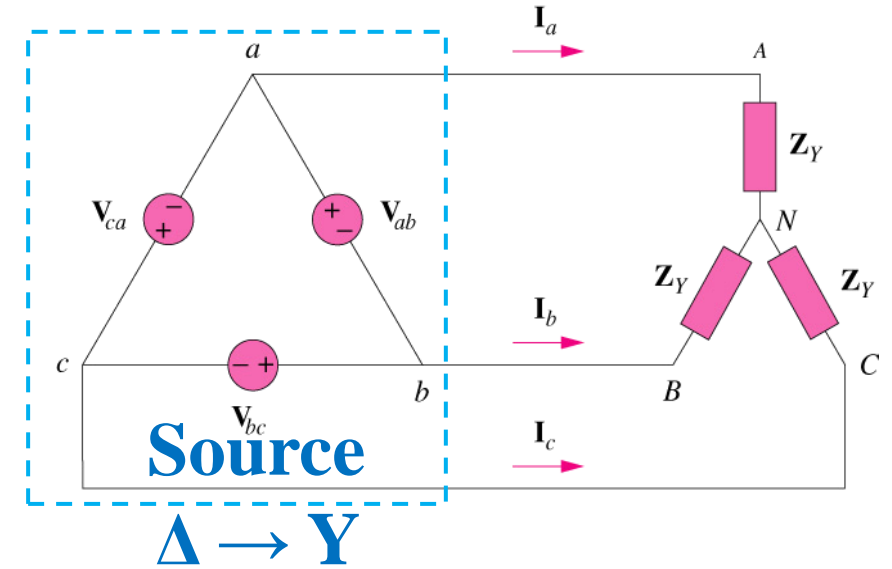
$$\begin{aligned} \mathbf{V}_{ab} &= \mathbf{V}_a - \mathbf{V}_b \\ &= \sqrt{3} V_p \angle 30^\circ \end{aligned}$$



$$\left\{ \begin{aligned} \mathbf{I}_a &= \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y} \\ \mathbf{I}_b &= \frac{\mathbf{V}_{bn}}{\mathbf{Z}_Y} = \mathbf{I}_a \angle (-120^\circ) \\ \mathbf{I}_c &= \frac{\mathbf{V}_{cn}}{\mathbf{Z}_Y} = \mathbf{I}_a \angle (-240^\circ) \end{aligned} \right\} \text{Line currents}$$

QUIZ 3.4

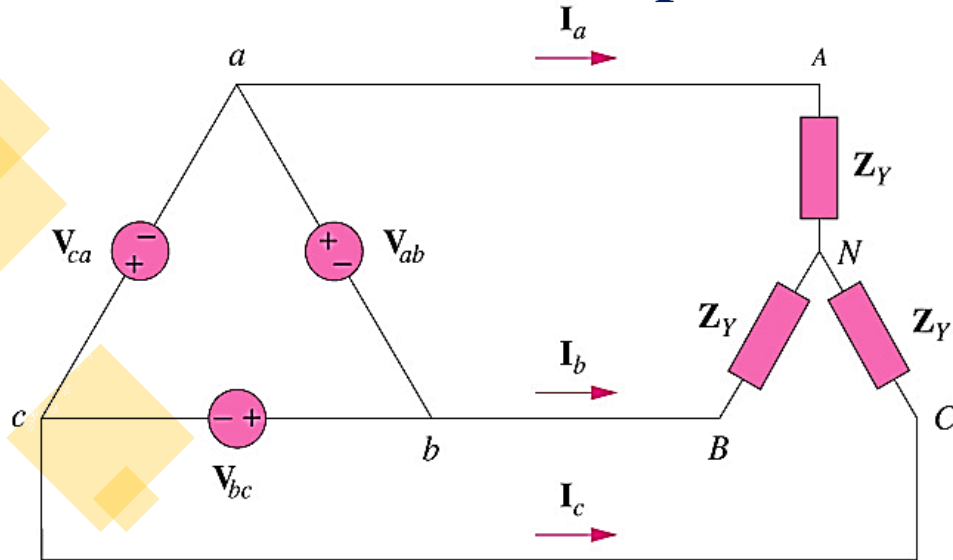A balanced Y-connected load with a phase impedance $40 + j25 \, \Omega$ is supplied by a balanced, positive-sequence Δ -connected source with a line voltage $\mathbf{V}_{ab} = 210 \, \text{V}$. Calculate the phase currents of loads (use \mathbf{V}_{ab} as reference).



SUMMARY

Connection	Phase Voltage	Phase Current	Line Voltage	Line Current
balanced Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle (-120^\circ)$ $V_{cn} = V_p \angle (-240^\circ)$	$I_L = I_p$	$V_{ab} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle (-120^\circ)$ $V_{ca} = V_{ab} \angle 120^\circ$	$I_a = \frac{V_{an}}{Z_Y}$ $I_b = I_a \angle (-120^\circ)$ $I_c = I_a \angle (-240^\circ)$
balanced Δ - Δ	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle (-120^\circ)$ $V_{ca} = V_p \angle (-240^\circ)$	$I_{AB} = V_{AB}/Z_\Delta$ $I_{BC} = V_{BC}/Z_\Delta$ $I_{CA} = V_{CA}/Z_\Delta$	$V_L = V_p$	$I_a = \sqrt{3}I_{AB} \angle (-30^\circ)$ $I_b = I_a \angle (-120^\circ)$ $I_c = I_a \angle (-240^\circ)$
balanced Y- Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle (-120^\circ)$ $V_{cn} = V_p \angle (-240^\circ)$	$I_{AB} = V_{AB}/Z_\Delta$ $I_{BC} = V_{BC}/Z_\Delta$ $I_{CA} = V_{CA}/Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle (-120^\circ)$ $V_{ca} = V_{CA} = V_{ab} \angle (-240^\circ)$	$I_a = \sqrt{3}I_{AB} \angle (-30^\circ)$ $I_b = I_a \angle (-120^\circ)$ $I_c = I_a \angle (-240^\circ)$
balanced Δ -Y	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle (-120^\circ)$ $V_{ca} = V_p \angle (-240^\circ)$	$I_L = I_p$	$V_{ab} = \sqrt{3} V_{Y-an} \angle 30^\circ$ $V_{bc} = V_{ab} \angle (-120^\circ)$ $V_{ca} = V_{ab} \angle (-240^\circ)$	$I_a = \frac{V_{an}}{Z_Y}$ $I_b = I_a \angle (-120^\circ)$ $I_c = I_a \angle (-240^\circ)$

QUIZ 3.5

1. In a **Y-connected** load, the line current and phase current on the load are equal.

(a) true

(b) false


2. In a **Δ - Δ** system, a phase voltage of 100 V produces a line voltage of:

(a) 100 V

(b) 141 V

(c) 71 V

(d) 173 V

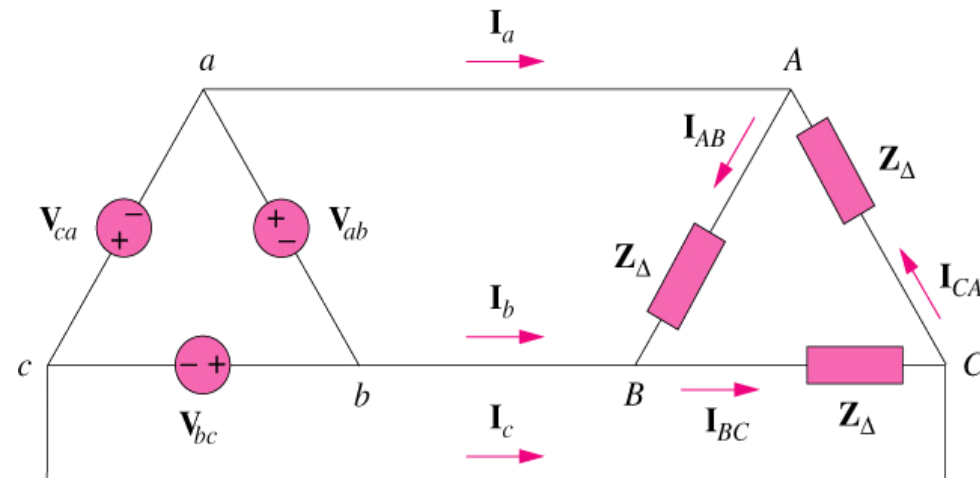

OUTLINE

- Overview
 - ✓ Industrial Applications
 - ✓ Single-phase and Three-phase Supply
- Balanced Three-phase Supply and Load
 - ✓ Y & Δ Connected Supply
 - ✓ Y & Δ Connected Load
- Balanced Three-phase Circuits
 - ✓ Four Connections: Y-Y; Δ - Δ ; Y - Δ ; Δ - Y
- **Power Calculations** in Balanced Three-phase Circuits

RECALL EEE103...

Voltage: $v(t) = V_m \cos(\omega t + \theta_v)$

Current: $i(t) = I_m \cos(\omega t + \varphi_i)$

Absorbed Instantaneous Power:

$$\begin{aligned} p(t) &= v(t)i(t) \\ &= V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \varphi_i) \\ &= \frac{1}{2} V_m I_m \cos(\theta_v - \varphi_i) \\ &\quad + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \varphi_i) \end{aligned}$$

Absorbed Average Power:

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta_v - \varphi_i) \frac{1}{T} \int_0^T dt + \frac{1}{T} \int_0^T \left(\frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \varphi_i) \right) dt \\ &= \frac{1}{2} V_m I_m \cos(\theta_v - \varphi_i) = V_{rms} I_{rms} \cos(\theta_v - \varphi_i) \quad V_{rms} = \frac{V_m}{\sqrt{2}} \quad I_{rms} = \frac{I_m}{\sqrt{2}} \end{aligned}$$

Instantaneous Power:

the rate at which an element absorbs energy.

$$p(t) = v(t)i(t)$$

Average Power (Real Power):


the average of the instantaneous power over one period.

$$P = \frac{1}{T} \int_0^T p(t) dt$$

RECALL EEE103...

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \varphi_i) = V_{rms} I_{rms} \cos(\theta_v - \varphi_i)$$


Pure resistive

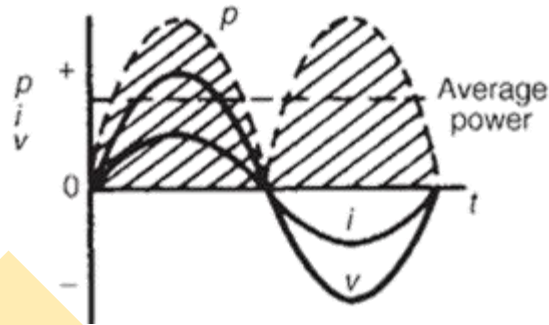

v, i in phase

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \varphi_i)$$
$$= \frac{1}{2} V_m I_m$$


Pure inductive

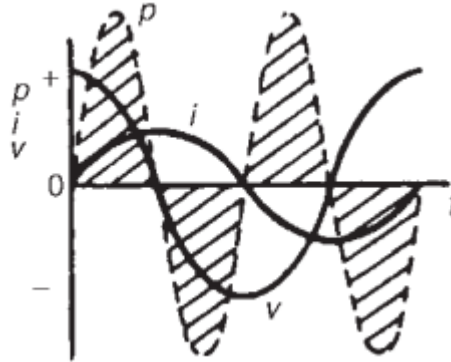

v leads i

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \varphi_i)$$
$$= \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

Pure capacitive

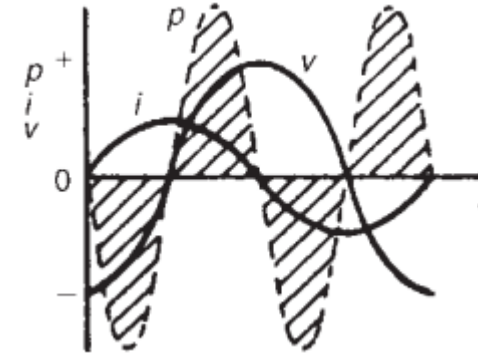

i leads v

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \varphi_i)$$
$$= \frac{1}{2} V_m I_m \cos(-90^\circ) = 0$$

A pure *reactive* element absorbs **zero average power.**

RECALL EEE103...

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \varphi_i) = V_{rms} I_{rms} \cos(\theta_v - \varphi_i) = S \cos(\theta_v - \varphi_i)$$

Apparent Power:

the product of the effective (*rms*) values of voltage and current

$$S = V_{rms} I_{rms} = V_{eff} I_{eff} \text{ VA}$$

Power Factor (*pf*): $\cos(\theta_v - \varphi_i)$

Power Factor Angle: $\phi = \theta_v - \varphi_i$

the phase difference between the voltage and current applied across an element, which is the angle of the load as well.

$$pf = \frac{\text{Average Power } P}{\text{Apparent Power } S} = \cos \phi$$

pf can be treated as the factor by which the apparent power must be multiplied to obtain the real power.

RECALL EEE103...

Considering a complex load $Z = R + jX$, the absorbed power is called the **complex power \mathbf{S}** (the product of the *rms* voltage phasor and the complex conjugate of the current phasor):

$$\mathbf{S} = \mathbf{V}_{rms} \mathbf{I}_{rms}^* = \boxed{V_{rms} I_{rms}} \angle (\theta_v - \phi_i) = \boxed{V_{rms} I_{rms} \cos(\theta_v - \phi_i)} + j \boxed{V_{rms} I_{rms} \sin(\theta_v - \phi_i)}$$

Complex Power

Apparent Power S
(VA)

Average (Real) Power P
(W)

Reactive Power Q
(var)

$S = |\mathbf{S}|$ magnitude of complex power

$$\text{Complex Power} = \mathbf{S} = P + jQ = \frac{1}{2} \mathbf{V} \mathbf{I}^*$$

$$= V_{rms} I_{rms} \angle (\theta_v - \phi_i)$$

$$\text{Apparent Power} = S = |\mathbf{S}| = V_{rms} I_{rms} = \sqrt{P^2 + Q^2}$$


$$\text{Real Power} = P = \text{Re}(\mathbf{S}) = S \cos(\theta_v - \phi_i)$$

$$\text{Reactive Power} = Q = \text{Im}(\mathbf{S}) = S \sin(\theta_v - \phi_i)$$

$$\text{Power Factor} = \frac{P}{S} = \cos(\theta_v - \phi_i)$$


\therefore the angle of the *pf* equals the angle of the load

$$\begin{aligned} \therefore \mathbf{S} &= \mathbf{V}_{rms} \mathbf{I}_{rms}^* = (Z I_{rms}) \mathbf{I}_{rms}^* \\ &= I_{rms}^2 Z = I_{rms}^2 (R + jX) \\ &= P + jQ \end{aligned}$$

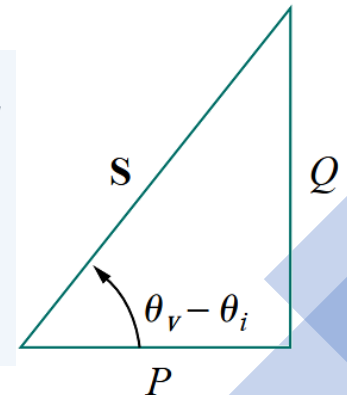

QUIZ 4.1

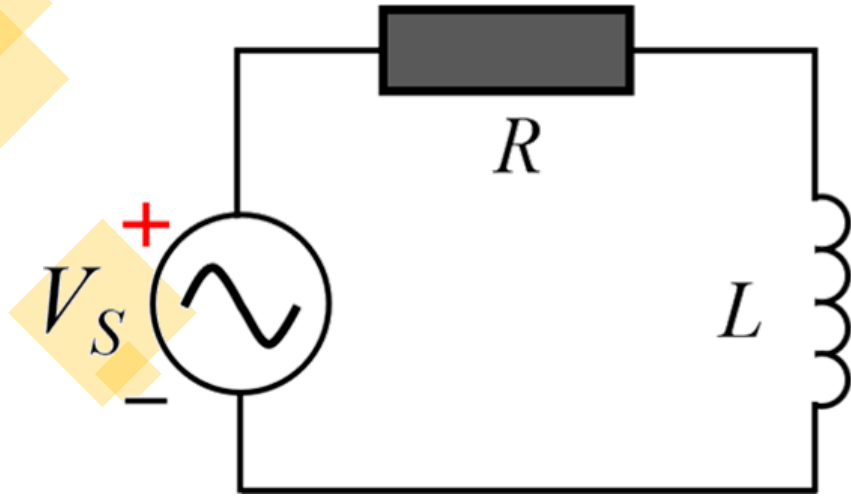
A series circuit of resistance $60\ \Omega$ and inductance $75\ \text{mH}$ is connected to a 110V , $60\ \text{Hz}$ supply. Calculate the power dissipated on the load and the power factor pf .



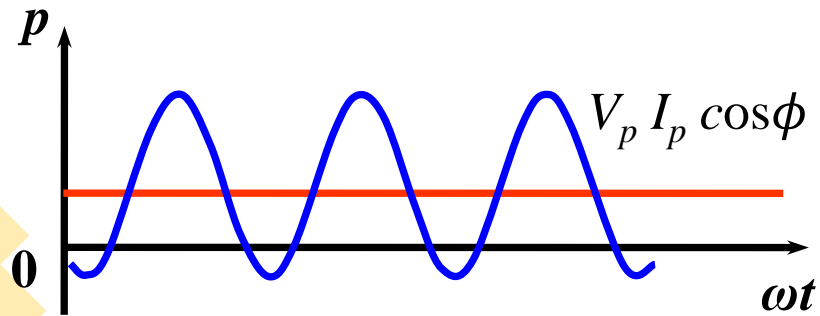4.1 IN THREE-PHASE SYSTEM

The power in a three-phase system is the **sum** of the power in each phase.

3 kinds of power used by power engineers: **Real power**, **Apparent power** & **Reactive power**



The instantaneous phase power is a function of time

$$\left. \begin{aligned} v_A(t) &= \sqrt{2}V_{rms} \cos \omega t \\ i_A(t) &= \sqrt{2}I_{rms} \cos(\omega t - \phi) \end{aligned} \right\} \text{Phase A}$$

$$\begin{aligned} p_A &= v_A i_A = 2V_{rms}I_{rms} \cos \omega t \cos(\omega t - \phi) \\ &= V_{rms}I_{rms} \cos \phi + V_{rms}I_{rms} \cos(2\omega t - \phi) \end{aligned}$$

Similarly:

$$p_B = v_B i_B = V_{rms}I_{rms} \cos \phi + V_{rms}I_{rms} \cos[2(\omega t - 120^\circ) - \phi]$$

$$p_C = v_C i_C = V_{rms}I_{rms} \cos \phi + V_{rms}I_{rms} \cos[2(\omega t + 120^\circ) - \phi]$$

Total Instantaneous Power:

$$p = p_A + p_B + p_C = 3V_{rms}I_{rms} \cos \phi = P$$

The **total** instantaneous power is *independent* of time

4.1 IN THREE-PHASE SYSTEM

Average (Real) Power P

Y connected

$$\left. \begin{array}{l} V_L = \sqrt{3}V_p \\ I_L = I_p \end{array} \right\} \begin{array}{l} P_{phase} = V_p I_p \cos \phi = \frac{1}{\sqrt{3}} V_L I_L \cos \phi \\ \therefore P_t = 3P_{phase} = \sqrt{3} V_L I_L \cos \phi \end{array}$$

Δ connected


$$\left. \begin{array}{l} V_L = V_p \\ I_L = \sqrt{3}I_p \end{array} \right\} \begin{array}{l} P_{phase} = V_p I_p \cos \phi = \frac{1}{\sqrt{3}} V_L I_L \cos \phi \\ \therefore P_t = 3P_{phase} = \sqrt{3} V_L I_L \cos \phi \end{array}$$

Independent on the connection methods

V_p, I_p : effective values (*rms*)

Complex Power:

$$S = P + jQ = 3V_p I_p^*$$

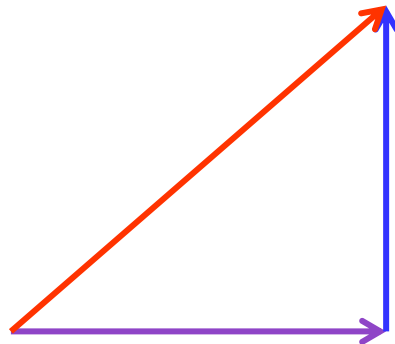

$$P = \sqrt{3} V_L I_L \cos \phi = 3V_p I_p \cos \phi$$


$$Q = \sqrt{3} V_L I_L \sin \phi = 3V_p I_p \sin \phi$$

$$S = \sqrt{3} V_L I_L = 3V_p I_p$$

QUIZ 4.2


A three-phase motor can be regarded as a **balanced Y-load**. A three-phase motor draws 5.6 kW when the effective value of the line voltage is 220 V_{rms} and the effective value of the line current is 18.2 A_{rms} .

Find the power factor pf of the motor.

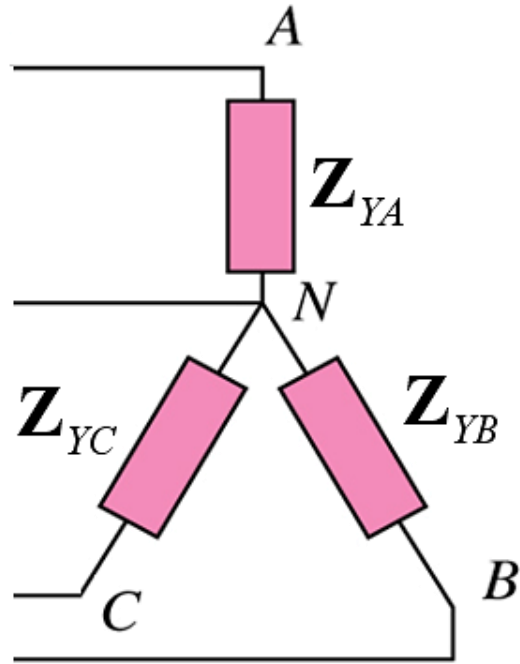

QUIZ 4.3

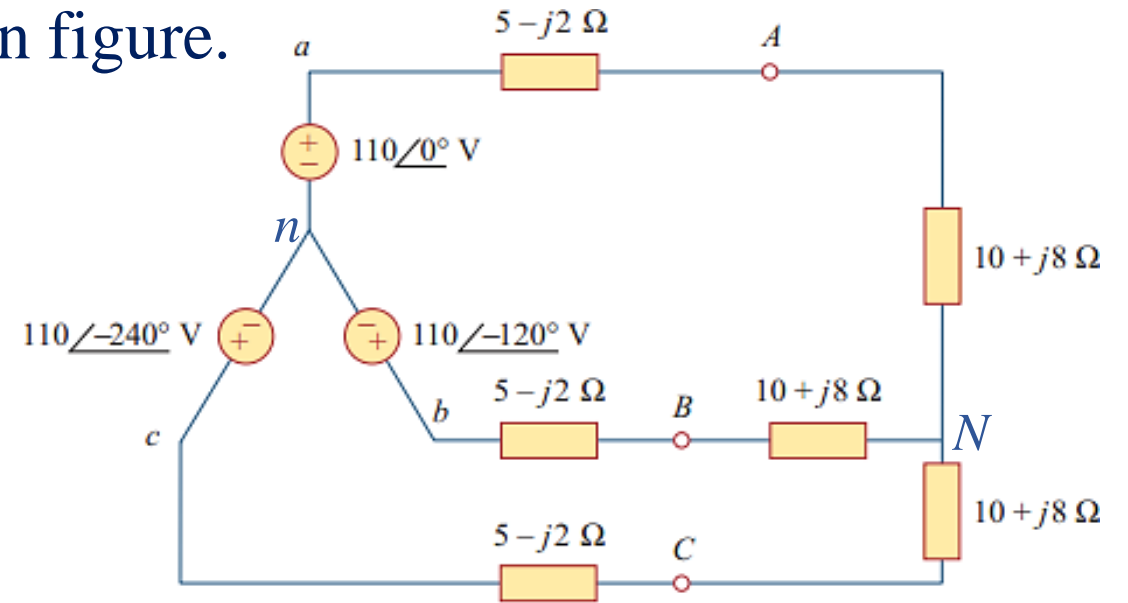Determine the total average power P , reactive power Q , and complex power S at the source, at the line, and at the load for the given figure.



*WHY STUDY THREE-PHASE SYSTEM?

- ALL electric power system in the world used 3-phase system to generate, transmit, and distribute
 - ✓ One phase, two phase, or three phase current can be taken from three phase system rather than generated independently.
- Instantaneous power can be constant (not pulsating) – smoother rotation of electrical machines
 - ✓ High power motors prefer a steady torque
- More economical than single phase – less wires for the same power transfer
 - ✓ The amount of wire required for a three-phase system is less than required for an equivalent single-phase system.

NEXT...



Tutorial & Revision

