

Lecture 9
of
EEE201

CMOS Digital Integrated Circuits

Department of Electrical & Electronic Engineering
Xi'an Jiaotong-Liverpool University (XJTLU)

Monday, 04th November 2024

□ Drawing CMOS IC Layout

- CMOS inverter: schematic to device structure
- seven mask layers
- drawing each mask layer to give the layout




CMOS Inverter

(from schematic design to device structures on wafer)

- ❑ To make the CMOS inverter (and in general CMOS digital ICs), the *p*MOSFET and *n*MOSFET fabrication on a silicon wafer need to be well-defined by a set of mask layers in the IC layout.

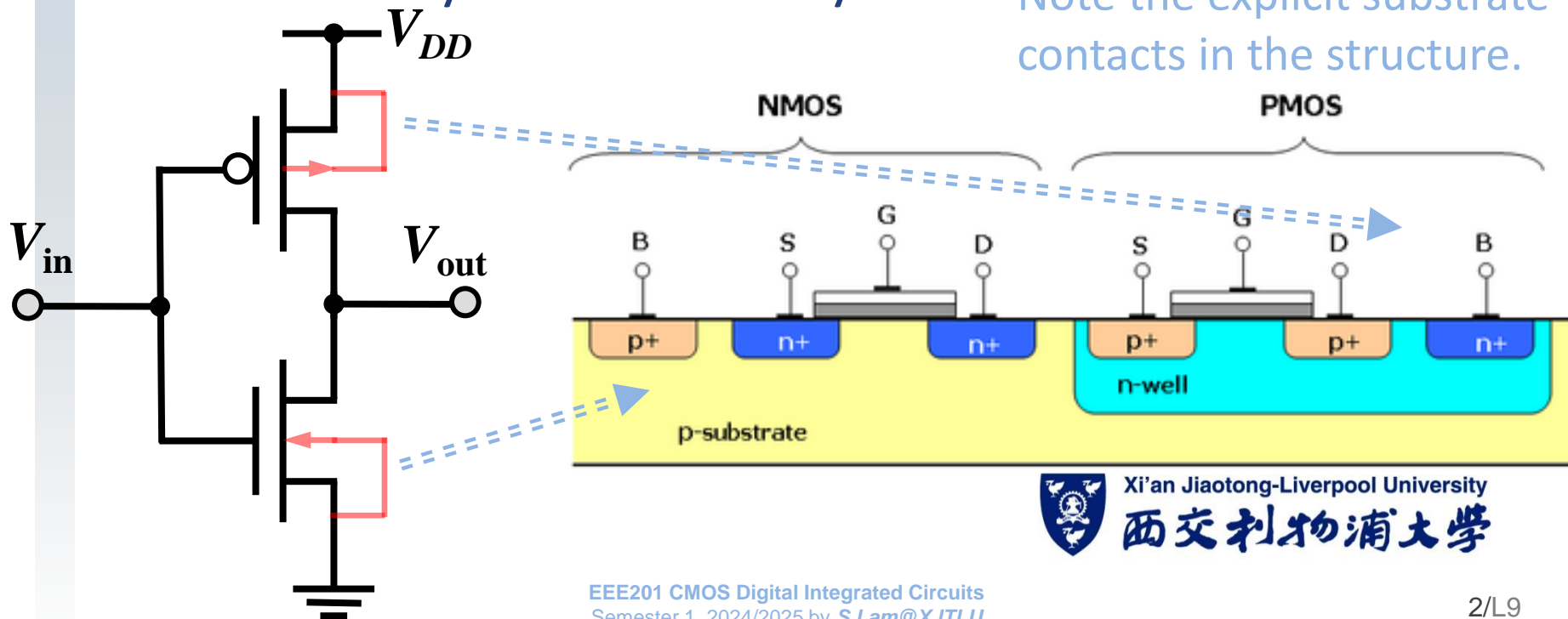Note the explicit substrate contacts in the structure.



CMOS Inverter

(from schematic design to device structures on wafer)

- ❑ To fabricate NMOS transistors alone on a *p*-type silicon wafer, at least four masks are needed.
⇒ four mask layers in the IC layout for NMOS transistors
- ❑ To fabricate both NMOS and PMOS transistors on a *p*-type silicon wafer, at least seven masks are needed: ⇒ 7 mask layers in the IC layout for CMOS circuits

Mask 1: *n*-well; Mask 2: **active**; Mask 3: **polysilicon** (gate)

Mask 4: *p*-select (for defining the *p*-type doping)

Mask 5: *n*-select (for defining the *n*-type doping)

Mask 6: **contact** (to active & polysilicon)

Mask 7: **metal 1**



CMOS IC Layout

(schematic circuit to physical structures in fabrication)

- ❑ In drawing the IC layout, we need to be aware of what device structure will be fabricated from each mask layer.
⇒ **physical layout design** in CMOS ICs (digital & analogue)
- ❑ In drawing the IC layout, it is a process of turning the schematic circuit into **physical design** in a planar representation (with very precise geometrical shapes & dimensions).
 - Electronic design automation (EDA) software (e.g. Cadence) is used nowadays to create the **layout design** for IC fabrication. Within Cadence, Virtuoso is the IC layout editor.
 - Other examples of EDA for IC layout design: Synopsys, Tanner L-edit

CMOS IC Layout

(schematic circuit to physical layout)

 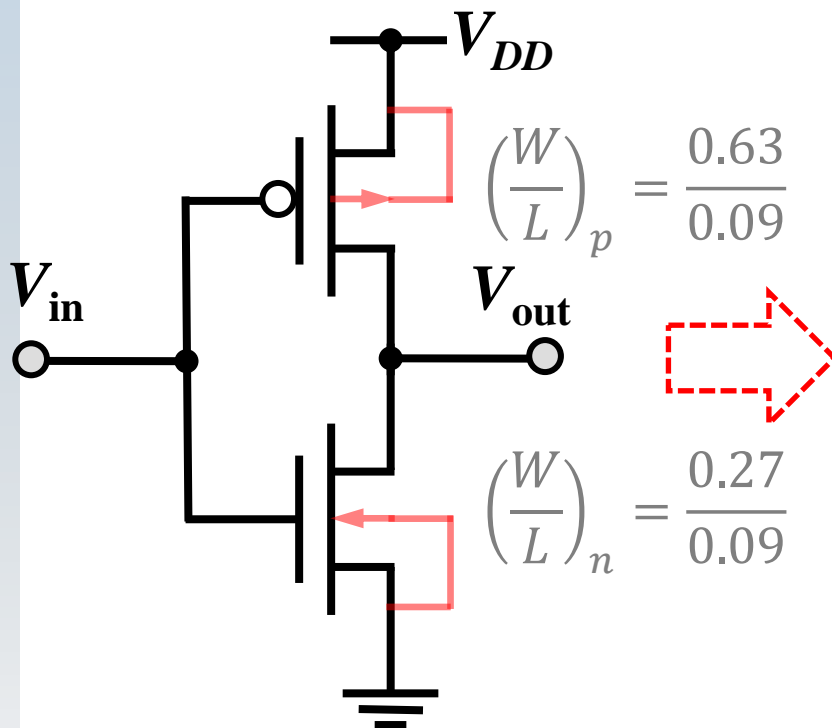

The mask number is the sequence in IC fabrication. But it doesn't matter in drawing which mask layers first & which later.



Xi'an Jiaotong-Liverpool University
西交利物浦大学


Drawing CMOS Layout with EDA

(start with the **active** mask layer for one MOSFET)

Mask 2: active


Start drawing NMOS transistor in this case.

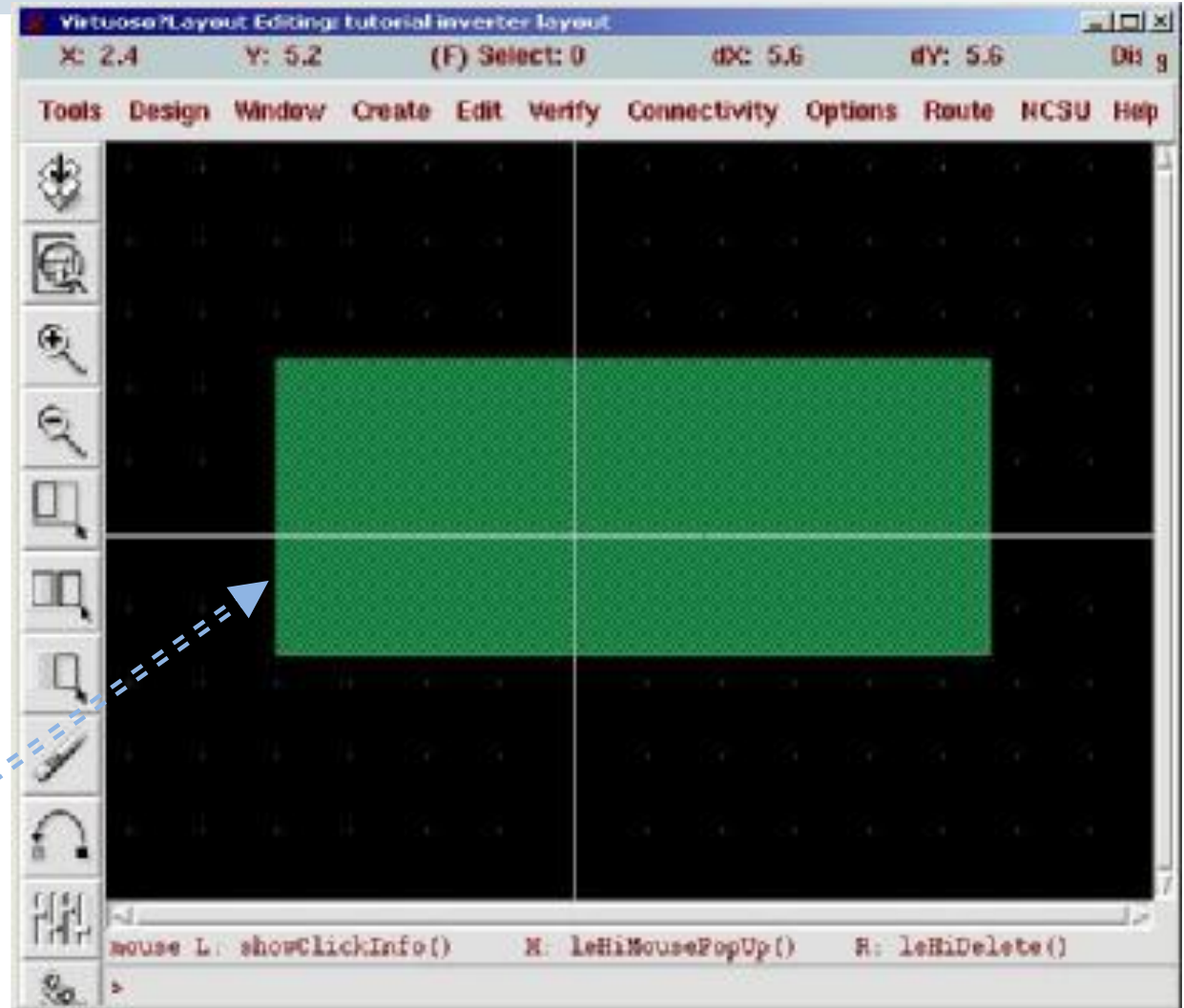Note that one dimension of the geometrical shape drawn for the **active** mask will define the channel width W of the MOSFET.




Drawing CMOS Layout with EDA

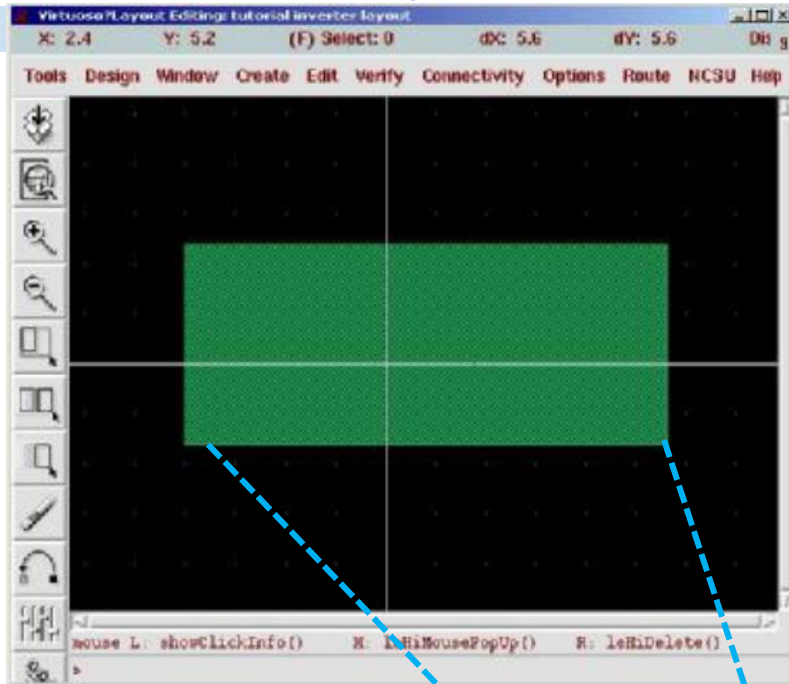(**active** mask layer for MOS transistor)



 - ❑ The **active** mask defines the regions where semiconductor **devices** (rather than e.g. inductors) will be located, hence without field oxide in the defined area.




Drawing CMOS Layout with EDA

(**polysilicon** mask layer for MOS transistor)

Mask 3:


polysilicon

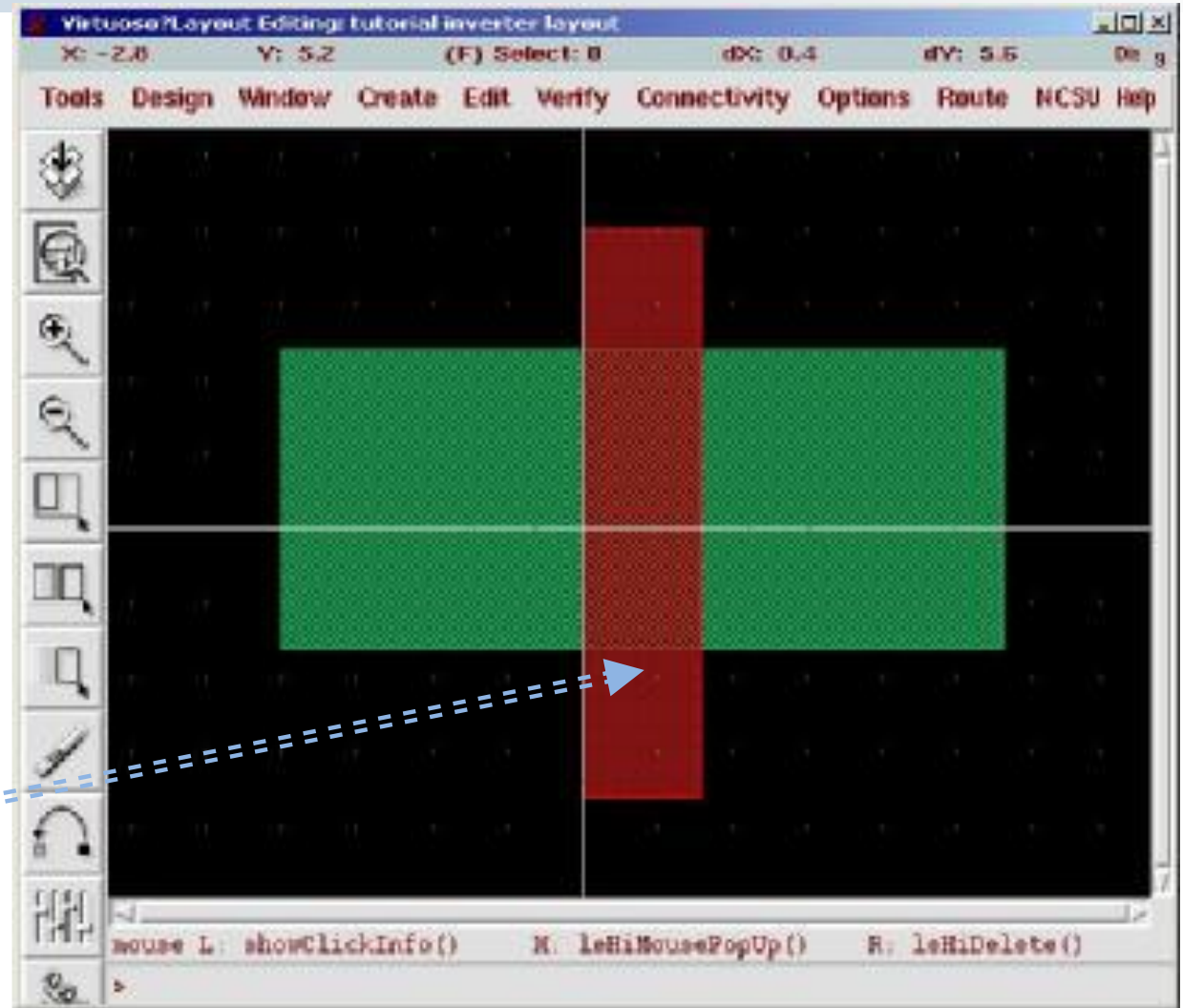Note that the smaller size of the geometrical shape drawn for the **polysilicon** gate will define the channel length L of the MOSFET.




Drawing CMOS Layout with EDA

(polysilicon gate of the MOSFET)

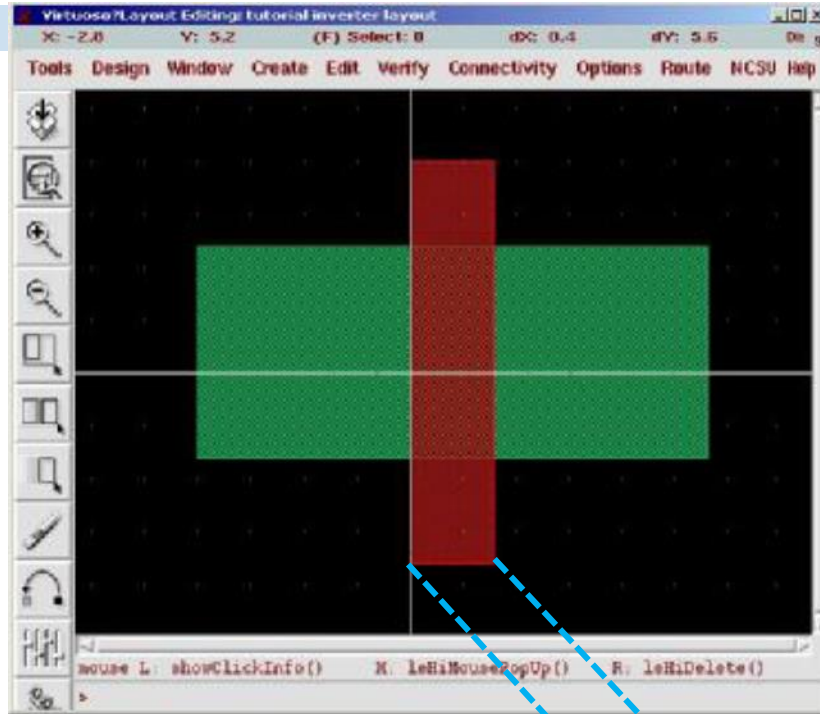

 - ❑ In the actual fabrication, the **polysilicon** gate is above a very thin gate oxide layer of the MOSFET.
- In modern nano-CMOS technology, the gate is made of **copper**, not polysilicon.




Drawing CMOS Layout with EDA

(one-sized square-shaped contact to active)

Mask 6: **contact**

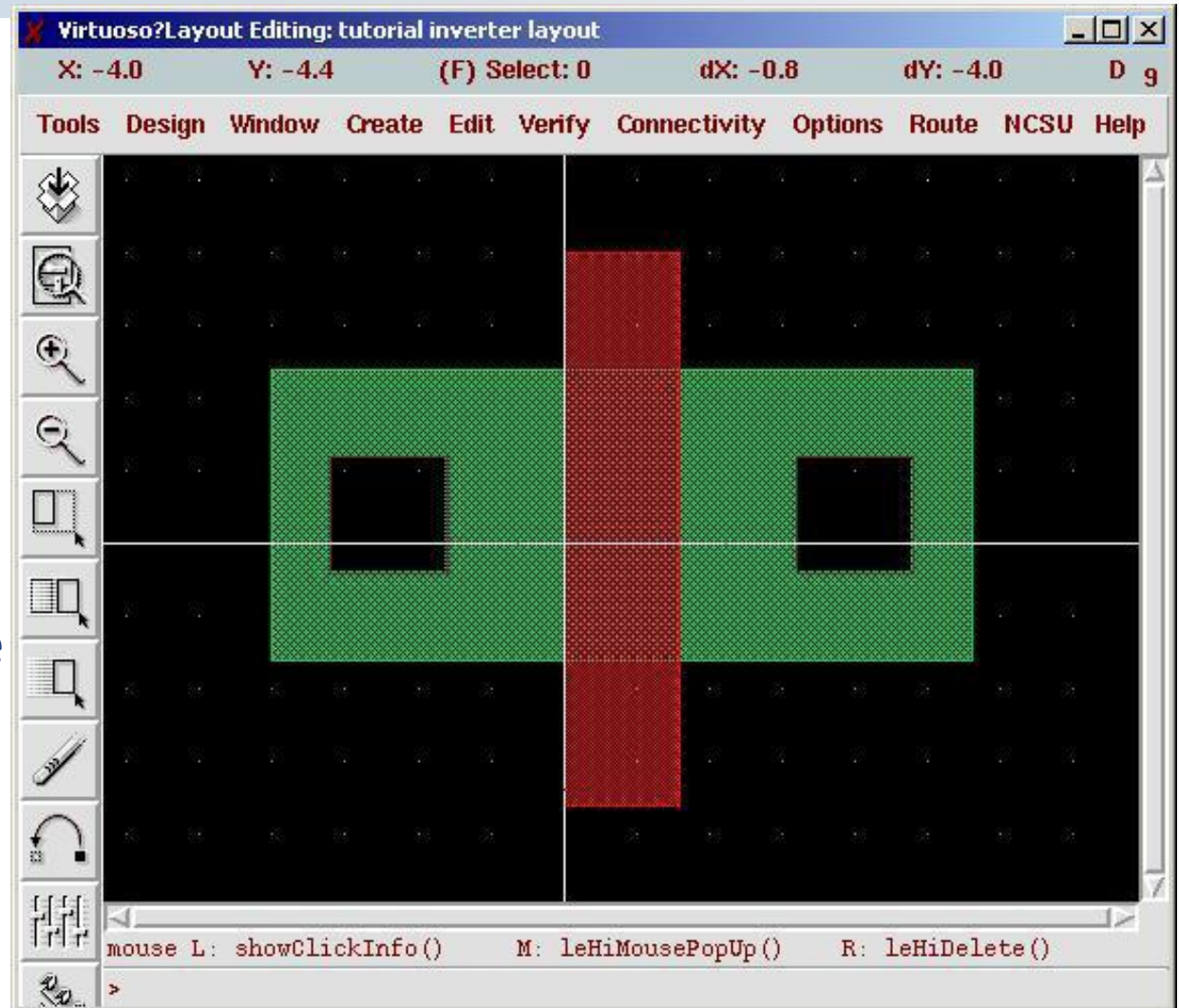The **contacts** shown here connect the source/drain regions. It is the same **contact** mask layer for connecting to polysilicon.




Drawing CMOS Layout with EDA

(covering contact with metal)


Mask 7: metal

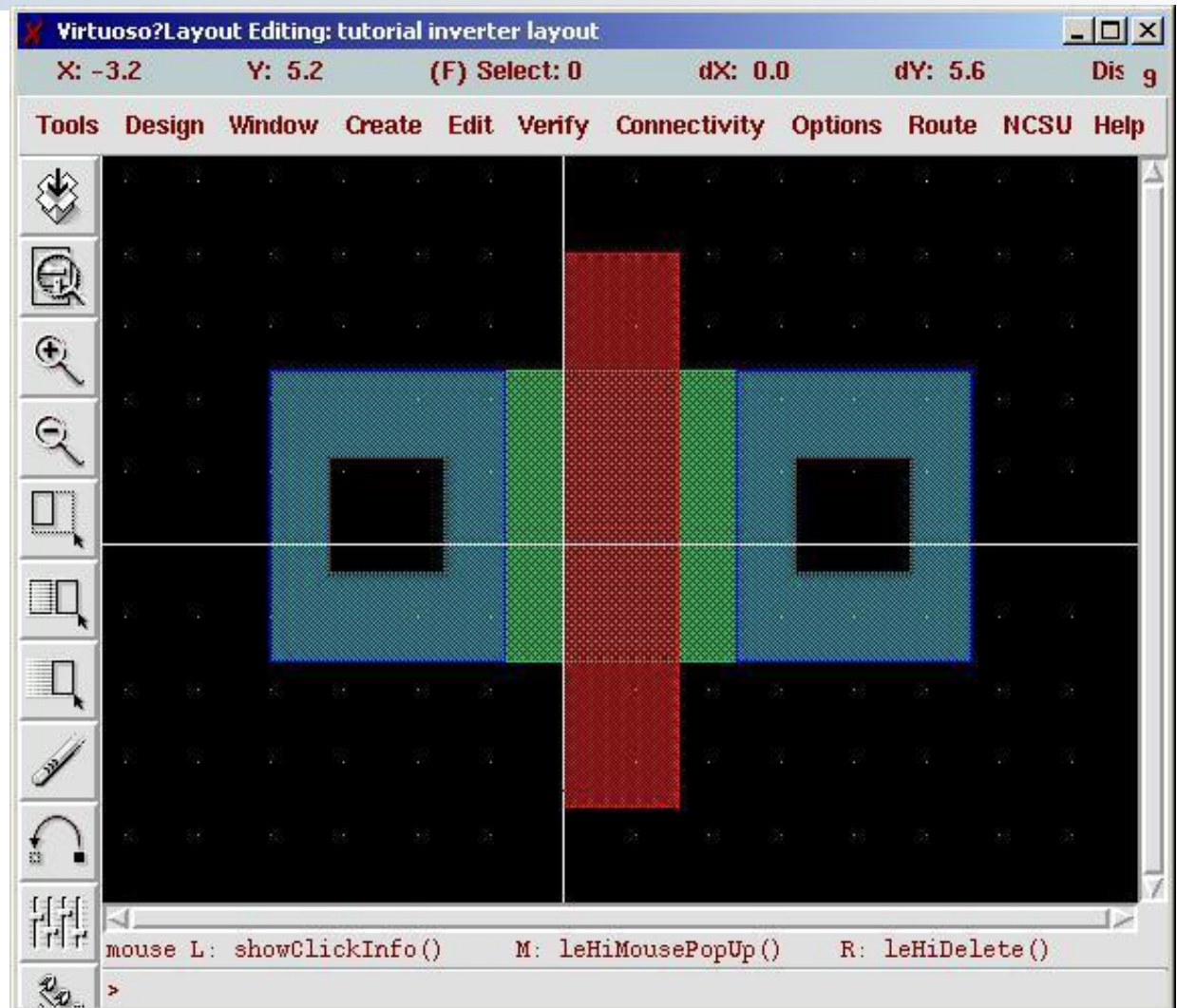The **contacts** must be covered with the **metal** mask layer, literally **metal 1**.




Drawing CMOS Layout with EDA

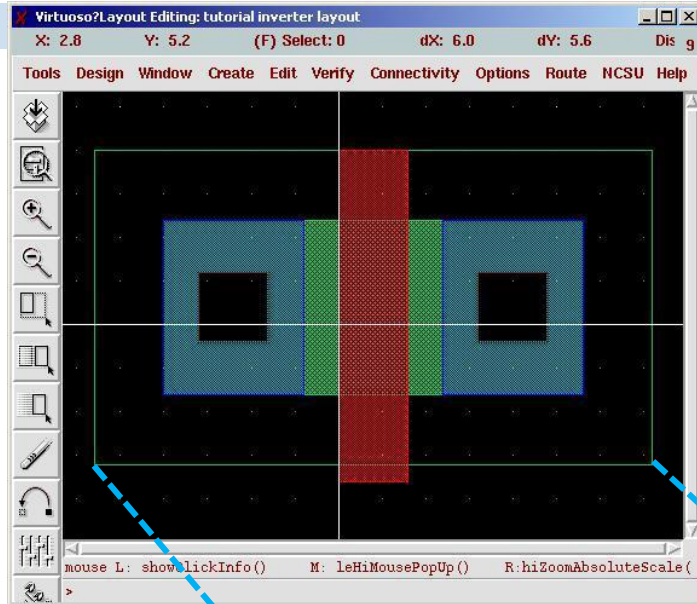(*n*-select or called *n*-diffusion implant)



 - ❑ In the fabrication of both NMOS and PMOS transistors on the same wafer, the NMOS source/drain regions are selected for *n*-type doping by the *n*-select mask layer.




Drawing CMOS Layout with EDA

(*n*-select for regions to be doped *n*-type)

Mask 5: *n*-select


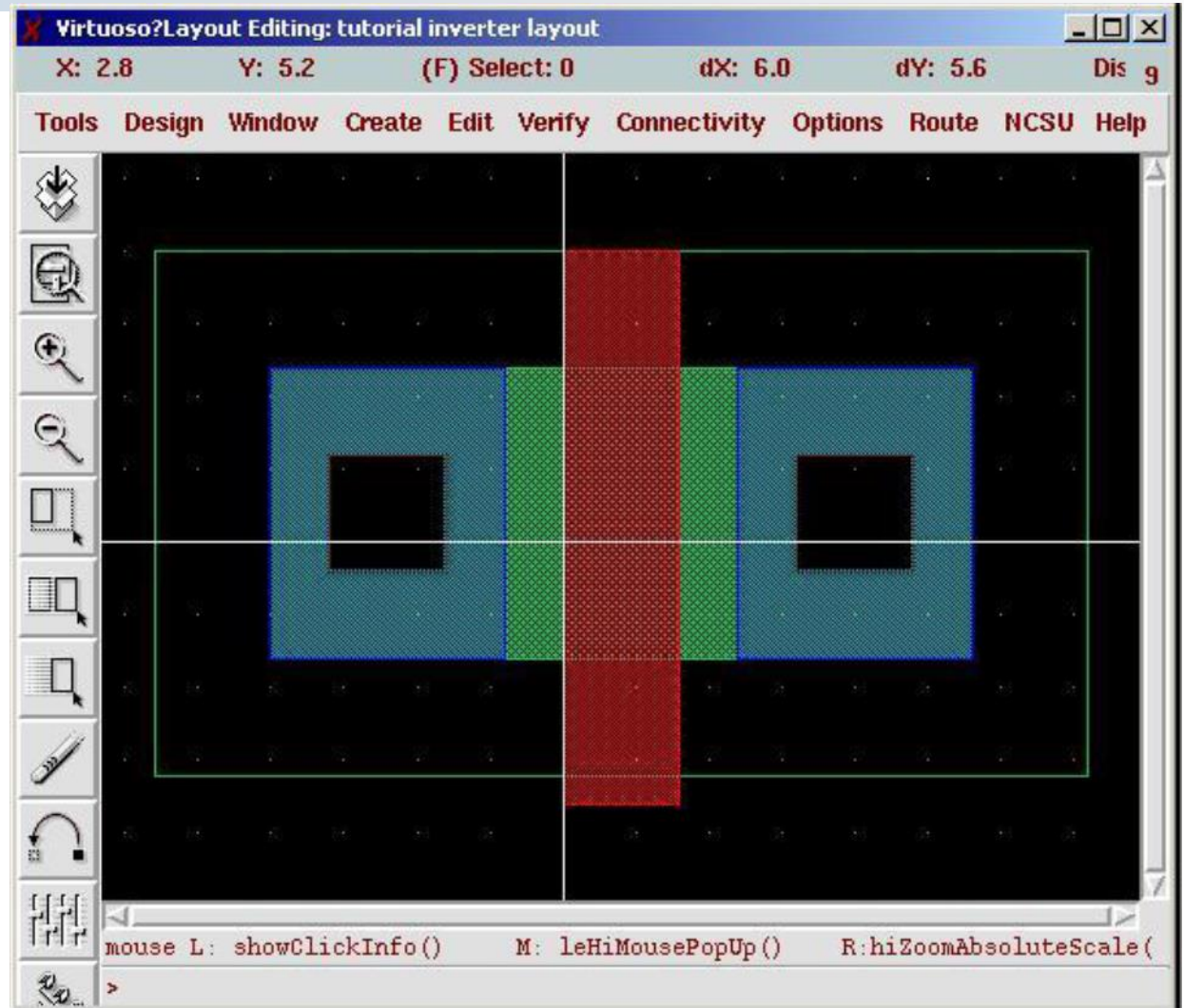
The *n*-select mask layer covers the **active** mask layer & the **polysilicon** mask layer in the NMOS transistor. \Rightarrow The polysilicon gate is heavily doped \Rightarrow more conducting



Drawing CMOS Layout with EDA

(substrate contact in NMOS transistor)

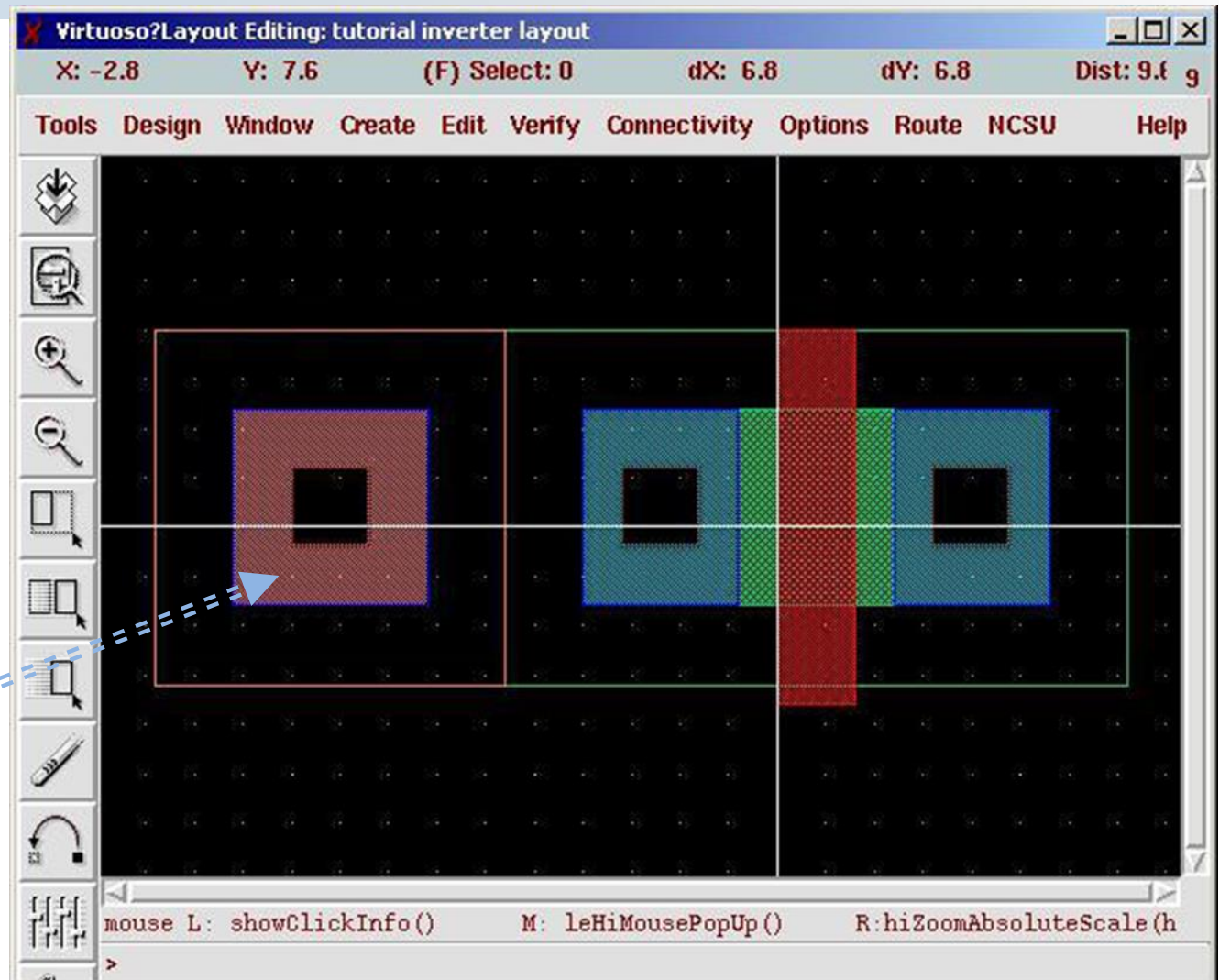 The substrate contact to the *p*-type wafer can be explicitly created in *n*MOSFET.



Drawing CMOS Layout with EDA

(same **active** mask layer for PMOS transistor)

Mask 2:

active

The PMOS transistor layout also starts with the **active** mask layer, which is essentially the same as that of the NMOS transistor.




Drawing CMOS Layout with EDA

(same **polysilicon** mask layer for PMOS transistor)

Mask 3:

polysilicon

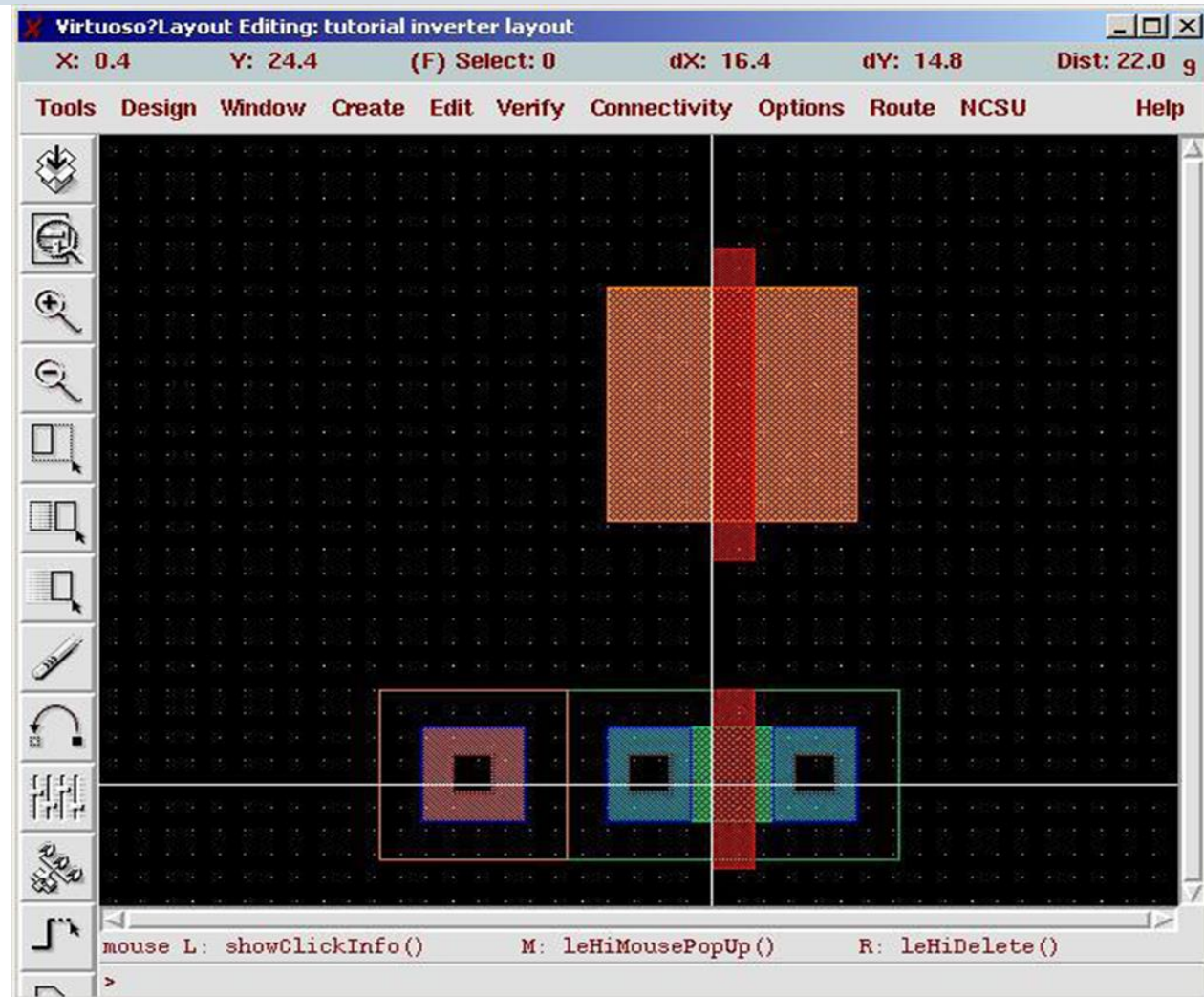The PMOS transistor's gate electrode is defined by the same **polysilicon** mask layer of the NMOS transistor, in the same way.




Drawing CMOS Layout with EDA

(**contact** to source/drain regions of PMOS transistor)

Mask 6: **contact**

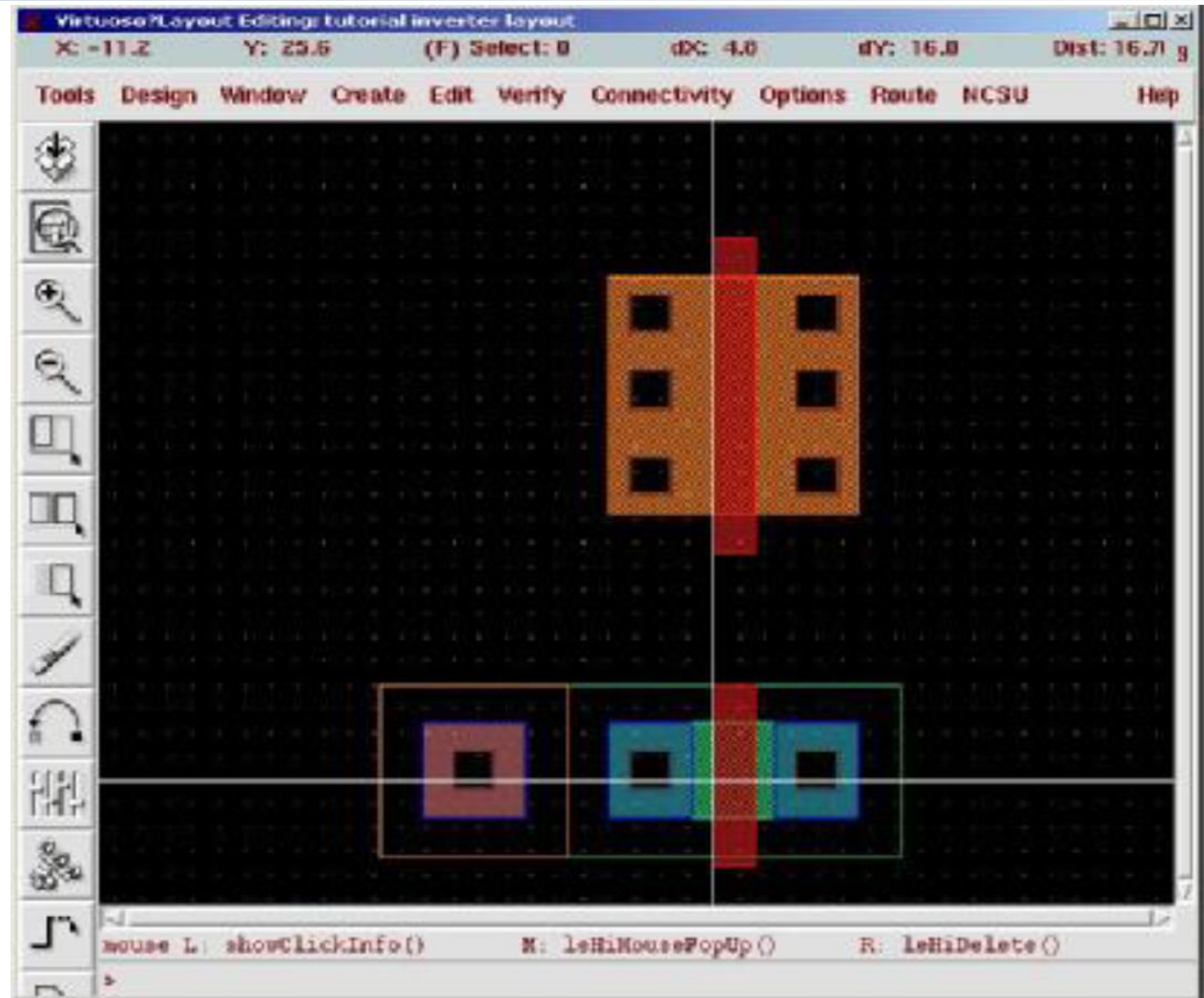The same
contact mask
layer in the
NMOS
transistor
applies to the
PMOS
transistor.




Drawing CMOS Layout with EDA

(same square **contact** covered with **metal**)

Mask 7:

metal

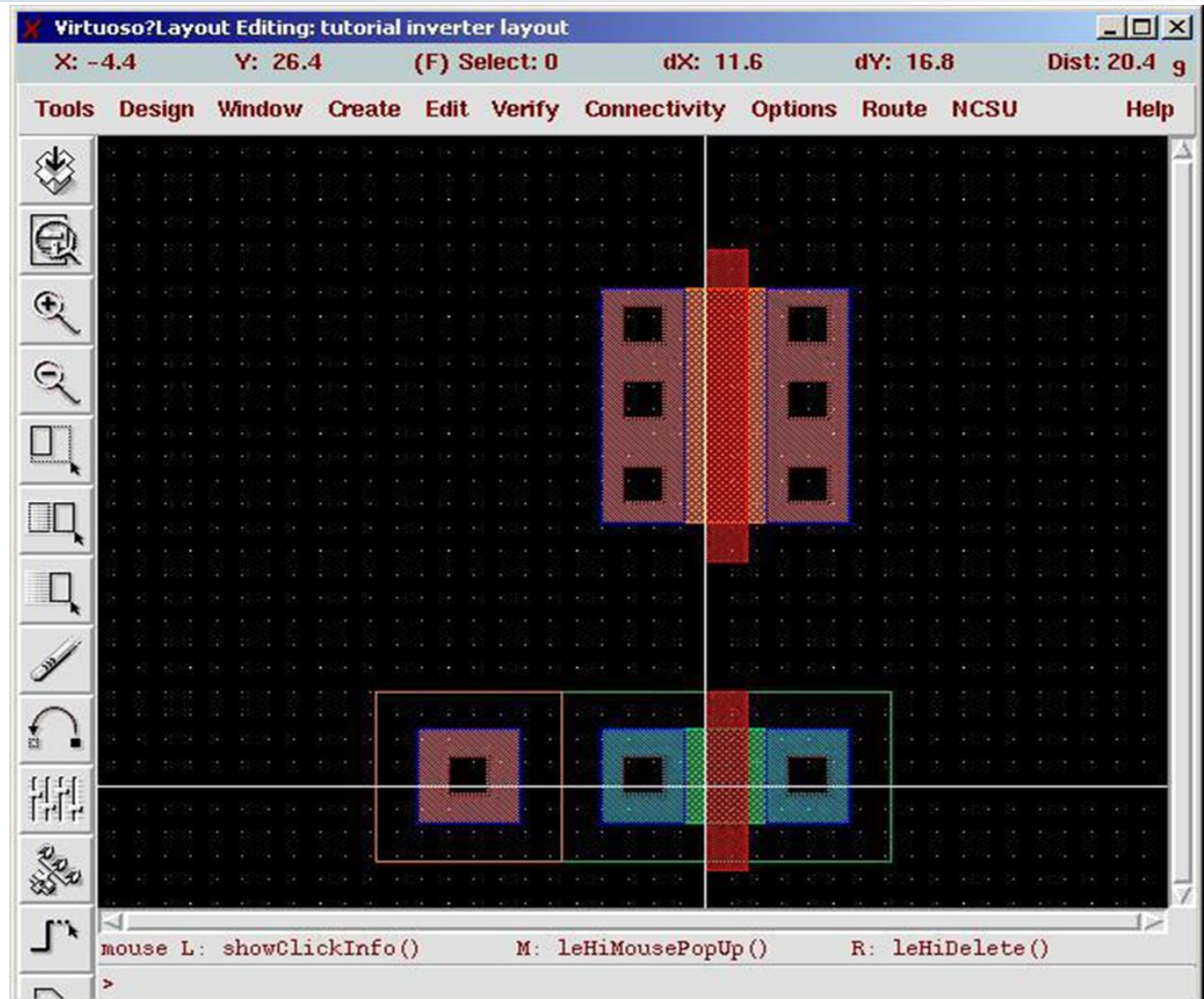The same one-sized square **contacts** of the PMOS transistor must also be covered with the **metal 1** mask layer.




Drawing CMOS Layout with EDA

(*p-select* for defining regions of *p*-type doping)

Mask 6: *p-select*

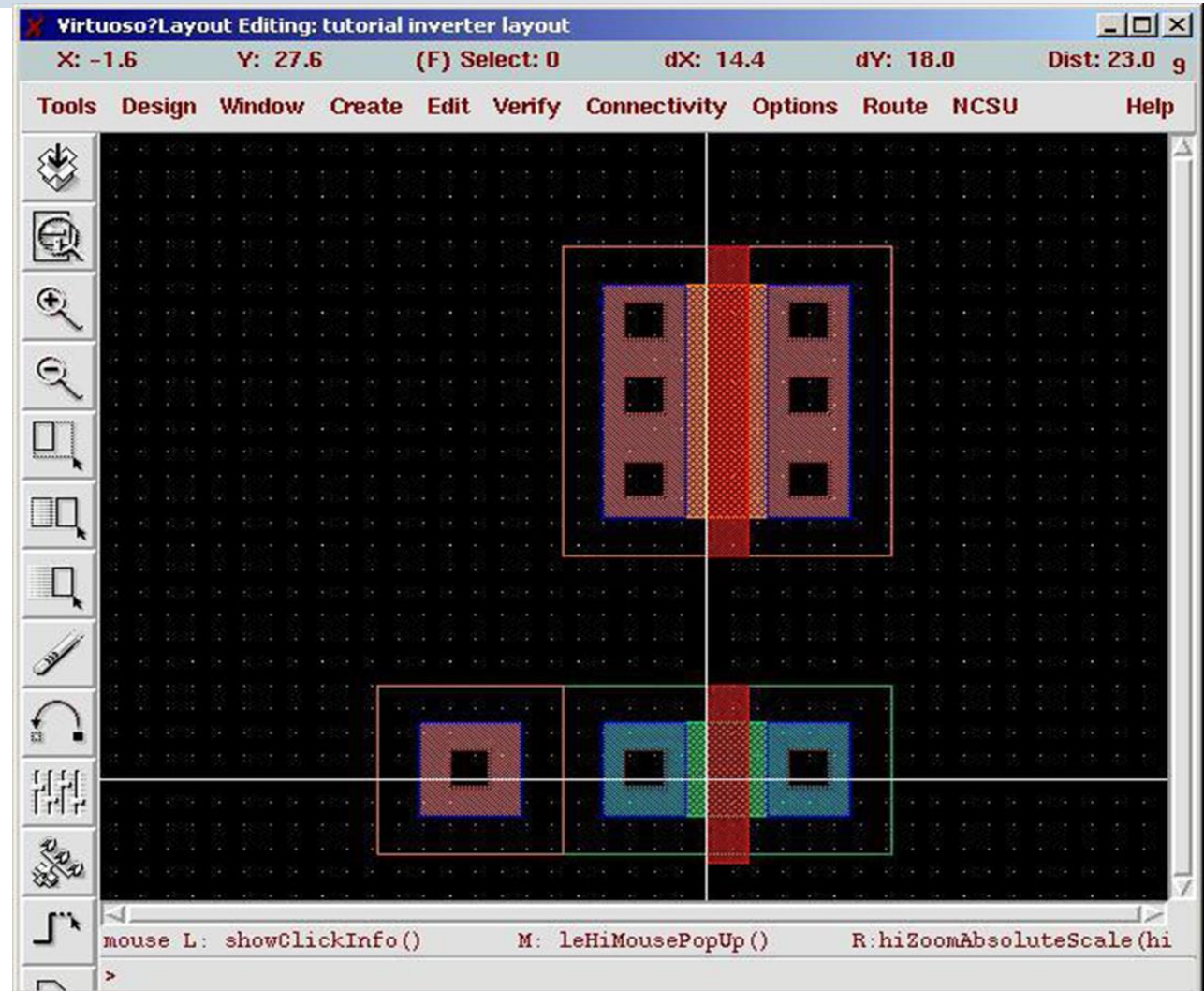In the PMOS transistor, the *p-select* mask layer defines the source/drain regions for *p*-type doping.




Drawing CMOS Layout with EDA

(*n*-well mask layer for PMOS transistor)

Mask 1:

n-well

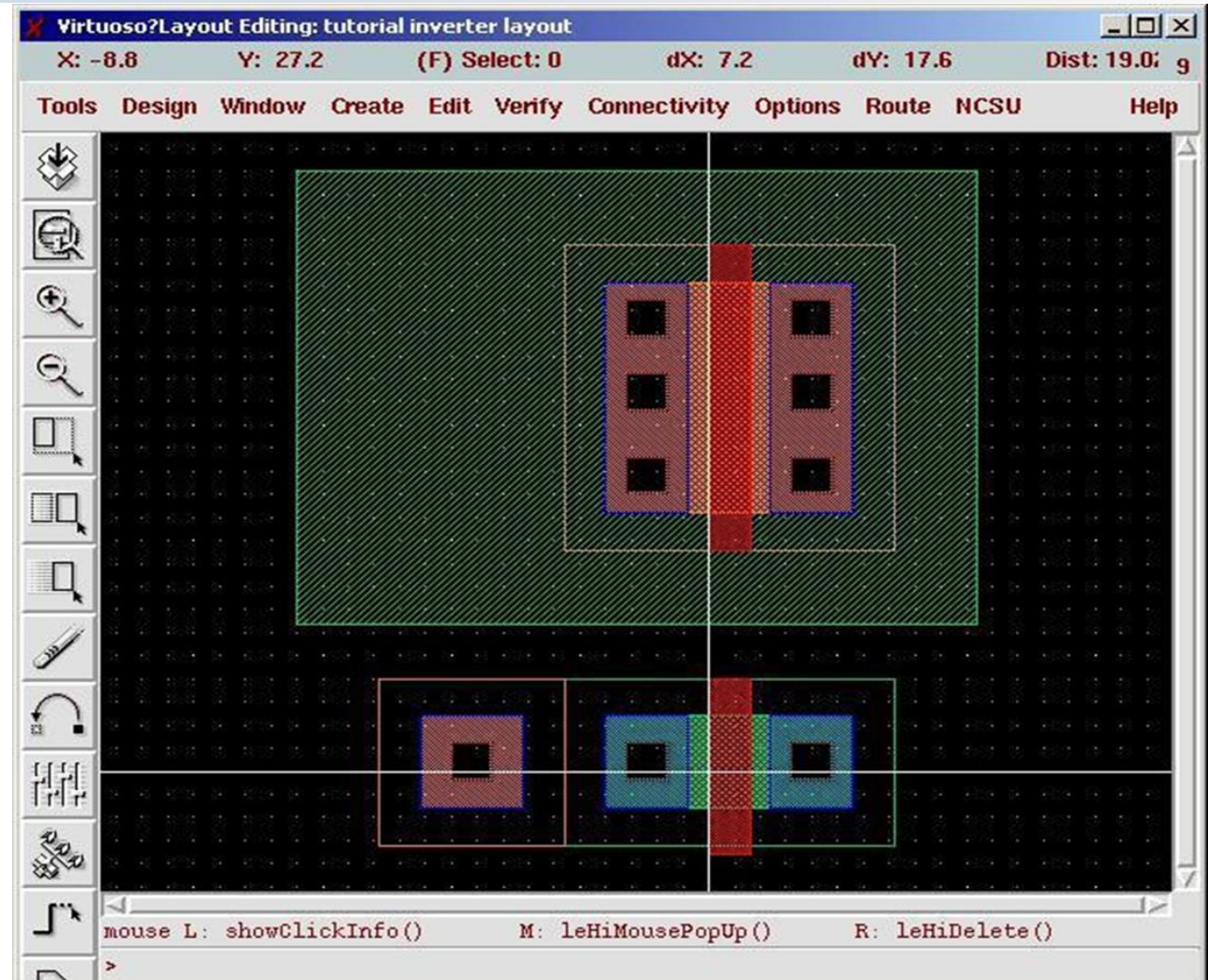To make PMOS transistors on a *p*-type wafer, the *n*-well mask layer defines an *n*-type region for the pMOSFET.




Drawing CMOS Layout with EDA

(substrate contact of PMOS transistor)

In the PMOS transistor, the **substrate contact** to the ***n*-well** is necessary.

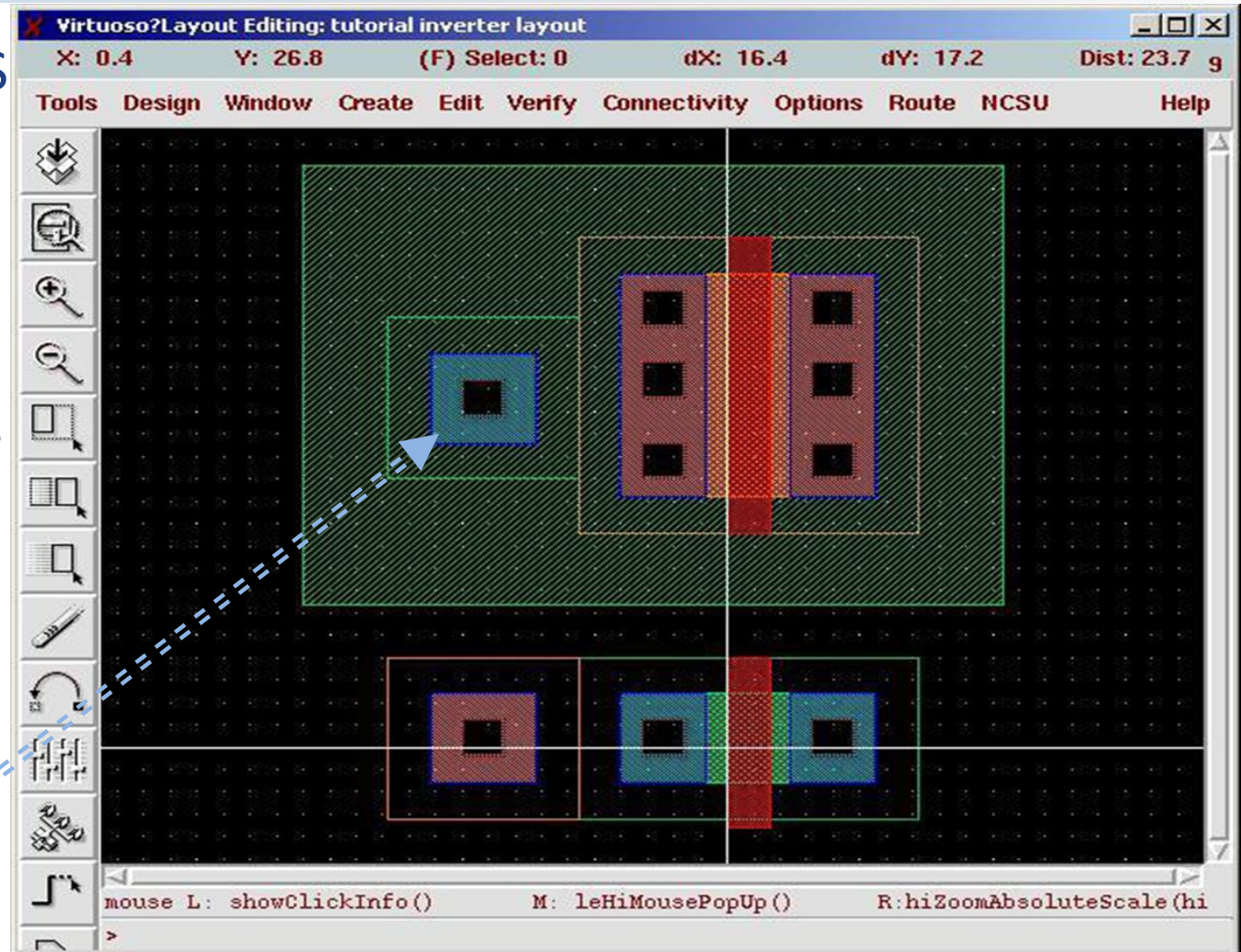Note 4 mask layers on ***n*-well**: active, contact, *n*-select & metal.




Drawing CMOS Layout with EDA

(use of **metal** mask layer for electrical wiring)

The **metal** mask layer is used to define the *interconnect* as **electrical wiring** of the circuit (e.g. connection to power supply & ground).


There can be metal 2, 3, ...

 

Drawing CMOS Layout with EDA

(polysilicon gates connection)

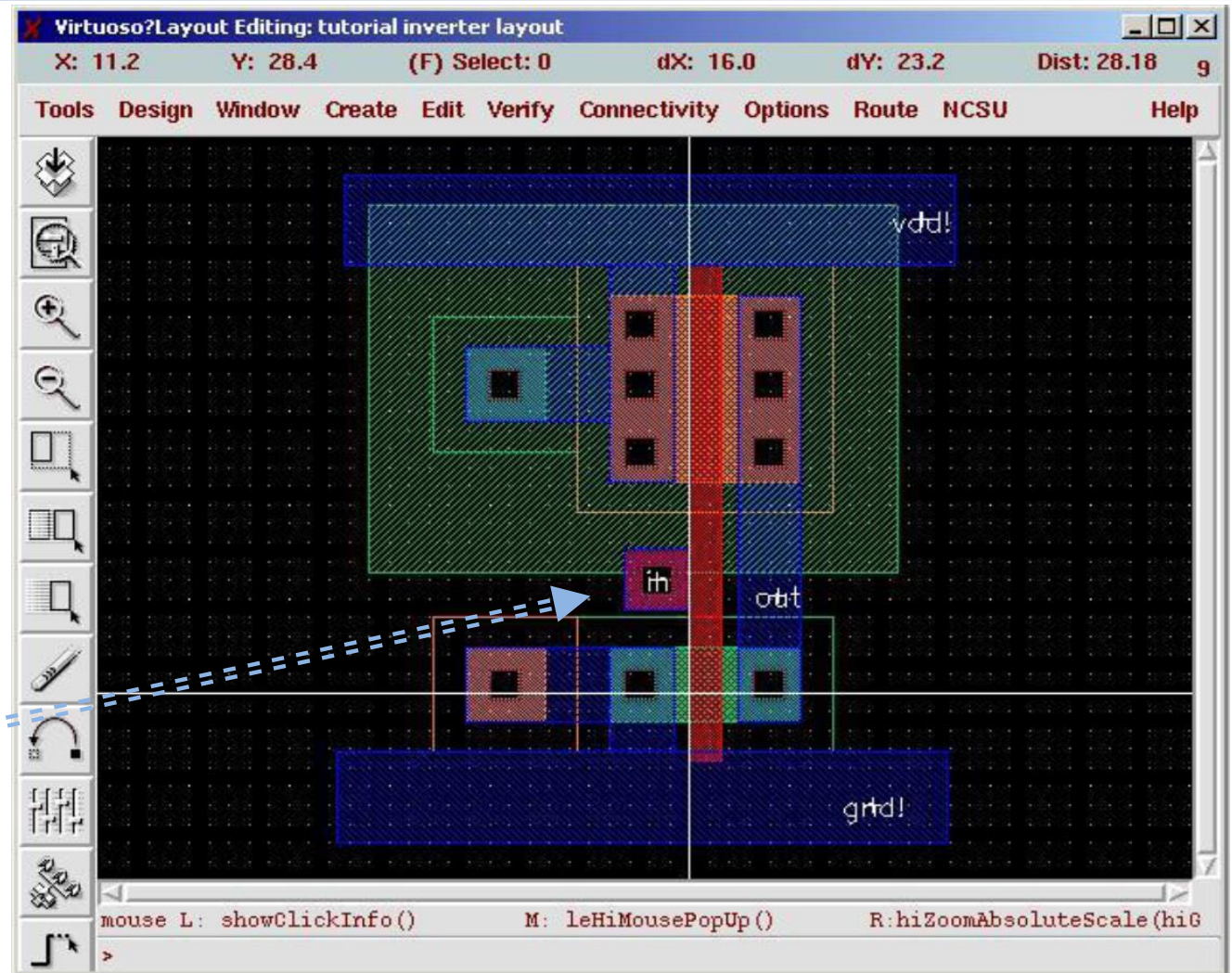
The polysilicon gates of the PMOS & NMOS transistors are connected together with a **contact & metal** to the input of the CMOS inverter.



IC Layout

(CMOS logic gate)

 - ❑ When given a simple CMOS digital IC layout, can you recognise the **logic circuit**?
- ❑ Can you also identify the **mask layers** in the layout?
 - What mask layers missing?



Adapted from: S.-M. Kang & Y. Leblebici,
*CMOS Digital Integrated Circuits:
Analysis & Design*, 3rd edition, © 2003
McGraw-Hill, USA.

IC Layout

(≥ 7 masks in CMOS)

Mask 1: *n*-well

Mask 2: active

Mask 3: polysilicon

Mask 6: contact

Mask 7: metal 1

Two mask layers are missing on the previous slide:

Mask 4: *p*-select

Mask 5: *n*-select

