

Lecture 8
of
EEE201

CMOS Digital Integrated Circuits

Department of Electrical & Electronic Engineering
Xi'an Jiaotong-Liverpool University (XJTLU)

Tuesday, 7th November 2023

□ Building CMOS Logic Inverter


- Intuitive understanding from switch model
- transistor size determination
- CMOS IC layout



CMOS Logic Inverter


(one *p*MOS & one *n*MOS)

 - As the very first fundamental logic gate, a **logic inverter** (i.e. NOT logic gate) can be implemented using one *p*MOSFET stacking over one *n*MOSFET.



- Based on the device operation of the MOSFETs, we can easily find out the input-output relationship for the logic NOT function.


V_{in}	V_{out}
0 V	V_{DD}
V_{DD}	0 V

 



Xi'an Jiaotong-Liverpool University
西交利物浦大學

CMOS Logic Inverter - $V_{in} = 0 \text{ V}$

(switch model for intuitive perspective)

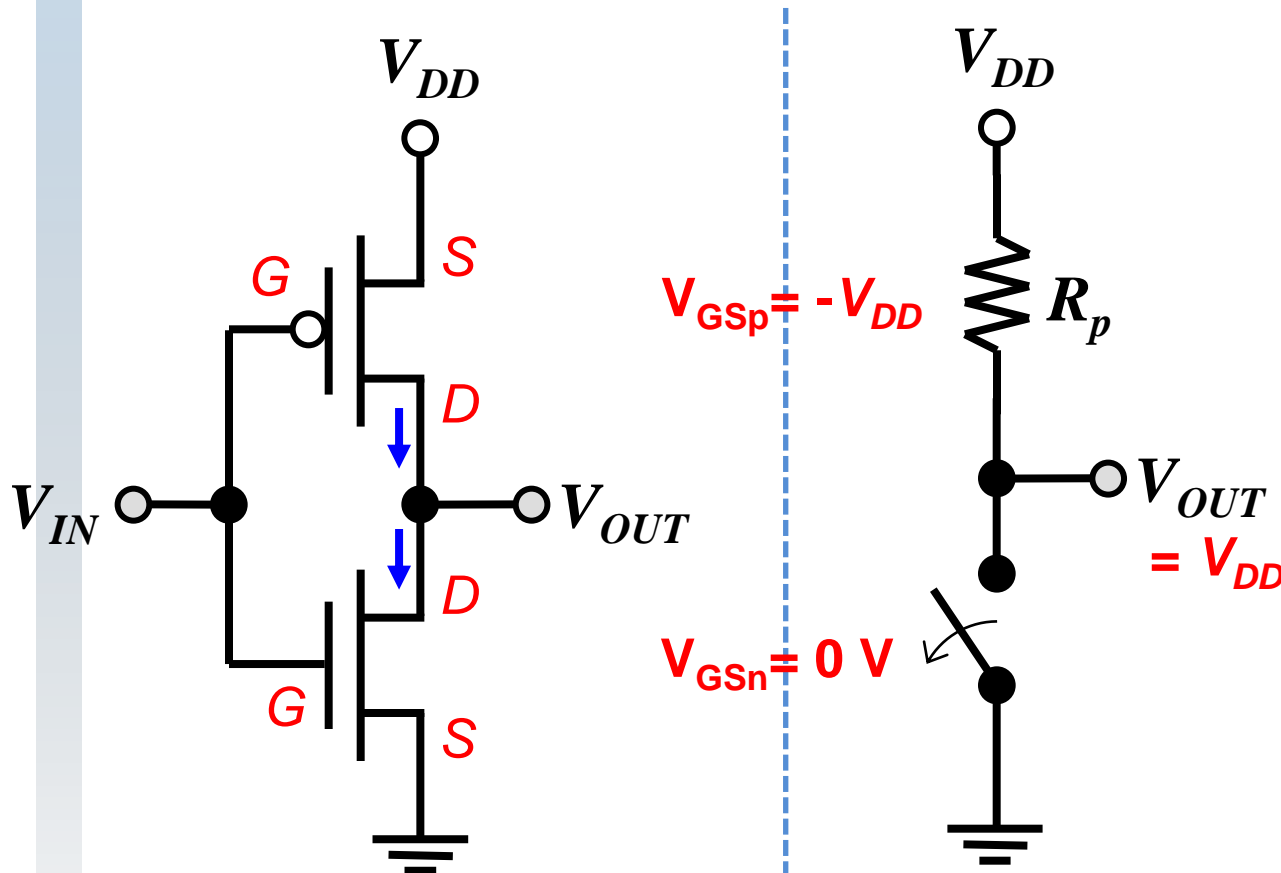


$$V_{IN} = 0 \text{ V}$$

  

Xi'an Jiaotong-Liverpool University
西交利物浦大学

CMOS Logic Inverter - $V_{in} = V_{DD}$


(switch model for intuitive perspective)

 

$$V_{IN} = V_{DD}$$

CMOS Logic Inverter

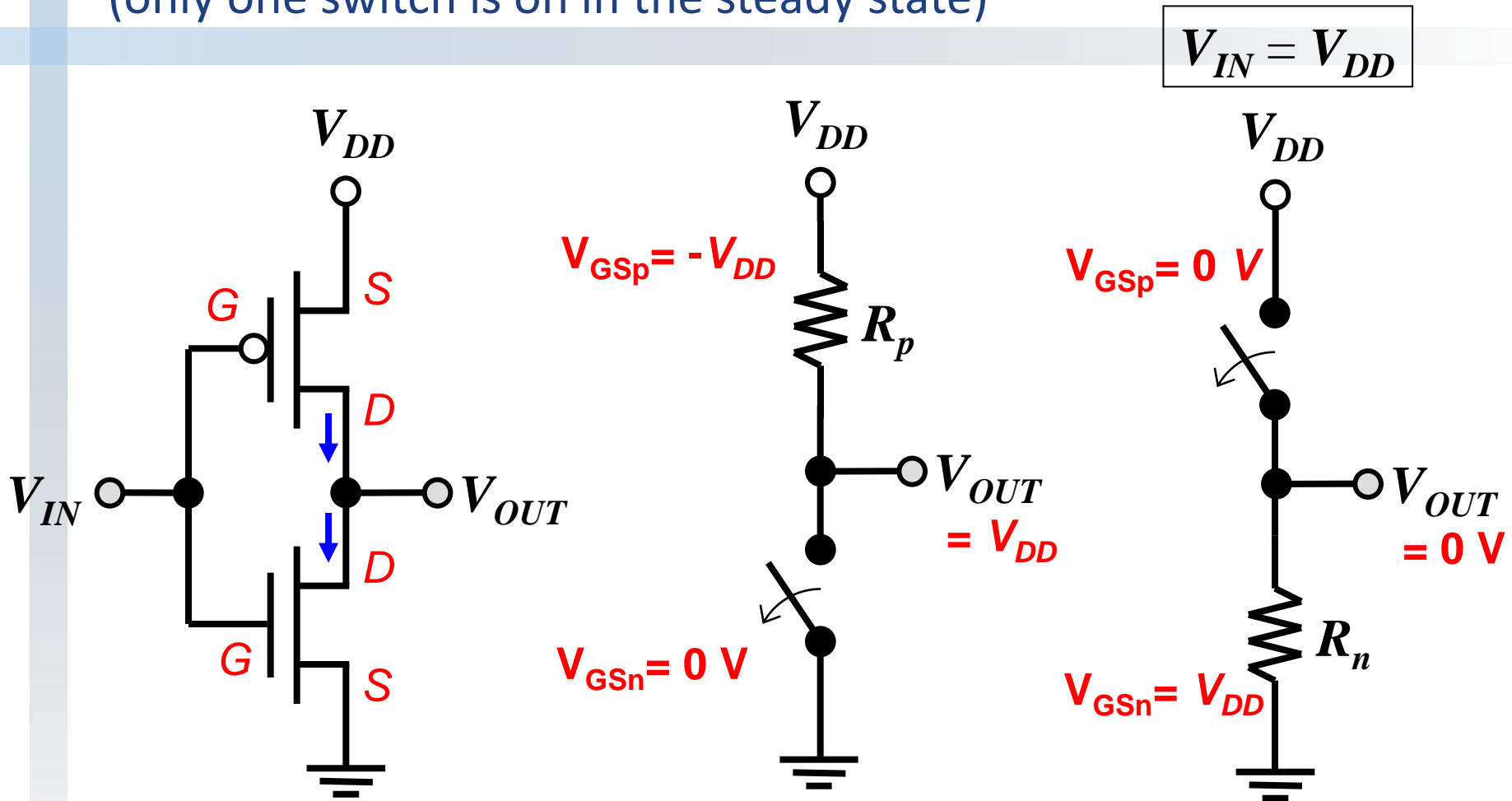(only one switch is on in the steady state)



□ Note the “zero” static power consumption.

$$V_{IN} = 0 \text{ V}$$





Xi'an Jiaotong-Liverpool University
西交利物浦大学

CMOS Logic Inverter

(dynamic behaviour in *charging* & *discharging* capacitances)

  
- Since there are **capacitances** associated with the MOSFETs, there will be *charging* and *discharging*.



- The logic gate response time is determined by the time to *charge* C_L through R_p (*discharge* C_L through R_n).

CMOS Logic Inverter – IC layout

(start from stick layout diagram)


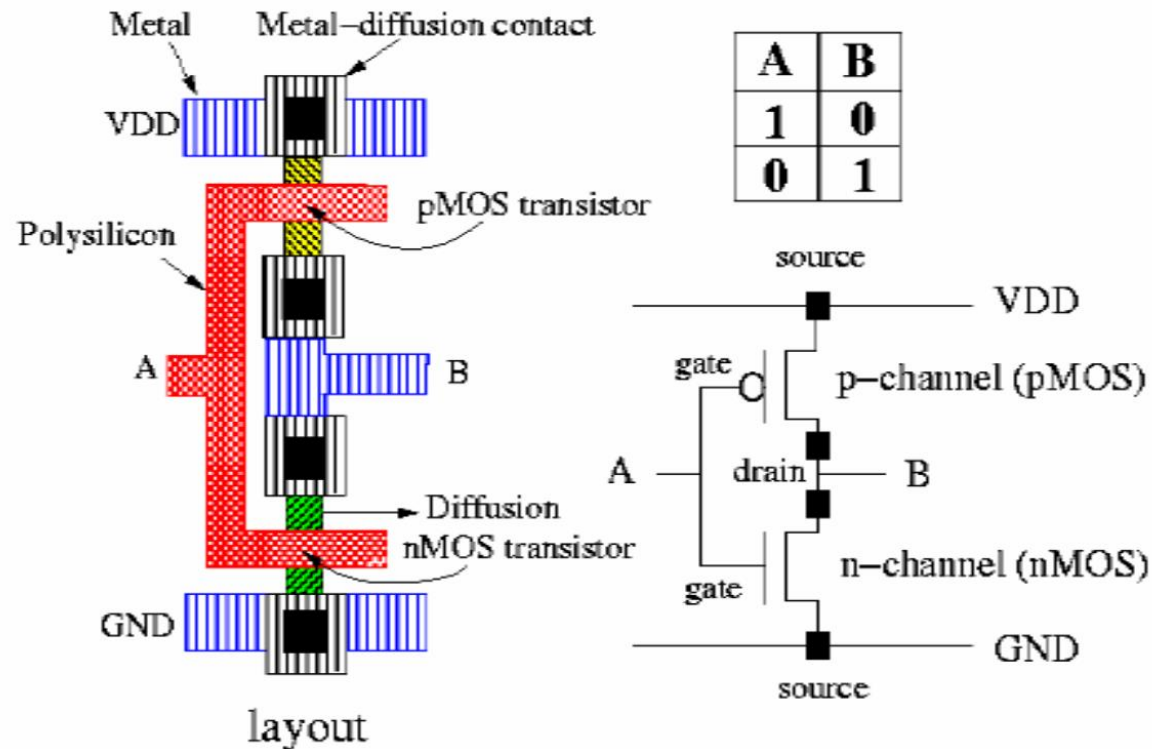


□ To design the IC layout of the logic gate, one approach is to start from the so-called stick layout.

metal 1: blue polysilicon: red p-diffusion: yellow (p-well: light yellow)
metal 2: brown contact/via: black n-diffusion: green (n-well: light green)


CMOS Logic Inverter – IC layout

(scratch to proper layout)

 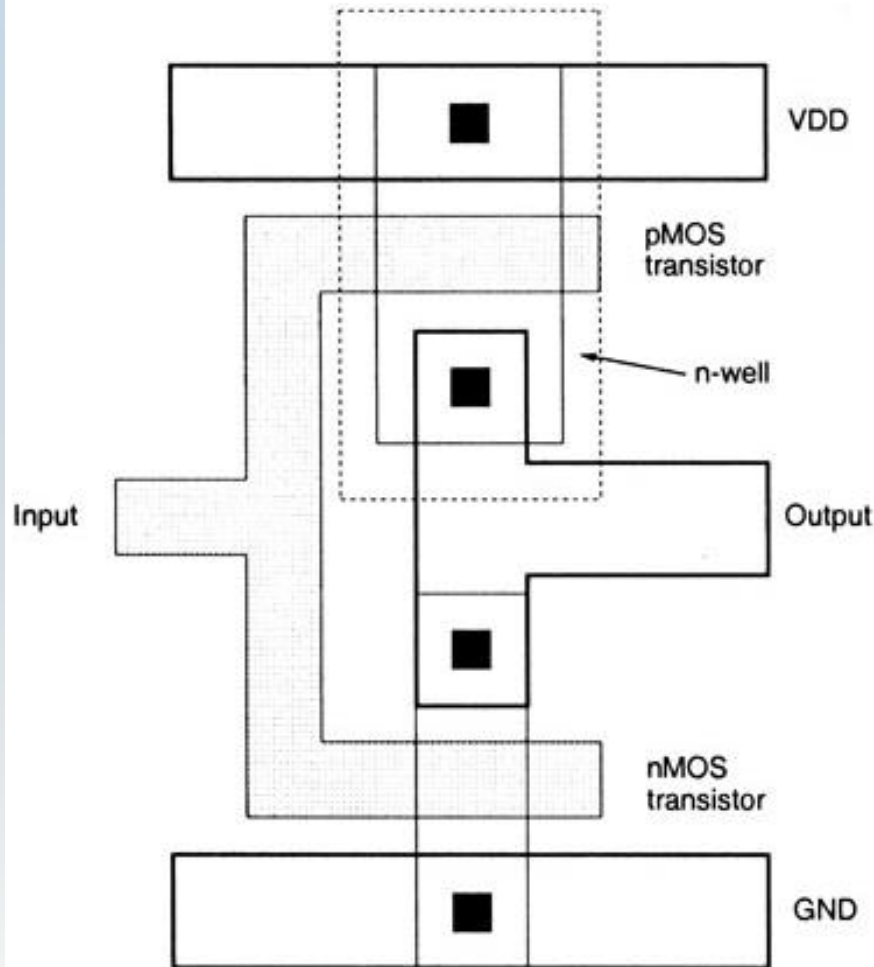

CMOS Logic Inverter – IC layout

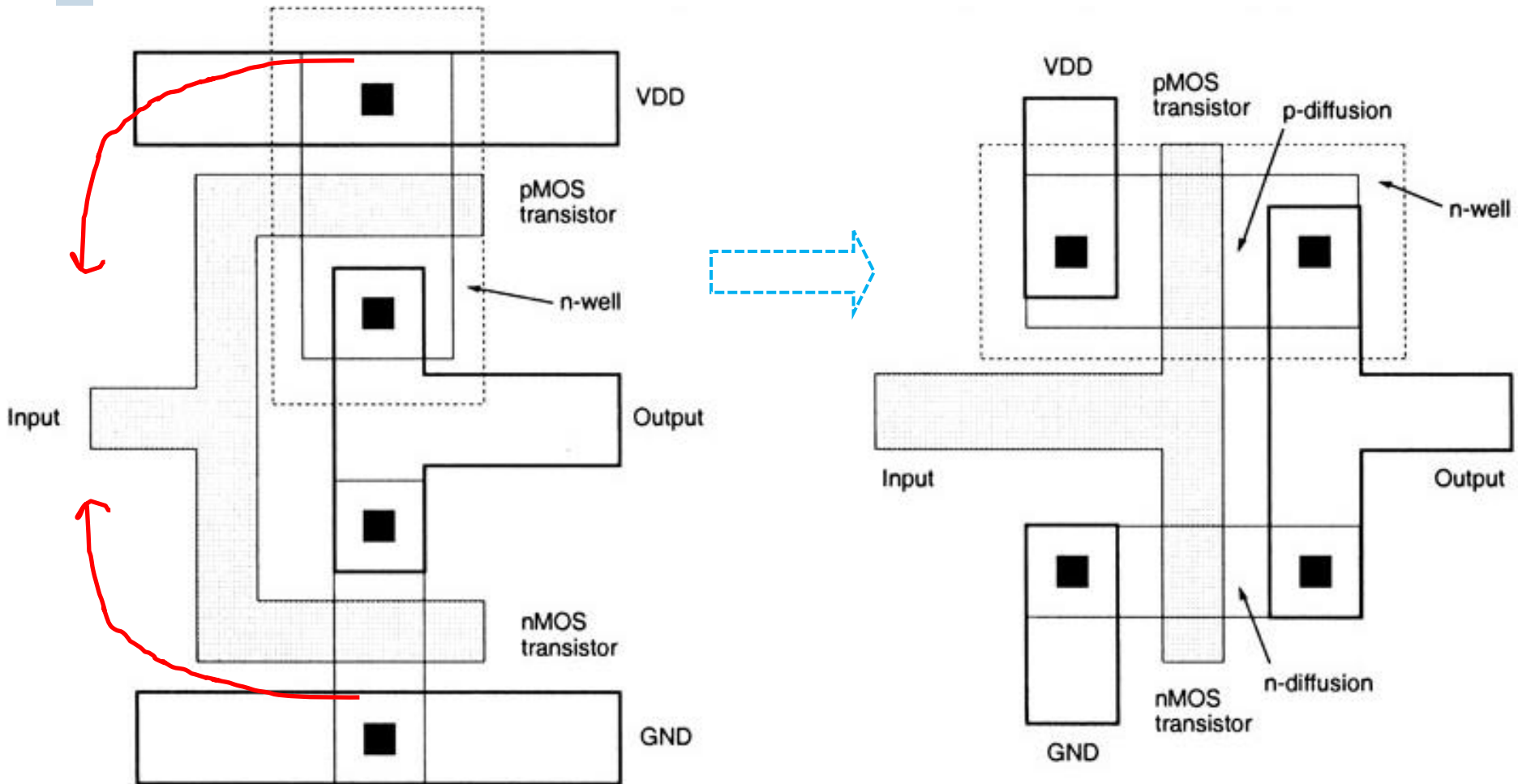(proper MOSFET layout orientation – less chip area)



CMOS Logic Inverter – IC layout

(MOS transistor sizes – essential design consideration)

- ❑ The sizes (W & L) of MOSFETs need to be designed in the layout.

If $V_{T0n} = |V_{T0p}|$



$I_{Dn} = I_{Dp}$
or $R_n = R_p$




$\mu_n \left(\frac{W}{L} \right)_n = \mu_p \left(\frac{W}{L} \right)_p$

$$I_{D,sat} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2$$

$$I_{D,lin} = \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

 
$R_{n/p}$: equivalent resistance of the MOSFET when turned on



CMOS Logic Inverter

(one *p*MOS & one *n*MOS)

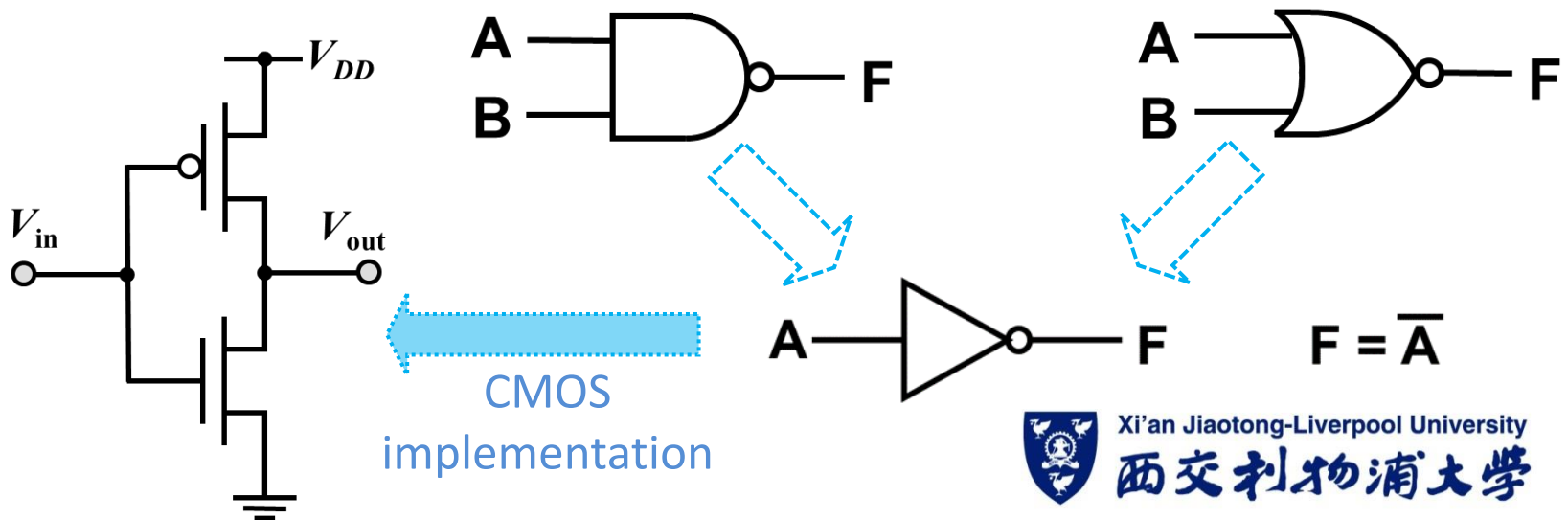- ❑ The **logic inverter** is an important start for understanding the operation and characteristics of CMOS logic circuits.
 - Digital circuits of a NAND and NOR logic gates can be *reduced* to a logic inverter. (Do you know why?)



Xi'an Jiaotong-Liverpool University
西交利物浦大学