

# EEE104 – Digital Electronics (I)

## Lecture 8

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

# In This Session

- Combinational Logic
  - Basic Combinational Logic Circuits
  - Implementation
  - Universal NAND and NOR Gates
  - Using NAND and NOR Gates

# Basic Combinational Logic Circuits

- A **combinational logic** circuit is one in which
  - Logic gates are connected together to implement a certain function (in contrast to *basic logic gates*).
  - There is no storage involved (in contrast to *sequential circuits*).
- Examples of combinational logic
  - Exclusive-OR gates
  - The AND-OR logic in an SOP implementation.

# Basic Combinational Logic Circuits

## Exclusive-OR Logic

- The output  $X$  is HIGH only when the two inputs are at **opposite** levels.

$$\begin{aligned} X &= \bar{A}B + A\bar{B} \\ &= A \oplus B \end{aligned}$$

## Exclusive-NOR Logic


- The output of an Exclusive-OR circuit is inverted.
- The output  $X$  is HIGH only when the two inputs are at the **same** levels.

$$X = \overline{A\bar{B} + \bar{A}B} = \overline{(A\bar{B})} \overline{(\bar{A}B)} = (\bar{A} + B)(A + \bar{B}) = \bar{A}\bar{B} + AB$$

# Basic Combinational Logic Circuits
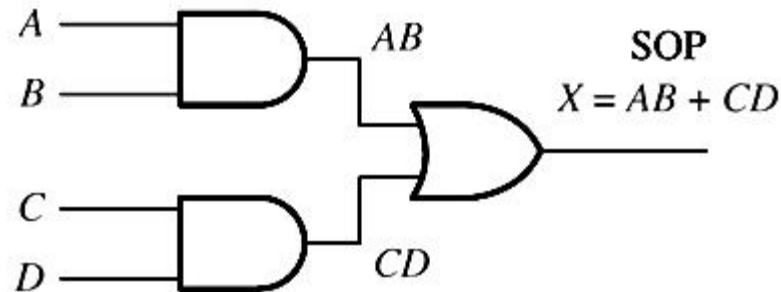
## AND-OR Logic

- The outputs of a number of AND gates connect to the inputs of an OR gate.
- It implements an SOP (sum-of-products) expression.





- An AND-OR-Invert logic implements a POS (product-of-sums) expression.

$$\overline{AB + CD} = \overline{AB} \overline{CD} = (\overline{A} + \overline{B})(\overline{C} + \overline{D})$$

# Implementation

## From a Boolean Expression to a Logic Circuit

$$X = AB(C\bar{D} + EF)$$

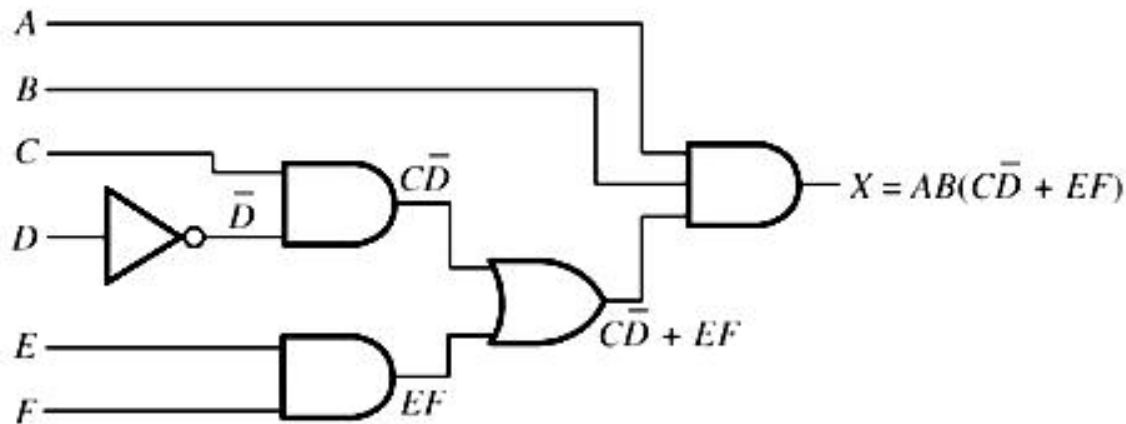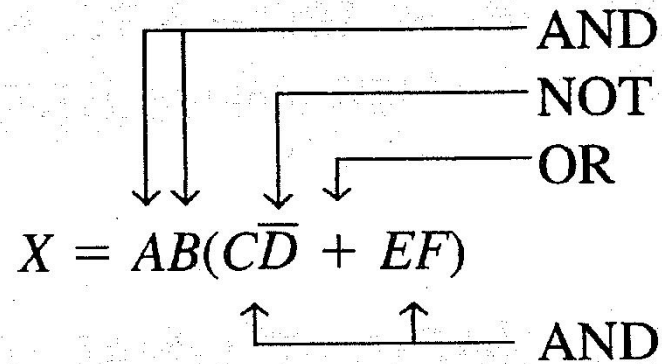

# Universal NAND and NOR Gates

- The NAND and NOR gates are **universal** because they can be used to produce any of other logic functions

## NAND gate

- NOT
- AND
- OR
- NOR

## NOR gate


- NOT
- AND
- OR
- NAND

# Universal NAND and NOR Gates

- NAND Gate as an Inverter




- Two NAND Gates as an AND Gate

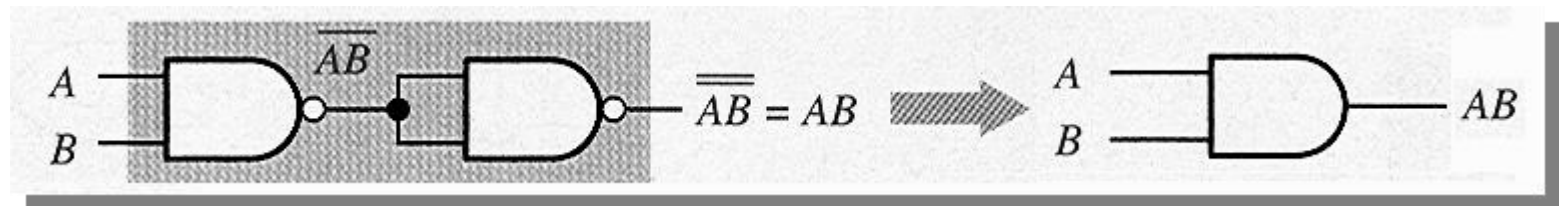




# Universal NAND and NOR Gates

- Three NAND Gates as an OR Gate

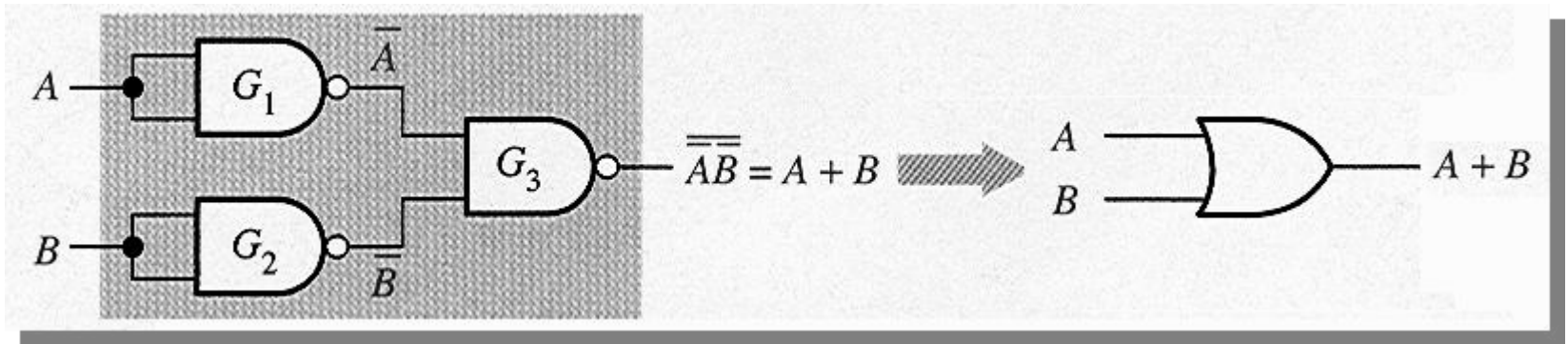

- Four NAND Gates as a NOR Gate

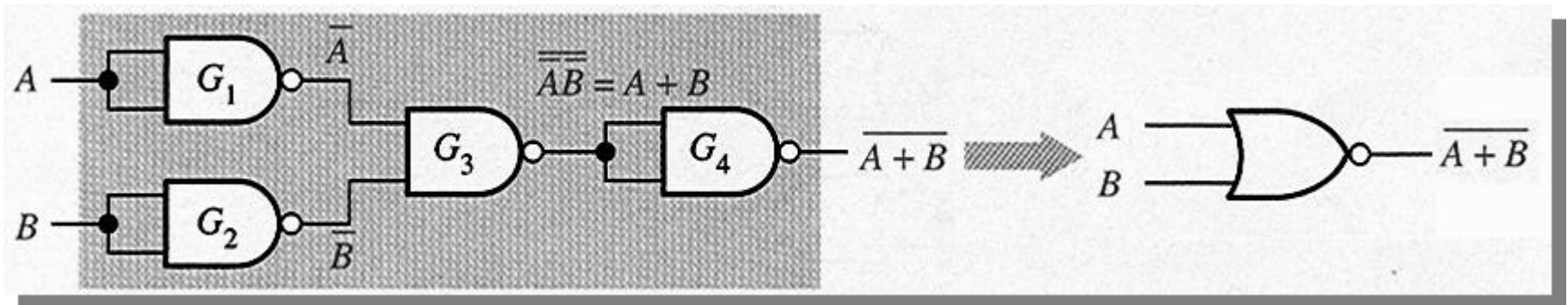


# Universal NAND and NOR Gates

- NOR Gate as an Inverter




- Two NOR Gates as an OR Gate

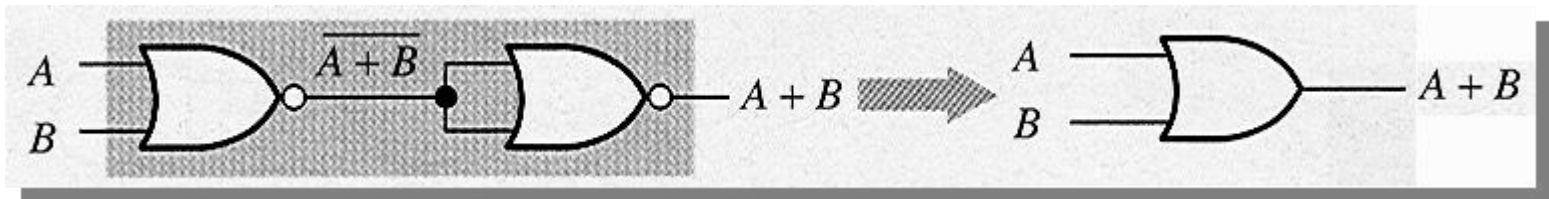


# Universal NAND and NOR Gates

- Three NOR Gates as an AND Gate

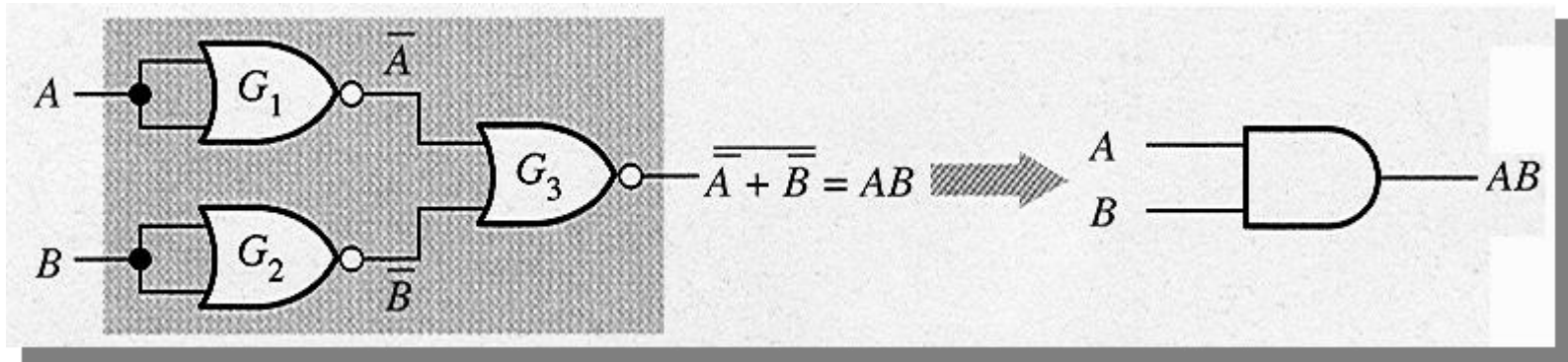


- Four NOR Gates as a NAND Gate

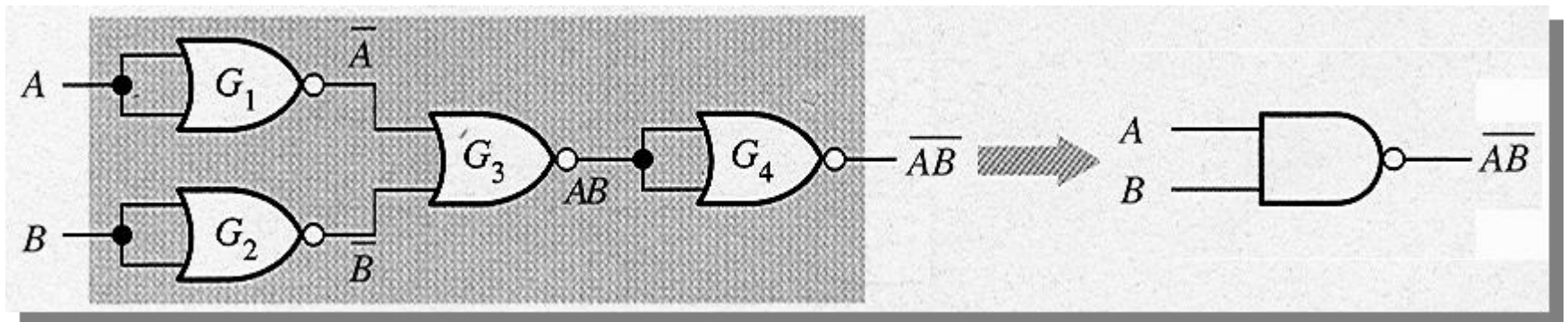

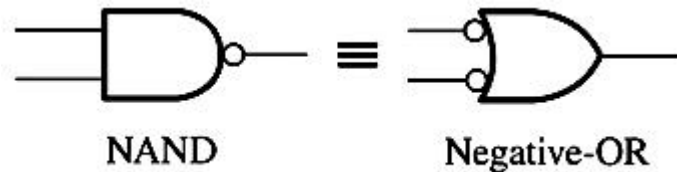
# Using NAND and NOR Gates

- The **NAND** gate is equivalent to the **negative-OR** gate. (dual symbols)



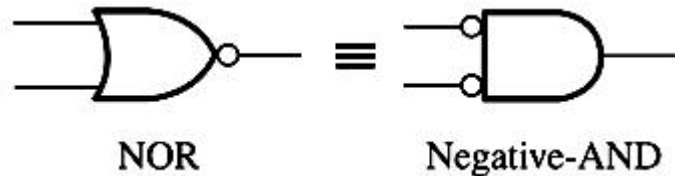
- The **NOR** gate is equivalent to the **negative-AND** gate. (dual symbols)



- To use the appropriate symbols will make “reading” a logic diagram easier.

# Using NAND and NOR Gates


- To read this logic diagram.

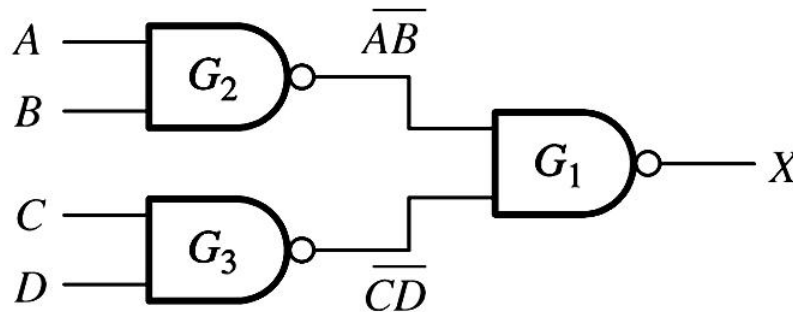

$$X = \overline{\overline{AB} \overline{CD}}$$


$$= \overline{\overline{AB + CD}} = AB + CD$$

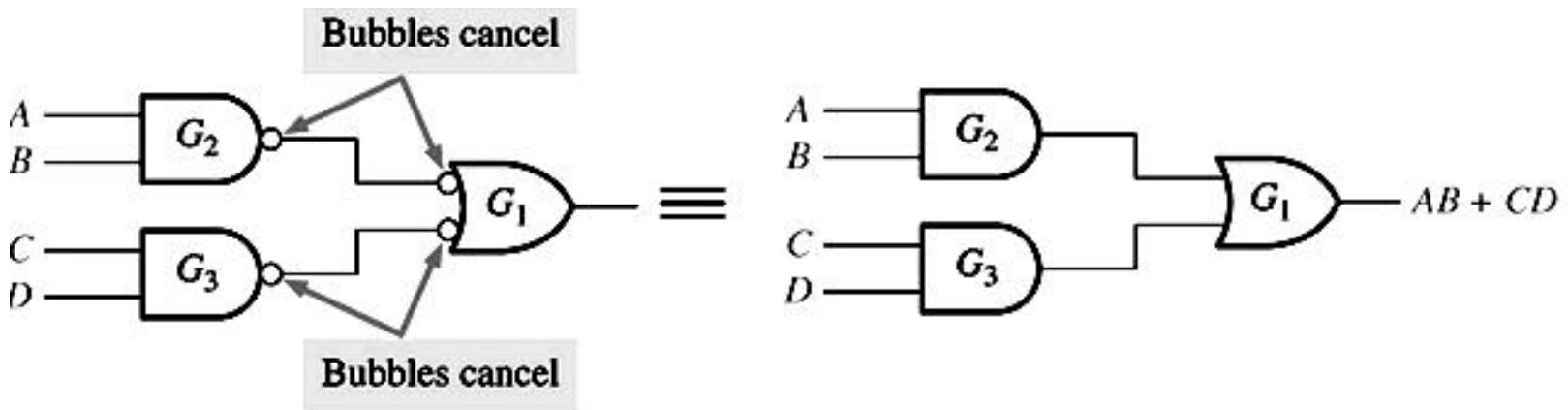- If a negative-OR symbol is used for  $G_1$ , the two bubbles (inversion) will cancel each other.



# Using NAND and NOR Gates

- To read this logic diagram.

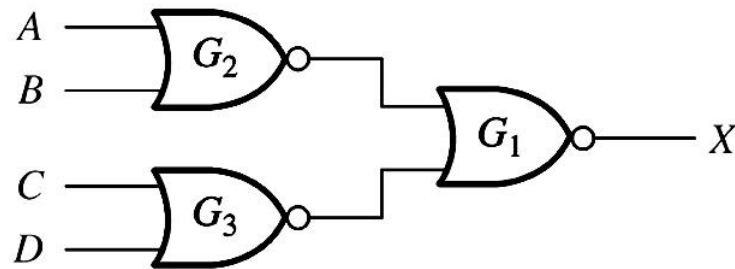

$$\begin{aligned}
 X &= \overline{\overline{A+B+C+D}} \\
 &= \overline{\overline{A+B}} \overline{\overline{C+D}} \\
 &= (A+B)(C+D)
 \end{aligned}$$

- If a negative-AND symbol is used for  $G_1$ , the two bubbles (inversion) will cancel each other.

