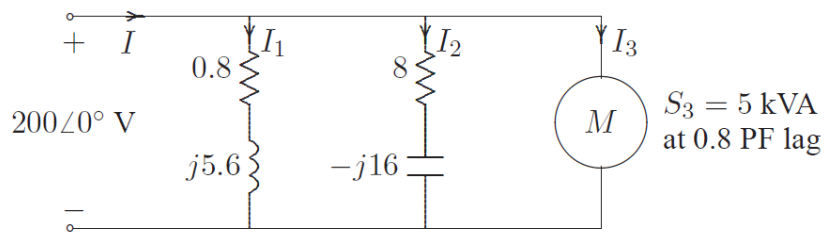



1. Two impedances, $Z_1 = 0.8 + j5.6\Omega$ and $Z_2 = 8 - j16\Omega$, and a single-phase motor are connected in parallel across a 200-V rms, 60-Hz supply as shown in Figure. The motor draws 5 kVA at 0.8 power factor lagging.



[30]

- Find the complex powers S_1 , S_2 for the two impedances, and S_3 for the motor. (10 marks)
- Determine the total power taken from the supply, the supply current, and the overall power factor. (10 marks)
- A capacitor is connected in parallel with the loads. Find the kvar and the capacitance in μF to improve the overall power factor to unity. What is the new line current I ? (10 marks)

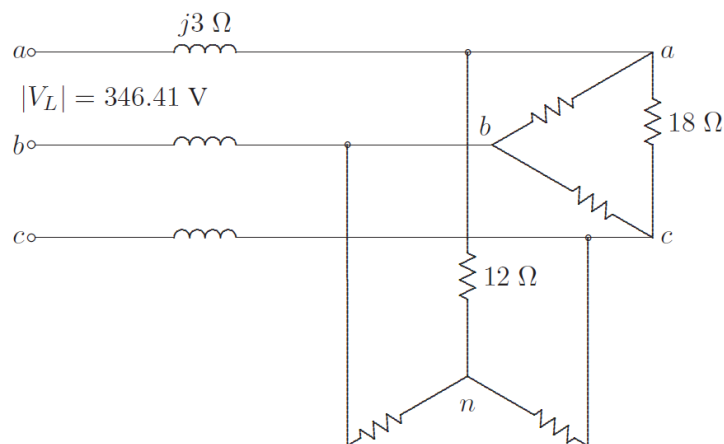2. A balanced Δ -connected load consisting of a pure resistance of 18Ω per phase is in parallel with a purely resistive balanced Y-connected load of 12Ω per phase as shown in the Figure. The combination is connected to a three-phase balanced supply of 346.41-V rms (line-to-line) via a three-phase line having an inductive reactance of $j3\Omega$ per phase. Taking the phase voltage V_{an} as reference, determine.



[20]

- Find the equivalent Y-connected load impedance for the balanced Δ -connected load consisting of a pure resistance of 18Ω per phase, and plot the phase 'a' equivalent circuit of the system. (5 marks)
- The current, real power, and reactive power drawn from the supply. (10 marks)
- The line-to-neutral and the line-to-line voltage of phase a at the combined load terminals? (5 marks)

3. **Essay Writing (Within 400 words)**

Title: The Smart Grid: A Double-Edged Sword?

Please discuss the potential benefits and challenges of implementing smart grid technologies, and select one of the factors like cybersecurity, privacy, and economic impacts to discuss in-depth. [50]