



# EEE109: Bipolar Junction Transistor

## Chapter 4

Dr. Guanying Chu  
guanying.chu02@xjtlu.edu.cn  
Office: SC427  
PPT: Guanying Chu

# Table of Content



- Discuss the physical structure and operation of the **Bipolar Junction Transistor (BJT)**.
  - NPN
  - PNP
- Understand the **DC analysis** and design techniques of bipolar transistor circuits.
- Examine **three basic applications** of bipolar transistor circuits.
  - Inverter function
  - Logic function
  - Amplifier function



# BASIC BIPOLAR JUNCTION TRANSISTOR

Understand the physical structure, operation, and characteristics of the bipolar junction transistors (BJT), including the **npn** and **pnp** devices.
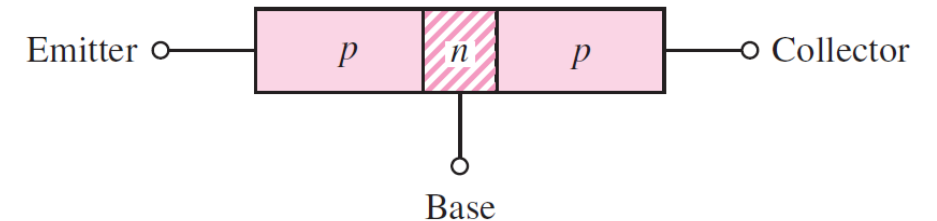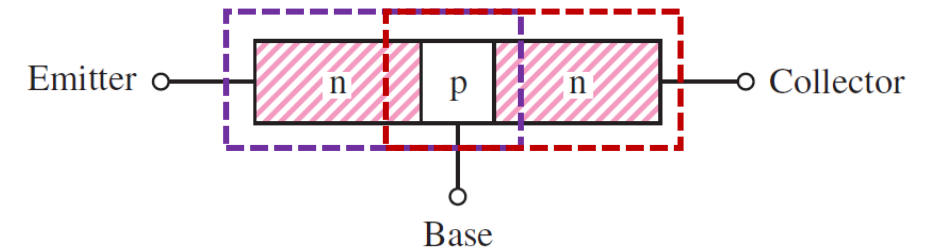
# Transistor Structure



- The **B**ipolar **J**unction **T**ransistor (BJT) has **three** separately doped regions and contains **two** pn junction
  - **n**p**n** bipolar transistor
  - **p**n**p** bipolar transistor
- Chinese Name: 三极管, “三” means three. However, “bi” in **b**ipolar means “two”. Why?




Current in the transistor is due to flow of both **E**lectrons and **H**oles, two carriers results in the name **b**ipolar

- Three terminals are **e**mitter, **b**ased and **c**ollector
  - The width of the **b**ased must be very narrow  $10^{-6}\text{m}$

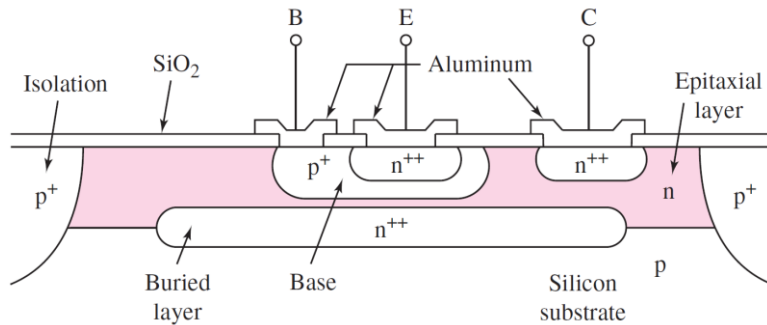
# Transistor Structure



- Cross section of a conventional integrated circuit of npn bipolar Transistor
- The actual model is more complex and device is not even symmetrical!
- Although the block diagram is **highly simplified**, it is still useful for presenting the basic transistor characteristic



Real world

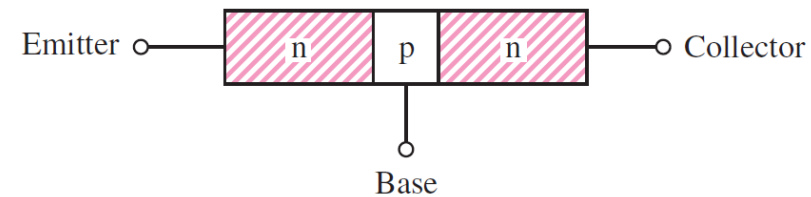


Fairytale

- Note: The trick to learning this chapter well is **not to dig too deeply**, because we are based on an simplified model.
- (有些地方目前不要挖掘太深，简化模型本来就够不精准，放过自己)

# Four bias modes (NPN)

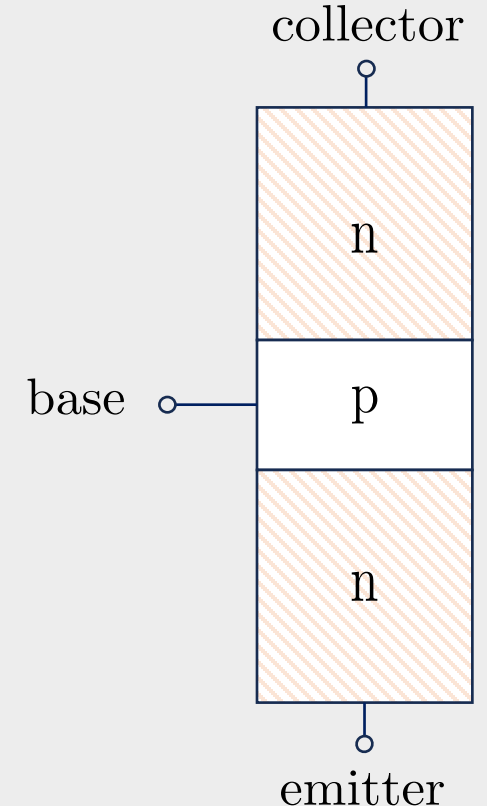


	NPN BJT Transistor	
Saturation	<ul style="list-style-type: none"><li>B-E and B-C junctions are forward-biased</li></ul>	 <p>The diagram illustrates the physical structure of an NPN BJT transistor. It consists of three vertically stacked rectangular regions. The top region is labeled 'collector' and has an 'n' (n-type) label inside. The middle region is labeled 'base' and has a 'p' (p-type) label inside. The bottom region is labeled 'emitter' and has an 'n' (n-type) label inside. Each region is connected to an external terminal, indicated by a small circle and a line. The collector terminal is at the top, the base terminal is on the left side of the middle region, and the emitter terminal is at the bottom.</p>
Cut-off	<ul style="list-style-type: none"><li>B-E and B-C junctions are reversed-biased</li></ul>	
<b>Forward-active mode</b>	<ul style="list-style-type: none"><li>B-E junction is forward biased</li><li>B-C junction is reversed-biased</li></ul>	
Inverse-active mode	<ul style="list-style-type: none"><li>B-E junction is reversed-biased</li><li>B-C junction is forward biased</li></ul>	



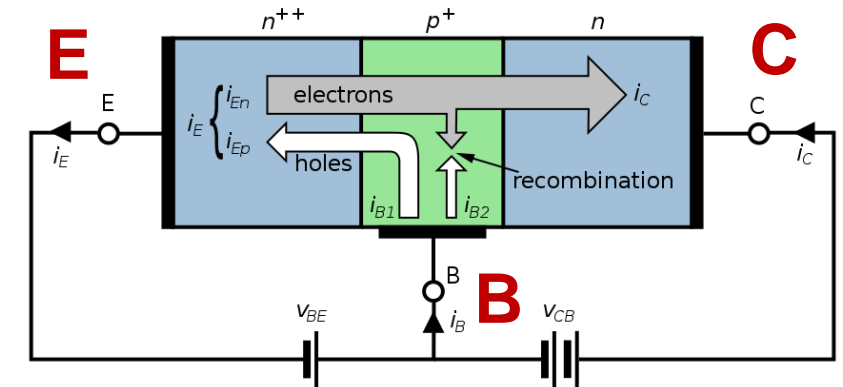
# Forward-active mode (NPN)



- The figure below shows an npn bipolar transistor biased in the forward-active mode.
- **B-E** junction is forward biased
  - Electrons are attracted from emitter to base region
  - Electrons concentration in base is increasing sharply
- **B-C** junction is reversed biased
  - Electrons concentration at the interface (B-C) of the junction is nearly **zero**
  - Then the electrons in the **base** region are attracted to **collector** region by a combination force with **diffusion** and **electric field force**.



# Forward-active mode (NPN)

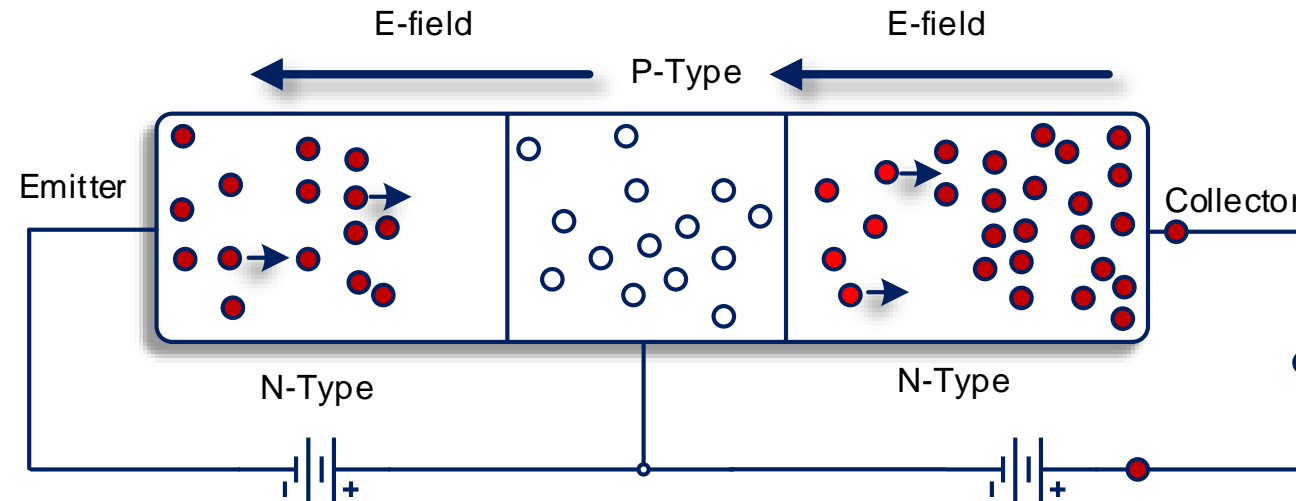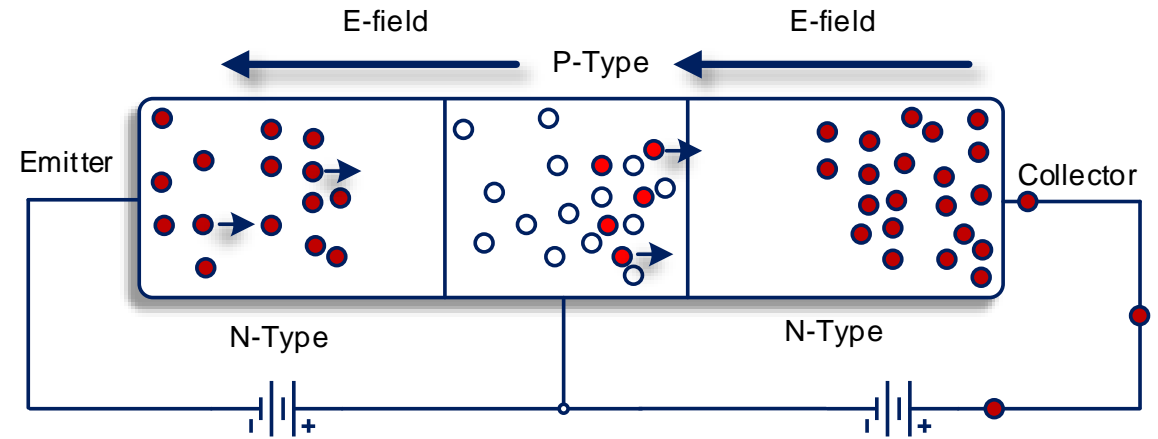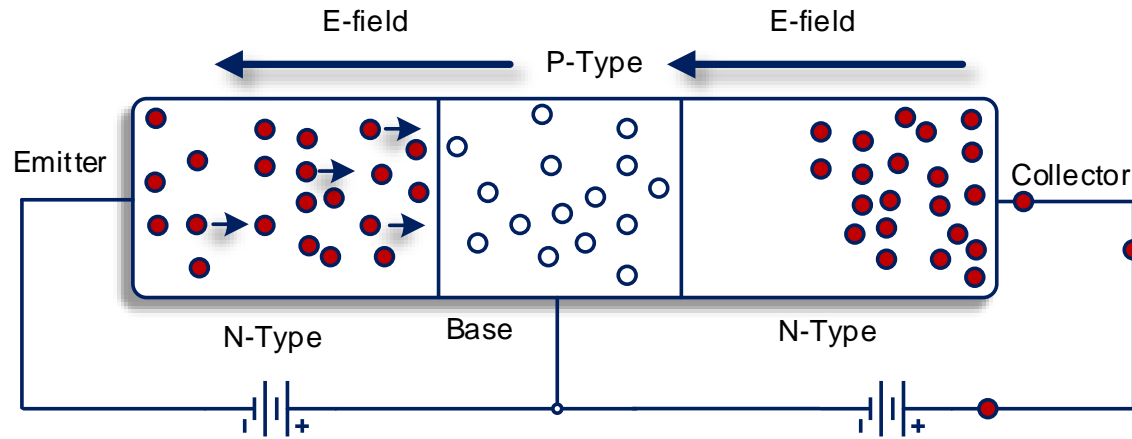



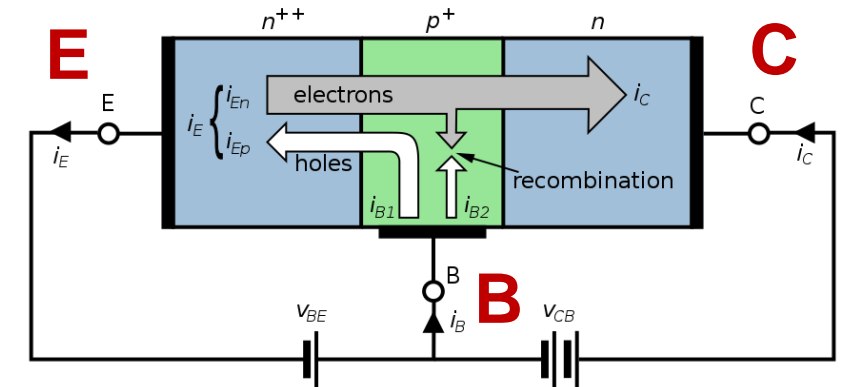
# Forward-active mode (NPN)



- The figure below shows an npn bipolar transistor biased in the forward-active mode.
- **B-E** junction is forward biased
  - Electrons are attracted from emitter to base region
  - Electrons concentration in base is increasing sharply
- **B-C** junction is reversed biased
  - Electrons concentration at the interface (B-C) of the junction is nearly **zero**
  - Then the electrons in the **base** region are attracted to **collector** region by a combination force with **diffusion** and **electric field force**.



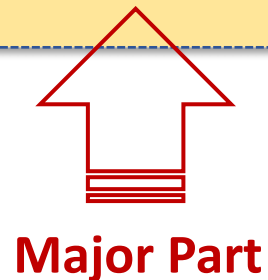
# Transistor current (active region)





- The current in a BJT consists of three parts
  1. Emitter current (results of **Electrons** Moving)
  2. Collector current (results of **Electrons** Moving)
  3. Based Current (results of **Holes** Moving)

Emitter Current = **Collector Current** + Based Current



**Major Part**

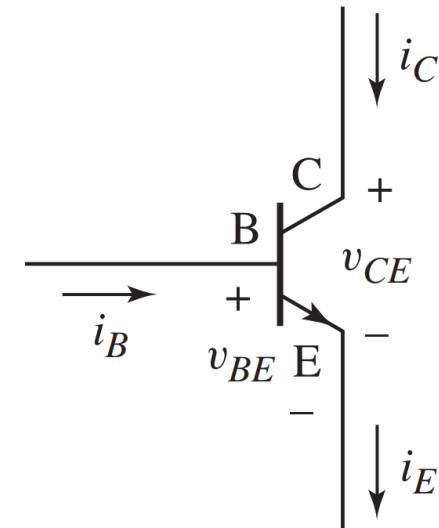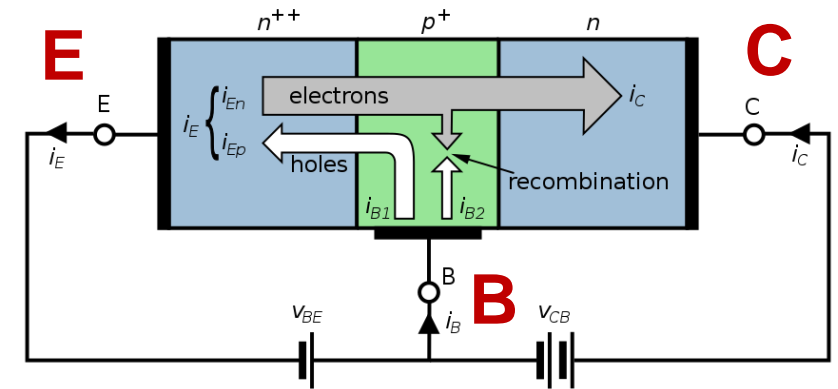

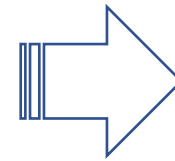
# Emitter Current




- The B-E junction is forward biased, the current through this junction to be exponential function of B-E voltage, consider that  $V_{BE} \gg V_T$  ( $V_T$  is thermal voltage = 0.026V)

$$i_E = i_{EO} \left( e^{\frac{v_{BE}}{V_T}} - 1 \right) \cong i_{EO} e^{\frac{v_{BE}}{V_T}}$$



It is the current equation of the diode  
(这个就是二极管的电流公式)

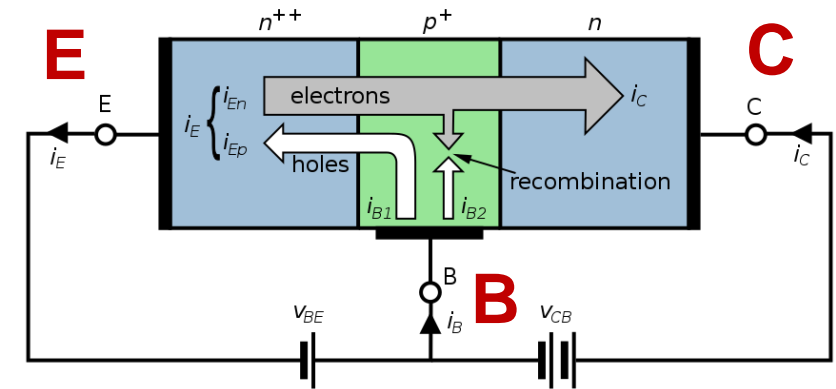
- The electrons flow from the **emitter** into the **base**
- The emitter current is out of the emitter terminal


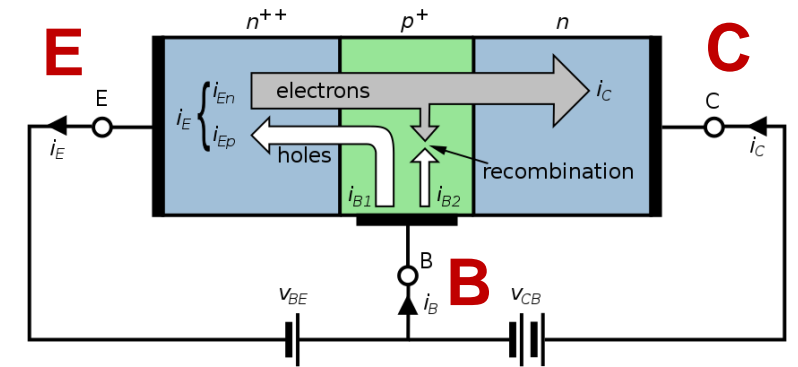
# Collector Current



- The number of the injected electrons reaching the collector is the major component of collector current, which is coming from the emitter current (流进C端的电流主要是从E端来的, 看下图箭头, 想象成河流分支)
- Therefore, collector current is dependent on the emitter current.
- **B-E** voltage affects the collector current, but B-C can not.



$$i_c = \alpha i_E$$

$\alpha$  is the **common-base current gain**, it must less than 1 (but very close to it)


# Base Current



- The base current consists of two parts
- B-E junction is forward biased
  - Holes from the base are injected in to the emitter due the electric filed,  $i_{B1}$
- A few holes recombine with the electrons coming from the emitter, the recombination current is  $i_{B2}$

$$i_B = i_{B1} + i_{B2}$$

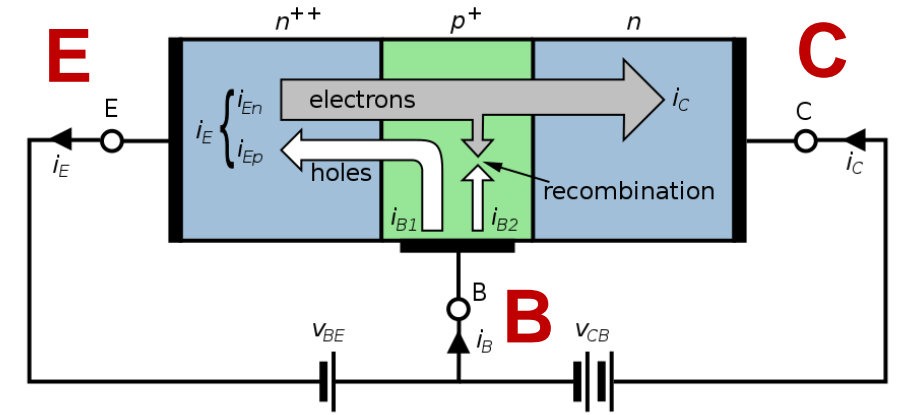- But the base current is extremely **small**



# Common-emitter current gain $\beta$



- In the BJT, **B-E** voltage can affect the collector current and base current. It means that collector current and base current are linearly related (线性相关). The ratio of collector and base current is defined:

$$\frac{i_C}{i_B} = \beta$$

- $\beta$  is the common-emitter current gain, usually  $50 < \beta < 300$ .
- Be caution, you should remember this ratio must **greater than 1**.
- Some factors may affect this ratio, such as the **temperature**.

# Current relationship in BJT



- If we treat the BJT as a single node, by KCL


$$i_E = i_B + i_C$$

- If the npn BJT is biased in the forward active-mode


$$i_C = \beta i_B \quad i_C = \alpha i_E$$

- With above three equations, we can derive  $i_E = (i_C / \beta) + i_C$
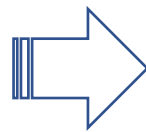
$$i_C = \left( \frac{\beta}{1 + \beta} \right) i_E = \alpha i_E$$



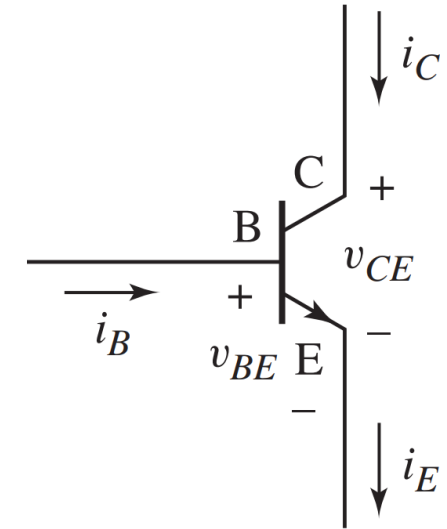
$$\alpha = \frac{\beta}{1 + \beta} \rightarrow \beta = \frac{\alpha}{1 - \alpha}$$


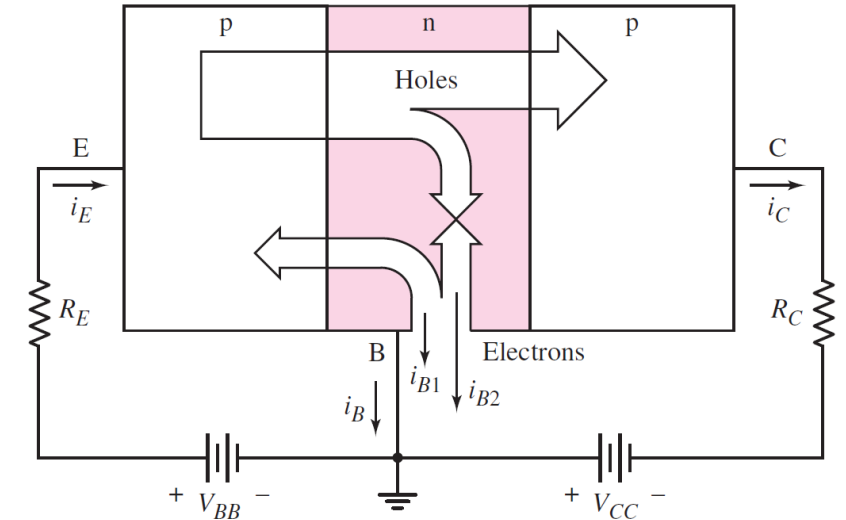
# Forward-active mode (PNP)






- Still consider the transistor biased in **forward-active** mode
- B-E junctions is forward biased
  - Holes are flow from the emitter in the based
- B-C junction is reversed bias
  - Hole concentration at the interface (B-C) of the junction is nearly zero
  - Then the Hole in the base region is attracting to collector region by a combination force with **diffusion** and **electric field** force.





# Forward-active mode (PNP)

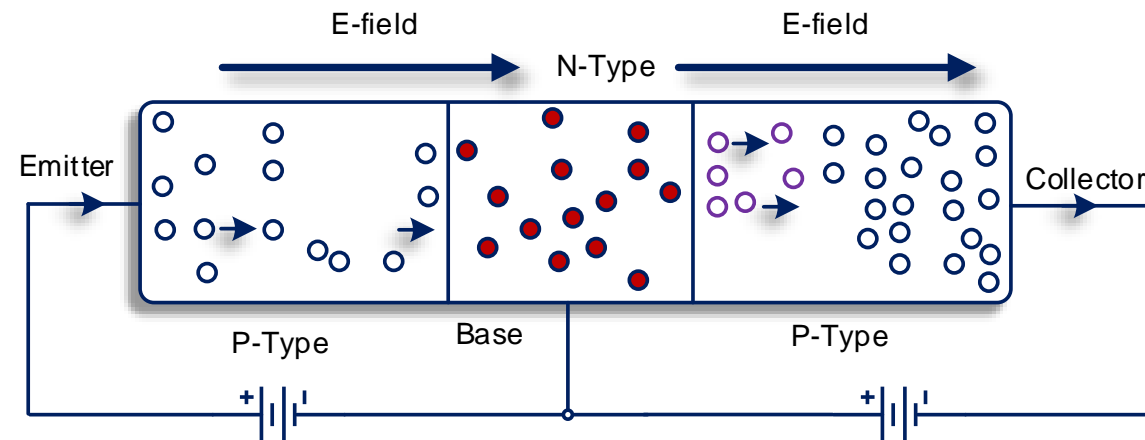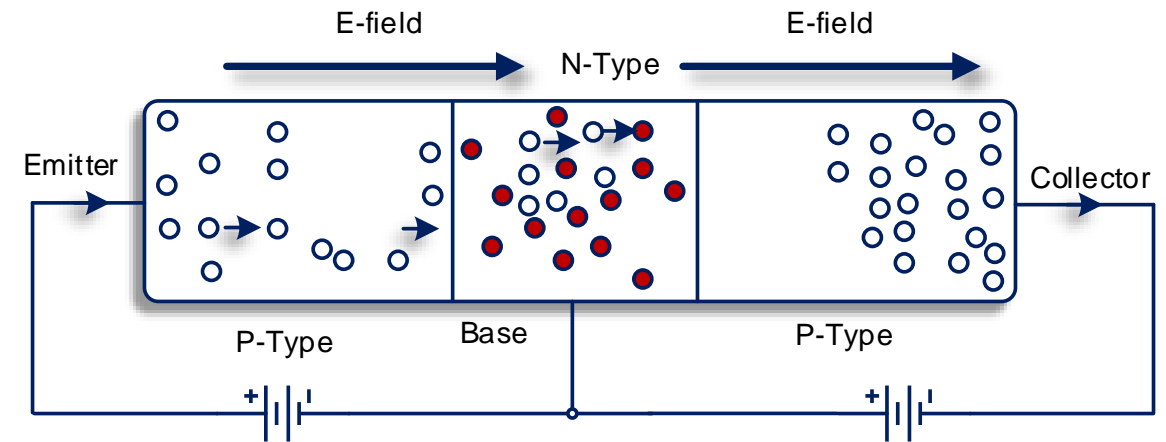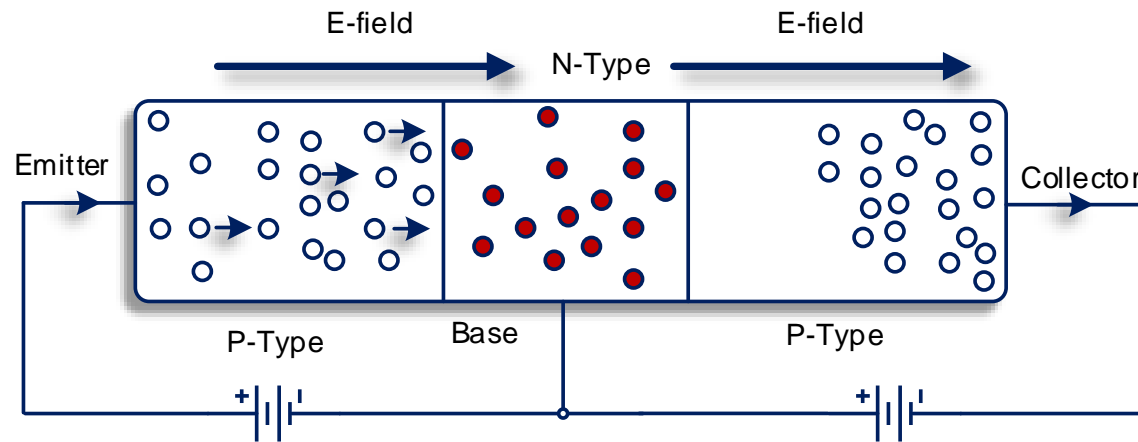

# Emitter and collector Current




- The B-E junction is forward biased, the current through this junction to be exponential function of B-E voltage, sider that  $V_{EB} \gg V_T$

$$i_E = i_{EO} \left( e^{\frac{v_{EB}}{V_T}} - 1 \right) \cong i_{EO} e^{\frac{v_{EB}}{V_T}}$$

- The collector current is an exponential function of the E-B voltage
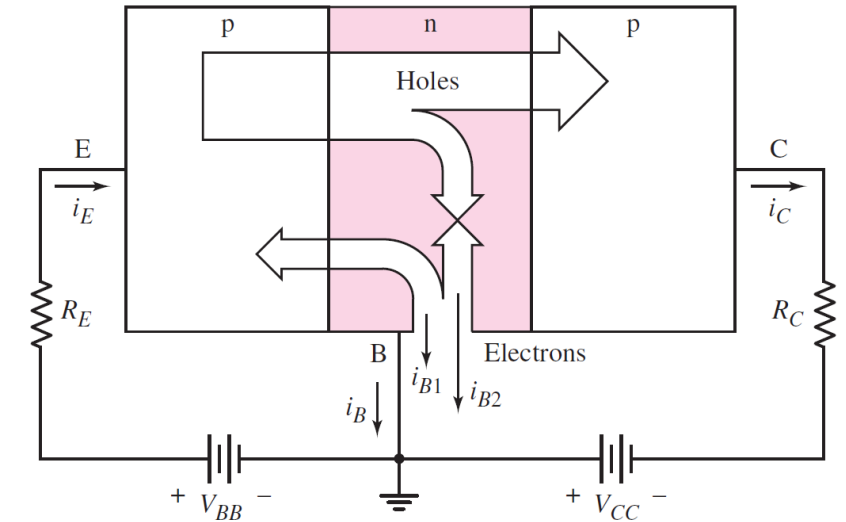
$$i_c = \alpha i_E = i_{EO} e^{\frac{v_{EB}}{V_T}}$$




# Base current (PNP)



- E-B junction is forward biased
  - Electrons from the base are injected in to the emitter due the electric field,  $i_{B1}$
- A few Electrons recombine with the holes coming from the emitter, this current is recombination current,  $i_{B2}$

$$i_B = i_{B1} + i_{B2}$$

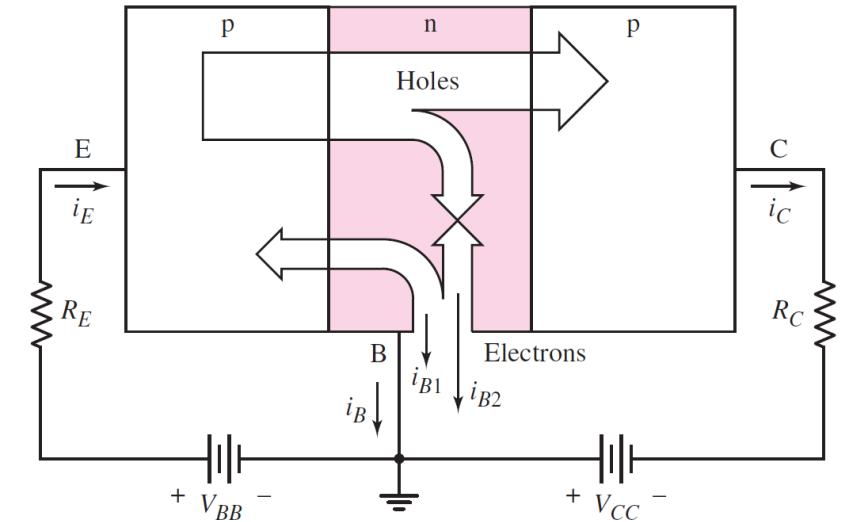
- But the base current is extremely **small**


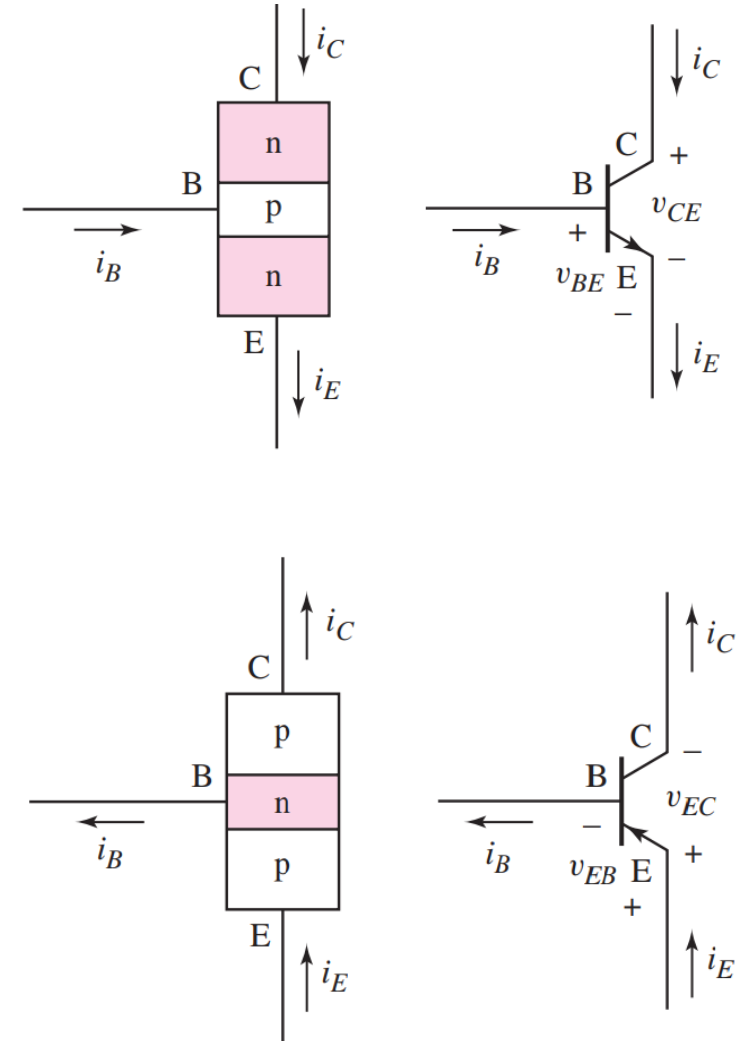
# Circuit symbol



- For **npn** device
  - Direction of the emitter current: out of the emitter
  - Collector current: caused by the movement of **Electron** (电子运动产生电流)
- For **pnp** device
  - Direction of the emitter current: into the emitter
  - Collector current: caused by the movement of **Hole** (空穴运动产生电流)




# Summary of BJT Equation



NPN	PNP
$i_E = i_{EO} e^{\frac{v_{BE}}{V_T}}$	$i_E = i_{EO} e^{\frac{v_{EB}}{V_T}}$
$i_C = \alpha i_E = i_{EO} e^{\frac{v_{BE}}{V_T}}$	$i_C = \alpha i_E = i_{EO} e^{\frac{v_{EB}}{V_T}}$
$i_B = i_C / \beta$	$i_B = i_C / \beta$

For both transistors
$i_E = i_B + i_C \quad i_E = (1 + \beta) i_B \quad i_C = \beta i_B \quad i_C = \alpha i_B$
$\alpha = \frac{\beta}{1 + \beta} \rightarrow \beta = \frac{\alpha}{1 - \alpha}$

# Reinforce Your Learning (Exercise)

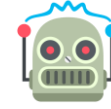

- An npn transistor is biased in the forward-active mode. The base current is  $I_B = 5\mu\text{A}$  and the collector current is  $I_C = 0.62\text{mA}$ . Determine  $I_E$ ,  $\beta$ , and  $\alpha$ .
- **Solution**


# DC ANALYSIS OF TRANSISTOR CIRCUIT

Understand and become familiar with the **DC** analysis and design techniques of bipolar transistor circuits

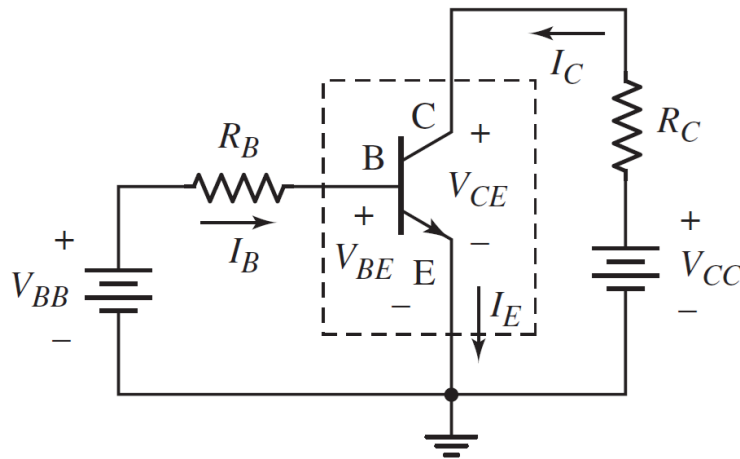
# Common Emitter circuit




- In forward-active region
  - B-E junction is **forward biased**, voltage drop is  $V_{BE(on)}$
  - B-C junction is reverse biased, it can be regarded as a dependent **current source**  $I_C = \beta I_B$



Common-emitter circuit

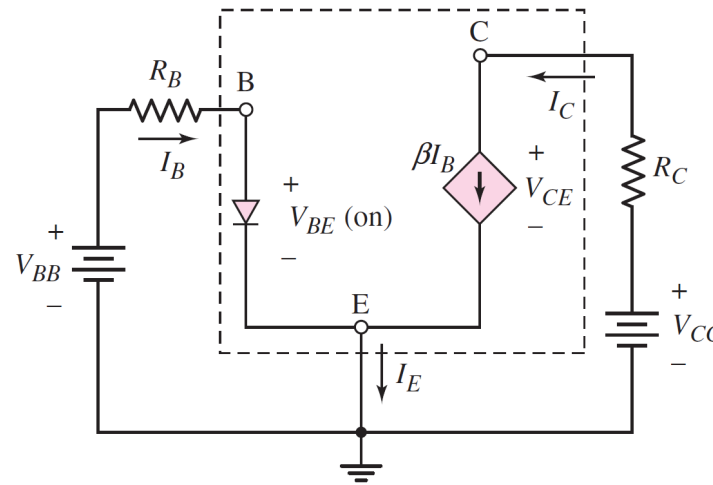

DC equivalent circuit

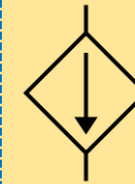

**Voltage controlled current source (VCCS)**: is a current source where the current is controlled by a voltage elsewhere in the circuit. Where? we will find it



# Common Emitter circuit (NPN)




- The base current is

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B}$$

$$I_C = \beta I_B \quad V_{CE} = V_{CC} - I_C R_C$$

- The power dissipated on the transistor is

$$P_T = I_B V_{BE(on)} + I_C V_{CE}$$

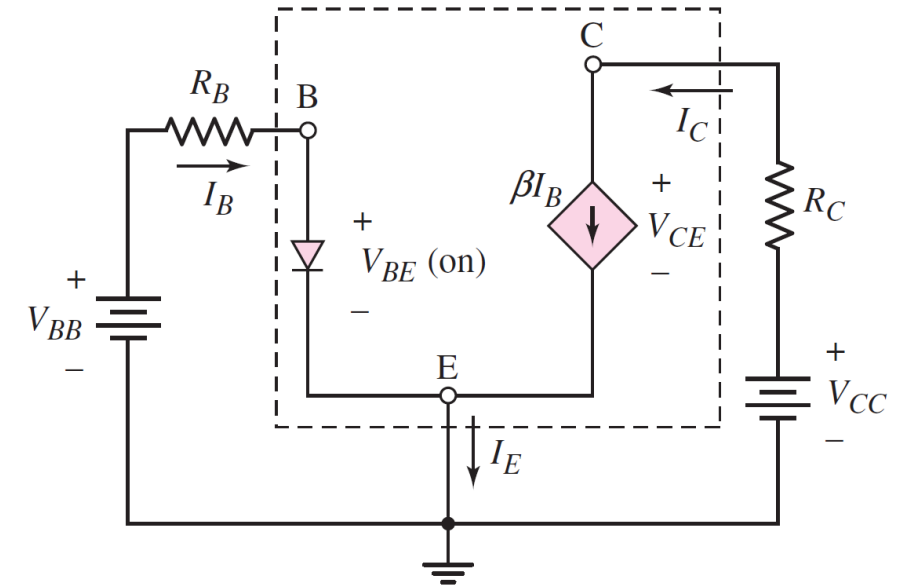

# BJT in saturation mode





- For the C-E portion of the circuit

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B} \quad V_{CE} = V_{CC} - I_C R_C$$

- If we increase  $V_{BB}$ ,  $I_B$  increase. To a point that  $I_C$  no longer increase, BJT switches to **Saturation mode**

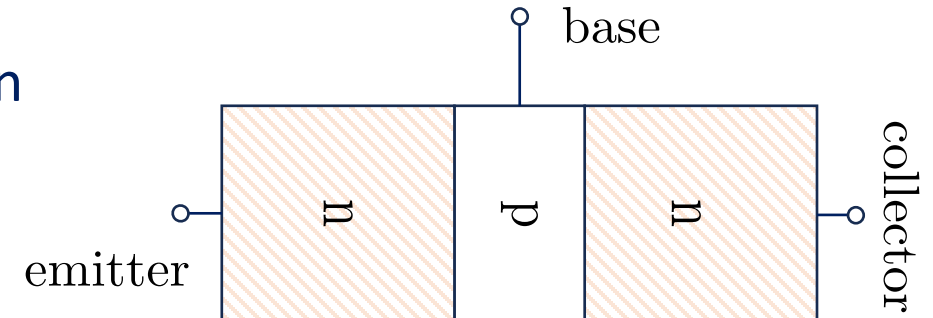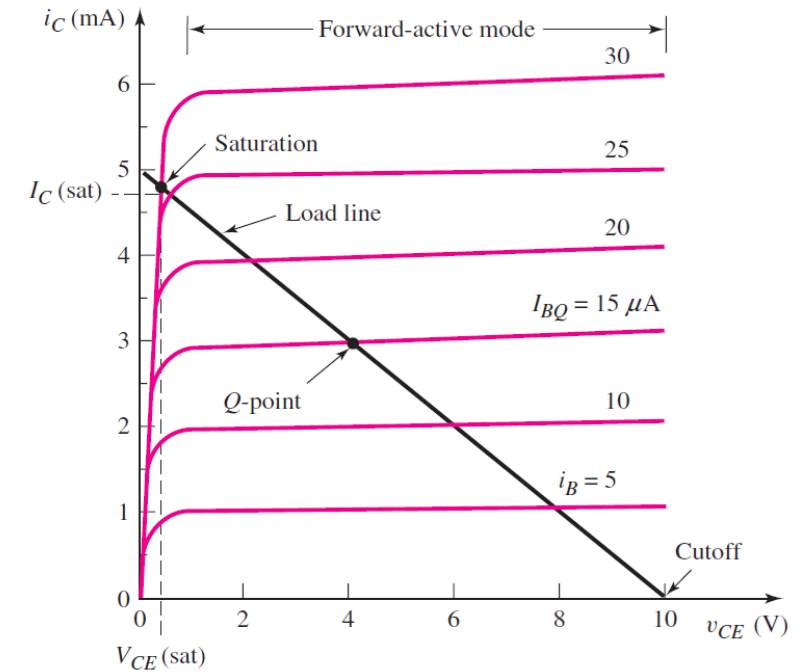
- B-C junction becomes forward biased
- C-E voltage in saturation  $V_{CE(sat)}$ , constant value in range of **0.1 to 0.3V**



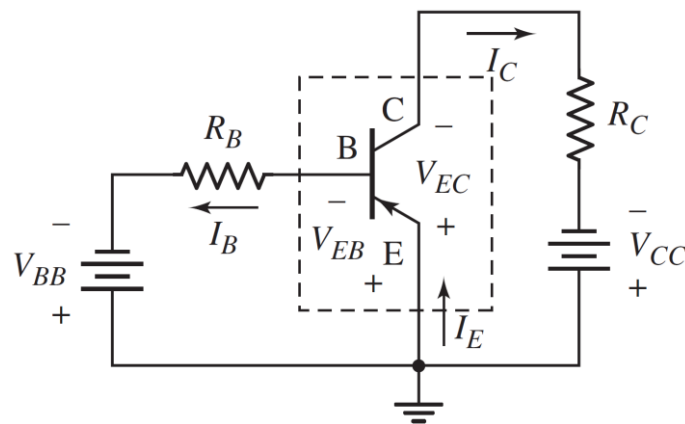
# Common-Emitter Circuit (PNP)




- In forward-active region
  - B-E junction is **forward biased**, voltage drop is  $V_{EB(on)}$
  - B-C junction is **reverse biased**, it can be regarded as a dependent current source  $I_C = \beta I_B$



Common-emitter circuit

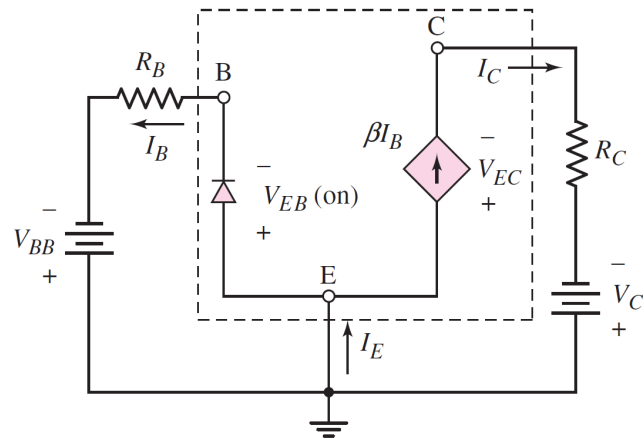

DC equivalent circuit

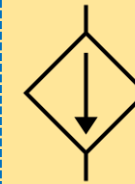

**Voltage controlled current source (VCCS):** is a current source where the current is controlled by a voltage elsewhere in the circuit. Where? we will find it

# Common-Emitter Circuit (PNP)




- The base current is

$$I_B = \frac{-V_{EB(on)} + V_{BB}}{R_B}$$

$$I_C = \beta I_B \quad V_{EC} = V_{CC} - I_C R_C$$

- The power dissipated is

$$P_T = I_B V_{BE(on)} + I_C V_{EC}$$

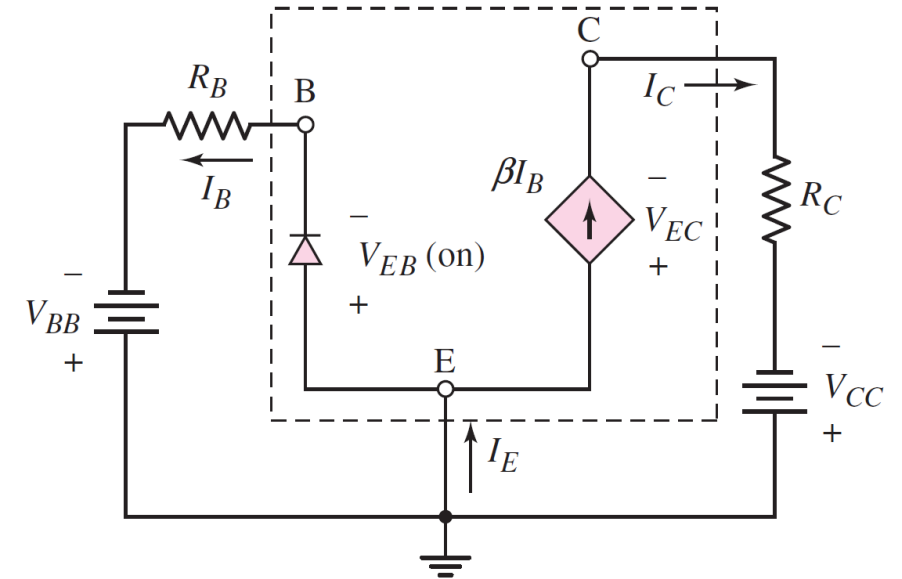

# Problem-Solving Technique



- As usual, we still need to make assumptions. Assume the state of the transistor, then analyze the circuit to determine if we have a solution consistent with initial guess

1. Assume that the BJT is biased in the forward-active mode


$$V_{BE} = V_{BE(on)} \quad I_B > 0 \quad I_C = \beta I_B$$

2. Analyze the “linear” Circuit with this assumption


3. Evaluate the resulting state of transistor

- If  $V_{CE} > V_{CE(sat)}$ , assumption is correct

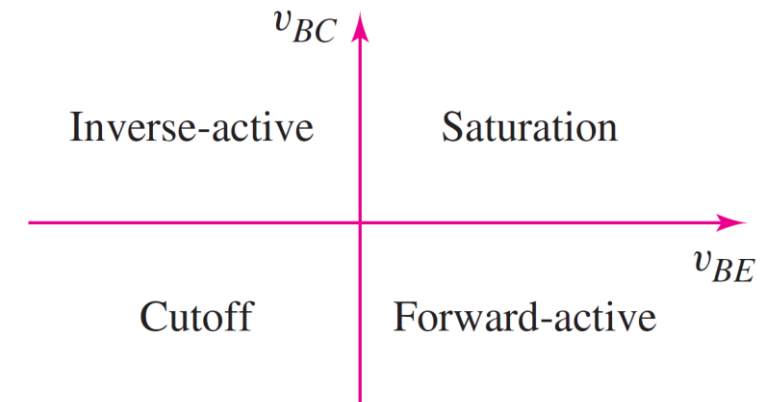
4. If the initial assumption is incorrect, we need make a new assumption and return to Step 2



# Reinforce Your Learning (Exercise)

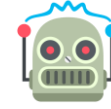

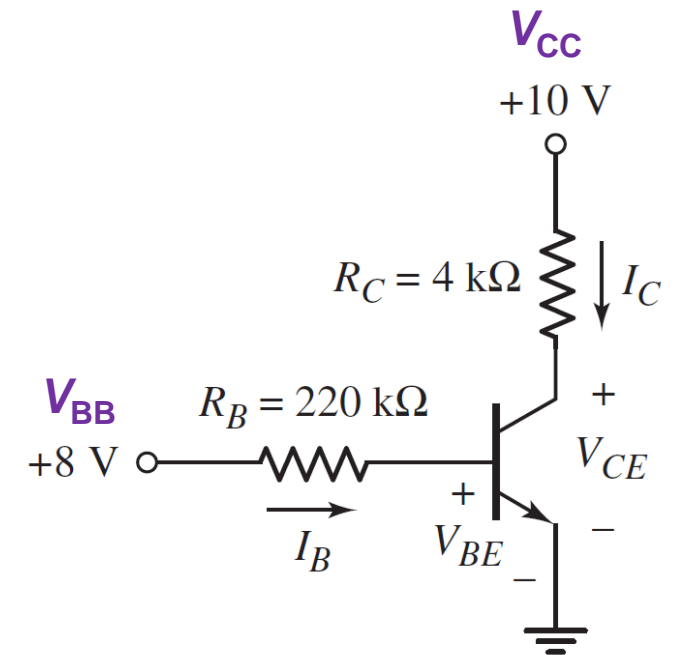
- Calculate the emitter currents and C-E voltages in a circuit. The transistor parameters are  $\beta = 100$ , and  $V_{BE}(\text{ON}) = 0.7\text{V}$ . If the transistor is biased in saturation, assume  $V_{CE}(\text{sat}) = 0.2\text{V}$ .
- **Solution** Try to assume the transistor is biased in the **forward-active region**


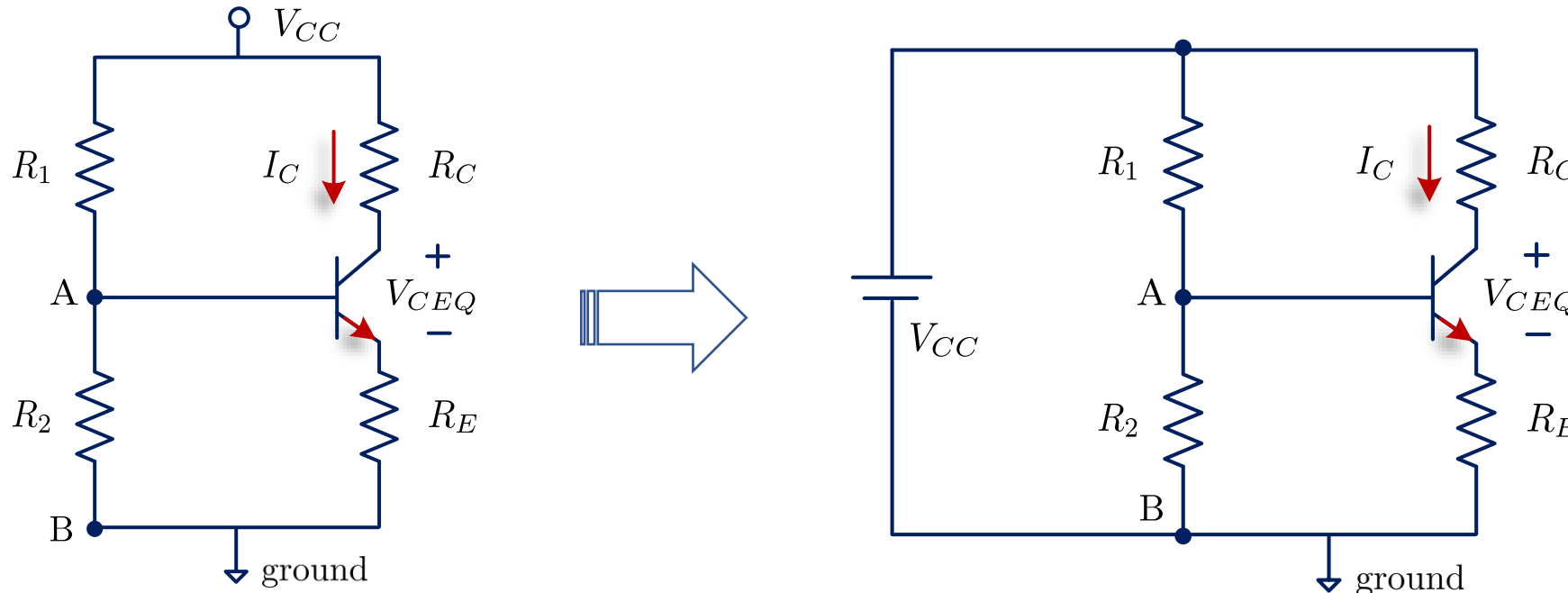
# Voltage Divider Biasing




- The circuit below is a common-emitter circuit with an emitter resistor and voltage divider bias circuit in the base.  $R_1$  and  $R_2$  are the bias resistor.  $R_C$  is the collector resistor and  $R_E$  is the emitter resistor.
- The **Thevenin equivalent circuit** can be used to analyze this circuit


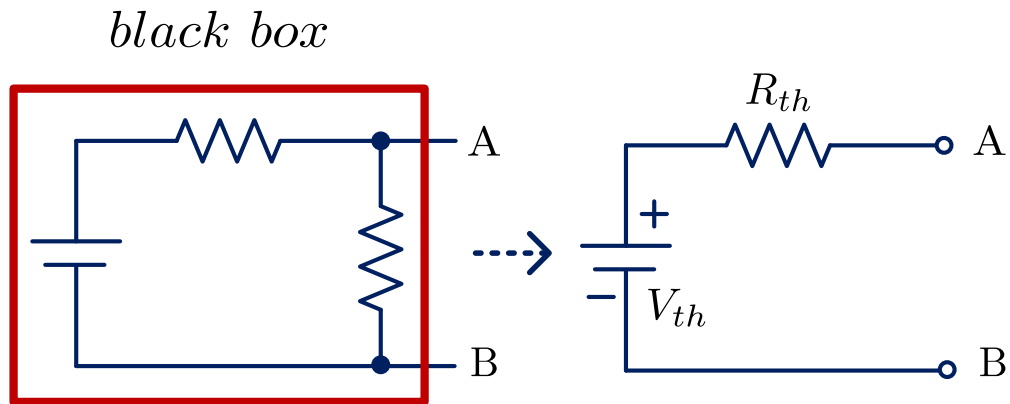
# Thevenin Equivalent Circuit



- Thevenin equivalent circuit is the content in EEE103. Let us review it together.




- Any combination of voltage and resistances with **two terminals** can be replaced by a single voltage source  $V_{th}$  and a single series resistor  $R_{th}$


- $V_{th}$ : The open-circuit voltage at the output of the original circuit;
- $R_{th}$ : The resistance measured across output into the circuit, by replacing voltage source with short circuit and current source with open circuit




# Example of Thevenin Circuit

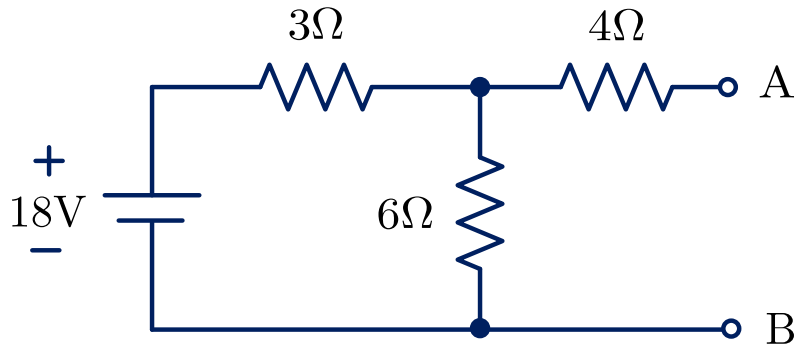
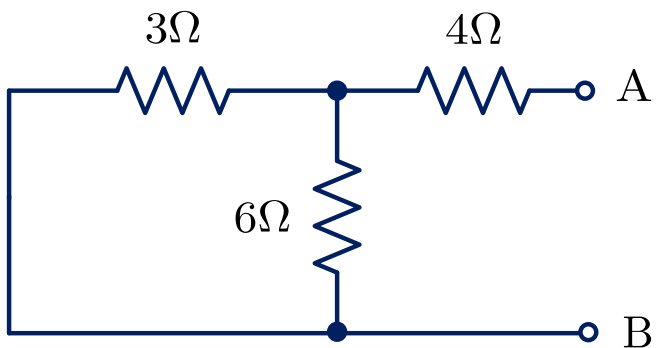
$$V_{th} = V_{AB} = 18 \times \left( \frac{6}{6 + 3} \right) = 12V$$


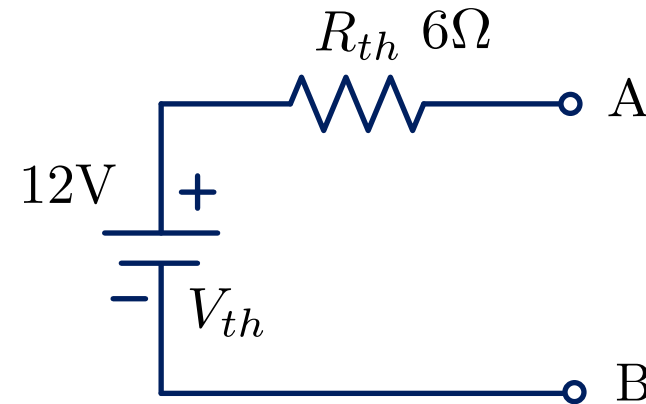
$$R_{th} = 4 + (6 \parallel 3) = 6\Omega$$



# Thevenin Equivalent Circuit



- Thevenin equivalent circuit

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$
$$R_{TH} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


- Apply KVL around the B-E Loop

$$V_{TH} = I_{BQ} R_{TH} + V_{BE}(on) + I_{EQ} R_E$$

$$I_{EQ} = (1 + \beta) I_{BQ} \quad I_{BQ} = \frac{V_{TH} - V_{BE}(on)}{R_{TH} + (1 + \beta) R_E} \quad I_{CQ} = \beta I_{BQ}$$


$$\Rightarrow V_{CEQ} = V_{CC} - I_{CQ} R_C - I_{EQ} R_E$$

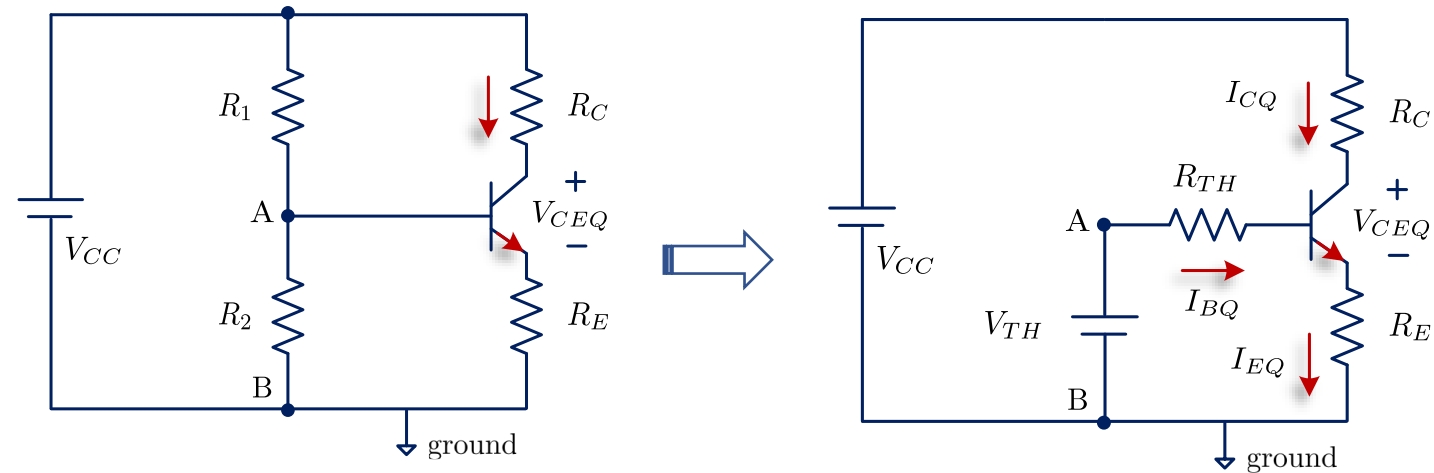Assume transistor biased in **active region**




**Q** here for quiescent, indicating the value for **DC** component

# Reinforce Your Learning (Exercise)

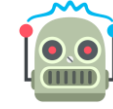

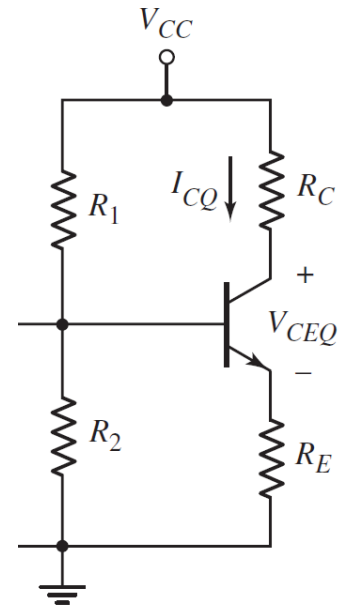- Analyze a circuit using a voltage divider bias circuit. Determine the value of  $R_{th}$ ,  $V_{TH}$ ,  $I_{BQ}$ ,  $I_{CQ}$  and  $V_{CEQ}$ .  $R_1 = 56k\Omega$ ,  $R_2 = 12.2k\Omega$ ,  $R_C = 2k\Omega$ ,  $R_E = 0.4k\Omega$ ,  $V_{CC} = 10V$ ,  $V_{BE(on)} = 0.7V$ ,  $\beta = 100$
- Solution** Using the Thevenin equivalent circuit




# BASIC TRANSISTOR APPLICATIONS

Examine three applications of bipolar transistor circuits: a **switch circuit**, **digital logic circuit**, and an **amplifier circuit**.
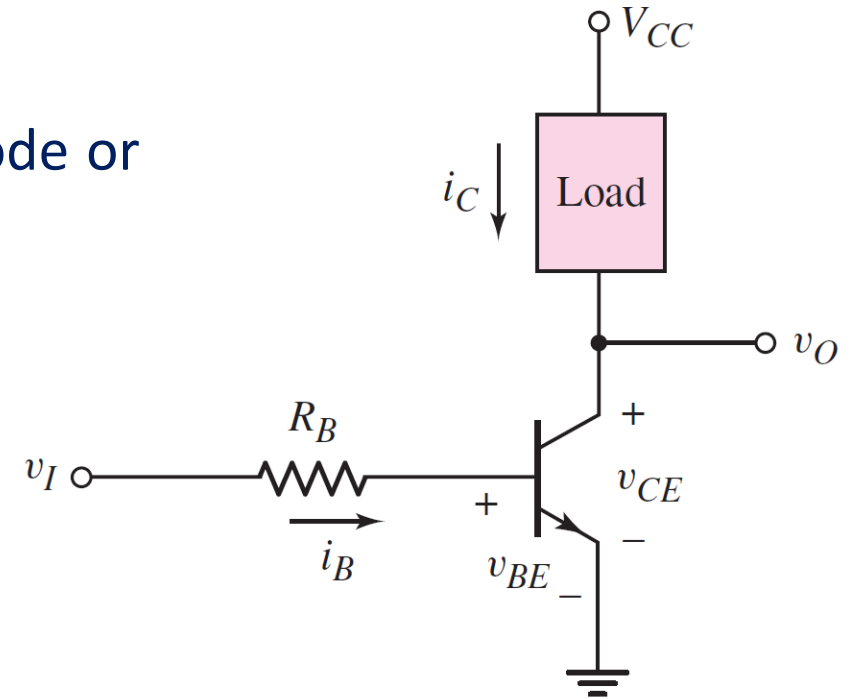
# Transistor Inverter circuit



- The bipolar circuit shown below is called an inverter
  - The transistor is switched between **cutoff** and **saturation**
- The load in this circuit could be a motor, a light-emitting diode or some other electrical device
- If  $V_i < V_{BE}(ON)$ 
  - The transistor is cutoff,  $i_c = 0$ ,  $v_o = V_{CC}$
- If  $V_i = V_{CC}$ 
  - The transistor is driven to saturation,  $v_o = V_{CE}(sat)$




Inverter circuit

$$i_C = I_C(sat) = \frac{V_{CC} - V_{CE}(sat)}{R_C}$$
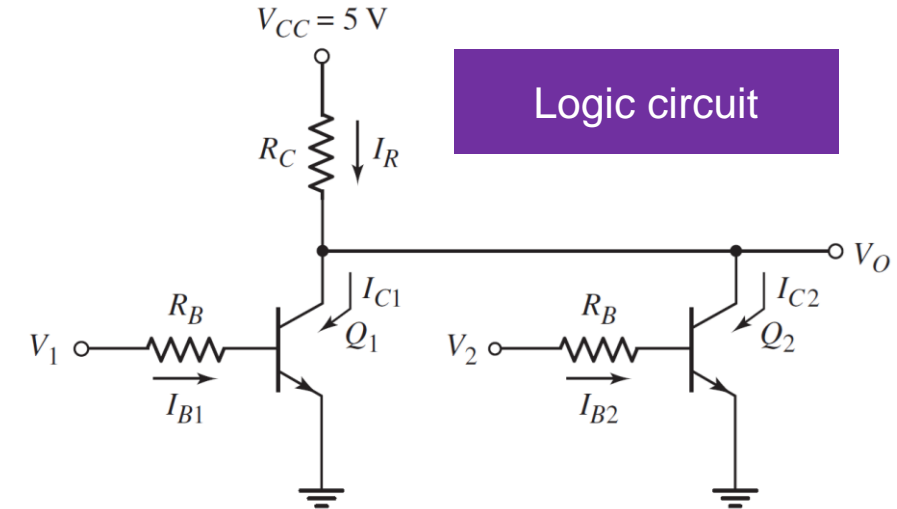
# Digital Logic Circuit



- When  $V_1 = V_2 = 0$  ( $Q_1$  and  $Q_2$  are cutoff.  $V_o = V_{CC}$  high-level)
- When  $V_1 = 5V$  and  $V_2 = 0V$ 
  - $Q_1$  is in saturation, and  $Q_2$  is cutoff
  - $V_o = V_{CE}(\text{sat}) = 0.2V$
- When  $V_1 = 0V$  and  $V_2 = 5V$ 
  - $Q_1$  is in cutoff, and  $Q_2$  is in saturation
  - $V_o = V_{CE}(\text{sat}) = 0.2V$
- When  $V_1 = V_2 = 5V$ 
  - $Q_1$  and  $Q_2$  is in saturation
  - $V_o = V_{CE}(\text{sat}) = 0.2V$




Bipolar NOR logic circuit response		
$V_1(V)$	$V_2(V)$	$V_o(V)$
0	0	<b>5 High</b>
5	0	0.2 Low
0	5	0.2 Low
5	5	0.2 Low

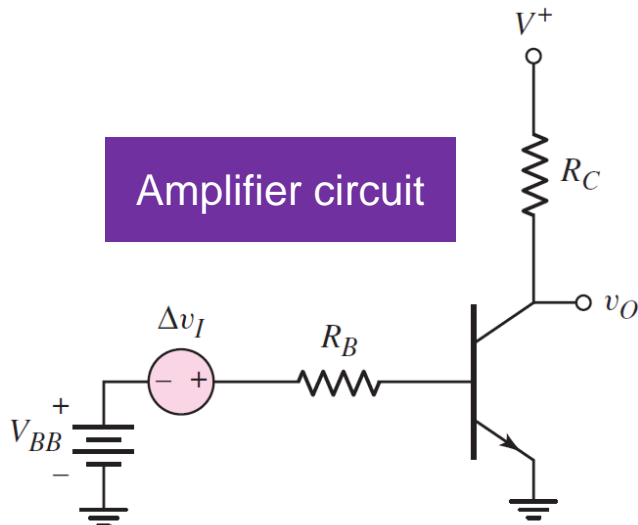
# Amplifier



- The bipolar circuit can also be used to amplify a time-varying signal. In this circuit:
  - $\Delta v_I$  is a time-varying voltage source (ac signal)
  - $V_{BB}$  is a constant DC-voltage. The function is to bias the transistor in the active region




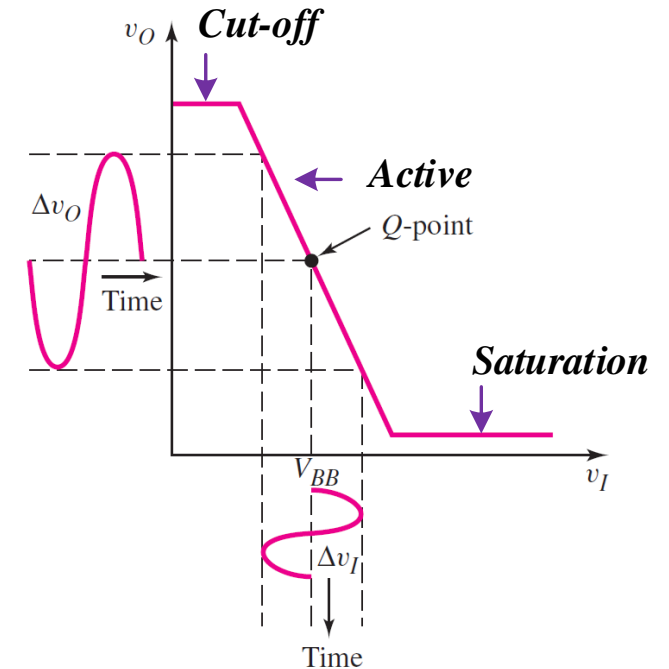- If the magnitude of the slope of the transfer characteristic is greater than 1, then the time-varying output signal will be greater than the time-varying input signal



Transfer Characteristic

# Reinforce Your Learning (Exercise)

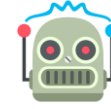

- The following circuit is a transistor inverter circuit. Determine the  $R_B$  such that  $V_o = 0.2V$  and  $I_C/I_B = 20$  when  $V_I = 5V$ , and  $V_{BE(ON)} = 0.7V$

- Solution**

