

Lecture 7
of
EEE201

CMOS Digital Integrated Circuits

Department of Electrical & Electronic Engineering
Xi'an Jiaotong-Liverpool University (XJTLU)

Tuesday, 24th October & 7th November 2023

□ Building Logic Gates from MOSFETs

- combinational logic circuits
- basic logic gates & their combinations
- MOSFETs in series or parallel to implement logic functions
- schematic circuit to IC layout



Digital Circuits from Logic Gates

(implementing Boolean functions)

- ❑ In CMOS digital integrated circuits (ICs), **MOSFETs** are used to build digital **logic gates**.
- ❑ Digital **logic gates** implement **Boolean functions** such as **NOT**, AND, OR, XOR, **NAND**, **NOR**, XNOR.
 - Any logic function/operation can be constructed from three basic logic gates: NOT, AND, and OR.
 - In CMOS digital ICs, NOT, NAND and NOR are adopted as the basic logic gates for implementing any complex logic function/operation.
 - Building complex digital circuits starts from the basic logic gates implemented by MOSFETs.
 - focus on NOT, NAND & NOR gates in EEE201




Xi'an Jiaotong-Liverpool University

西交利物浦大學

Combinational Logic Circuits

(outputs depends on only current inputs)

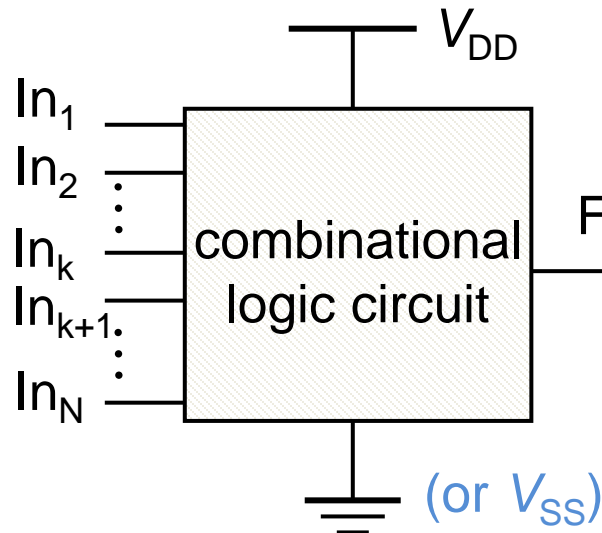- ❑ Such digital circuits of implementing any **Boolean function** are called **combinational logic circuits**, of which the outputs depend only on the current inputs.



➤ A **combinational logic circuit** is a **memoryless** system.

➤ This is in contrast to **sequential logic circuits**, of which the outputs depend on both the current inputs and previous inputs

➤ **Sequential logic circuits** requires **memory** to store previous inputs.

Combinational Logic Circuits

(basic logic gates)

- The **memoryless** nature of **combinational logic circuits** can be easily understood from the operation of the basic logic gates.

“NOT”


A —  — F

$F = \overline{A}$

A	F
0	1
1	0

also called **inverter**

“OR”

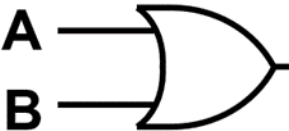
A —  — F

B

$F = A + B$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

“AND”

A —  — F

B

$F = A \cdot B$

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

- Output F is a function of only current inputs A and B .




Xi'an Jiaotong-Liverpool University

西交利物浦大学

Basic Logic Gates

(XOR as combinational logic)


“NOR”

 

$$F = \overline{A+B}$$

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0


“NAND”

 

$$F = \overline{A \cdot B}$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

“XOR”
(exclusive OR)

 

$$F = A \oplus B$$

$$= A\overline{B} + \overline{A}B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

- Note that the XOR logic function is a combination of NOT, AND and OR.



Xi'an Jiaotong-Liverpool University

西交利物浦大學

Basic Logic Gates

(OR & AND gates from NOR & NAND gates)

“NOR” + Inverter = “OR”



“AND” + Inverter = “NAND”



“XOR” + Inverter = “XNOR”




Combination of Logic Gates

(AOI & OAI)


- AND-OR-Inverter (AOI) such as

$$X = \overline{(AB) + (CD)}$$

 

- OR-AND-Inverter (OAI) such as
 
$$Y = \overline{(A_1 + A_2)(B_1 + B_2)}$$




Combination of Logic Gates

(AOI & OAI)


- AND-OR-Inverter (AOI) such as

$$F = \overline{(AB) + (CD) + E}$$

 

- OR-AND-Inverter (OAI) such as

$$G = \overline{A(B + C)}$$

 

CMOS Digital ICs


(start from 3 basic logic gates)

- ❑ Digital logic circuits can be constructed using combinations of the three basic logic gates.
- ❑ The fundamental start in CMOS digital ICs is to design and construct the three logic gates using MOS transistors.
 - In using MOS transistors, there are a few different ways in the design and construction of the three logic gates.
 - The CMOS way (i.e. using both pMOSFETs and nMOSFETs for complementary circuit operation) is the best so far in terms of speed, power consumption, robustness, etc.

The MOSFET as a Switch

(NOT, AND, OR operations from switches)

 - When the MOSFET as a 3-terminal device is used as a **switch**, the NOT, AND, and OR logic functions are achieved by the series and parallel connections of MOSFETs.



➤ design & implementation consideration:


- how close are the MOSFETs' behaviour as that of an (*ideal*) **switch**?
- how can the MOSFETs be modelled as **switches** in digital circuits?



Xi'an Jiaotong-Liverpool University
西交利物浦大學

The MOSFET as a Switch

(NOT, AND, OR operations from switches)

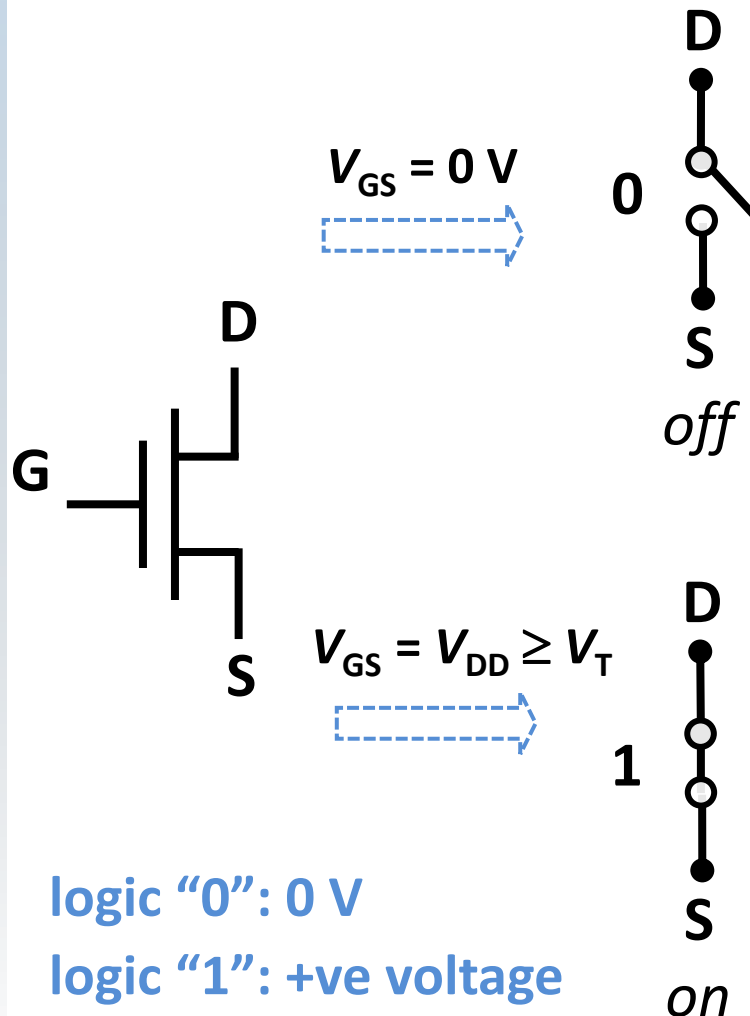

- In its off state, the MOSFET behaves as open circuit (as an *ideal* switch).



Note that here logic "0" is represented by 0 V or negative supply voltage; logic "1" by positive supply voltage.

- When turned on, the MOSFET behaves as short circuit (*ideally* with zero resistance).

*n*MOSFETs in Series

(AND logic function)

  - The AND logic function is achieved by two *n*MOSFETs connected in series (i.e. stacking over another):



$$Output = (G_A \bullet G_B)$$








Xi'an Jiaotong-Liverpool University
西交利物浦大學

*n*MOSFETs in Parallel

(OR logic function)

     - The OR logic function is achieved by two *n*MOSFETs connected in parallel:



$$Output = (G_A + G_B)$$




Xi'an Jiaotong-Liverpool University
西交利物浦大學


*p*MOSFETs in Series

(NOR logic function)

 - When *p*MOSFETs are connected in series (i.e. stacking over another), the NOR logic function is achieved:


 
$$Output = (\overline{G_A} \bullet \overline{G_B}) = \overline{(G_A + G_B)}$$




- exactly opposite to that *n*MOSFETs in parallel

*p*MOSFETs in Parallel

(NAND logic function)

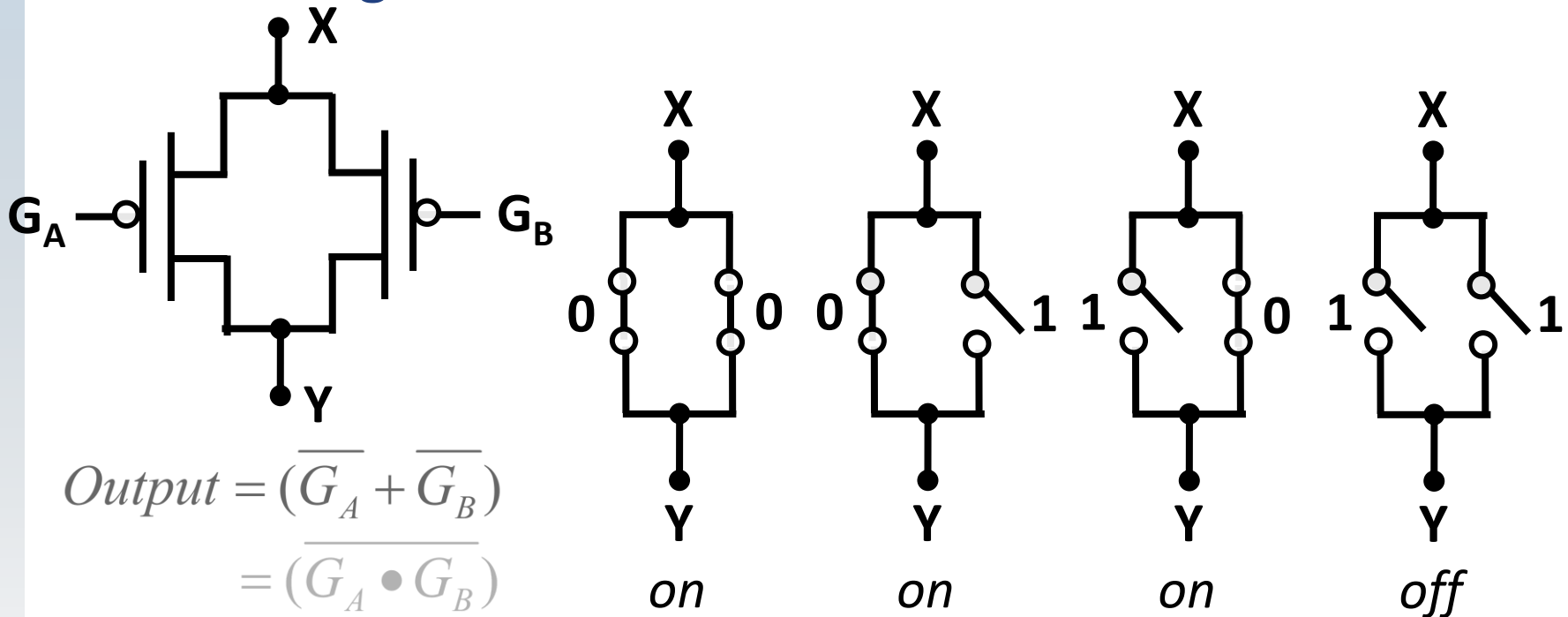
- When *p*MOSFETs are connected in parallel, the NAND logic function is achieved:



- exactly opposite to that *n*MOSFETs in series



IC Layout of MOSFETs - sketch

(two MOSFETs in series)

 

IC Layout of MOSFETs - sketch


(three & four MOSFETs in series)

  

- The shared common drain regions of MOSFETs can be made even smaller if connection not needed.

IC Layout of MOSFETs - sketch


(two MOSFETs in parallel)

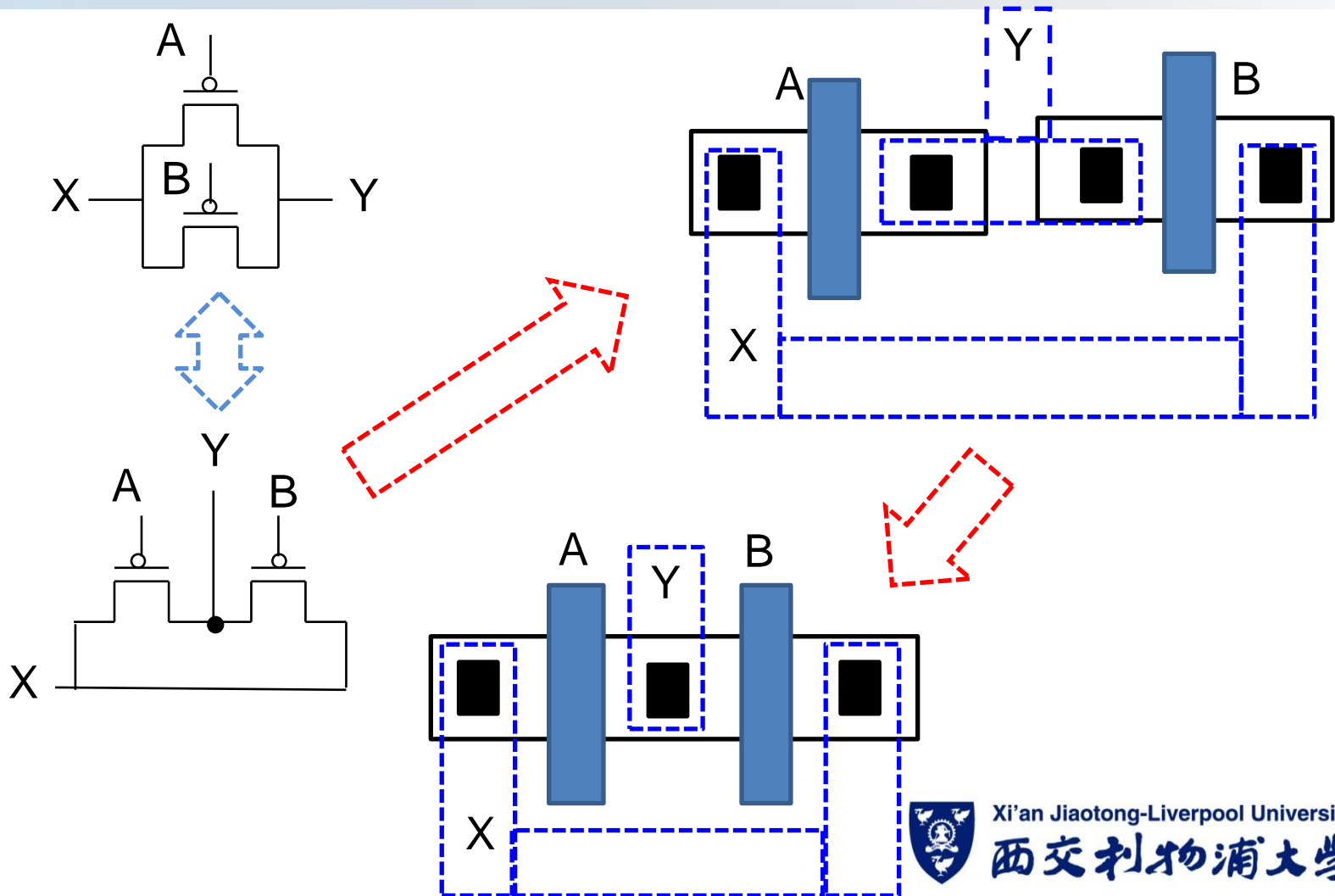

Xi'an Jiaotong-Liverpool University
西交利物浦大學


IC Layout of MOSFETs - sketch

(three MOSFETs in parallel)

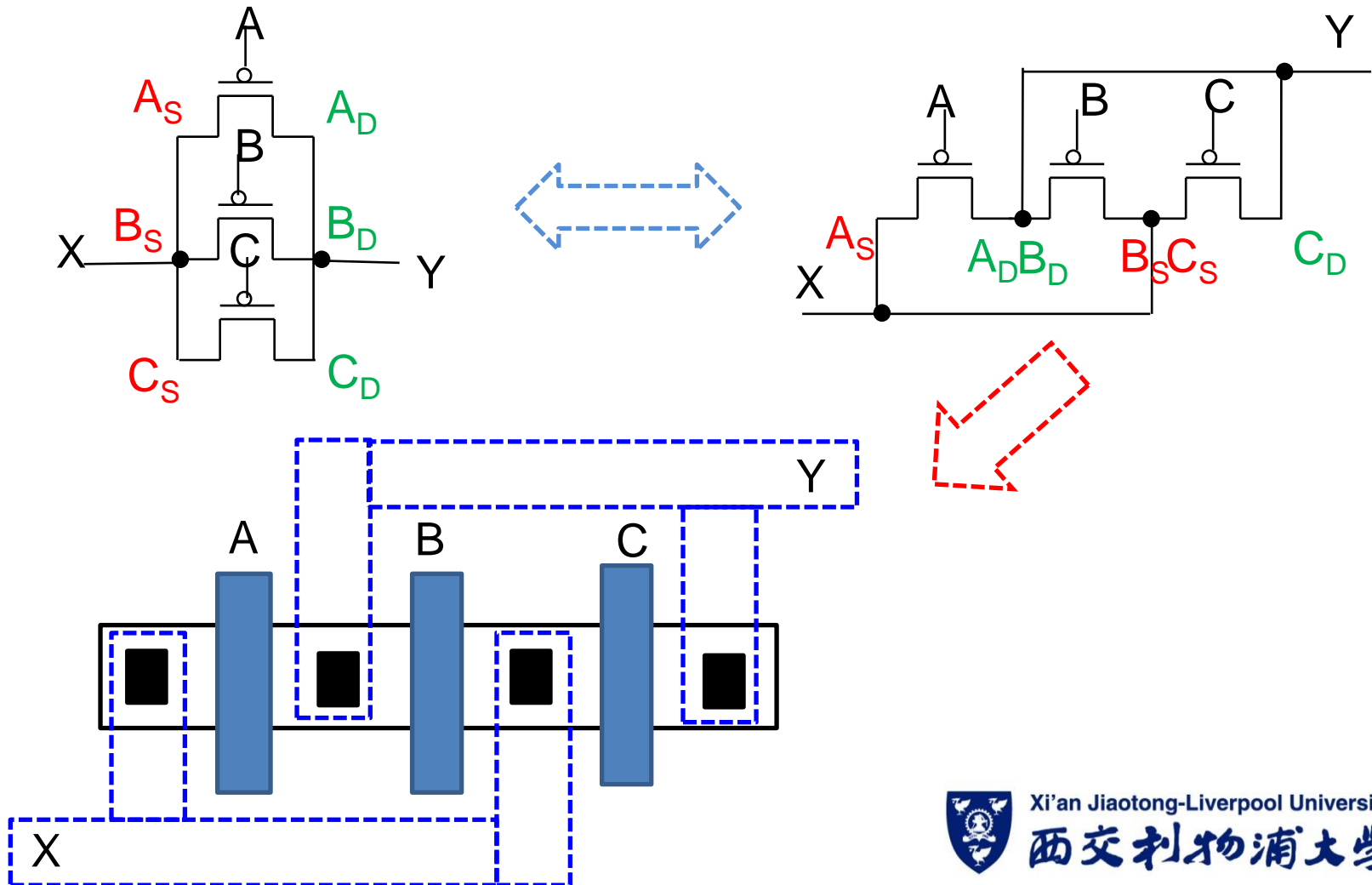

IC Layout of MOSFETs - sketch



(four MOSFETs in parallel)

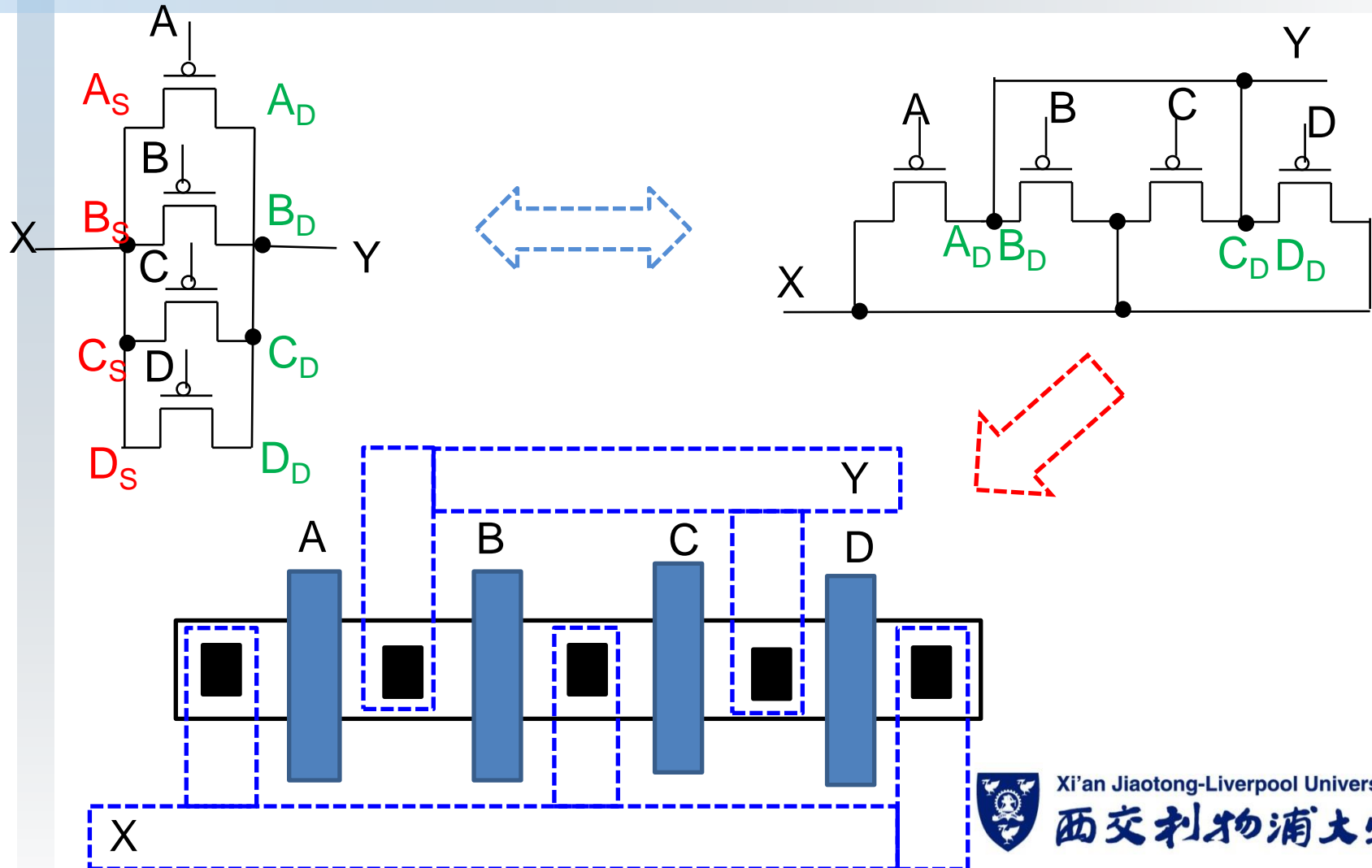

Xi'an Jiaotong-Liverpool University
西交利物浦大學


Logic Gates Made of MOSFETs

  (nMOSFETs & pMOSFETs in series & parallel)



IC Layout of 4-input NOR Gate

(four *p*MOSFETs in series)


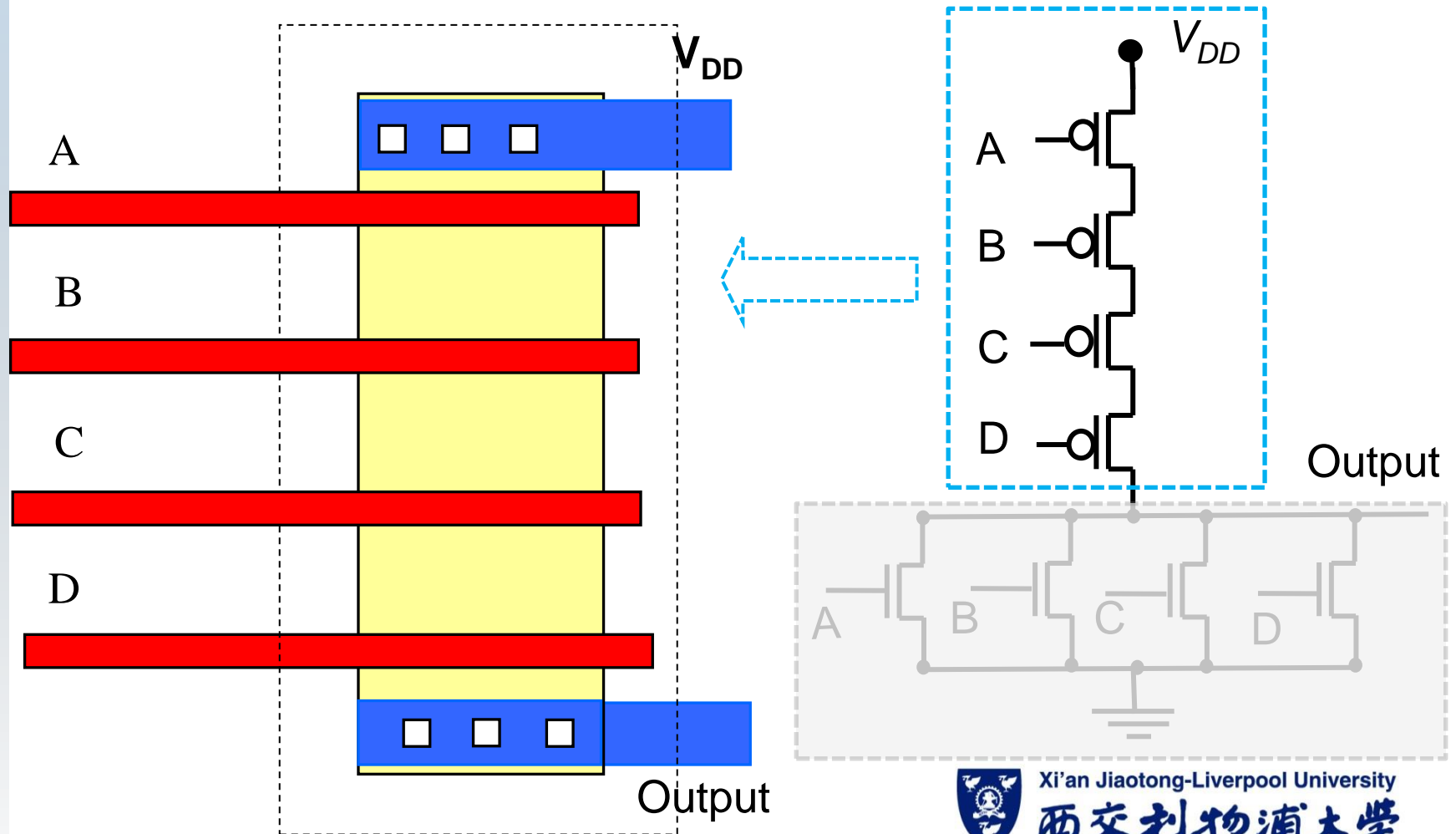


Xi'an Jiaotong-Liverpool University
西交利物浦大學

IC Layout of 4-input NOR Gate


(two MOSFETs in series)

  - ❑ The IC layout of the MOSFETs can be oriented in such a way for better use of chip area and easier routing.




IC Layout of 4-input NOR Gate

(four *n*MOSFETs in parallel)

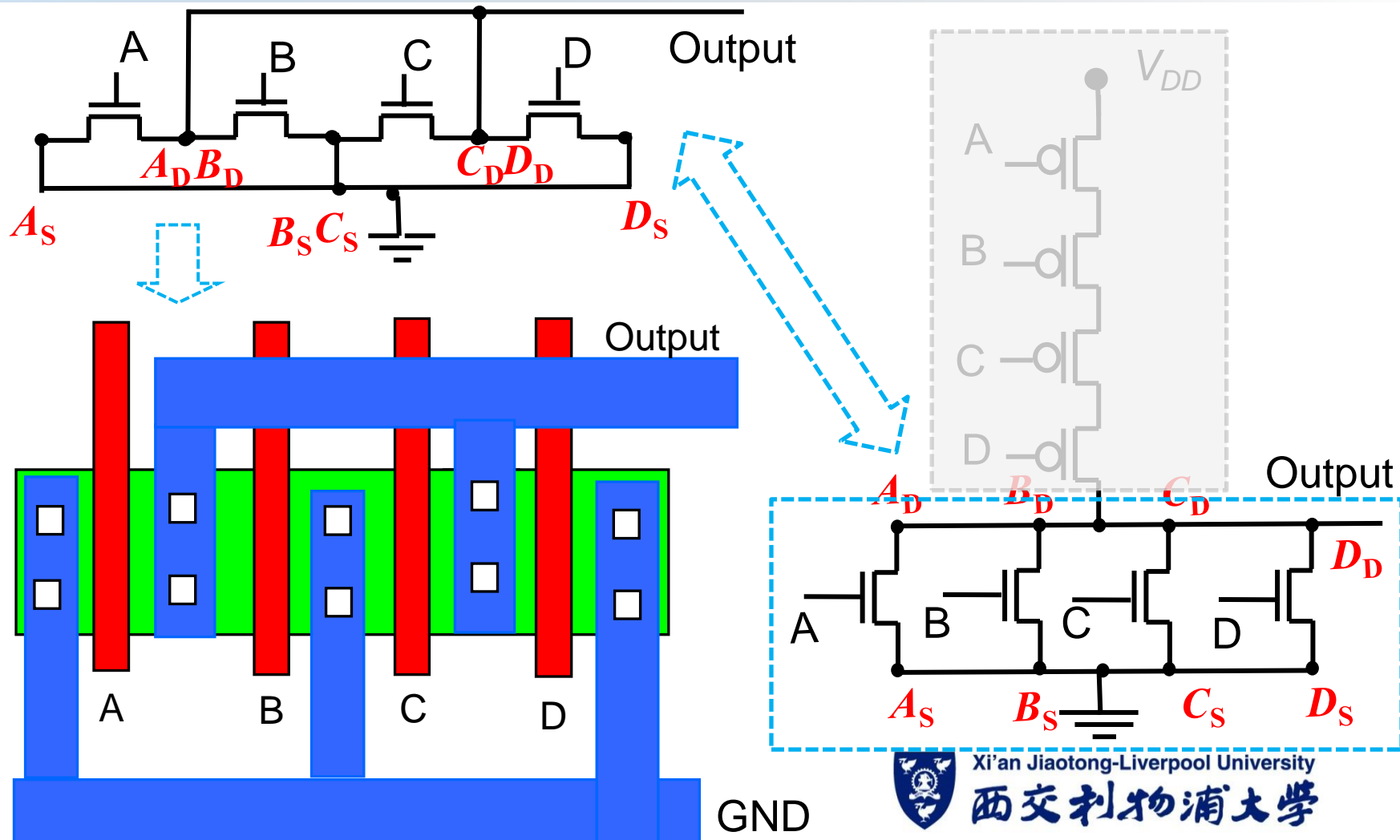


IC Layout of 4-input NOR Gate

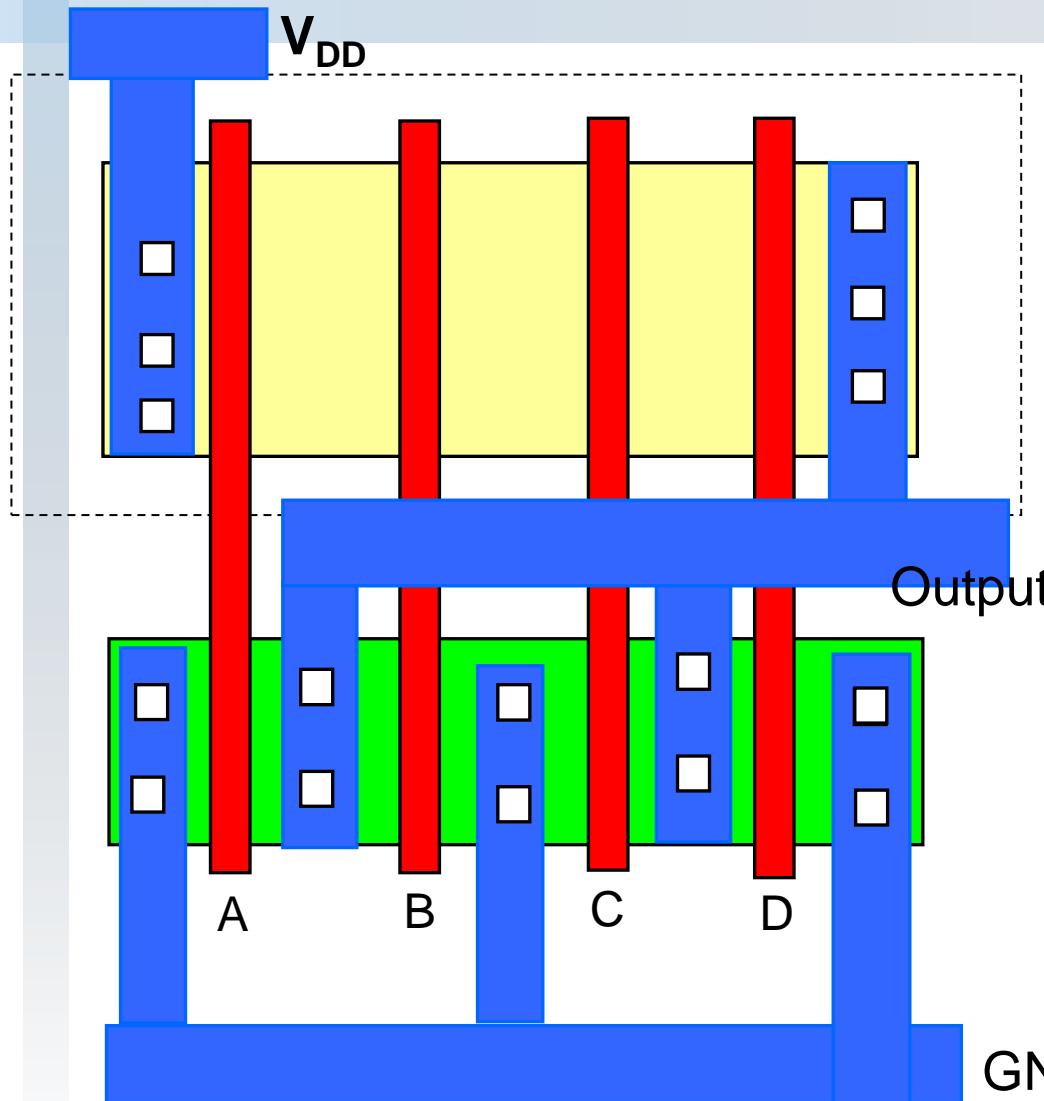(final layout optimised in chip area & routing)





schematic
circuit
to
IC layout

 

Xi'an Jiaotong-Liverpool University
西交利物浦大學

IC Layout of 4-input NAND Gate

(similar methods)

  


Xi'an Jiaotong-Liverpool University
西交利物浦大学

Drawing IC Layout

(precise geometrical shapes & dimensions)

- ❑ In drawing the actual layout for IC fabrication, the geometrical shapes and dimensions need to be *very precise*, rather than sketches like those shown in previous slides.

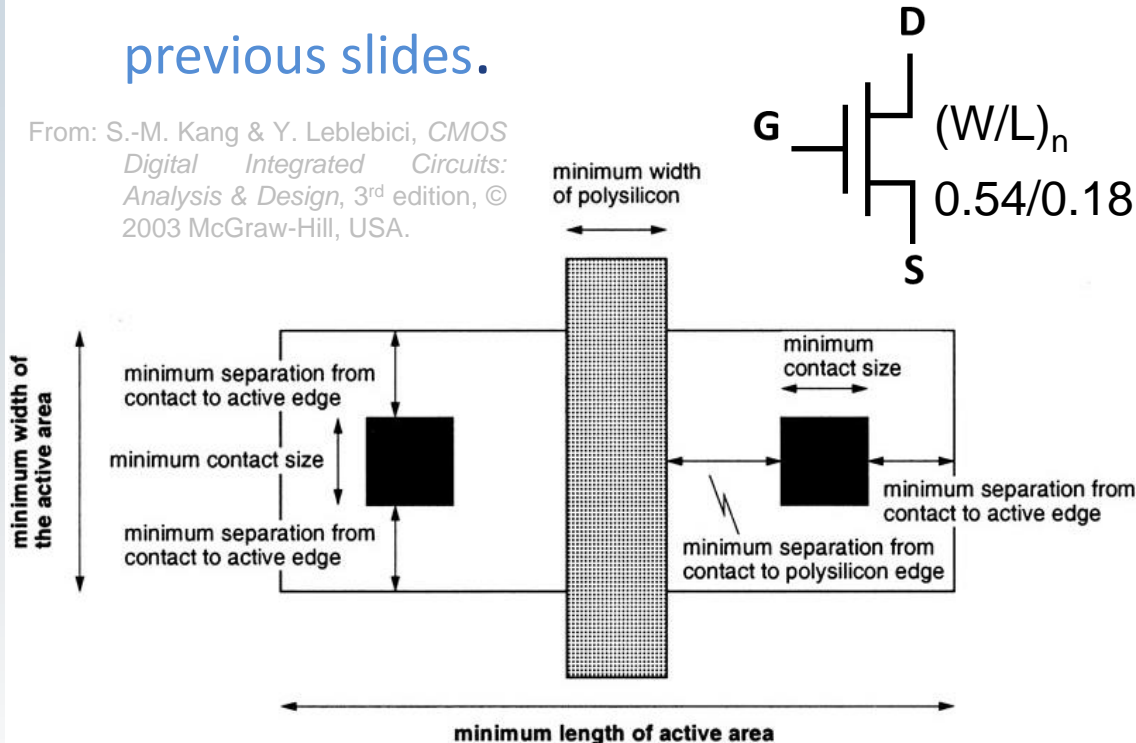From: S.-M. Kang & Y. Leblebici, *CMOS Digital Integrated Circuits: Analysis & Design*, 3rd edition, © 2003 McGraw-Hill, USA.



- An example of drawing precisely the IC layout of an nMOSFET in a 0.18- μm CMOS technology is shown on the left.





Xi'an Jiaotong-Liverpool University
西交利物浦大學

Precise Drawing of IC Layout

(pMOSFET)

  - An example of the precise drawing the IC layout of a pMOSFET in a 0.18- μm CMOS technology is shown below:



- There is the additional **n-well** layer (assuming a **p**-type wafer).

- The **n-well** needs certain separation distance from the **n**-type diffusion regions (source/drain) of **n**MOSFETs.

From: S.-M. Kang & Y. Leblebici, *CMOS Digital Integrated Circuits: Analysis & Design*, 3rd edition, © 2003 McGraw-Hill, USA.



Xi'an Jiaotong-Liverpool University
西交利物浦大學

Rules in Drawing IC Layout

Rule number Description

Active area rules

- R1 Minimum active area width
R2 Minimum active area spacing

Polysilicon rules

- R3 Minimum poly width
R4 Minimum poly spacing
R5 Minimum gate extension of poly over active
R6 Minimum poly-active edge spacing
(poly outside active area)
R7 Minimum poly-active edge spacing
(poly inside active area)

Metal rules

- R8 Minimum metal width
R9 Minimum metal spacing

Contact rules

- R10 Poly contact size
R11 Minimum poly contact spacing
R12 Minimum poly contact to poly edge spacing
R13 Minimum poly contact to metal edge spacing
R14 Minimum poly contact to active edge spacing

R15 Active contact size
R16 Minimum active contact spacing
(on the same active region)
R17 Minimum active contact to active edge spacing
R18 Minimum active contact to metal edge spacing
R19 Minimum active contact to poly edge spacing
R20 Minimum active contact spacing
(on different active regions)

λ -Rule

3λ
 3λ

2λ
 2λ
 2λ
 1λ
 3λ



3λ
 3λ

2λ
 2λ
 1λ
 1λ
 3λ

2λ
 2λ

1λ
 1λ
 3λ

1λ

  

From: S.-M. Kang & Y. Leblebici, *CMOS Digital Integrated Circuits: Analysis & Design*, 3rd edition, © 2003 McGraw-Hill, USA.