

CAN209 Advanced Electrical Circuits and Electromagnetics

Lecture 11 Transient Response of 2nd-Order Circuits (**Natural** Response)

Dr. Zhenzhen Jiang

Assistant Professor, FHEA

Faculty: School of Advanced Technology

Email: zhenzhen.jiang02@xjtlu.edu.cn

OUTLINE

- Concepts and Applications
- Analysis of Parallel RLC Circuits
 - ✓ Determine a Response Form
 - ✓ Find General Solutions
- Analysis of Series RLC Circuits
 - ✓ Determine a Response Form
 - ✓ Find General Solutions

2nd-order linear differential equations – General Solutions
二阶线性微分方程解的结构


1.1 BASIC CONCEPTS

A second-order circuit is characterised by a second-order differential equation. It consists of resistors and **TWO equivalent** energy storage elements.

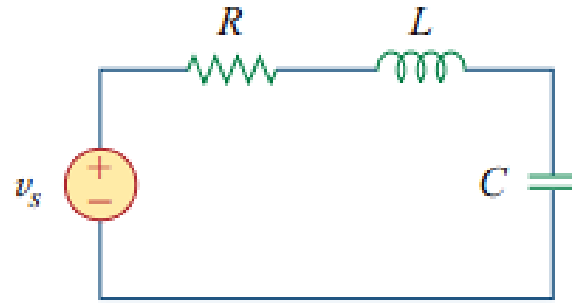
Examples:

- ✓ Series RLC circuit
- ✓ Parallel RLC circuit
- ✓ RLL circuit
- ✓ RCC circuit


voltage source \rightarrow s.c.
current source \rightarrow o.c.




(a)

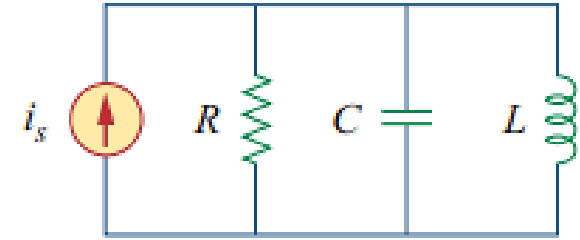

(b)

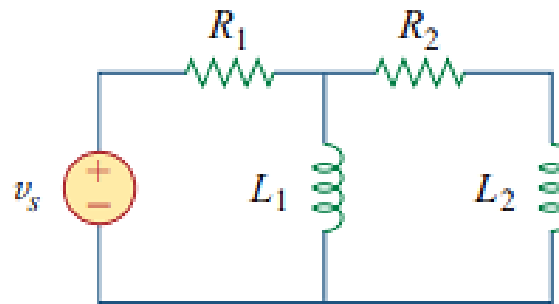

(c)

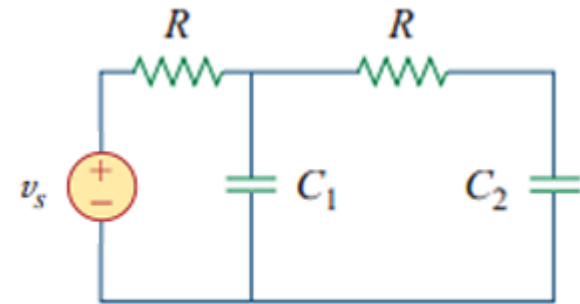


(d)

1.2 INSIGHT & REAL-LIFE APPLICATIONS




LCR Digital Metres

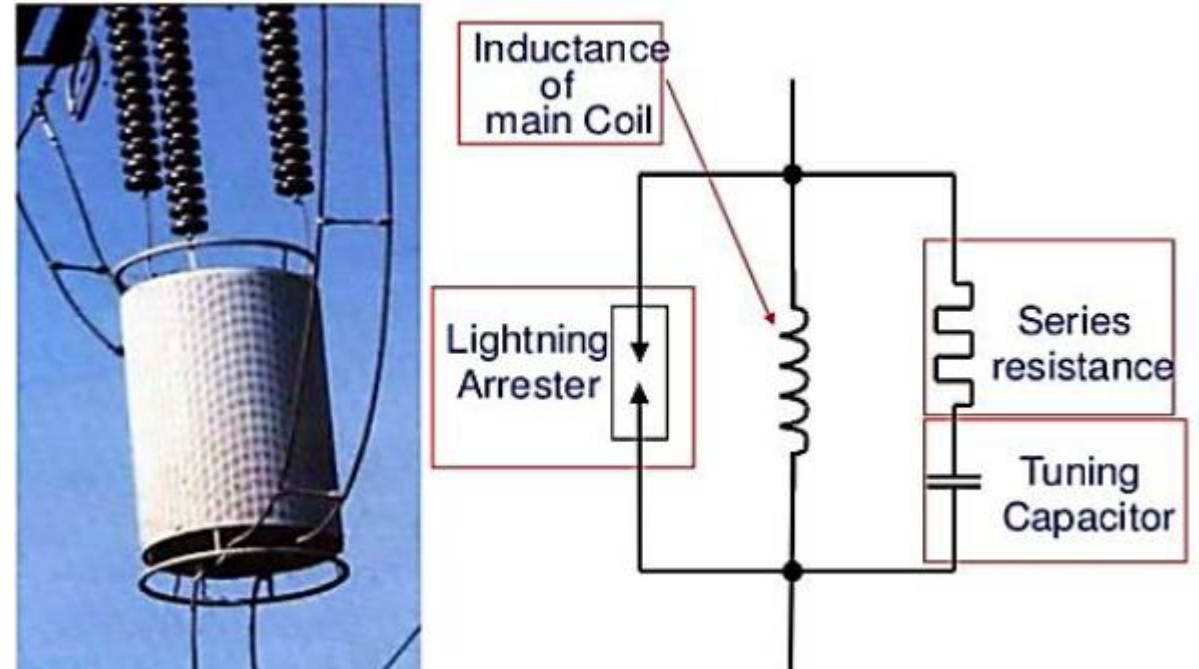


Line Trap Circuit

1.2 INSIGHT & REAL-LIFE APPLICATIONS

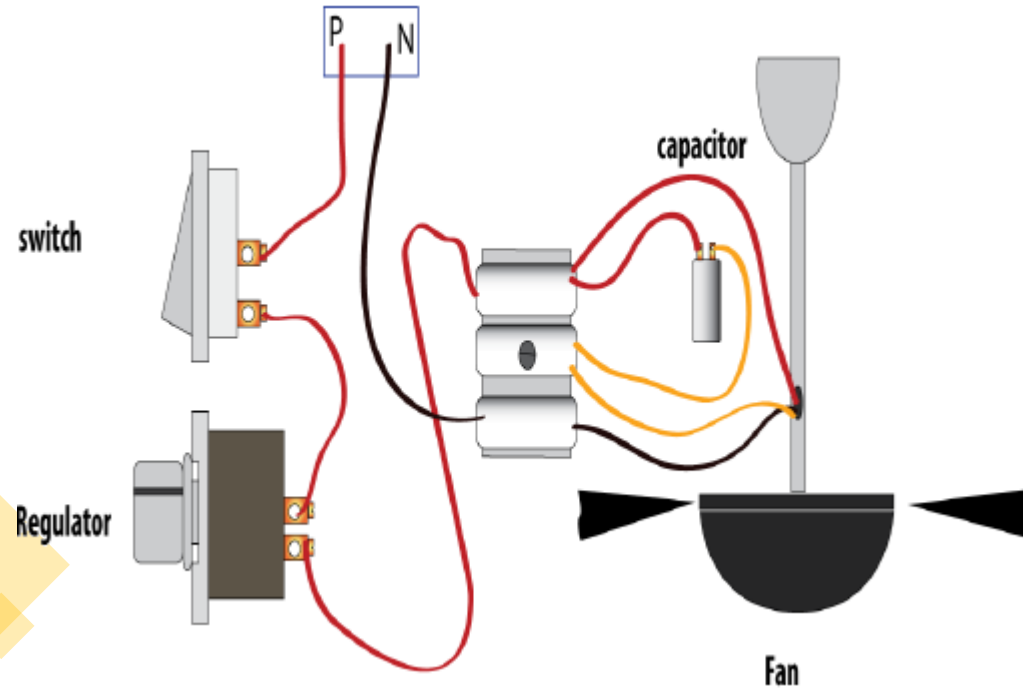

Electric Ceiling Fan

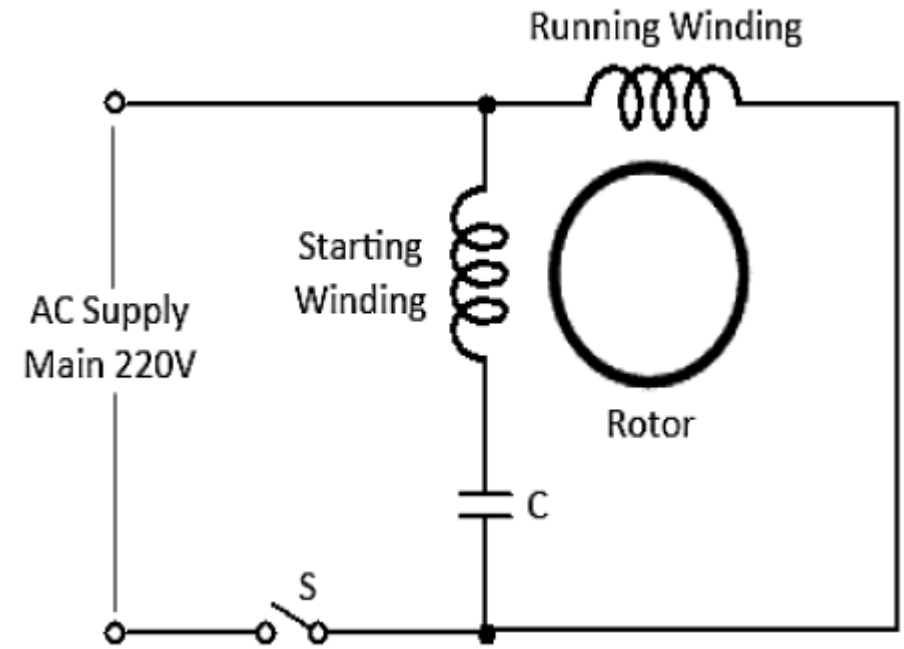

Ceiling Fan Wiring Diagram

1.3 GENERAL IDEA

Last week, we looked at the transient response of **first**-order circuits. General procedure to solve this kind of circuits is:

- Apply KVL or KCL
 - ✓ Find the governing first-order differential equation
- Solve the ODE
 - ✓ Determine the complete expression

For transient response of **second**-order circuits, general procedure is similar:

- Apply KVL or KCL
 - ✓ Find the governing second-order differential equation
- Solve the ODE
 - ✓ Determine the complete expression


OUTLINE

- Concepts and Applications
- Analysis of **Parallel** RLC Circuits
 - ✓ Determine a Response Form
 - ✓ Find General Solutions
- Analysis of Series RLC Circuits
 - ✓ Determine a Response Form
 - ✓ Find General Solutions

2nd-order linear differential equations – General Solutions
二阶线性微分方程解的结构

2.1 METHOD 1

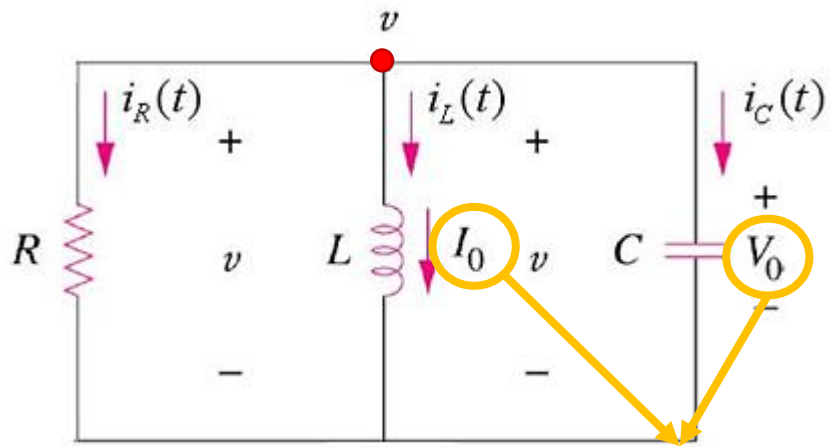Task: given the initial energy stored in the inductor or capacitor, find $v(t)$ for $t \geq 0$.



**Initial
Condition**

$$\begin{cases} i_R(t) = \frac{v}{R} \\ i_C(t) = C \frac{dv}{dt} \\ i_L(t) = \frac{1}{L} \int_0^t v dt' + i(t=0) \end{cases}$$

Get the ODE

Apply KCL at the node:


$$i_C(t) + i_R(t) + i_L(t) = 0$$

$$\therefore C \frac{dv}{dt} + \frac{v}{R} + \frac{1}{L} \int_0^t v dt' + I_0 = 0$$

Take derivative of both sides & divide by C:

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

CONTINUE...

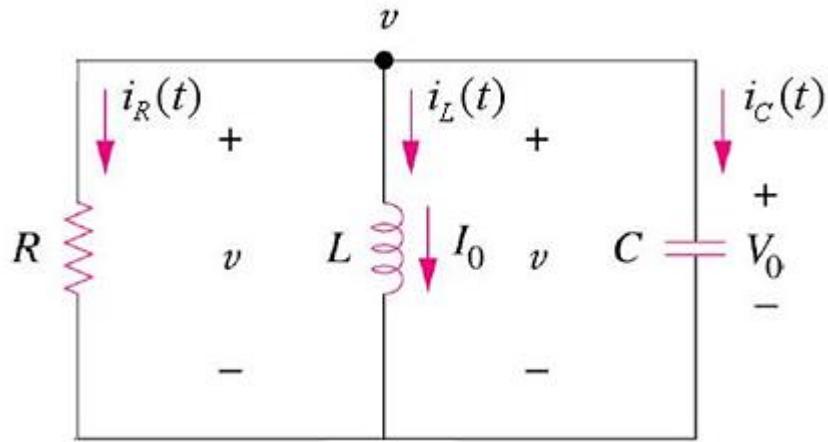

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

This equation is:

- ✓ Homogeneous 2nd ODE
- ✓ Constant coefficients

Solve the ODE

The *characteristic equation* is

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

Define:

ω_0 as the resonant (natural) frequency (rad/s)

α as the neper frequency (rad/s)
(exponential damping coefficient)

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \alpha = \frac{1}{2RC}$$

The characteristic eq. becomes:

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$\therefore s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \text{and} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

s_1 and s_2 are called complex frequencies.

CONTINUE...

The value of the term $\sqrt{\alpha^2 - \omega_0^2}$ determines the behavior of the response.

➤ **Over Damped** $\rightarrow \alpha > \omega_0$:

s_1 & s_2 are two unequal real numbers

Response: $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

➤ **Critical Damped** $\rightarrow \alpha = \omega_0$:

s_1 & s_2 are two equal real numbers

Response: $v_C(t) = e^{-\alpha t} (A_1 t + A_2)$

➤ **Under Damped** $\rightarrow \alpha < \omega_0$:

s_1 & s_2 are two complex numbers

Response:

$$\left\{ \begin{array}{l} s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} \\ s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2} \end{array} \right.$$
$$v_C(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

A_1 and A_2 : constant determined by initial conditions


B_1 and B_2 : determined by initial conditions

natural resonant (damped) frequency **10**

CONTINUE...

Find the Coefficients

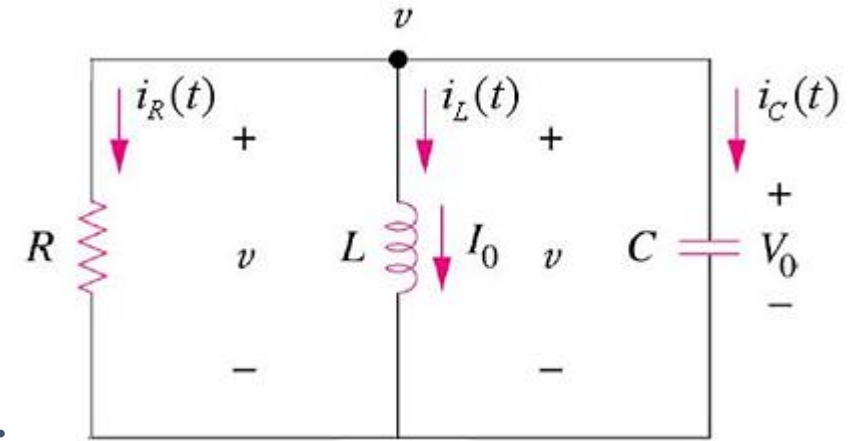- ✓ Polarity of voltage across the C , and the direction of the current through the L .
- ✓ The capacitor's voltage is always continuous, and the inductor's current is always continuous.



Normally start from finding variables that **cannot** change abruptly:

$$v_C(t = 0^+) = v_C(t = 0^-)$$

$$i_L(t = 0^+) = i_L(t = 0^-)$$

CONTINUE...

Find the Coefficients

- Over Damped $\rightarrow \alpha > \omega_0$:

$$v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\begin{cases} v_C(0^+) = A_1 + A_2 \\ \frac{dv_C(0^+)}{dt} = A_1 s_1 + A_2 s_2 \end{cases}$$

- Critical Damped $\rightarrow \alpha = \omega_0$:

$$v_C(t) = e^{-\alpha t} (A_1 t + A_2)$$

$$\begin{cases} v_C(0^+) = A_2 \\ \frac{dv_C(0^+)}{dt} = A_1 - A_2 \alpha \end{cases}$$

- Under Damped $\rightarrow \alpha < \omega_0$:


$$v_C(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\begin{cases} v_C(0^+) = B_1 \\ \frac{dv_C(0^+)}{dt} = -\alpha B_1 + \omega_d B_2 \end{cases}$$


2.2 RULES FOR CIRCUIT DESIGNERS

- ✓ If one desires the circuit **reaches the final value** as **fast** as possible while the minor oscillation is of less concern, choosing R , L , C values to satisfy under-damped condition.
- ✓ If one concerns that the response **not exceed its final value** to **prevent potential damage**, designing the system to be over-damped at the cost of slower response.


Over Damped

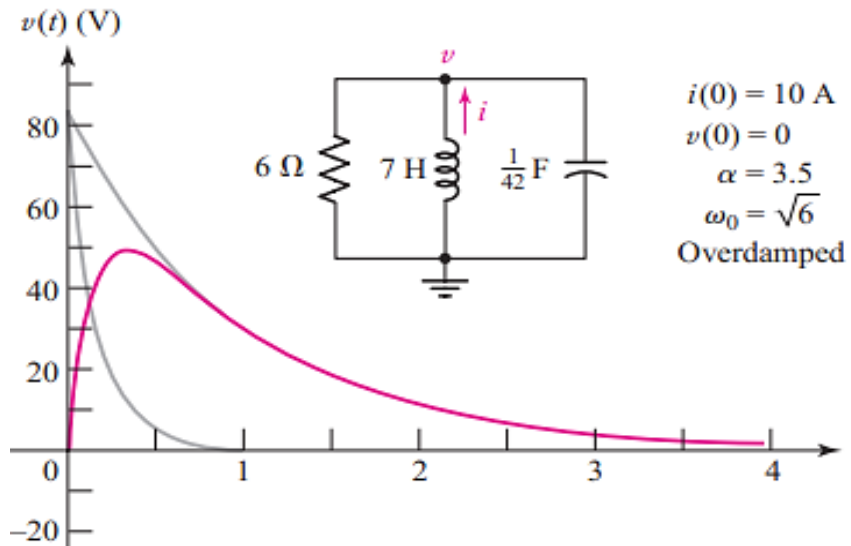



Under Damped

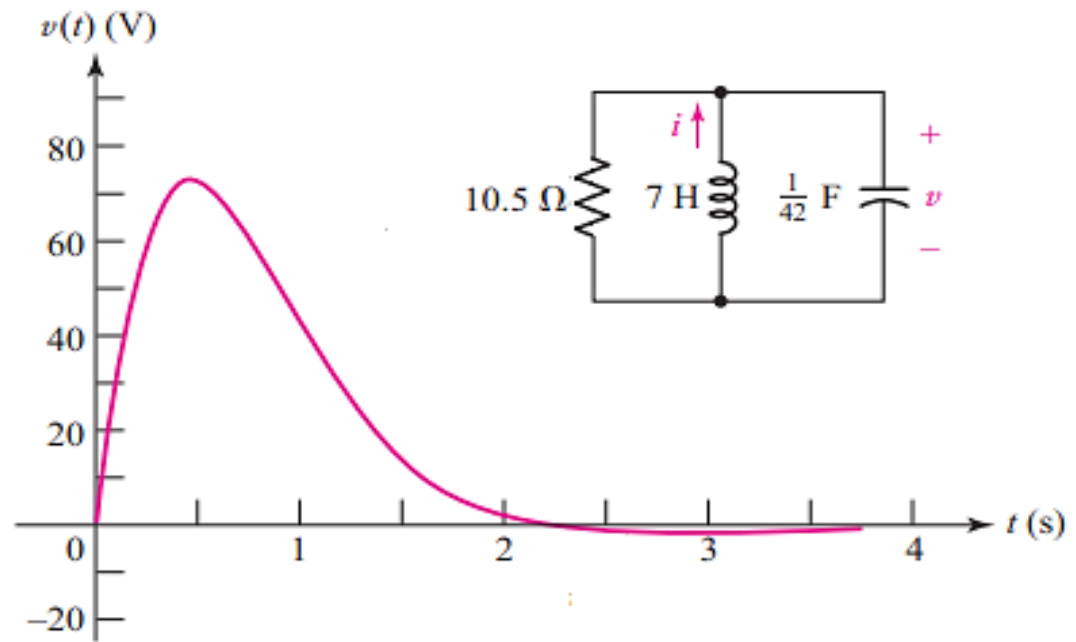

Critical Damped

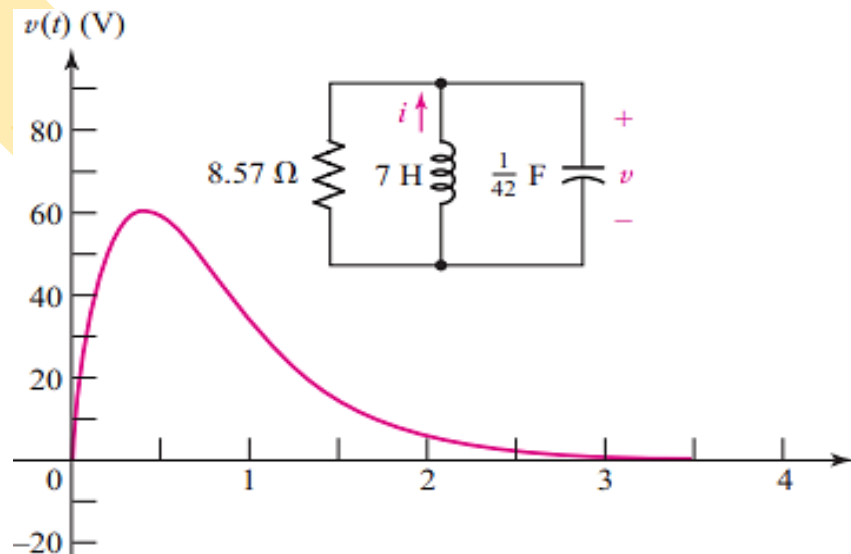

2.3 ROLE OF THE RESISTOR

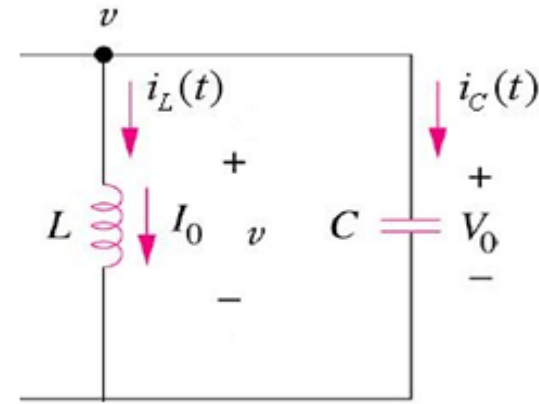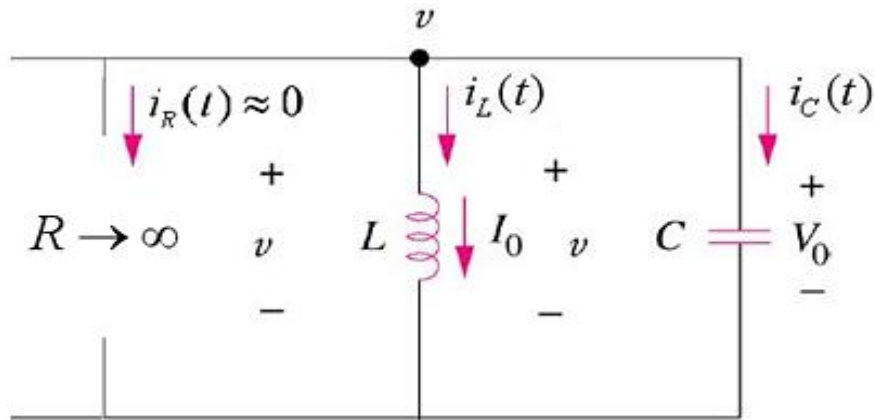

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha = \frac{1}{2RC} \rightarrow 0$$


$$\alpha \ll \omega_0 \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2} \approx \omega_0$$

$$\therefore v_C(t) = B_1 \cos \omega_0 t + B_2 \sin \omega_0 t$$

A parallel RLC circuit can be made to have an effective value of R to be big enough that a **natural *undamped* sinusoidal response** can be maintained for years without supplying any additional energy.

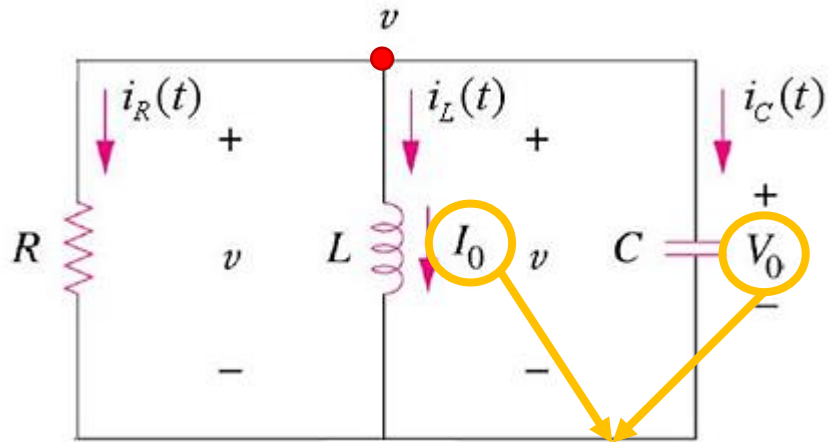2.4 METHOD 2

Alternatively, we can start with finding an ODE of inductor's current:



Initial Condition

$$\begin{cases} i_R(t) = \frac{v}{R} = \frac{L}{R} \frac{di_L}{dt} \\ i_C(t) = C \frac{dv}{dt} = LC \frac{d^2 i_L}{dt^2} \\ v_L(t) = L \frac{di_L}{dt} \end{cases}$$

Get the ODE

Applying KCL at the node:

$$i_C(t) + i_R(t) + i_L(t) = 0$$

$$\therefore LC \frac{d^2 i_L}{dt^2} + \frac{L}{R} \frac{di_L}{dt} + i_L = 0$$

Divide by LC on both sides:

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = 0$$


QUIZ 1

The circuit below has the following parameters:

$$R = 500 \, \Omega, C = 1 \, \mu\text{F}, L = 0.2 \, \text{H}.$$

The initial conditions are $i_L(0) = 50 \, \text{mA}$ and $v(0) = 0 \, \text{V}$.


Determine expressions of $i_L(t)$, $i_R(t)$ and $v_c(t)$ for $t \geq 0$.

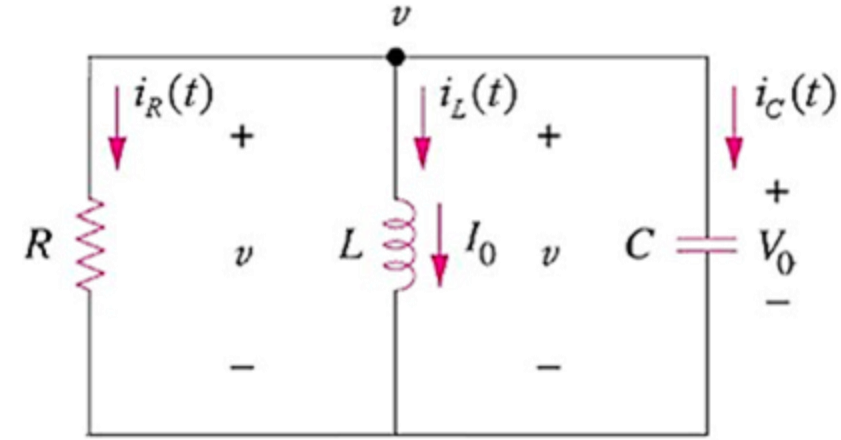

QUIZ 2


1. For the circuit as shown, the capacitor voltage at $t = 0^+$ (just after the switch is closed) is

- (a) 0 V (b) 4 V (c) 8 V (d) 12 V

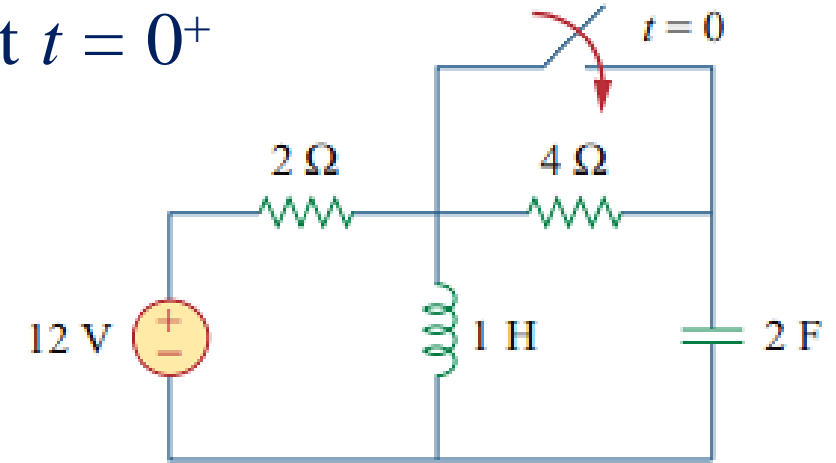

2. For the same circuit, the inductor voltage at $t = 0^+$ (just after the switch is closed) is

- (a) 0 V (b) 4 V (c) 8 V (d) 12 V

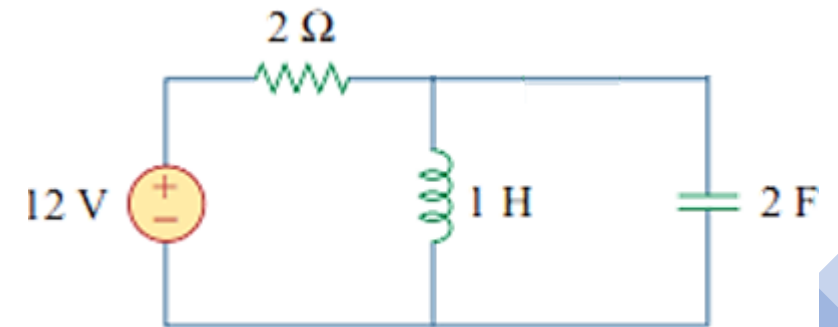

QUIZ 3

1. If the roots of the characteristic equation of an RLC circuit are -2 and -3 , the response is:

(a) $Ae^{-2t} + Be^{-3t}$

(b) $e^{-3t}(At + B)$

(c) $e^{-3t}(A \cos 2t + B \sin 3t)$

(d) $Ae^{-2t} + Bte^{-3t}$

2. A parallel RLC circuit has $L = 4$ H and $C = 0.25$ F. The value of R that will produce under damping factor is:

(a) 0.5Ω

(b) 1Ω

(c) 2Ω

(d) 4Ω


OUTLINE

- Concepts and Applications
- Analysis of Parallel RLC Circuits
 - ✓ Determine a Response Form
 - ✓ Find General Solutions
- Analysis of **Series** RLC Circuits
 - ✓ Determine a Response Form
 - ✓ Find General Solutions

2nd-order linear differential equations – General Solutions
二阶线性微分方程解的结构

3.1 SERIES RLC CIRCUIT

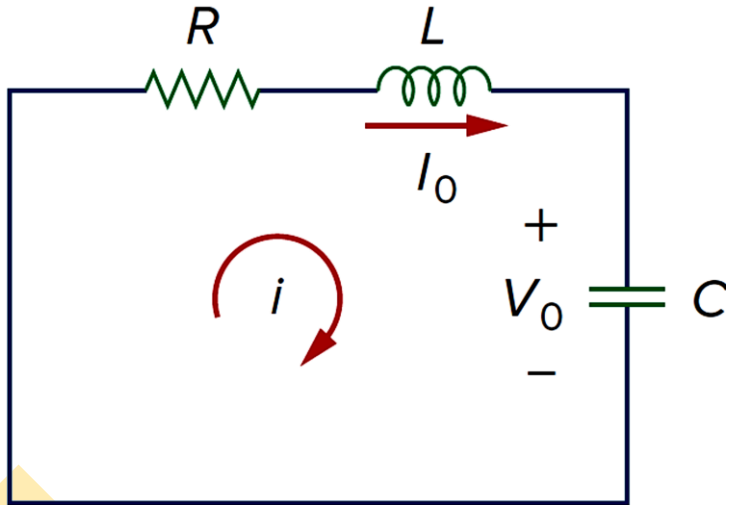Problem: given the initial energy stored in the inductor and/or capacitor, find $v(t)$ for $t \geq 0$.



Get the ODE

Apply KVL:

$$v_C(t) + v_R(t) + v_L(t) = 0$$

$$\therefore LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = 0$$

Divide by LC on both sides:

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = 0$$

Alternatively:


$$v_C(t) = \frac{q(t)}{C} = \frac{1}{C} \int_{-\infty}^t i(t) dt$$



$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$\left\{ \begin{aligned} i_R &= i_L = i_C(t) = C \frac{dv_C}{dt} \\ v_R &= Ri_R = RC \frac{dv_C}{dt} \\ v_L(t) &= L \frac{di_L}{dt} = LC \frac{d^2 v_C}{dt^2} \end{aligned} \right.$$

CONTINUE...

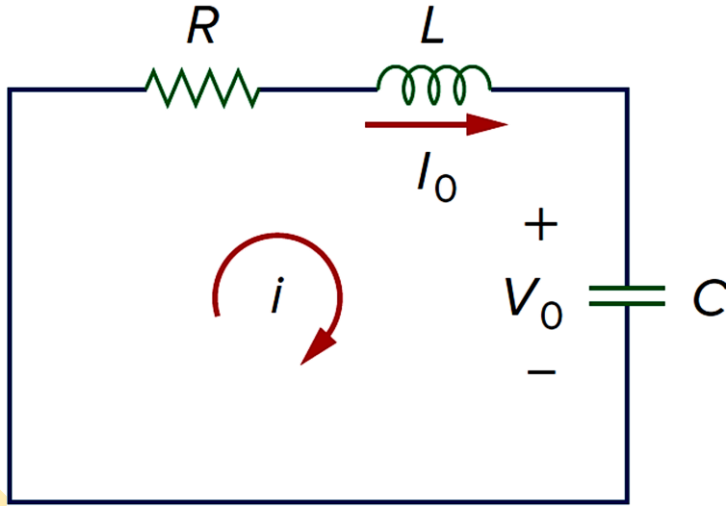

$$\frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = 0$$

This equation is:

- ✓ Homogeneous 2nd ODE
- ✓ Constant coefficients

Solve the ODE

The *characteristic equation* is

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

Define:

ω_0 as the resonant (natural) frequency (rad/s)

α as the neper frequency (rad/s)
(exponential damping coefficient)

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \alpha = \frac{R}{2L}$$

The characteristic eq. becomes:

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$\therefore s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \text{and} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

s_1 and s_2 are called complex frequencies.

CONTINUE...

The value of the term $\sqrt{\alpha^2 - \omega_0^2}$ determines the behaviour of the response:

➤ **Over Damped** $\rightarrow \alpha > \omega_0$:

s_1 & s_2 are two unequal real numbers

Response: $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

➤ **Critical Damped** $\rightarrow \alpha = \omega_0$:

s_1 & s_2 are two equal real numbers

Response: $v_C(t) = e^{-\alpha t}(A_1 t + A_2)$

➤ **Under Damped** $\rightarrow \alpha < \omega_0$:

s_1 & s_2 are two complex numbers

Response:

$$v_C(t) = e^{-\alpha t}(B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\begin{cases} s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} \\ s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2} \end{cases}$$

$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$
*natural resonant
(damped) frequency*


A_1 and A_2 : constant determined by initial conditions

B_1 and B_2 : determined by initial conditions

CONTINUE...

Find the Coefficients

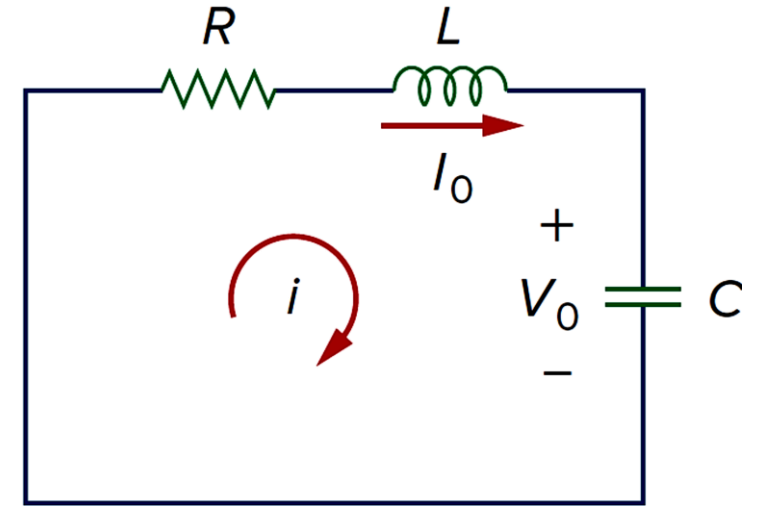- ✓ Polarity of voltage across the C , and the direction of the current through the L .
- ✓ The capacitor voltage is always continuous, and the inductor current is always continuous.



Normally start from finding variables that **cannot** change abruptly.

$$v_C(t = 0^+) = v_C(t = 0^-)$$
$$i_L(t = 0^+) = i_L(t = 0^-)$$

CONTINUE...

Find the Coefficients

- Over Damped $\rightarrow \alpha > \omega_0$:

$$v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\left\{ \begin{array}{l} v_C(0^+) = A_1 + A_2 \\ \frac{dv_C(0^+)}{dt} = A_1 s_1 + A_2 s_2 \end{array} \right.$$

- Critical Damped $\rightarrow \alpha = \omega_0$:

$$v_C(t) = e^{-\alpha t} (A_1 t + A_2)$$

$$\left\{ \begin{array}{l} v_C(0^+) = A_2 \\ \frac{dv_C(0^+)}{dt} = A_1 - A_2 \alpha \end{array} \right.$$

- Under Damped $\rightarrow \alpha < \omega_0$:

$$v_C(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\left\{ \begin{array}{l} v_C(0^+) = B_1 \\ \frac{dv_C(0^+)}{dt} = -\alpha B_1 + \omega_d B_2 \end{array} \right.$$


QUIZ 4

The circuit below has the following parameters:

$$R = 8.5 \text{ k}\Omega, C = 0.25 \text{ }\mu\text{F}, L = 1 \text{ H}$$

The switch has been open for a long time and is closed at $t = 0$. The initial conditions are $i_L(0) = 0$ and $v_C(0) = 15\text{V}$.

Find the capacitor's voltage for $t \geq 0$.

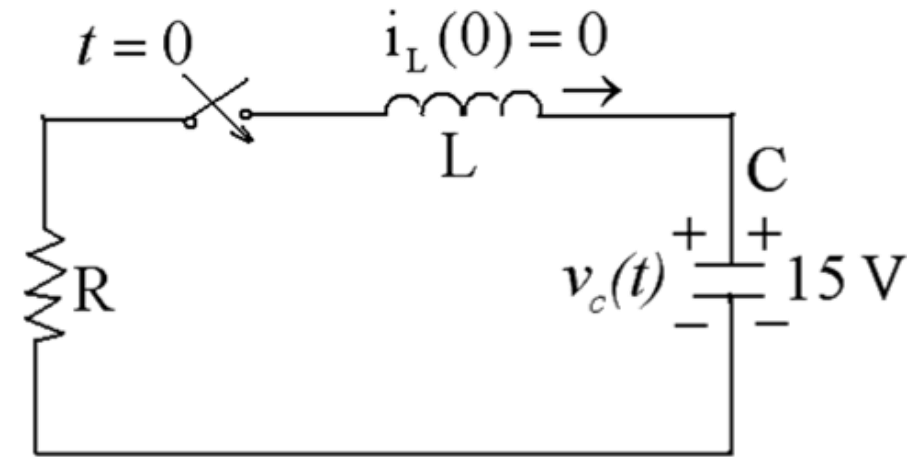


QUIZ 5

The circuit below has the following parameters:

$$R = 4 \text{ k}\Omega, C = 0.25 \text{ }\mu\text{F}, L = 1 \text{ H}$$

The switch has been open for a long time and is closed at $t = 0$. The initial conditions are $i_L(0) = 0$ and $v_C(0) = 15\text{V}$.

Find the capacitor's voltage for $t \geq 0$.

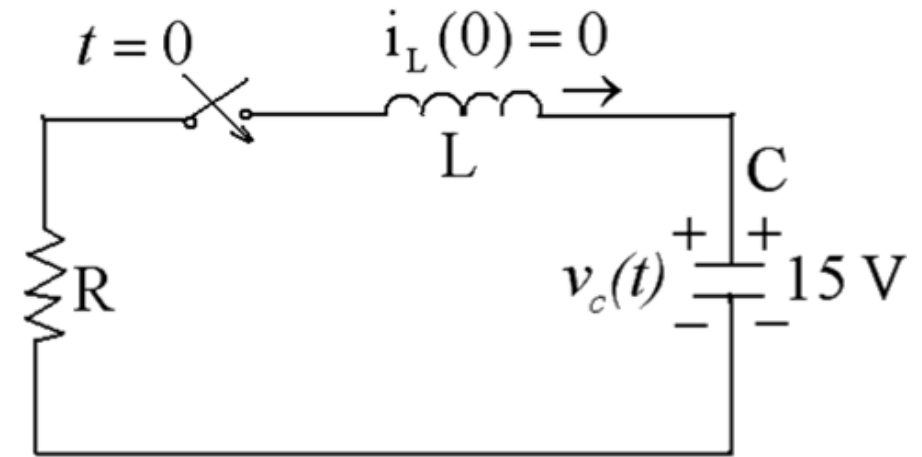


QUIZ 6



The circuit below has the following parameters:

$$R = 1 \text{ k}\Omega, C = 0.25 \text{ }\mu\text{F}, L = 1 \text{ H}$$

The switch has been open for a long time and is closed at $t = 0$. The initial conditions are $i_L(0) = 0$ and $v_C(0) = 15\text{V}$.

Find the capacitor's voltage for $t \geq 0$.

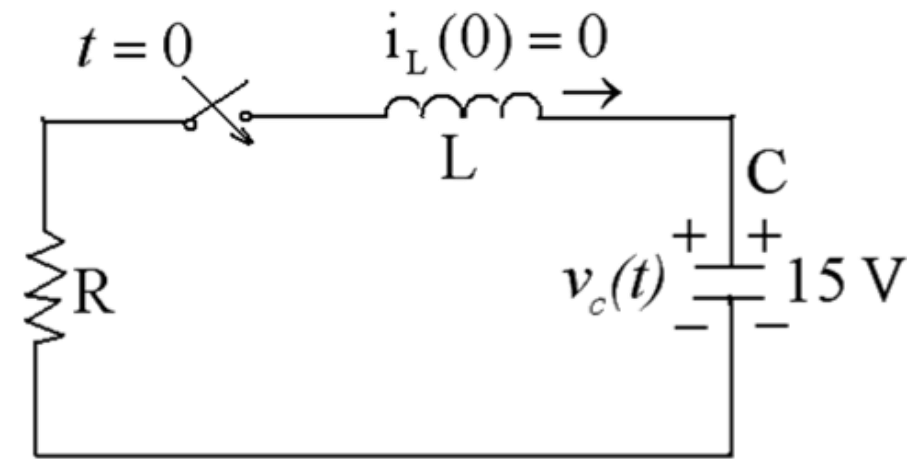

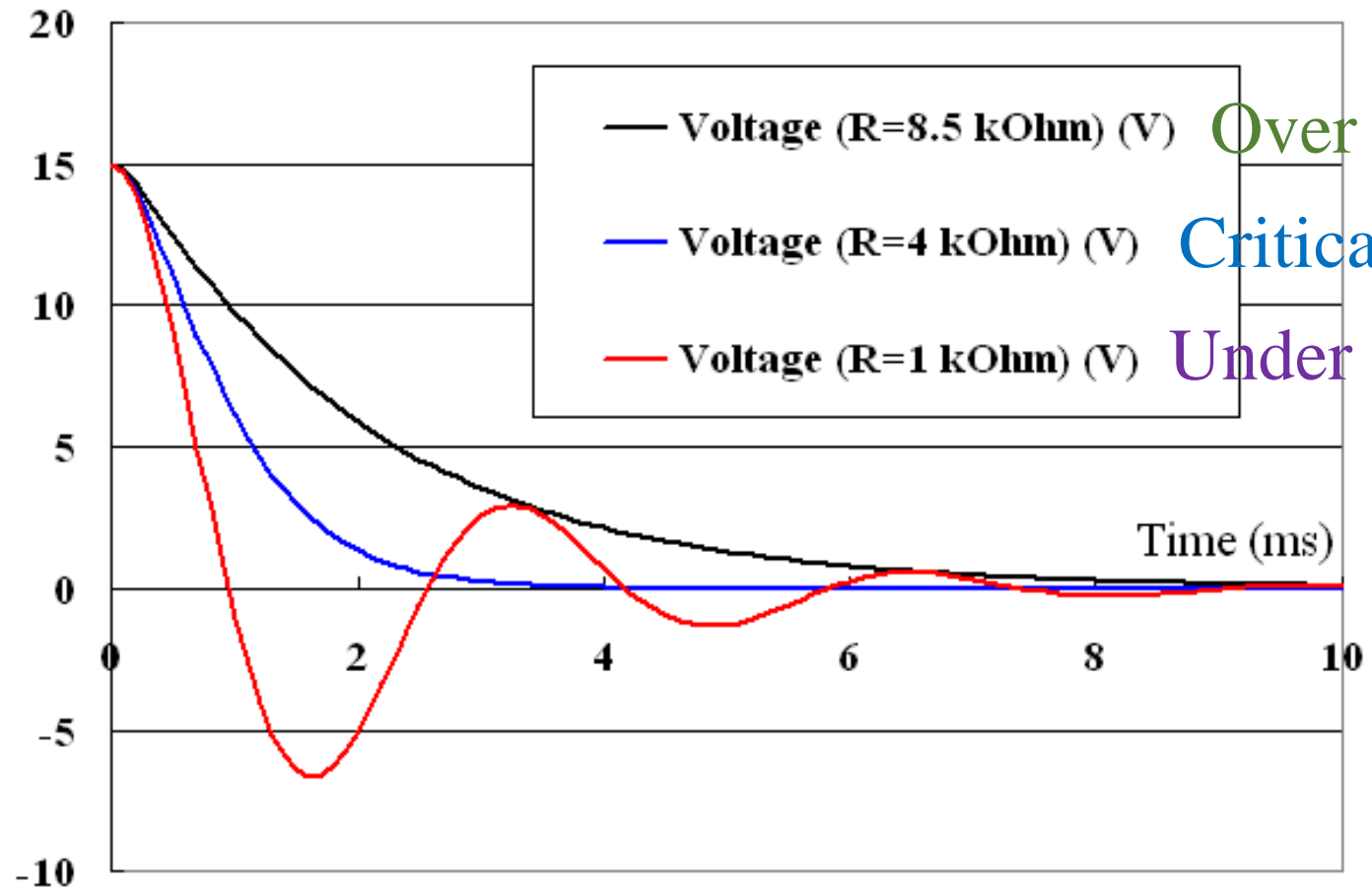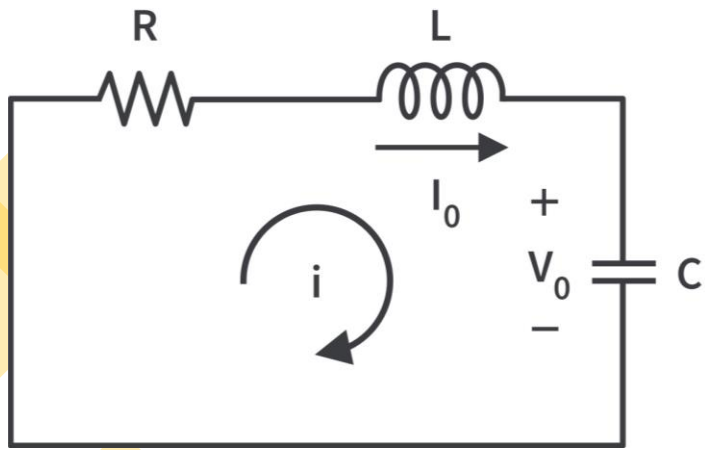


QUIZ 7

The circuit below has the following parameters:

$$C = 0.25 \mu\text{F}, L = 1 \text{ H}$$

The switch has been open for a long time and is closed at $t = 0$. The initial conditions are $i_L(0) = 0$ and $v_C(0) = 15\text{V}$.


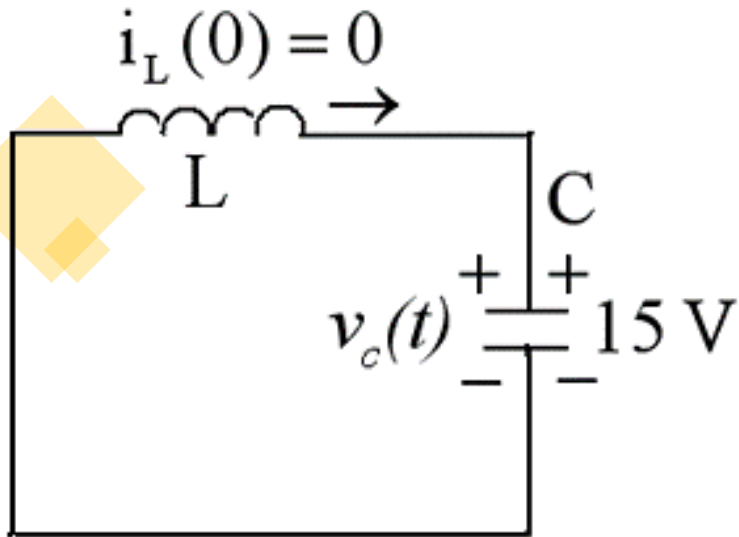
Find the capacitor voltage for $t \geq 0$.



SUMMARY

- ✓ The **damping effect** is due to the presence of resistance R .
- ✓ The damping factor α determines the **rate** at which the response is damped.
- ✓ If $R = 0$, then $\alpha = 0$ and we have an LC circuit with $\frac{1}{\sqrt{LC}}$ as the undamped natural frequency. The response in such a case is undamped and purely oscillatory. This circuit is said to be lossless because the dissipating or damping element (R) is absent.
- ✓ The **over-damped** has the **longest** settling time because it takes the longest time to dissipate the initial stored energy.
- ✓ If we desire the **fastest** response **without oscillation** or ringing, the **critical-damped** circuit is the right choice.

SUMMARY

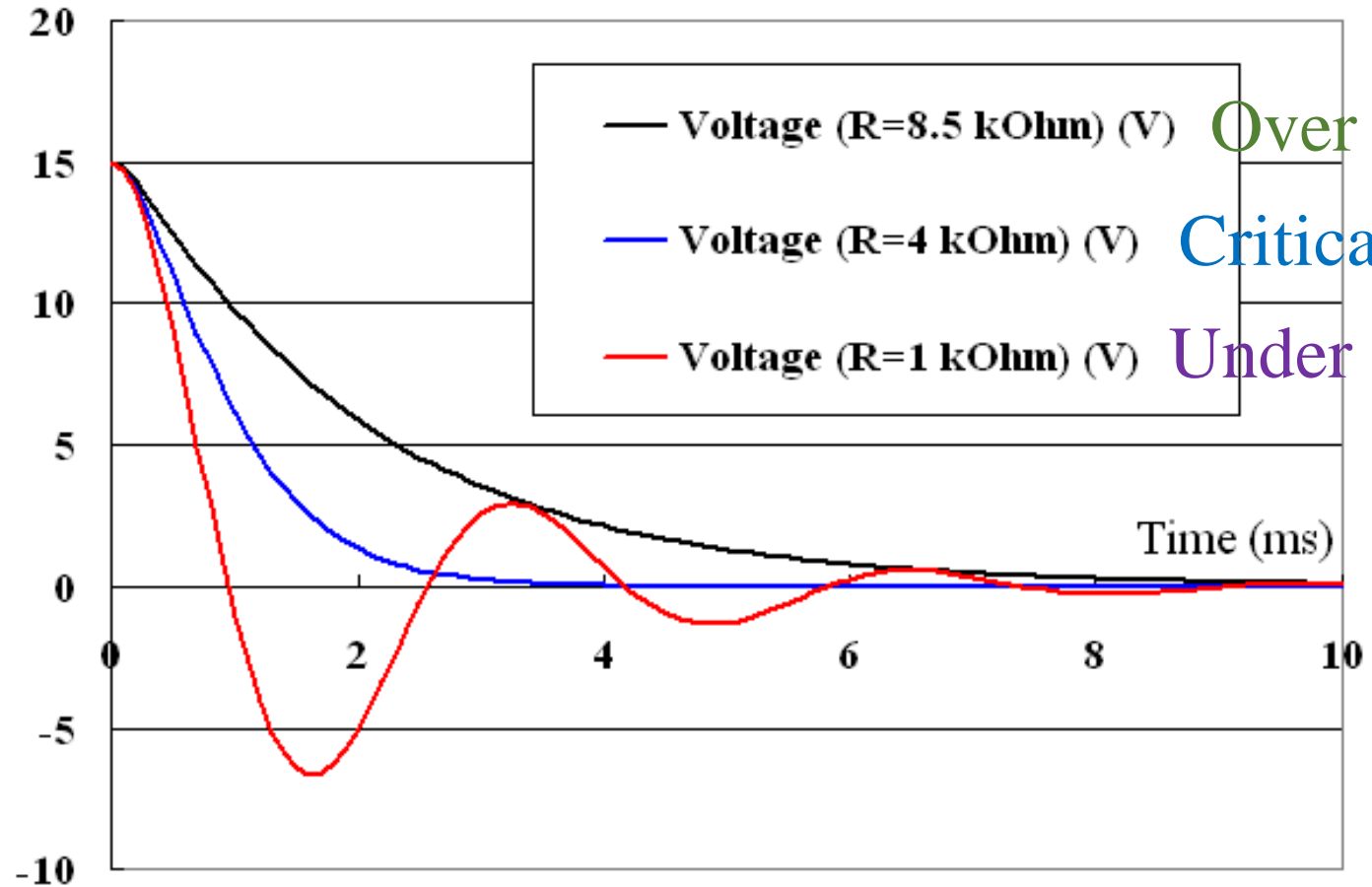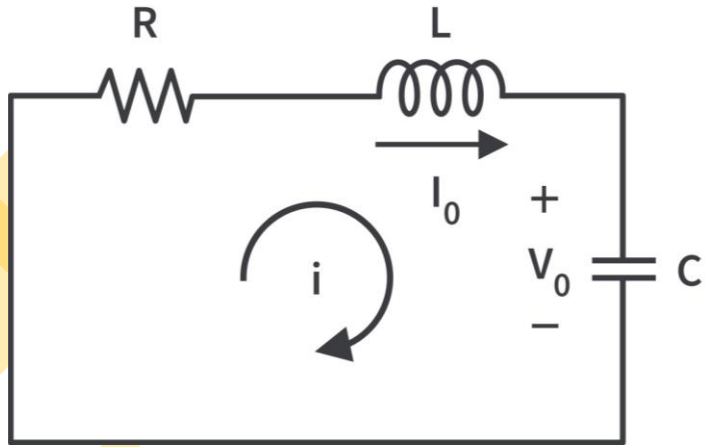

Over Damped


Critical Damped

Under Damped

QUIZ 8


1. Refer to the given series RLC circuit, what kind of natural response will it produce?

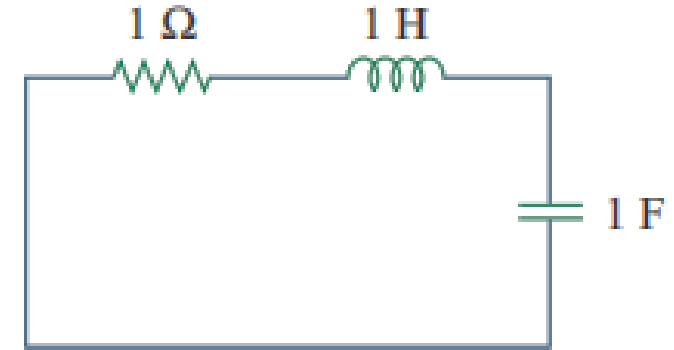- (a) under damped
- (b) over damped
- (c) critical damped
- (d) un-damped




2. Match the circuits with the following items:

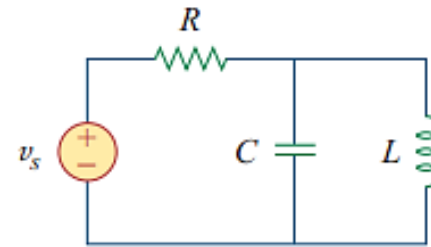
- (1) 1st-order circuit
- (2) 2nd-order series circuit
- (3) 2nd-order parallel circuit
- (4) None of the above




A

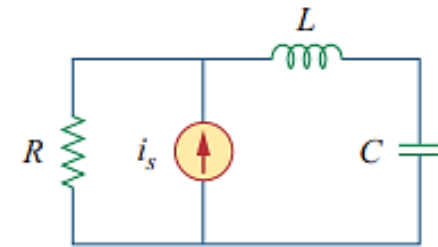


B

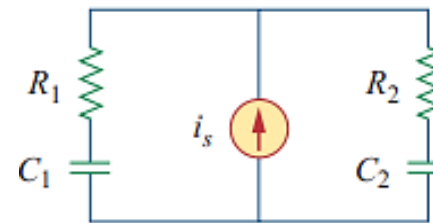

C

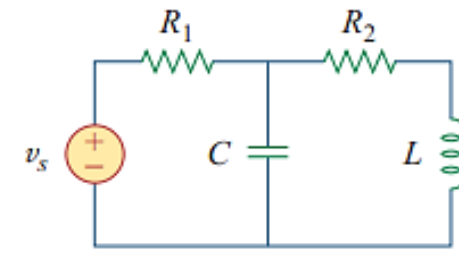

D

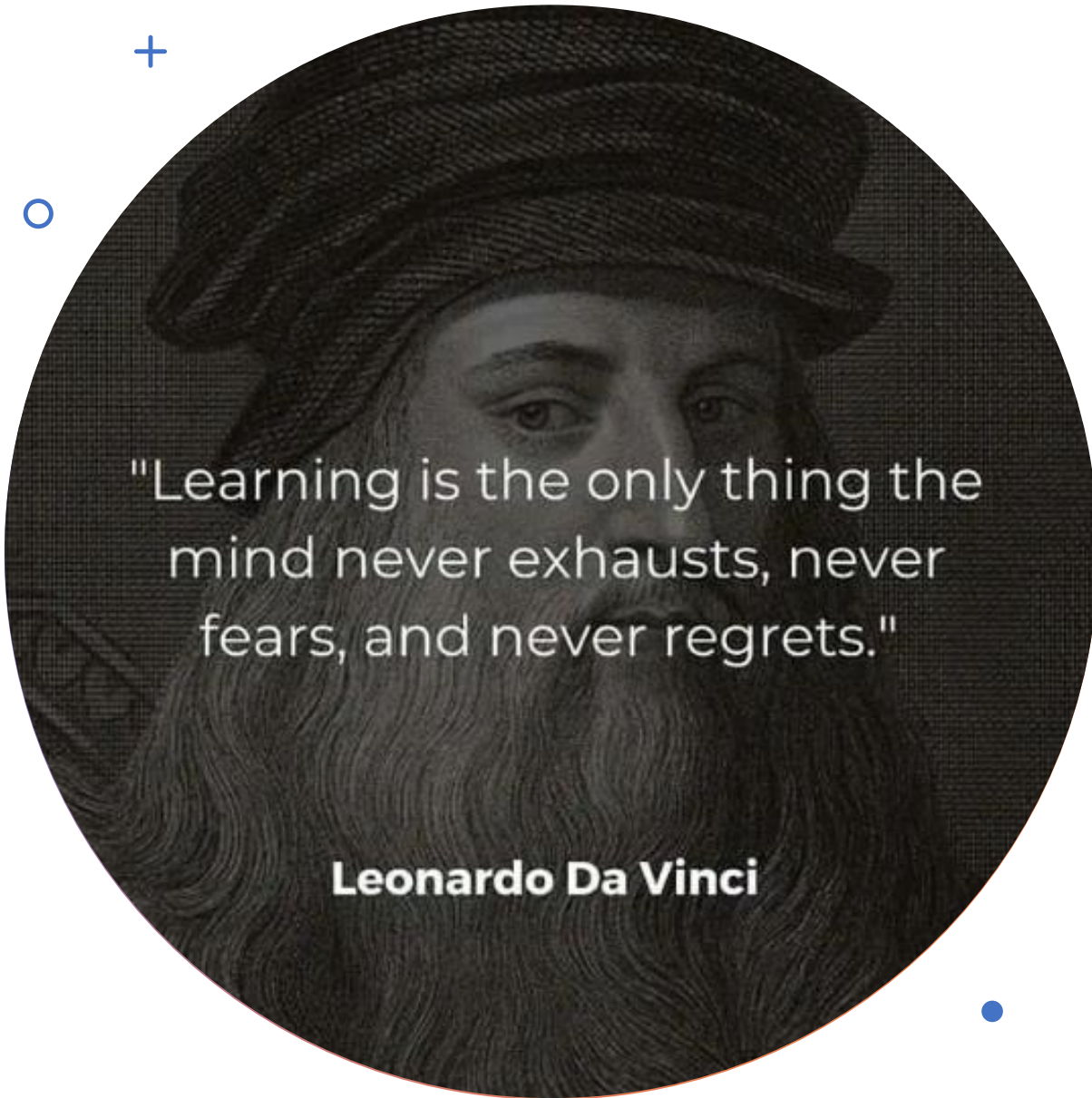

"Learning is the only thing the
mind never exhausts, never
fears, and never regrets."

Leonardo Da Vinci

NEXT...

Transient Response of 2nd-Order Circuits (Step Response)