

EEE205 – Digital Electronics (II)

Lecture 12

Xiaoyang Chen, Jiangmin Gu, Ming Xu


Dept of Electrical & Electronic Engineering

XJTLU

In This Session


- Moore and Mealy Sequential Circuits
- State Tables and Graphs
- Derivation of State Tables

General Form of A Sequential Circuit.

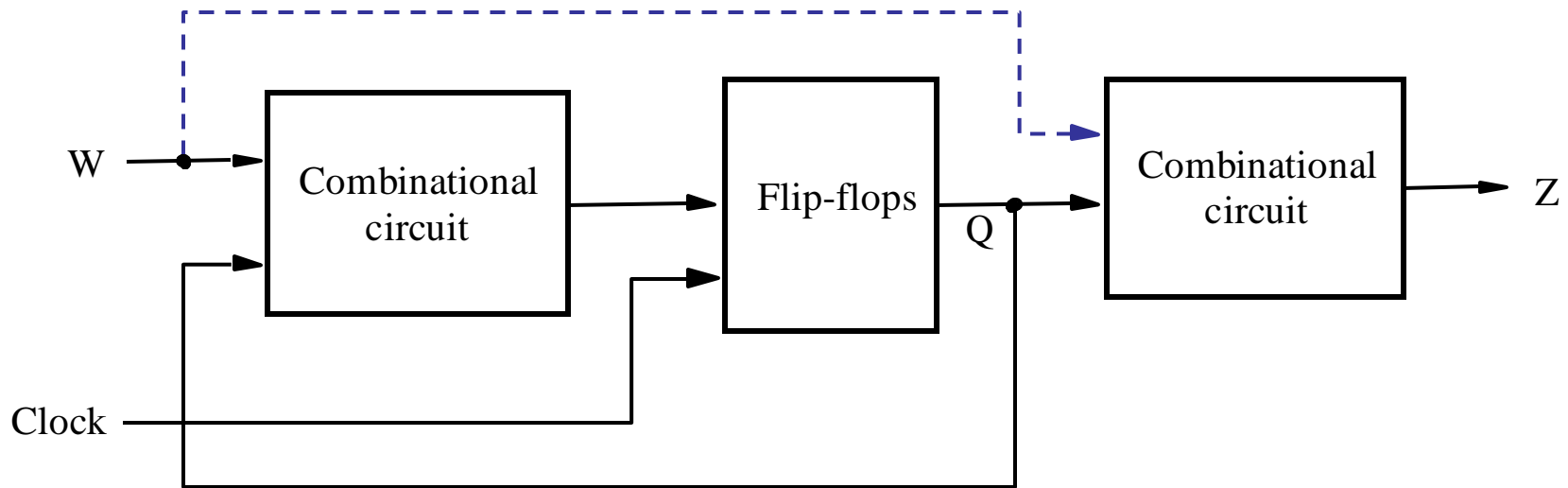

- Sequential circuits are called **finite state machines (FSM)**.
- Combinational circuit 1 has inputs from the input W and the state Q of the flip-flops.
- The output Z always depends on the state Q of the flip-flops and possibly on the input W .

General Form of A Sequential Circuit.

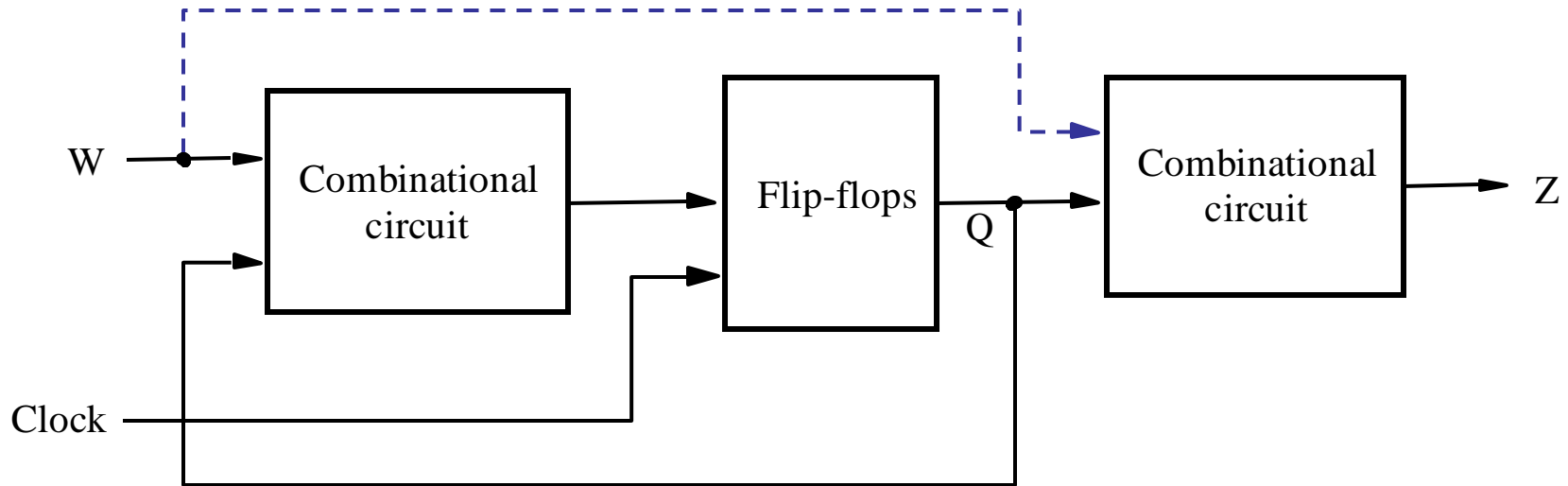

- The sequential circuits whose outputs depend only on the state of the circuit are of **Moore type**.
- Those whose outputs depend on both the state and the inputs are of **Mealy type**.


State Tables and Graphs

- A **state table**, also called a *state transition table*, specifies the next state and output of a sequential circuit in terms of its present state and input

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

State Tables and Graphs

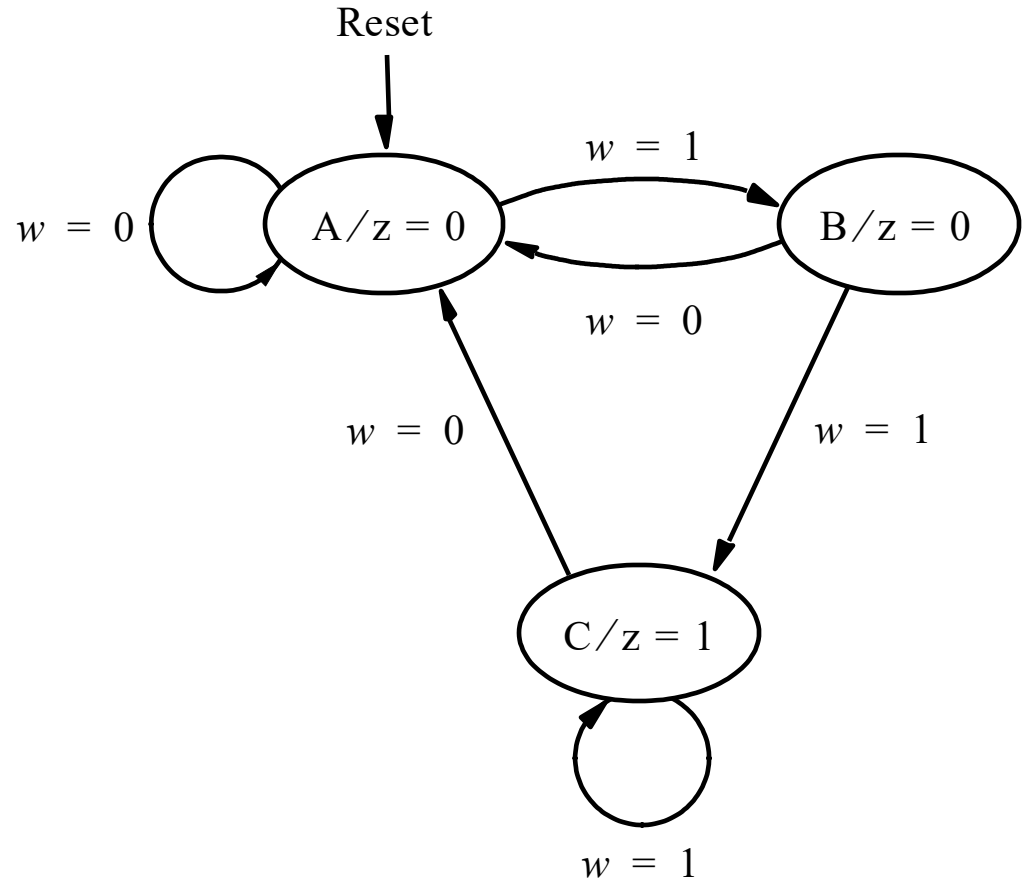
- A **state graph** is a graphical representation of the state table, in which each *node* represents a state and the *arc* joining the nodes is labelled with the input causing the state change.



State Tables and Graphs

The method to construct the state table and graph from a given circuit:

A Moore
sequential circuit

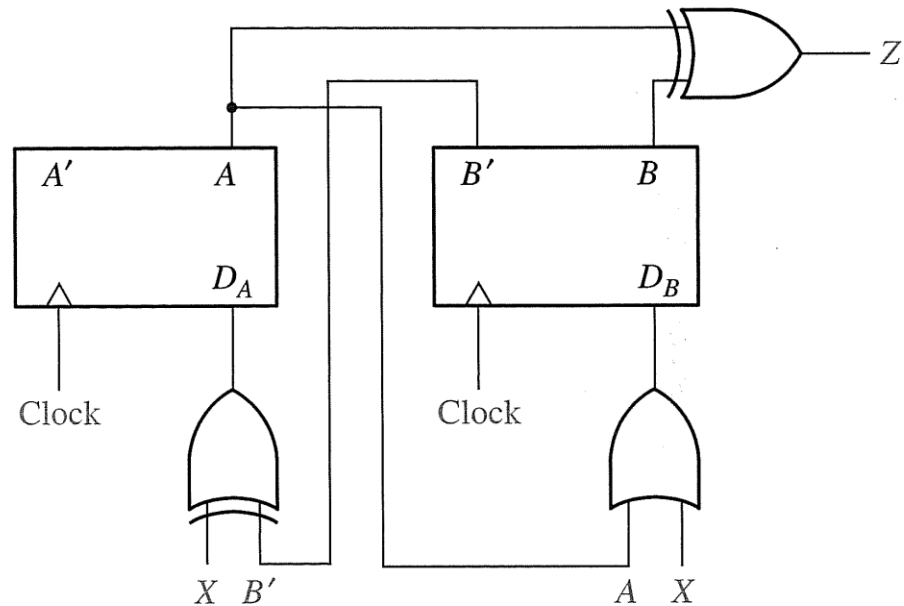

1. Determine the flip-flop input equations and the output equations from the circuit.

$$D_A = X \oplus B' \quad D_B = X + A \quad Z = A \oplus B$$

State Tables and Graphs

D flip flop

D	Q ⁺
0	0
1	1

$$Q^+ = D$$

D-CE flip flop

CE	D	Q ⁺
0	X	Q
1	0	0
1	1	1

$$Q^+ = D \cdot CE + Q \cdot CE'$$

T flip flop

T	Q ⁺
0	Q
1	Q'

$$Q^+ = T \oplus Q$$

State Tables and Graphs

S-R flip flop

S	R	Q ⁺
0	0	Q
1	0	1
0	1	0

$$Q^+ = S + R'Q$$

J-K flip flop

J	K	Q ⁺
0	0	Q
1	0	1
0	1	0
1	1	Q'

$$Q^+ = JQ' + K'Q$$

State Tables and Graphs

2. Derive the next-state equation for each flip-flop from its input equations, using one of the these:

D flip-flop $Q^+ = D$

D-CE flip-flop $Q^+ = D \cdot CE + Q \cdot CE'$

T flip-flop $Q^+ = T \oplus Q$

S-R flip-flop $Q^+ = S + R'Q$

J-K flip-flop $Q^+ = JQ' + K'Q$

The next-state equations for the flip-flops are:

$$A^+ = X \oplus B' \quad B^+ = X + A$$

State Tables and Graphs

3. Form the state table.

$$A^+ = X \oplus B' \quad B^+ = X + A \quad Z = A \oplus B$$


AB	A^+B^+		Z
	$X = 0$	$X = 1$	
00	10	01	0
01	00	11	1
11	01	11	0
10	11	01	1

State Tables and Graphs

4. Replace each combination of states with a single symbol. Draw the state graph.

Replacing 00 with S_0 , 01 with S_1 , 11 with S_2 , and 10 with S_3 .



Present State	Next State		Present Output (Z)
	$X = 0$	$X = 1$	
S_0	S_3	S_1	0
S_1	S_0	S_2	1
S_2	S_1	S_2	0
S_3	S_2	S_1	1

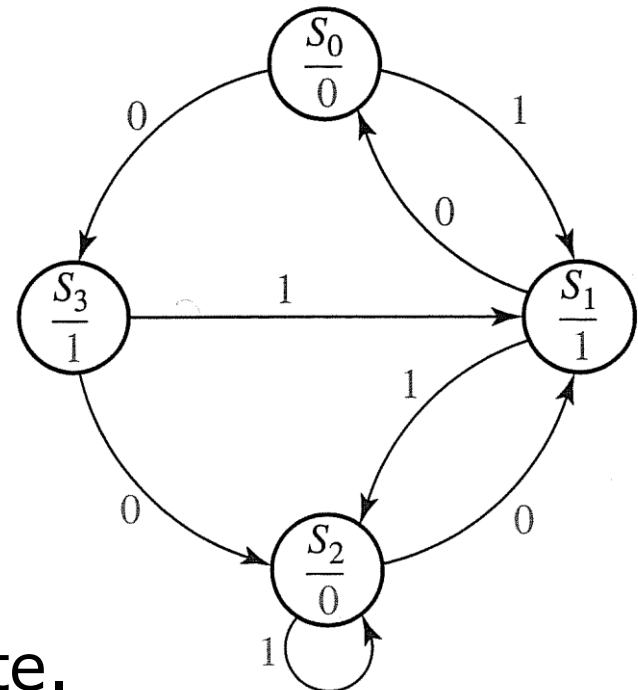

In a Moore state graph, the output is written with the state.

State Tables and Graphs

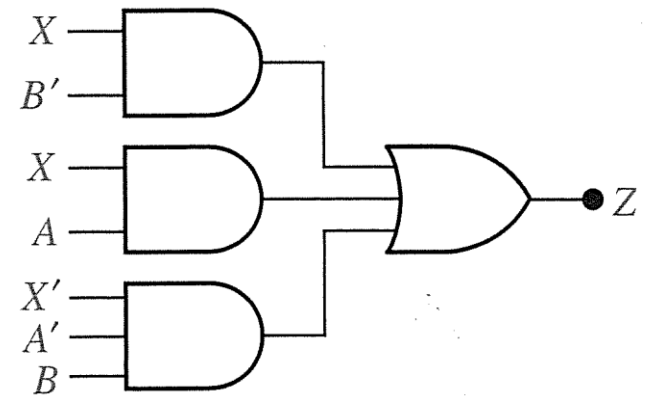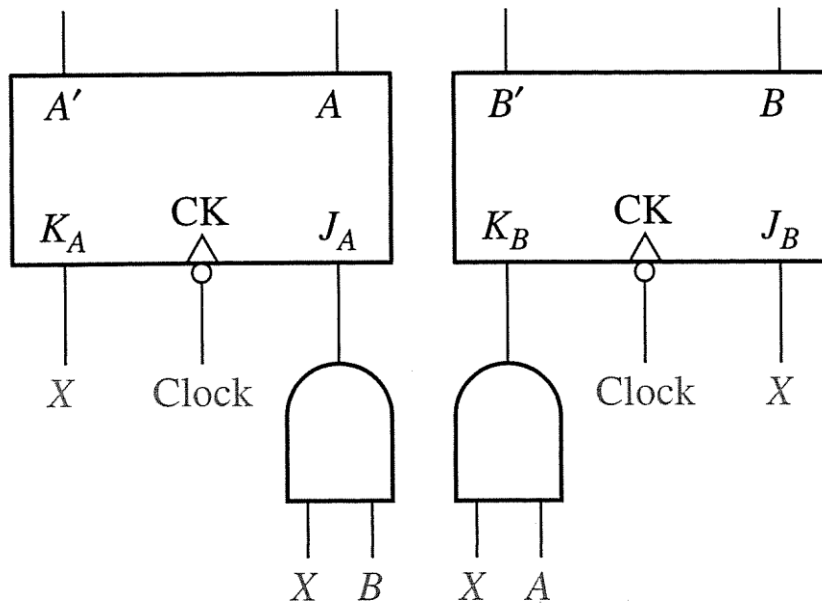Another example for a Mealy sequential circuit:



$$J_A = XB \quad K_A = X$$

$$Z = XB' + XA + X'A'B$$

$$J_B = X$$

$$K_B = XA$$

State Tables and Graphs

The next-state and output equations are:

$$A^+ = J_A A' + K'_A A = XBA' + X'A$$

$$B^+ = J_B B' + K'_B B = XB' + (AX)'B = XB' + X'B + A'B$$

$$Z = X'A'B + XB' + XA$$

Recall that $Q^+ = JQ' + K'Q$ for J-K flip flops

$$J_A = XB \quad K_A = X \quad J_B = X \quad K_B = XA$$

State Tables and Graphs

$$A^+ = J_A A' + K'_A A = XBA' + X'A$$

$$B^+ = J_B B' + K'_B B = XB' + (AX)'B = XB' + X'B + A'B$$

$$Z = X'A'B + XB' + XA$$


AB	A^+B^+		Z	
	X = 0	1	X = 0	1
00	00	01	0	1
01	01	11	1	0
11	11	00	0	1
10	10	01	0	1

Present State	Next State		Present Output	
	X = 0	1	X = 0	1
S_0	S_0	S_1	0	1
S_1	S_1	S_2	1	0
S_2	S_2	S_0	0	1
S_3	S_3	S_1	0	1

State Tables and Graphs

AB	A^+B^+		Z	
	X = 0	1	X = 0	1
00	00	01	0	1
01	01	11	1	0
11	11	00	0	1
10	10	01	0	1

Present State	Next State		Present Output	
	X = 0	1	X = 0	1
S_0	S_0	S_1	0	1
S_1	S_1	S_2	1	0
S_2	S_2	S_0	0	1
S_3	S_3	S_1	0	1

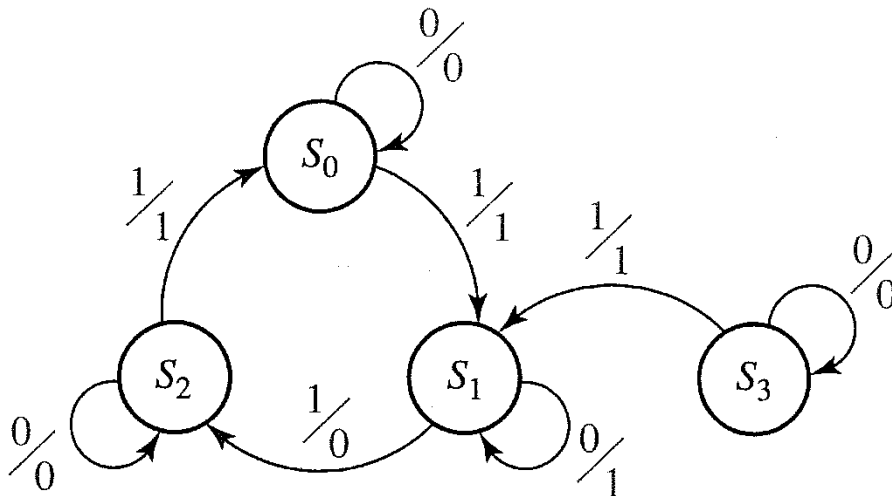

- The labels on the arcs are X/Z, where X is the input and Z is the output.
- In a Mealy state graph, the output is written with the transition.