

EEE103 ELECTRICAL CIRCUITS

WEEK1- BASIC COMPONENTS AND ELECTRIC CIRCUITS

Ye Wu

ye.wu@xjtlu.edu.cn



Xi'an Jiaotong-Liverpool University

西交利物浦大學



Overview of Part 1

LO: Be familiar with the various laws and theorems in electrical circuit analysis.

- Week 1: Basic Components and Electric Circuits
- Week 2: Voltage and Current Laws
- Week 3: Basic Nodal and Mesh Analysis
- Week 4: Handy Circuit Analysis Techniques

Homework Assignment 1: **Due Week 5**

In Class Quiz 1: **Week4 tutorial time. (Take in class).**



CONTENT

- Units and Scale
- Charge, Current, Voltage, Power and Energy
- Voltage and Current Source
- Ohm's Law



The SI System

The value of measurable quantity must have both a **number** and a **unit**.

- Base units:

Base Quantity	Name	Symbol
length	meter	m
mass	kilogram	kg
time	second	s
electric current	ampere	A
thermodynamic temperature	kelvin	K
amount of substance	mole	mol
luminous intensity	candela	cd

- Derived units:

Units for other quantities can be derived from these seven base units.

- ✓ work or energy: joule (J) ($\text{kg m}^2 \text{s}^{-2}$ in SI base units)
- ✓ power (rate of doing work): watt (W)
- ✓ $1 \text{ W} = 1 \text{ J/s}$



SI: Units and Prefixes

Any measurement can be expressed in terms of a unit, or a unit with a “prefix” modifier.

Factor	Name	Symbol	Factor	Name	Symbol
10^{-24}	yocto	y	10^{24}	yotta	Y
10^{-21}	zepto	z	10^{21}	zetta	Z
10^{-18}	atto	a	10^{18}	exa	E
10^{-15}	femto	f	10^{15}	peta	P
10^{-12}	pico	p	10^{12}	tera	T
10^{-9}	nano	n	10^9	giga	G
10^{-6}	micro	μ	10^6	mega	M
10^{-3}	milli	m	10^3	kilo	k
10^{-2}	centi	c	10^2	hecto	h
10^{-1}	deci	d	10^1	deka	da

“Engineering Units”

- ✓ Number between 1-999
- ✓ Metric unit using a power divided by 3

Example: $0.048 \text{ W} = 48 \text{ mW} = 4.8 \text{ cW} = 4.8 \times 10^{-2} \text{ W}$
 $= 48000 \mu\text{W}$



Current and Charge


- Charge

Symbol: Q or q ; units are coulomb (C).

The smallest charge, the *electronic charge*, is carried by

an electron (-1.602×10^{-19} C)

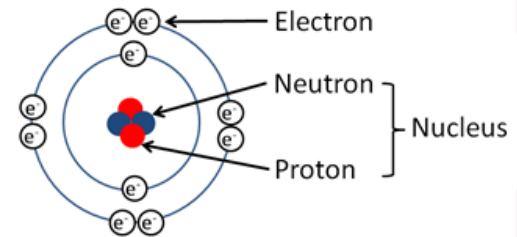or a proton ($+1.602 \times 10^{-19}$ C).




Charge is *conserved*: neither created nor destroyed.

- Current

Symbol: I or i ; units are ampere (A)



Current is the rate of charge flow:

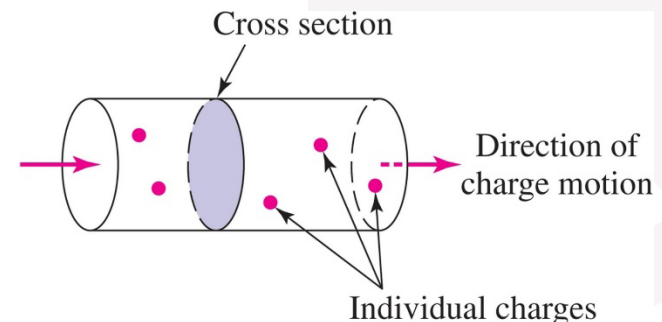1 ampere = 1 coulomb/second (or $1 \text{ A} = 1 \text{ C/s}$)



Current and Charge

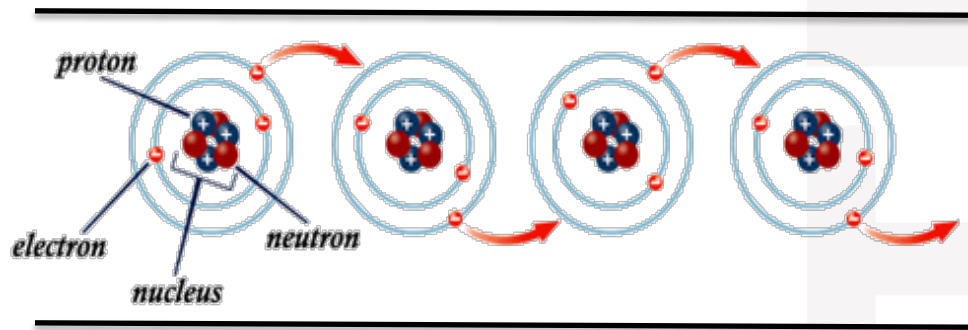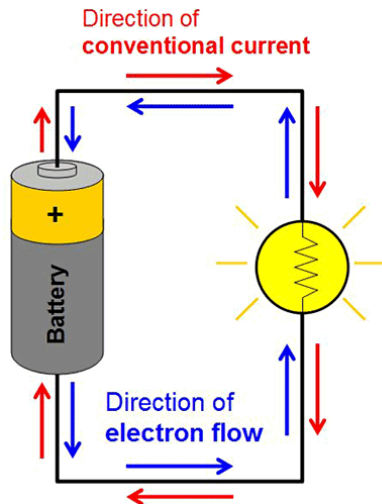- Conventional current and Electron current





Electron flow model: Electrons flow from the negative terminal to the positive terminal of the source

Conventional current: Positive charges were thought to carry current



Current and Charge

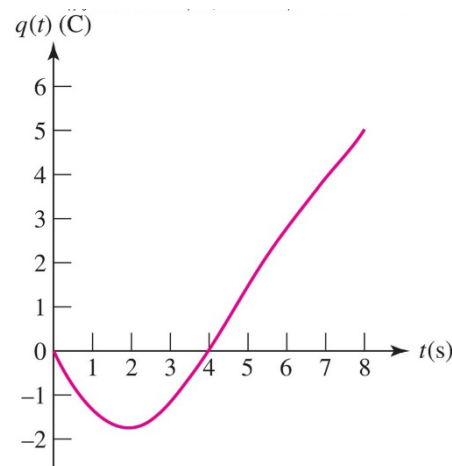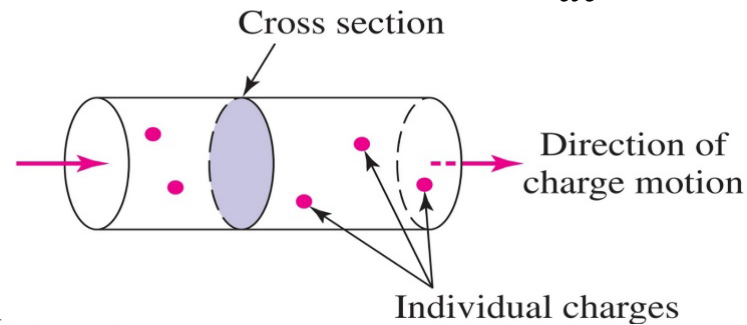Current is the rate of charge flow: $i = \frac{dq}{dt}$




(a)

A graph of the instantaneous value of the total charge $q(t)$ that has passed a given reference point since $t = 0$.

$$i = \frac{dq}{dt}$$



$$q(t) = \int_{t_0}^t i dt' + q(t_0)$$

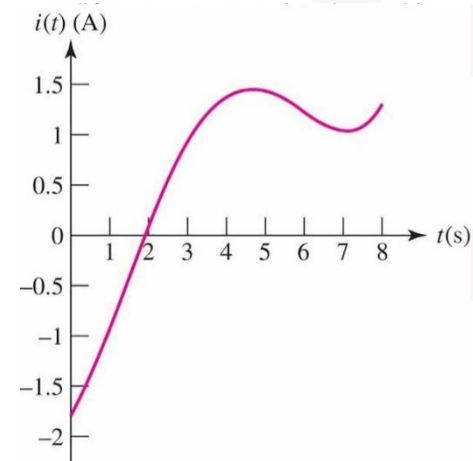


(b)

The instantaneous current $i = dq/dt$, where q is given in (a)



Current and Charge

Several types of current:

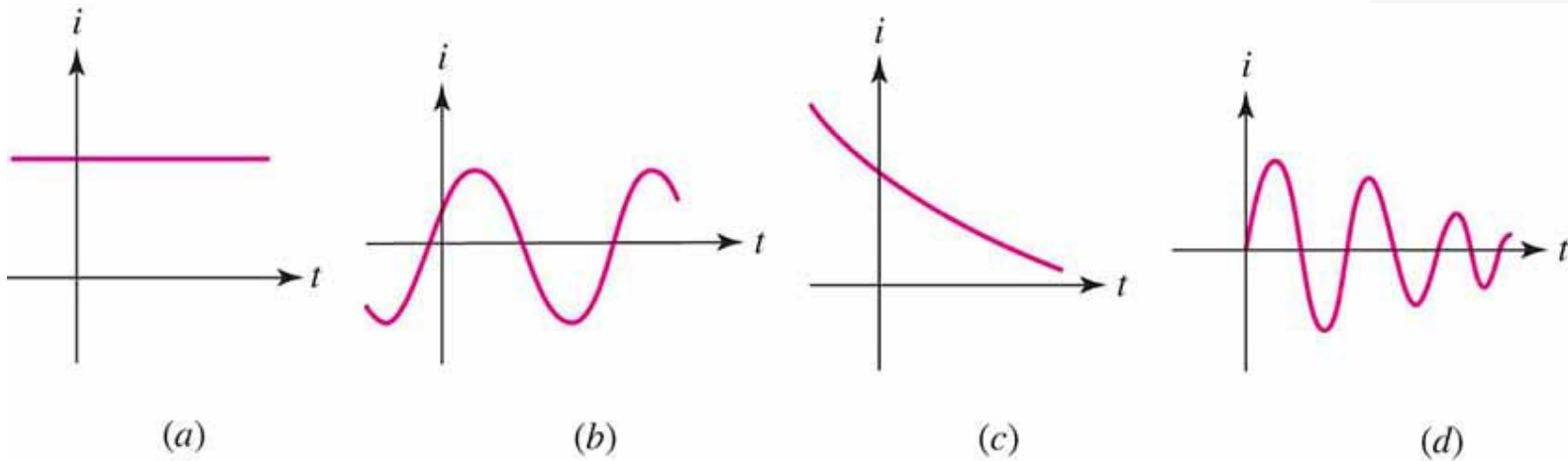


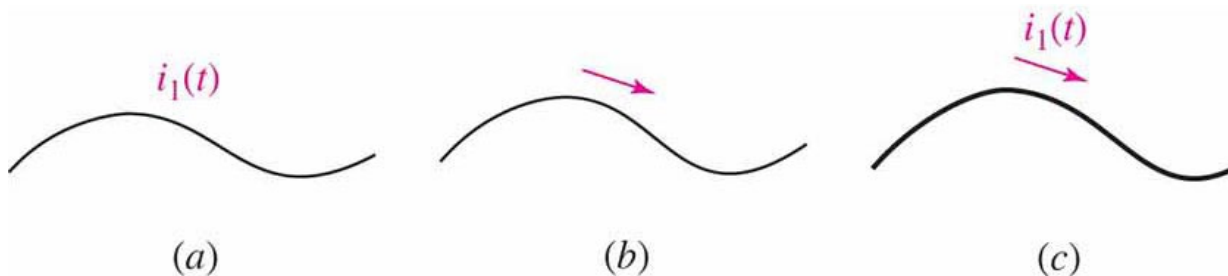(a) Direct current (dc). (b) Sinusoidal current (ac). (c) Exponential current. (d) Damped sinusoidal current.



Current and Charge

Current must be designated with **both a direction and a magnitude**



(a, b) Incomplete, improper, and incorrect definitions of a current. (c) The correct definition of $i_1(t)$.



Two methods of representation for the exact same current.



Example: Current and Charge

Electrons are moving *left to right* to create a current of 1 mA. Determine I_1 and I_2 .



- The direction of electron movement is opposite to the current direction
- Current direction is from right to left.
- $I_1 = -1 \text{ mA}$, $I_2 = +1 \text{ mA}$



Voltage

- Circuit Elements

A circuit element usually has two terminals (sometimes three or more).




The relationship between the voltage v across the terminals and the current i through the device defines the circuit element model.

- Voltage

Symbol: V or v ; units are volt (V)

When 1 J of work is required to move 1 C of charge from A to B, there is a voltage of 1 volt between A and B.

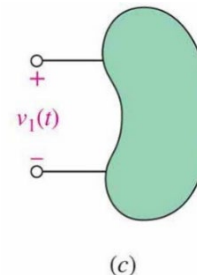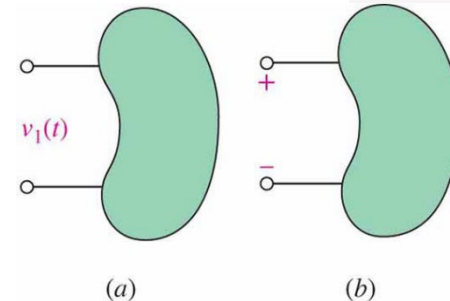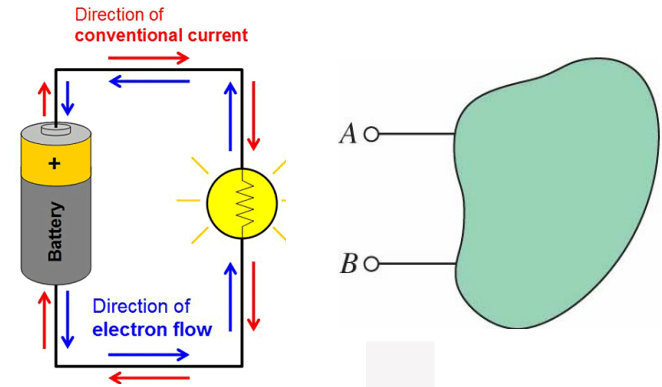
Voltage (V or v) across an element requires both a **magnitude** and a **polarity**.




(a, b) inadequate definitions of a voltage. (c) A correct definition




Example: Voltage

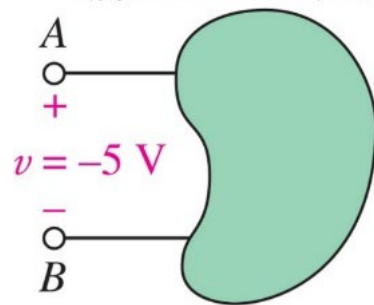


(a)

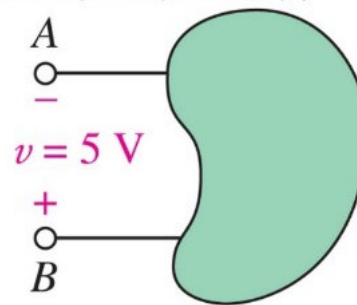

(b)

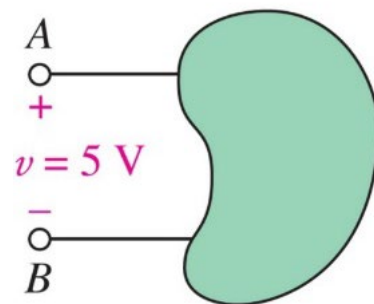

(c)

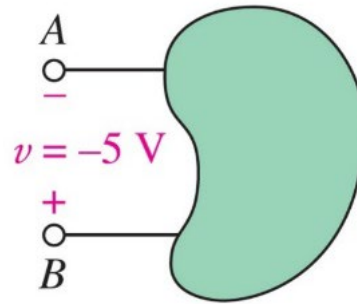

(d)

(a)=(b), (c)=(d)



Power: $p = vi$


Symbol: P or p ; units are watt (W)

The power required to push a current i (C/s) into a voltage v (J/C) :


$$p = vi \text{ (J/s = W)}$$

Passive sign convention: the current arrow is directed into the element at the plus marked terminal.

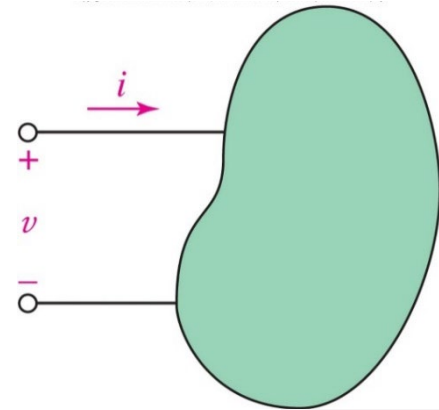When power is **positive**, the element is **absorbing** energy. When power is **negative**, the element is **supplying** energy.



Example: Power Absorbed

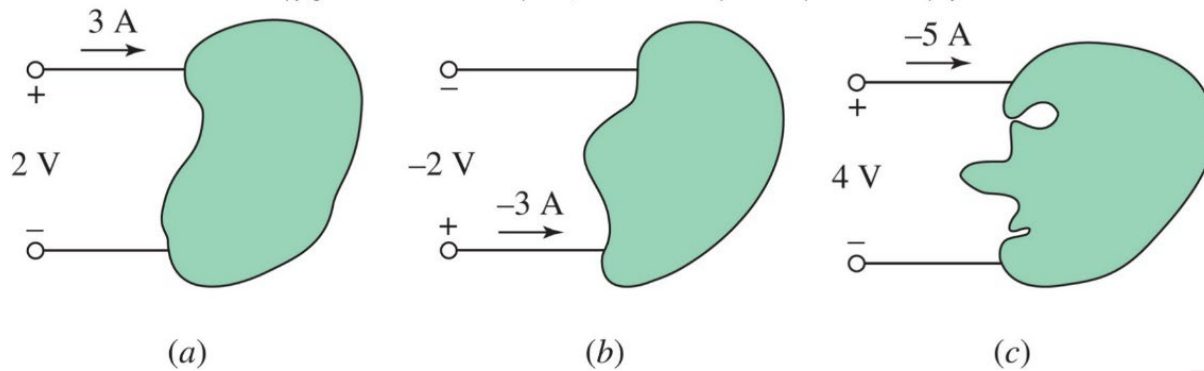

How much power is absorbed by the three elements above?

(a) $P = 2\text{ V} \cdot 3\text{ A} = 6\text{ W}$


(b) $P = -2\text{ V} \cdot (-3)\text{ A} = 6\text{ W}$

(c) $P = 4\text{ V} \cdot (-5)\text{ A} = -20\text{ W}$

*(Note: (c) is actually supplying power)



Example: Power Absorbed

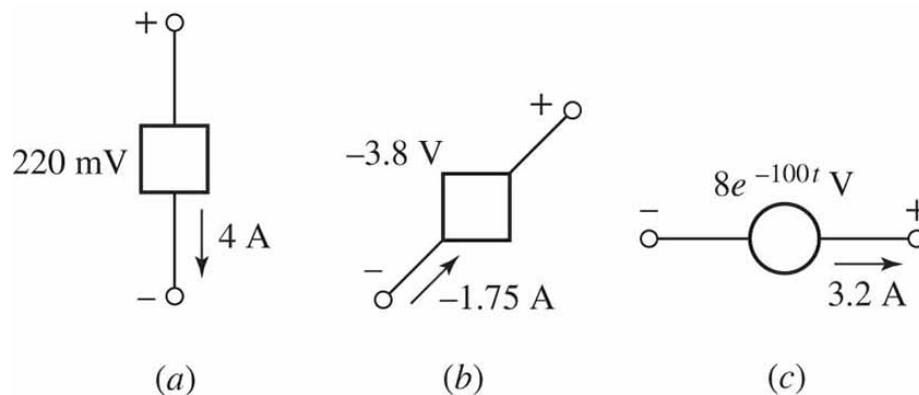

How much power is absorbed by the three elements above?



Energy (w)

Symbol: W or w; units are joule (J)

Energy is integral of power (Power is rate of work/energy)

$$w(t) = \int_{t_0}^t p \, dt = \int_{t_0}^t vi \, dt$$

(1 joule = 1 watt × 1 second)

Energy determines total electricity need or how long your battery will last.

Other convenient energy unit:

- ✓ watt hours(Wh): 1 Wh = 3600 J
- ✓ kilowatt hours(kWh): 1 kWh = 3.6×10^6 J



Energy Example: Battery

Battery Energy in units of joules (J) or watt-hours (Wh)

Battery capacity often given in amp-hours (Ah)

$$w = \int v i \, dt = V \int i \, dt = VQ$$

$$w = (\text{battery voltage}) \times (\text{capacity in Ah})$$


A 1.5 V battery with capacity of 2 Ah:

- Has total energy of 3 Wh = 10.8 kJ
- Can supply a circuit drawing 200 mA for 10 h




Independent Voltage Sources

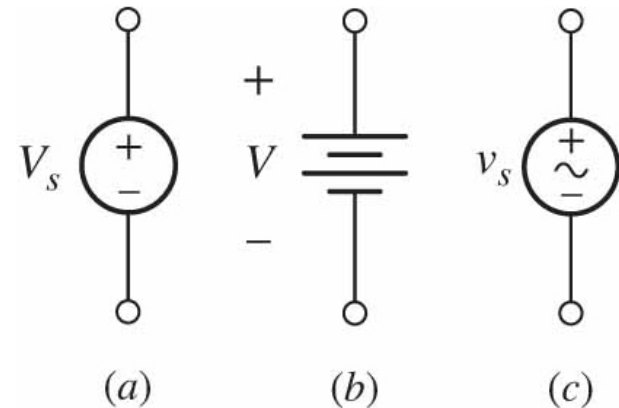- An ideal voltage source is a circuit element that will maintain the specified voltage v_s across its terminals.
- The current will be determined by other circuit elements.
- An ideal voltage source has no current limit.



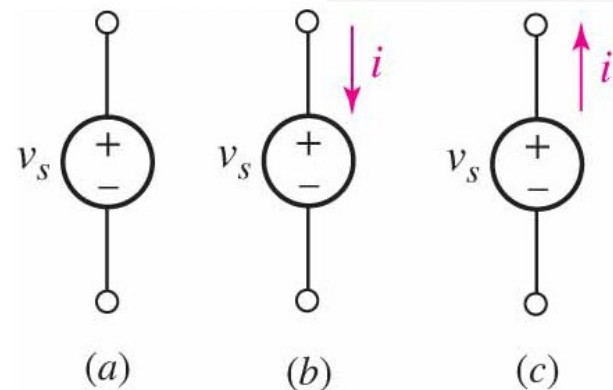
(a) DC voltage source symbol;
(b) battery symbol; (c) ac voltage source symbol



Independent Current Sources

An ideal current source is a circuit element that maintains the specified current flow i_s through its terminals.

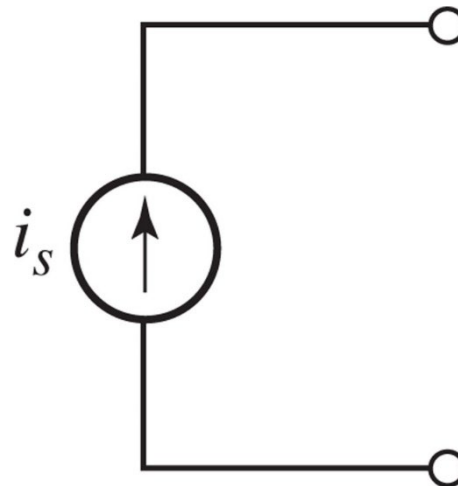
The voltage is determined by other circuit elements ($V \neq 0$).



Dependent Sources

Dependent current sources (a) and (b) maintain a *current* specified by another circuit variable.

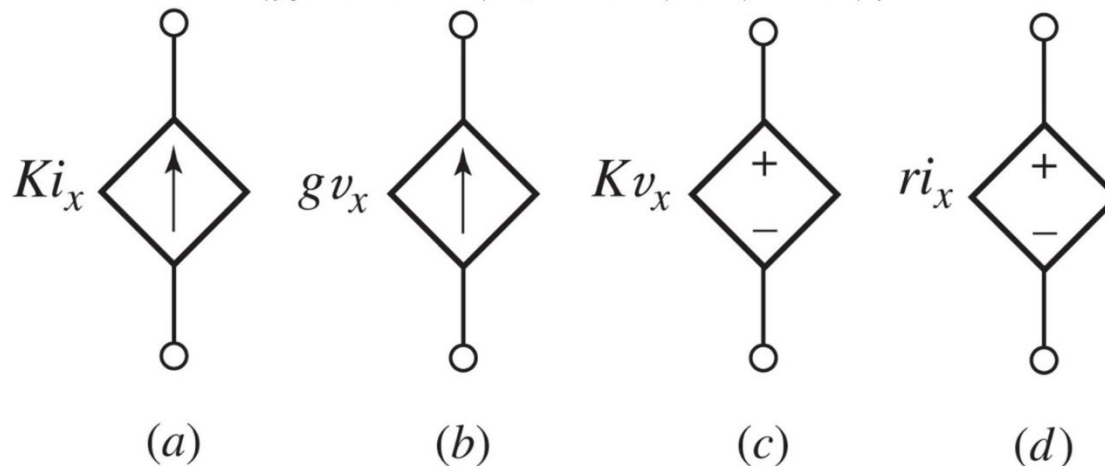Dependent voltage sources (c) and (d) maintain a *voltage* specified by another circuit variable.




K: dimensionless scaling constant
g: scaling factor with units of A/V
r: scaling factor with units of V/A



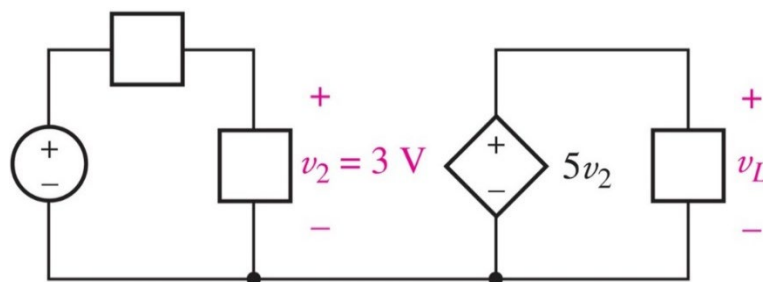Example: Dependent Sources

If v_2 is known to be 3V, find the voltage v_L in the circuit below.




$$v_L = 5v_2 = 5 * 3V = 15V$$



Practice

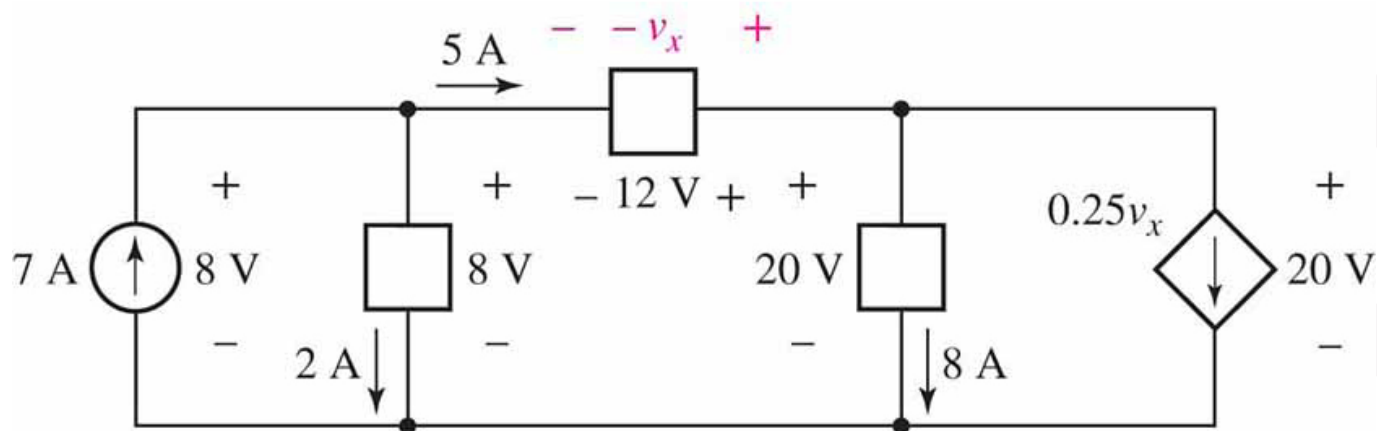Find the power absorbed by each element in the circuit




Networks and Circuits

Network: The interconnection of two or more simple *circuit elements* forms an electrical network.

Circuit: If the network contains at **least one closed path**, it is also an electric circuit.

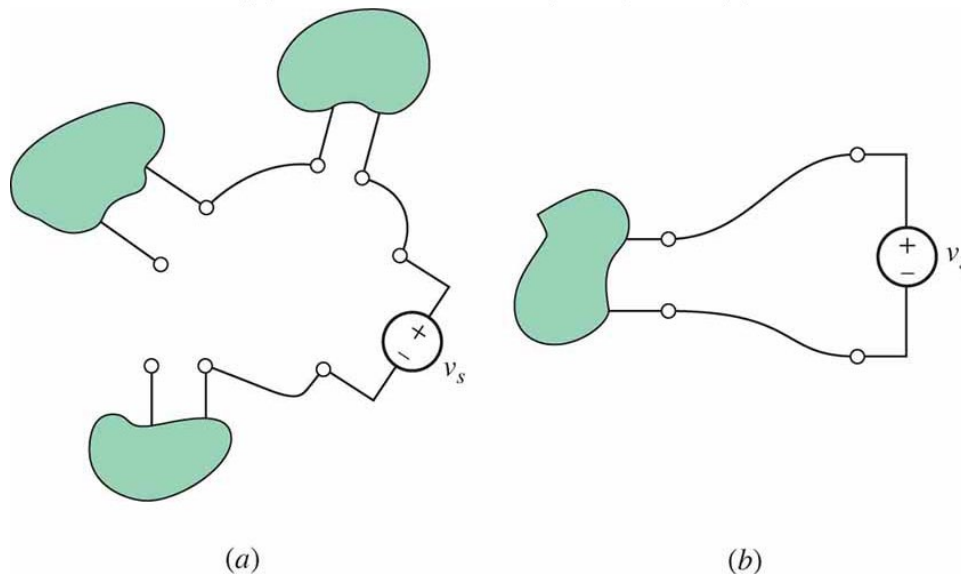(Note: Every circuit is a network, but not all networks are circuits)




(a) A network that is not a circuit.

(b) A network that is a circuit.




Basic Components

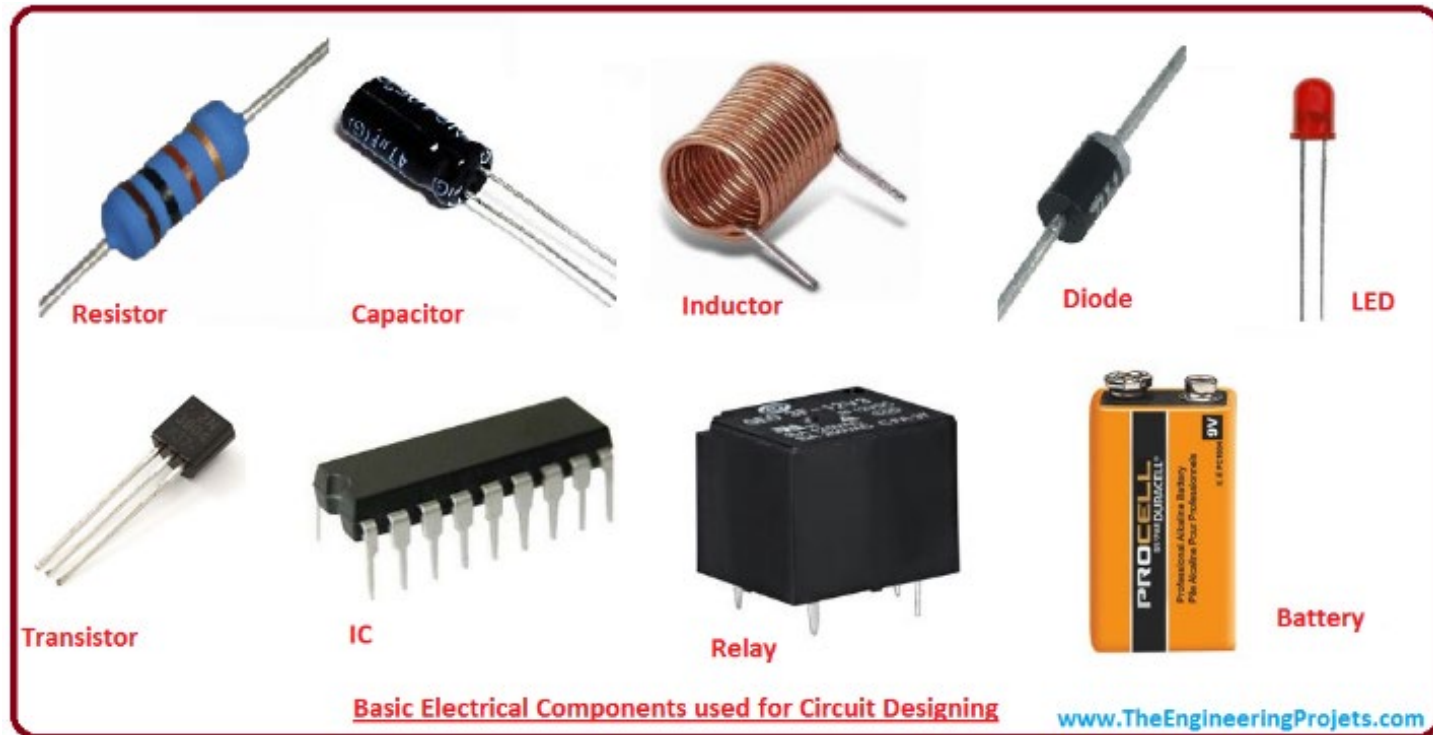

Resistors

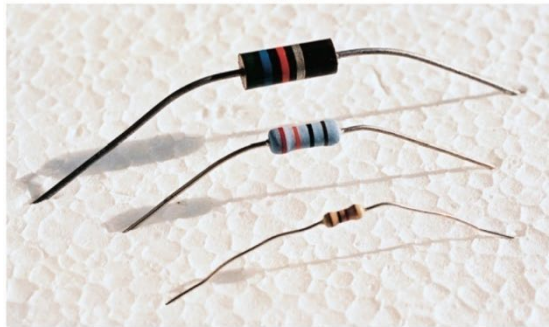
- (a) typical resistors (b) power resistor
(c) a 10 T Ω resistor (d) circuit symbol



(a)



(b)

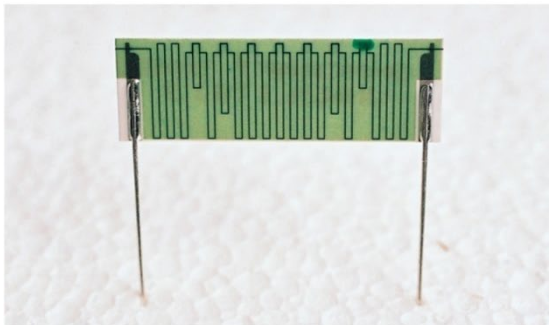

(c)



(d)



Ohm's Law: Resistance

A (linear) resistor is an element for which

$$v = iR$$




where the constant R is a resistance.

The equation is known as “Ohm’s Law.”

The unit of resistance is **ohm (Ω)**.

$$1 \Omega = 1 \text{ V/A}$$

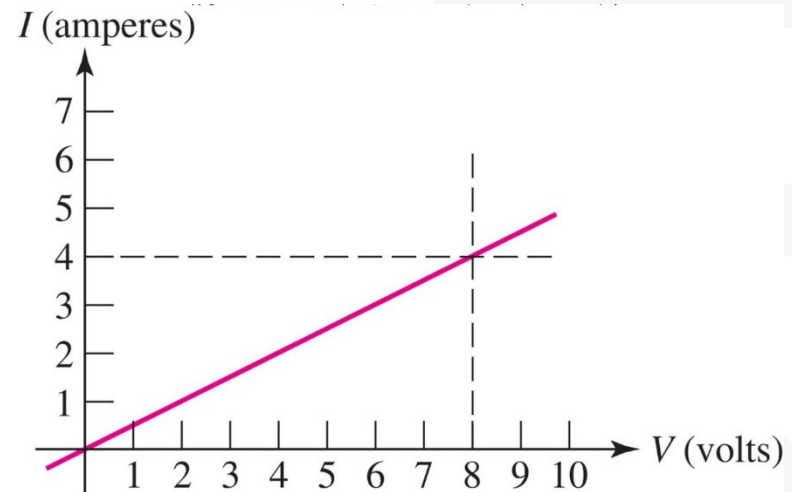

In this example, the slope is $4\text{A}/8\text{V}$ or $0.5 \Omega^{-1}$.

This is the graph for a 2 ohm resistor



Power Absorption

Resistors absorb power: since $v = iR$

(v and i are selected to satisfy the passive sign convention)



$$p = vi = v^2 / R = i^2 R$$

Positive power means the device is absorbing energy.

Power is always positive for a resistor! (or a resistor is always absorbing energy)



Example: Resistor Power

A $560\ \Omega$ resistor is connected to a circuit which causes a current of 42.4 mA to flow through it.

Calculate the voltage across the resistor and the power it is dissipating.

$$v = iR = (0.0424)(560) = 23.7\text{ V}$$


$$p = vi = (23.7\text{V})(42.4\text{mA}) = 1.005\text{W}$$

Alternatively:

$$p = i^2 R = (0.0424)^2 (560) = 1.007\text{ W}$$

Or:
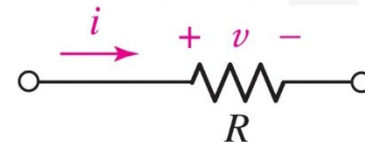
$$p = v^2 / R = (23.7)^2 / 560 = 1.003\text{W}$$



Ohms Law Formulas


Ohms Law Formulas				
Known Values	Resistance (R)	Current (I)	Voltage (V)	Power (P)
Current & Resistance	---	---	$V = I \times R$	$P = I^2 \times R$
Voltage & Current	$R = \frac{V}{I}$	---	---	$P = V \times I$
Power & Current	$R = \frac{P}{I^2}$	---	$V = \frac{P}{I}$	---
Voltage & Resistance	---	$I = \frac{V}{R}$	---	$P = \frac{V^2}{R}$
Power & Resistance	---	$I = \sqrt{\frac{P}{R}}$	$V = \sqrt{P \times R}$	---
Voltage & Power	$R = \frac{V^2}{P}$	$I = \frac{P}{V}$	---	---



Wire Gauge and Resistivity

The resistance of a wire is determined by the resistivity of the conductor as well as the geometry:

$$R = \rho l / A$$

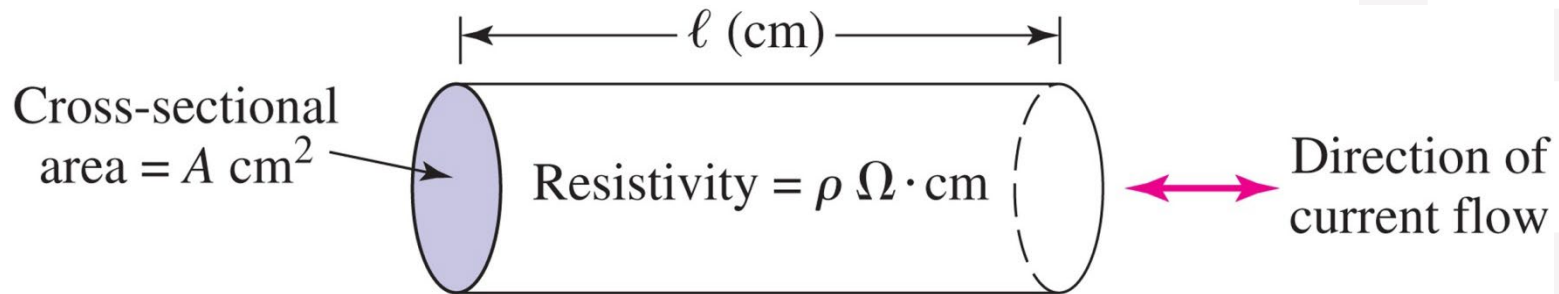

[In most cases, the resistance of wires can be assumed to be 0 ohms.]



Common Electrical Wire Materials and Resistivities

ASTM Specification**	Temper and Shape	Resistivity at 20°C ($\mu\Omega \cdot \text{cm}$)
B33	Copper, tinned soft, round	1.7654
B75	Copper, tube, soft, OF copper	1.7241
B188	Copper, hard bus tube, rectangular or square	1.7521
B189	Copper, lead-coated soft, round	1.7654
B230	Aluminum, hard, round	2.8625
B227	Copper-clad steel, hard, round, grade 40 HS	4.3971
B355	Copper, nickel-coated soft, round Class 10	1.9592
B415	Aluminum-clad steel, hard, round	8.4805

* C. B. Rawlins, "Conductor materials," *Standard Handbook for Electrical Engineering*, 13th ed., D. G. Fink and H. W. Beaty, eds. New York: McGraw-Hill, 1993, pp. 4-4 to 4-8.

** American Society of Testing and Materials.



Conductance

We sometimes prefer to work with *the reciprocal of resistance* ($1/R$), which is called conductance (symbol G , unit siemens (S)).

A resistor R has conductance $G = 1/R$.

Ohm's law (i - v equation) can be written as

$$i = Gv$$



Open and Short Circuits

An open circuit between A and B means $I = 0$.



Voltage across an open circuit: any value.


An open circuit is equivalent to $R = \infty \Omega$.

A short circuit between A and B means $V = 0$.

Current through a short circuit: any value.

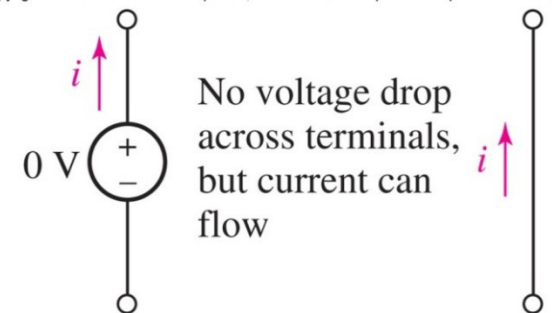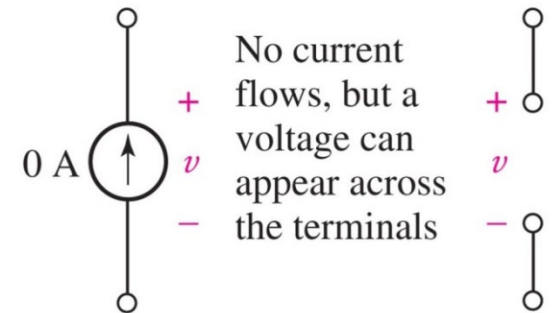A short circuit is equivalent to $R = 0 \Omega$.



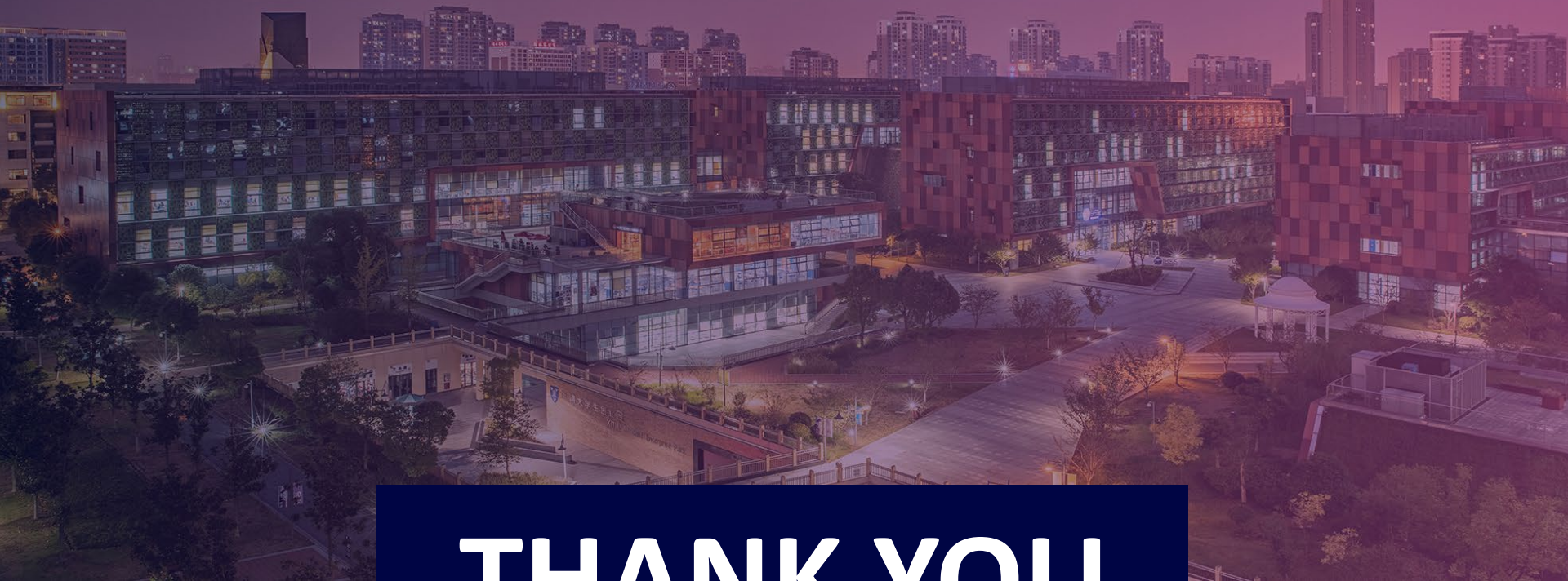

THANK YOU



Xi'an Jiaotong-Liverpool University
西交利物浦大學

